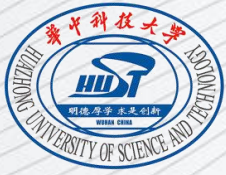


Huazhong University
of Science & Technology

Electronic Circuit of Communications



School of Electronic Information
and Communications

Jiaqing Huang




Quartz Crystal Filter

Frequency Selective Circuits

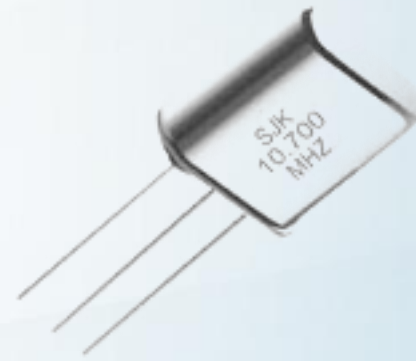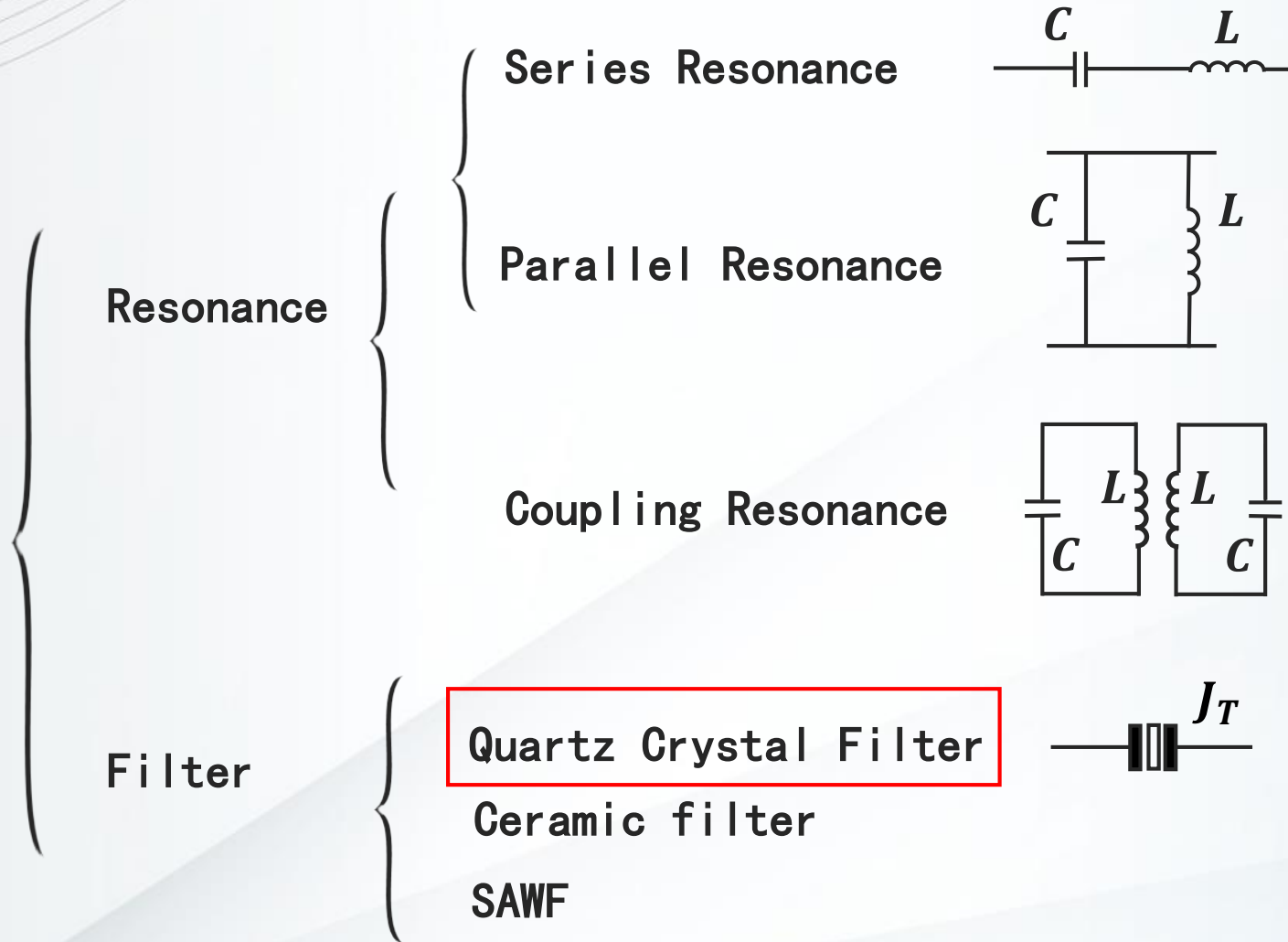


Piezoelectric Effect

Quartz Crystal Filter

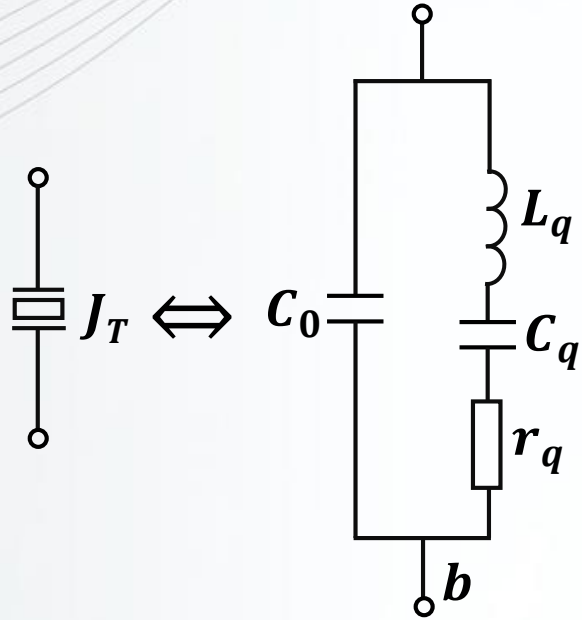

Equivalent Circuit ($C_q \ll C_0$)

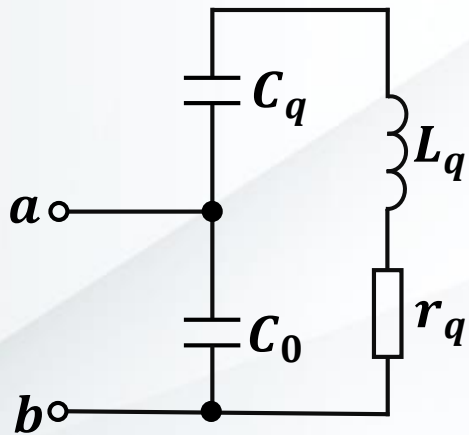

$$\left\{ \begin{array}{ll} \text{Series Frequency} & \omega_q = \frac{1}{\sqrt{L_q C_q}} \\ \text{Parallel Frequency} & \omega_p = \frac{1}{\sqrt{L_q \frac{C_0 C_q}{C_0 + C_q}}} \end{array} \right.$$


$\frac{C_0 C_q}{C_0 + C_q}$

$C_0 + C_q$


(1) $p \approx \frac{C_q}{C_0}$ Very Small 10^{-3}

(2) $Q = \frac{1}{r_q} \sqrt{\frac{L_q}{C_q}}$ Very Large

Quartz Crystal Filter

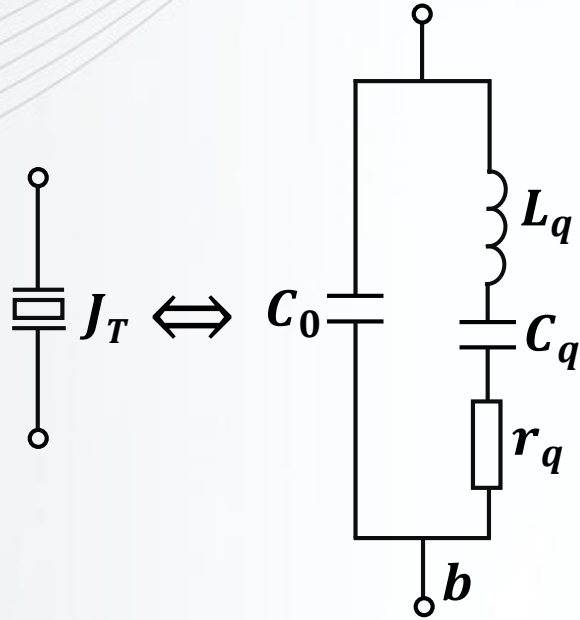

Equivalent Circuit ($C_q \ll C_0$)

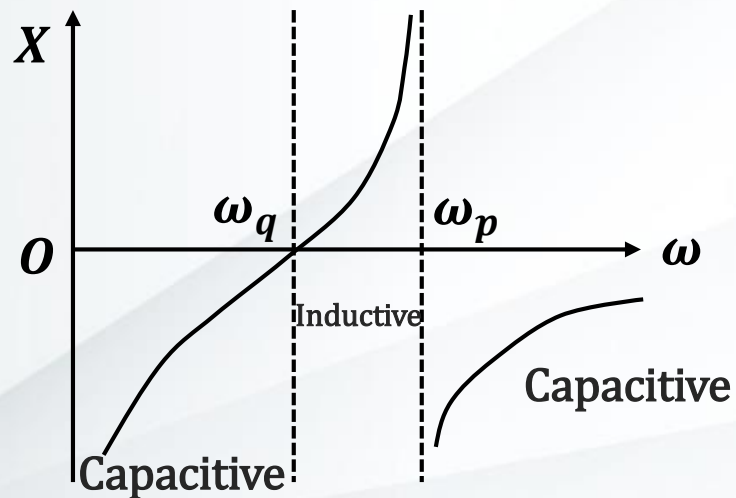

Series Frequency $\omega_q = \frac{1}{\sqrt{L_q C_q}}$

Parallel Frequency $\omega_p = \frac{1}{\sqrt{L_q \frac{C_0 C_q}{C_0 + C_q}}}$

$C_0 + C_q$

(1) $p \approx \frac{C_q}{C_0}$ Very Small


(2) $Q = \frac{1}{r_q} \sqrt{\frac{L_q}{C_q}}$ Very Large

(3) $\omega_p > \omega_q$


(4) $\omega_p = \omega_q \sqrt{1 + \frac{C_q}{C_0}} = \omega_q \sqrt{1 + p}$

ω_p ω_q Very Close


Quartz Crystal Filter

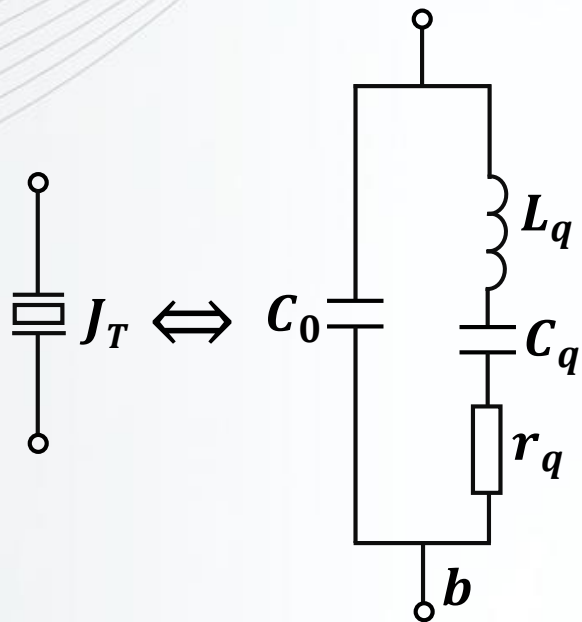


Equivalent Circuit ($C_q \ll C_0$)

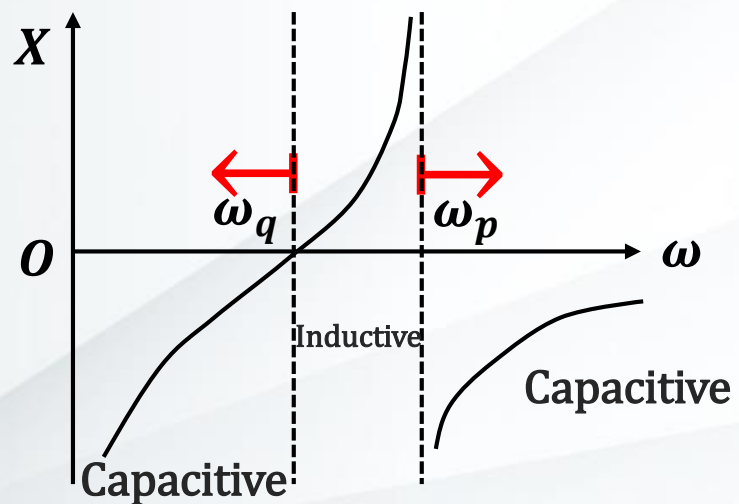

Increase bandwidth

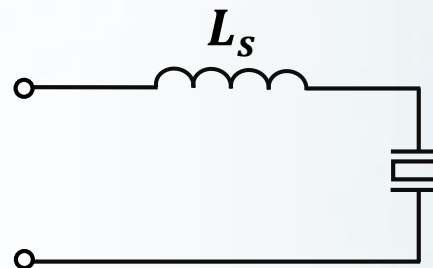

Decrease ω_q



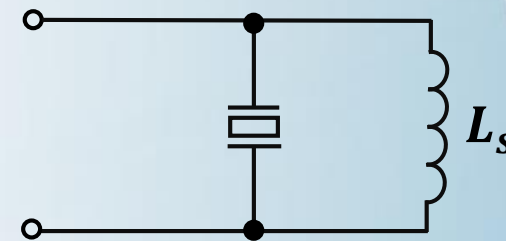


Increase ω_p




Ceramic Filter


Frequency Selective Circuits

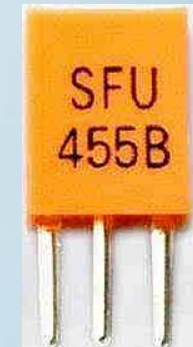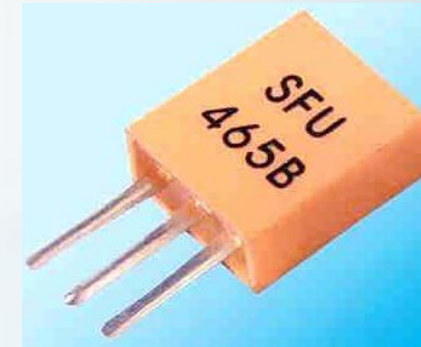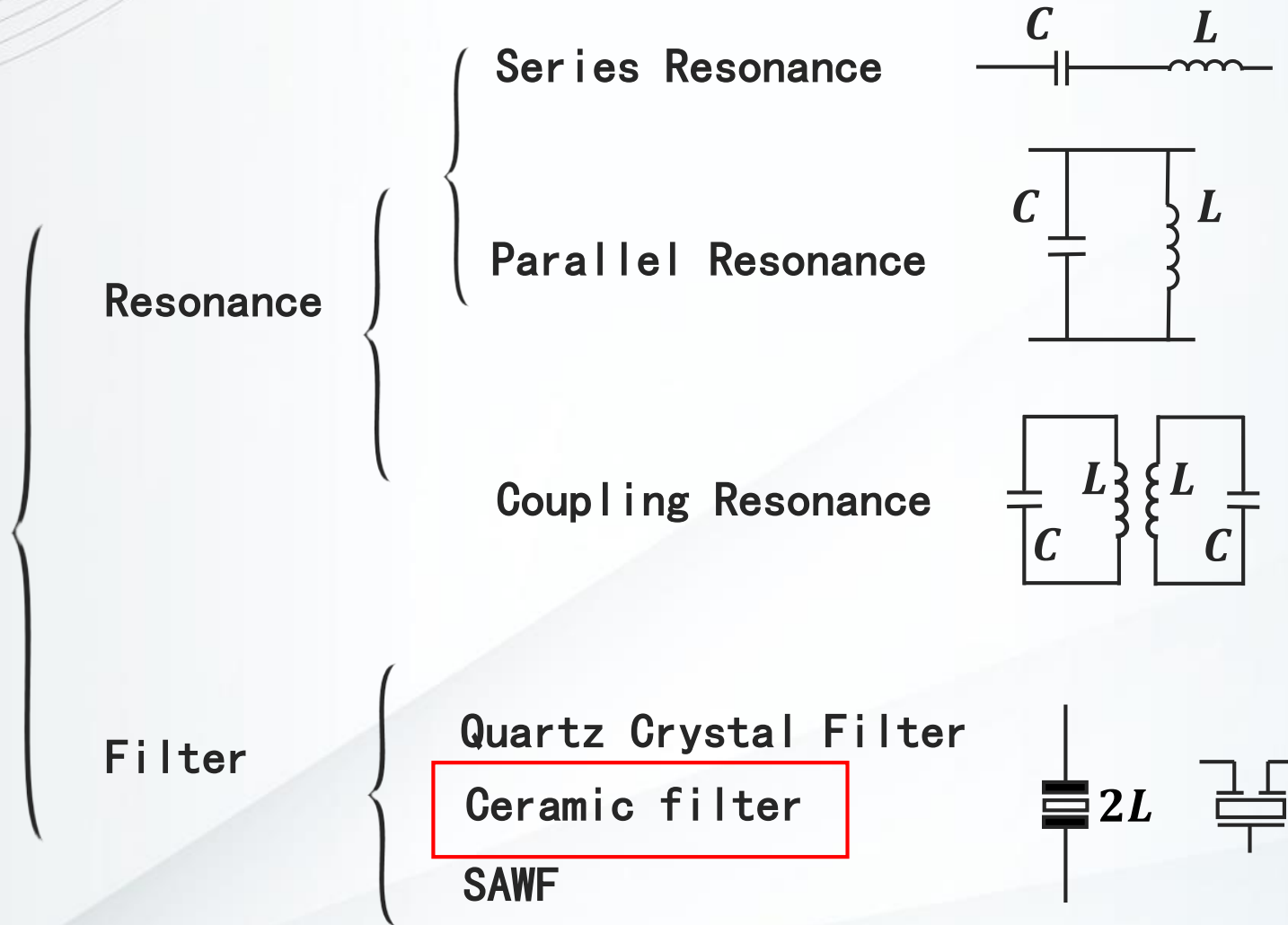

Ceramic Filter_a

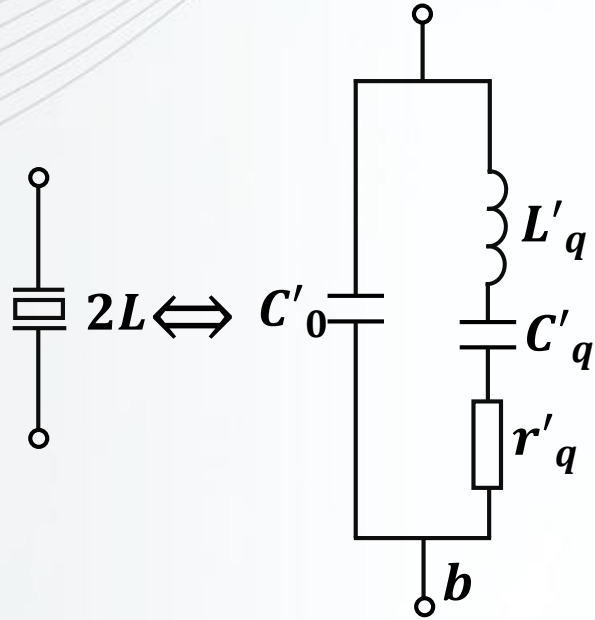

Equivalent Circuit

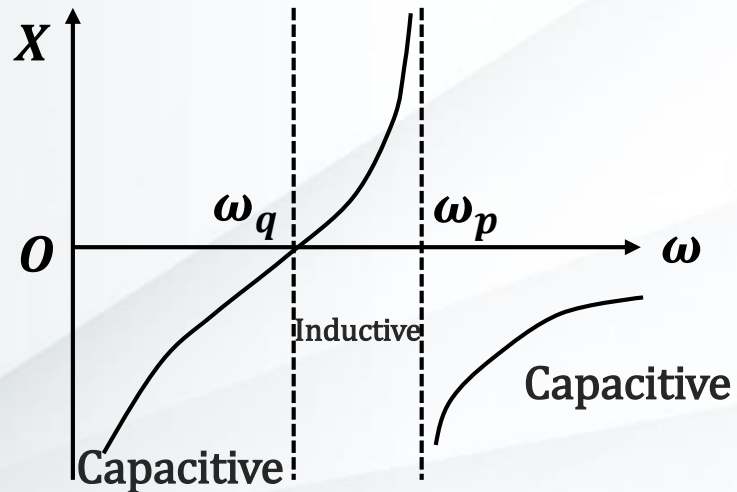

Series Frequency $\omega_q = \frac{1}{\sqrt{L'_q C'_q}}$


Parallel Frequency $\omega_p = \frac{1}{\sqrt{L'_q \frac{C'_0 C_q}{C'_0 + C_q}}}$

$C'_0 + C'_q$

- LC Resonator $< Q < \text{Quartz Crystal}$


Ceramic Filter

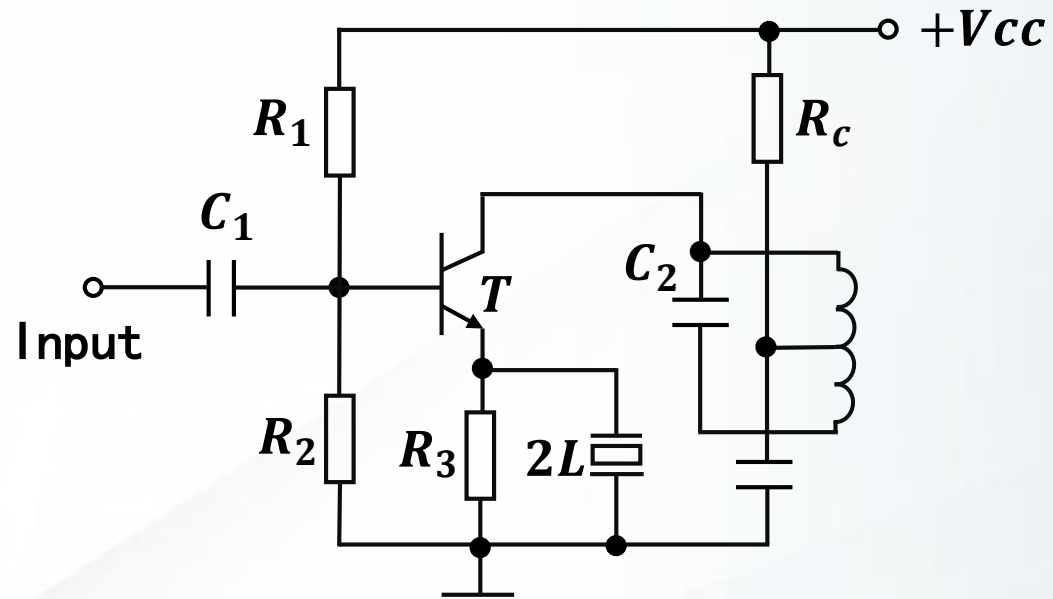Exp1: $f_0 = 465kHz$, analyze the circuit function.



Ceramic Filter

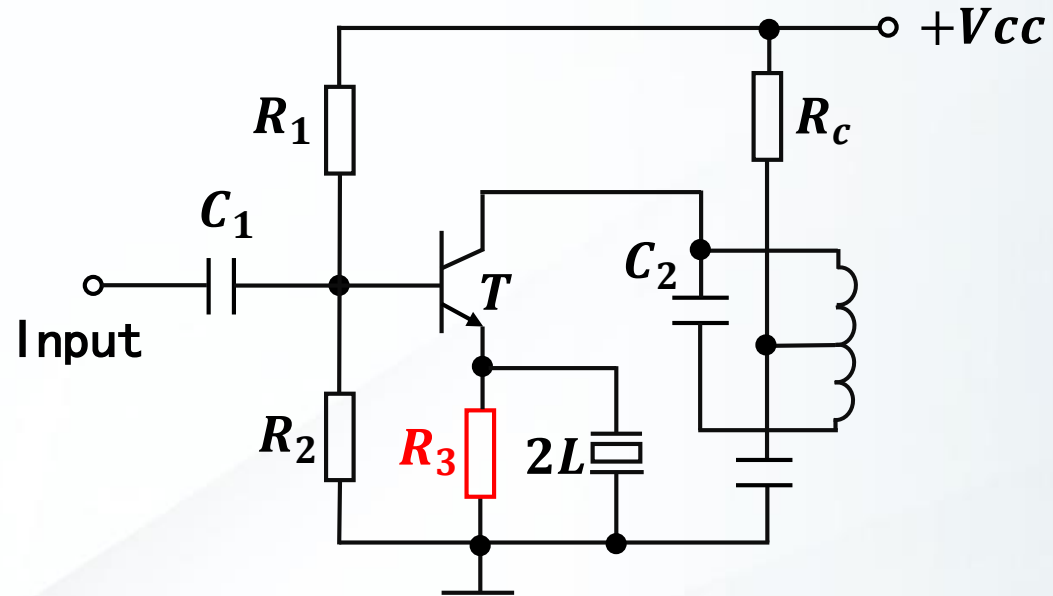
Exp1: $f_0 = 465kHz$, analyze the circuit function.




Solve: Series frequency of $2L = 465kHz$

For $465kHz$, Impedance \downarrow , Negative Feedback \downarrow , Gain \uparrow

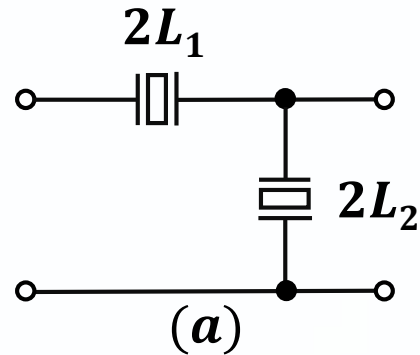
Four-terminal Ceramic Filter : Ceramic Resonator



2 Ceramic Resonator

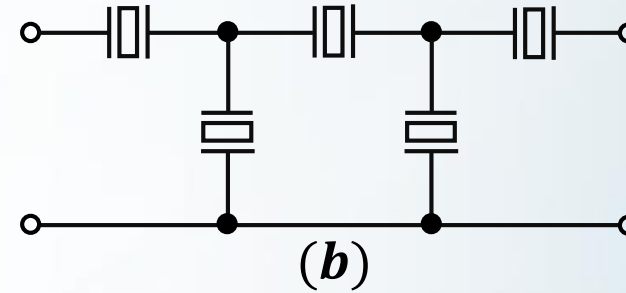

5 Ceramic Resonator

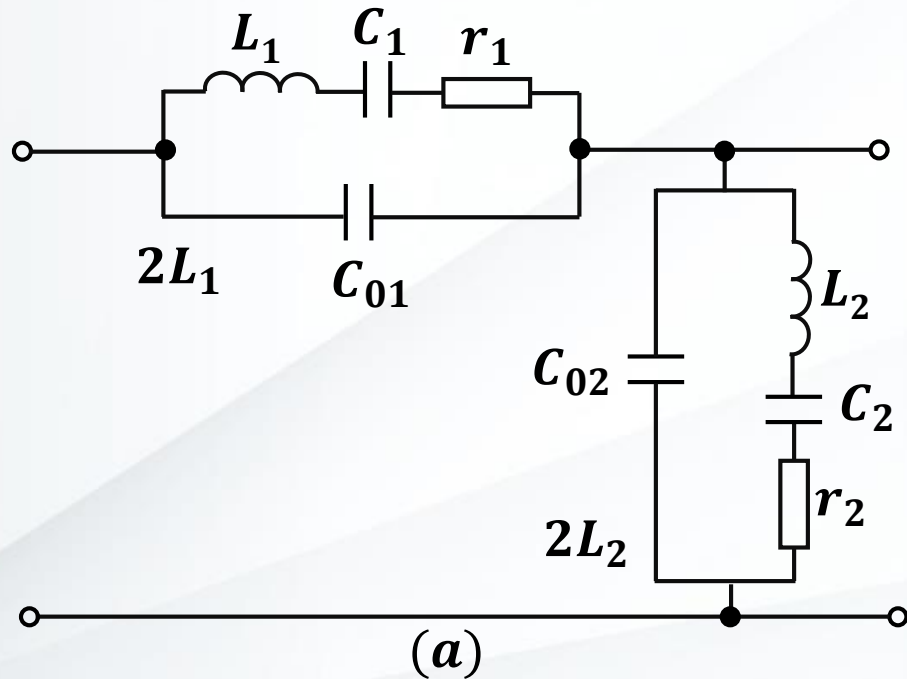

Four-terminal Ceramic Filter


Exp2: How to design $(465 \pm 5)kHz$ filter?

Solve: For $465kHz$:

$2L_1$ Series frequency = $465kHz$

$2L_2$ Parallel frequency = $465kHz$
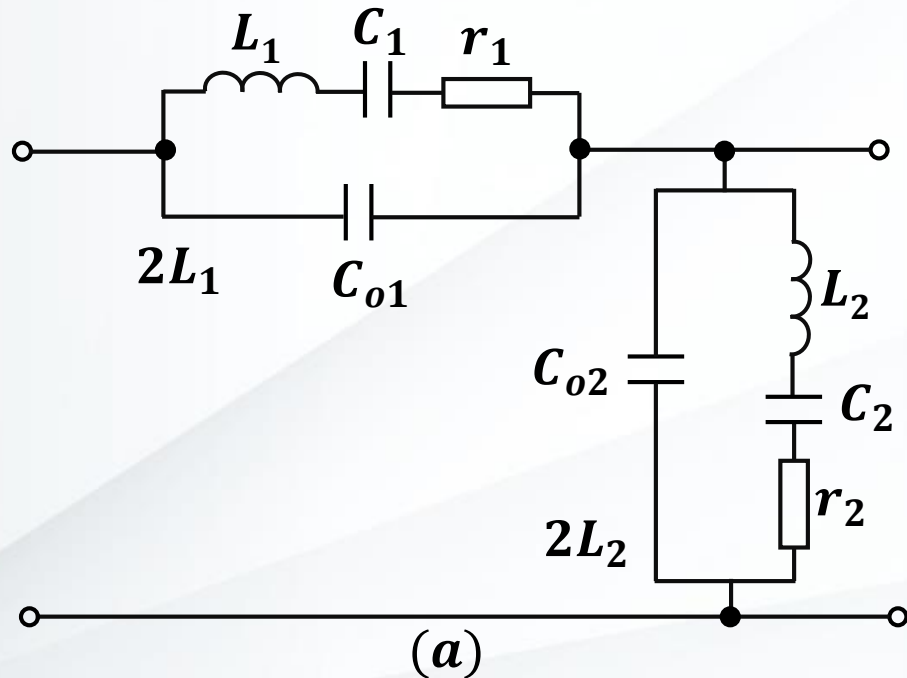
$$f_{q1} = 465kHz \quad f_{p1} = (465 + 5)kHz$$



$$f_{q2} = (465 - 5)kHz$$

$$f_{p2} = 465kHz$$

