



**Huazhong University of Science and Technology**  
**The Department of Electronics and Information Engineering**

# **Electronic Circuit Analysis and Design**

**Dr. Tianping Deng**

**Email: [dengtp@hust.edu.cn](mailto:dengtp@hust.edu.cn)**

# Contents

## PART 1 SEMICONDUCTOR DEVICES AND BASIC APPLICATIONS

Chapter 1 Semiconductor Materials and Diodes

Chapter 2 Diode Circuits

Chapter 3 The Field-Effect Transistor

Chapter 4 Basic FET Amplifiers

 Chapter 5 The Bipolar Junction Transistor

Chapter 6 Basic BJT Amplifiers

Chapter 7 Frequency Response

Chapter 8 Output Stages and Power Amplifiers

## PART 2 ANALOG ELECTRONICS

Chapter 9 Ideal Operational Amplifiers and Op-Amp Circuits

Chapter 10 Integrated Circuit Biasing and Active Loads

Chapter 11 Differential and Multistage Amplifiers

Chapter 12 Feedback and Stability

Chapter 13 Operational Amplifier Circuits

Chapter 14 Nonideal Effects in Operational Amplifier Circuits

Chapter 15 Applications and Design of Integrated Circuits

# Ch5. The Bipolar Junction Transistor

---

## 5.1 Basic Bipolar Junction Transistor


## 5.2 DC Analysis of Transistor Circuits

## 5.3 Basic Transistor Application

## 5.4 Basic Transistor Biasing

## 5.5 Multistage Circuits

P287—P352

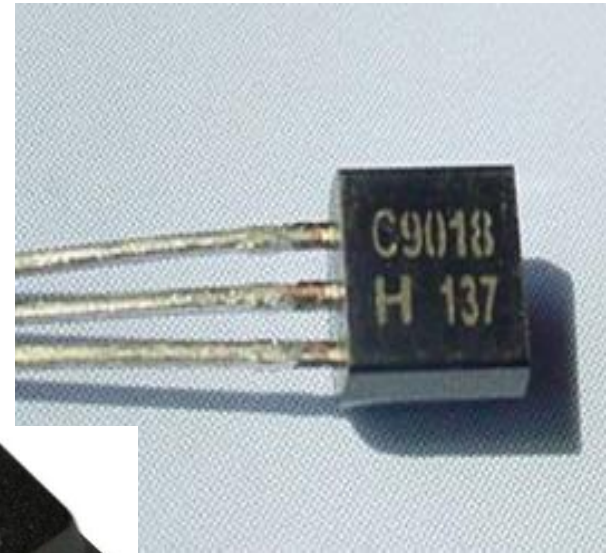

# Ch5. The Bipolar Junction Transistor

---

## 5.1 Basic Bipolar Junction Transistor

### 5.1.1 Transistor Structure

### 5.1.2 NPN Transistor: Forward-Active Mode Operation

### 5.1.3 PNP Transistor: Forward-Active Mode Operation

### 5.1.4 Circuit Symbols and Conventions

### 5.1.5 Current-voltage Characteristics

### 5.1.6 Nonideal Transistor Leakage Current and Breakdown Voltage




# Review:

P

N

Forward  
Bias


Reverse  
Bias

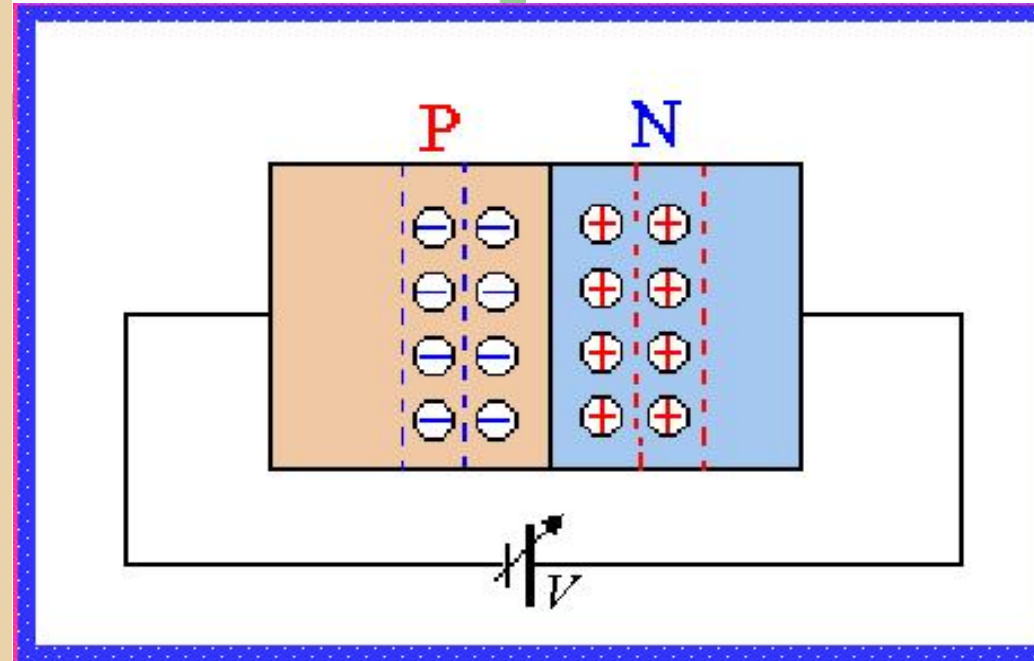
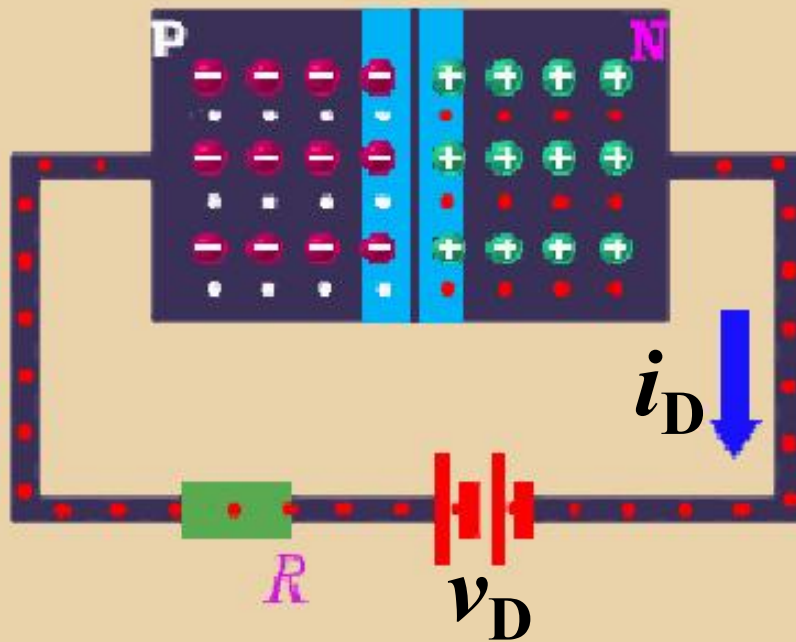
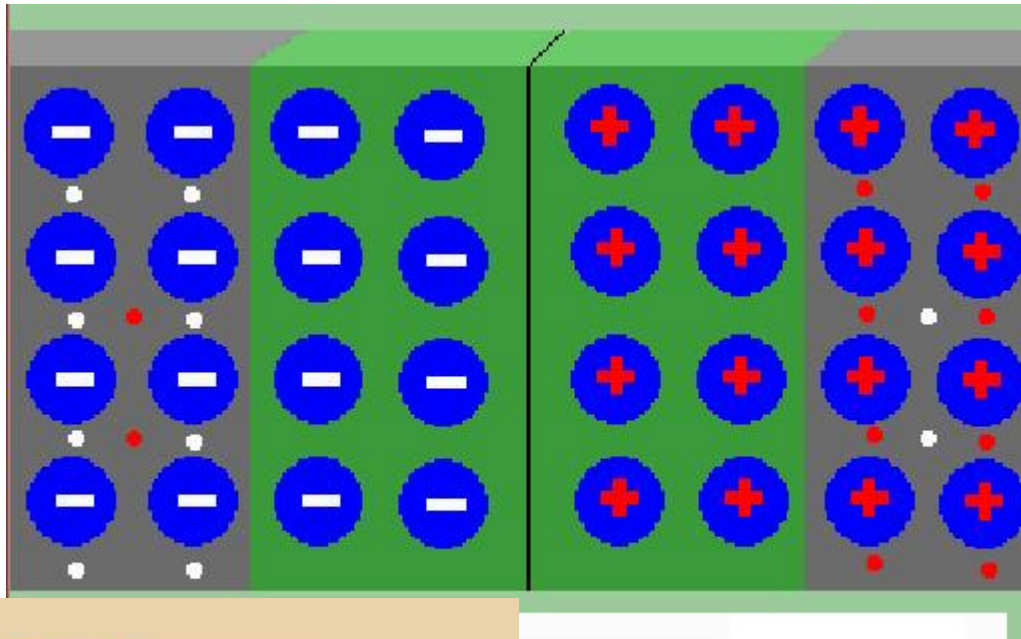


# 5.1 Basic Bipolar Junction Transistor (BJT)

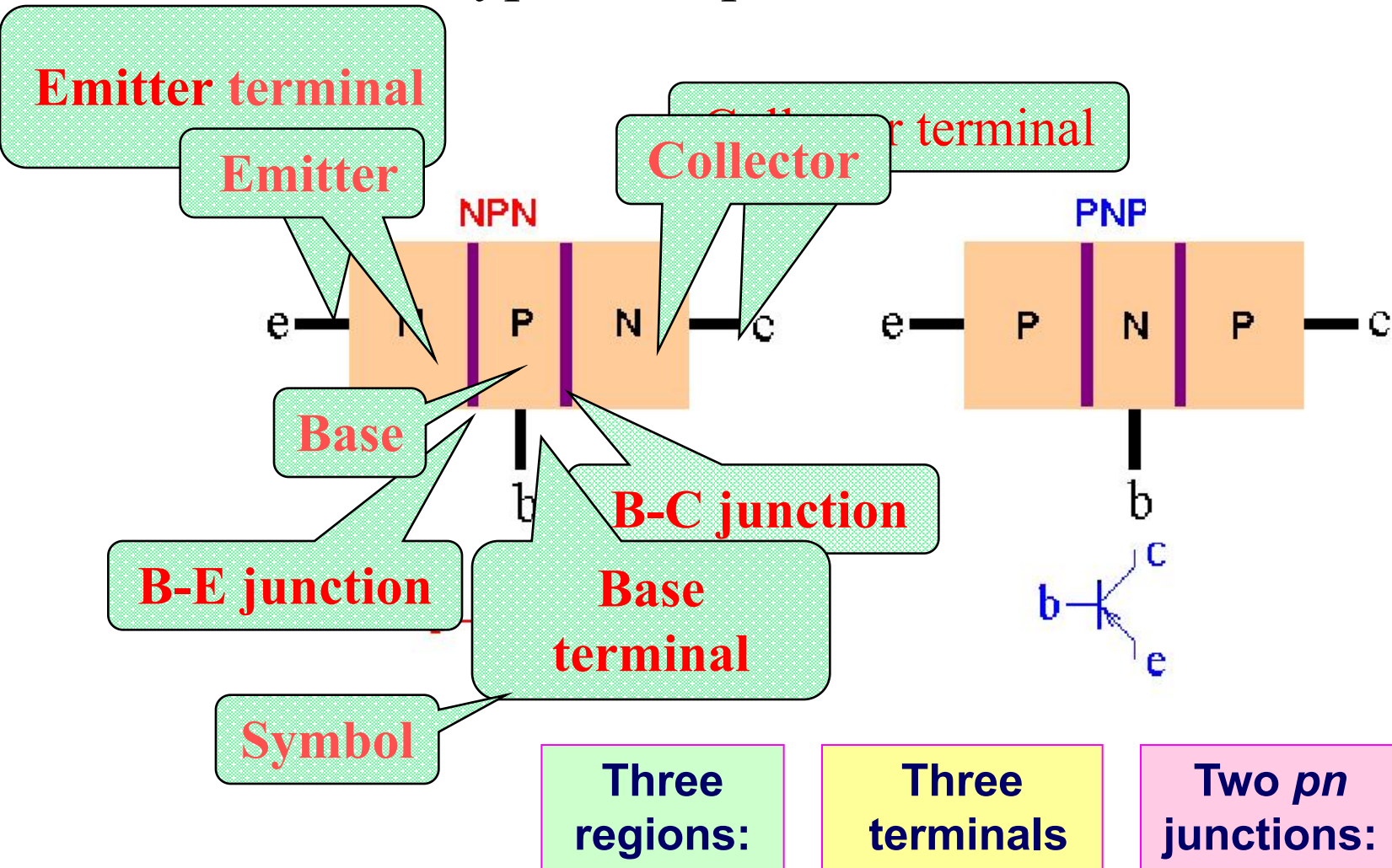
## 5.1.1 Transistor Structure

- There are two types of bipolar transistor: **NPN** and **PNP**.



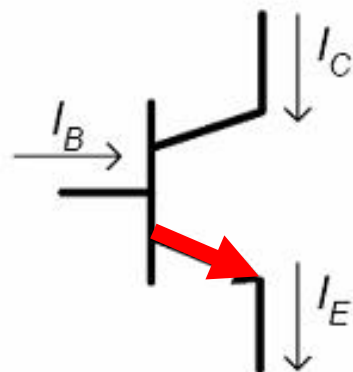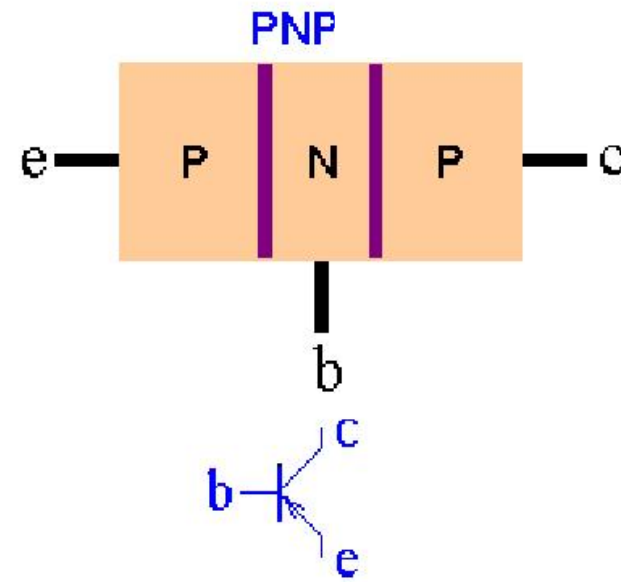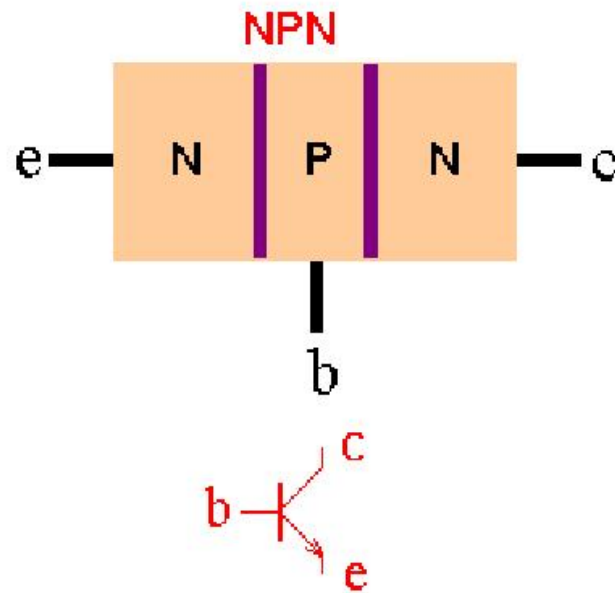

npn

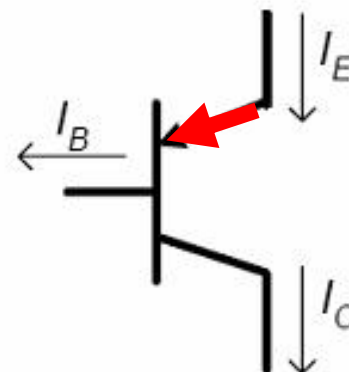


pnnp

**The emitter is distinguished by the arrowhead.**

# 5.1.1 Transistor Structure
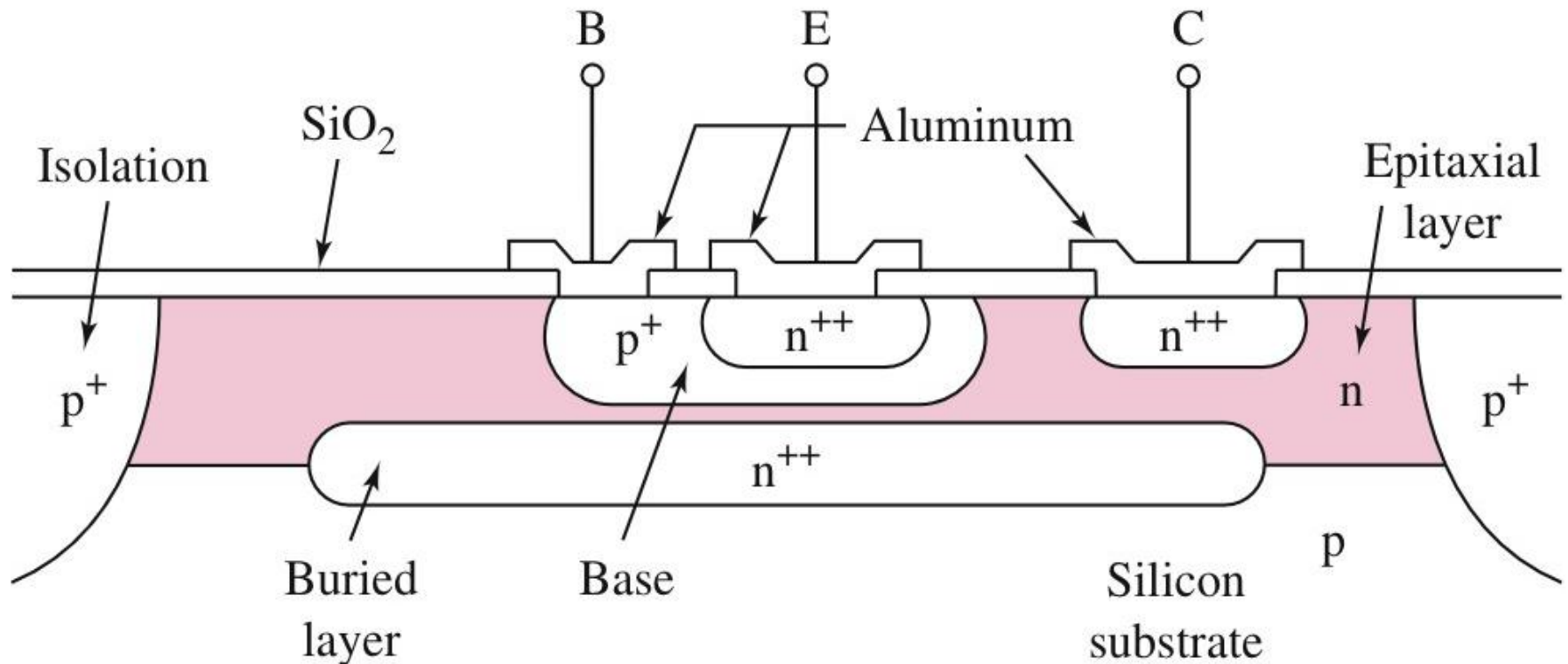
## Cross Section of Integrated Circuit NPN Transistor



Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.


**Not symmetrical**


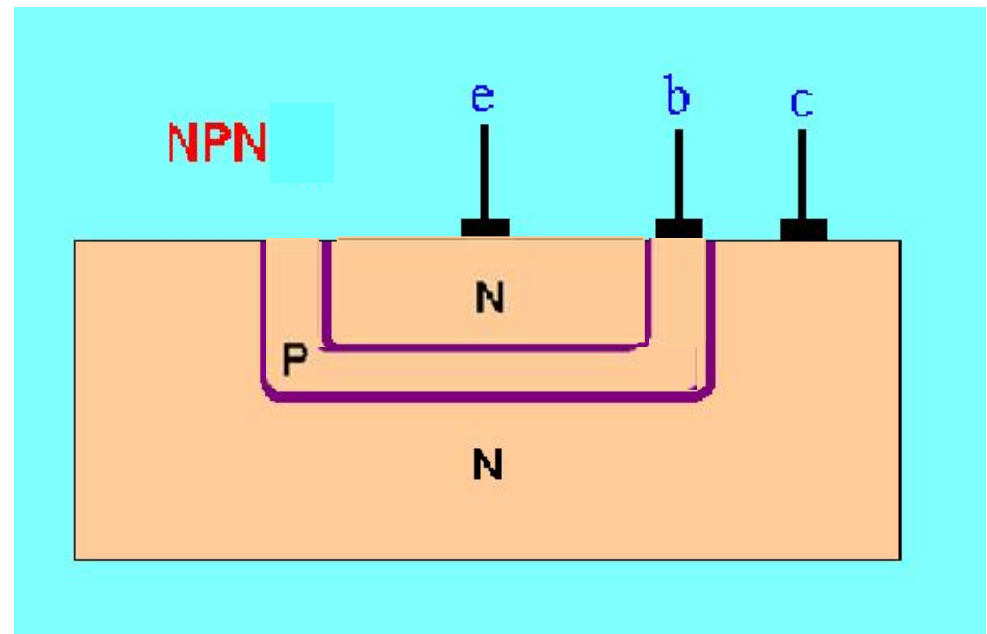
## 5.1.1 Transistor Structure

- Feature of transistor structure 浓度
  - (1) Impurity doping **concentration** in emitter region is much larger than other two regions.
  - (2) Area of collector region is bigger than that of emitter.
  - (3) Base must be very narrow.

- Emitter: heavily doped
- Base: very thin



Cross section of NPN bipolar Transistor




## 5.1.2 NPN Transistor: Forward-Active Mode Operation

- Amplification condition

If transistor is used as an amplifying device.


- **B-E junction is forward biased.**
- **B-C junction is reverse biased.**

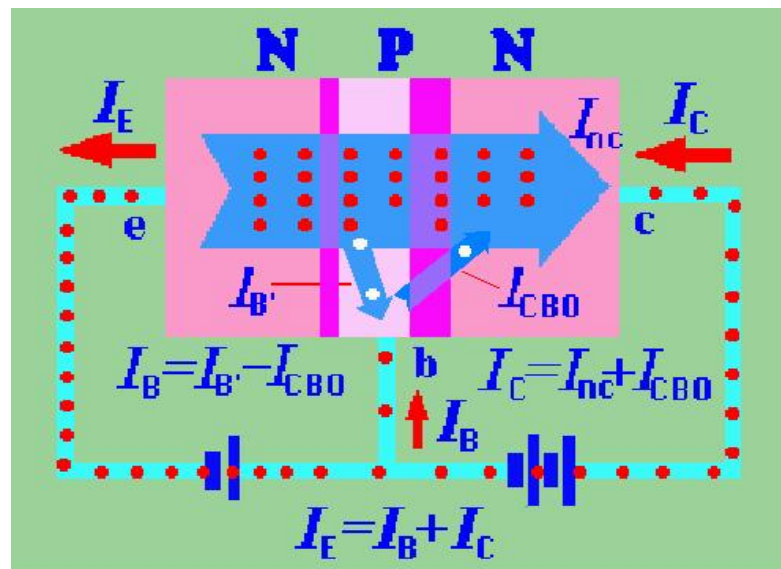It is called the forward-active operating mode, or active region.




**NPN bipolar transistor biased  
in the forward-active mode**

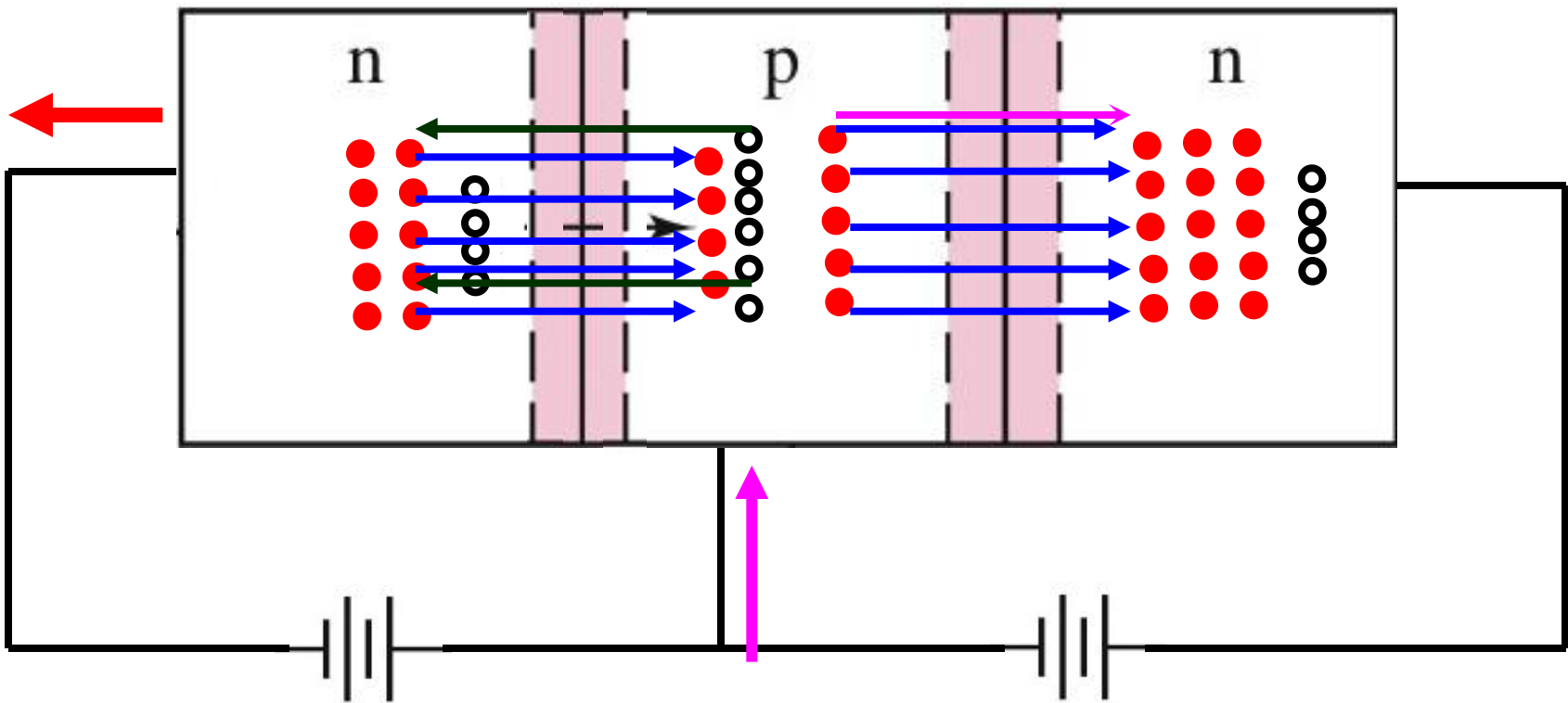- B-E junction is forward biased.
- B-C junction is reverse biased.


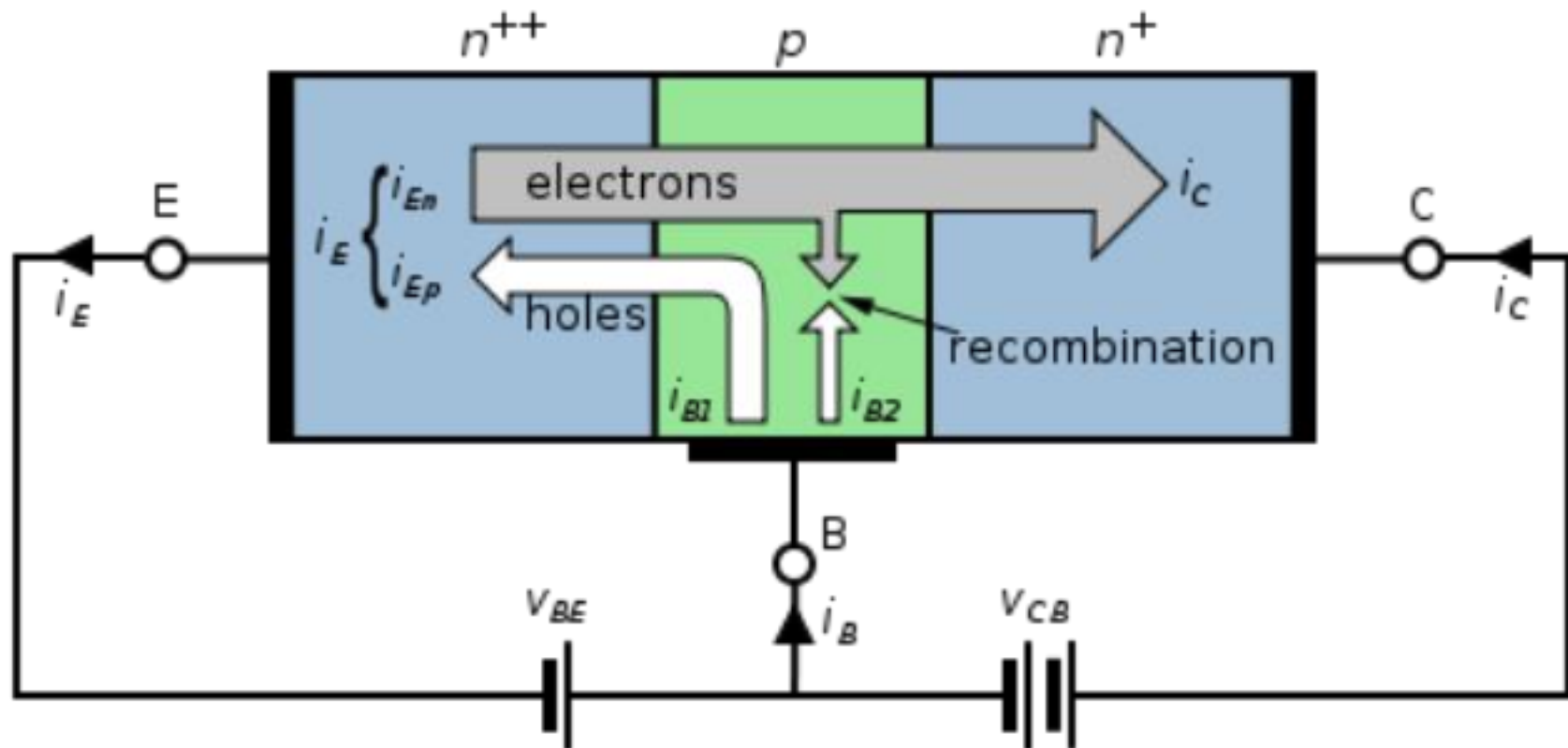
## 5.1.2 NPN Transistor: Forward-Active Mode Operation(P289)




## 5.1.2 NPN Transistor: Forward-Active Mode Operation


- Amplification condition

### 1. Transfer process of carriers in npn

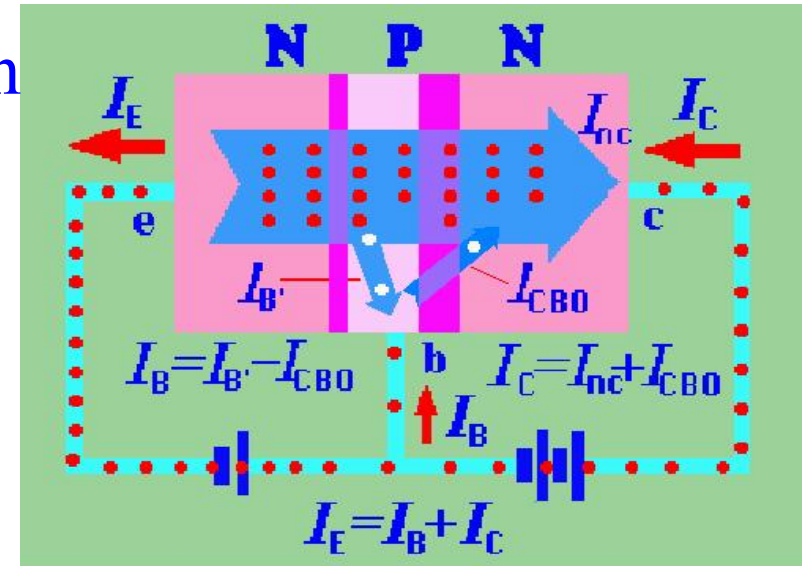- (1) Emitter region **emit** electrons into base.
- (2) Collector region **collect** electrons injected base from emitter.
- (3) B-E voltage controls collector current.




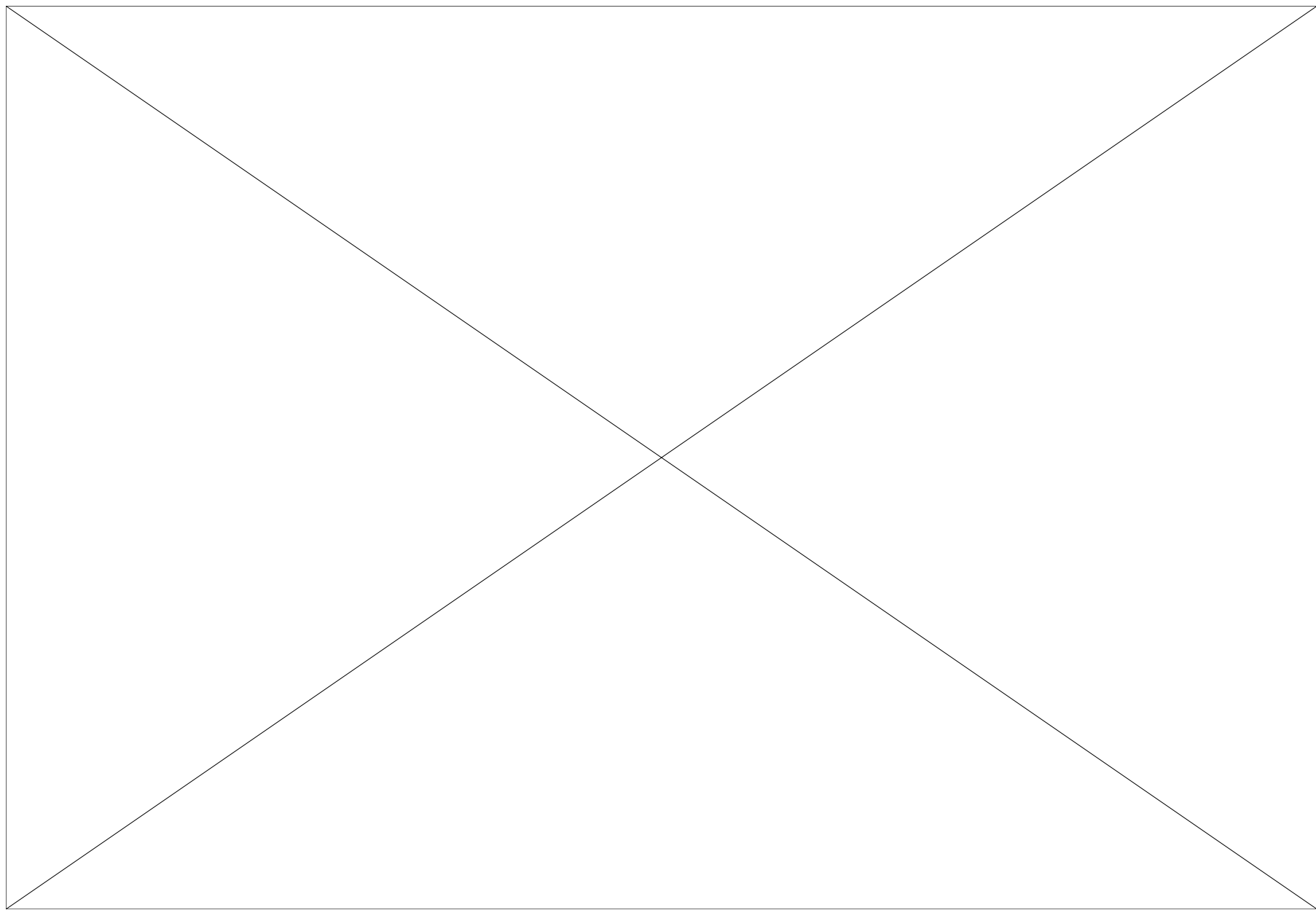**NPN bipolar transistor biased in the forward-active mode**


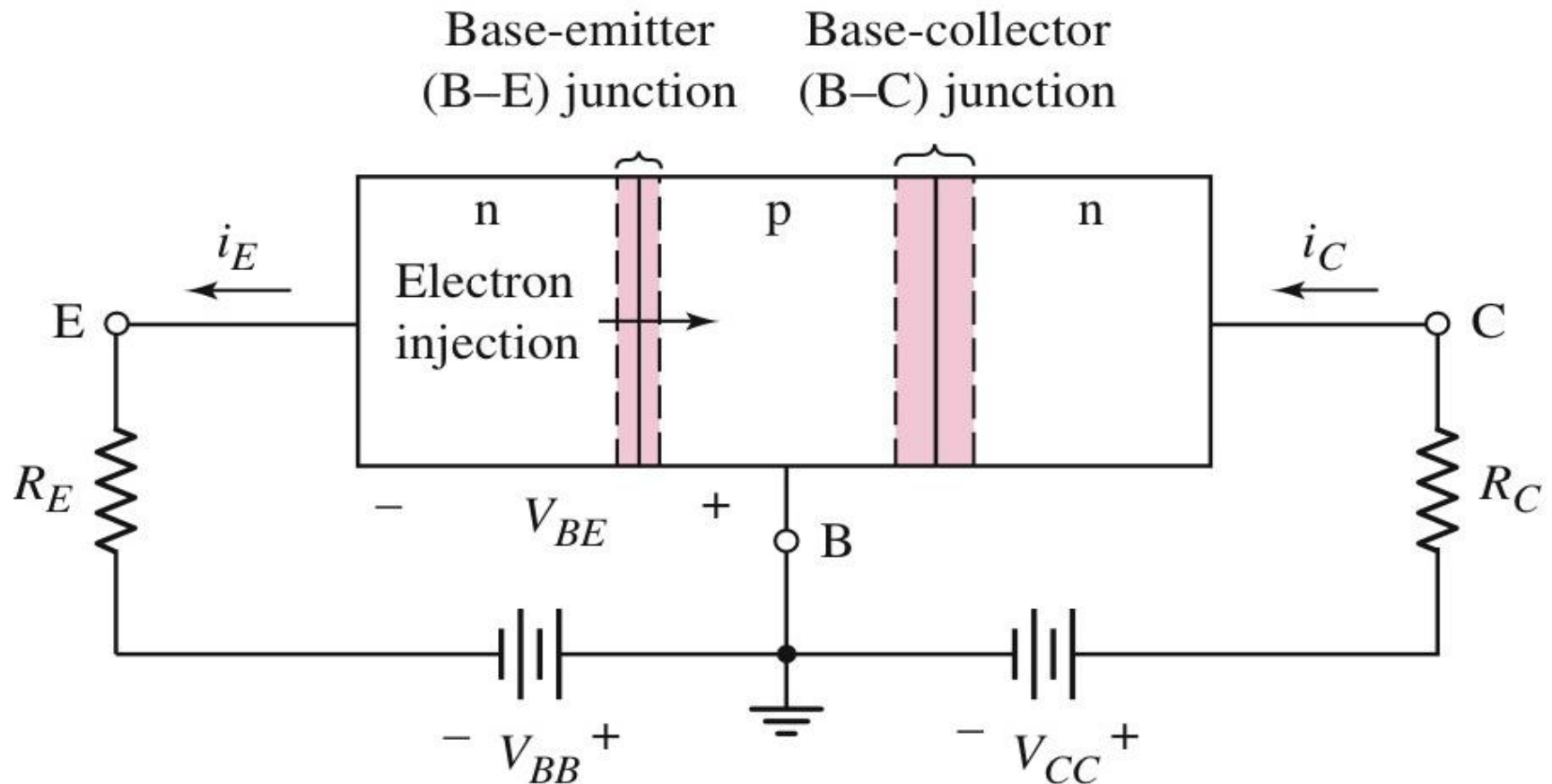
## 5.1.2 NPN Transistor: Forward-Active Mode Operation


- There are two types of carriers, electrons and holes contributing to the current, so the transistor is called **bipolar junction transistor (BJT)**.



## 5.1.2 NPN Transistor: Forward-Active Mode Operation

### Electrons and Holes in NPN BJT (P290)

#### •Emitter Current

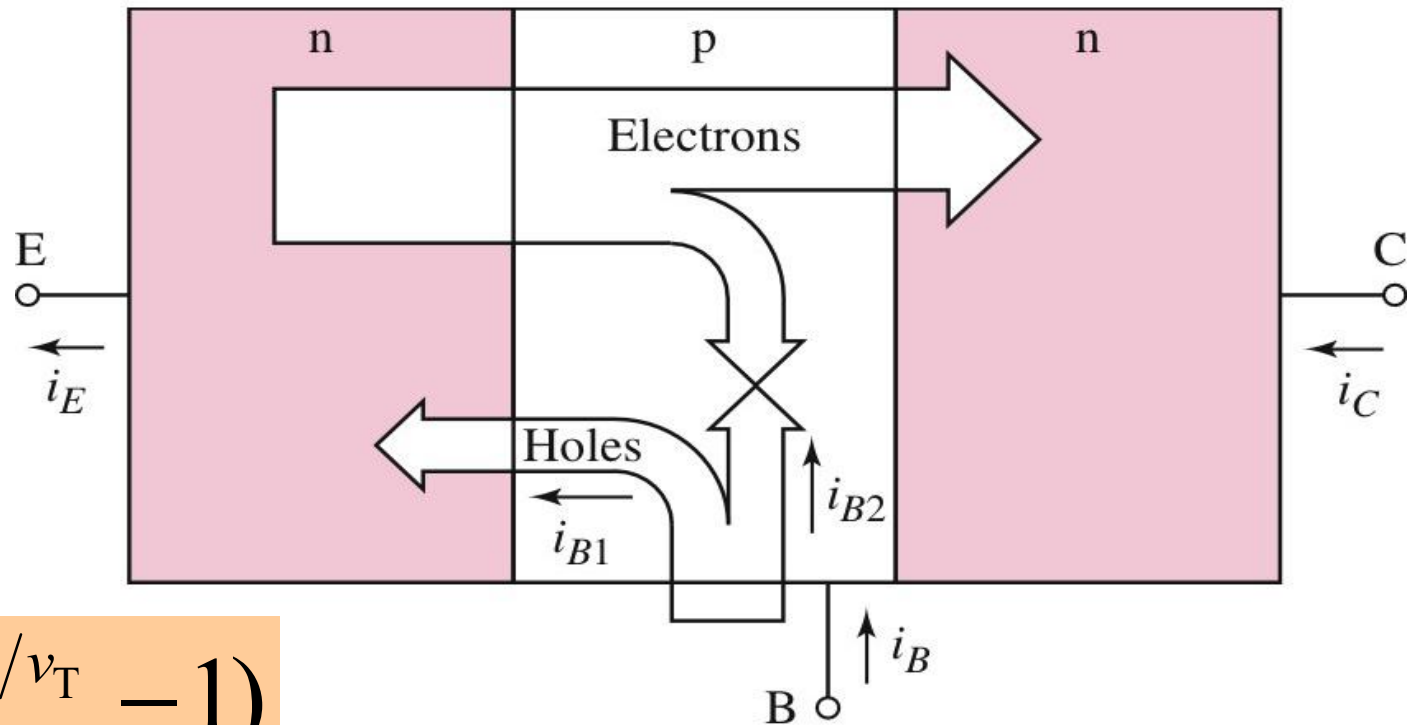

$$i_E = I_{ES} (e^{v_{BE}/v_T} - 1)$$

$$\approx I_{ES} e^{v_{BE}/v_T}$$

$V_T$  \_\_ thermal voltage

$I_{ES}$  \_\_ emitter leakage current



## 2. Current relationships

- We know from transfer process of carriers

$$I_E = I_B + I_C, \quad I_C = I_{nC} + I_{CBO}, \quad I_B = I_{B'} - I_{CBO}$$


Assume  $\alpha = \frac{\text{Collector current}}{\text{Emitter current}}$

that is  $\alpha = \frac{I_{nC}}{I_E}$

generally  $I_C \gg I_{CBO}$

then  $\alpha \approx \frac{I_C}{I_E}$

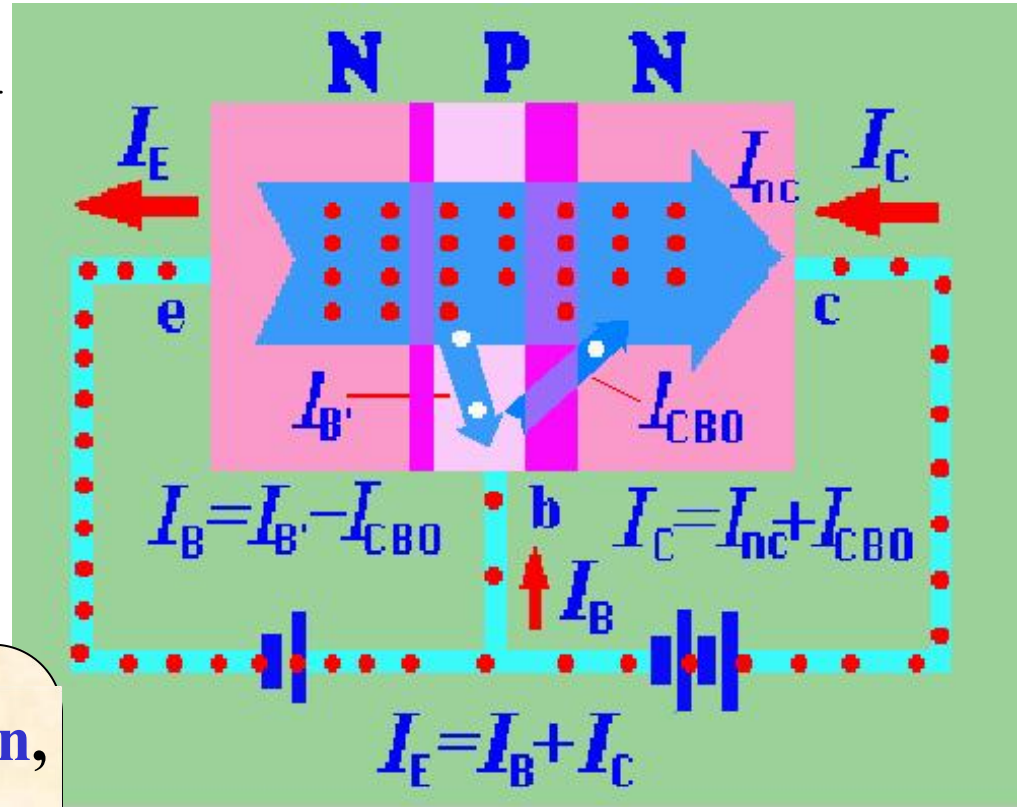$\alpha$  --common-base current gain,  
only depend on geometries and  
concentration, no relation with  
voltages. Generally  $\alpha = 0.9 \sim 0.99$



Transfer process of carriers

## 2. Current relationships

assume  $\beta = \frac{\alpha}{1-\alpha}$  since  $I_E = I_B + I_C$ ,  $I_C = I_{nC} + I_{CBO}$ ,  $\alpha = \frac{I_{nC}}{I_E}$

$$\beta = \frac{(I_C - I_{CBO})/I_E}{1 - (I_C - I_{CBO})/I_E} = \frac{I_C - I_{CBO}}{I_E - I_C + I_{CBO}}$$

then  $I_C = \beta(I_E - I_C) + (1 + \beta)I_{CBO}$

assume  $I_{CEO} = (1 + \beta)I_{CBO}$  (leakage current)

then  $\beta = \frac{I_C - I_{CEO}}{I_B}$  when  $I_C \gg I_{CEO}$ ,

$$\beta \approx \frac{I_C}{I_B}$$


$\beta$  is **common-emitter current gain**, also, only depend on geometries and impurity concentration, independent of B-C and B-E voltages. Generally  $50 < \beta < 300$ .

## 2. Current relationships


---

$$\begin{aligned} I_E &= I_B + I_C \\ \alpha &= \frac{I_C}{I_E} \quad \longrightarrow \quad I_C = \alpha I_E \quad 1 \leftarrow \alpha < 1 \\ \beta &= \frac{I_C}{I_B} \quad \longrightarrow \quad I_C = \beta I_B \quad \beta \gg 1 \end{aligned}$$
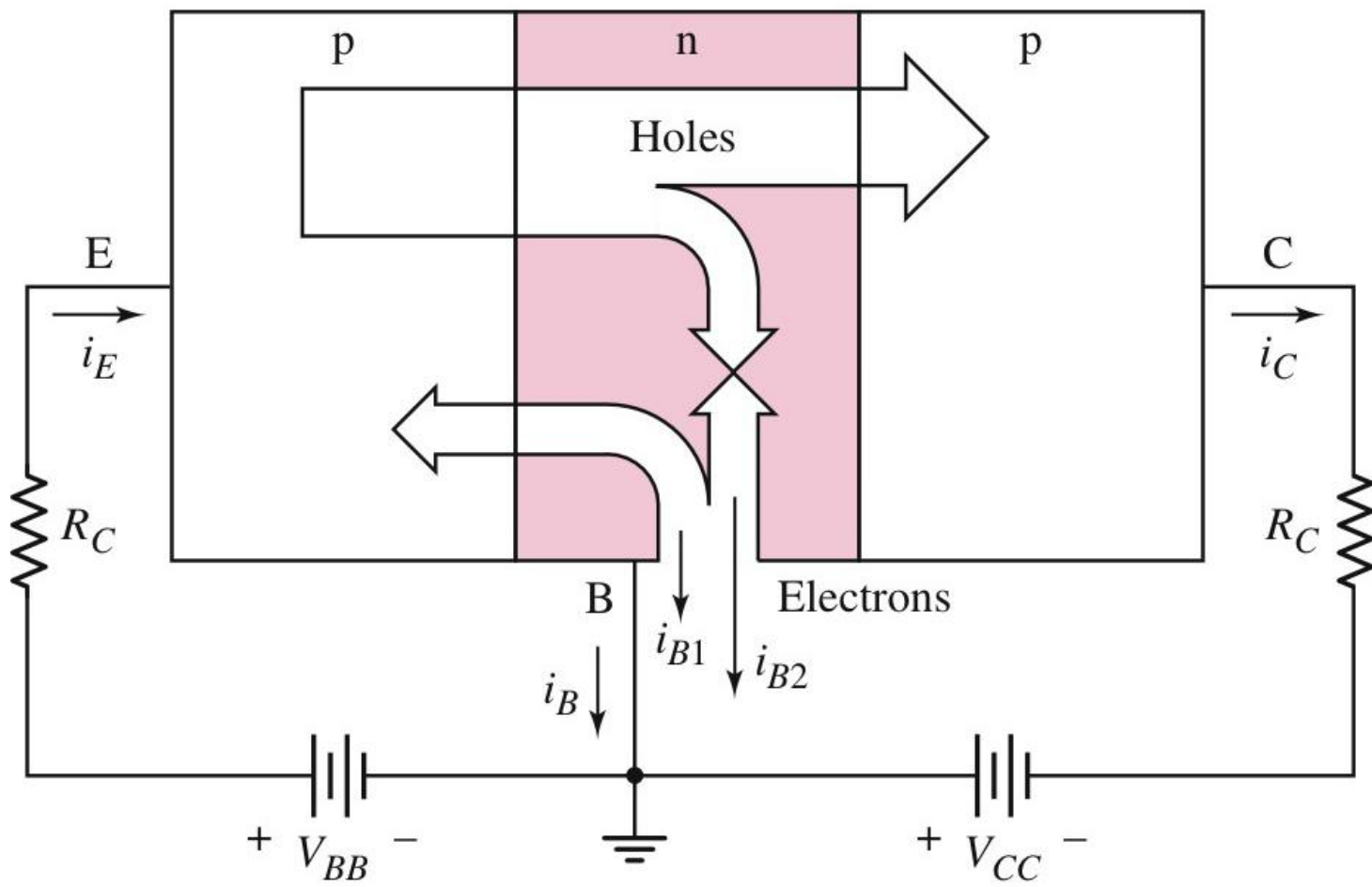
# 5.1.3 PNP Transistor: Forward-Active Mode Operation



# Three Types of Circuit Configurations

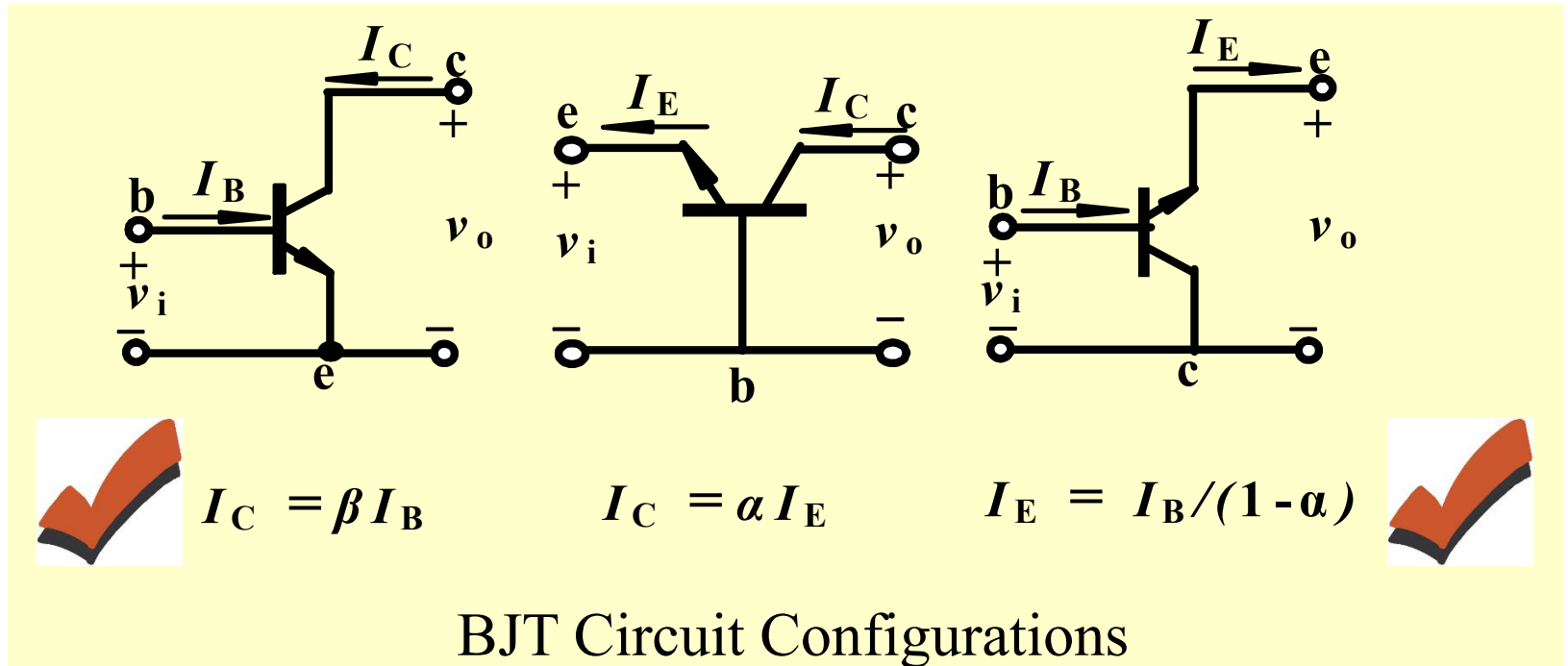


**Common-emitter**, emitter is a common terminal, briefly **CE**;  
**Common-base**, base is a common terminal, briefly **CB**;  
**Common-collector**, collector is a common terminal, briefly **CC**;


Which Configuration can amplify current?



# 5.1.4 Circuit Symbols and Conventions

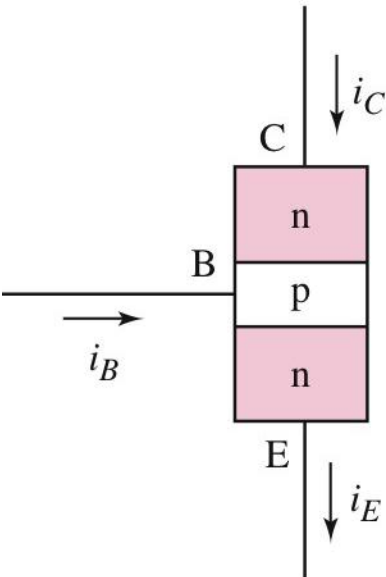


(a)

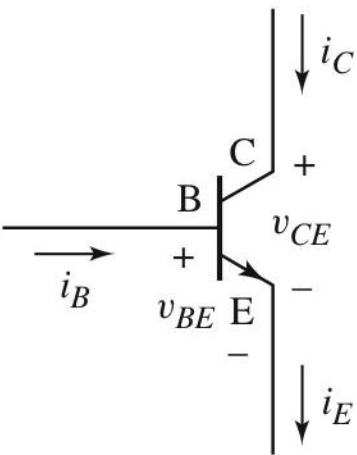


(b)

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

NPN

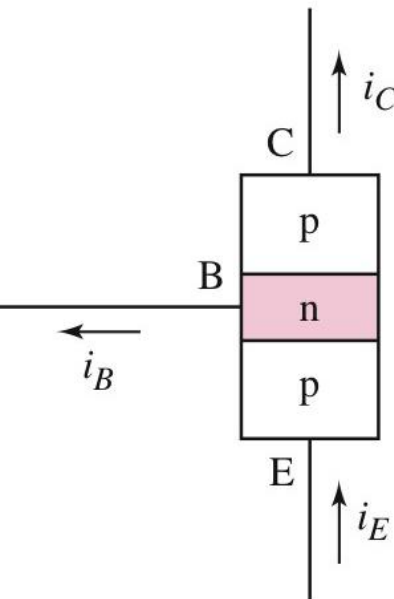

(a)

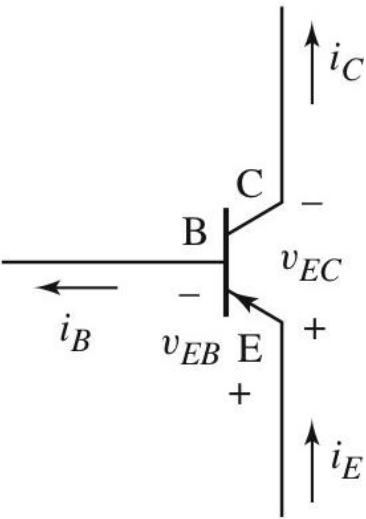

(b)

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.


PNP

# 5.1.4 Circuit Symbols and Conventions





## Common Emitter

## PNP


### NPN

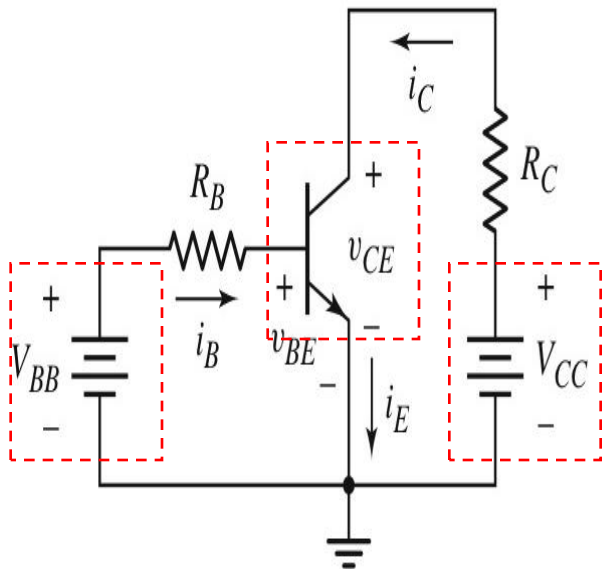

### PNP

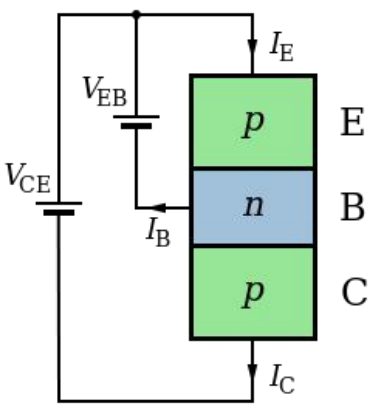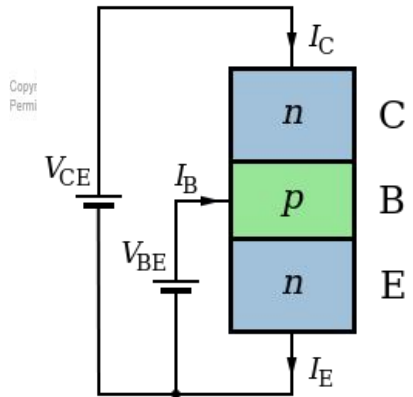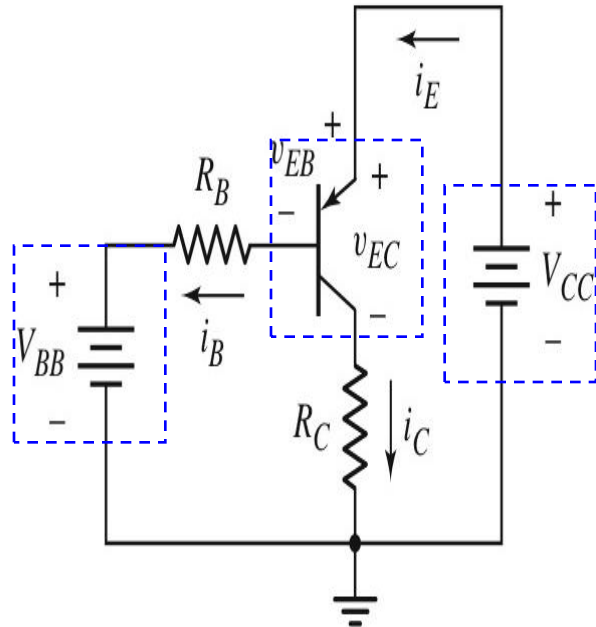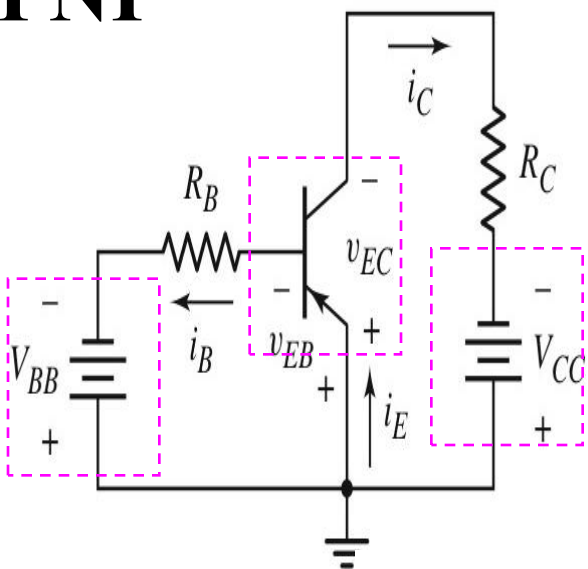

b)

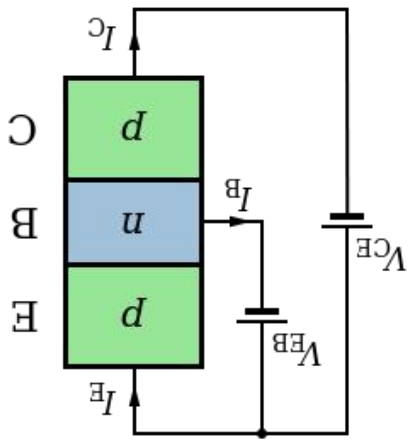

(c)

# 5.1.5 Current-Voltage Characteristics


## 1. Input characteristic of CE

(Taking CE circuit as e.g.)


$$i_B = f(v_{BE}) \Big|_{v_{CE} = \text{const}}$$

(1) when  $v_{CE} = 0V$ , it is same as forward exponential relation of a diode .

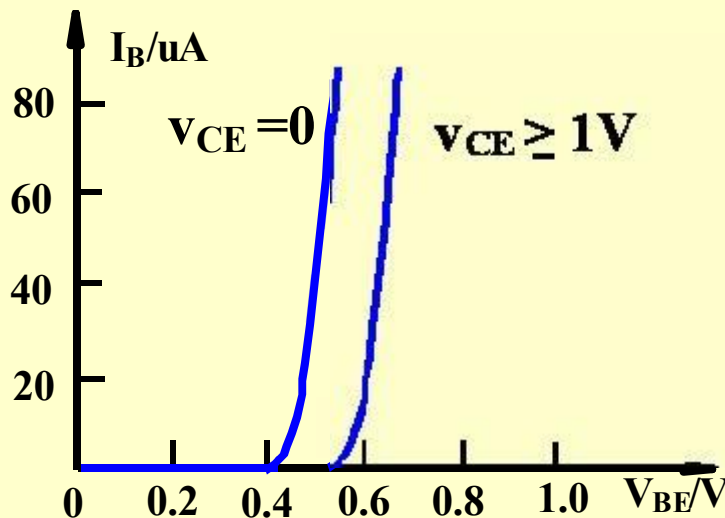(2) When  $v_{CE} \geq 1V$ ,  $v_{CB} = v_{CE} - v_{BE} > 0$ , B-C is reverse biased, some electrons begin to sweep into collector, recombination decreases in base, so  $I_B$  reduces under same  $v_{BE}$ , curve shifts to right.



Simulation

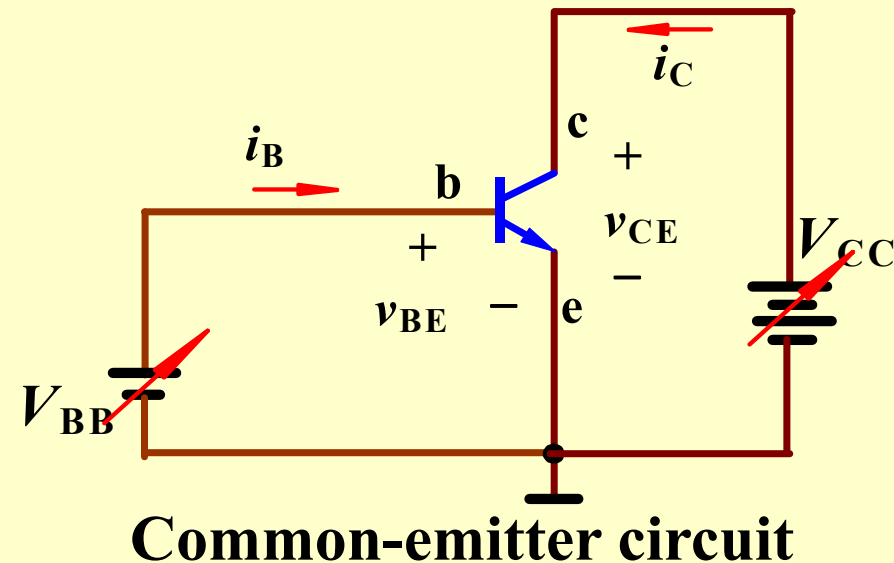




## 5.1.5 Current-Voltage Characteristics
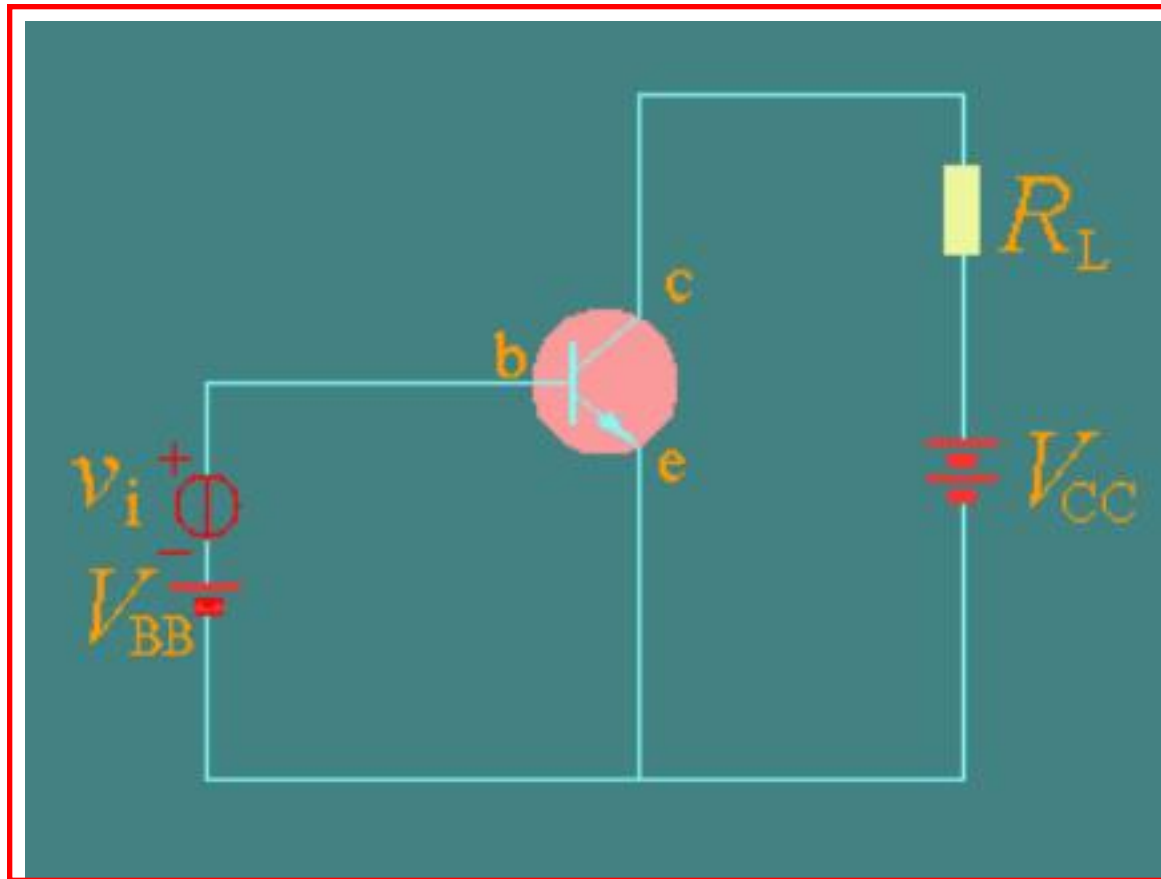
### 2. The output Characteristic of CE

$$i_C = f(v_{CE}) \mid i_B = \text{const}$$



**Simulation**


## 5.1.5 Current-Voltage Characteristics

### 2. Output characteristic of CE (Transistor characteristic)

$$i_C = f(v_{CE}) \big|_{i_B = \text{const}}$$

Four regions for characteristic

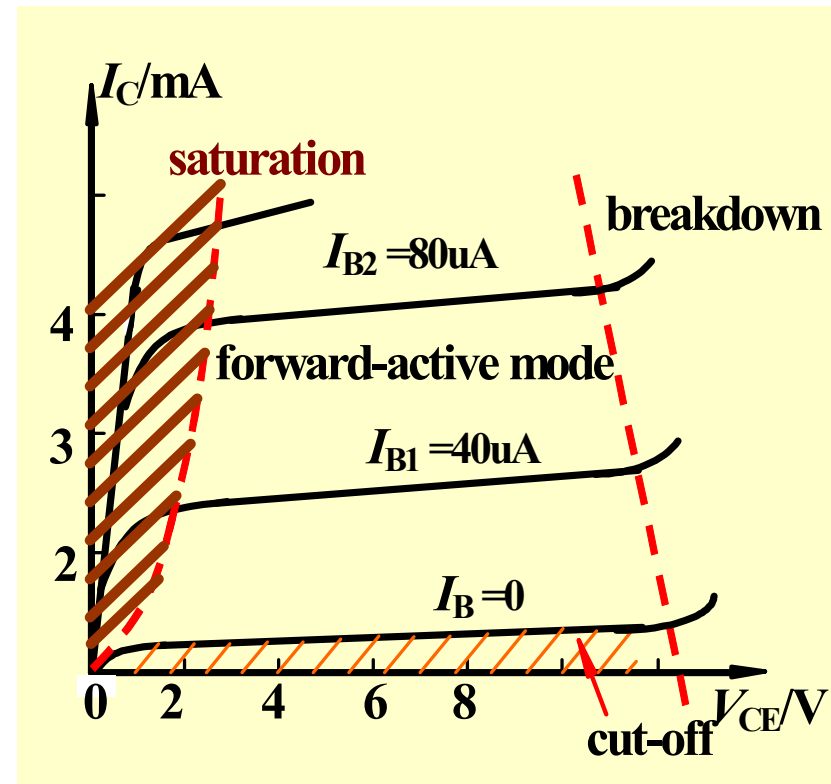**Saturation:**  $i_C$  is controlled by  $v_{CE}$ ,  $i_C$  increases rapidly as  $v_{CE}$  increases, and  $v_{CE} < 0.7V$  (Silicon). **B-E is forward biased, B-C is forward biased, too**, or voltage of reverse biased is very small.




## 5.1.5 Current-Voltage Characteristics

### 2. Output characteristic of CE (Transistor characteristic)

$$i_C = f(v_{CE}) \mid i_B = \text{const}$$

Four regions for characteristic

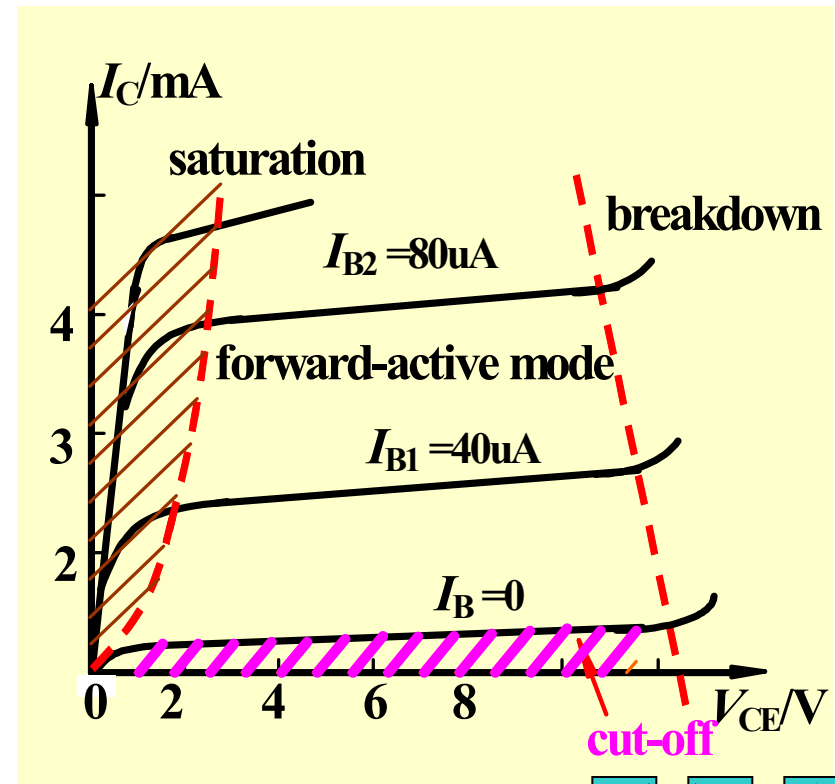**Cut-off:**  $i_C$  is nearly zero, Cut-off region is under  $i_B=0$ .  $V_{BE} < V_{th}$  (turn in voltage), B-C is reverse biased.




## 5.1.5 Current-Voltage Characteristics

### 2. Output characteristic of CE (Transistor characteristic)

$$i_C = f(v_{CE}) \mid i_B = \text{const}$$

Four regions for characteristic

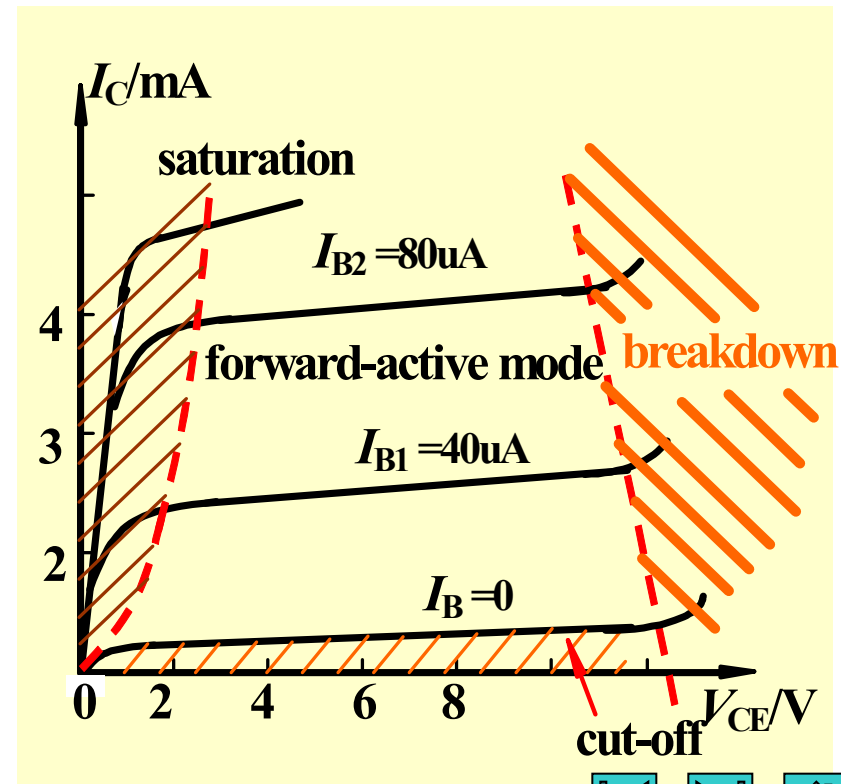**Breakdown:** Reverse-bias voltage of B-C increases too much, B-C junction begin to breakdown.




## 5.1.5 Current-Voltage Characteristics

### 2. Output characteristic of CE (Transistor characteristic)

$$i_C = f(v_{CE}) \mid i_B = \text{const}$$

Four regions for characteristic

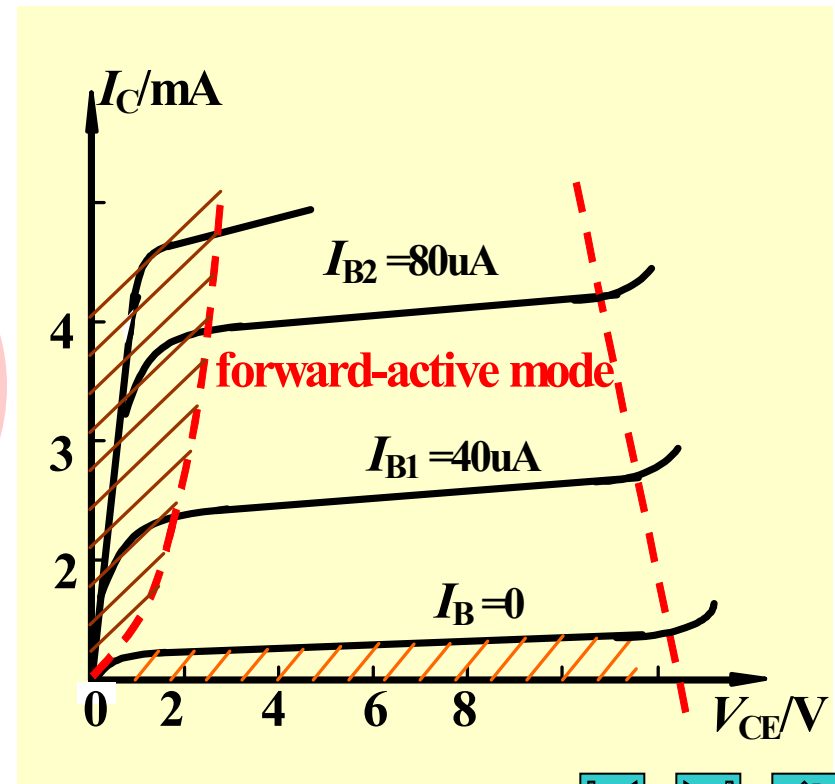**Forward-active mode:**  $i_C$  and  $i_B$  are related by  $i_C = \beta i_B$ . Curves are parallel and equidistance. **B-E is forward biased, B-C is reverse biased.**




# Modes of Operation

<b>Modes</b>	<b>EBJ</b>	<b>CBJ</b>
<b>Cutoff</b>	<b>Reverse</b>	<b>Reverse</b>
<b>Saturation</b>	<b>Forward</b>	<b>Forward</b>
<b>Active</b>	<b>Forward</b>	<b>Reverse</b>

## 5.1.5 Current-Voltage Characteristics

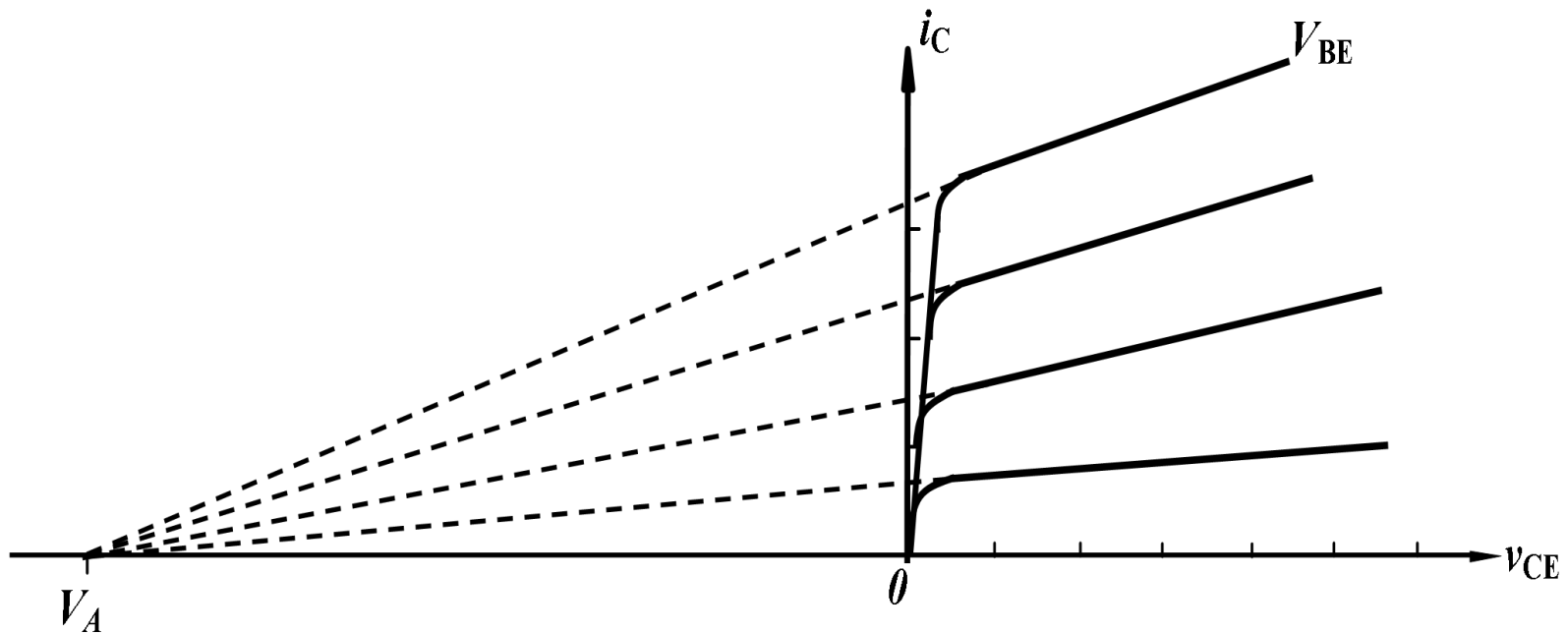
### 2. The output Characteristic of CE

Current-voltage characteristics for the common-emitter circuit, showing the Early voltage



## 5.1.5 Current-Voltage Characteristics




### 2. The output Characteristic of CE

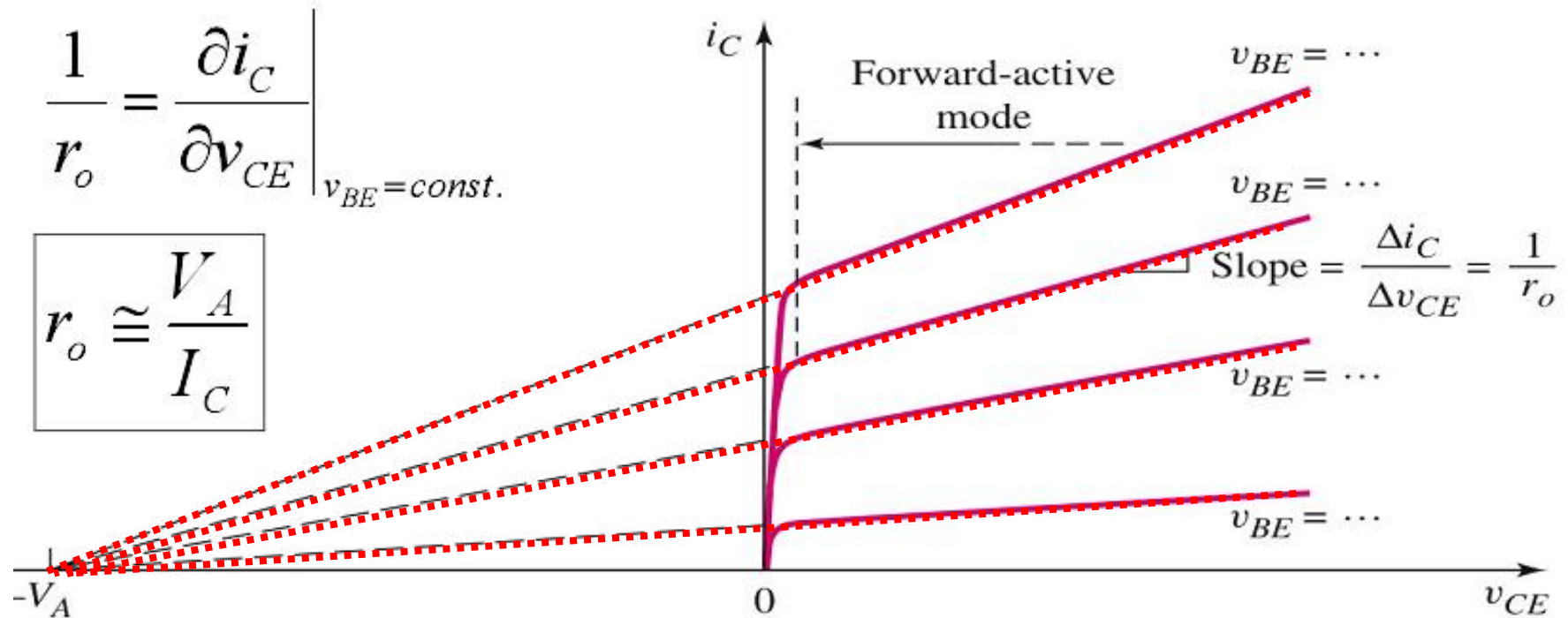

- $V_A$ : Early voltage : a point at negative voltage axis where all curves meet
- Nonzero slope: finite output resistance  $r_o$  looking into collector



# 5.1.5 Current-voltage Characteristics

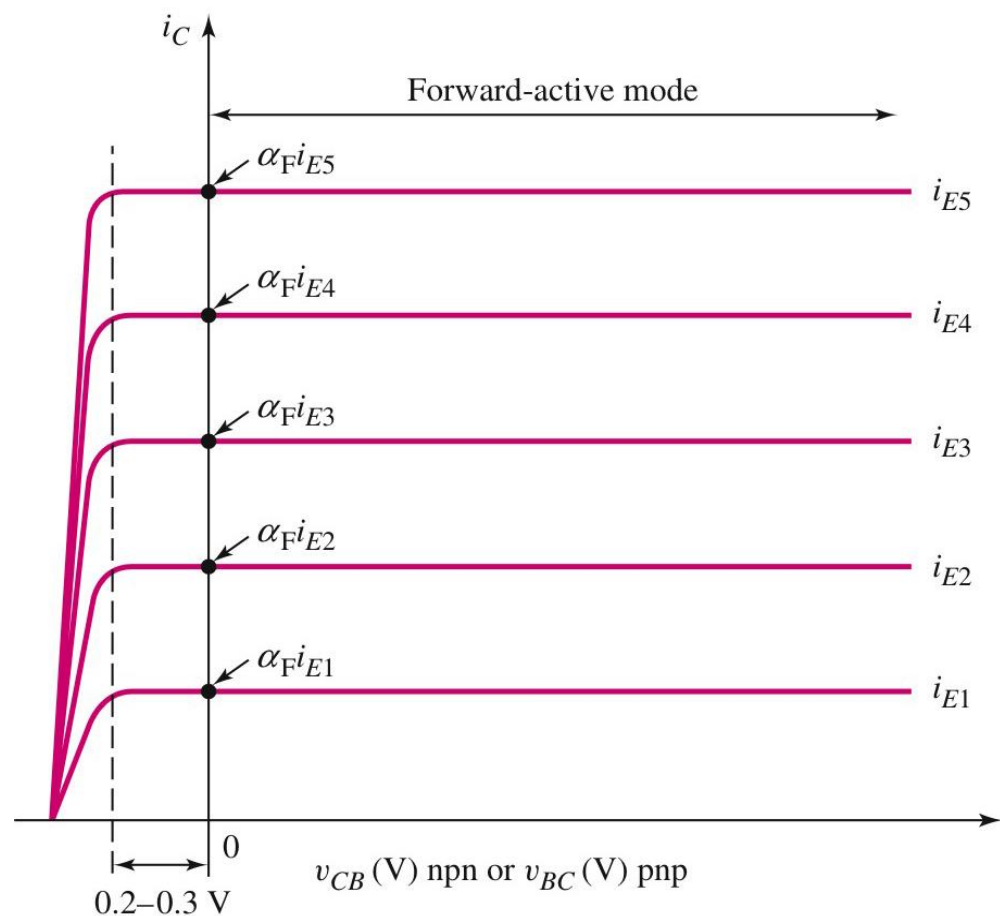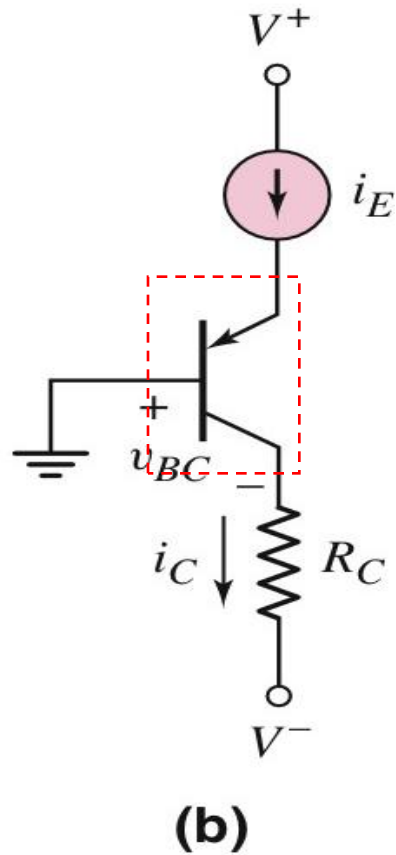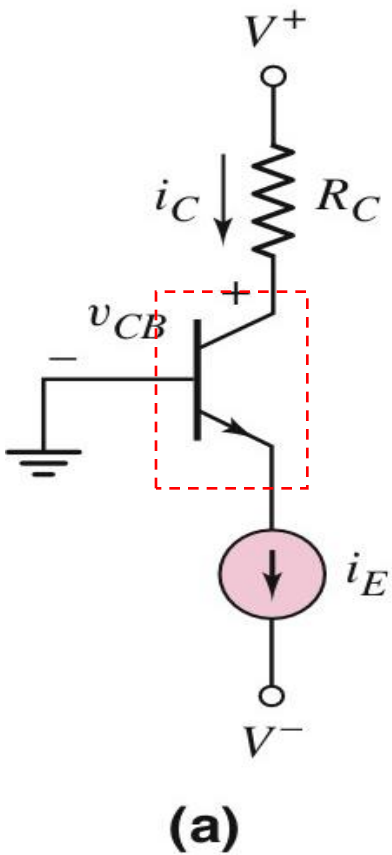

Common Base

Current-voltage Characteristics

### 1. Reverse-bias Leakage Currents


#### (1) Collector-base leakage current $I_{CBO}$

$I_{CBO}$  is the collector leakage current in common-base configuration, when the emitter is an open circuit.

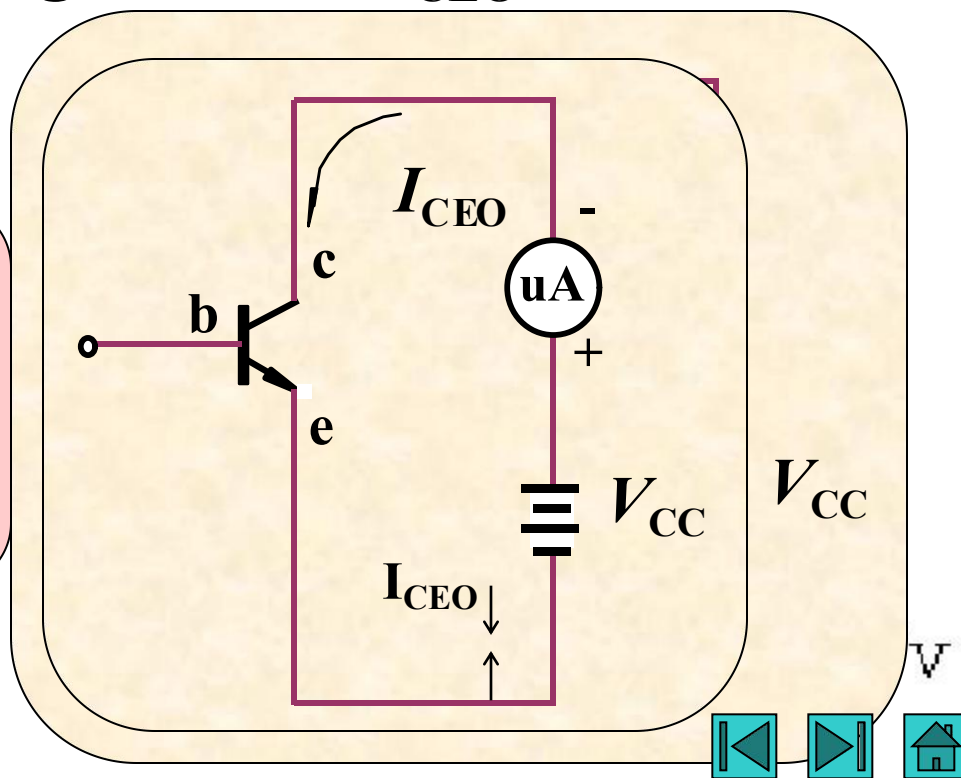
#### (2) Collector-emitter leakage current $I_{CEO}$

$$I_{CEO} = (1 + \beta_F) I_{CBO}$$

In most instances in this text, leakage will be completely negligible.


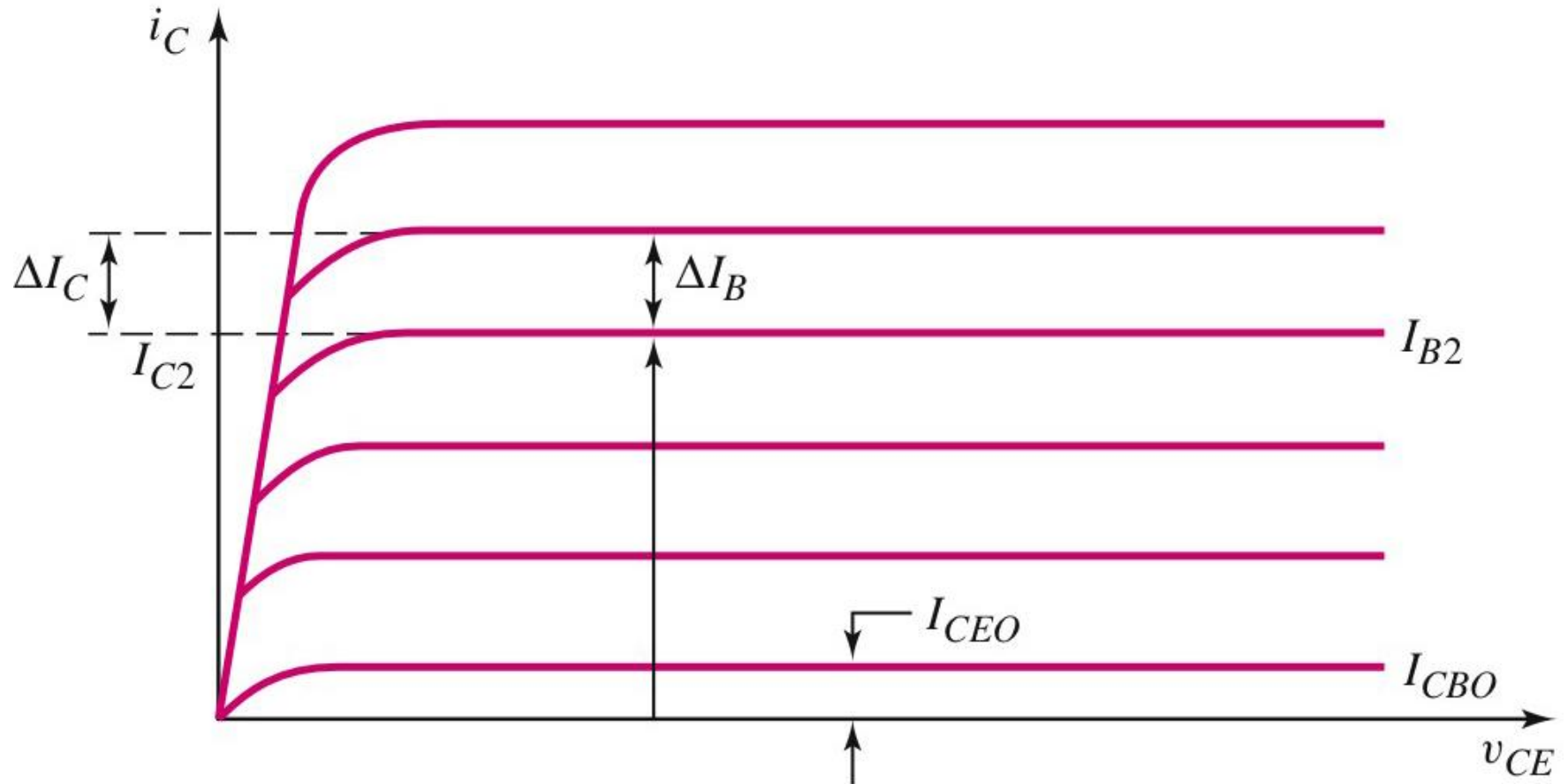
# Effects of Leakage Currents on I-V Characteristics



## 5.1.6 Nonideal Transistor Leakage Current and Breakdown Voltage

---

### 2. Breakdown Voltage

$BV_{CBO}$ ——Collector-base junction breakdown voltage in open-emitter configuration.

$BV_{CEO}$ ——Breakdown voltage between collector and emitter in open-base configuration.


$BV_{EBO}$ ——Base-emitter junction breakdown voltage in open-collector configuration.

$$V_{(BR)CBO} > V_{(BR)CEO} > V_{(BR)EBO}$$


- These will be a limiting factors in the size of the dc bias voltages which can be used.



# Review Questions

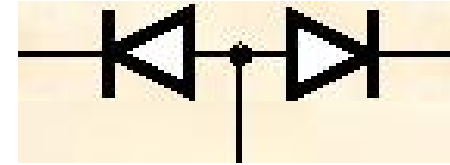

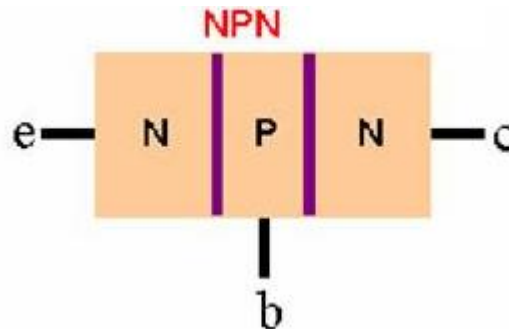- (1) Due to a BJT has two pn junction, can we conjoin two back-to-back diodes to be as a BJT? Why?
- (2) Can we exchange the emitter and collector terminals of a BJT, when we use it as a amplifying device?
- (3) Why we call a BJT as a current-controlled device?






# Review Questions

---

4. The voltage values for three terminals are given, determine the region which BJT operates in.

- (1)  $V_C=6V$  ,  $V_B=0.7V$  ,  $V_E=0V$  ,
- (2)  $V_C=6V$  ,  $V_B=6V$  ,  $V_E=5.4V$  ,
- (3)  $V_C=6V$  ,  $V_B=4V$  ,  $V_E=3.6V$  ,
- (4)  $V_C=3.6V$  ,  $V_B=4V$  ,  $V_E=3.4V$  ,

$$(1) V_C = 6V, V_B = 0.7V, V_E = 0V$$

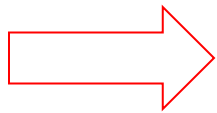


$$V_{BE} = 0.7V > V_{th} = 0.5V$$

$$V_{CE} = 6V$$

$$V_C > V_B > V_E$$

**Forward active region**

$$(2) V_C = 6V, V_B = 6V, V_E = 5.4V$$

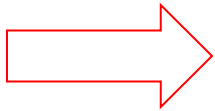

$$V_{BE} = 0.6V > V_{th} = 0.5V$$


$$V_{CE} = 0.6V$$

$$V_C = V_B > V_E$$

**Saturation Region**




$$(3) V_C = 6V, V_B = 4V, V_E = 3.6V$$

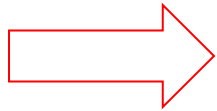

$$V_{BE} = 0.4V < 0.5V$$

**Cut off region**

$$4) V_C = 3.6V, V_B = 4V, V_E = 3.4V$$

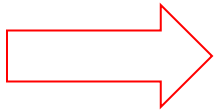

$$V_{BE} = 0.6V$$

$$V_{CE} = 0.2V$$

**Saturation Region**




## Review Questions

5. Assume  $I_1 = -1.2\text{mA}$ ,  $I_2 = -0.03\text{mA}$ ,  $I_3 = 1.23\text{mA}$ ,

(1) Determine ① is **C** , ② is **B** , ③ is **E** .

(2)  $\beta = ?$   **$1.2/0.03=40$**

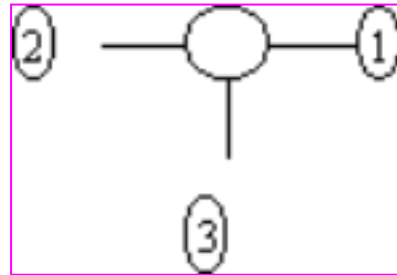




## Review Questions

6. In an amplifier, the voltage of the three **terminals** is  
0V, - 10V, -9.3V,  
Determine the BJT is NPN or PNP, is made of Si or Ge?

**Sol:**

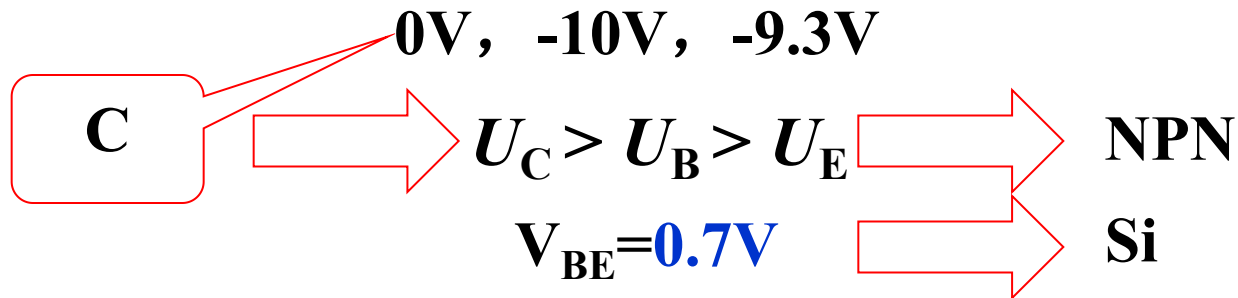

# Contents

## PART 1 SEMICONDUCTOR DEVICES AND BASIC APPLICATIONS

Chapter 1 Semiconductor Materials and Diodes

Chapter 2 Diode Circuits

Chapter 3 The Field-Effect Transistor

Chapter 4 Basic FET Amplifiers

 Chapter 5 The Bipolar Junction Transistor

Chapter 6 Basic BJT Amplifiers

Chapter 7 Frequency Response

Chapter 8 Output Stages and Power Amplifiers

## PART 2 ANALOG ELECTRONICS

Chapter 9 Ideal Operational Amplifiers and Op-Amp Circuits

Chapter 10 Integrated Circuit Biasing and Active Loads

Chapter 11 Differential and Multistage Amplifiers

Chapter 12 Feedback and Stability

Chapter 13 Operational Amplifier Circuits

Chapter 14 Nonideal Effects in Operational Amplifier Circuits

Chapter 15 Applications and Design of Integrated Circuits

# Ch5. The Bipolar Junction Transistor

---


## 5.1 Basic Bipolar Junction Transistor


## 5.2 DC Analysis of Transistor Circuits

## 5.3 Basic Transistor Application


## 5.4 Basic Transistor Biasing

## 5.5 Multistage Circuits

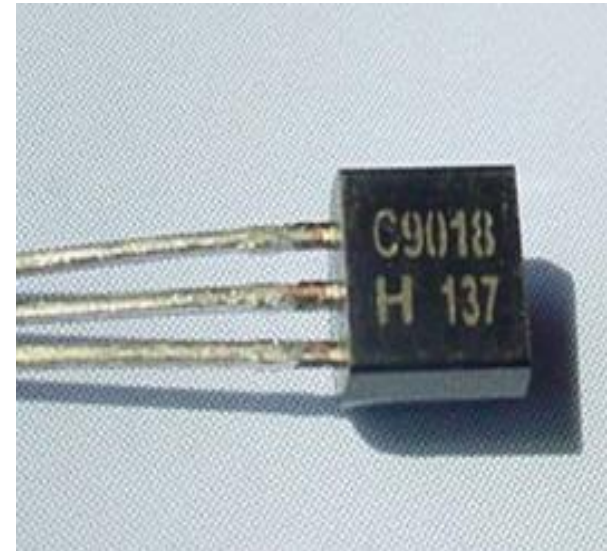


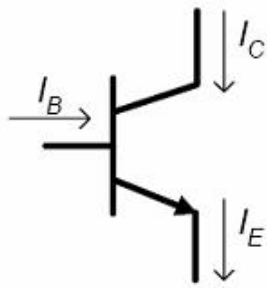

npn

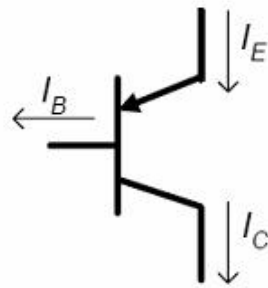

pnp



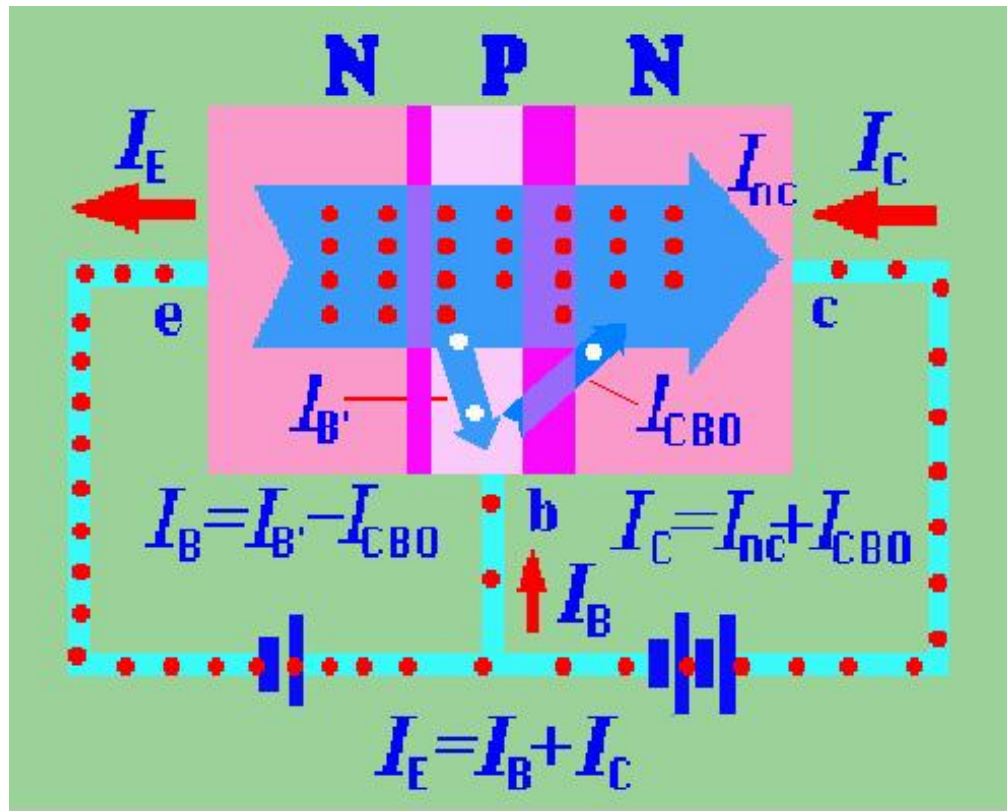


Transfer process of carriers

$$I_E = I_B + I_C$$

$$\alpha = \frac{I_C}{I_E}$$

$$\beta = \frac{I_C}{I_B}$$

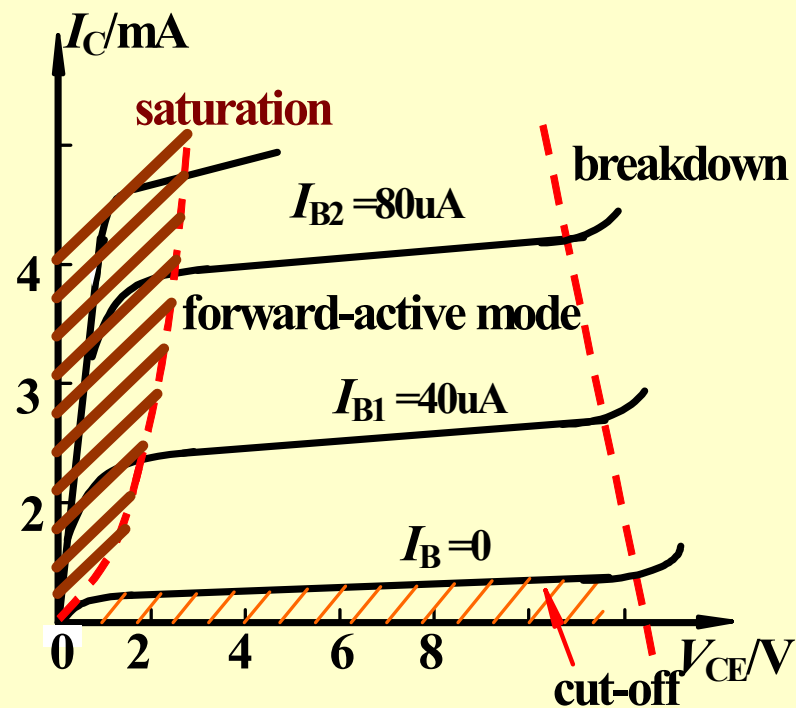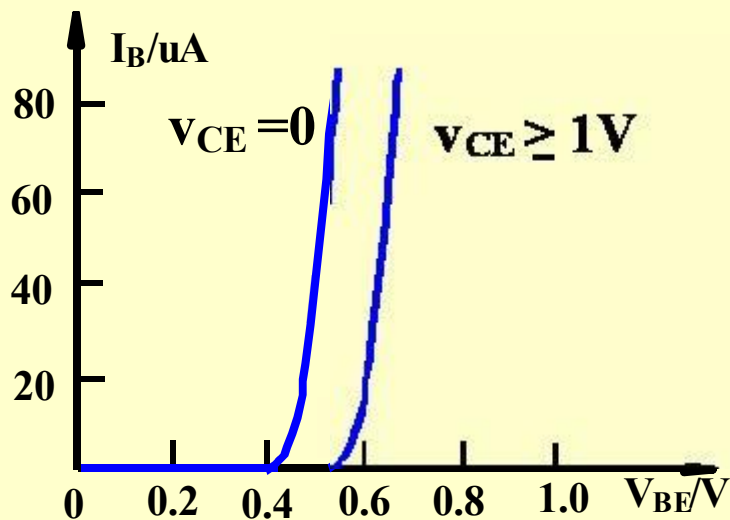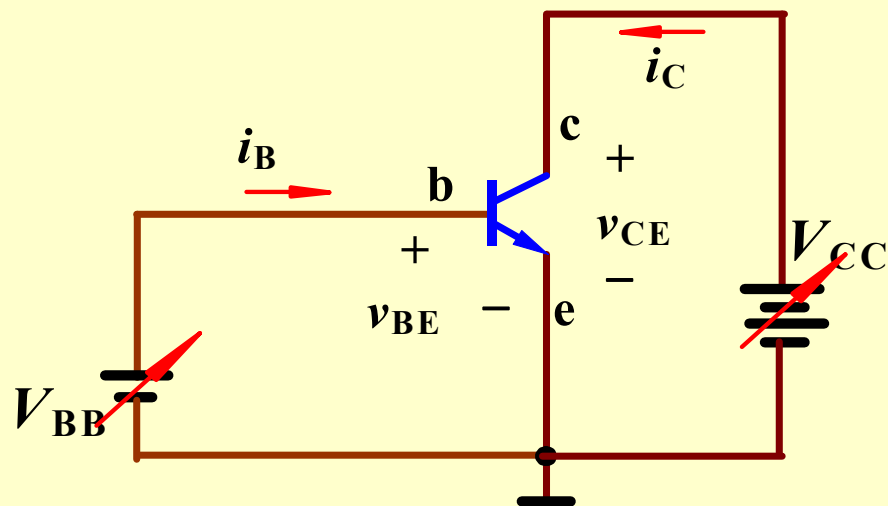



# Ch5. The Bipolar Junction Transistor

---

## 5.2 DC Analysis of Transistor Circuits(P303)

### 5.2.1 Common Emitter Circuit

### 5.2.2 Load Line and Modes of Operation


### 5.2.3 Voltage Transfer Characteristics

### 5.2.4 Commonly Used Bipolar Circuit : DC Analysis


## 5.2.1 Common Emitter Circuit

### DC Equivalent Circuit

Figure 5.19

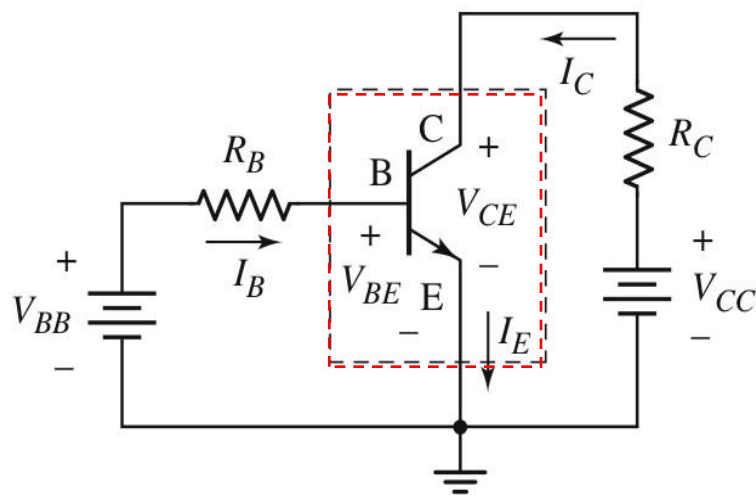

(a)

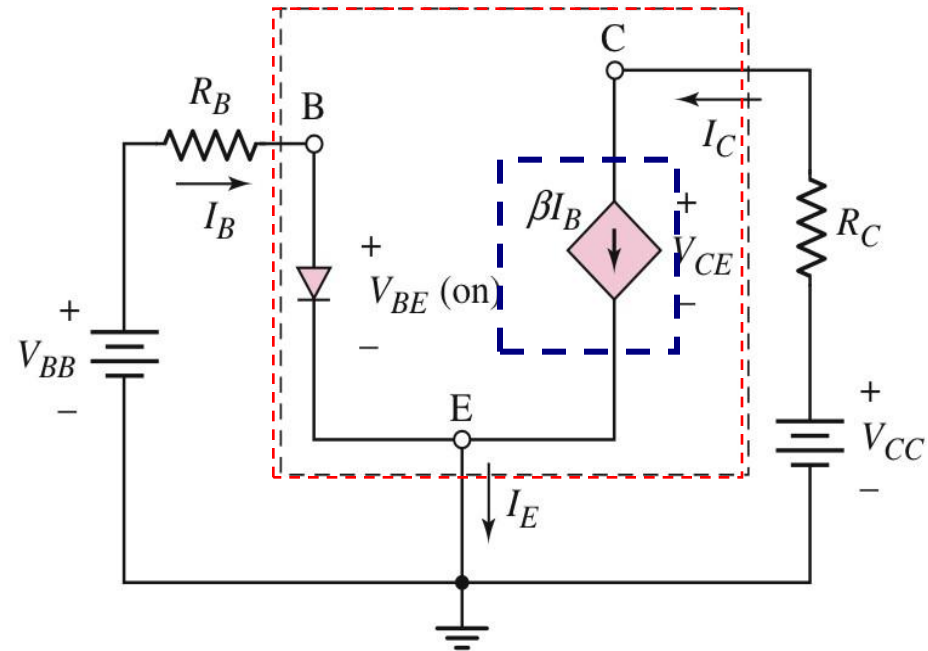

(b)

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.


Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

## Common Emitter Circuit


$$\beta I_B = I_C$$

## 5.2.1 Common Emitter Circuit

Figure 5.19

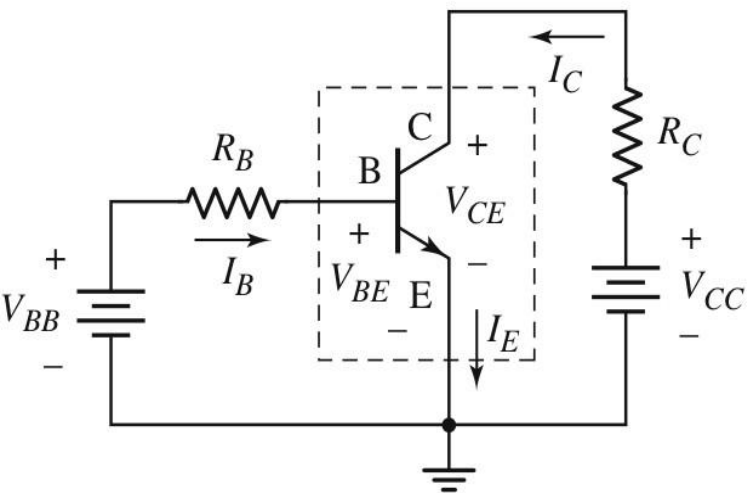

(a)

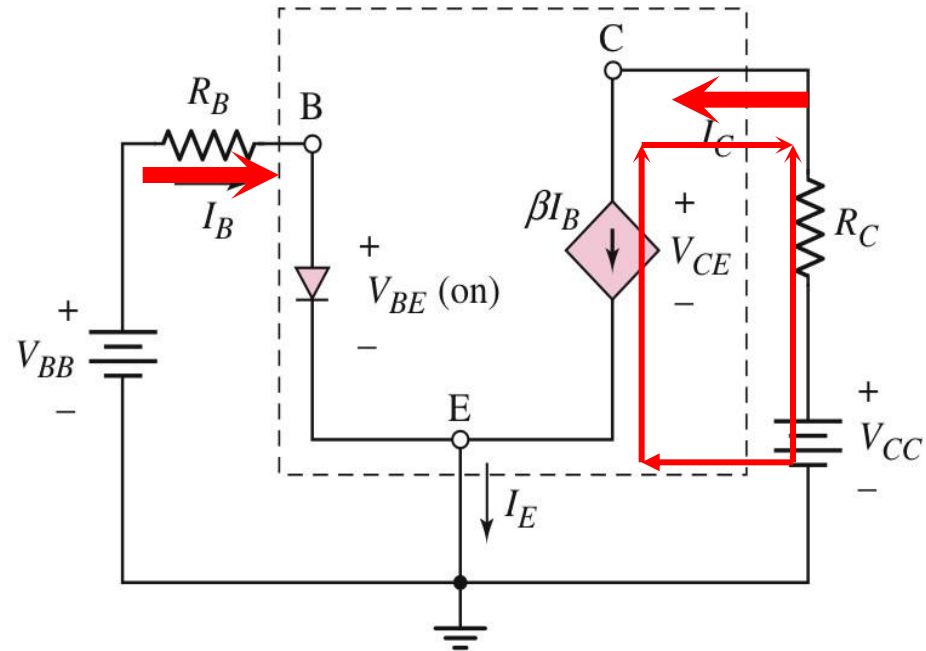

(b)

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.


$$I_B = \frac{V_{BB} - V_{BE(\text{on})}}{R_B}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

## 5.2.1 Common Emitter Circuit

Figure 5.20

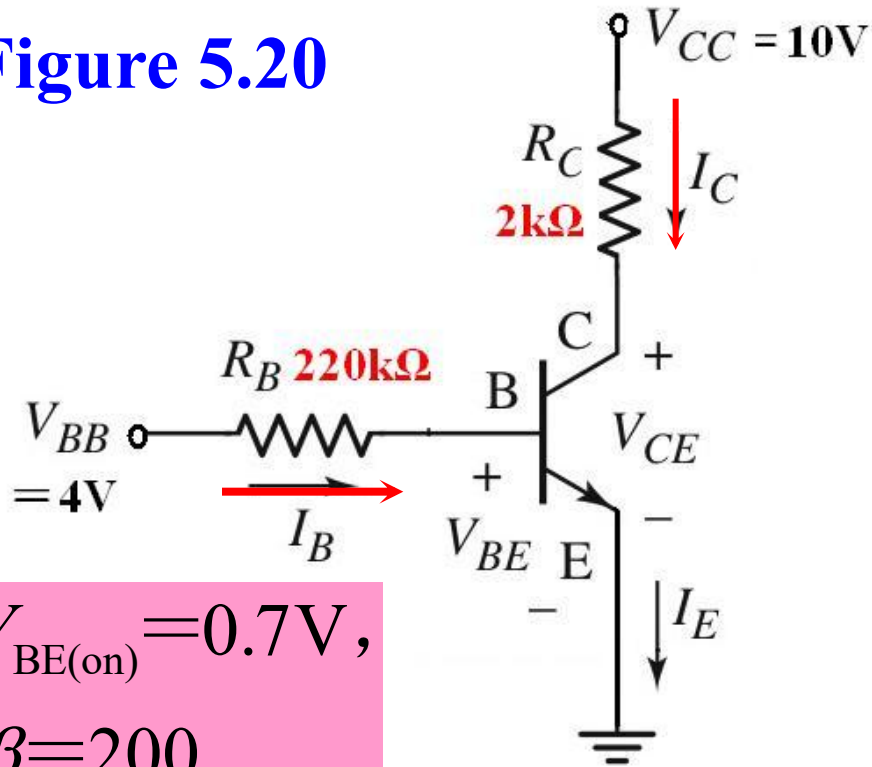

$$V_{BE(on)} = 0.7V,$$
$$\beta = 200$$

Calculate the Q-point ( $I_B$ ,  $I_C$ ,  $V_{CE}$ ).

Simulation

$$I_B = \frac{V_{BB} - V_{BE(on)}}{R_B}$$
$$= \frac{4 - 0.7}{220} = 15\mu A$$

$$I_C = \beta I_B$$

$$= 200 \cdot 15\mu A = 3mA$$


$$V_{CE} = V_{CC} - I_C R_C$$

$$= 10 - 3 \cdot 2$$

$$= 4V > 1V$$

# 5.2.1 Common Emitter Circuit

Figure 5.20

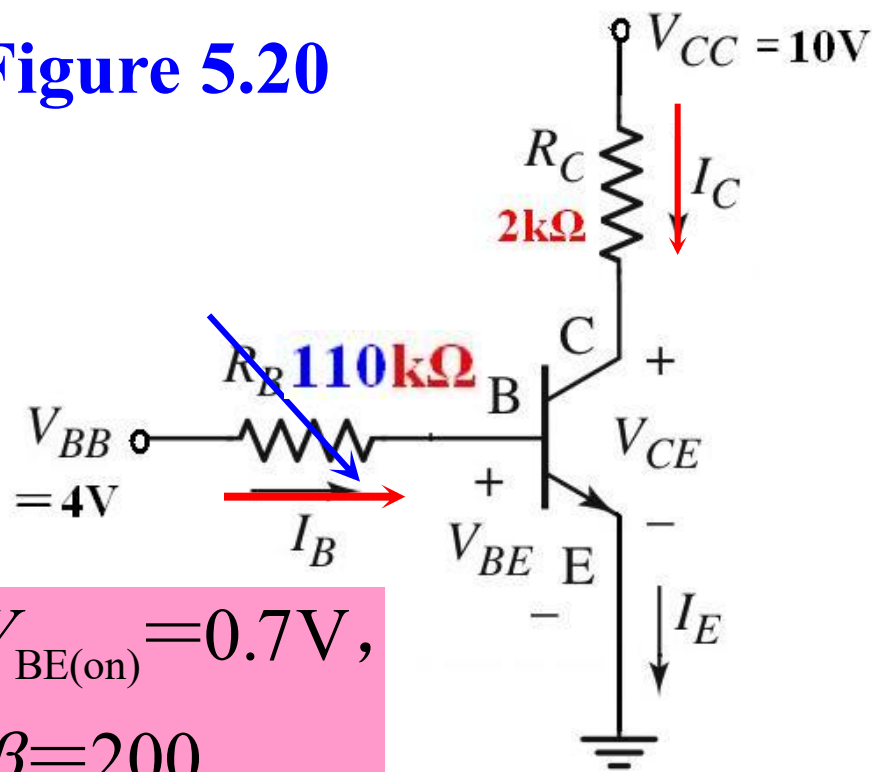

$V_{BE(on)} = 0.7V,$   
 $\beta = 200$

Calculate the Q-point ( $I_B, I_C, V_{CE}$ ).

$$I_B = \frac{V_{BB} - V_{BE(on)}}{R_B}$$
$$= \frac{4 - 0.7}{110} = 30\mu A$$

~~$I_C = \beta I_B$~~


$$= 200 \cdot 30\mu A = 6mA$$

$$V_{CE} = V_{CC} - I_C R_C$$
$$= 10 - 6 \cdot 2$$
$$= -2V$$




## 5.2.1 Common Emitter Circuit

Figure 5.21

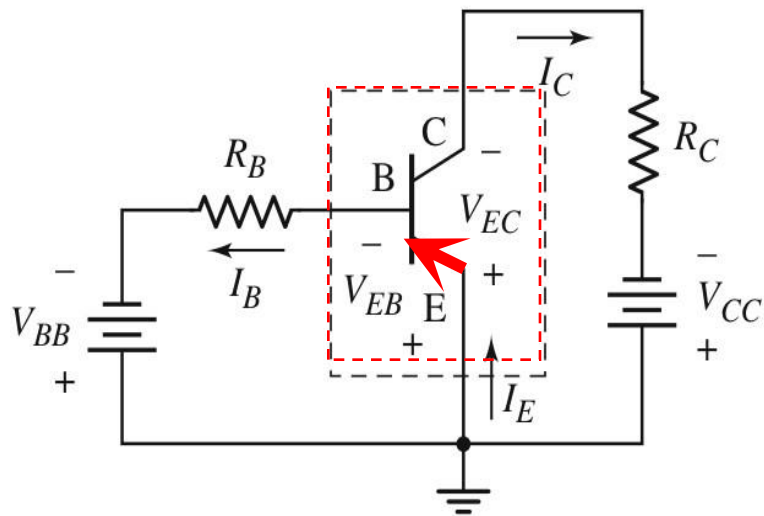

(a)

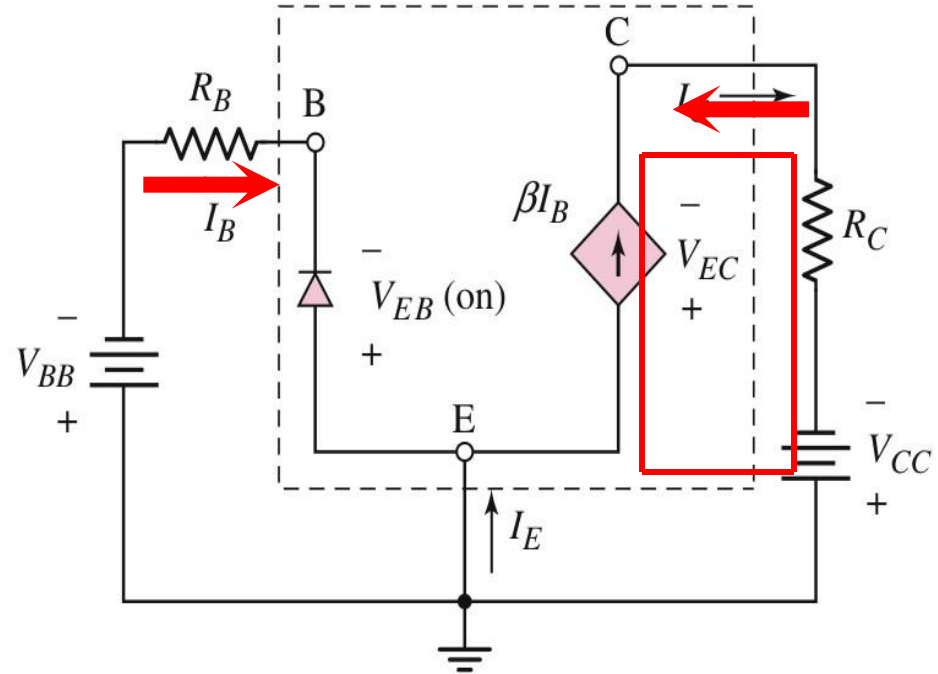

(b)


$$I_B = \frac{V_{BB} - V_{EB(\text{on})}}{R_B}$$

$$I_C = \beta I_B$$

$$V_{EC} = V_{CC} - I_C R_C$$

## 5.2.1 Common Emitter Circuit

Figure 5.22

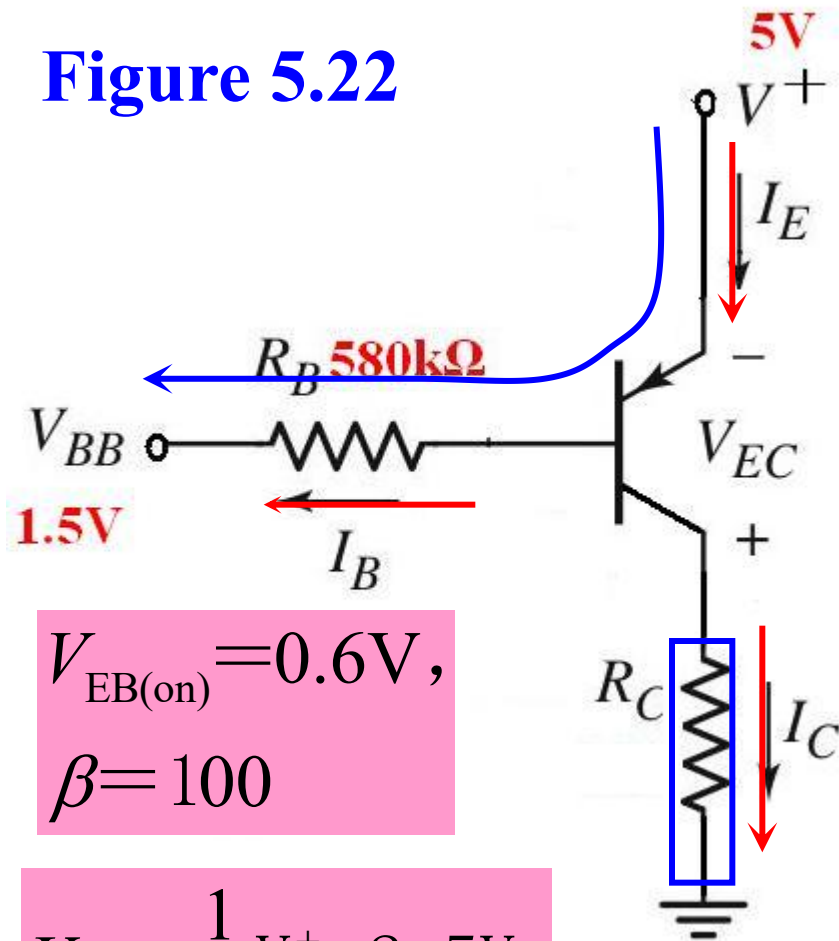

$$V_{EB(on)} = 0.6V,$$
$$\beta = 100$$

$$V_{EC} = \frac{1}{2} V^+ = 2.5V,$$

Find  $I_B$ ,  $I_C$ ,  $I_E$ ,  $R_C$ .

$$I_B = \frac{V^+ - V_{EB(on)} - V_{BB}}{R_B}$$
$$= \frac{5 - 0.6 - 1.5}{580} = 5\mu A$$


$$I_C = \beta I_B = 0.5mA$$

$$I_E = (1 + \beta) I_B$$
$$= 0.505mA$$

$$R_C = \frac{V^+ - V_{EC}}{I_C} = \frac{5 - 2.5}{0.5} = 5k\Omega$$

## 5.2.1 Common Emitter Circuit

Figure 5.20

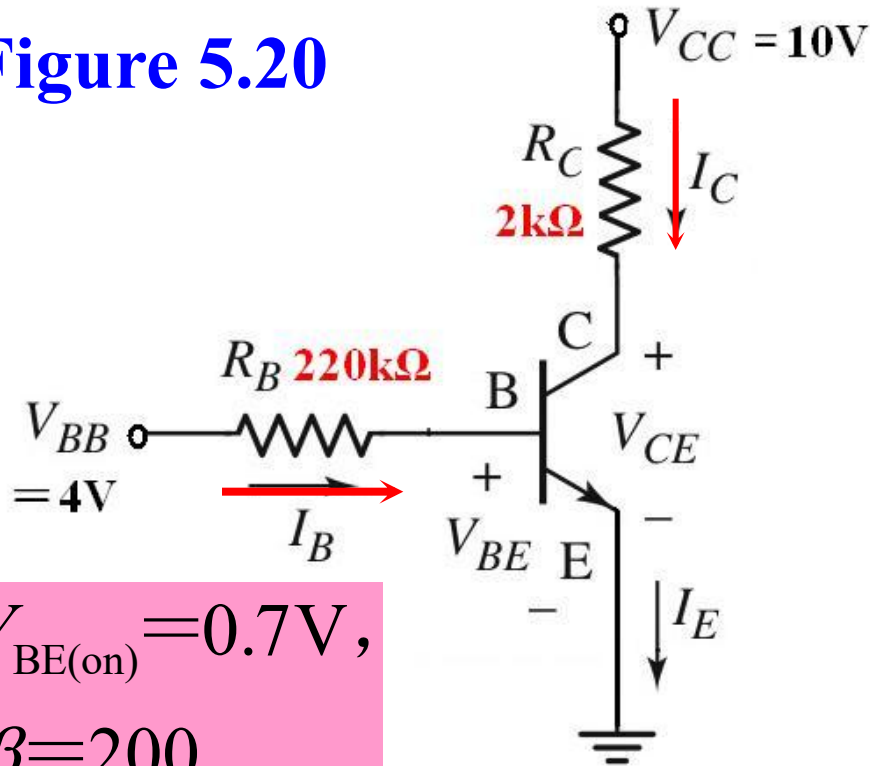

$$V_{BE(on)} = 0.7V,$$
$$\beta = 200$$

Calculate the Q-point ( $I_B, I_C, V_{CE}$ ).

$$I_B = \frac{V_{BB} - V_{BE(on)}}{R_B}$$
$$= \frac{4 - 0.7}{220} = 15\mu A$$

$$I_C = \beta I_B$$


$$= 200 \cdot 15\mu A = 3mA$$

$$V_{CE} = V_{CC} - I_C R_C$$
$$= 10 - 3 \cdot 2$$
$$= 4V$$




## 5.2.2 Load Line and Modes of Operation

Figure 5.20

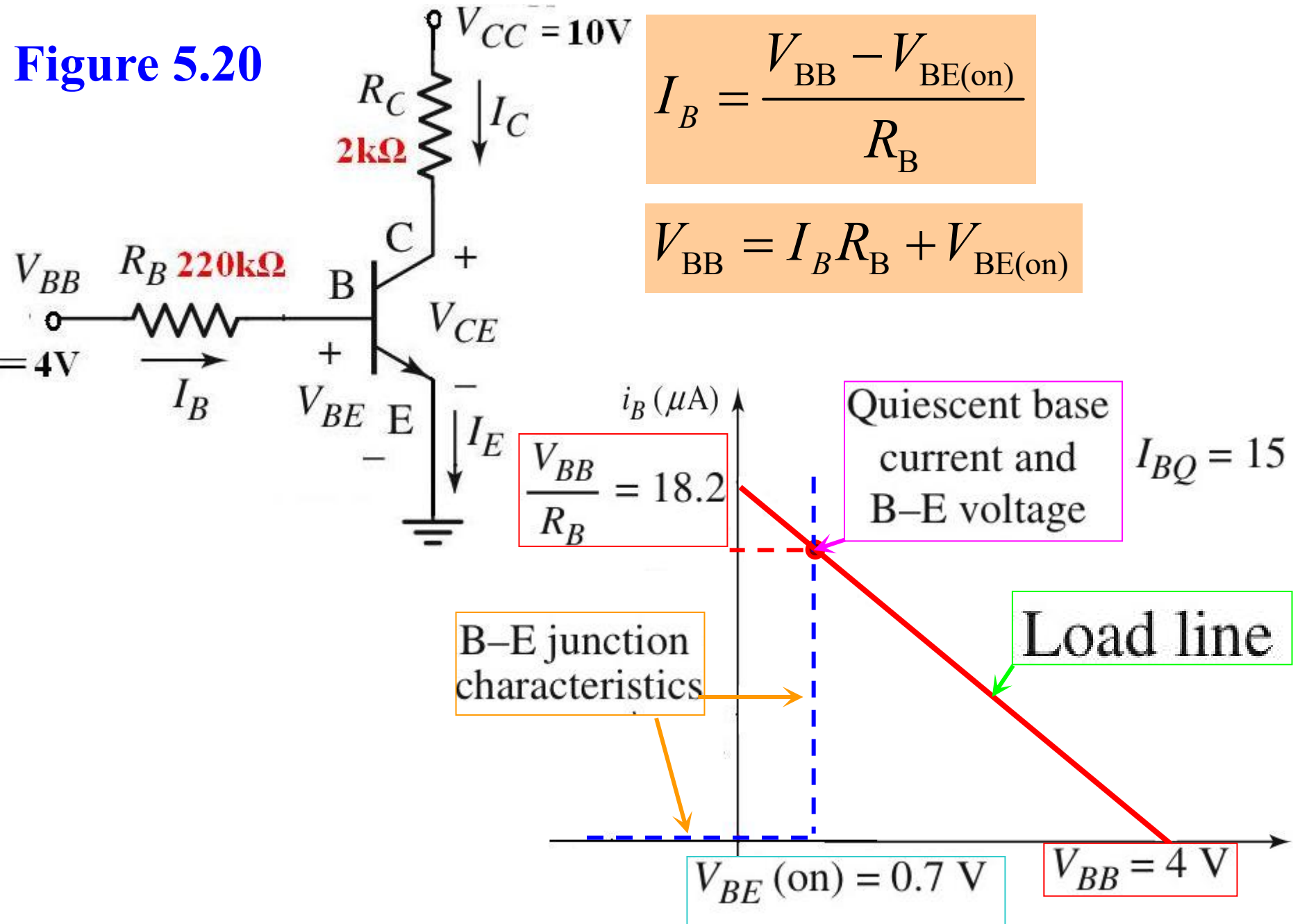


## 5.2.2 Load Line and Modes of Operation

Figure 5.20


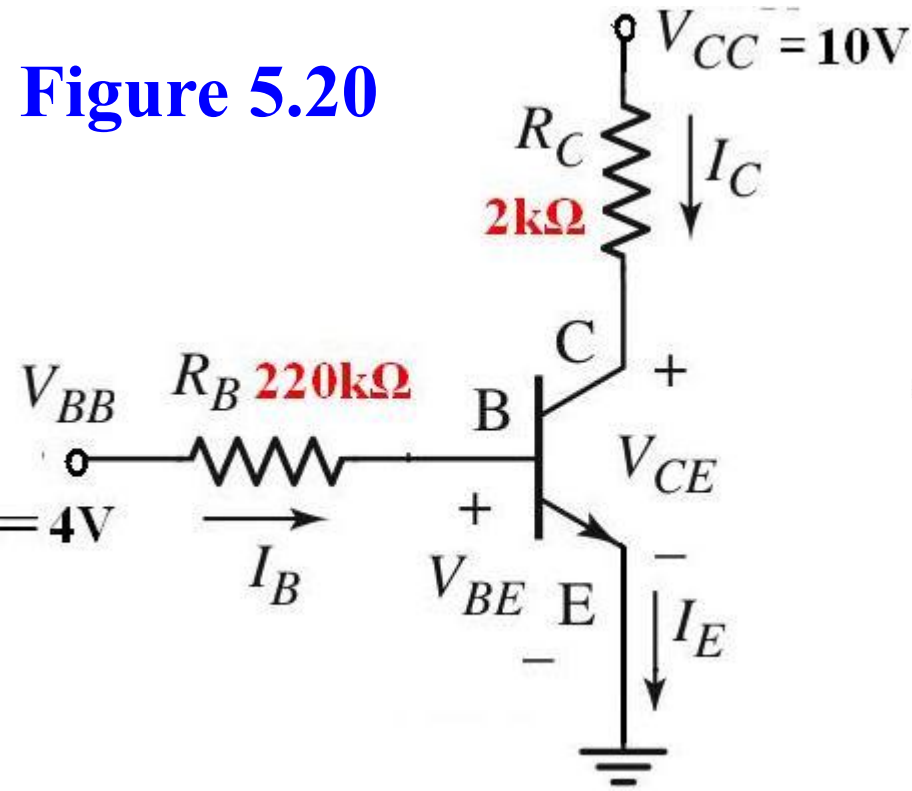


$$V_{CE} = V_{CC} - I_C R_C$$

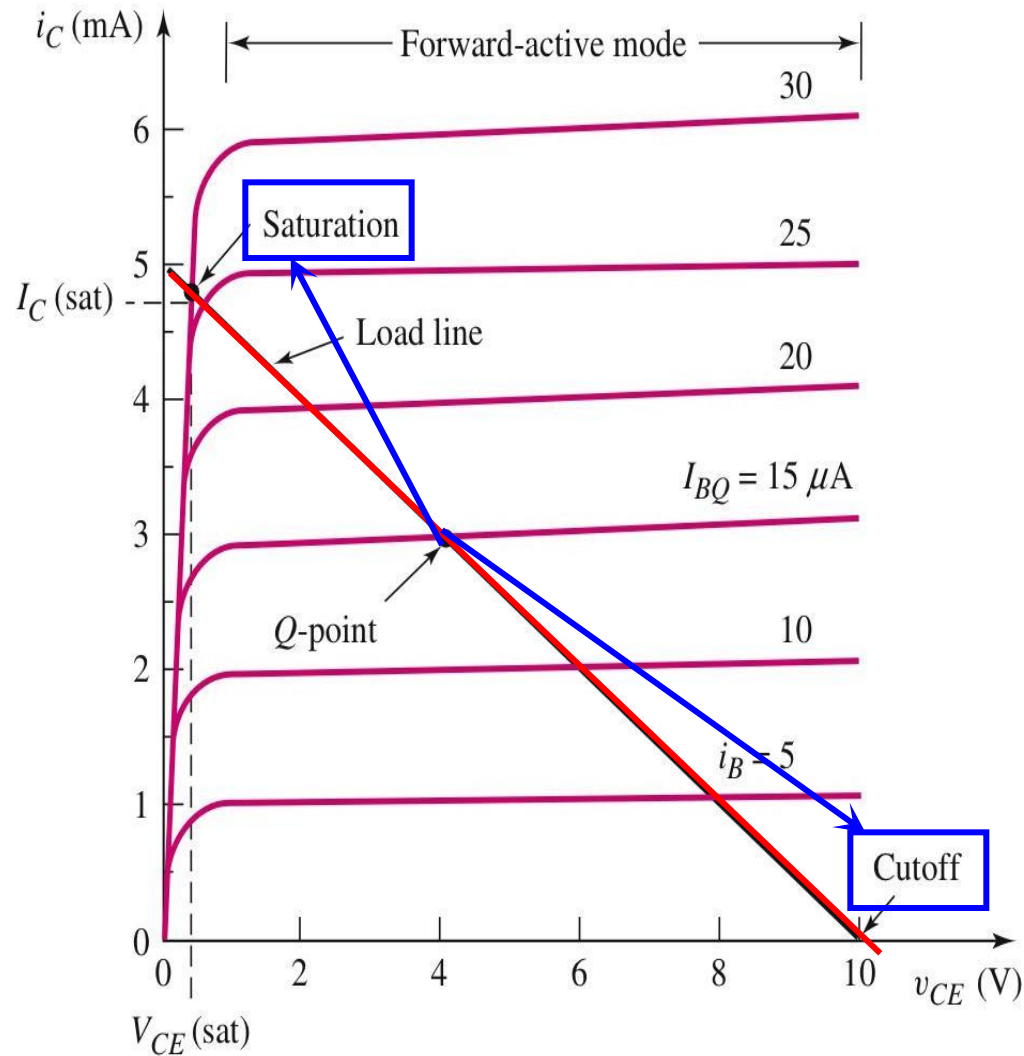


(b)
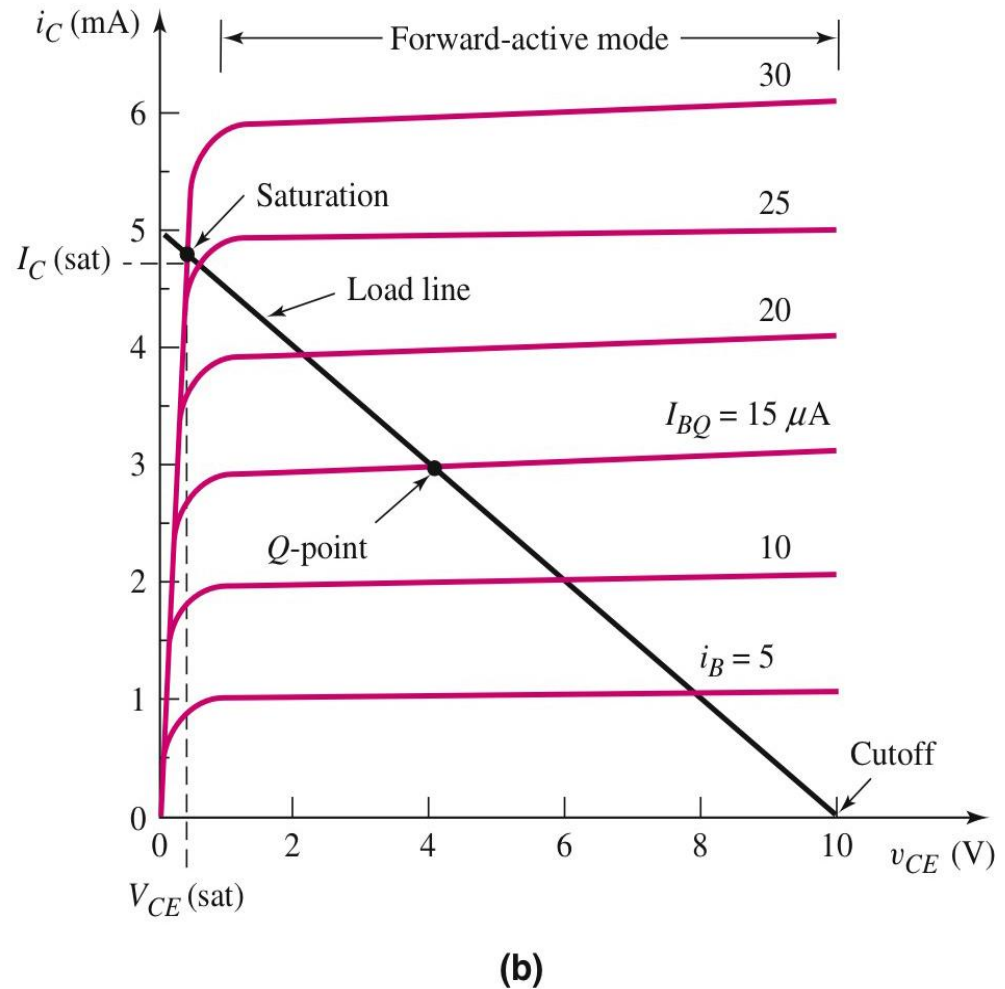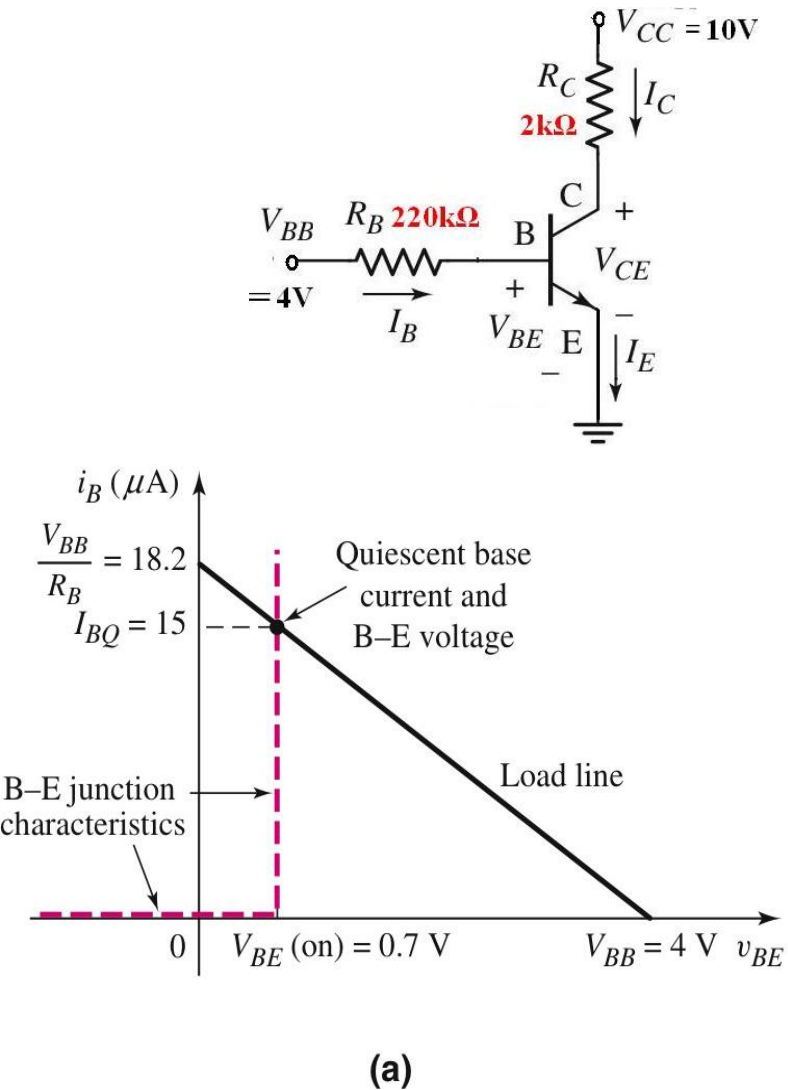
## 5.2.2 Load Line and Modes of Operation


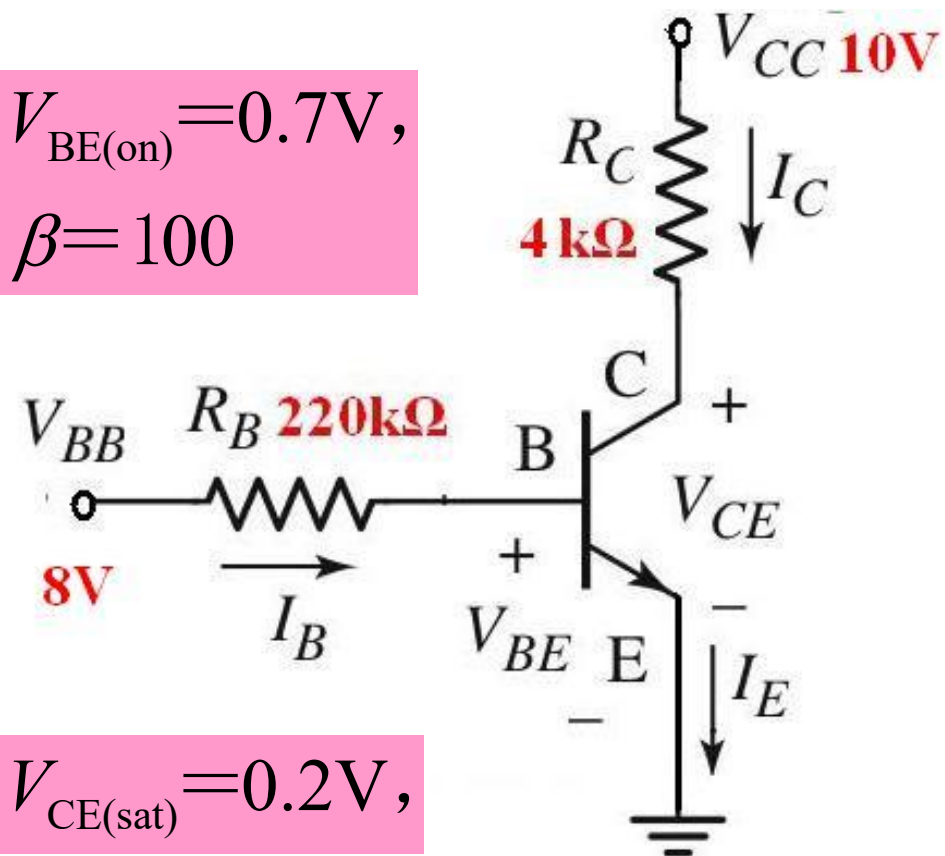
## 5.2.2 Load Line and Modes of Operation



$$I_B = \frac{V_{BB} - V_{BE(on)}}{R_B}$$
$$= \frac{8 - 0.7}{220} = 33.2 \mu A$$

$$I_C = \beta I_B$$

$$= 100 \cdot 33.2 \mu A = 3.32 \text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$= 10 - 3.32 \cdot 4 = -3.28 \text{ V}$$


**When the transistor is in the Saturation region, calculate the currents and voltages.**

$$I_C = \frac{V_{CC} - V_{CE(sat)}}{R_C} = \frac{10 - 0.2}{4} = 2.45 \text{ mA}$$

# Problem-Solving Technique: Bipolar DC Analysis

1. Assume that the transistor is biased in forward active mode
  - a.  $V_{BE} = V_{BE}(\text{on})$ ,  $I_B > 0$ , &  $I_C = \beta I_B$
2. Analyze 'linear' circuit.
3. Evaluate the resulting state of transistor.
  - a. If  $V_{CE} > V_{CE}(\text{sat})$ , assumption is correct
  - b. If  $I_B < 0$ , transistor likely in cutoff
  - c. If  $V_{CE} < 0$ , transistor likely in saturation
4. If initial assumption is incorrect, make new assumption and return to Step 2.
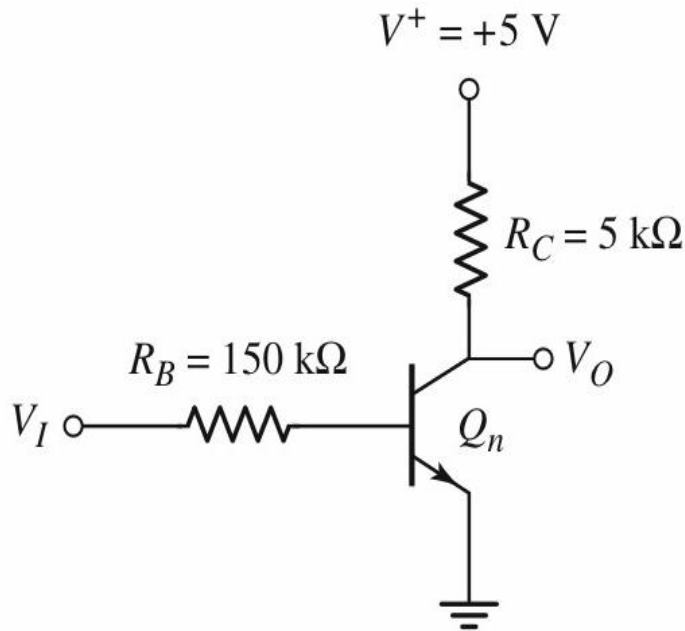
# Voltage Transfer Characteristic for npn Circuit



(a)

$$V_I \leq 0.7V$$

Which region?      Cut off

$$I_B = I_C = 0 \quad V_O = ? \quad V_O = V^+ = 5V$$

$$V_I > 0.7V$$

Which region?      Forward active or  
Saturation region

Forward active region

$$I_B = \frac{V_I - 0.7}{R_B}$$

$$I_C = \beta I_B$$


$$V_O = 5 - I_C R_C$$

# Voltage Transfer Characteristic for npn Circuit

Forward active region

$$I_B = \frac{V_I - 0.7}{R_B}$$

$$I_C = \beta I_B$$

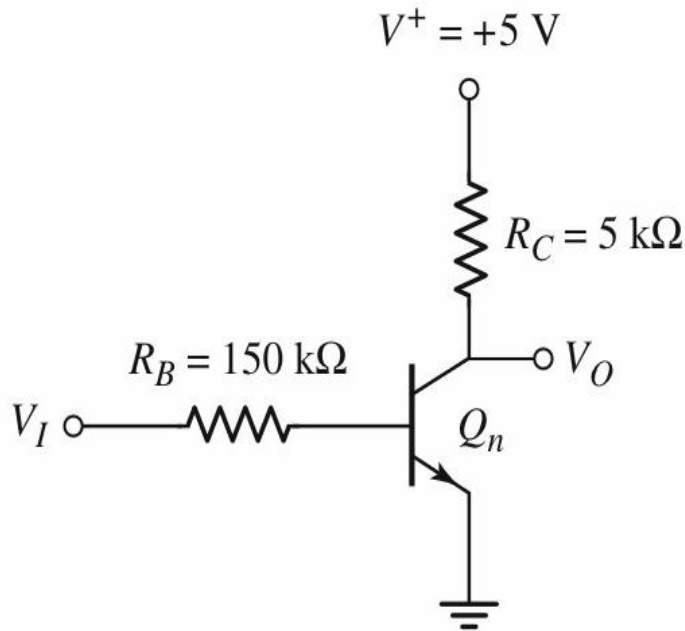


(a)

$$V_O = 5 - I_C R_C$$

$$= 5 - \frac{\beta(V_I - 0.7)R_C}{R_B}$$

$$0.2 \leq V_O \leq 5V$$
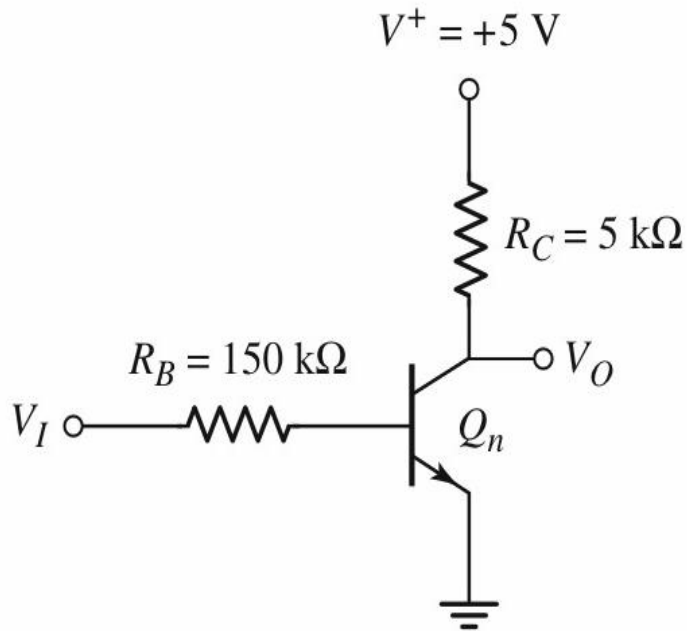
# Voltage Transfer Characteristic for npn Circuit



(a)

$$V_O = 0.2 \text{ V}$$

Which region?

**Saturation region**


$$V_I = ? \quad V_O = 5 - \frac{\beta(V_I - 0.7)R_C}{R_B} = 0.2$$

$$V_I = 1.9 \text{ V}$$

$V_I \geq 1.9 \text{ V}$       **Saturation region**


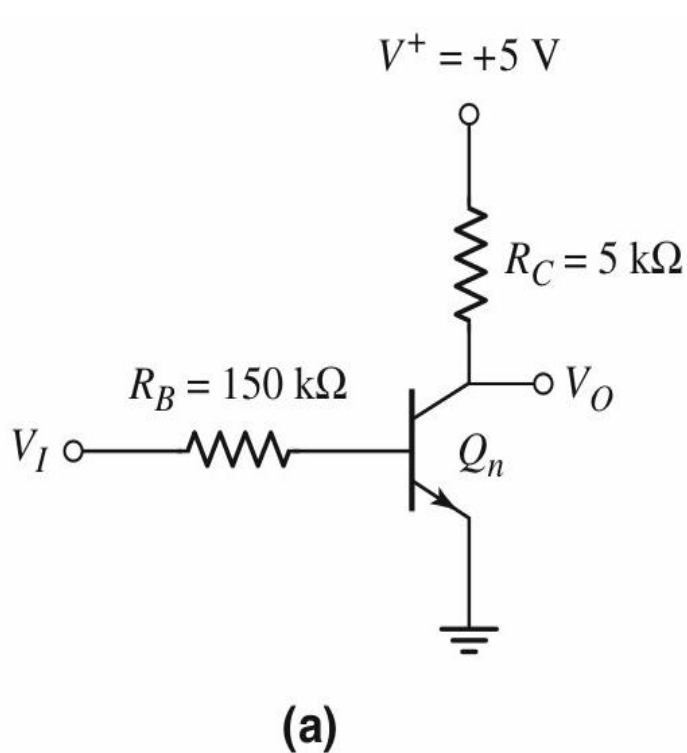
# Voltage Transfer Characteristic for npn Circuit



$$V_I \leq 0.7\text{ V}$$


$$V_O = V^+ = 5\text{ V}$$

$$V_I \geq 1.9\text{ V}$$


$$V_O = 0.2\text{ V}$$

$$0.7\text{ V} < V_I < 1.9\text{ V}$$

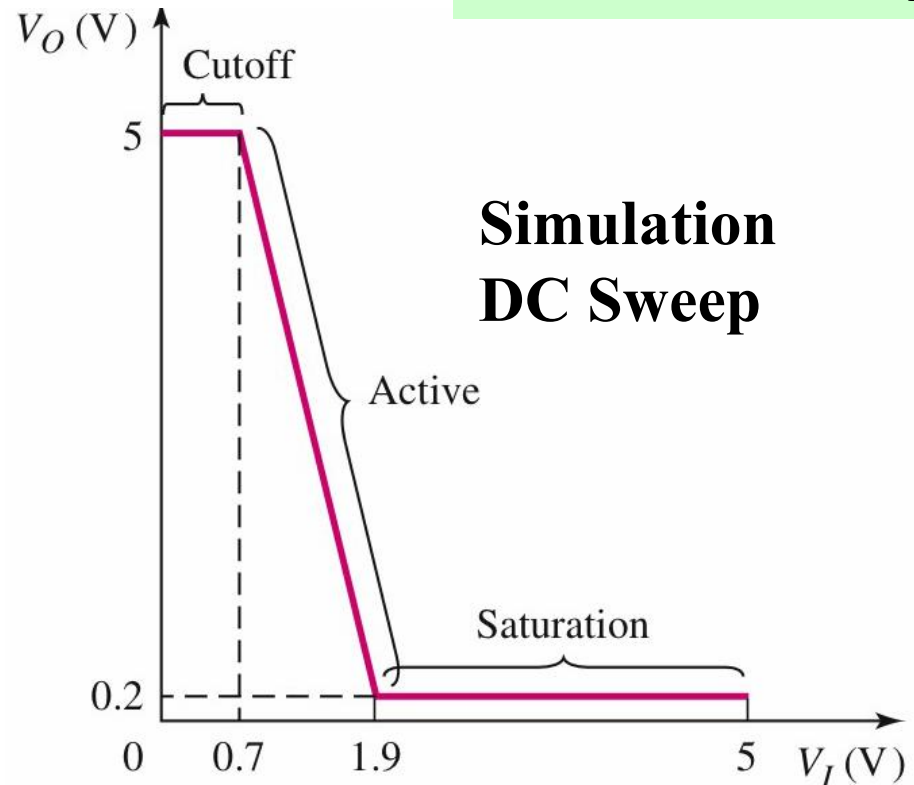
$$V_O = 5 - \frac{\beta(V_I - 0.7)R_C}{R_B}$$



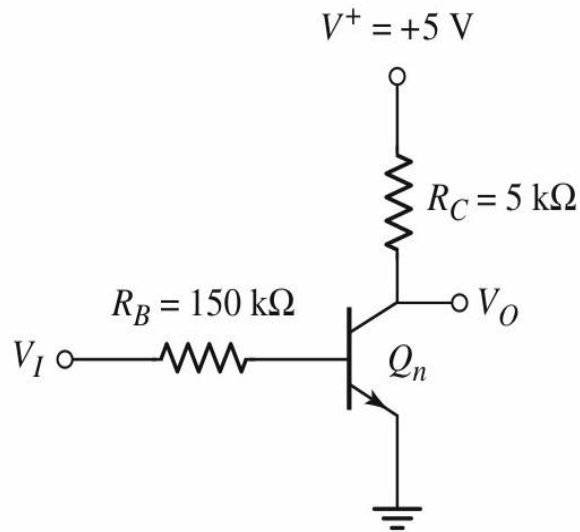
# Voltage Transfer Characteristic for npn Circuit



(a)

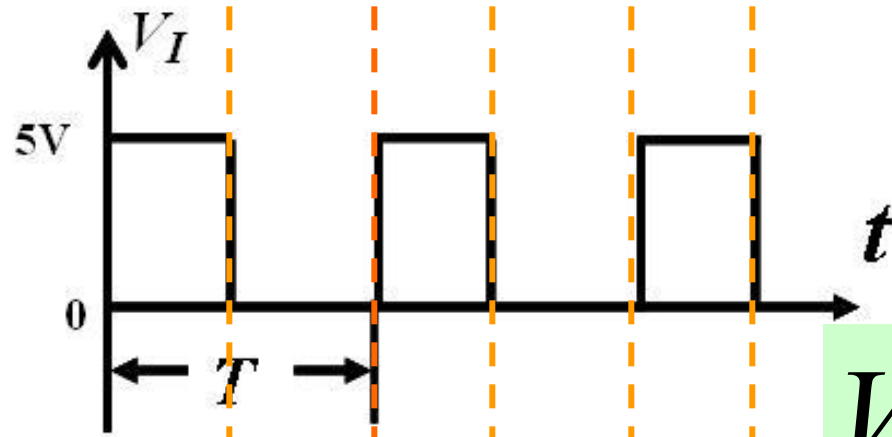


$V_O = ?$


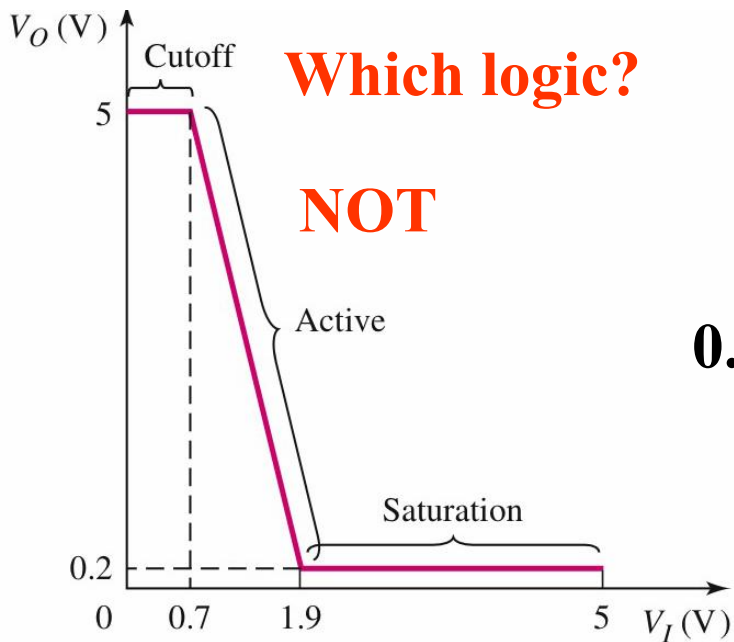


Which logic?

NOT

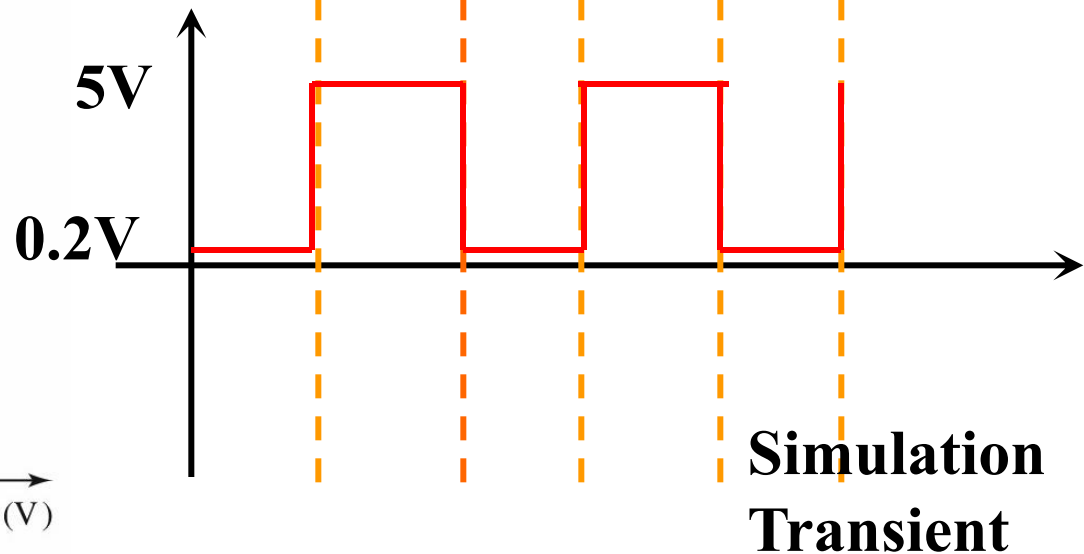

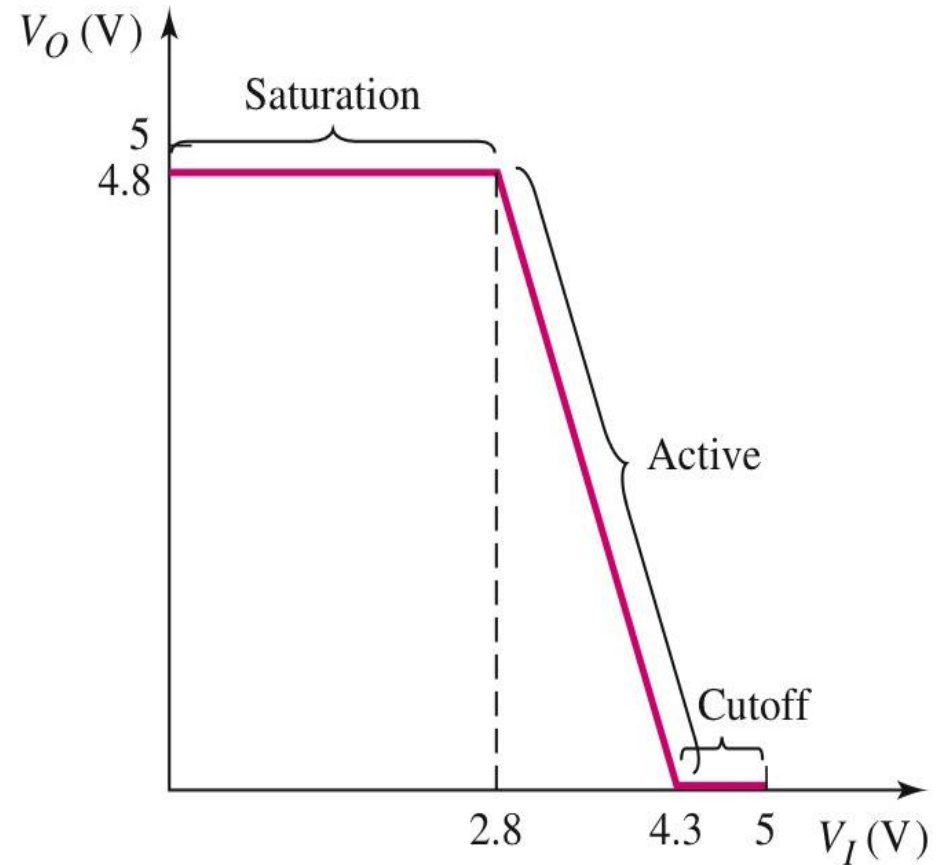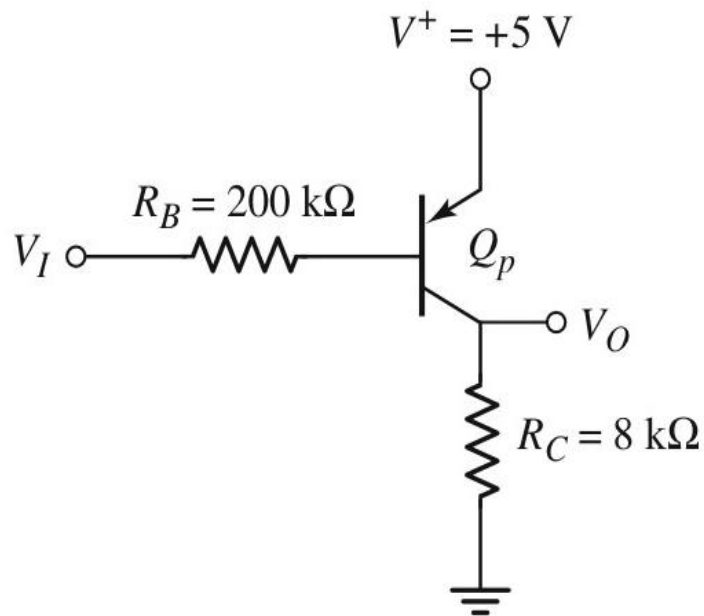
# Voltage Transfer Characteristic for pnp Circuit





# Review Questions

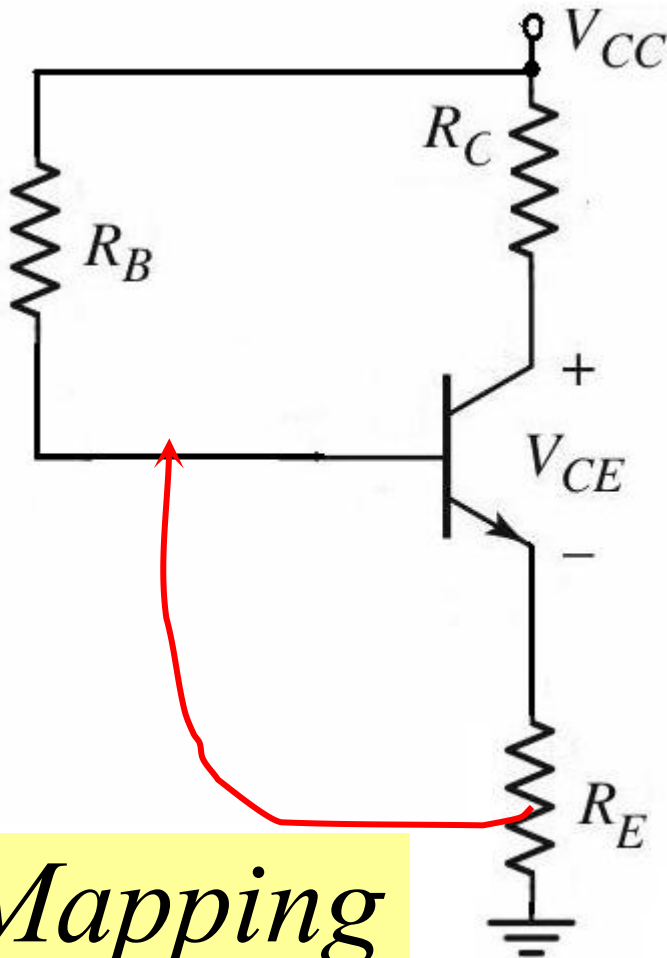

$$I_B = \frac{V_{BB} - V_{BE(on)}}{R_B + (1 + \beta)R_E}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

*Mapping*

Calculate the Q-point ( $I_B$ ,  $I_C$ ,  $V_{CE}$ ).

# Contents

## PART 1 SEMICONDUCTOR DEVICES AND BASIC APPLICATIONS

Chapter 1 Semiconductor Materials and Diodes

Chapter 2 Diode Circuits

Chapter 3 The Field-Effect Transistor

Chapter 4 Basic FET Amplifiers

 Chapter 5 The Bipolar Junction Transistor

Chapter 6 Basic BJT Amplifiers

Chapter 7 Frequency Response

Chapter 8 Output Stages and Power Amplifiers

## PART 2 ANALOG ELECTRONICS

Chapter 9 Ideal Operational Amplifiers and Op-Amp Circuits

Chapter 10 Integrated Circuit Biasing and Active Loads

Chapter 11 Differential and Multistage Amplifiers

Chapter 12 Feedback and Stability

Chapter 13 Operational Amplifier Circuits

Chapter 14 Nonideal Effects in Operational Amplifier Circuits

Chapter 15 Applications and Design of Integrated Circuits

# Ch5. The Bipolar Junction Transistor

---


## 5.1 Basic Bipolar Junction Transistor

## 5.2 DC Analysis of Transistor Circuits

## 5.3 Basic Transistor Application



## 5.4 Basic Transistor Biasing

## 5.5 Multistage Circuits

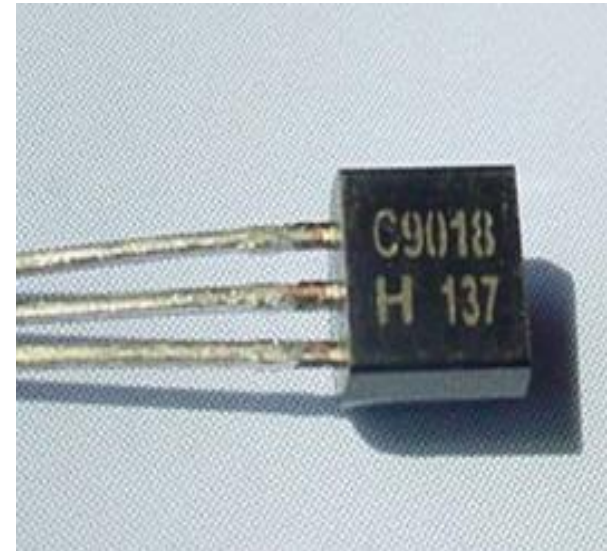

## 5.3.1

## Switch

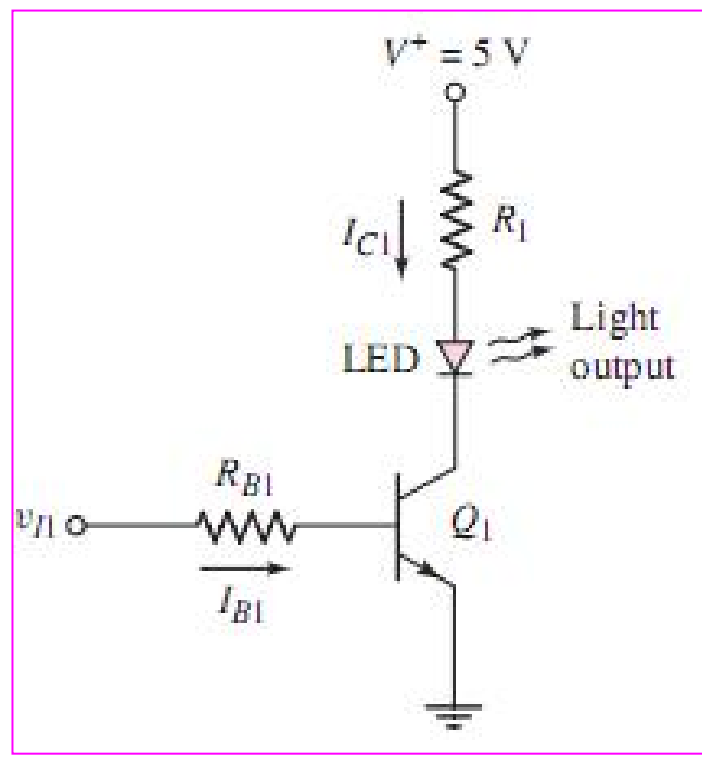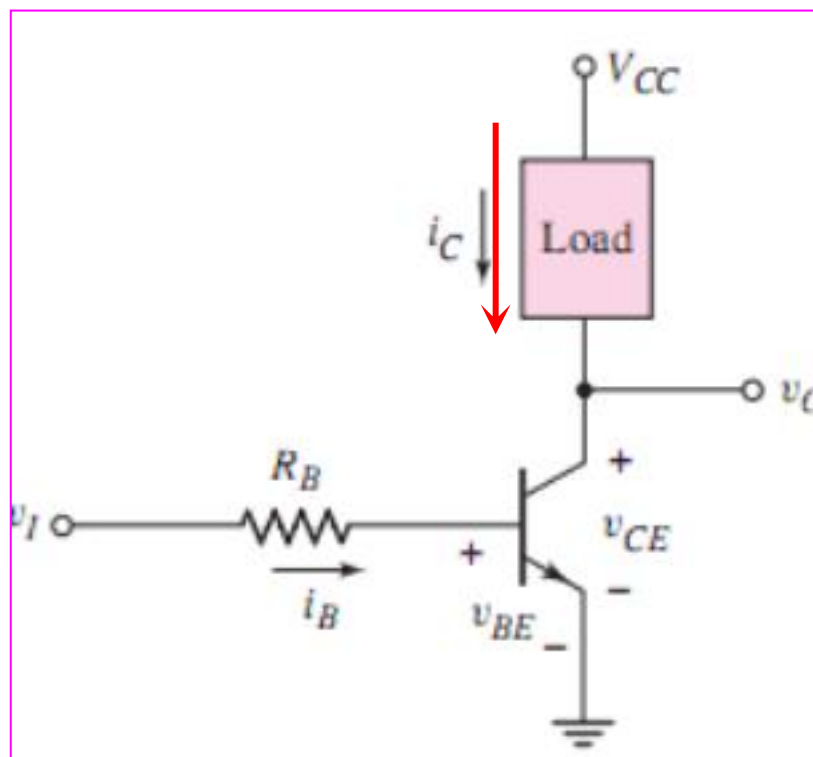


If  $v_I < V_{BE}(\text{on})$  the transistor is cut off  $i_B = i_C = 0$   
 $v_O = V_{CC}$

---


$v_I = V_{CC}$   $\frac{R_B}{R_C} < \beta$  saturation  $v_O = V_{CE}(\text{sat})$

# 5.3.3 Amplifier

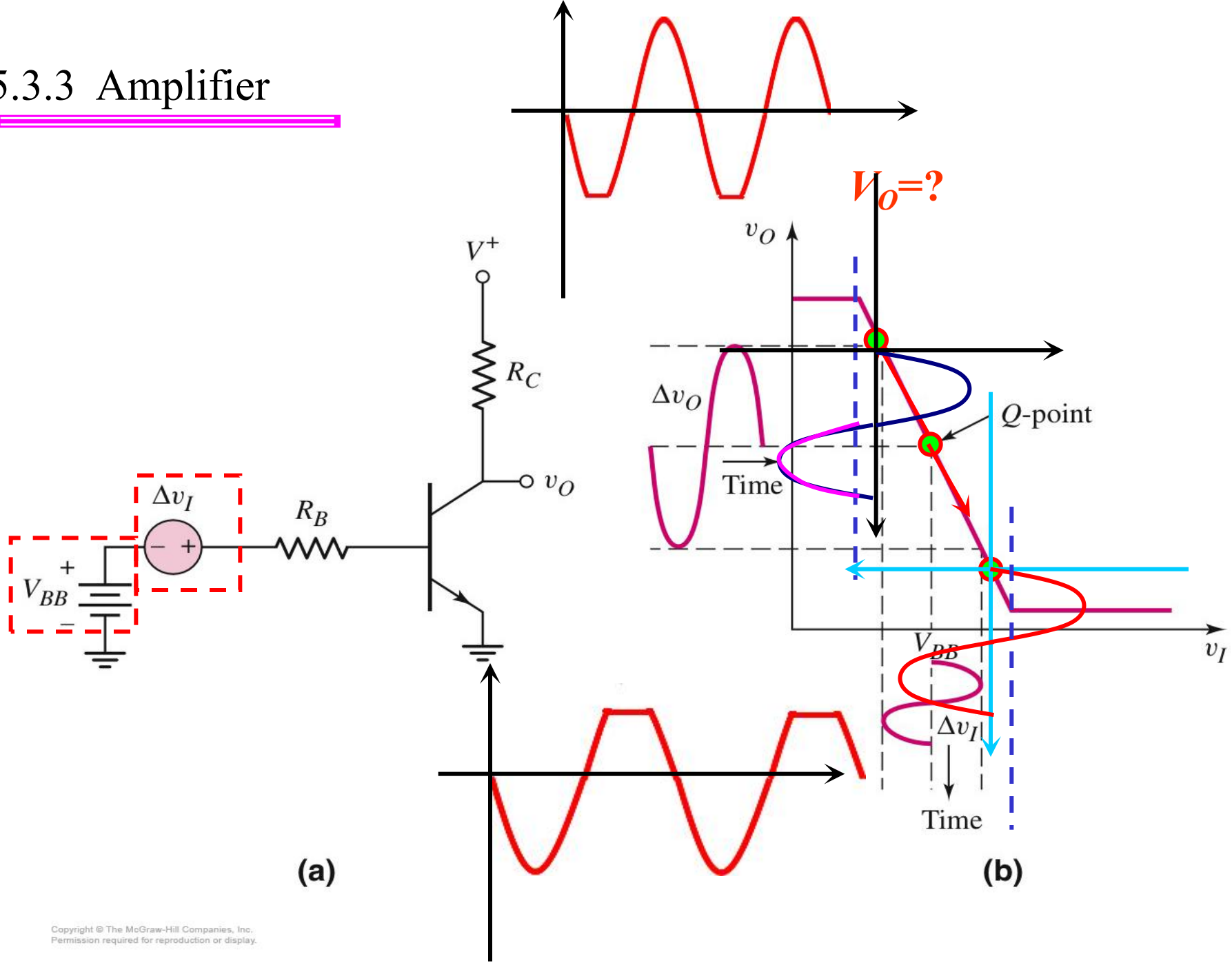



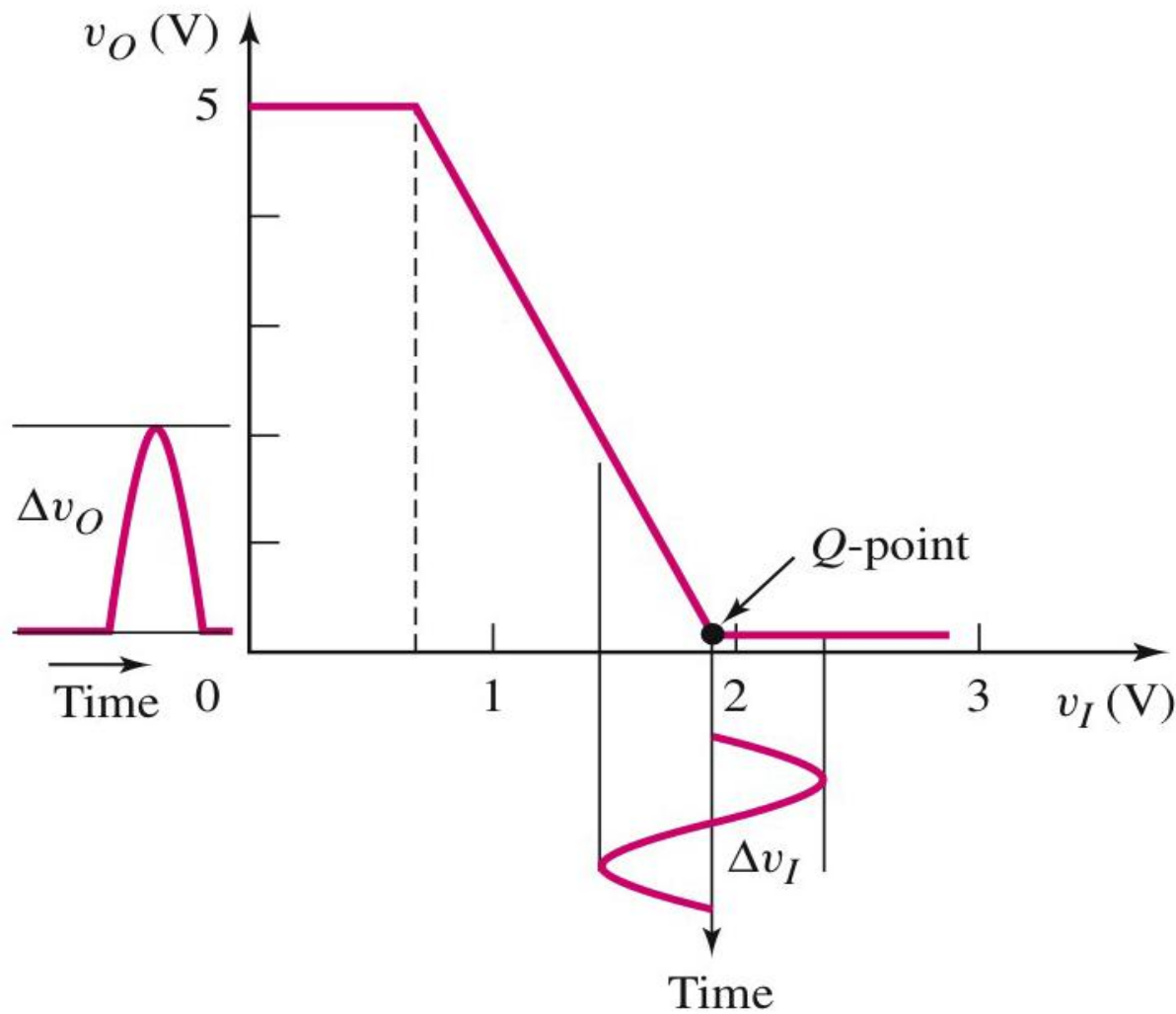
# Effect of Improper Biasing on Amplified Signal Waveform


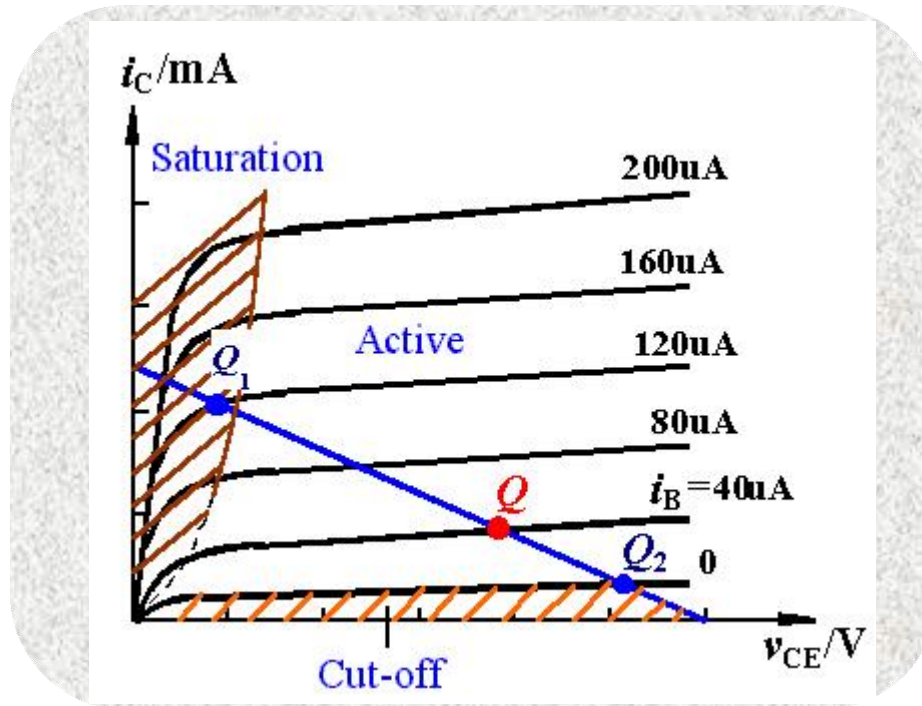
# Effect of Improper Biasing on Amplified Signal Waveform




The  $i$ - $v$  characteristic of npn


# Effect of Improper Biasing on Amplified Signal Waveform

saturation distortion

For NPN BJT and the CE circuit

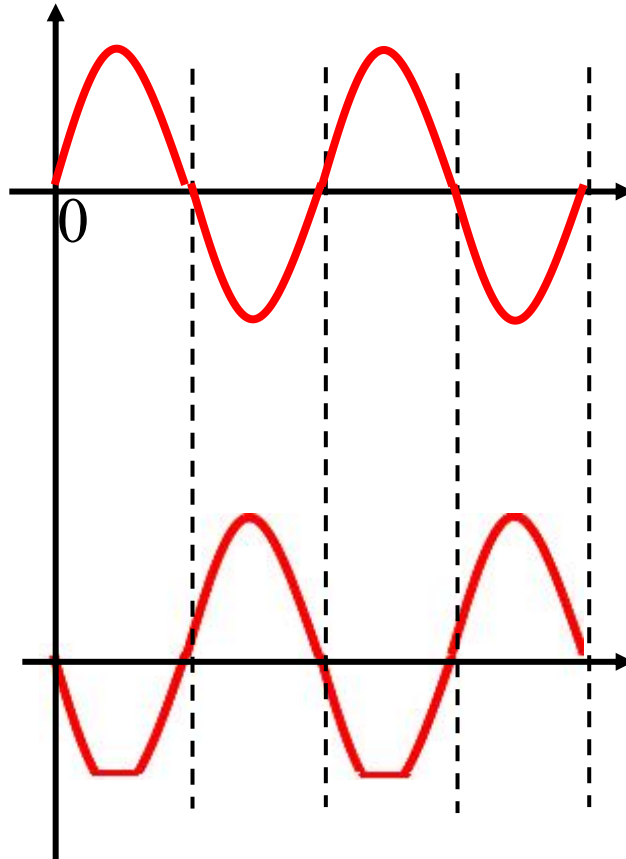


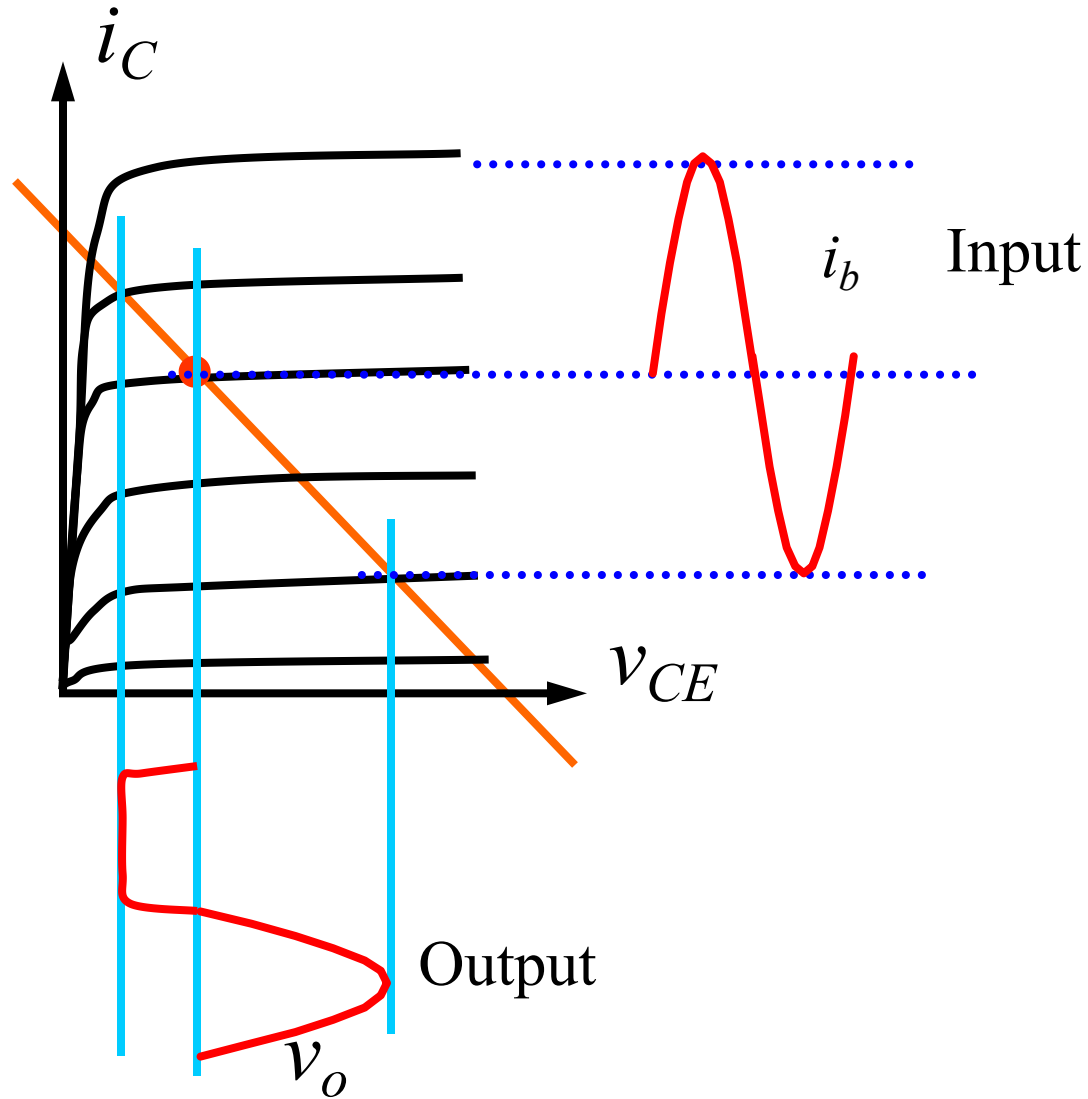- The Q-point is too high, output waveform is distorted.




## Cut-off distortion


For NPN BJT and the CE circuit

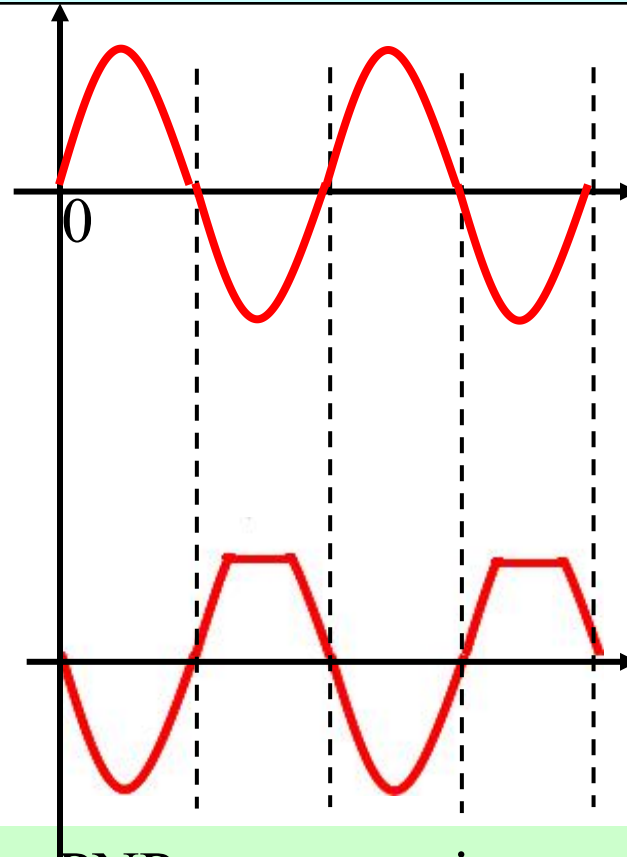


Note: For the PNP, as a negative power supply, the distortion is against to NPN.

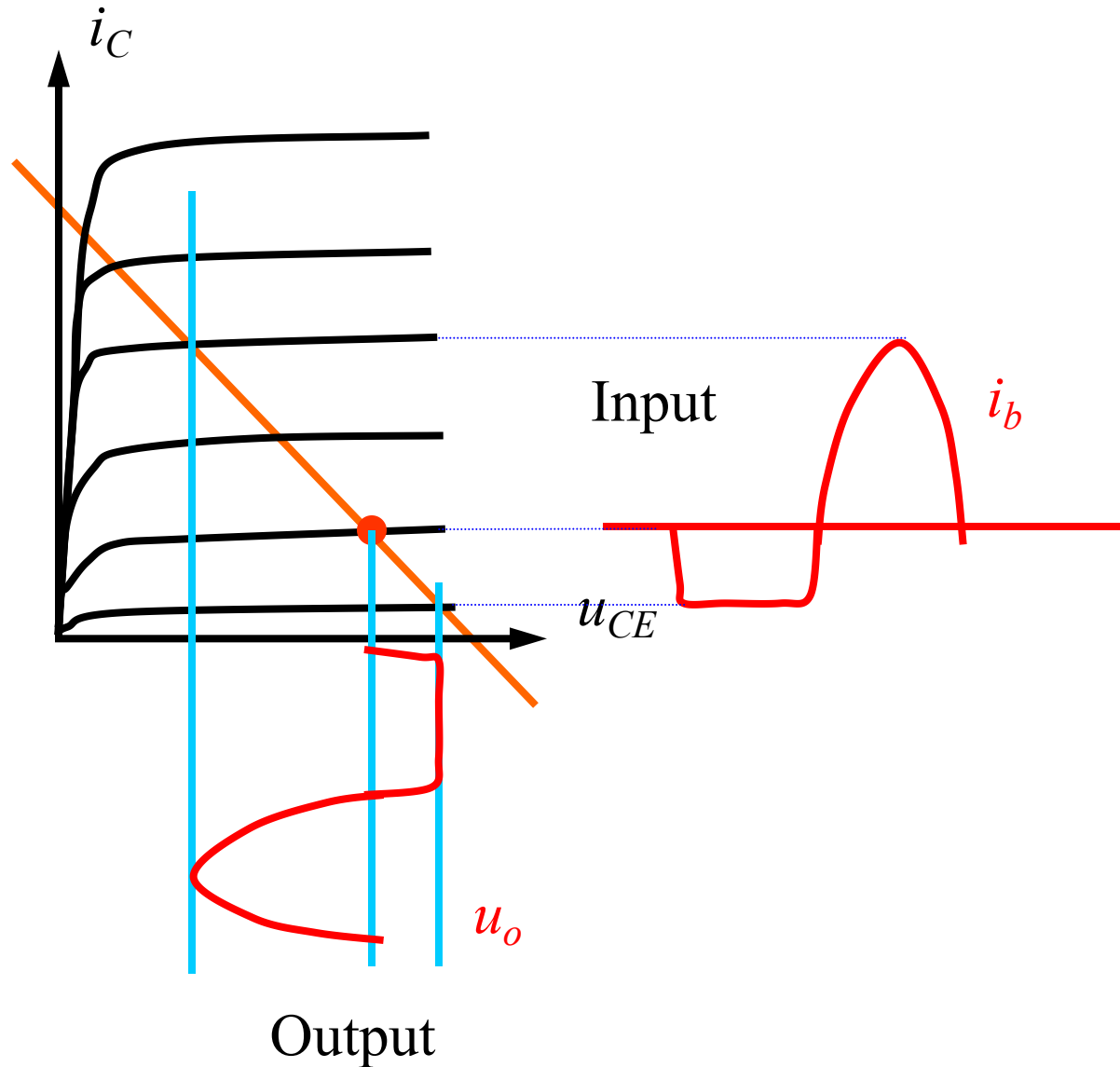
- The Q-point is too low, output waveform is distorted.



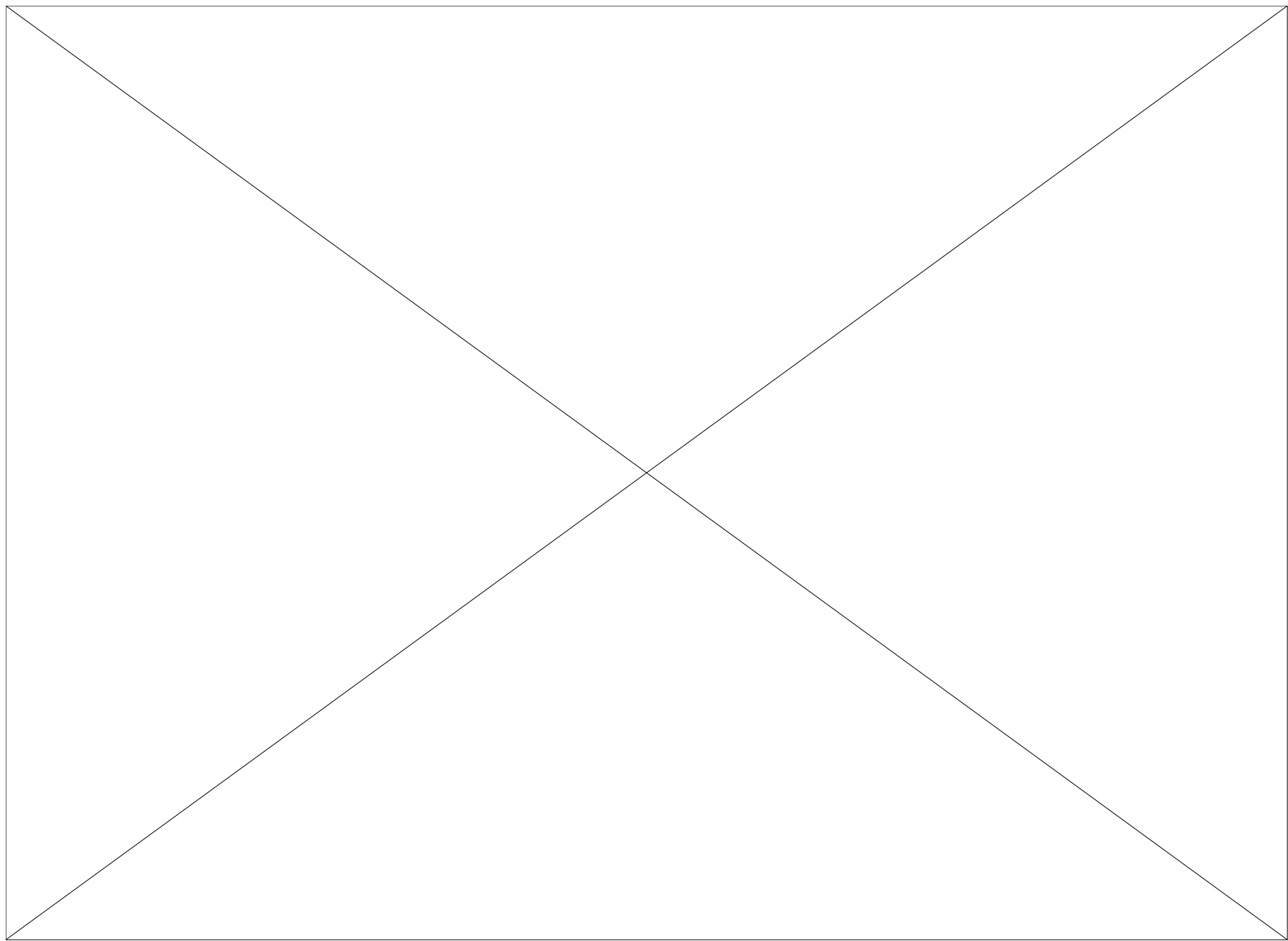


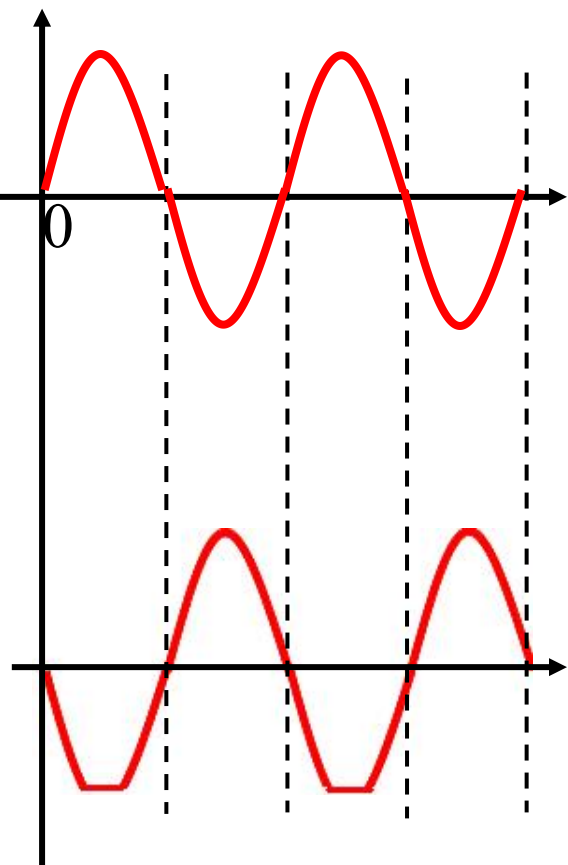

saturation distortion

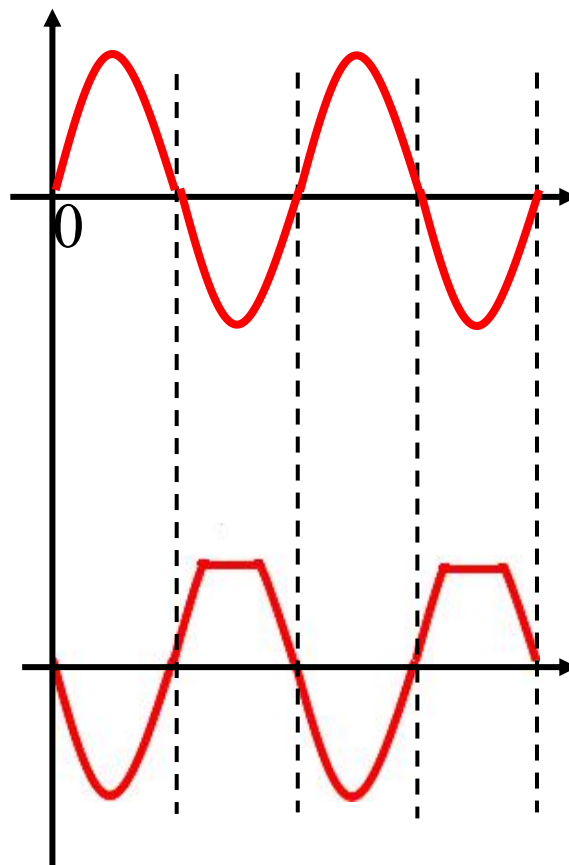

Cut-off  
distortion

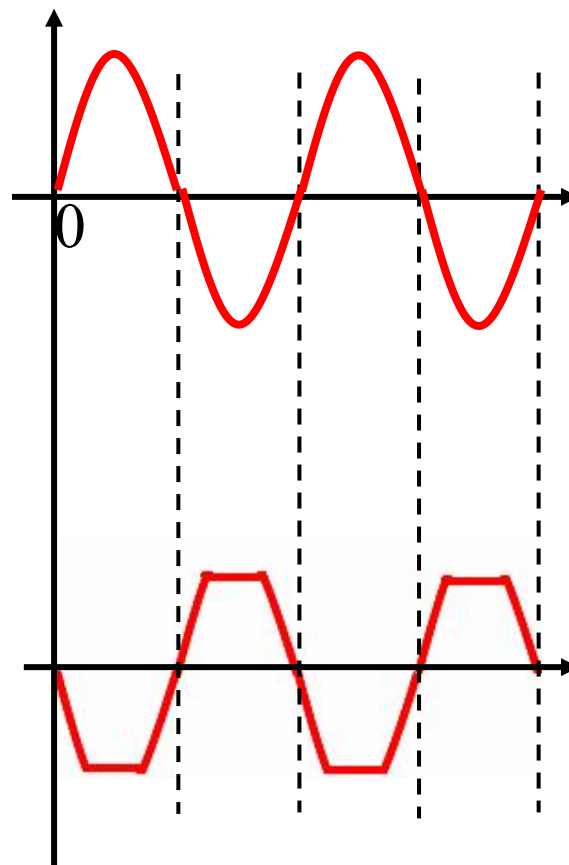


Clipping distortion



## 5.4 Basic Transistor Biasing

---

DC Biasing

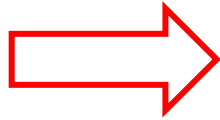


Establish Q-point




Forward active region

# 5.4.1 Single Base Resistor Biasing

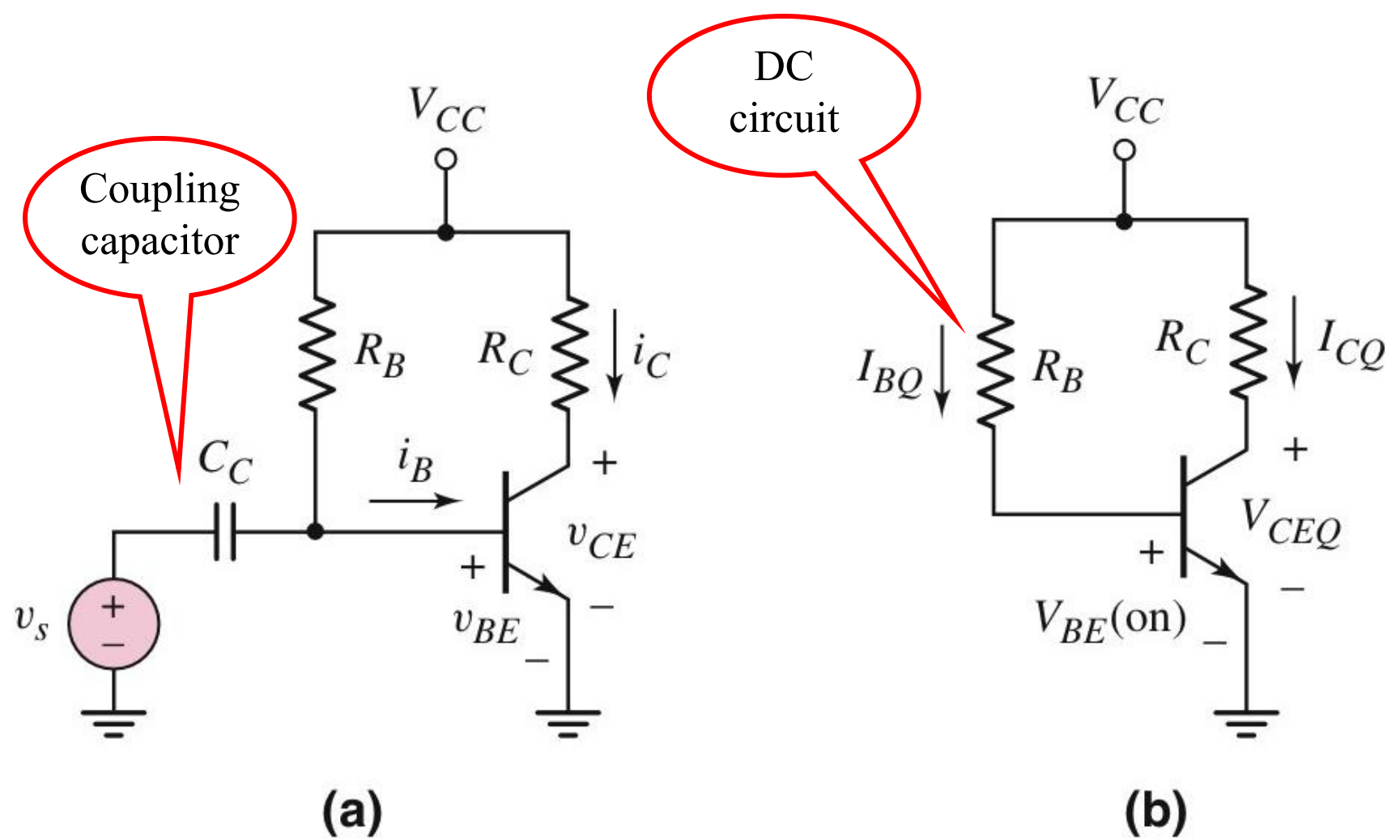

5.4.1 Single Base Resistor Biasing

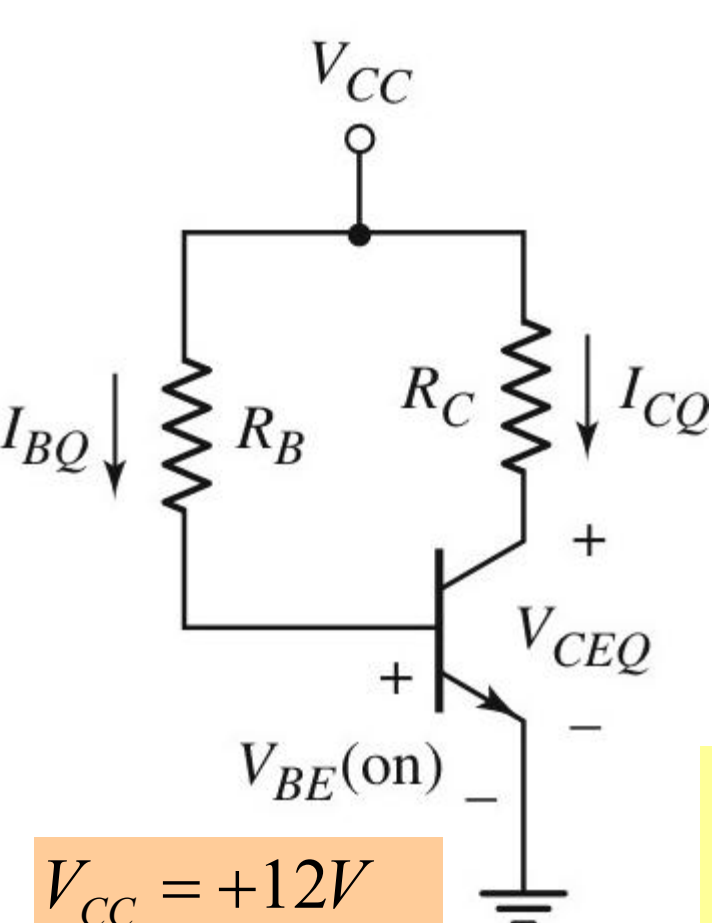

Find  $R_C$ ,  $R_B$ ,  
for  $I_{CQ}=1\text{mA}$ ,  $V_{CEQ}=6\text{V}$

$$R_C = \frac{V_{CC} - V_{CEQ}}{I_C} = \frac{12 - 6}{1} = 6\text{k}\Omega$$


$$I_B = \frac{I_C}{\beta} = \frac{1\text{mA}}{100} = 10\mu\text{A}$$

$$R_B = \frac{V_{CC} - V_{BE(on)}}{I_{BQ}}$$

$V_{CC} = +12\text{V}$   
 $\beta = 100$   
 $V_{BE(on)} = 0.7\text{V}$


IF Cut-off distortion?
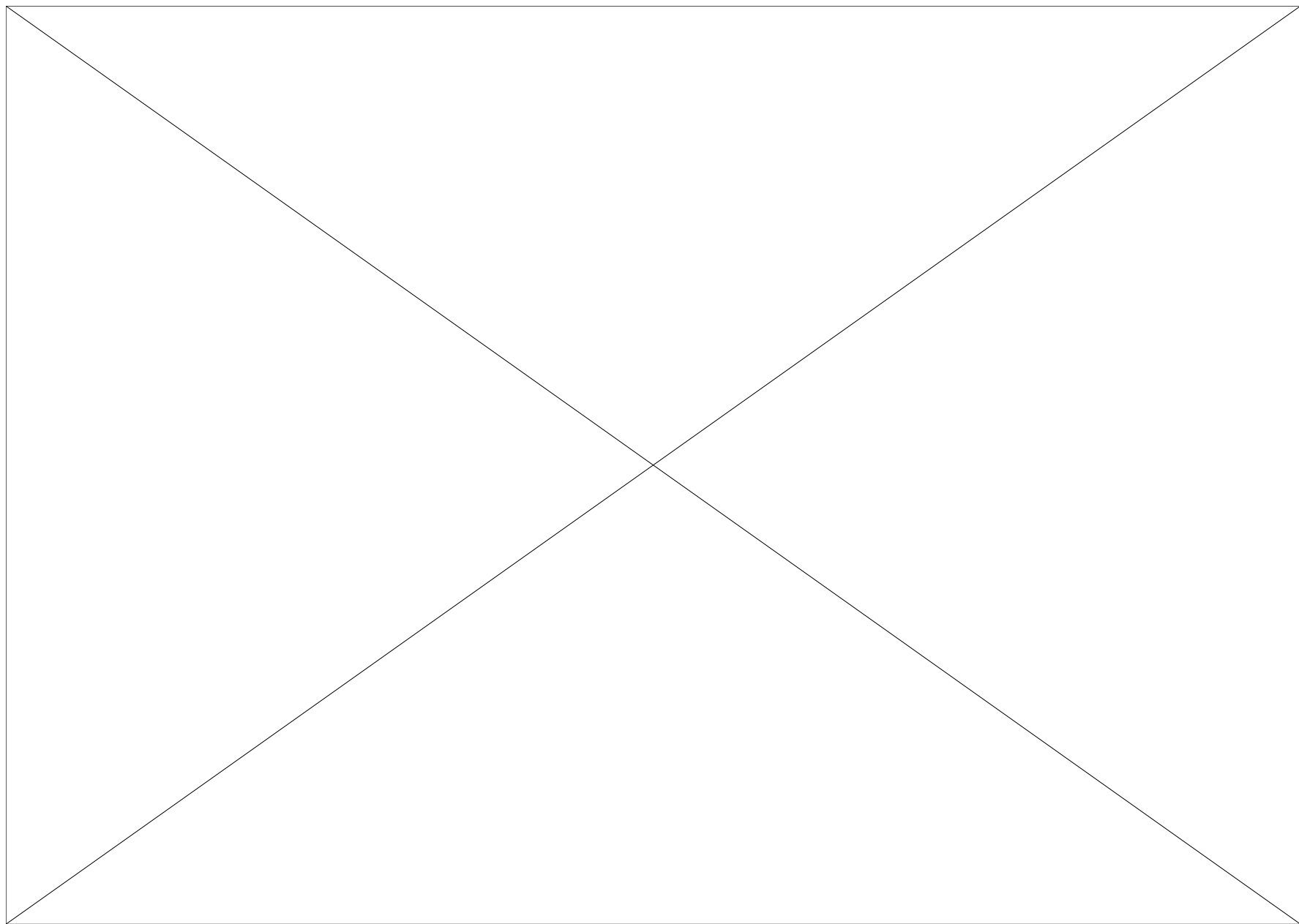
$$= \frac{12 - 0.7}{10\mu\text{A}} = 1.13\text{M}\Omega$$



# 5.4.2 Voltage Divider Biasing and Bias Stability


DC circuit

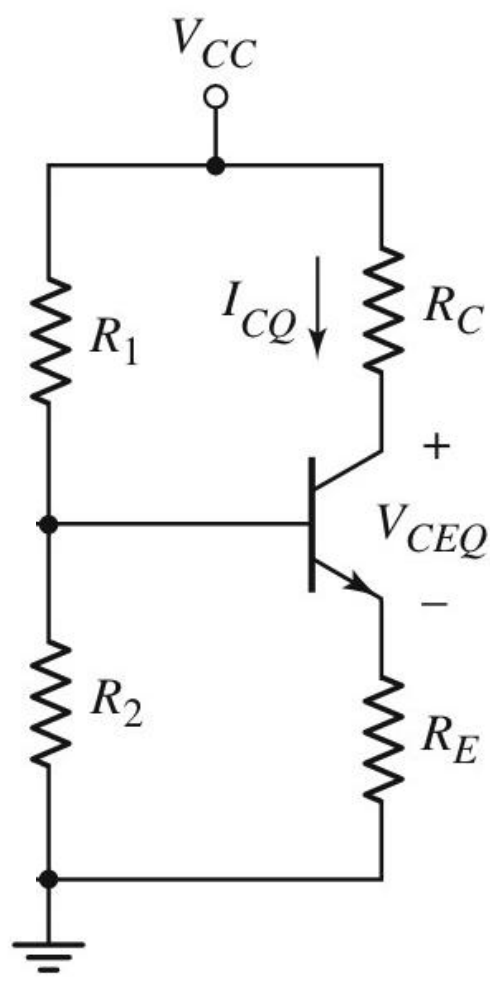

$V_{TH} = ?$

$V_{TH} = [R_2 / (R_1 + R_2)]V_{CC}$

Thevenin  
equivalent

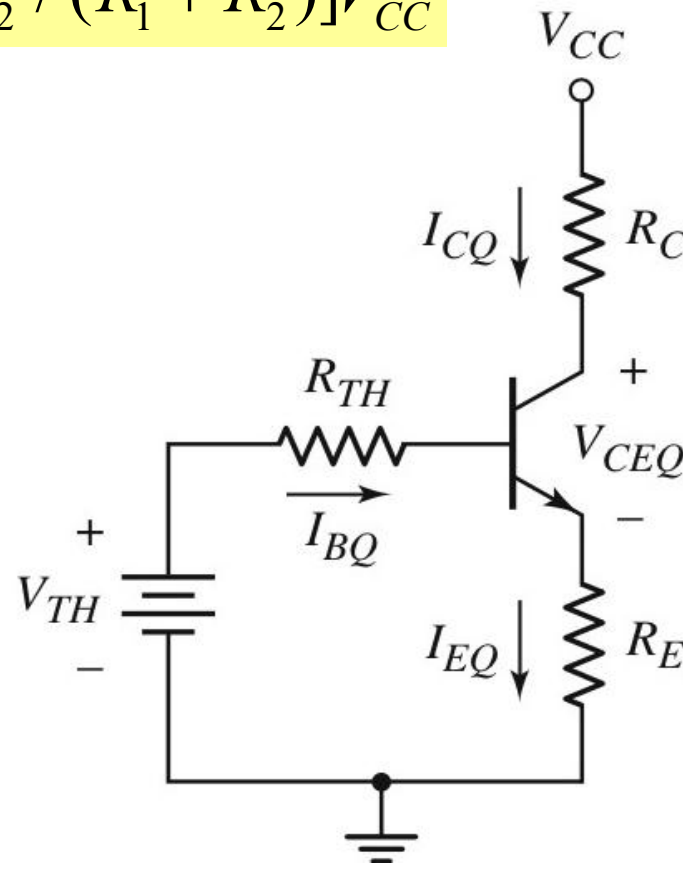

$R_{TH} = ?$


$R_{TH} = R_1 // R_2$

# 5.4.2 Voltage Divider Biasing and Bias Stability

$$V_{TH} = [R_2 / (R_1 + R_2) V_{CC}$$
$$R_{TH} = R_1 // R_2$$

Input loop

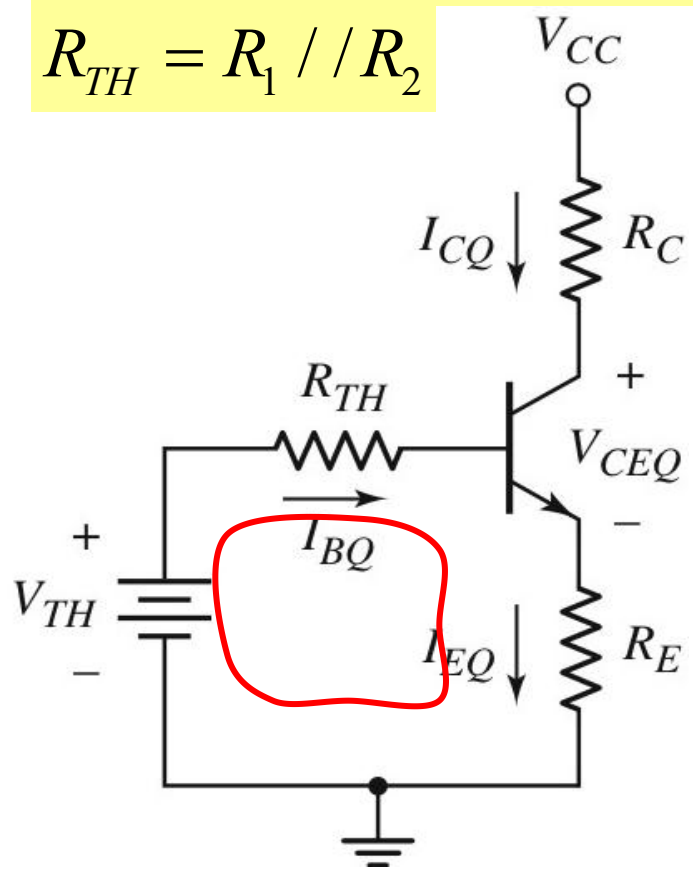
$$V_{TH} = I_B R_{TH} + V_{BE} + I_E R_E$$
$$I_E = (1 + \beta) I_B$$



Q-point

$$\left\{ \begin{array}{l} I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta) R_E} \\ I_C = \beta I_B \\ V_{CEQ} = V_{CC} - I_C R_C - I_E R_E \end{array} \right.$$
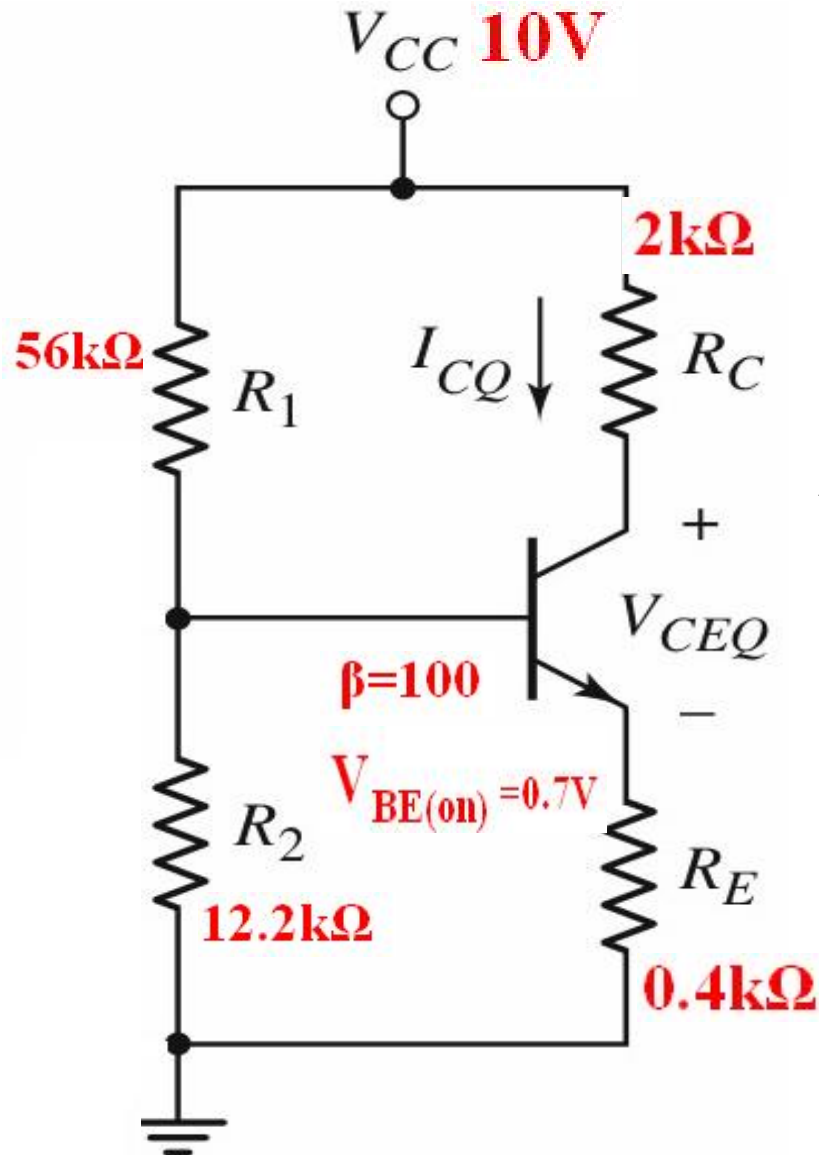
## 5.4.2 Voltage Divider Biasing and Bias Stability



Find Q-point.

$$R_{TH} = R_1 // R_2 \approx 10k\Omega$$


$$V_{TH} = [R_2 / (R_1 + R_2)] V_{CC} = 1.79V$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta)R_E} = 21.6\mu A$$

$$I_C = \beta I_B = 2.16mA$$

$$V_{CEQ} = V_{CC} - I_C R_C - I_E R_E = 4.81V$$
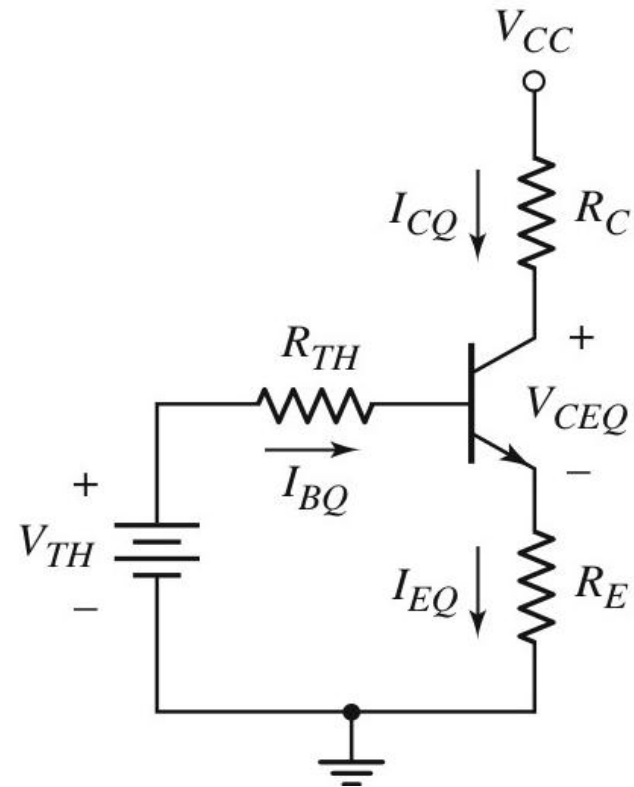
## 5.4.2 Voltage Divider Biasing and Bias Stability



Forward active region


**General rule of bias stable:**

$$R_{TH} \ll (1 + \beta)R_E$$

and  $R_{TH} \cong 0.1(1 + \beta)R_E$


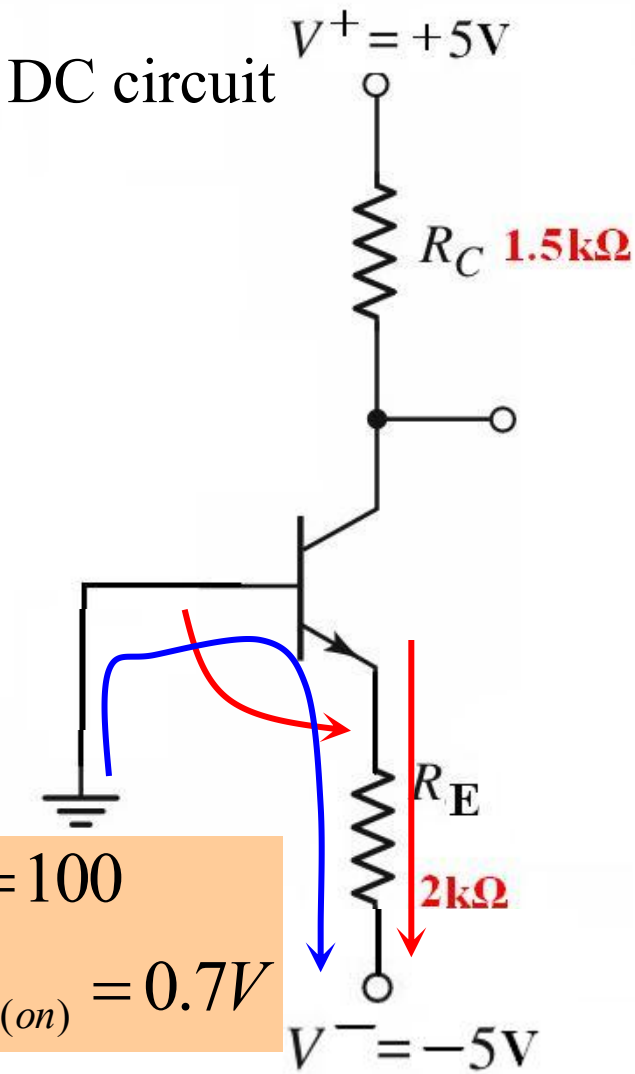
### 5.4.3 Positive and Negative Voltage Biasing



Forward active region?



Find the Q-point?

$$0 = I_{EQ} R_E + V_{BE(on)} + V^-$$

$$I_{EQ} = -\frac{V_{BE(on)} + V^-}{R_E} = -\frac{0.7 - 5}{2} = 2.15mA$$

$$I_{CQ} = I_{EQ}$$



$$\begin{aligned} V_{CEQ} &= V^+ - V^- - I_C R_C - I_E R_E \\ &= 2V^+ - I_C R_C - I_E R_E \end{aligned}$$

### 5.4.3 Positive and Negative Voltage Biasing

Find the Q-point?

DC circuit


$R_{TH} = R_1 // R_2$

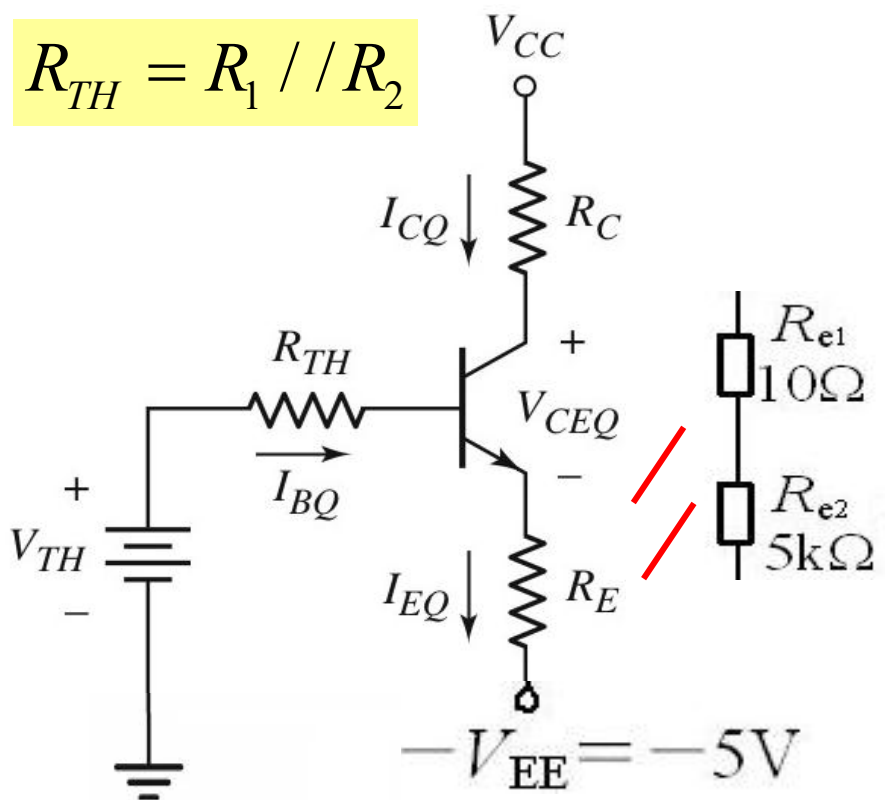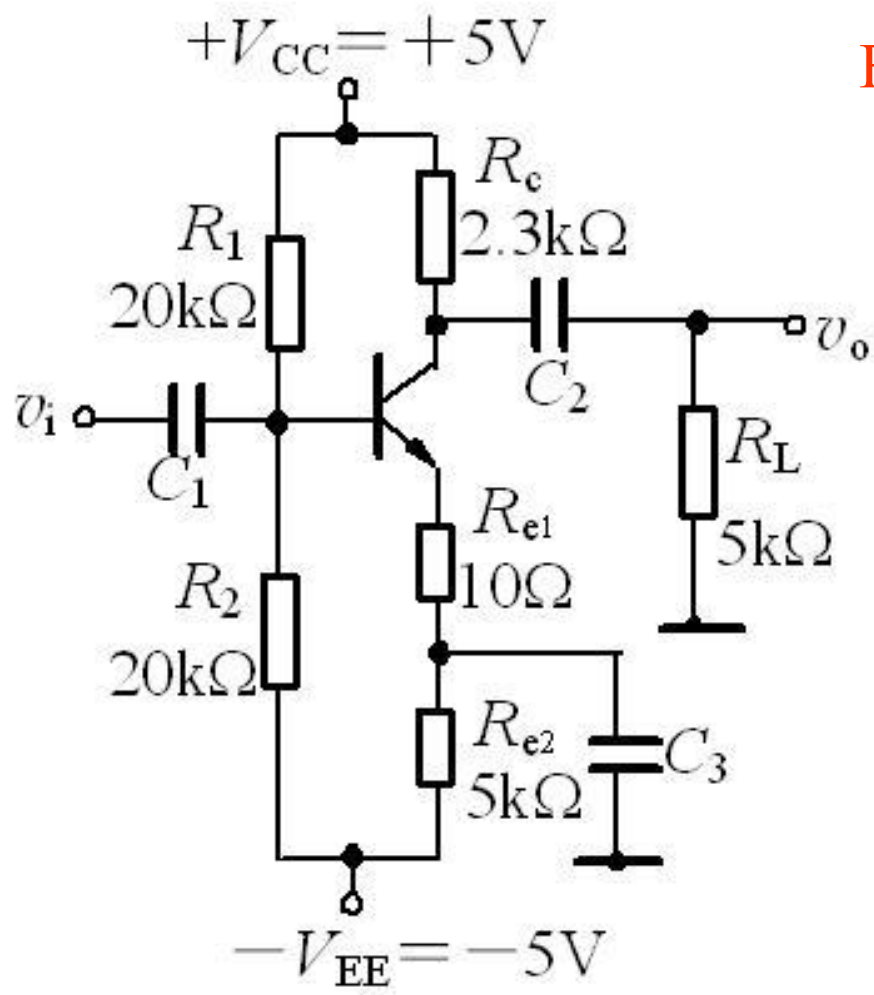

$\beta = 125$   
 $V_{BE(on)} = 0.7V$



$V_{TH} = [R_2 / (R_1 + R_2)][V_{CC} + V_{EE}] - V_{EE}$

## 5.4.4 Integrated Circuit Biasing

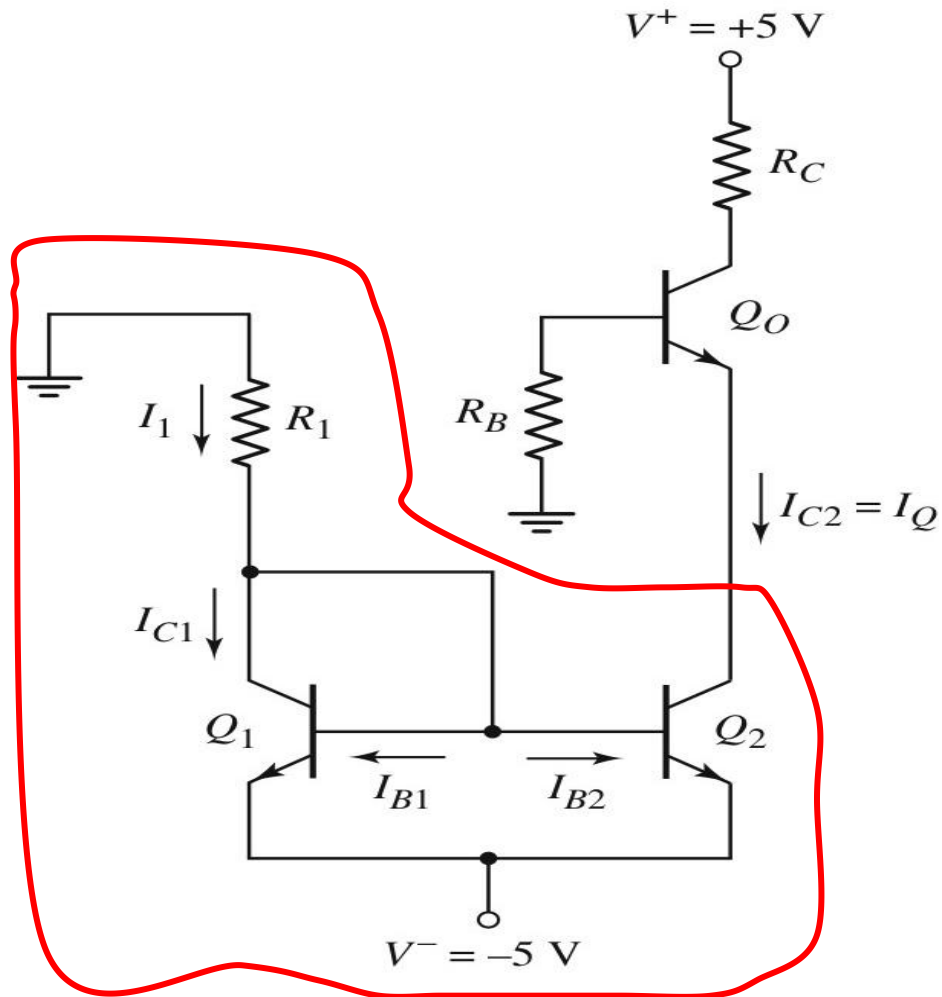


Current source

Chapter 10

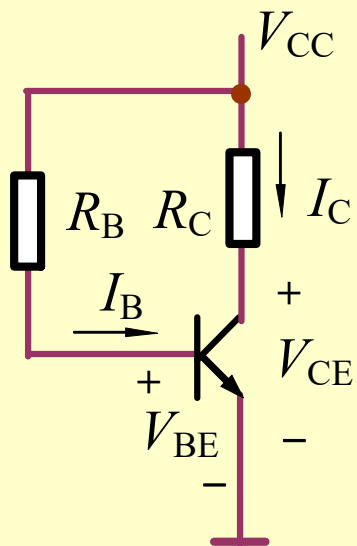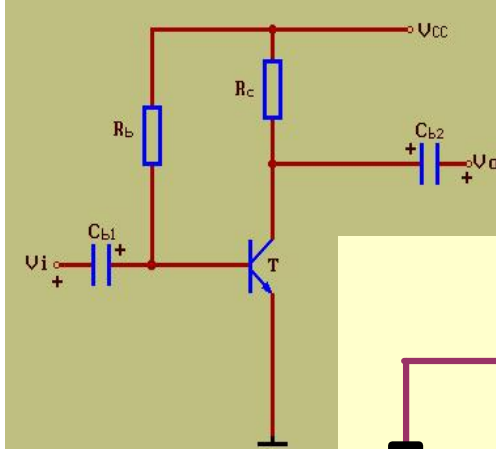


DC equivalent circuit

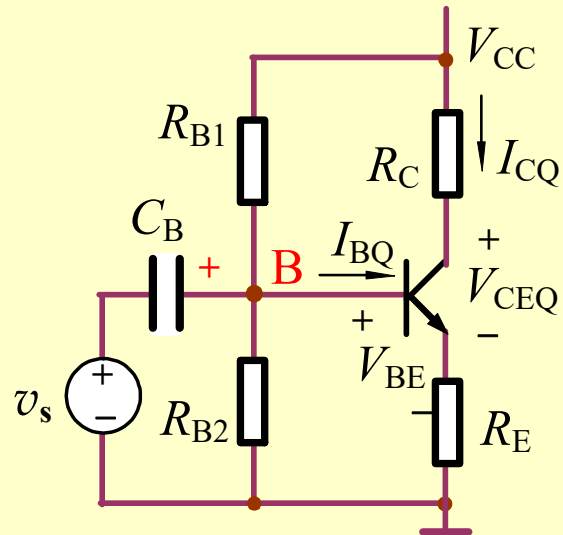

$$V_{TH} \approx \frac{R_{B2}}{R_{B1} + R_{B2}} \cdot V_{CC}$$

$$R_{TH} = R_{B1} // R_{B2}$$

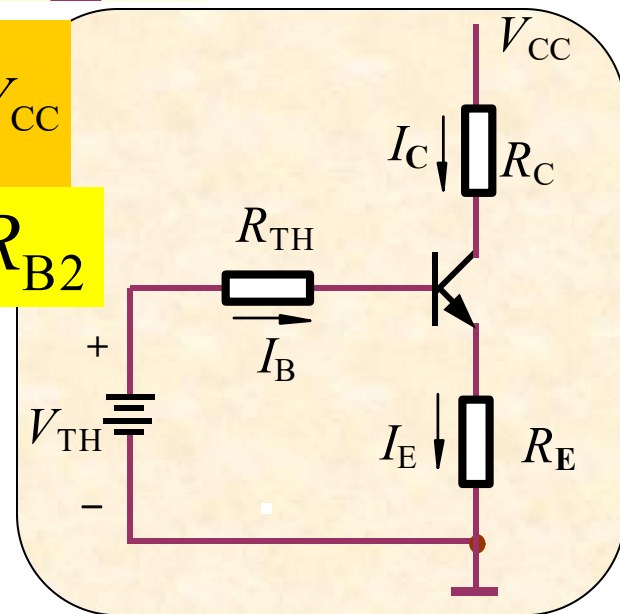

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta) R_E}$$

$$I_C = \beta I_B$$

$$V_{CEQ} = V_{CC} - I_C R_C - I_E R_E$$

### Example 1

Assume  $\beta=50$ , find out  $V_{CQ}=?$   $V_{CC}=12V$ ,  $U_{CES}=0.5V$ 。

(1) Normal; (2)  $R_{b1}$  is short; (3)  $R_{b1}$  is open; (4)  $R_{b2}$  open;

(5)  $R_C$  short。

Sol: assume  $U_{BE}=0.7V$ 。 then

$$(1) I_B = \frac{V_{CC} - U_{BE}}{R_{b2}} - \frac{U_{BE}}{R_{b1}} \approx 0.022mA$$

$$U_C = V_{CC} - I_C R_c \approx 6.4V$$


$$(2) U_{BE}=0V \rightarrow T \text{ cut off} \rightarrow U_C=12V$$

$$(3) I_B = \frac{V_{CC} - U_{BE}}{R_{b2}} \approx 0.22mA$$

$$I_{BS} = \frac{V_{CC} - U_{CES}}{\beta R_c} \approx 0.045mA$$

$I_B > I_{BS}$ , T saturation,  $U_C = U_{CES} = 0.5V$ 。

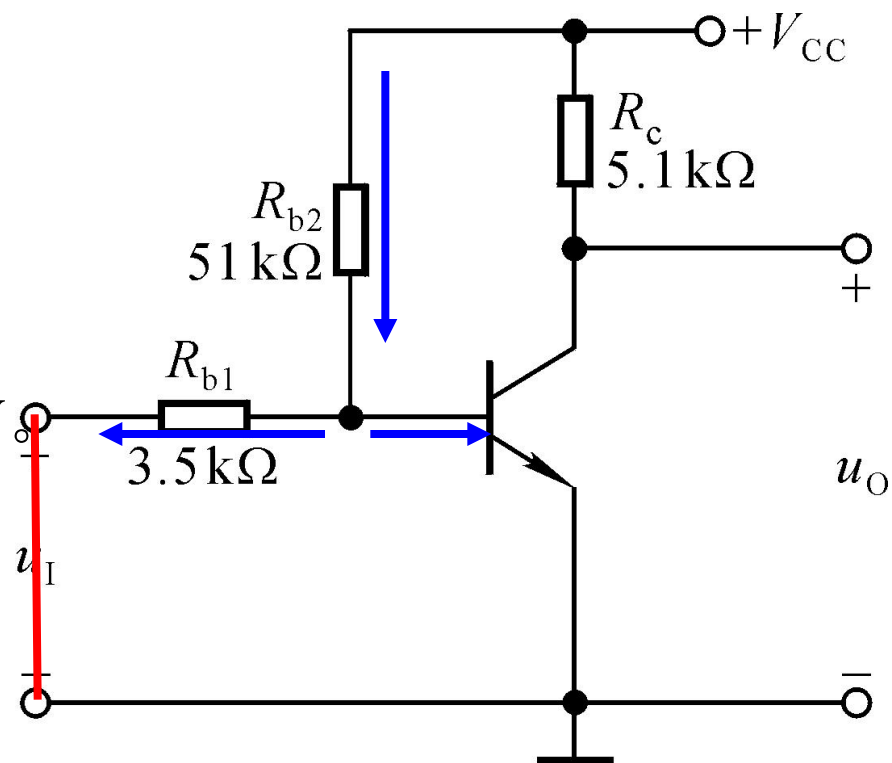(4) T cutoff,  $U_C = 12V$ 。 (5)  $U_C = V_{CC} = 12V$





# Review Questions

2. When  $V_{CE}$  of BJT is nearly equal  $V_{CC}$ , Which region is it operating in? What may the reasons?


**Answer:** Cut-off region

Reasons may:

- $R_b$  may open circuit,  $I_B=0$ ,  $I_C=0$ ,  $V_{CE}=V_{CC}-I_C R_c=V_{CC}$ .

- $C_1$  may short circuit
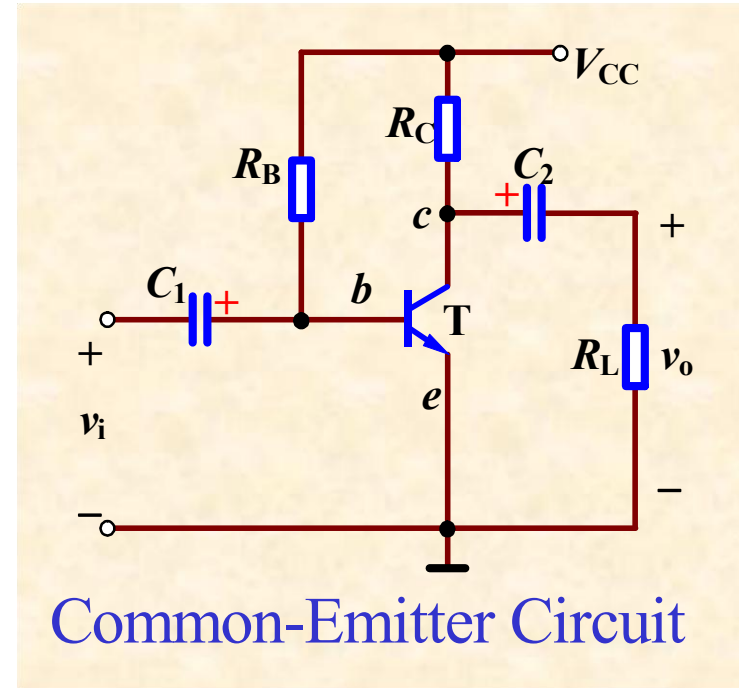
$$V_{BE}=0, \quad I_B=0, \quad I_C=0, \quad V_{CE}=V_{CC}-I_C R_c=V_{CC}.$$



# Contents

## PART 1 SEMICONDUCTOR DEVICES AND BASIC APPLICATIONS

Chapter 1 Semiconductor Materials and Diodes

Chapter 2 Diode Circuits

Chapter 3 The Field-Effect Transistor

Chapter 4 Basic FET Amplifiers

 Chapter 5 The Bipolar Junction Transistor

Chapter 6 Basic BJT Amplifiers

Chapter 7 Frequency Response

Chapter 8 Output Stages and Power Amplifiers

## PART 2 ANALOG ELECTRONICS

Chapter 9 Ideal Operational Amplifiers and Op-Amp Circuits

Chapter 10 Integrated Circuit Biasing and Active Loads

Chapter 11 Differential and Multistage Amplifiers

Chapter 12 Feedback and Stability

Chapter 13 Operational Amplifier Circuits

Chapter 14 Nonideal Effects in Operational Amplifier Circuits

Chapter 15 Applications and Design of Integrated Circuits

# Ch5. The Bipolar Junction Transistor

---


## 5.1 Basic Bipolar Junction Transistor

## 5.2 DC Analysis of Transistor Circuits

## 5.3 Basic Transistor Application


## 5.4 Basic Transistor Biasing

## 5.5 Multistage Circuits

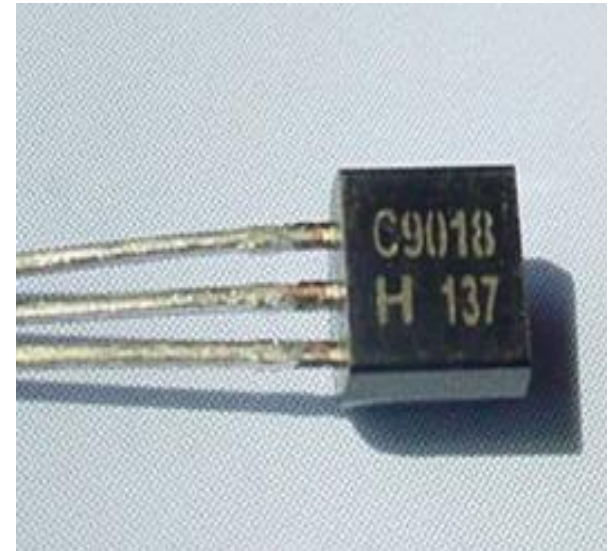




# Review

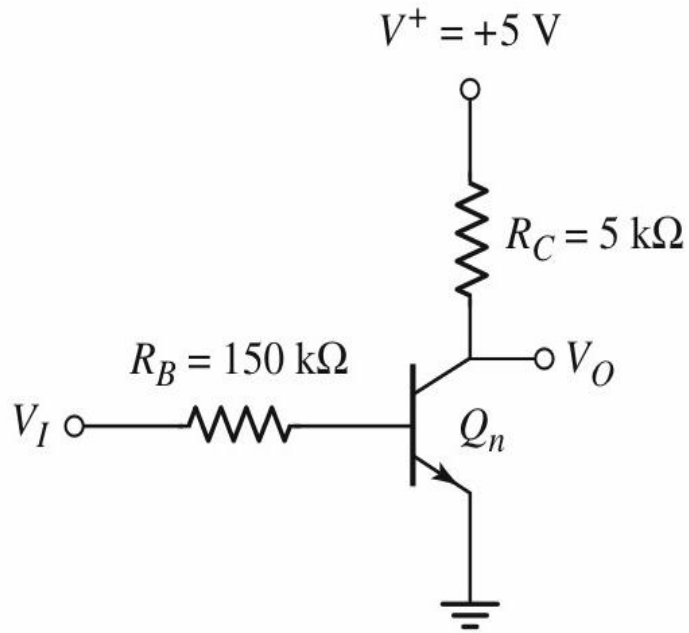


(a)

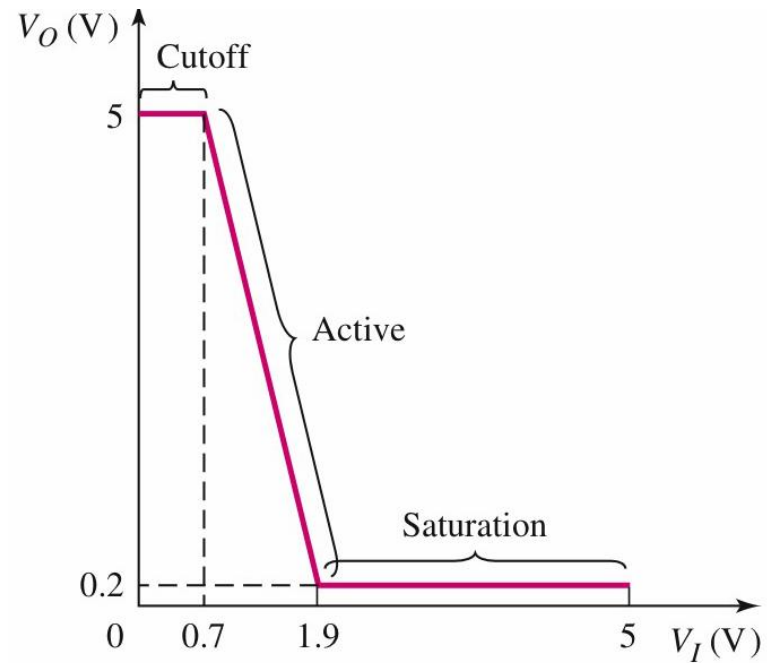


Voltage Transfer Characteristic

# Review

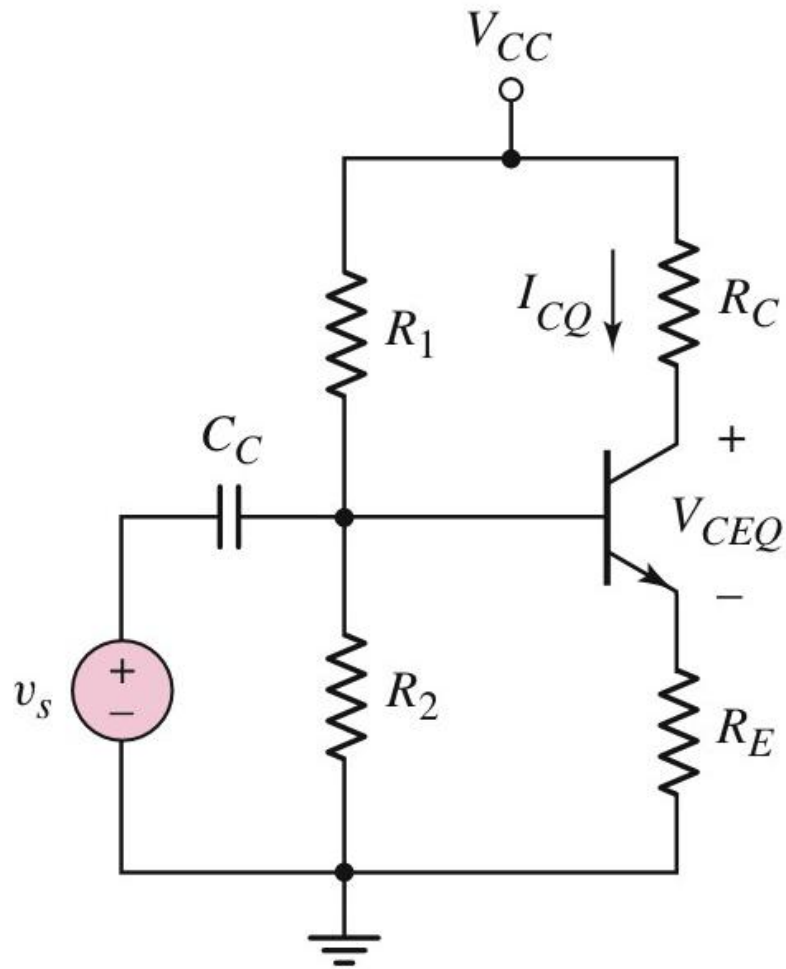

DC Circuit

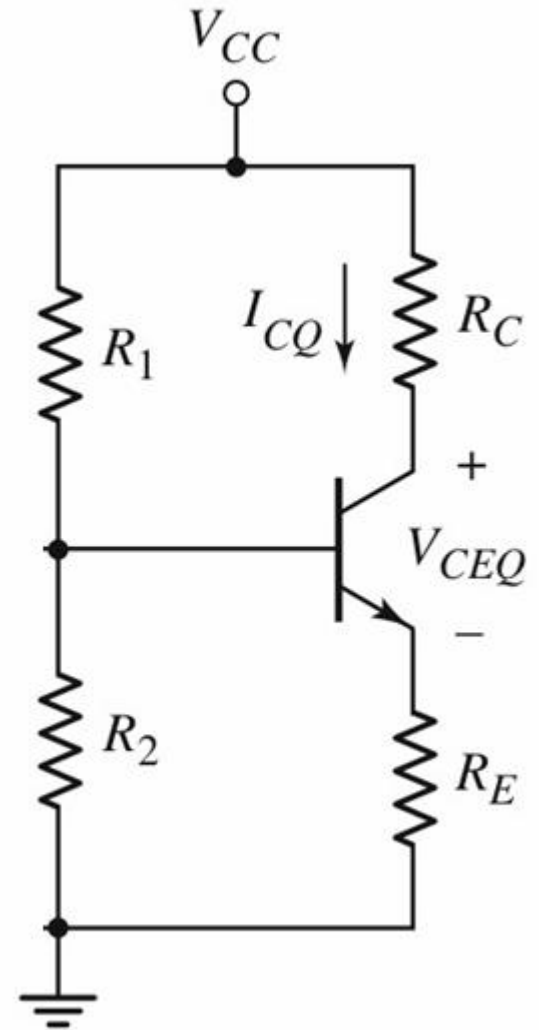


# Review

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta)R_E}$$


$$I_C = \beta I_B$$

$$V_{CEQ} = V_{CC} - I_C R_C - I_E R_E$$

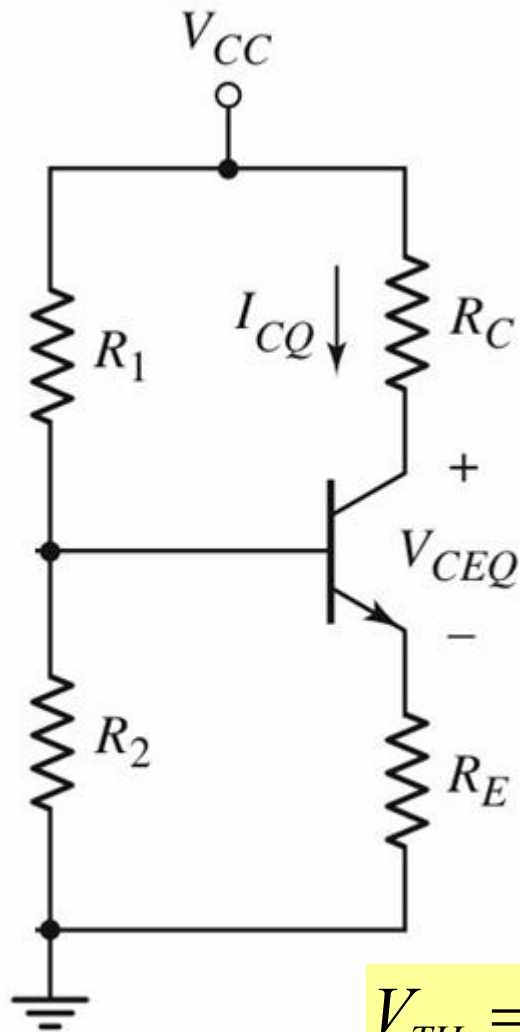

Thevenin  
equivalent

$$R_{TH} = R_1 // R_2$$

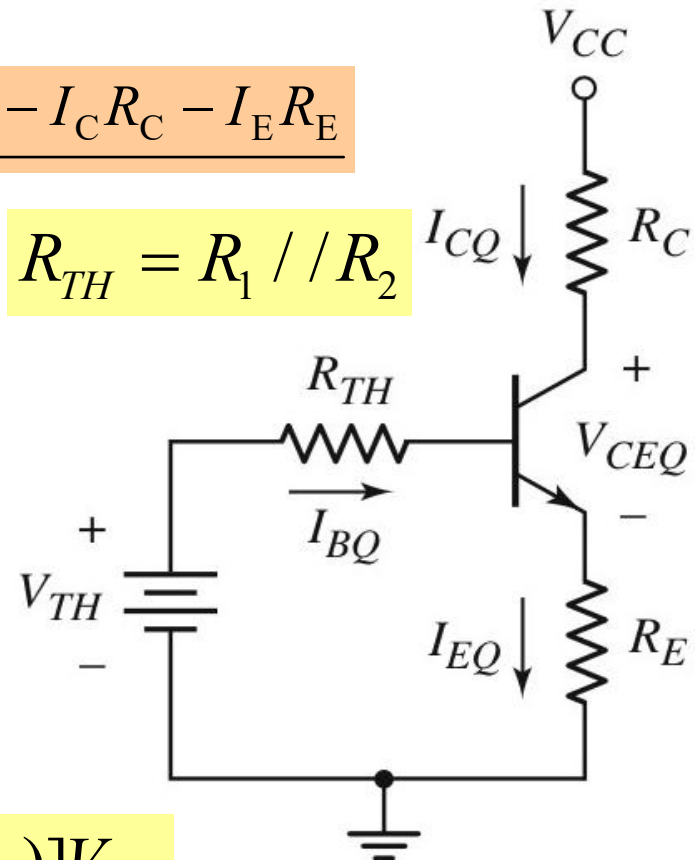




$$V_{TH} = [R_2 / (R_1 + R_2)] V_{CC}$$

# 5.5 Multistage Circuits

$$V_{TH} = [R_2 / (R_1 + R_2)][10] - 5 = -1.67V$$

$\beta = 100$   
 $V_{BE(on)} = 0.7V$

Find Q-point for each transistor

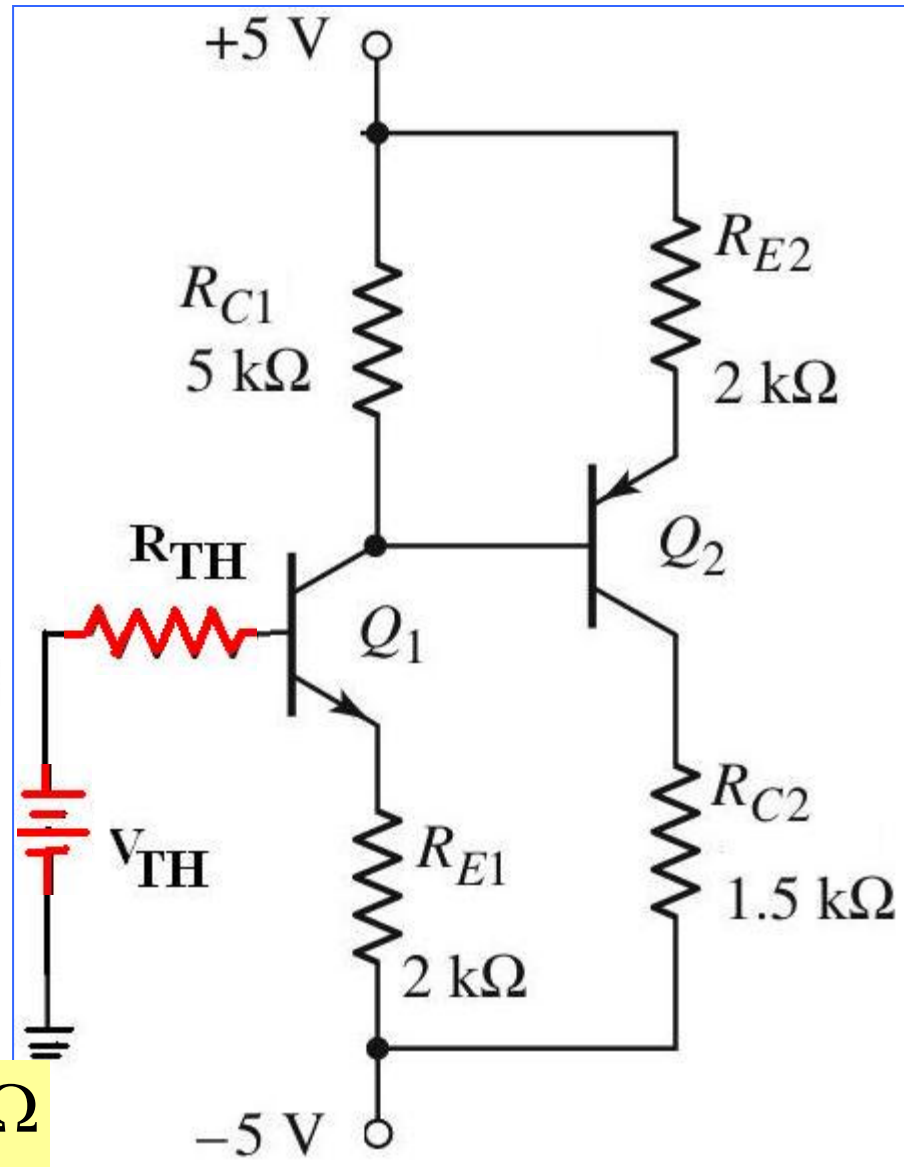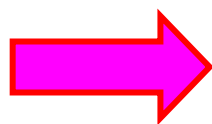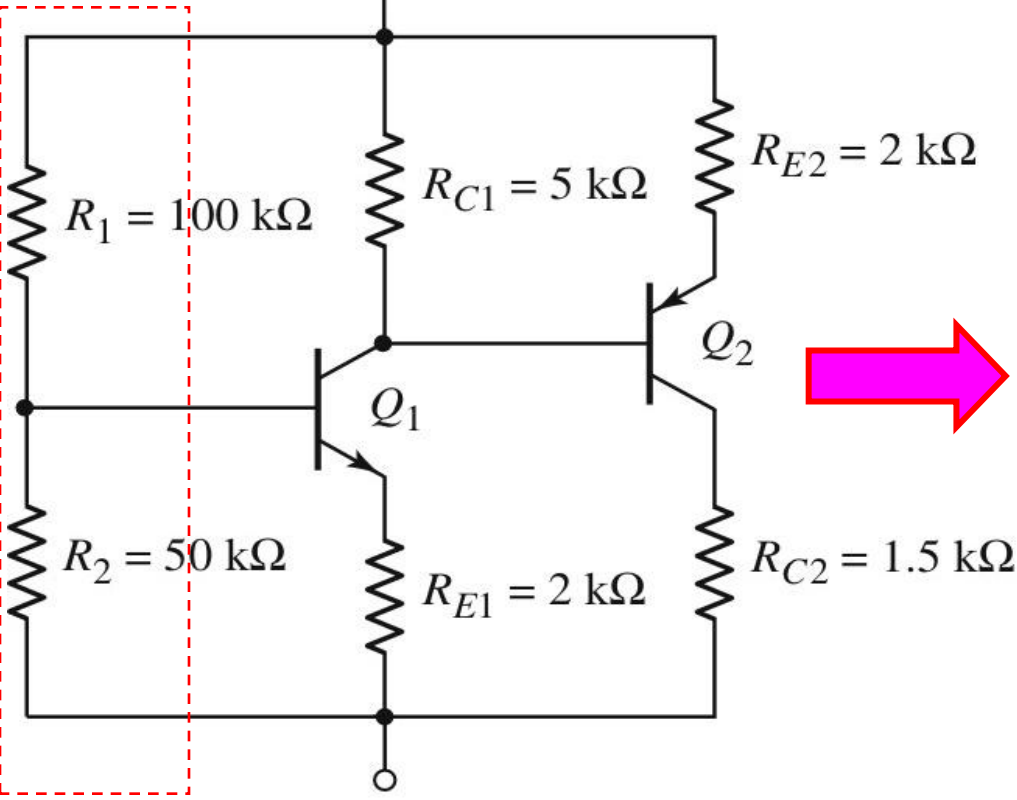


Cascade Transistor Circuit


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

级联

$$R_{TH} = R_1 // R_2 = 33.3k\Omega$$

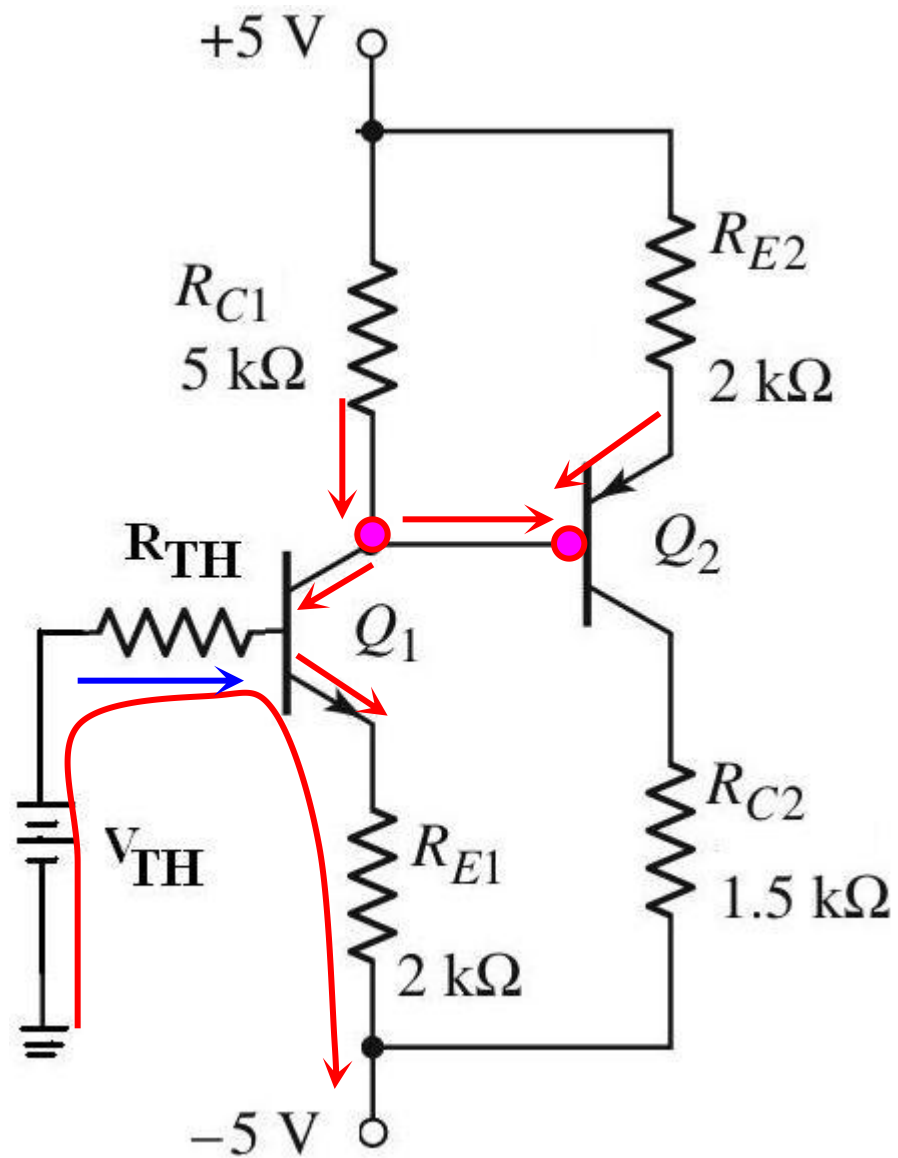

## 5.5 Multistage Circuits

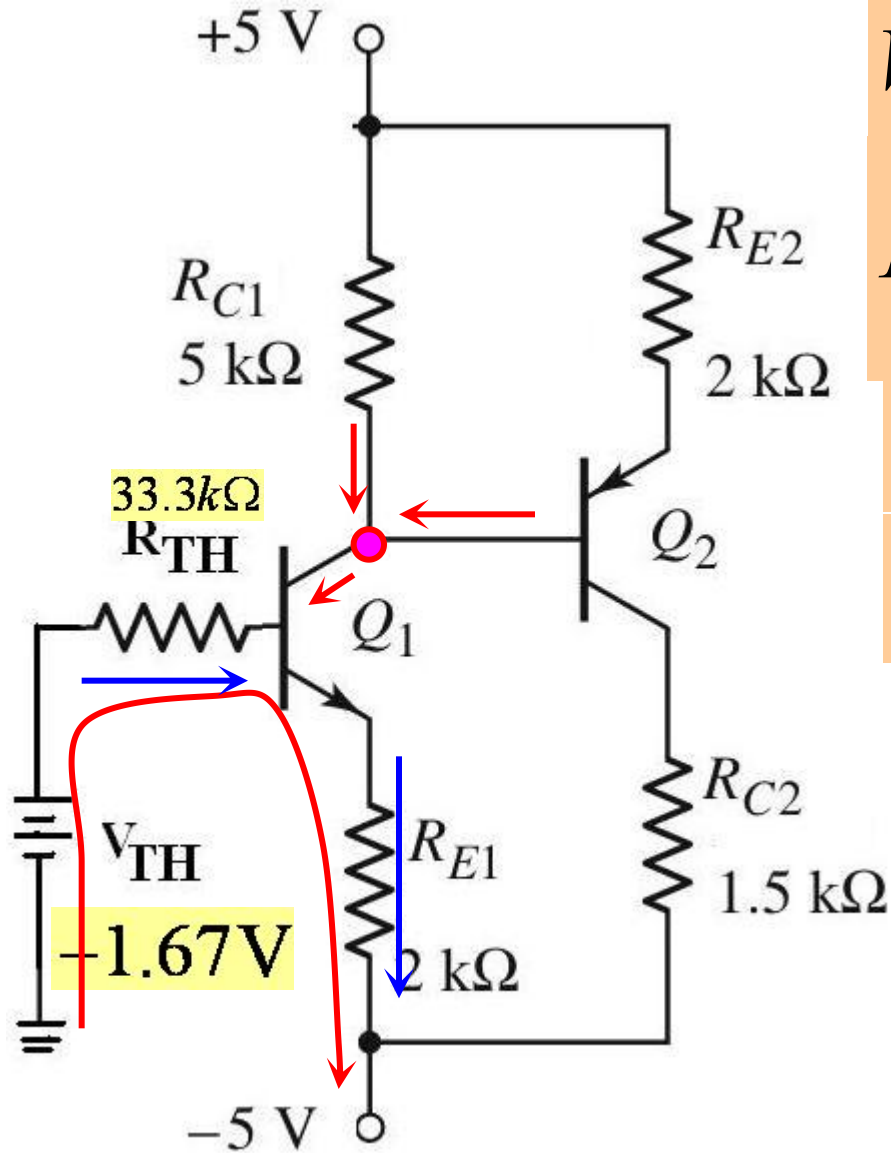

$$V_{TH} = I_{B1}R_{TH} + V_{BE(\text{on})} + I_{E1}R_{E1} - 5$$

$$I_{B1} = \frac{-1.67 + 5 - 0.7}{33.3 + (101)(2)} = 11.2\mu\text{A}$$


$$I_{C1} = \beta I_{B1} = 1.12\text{mA}$$

$$I_{E1} = (1 + \beta) I_{B1} = 1.13\text{mA}$$

$$I_{RC1} + I_{B2} = I_{C1}$$

$$\frac{5 - V_{C1}}{R_{C1}} + I_{B2} = I_{C1}$$

## 5.5 Multistage Circuits

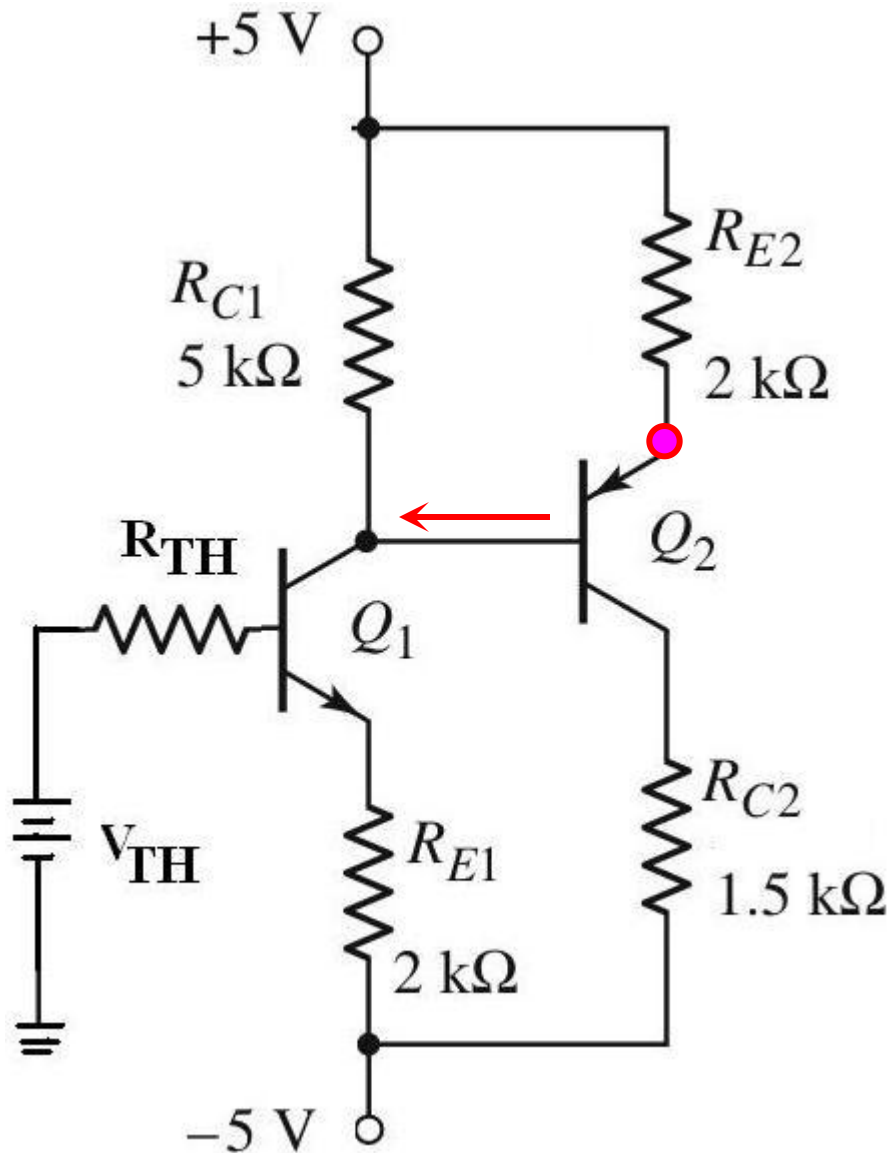

$$\frac{5 - V_{C1}}{R_{C1}} + I_{B2} = I_{C1} \dots\dots(1)$$


$$I_{B2} = \frac{I_{E2}}{1 + \beta} = \frac{5 - V_{E2}}{(1 + \beta) R_{E2}}$$

$$\Rightarrow I_{B2} = \frac{5 - (V_{C1} + 0.7)}{(1 + \beta) R_{E2}} \dots\dots(2)$$

$$I_{C1} = 1.12\text{ mA}$$

$$\Rightarrow \begin{cases} V_{C1} = -0.482\text{ V} \\ I_{B2} = 23.7\text{ }\mu\text{A} \end{cases}$$

# 5.5 Multistage Circuits

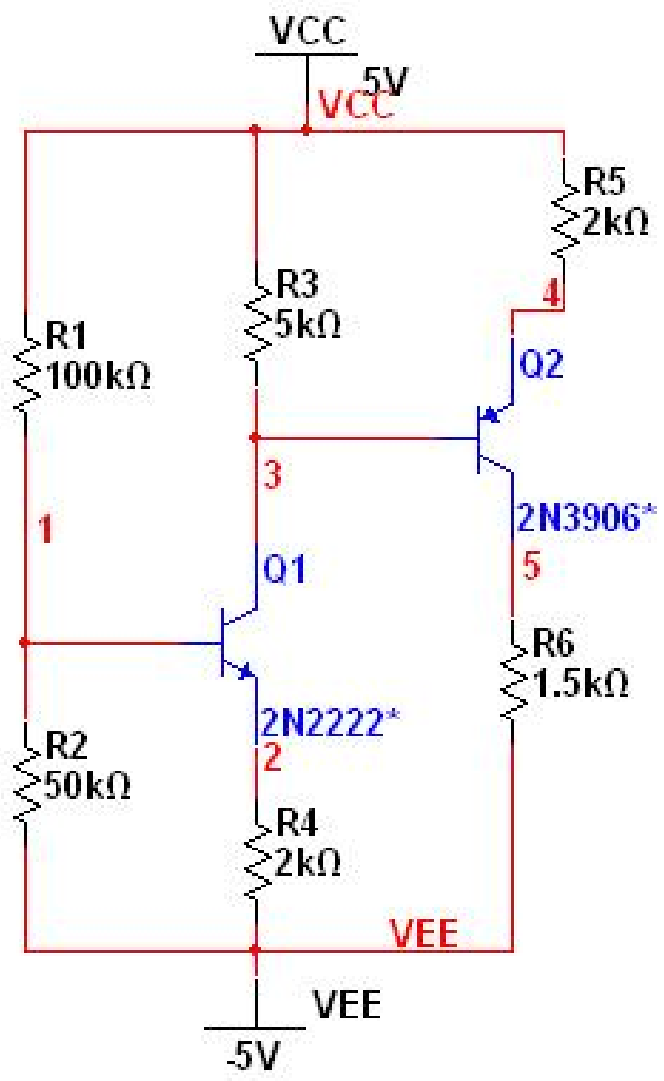


multistage  
DC Operating Point

	DC Operating Point	
1	I(Q1[IC])	$I_{C1} = 1.12mA$ 1.09647 m
2	I(Q1[IB])	$I_{B1} = 11.2\mu A$ 14.35467 u
3	I(Q2[IC])	2.30005 m
4	I(Q2[IB])	$I_{B2} = 23.7\mu A$ 22.22821 u
5	V(5)	-1.54992
6	V(4)	355.44306 m
7	V(2)	-2.77835
8	V(3)	$V_{C1} = -0.482V$ -371.20615 m



## 5.5 Multistage Circuits

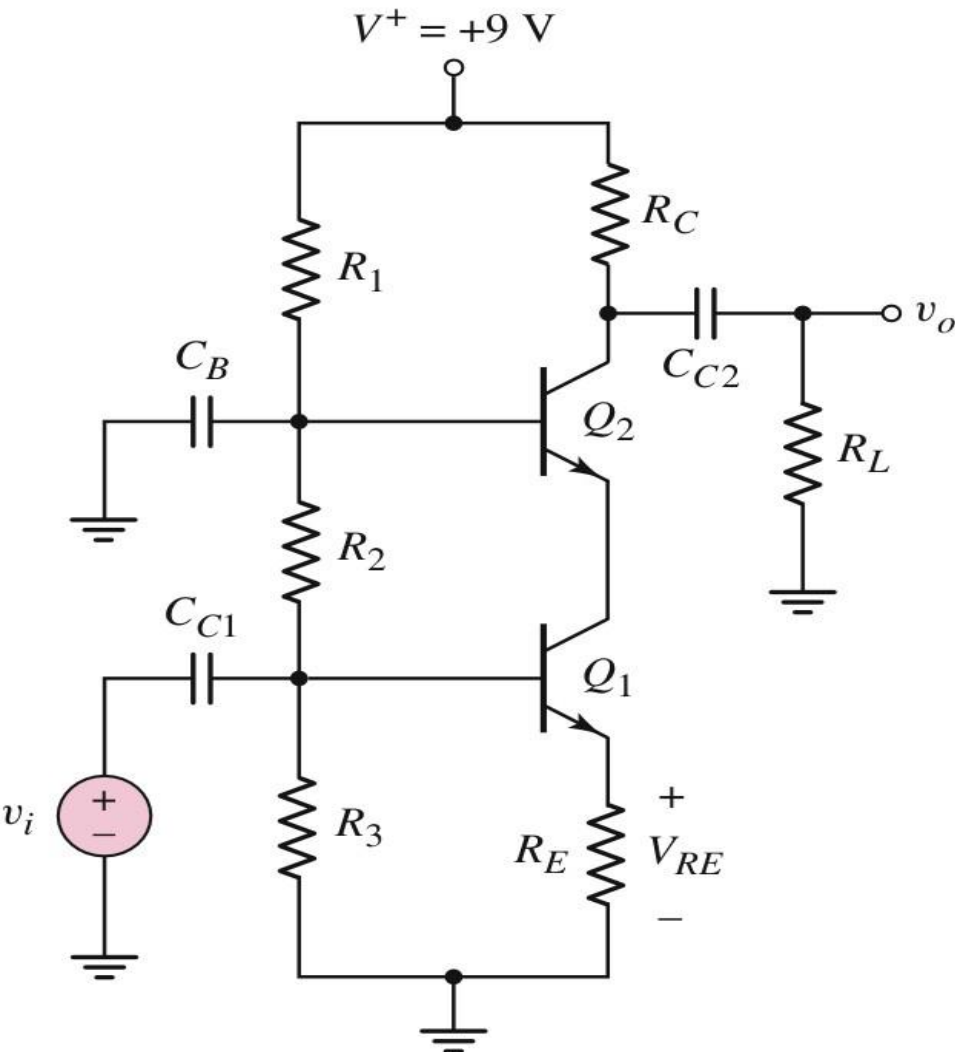

$$V_{CE1} = V_{CE2} = 2.5\text{V}$$

$$V_{RE} = 0.7\text{V}$$



$$I_{C1} = I_{C2} = 1\text{mA}$$

$$I_{R1} = I_{R2} = I_{R3} = 0.1\text{mA}$$

Design the circuit


**Cascode** Transistor Circuit

# Cascode

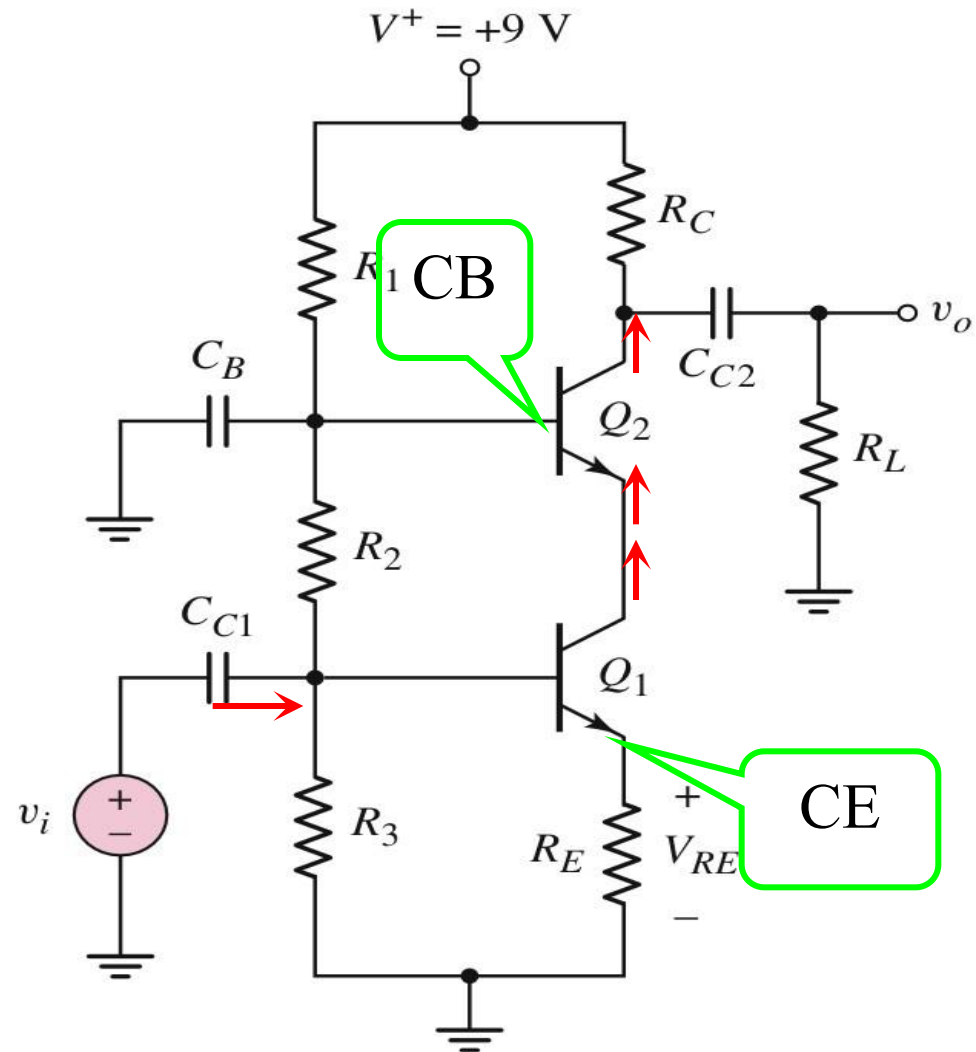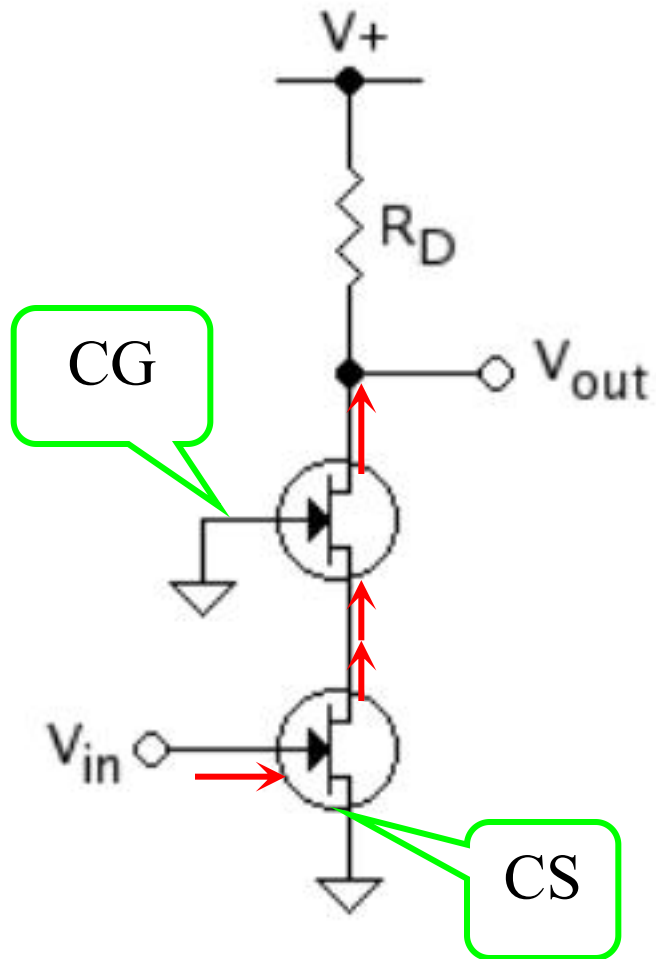


# Simulation Homework

Ckt A

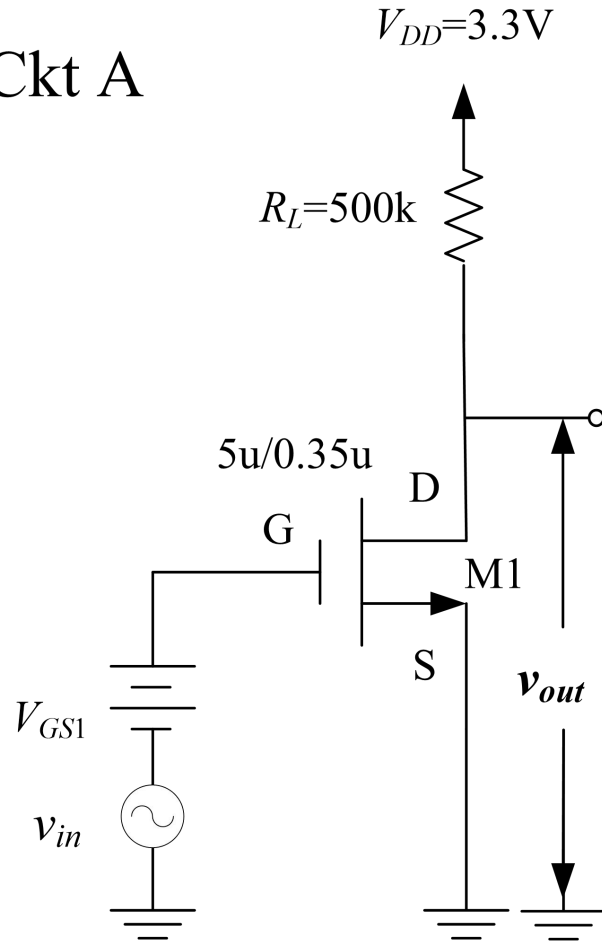


Ckt B

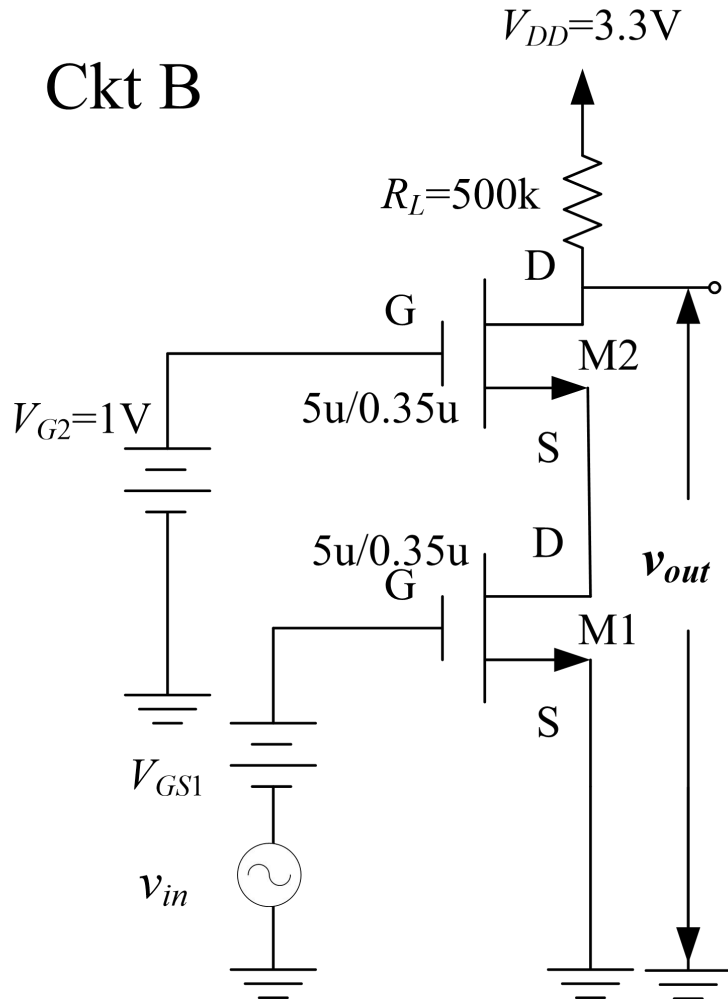

Comparing the I-V Curves of the Two Amplifiers.

## 5.5 Multistage Circuits

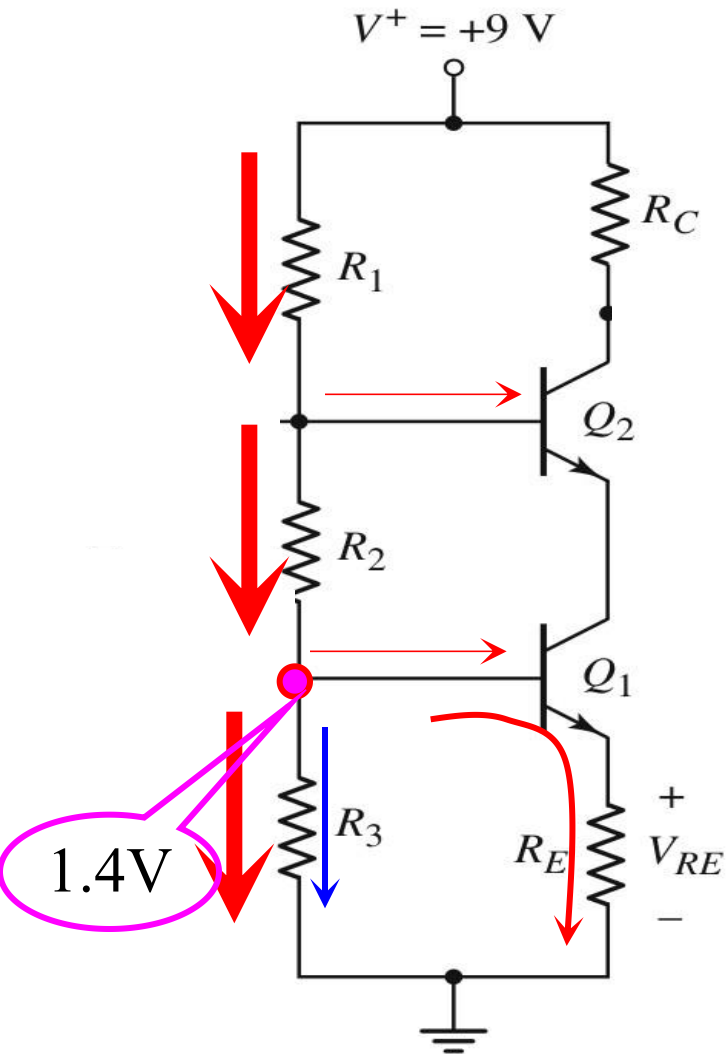

$$V_{CE1} = V_{CE2} = 2.5V$$

$$V_{RE} = 0.7V$$

$$I_{C1} = I_{C2} = 1mA$$

$$I_{R1} = I_{R2} = I_{R3} = 0.1mA$$

## Design the circuit


$$I_{Bias} = I_{R1} = I_{R2} = I_{R3} = 0.1mA$$

$$R_1 + R_2 + R_3 = \frac{V^+}{I_{Bias}} = \frac{9}{0.10} = 90k\Omega$$

$$V_{RE} = 0.7V$$

$$V_{\text{BE(on)}} = 0.7V$$

## 5.5 Multistage Circuits

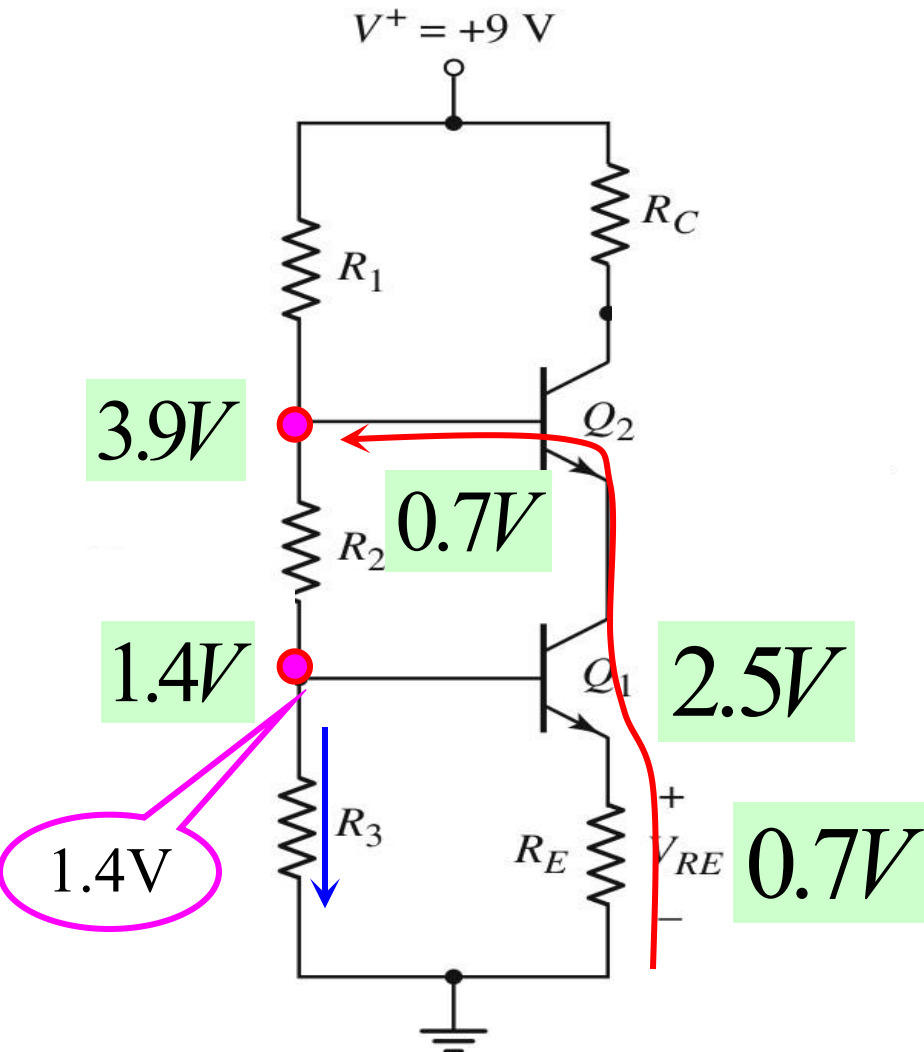

$$V_{CE1} = V_{CE2} = 2.5\text{V}$$

$$V_{RE} = 0.7\text{V}$$

$$I_{C1} = I_{C2} = 1\text{mA}$$

$$I_{R1} = I_{R2} = I_{R3} = 0.1\text{mA}$$


Design the circuit

$$R_3 = \frac{1.4\text{V}}{0.1\text{mA}} = 14\text{k}\Omega$$

$$R_2 = \frac{3.9\text{V} - 1.4\text{V}}{0.1\text{mA}} = 25\text{k}\Omega$$

$$R_1 = 90 - 25 - 14 = 51\text{k}\Omega$$

## 5.5 Multistage Circuits

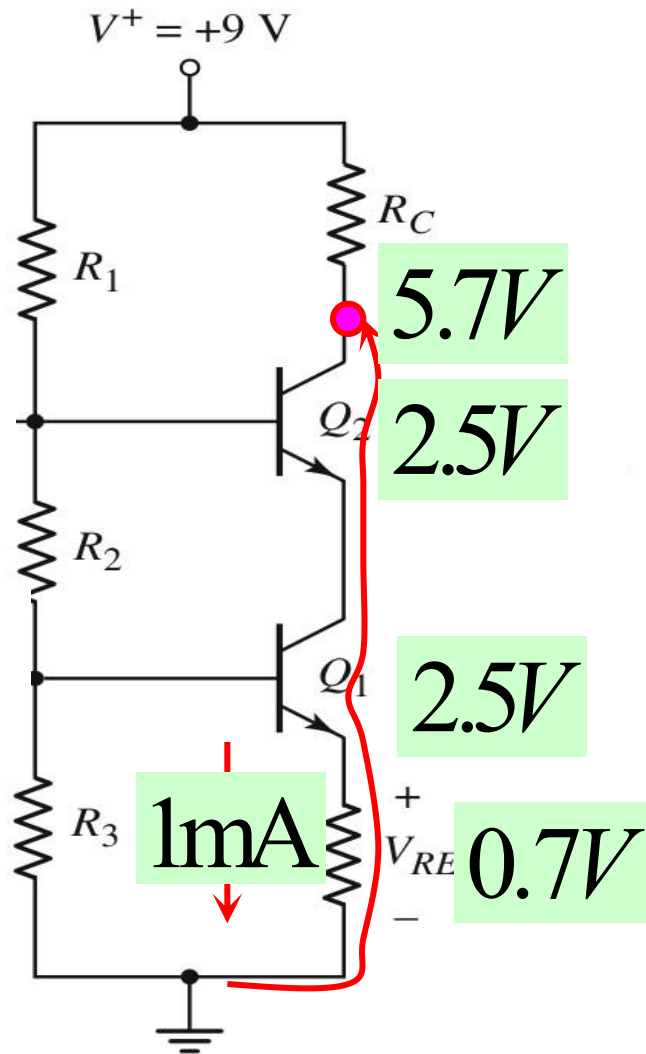

$$V_{CE1} = V_{CE2} = 2.5V$$

$$V_{RE} = 0.7V$$

$$I_{C1} = I_{C2} = 1mA$$


$$I_{R1} = I_{R2} = I_{R3} = 0.1mA$$

Design the circuit

$$R_E = \frac{0.7V}{1mA} = 0.7k\Omega$$

$$R_C = \frac{9 - 5.7}{1mA} = 3.3k\Omega$$

## 5.5 Multistage Circuits

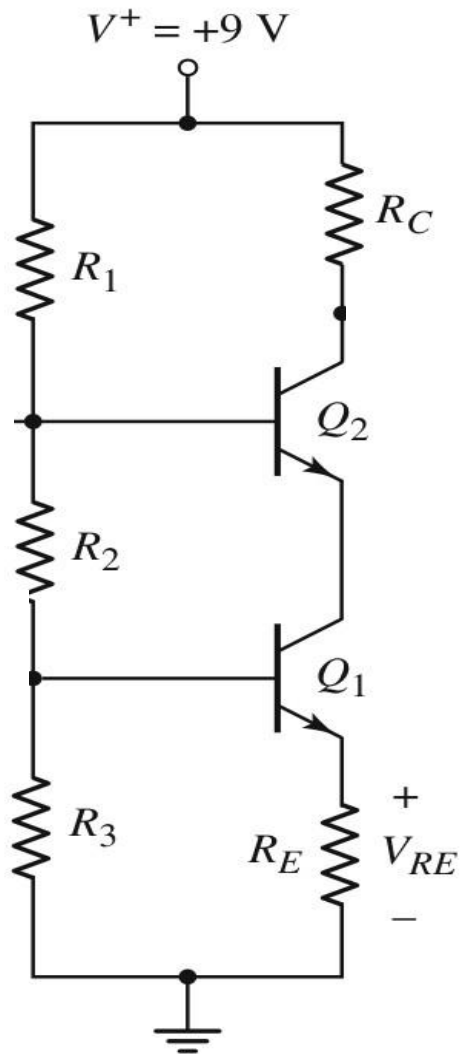

$$V_{CE1} = V_{CE2} = 2.5V$$


$$V_{RE} = 0.7V$$

$$I_{C1} = I_{C2} = 1mA$$

$$I_{R1} = I_{R2} = I_{R3} = 0.1mA$$

Design the circuit

## 5.7 Summary

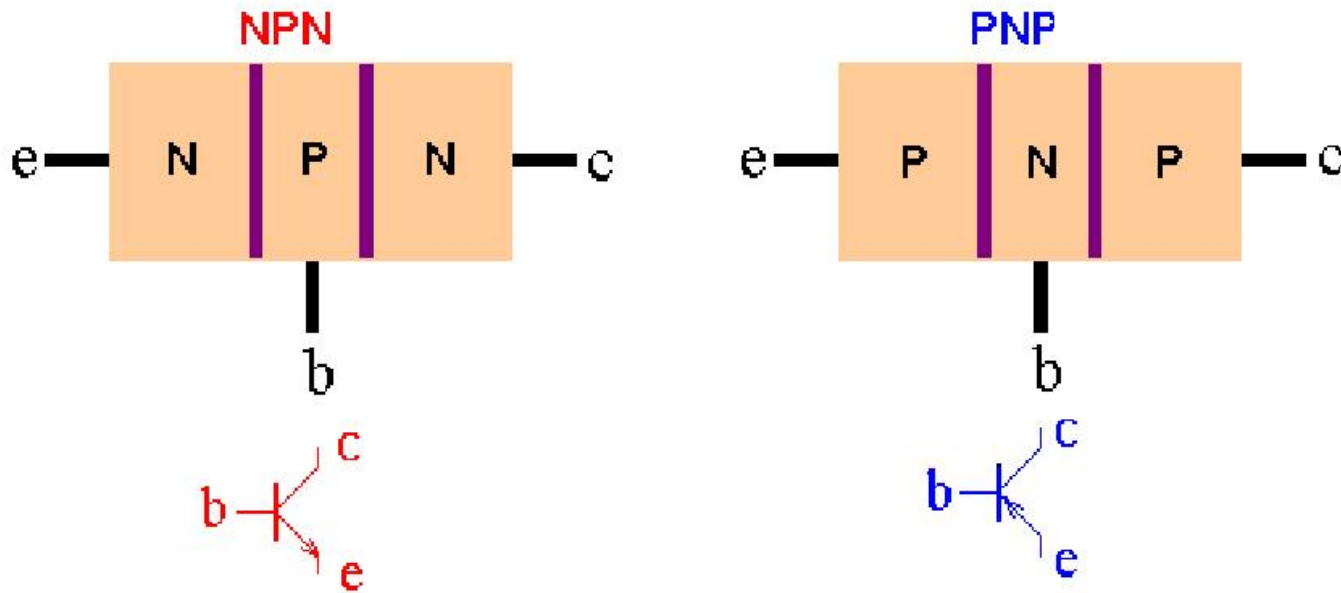

Three  
regions:

Three  
terminals

Two *pn* junctions:




## 5.7 Summary

### Modes of Operation


<b>Modes</b>	<b>EBJ</b>	<b>CBJ</b>
<b>Cutoff</b>	<b>Reverse</b>	<b>Reverse</b>
<b>Saturation</b>	<b>Forward</b>	<b>Forward</b>
<b>Active</b>	<b>Forward</b>	<b>Reverse</b>

## 5.7 Summary

### DC Equivalent Circuit

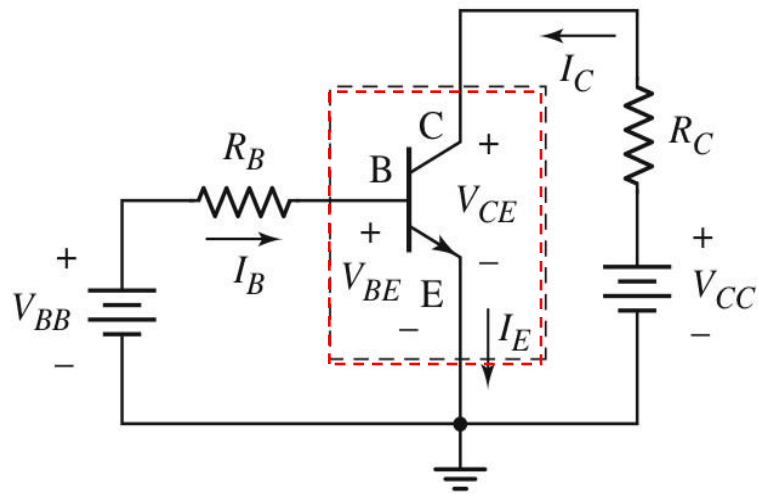

(a)

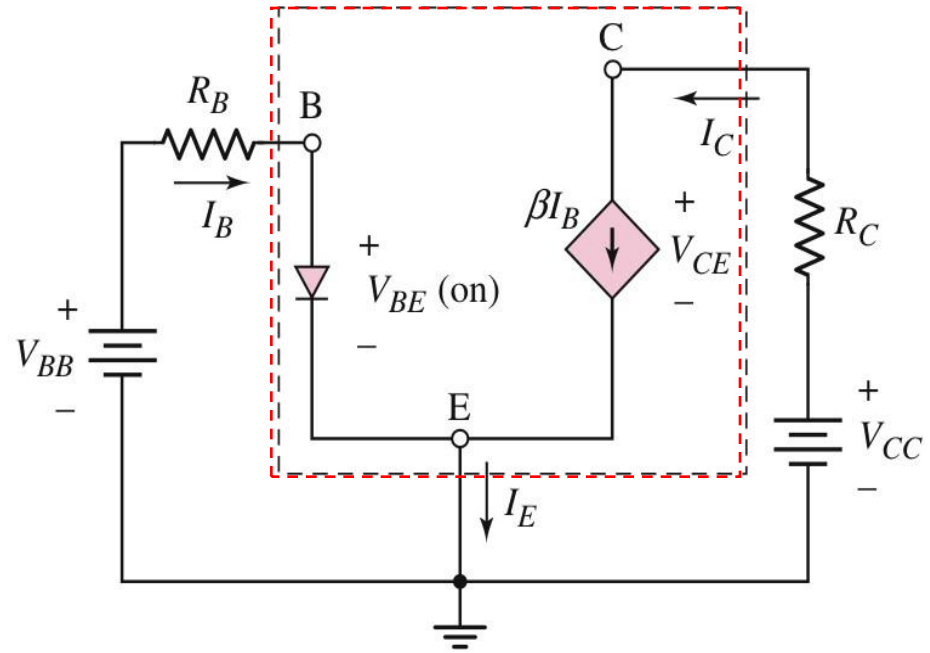

(b)

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.

### Common Emitter Circuit

# 5.7 Summary

