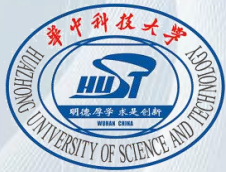


Huazhong University
of Science & Technology

Electronic Circuit of Communications

School of Electronic Information
and Communications

Jiaqing Huang



Stability of Oscillator

Stability of Oscillator

➤ Frequency Accuracy:

Difference between practical frequency f and f_0

$$\left\{ \begin{array}{ll} \text{Absolute Accuracy} & \Delta f = |f - f_0| \\ \text{Relative Accuracy} & \frac{\Delta f}{f_0} = \frac{|f - f_0|}{f_0} \end{array} \right.$$

➤ Frequency Stability δ

During Δt , the max value Δf_{max} of frequency accuracy

$$\delta = \left. \frac{\Delta f_{max}}{f_0} \right|_{t=\Delta t}$$

Stability of Oscillator

Active devices, quartz crystals...

- Long-term Stability:
 ≥ 1 day to several months

- Short-term Stability:
 < 1 day

Temperature, power supply, circuit

- Instantaneous Stability:
s or ms

Phase noise

Internal noise

Frequency Stability Factors

➤ Oscillator Parameters


$$\left\{ \begin{array}{l} \text{Frequency} \quad \omega_0 \approx \frac{1}{\sqrt{LC}} \\ \text{Relative Change} \quad \frac{\Delta\omega_0}{\omega_0} = -\frac{1}{2} \left(\frac{\Delta L}{L} + \frac{\Delta C}{C} \right) \end{array} \right.$$

➤ Q

$Q \uparrow$ Same $\Delta\varphi \rightarrow \Delta\omega \downarrow$

➤ Active Device Parameter

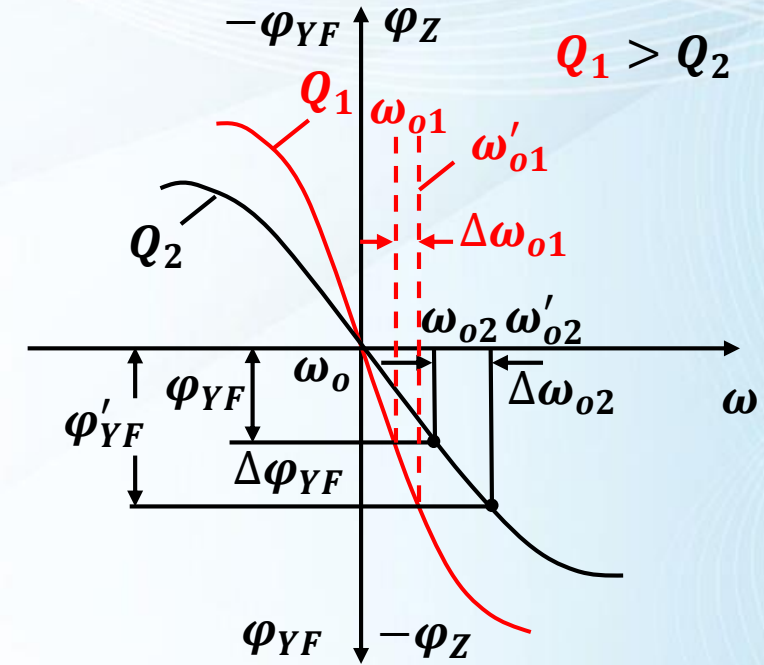- Δh Δh_i of Active Devices
- External Factors (For Example, Power Supply, Temperature, Humidity)



Frequency Stability Methods

1. Remove External Factors

(1) Temperature:

- Constant Temperature Box
- Far Away from Heat Source
- L 、 C with Positive/Negative Temperature Coefficient,
Compensate ΔL 、 ΔC

(2) Power Supply:

- 2nd Regulated Power Supply
- Independent Power Supply

(3) Humidity & Atmospheric Pressure: Seal

(4) Magnetic Field Induction: Shield

(5) Mechanical Vibration: Robber Absorber

Frequency Stability Methods

1. Remove External Factors

(6) Decrease Influence of Load

- Buffer between Oscillator & Load (Emitter Follower),
Increase Q
- Low-Impedance Output (Emitter Follower)
- Loose Coupling (with Small Capacitor)
- Clapp & Seiler Circuit

Frequency Stability Methods


1. Remove External Factors


2. Increase Standard

Decrease ΔL and ΔC

3. Decrease φ_{YF} and $\Delta\varphi_{YF}$

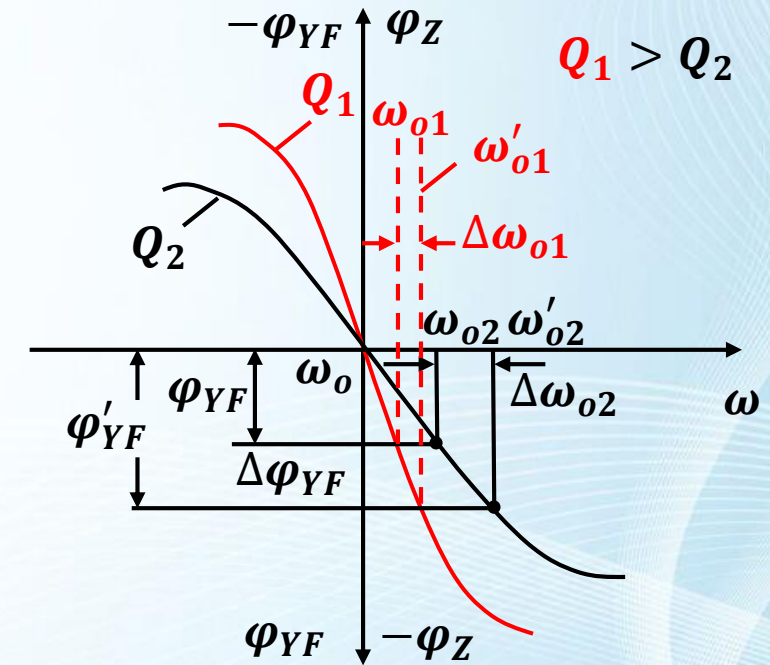Example: Capacitive Feedback Oscillator
to decrease φ_{YF}



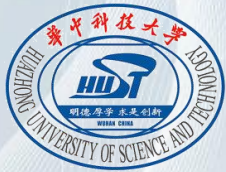


Quartz Crystal Oscillator


Quartz Crystal



(a) Symbol

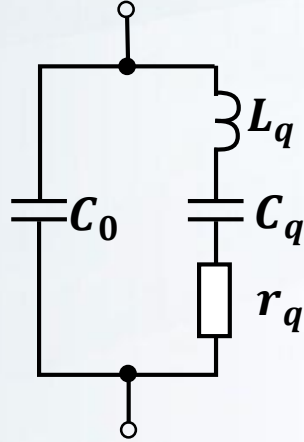

(b) Basic Frequency
($C_q \ll C_0$)

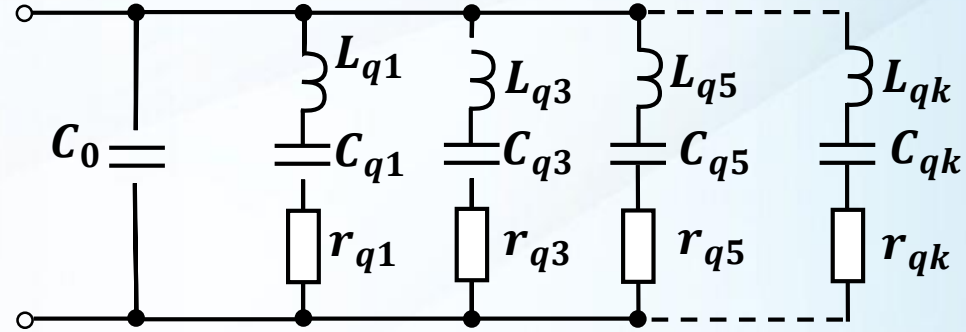

(c) Complete Equivalent Circuit

➤ Multi-harmonic Crystal


➤ Basic Frequency

➤ Overtone Frequency → Odd Harmonic Frequency


Quartz Crystal - Equivalent Circuit



(a) Symbol

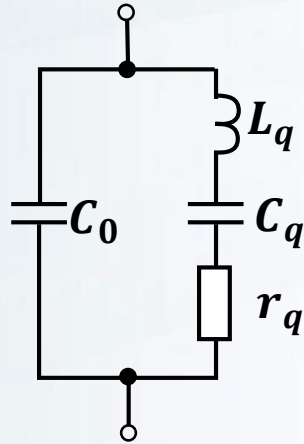

(b) Basic Frequency
($C_q \ll C_o$)

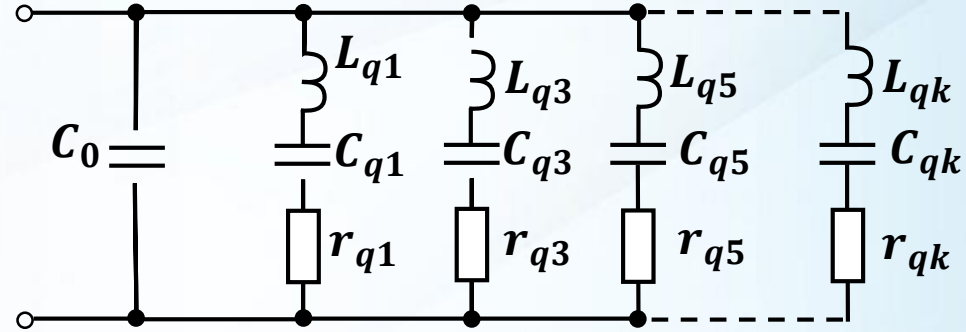


(c) Complete Equivalent Circuit


➤ $Q = \frac{1}{r_q} \sqrt{\frac{L_q}{C_q}} = \frac{1}{r_q} \rho$ Huge (L_q very big, C_q & r_q very small)

➤ $p = C_q / (C_o + C_q)$ Tiny ($C_q \ll C_o$)

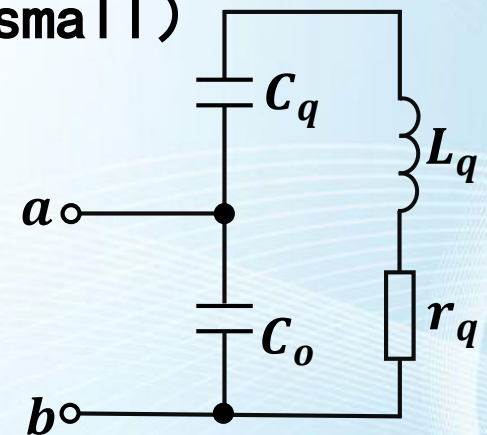
→ little effect on quartz crystal circuit



Quartz Crystal – Frequency

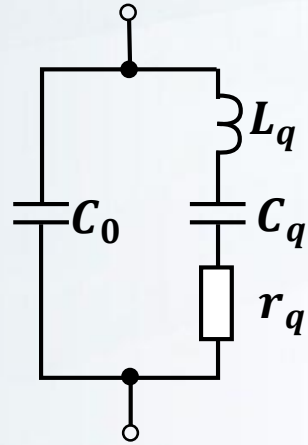

(b) Basic Frequency
($C_q \ll C_o$)

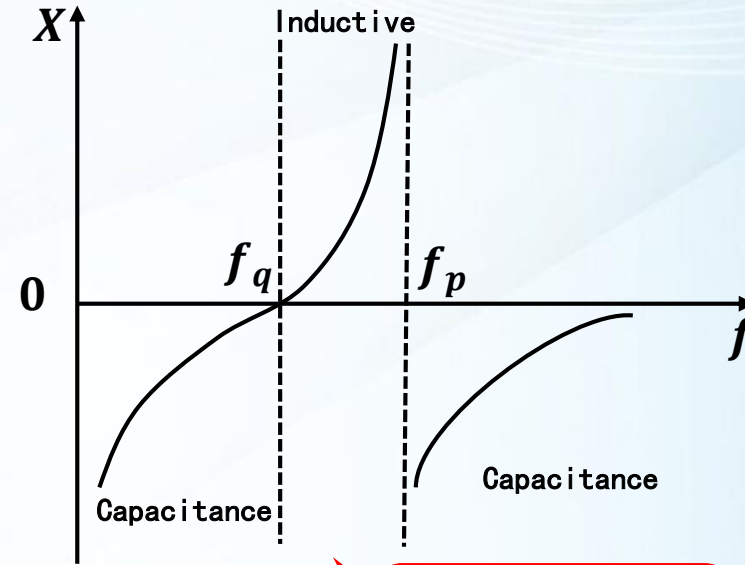

$f_p \approx f_q$
Narrow

➤ Equivalent Circuit Frequency


Series Resonance Frequency:

$$f_q = \frac{1}{2\pi\sqrt{L_q C_q}}$$

Parallel Resonance Frequency:

$$f_p = \frac{1}{2\pi\sqrt{L_q \frac{C_q C_0}{C_0 + C_q}}} = \frac{f_q}{\sqrt{\frac{C_0}{C_0 + C_q}}} = f_q \sqrt{1 + \frac{C_q}{C_0}}$$

Quartz Crystal - Stable Frequency

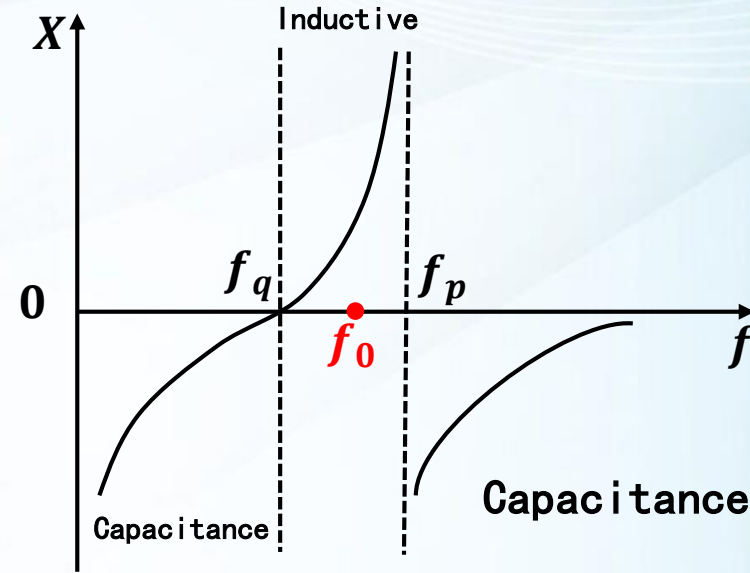

➤ $f_q \sim f_p$ inductive range:



➤ **Sharp** curve, very big slope: $f_0 \uparrow \rightarrow \text{Equivalent } L \uparrow$

➤ $f_0 = \frac{1}{2\pi\sqrt{LC}} :$


$L \uparrow \rightarrow f_0 \downarrow$


Nominal Frequency f_N with C_L

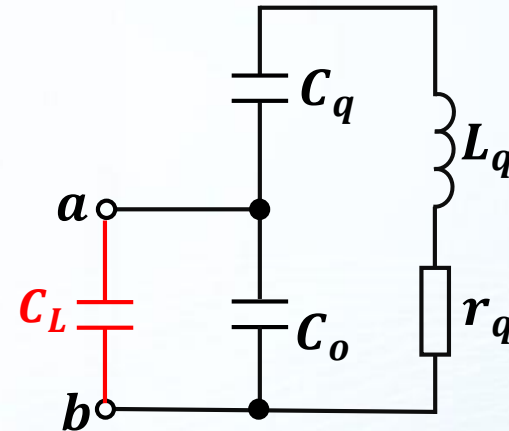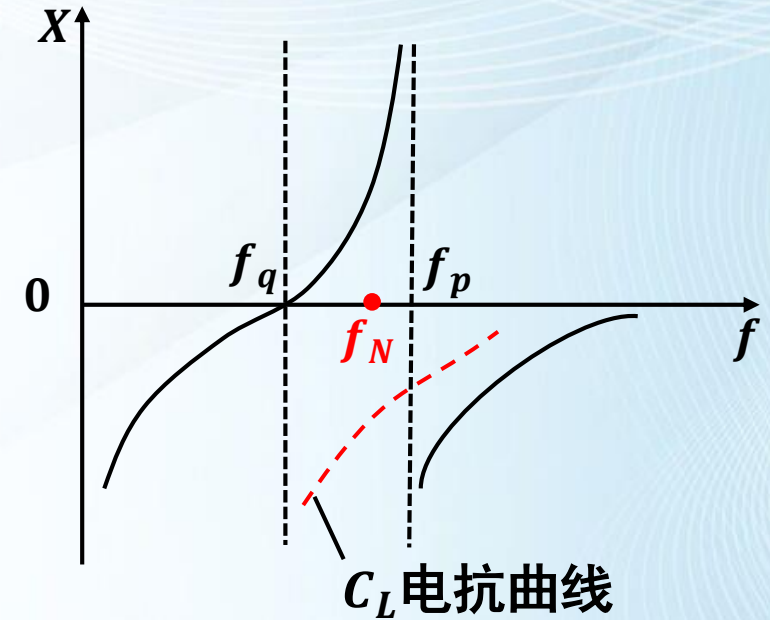- Nominal Frequency f_N
 - With Load Capacitor C_L
- Load Capacitor C_L
 - Equivalent Capacitance between ab
 - C_L curve - red dashed line




Oscillators Classification

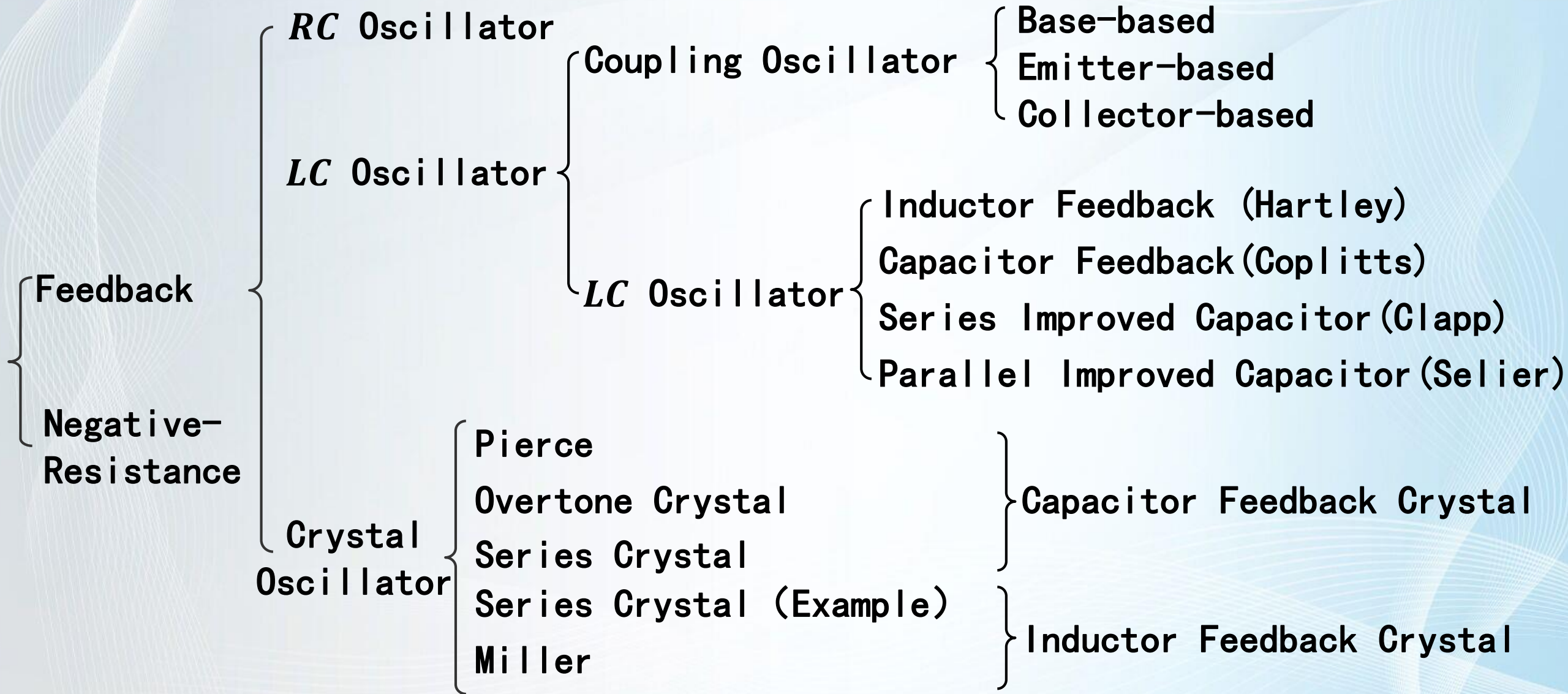

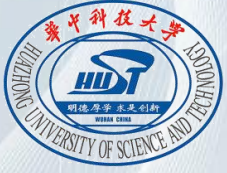



Pierce Oscillator

Oscillators Classification

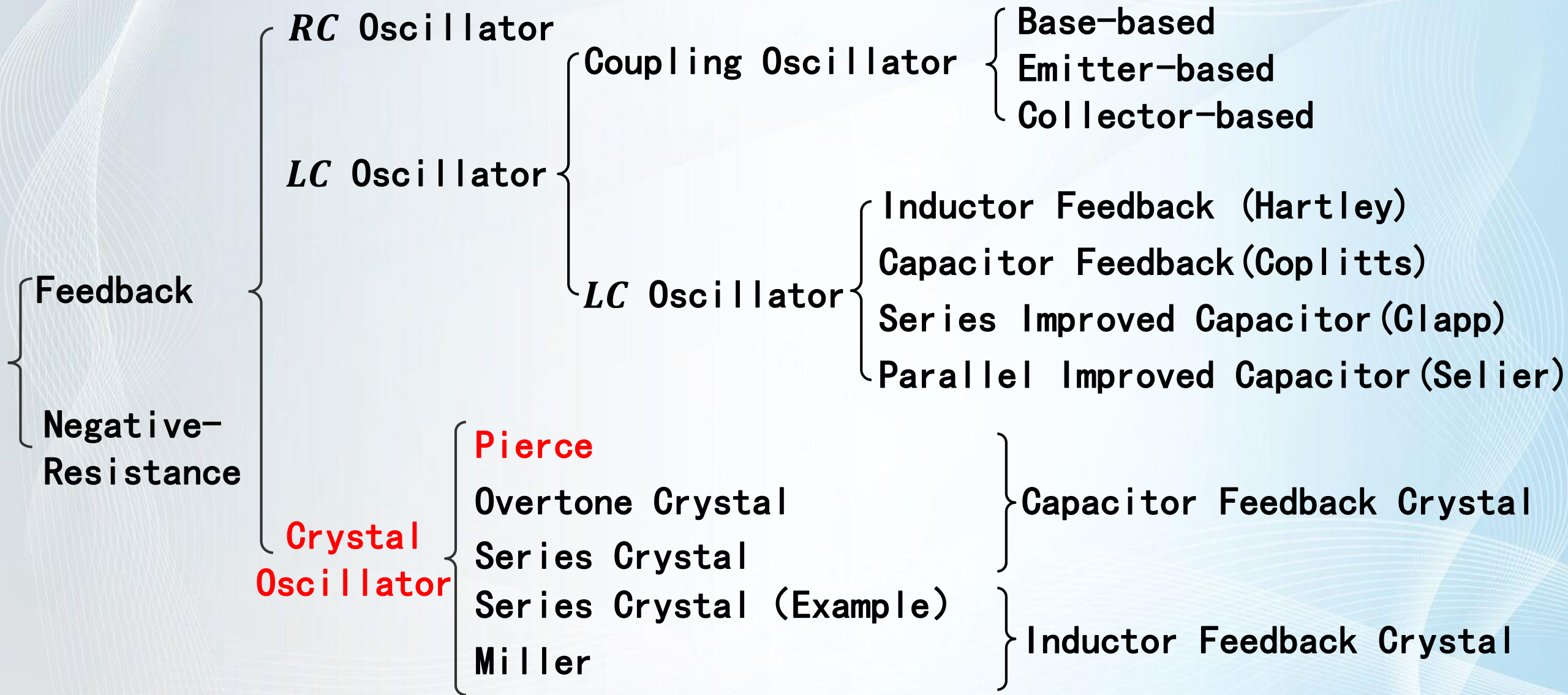

Pierce Oscillator

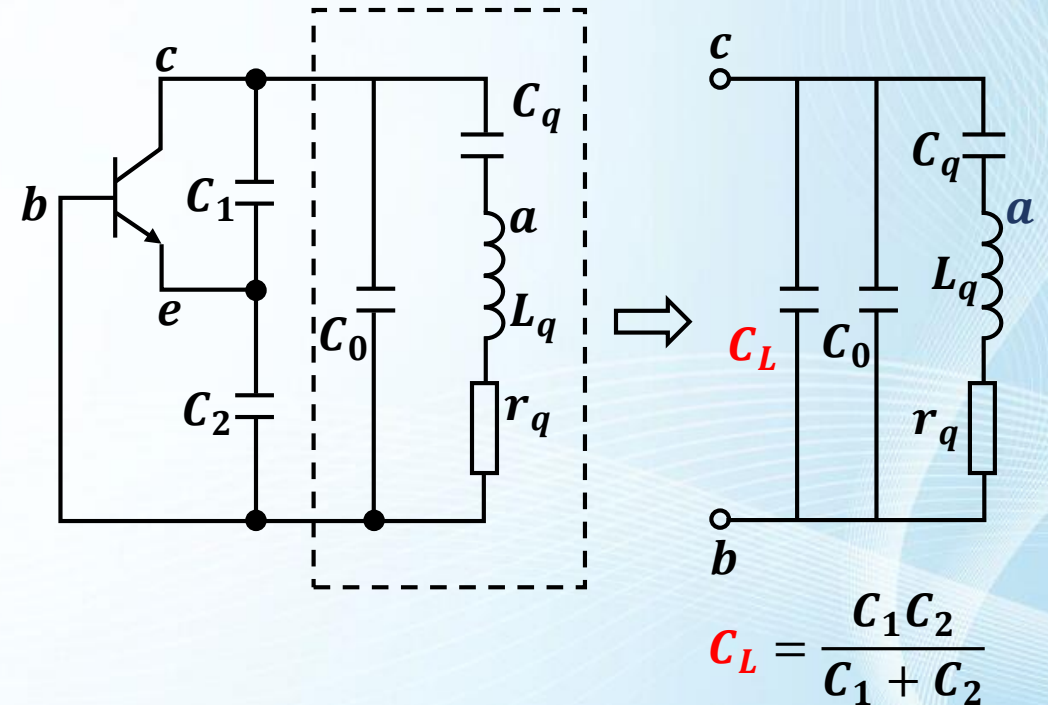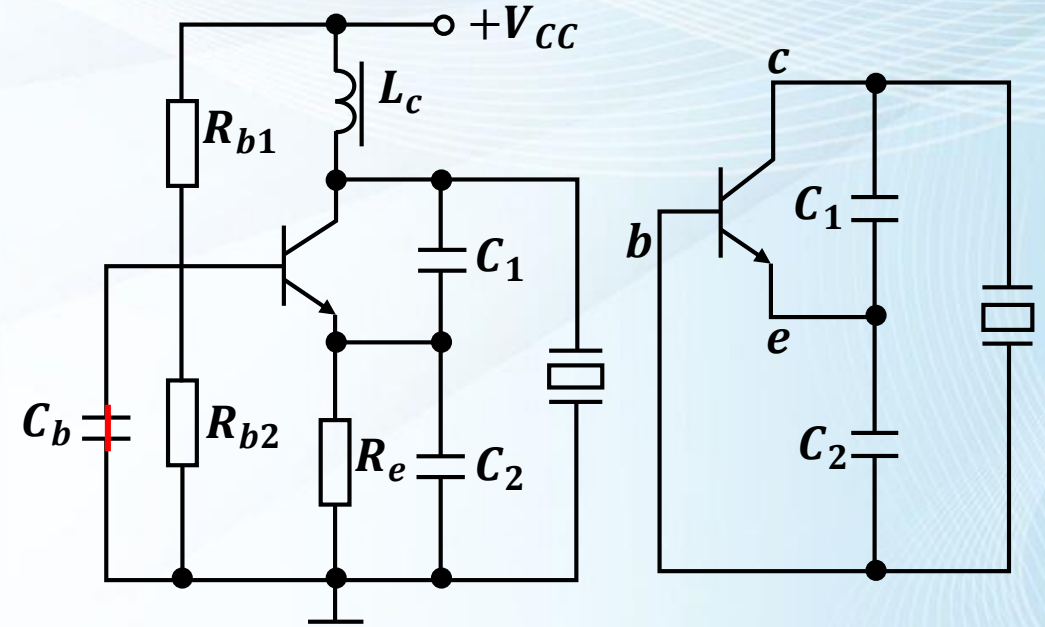- RF AC Equivalent Circuit Principle
 - Resistor Open: R_{b1} 、 R_{b2} 、 R_e
 - Inductor Open: RF Choke L_c
 - Capacitor Short:
 - Bypass Capacitor: None
 - Coupling Capacitor: C_b
 - Power Filter Capacitor: None



Pierce Oscillator

(1) Weak Coupling


Access Factor:

$$p_{cb} = \frac{C_{ab}}{C_{cb}} = \frac{C_q}{C_q + (C_0 + C_L)}$$

$$\begin{cases} C_{ab} = \frac{C_q \cdot (C_0 + C_L)}{C_q + (C_0 + C_L)} \approx C_q \\ C_{cb} = (C_0 + C_L) \end{cases}$$

$$C_q + C_0 + C_L \gg C_q \Rightarrow p_{cb} \downarrow\downarrow, \text{ around } 10^{-4}$$

Stability $\uparrow\uparrow$

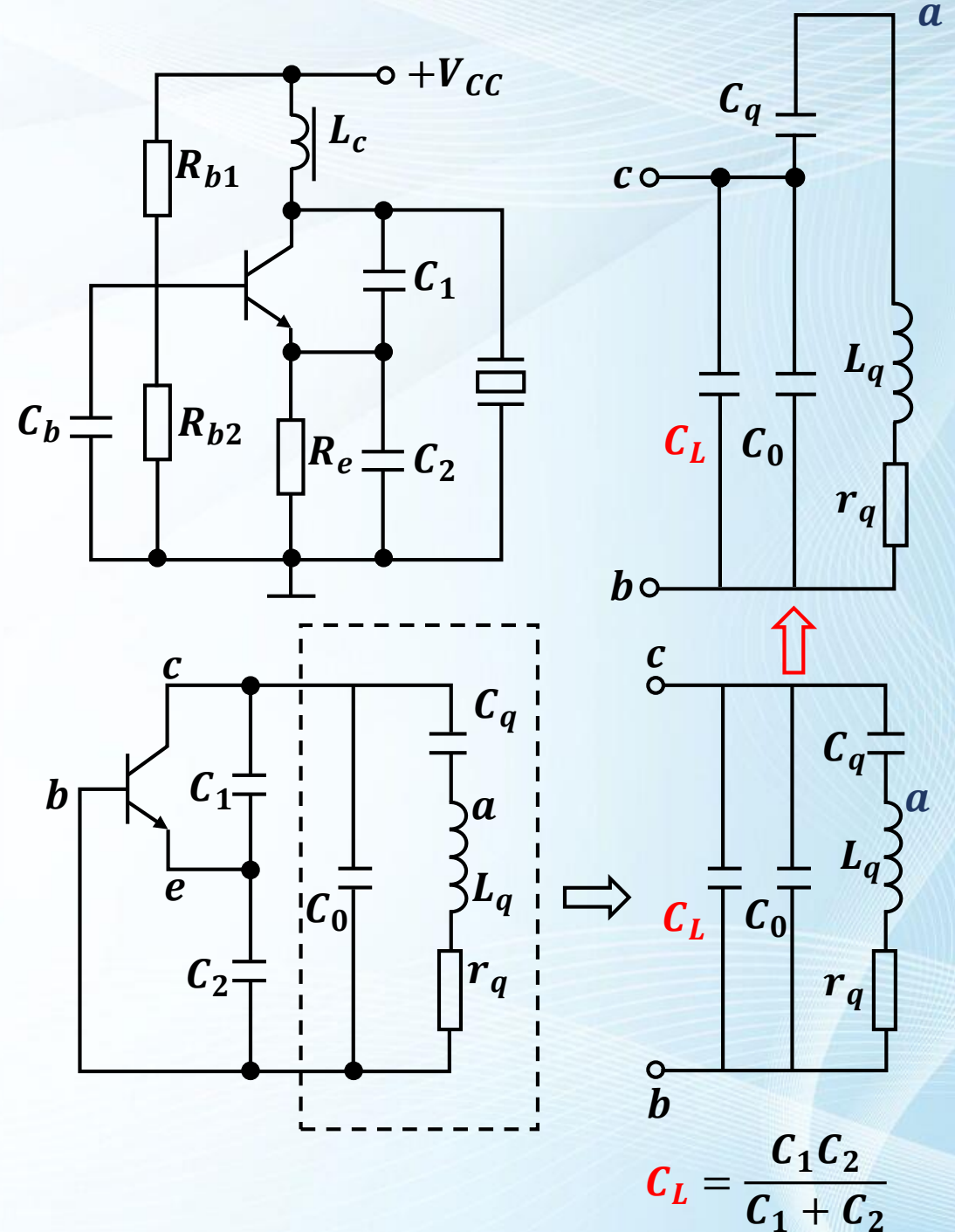

Pierce Oscillator


(2) f_0 determined by quartz crystal, which is stable

$$f_0 = \frac{1}{2\pi \sqrt{L_q \frac{C_q(C_0 + C_L)}{C_q + (C_0 + C_L)}}}$$

Load Capacitor $C_L = \frac{C_1 C_2}{C_1 + C_2}$


Note: outside crystal

$$C_L = \frac{C_1 C_2}{C_1 + C_2}$$

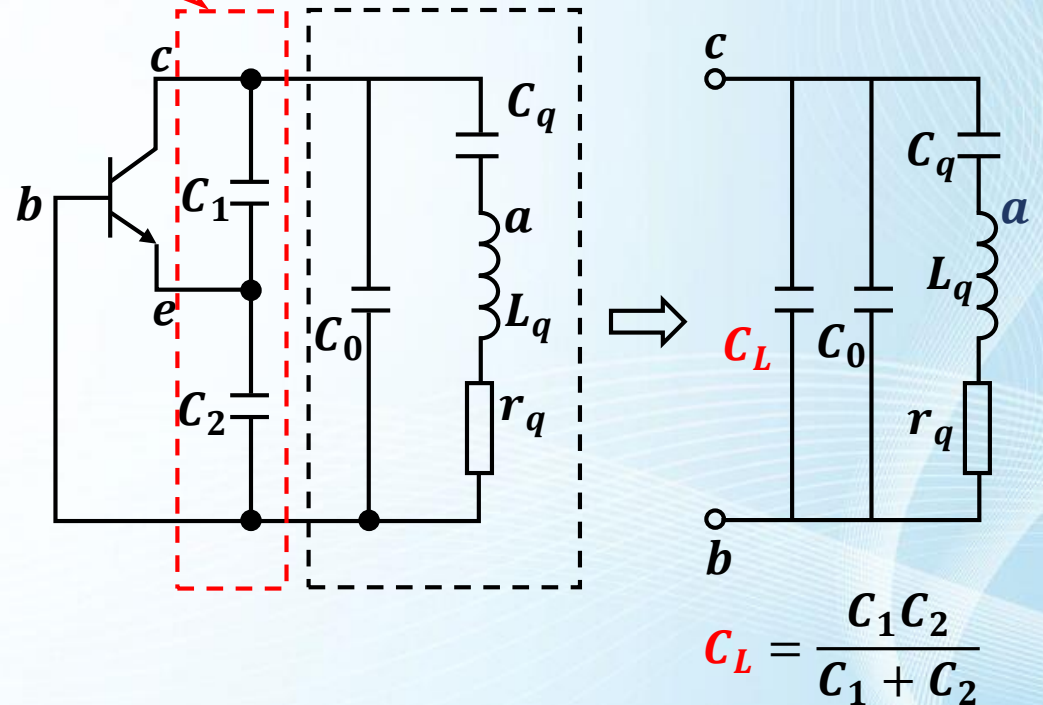

Pierce Oscillator

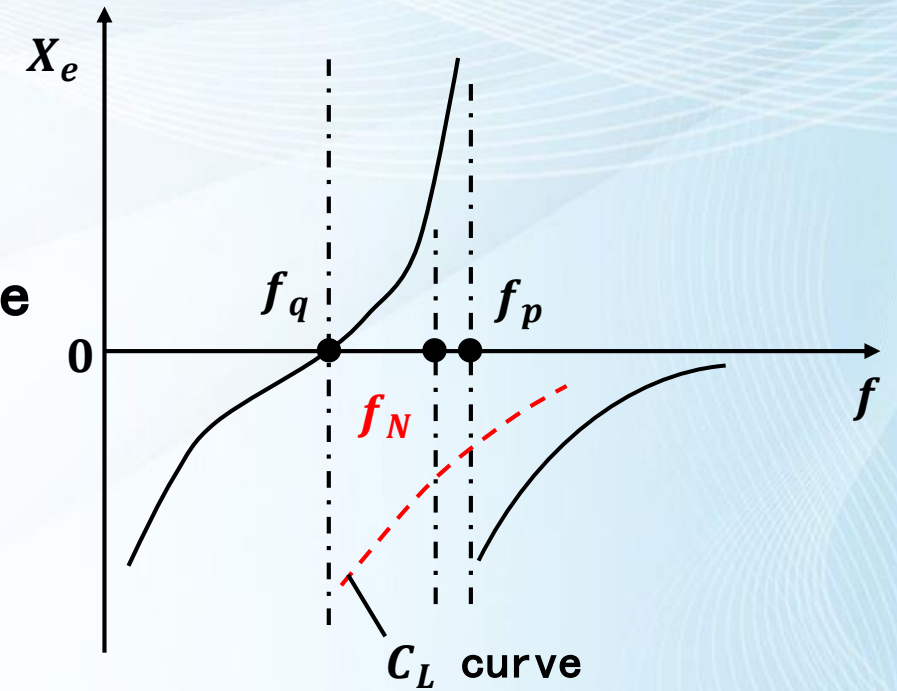
(3) $f_0 = f_N$, inductive, sharp curve, stable



(4) $Q \uparrow \uparrow \rho \uparrow \uparrow \rightarrow R_p \uparrow \uparrow (\geq 10^{10} \Omega)$


Even if access factor is very small, equivalent R_p is still big

→ Startup condition is easily satisfied

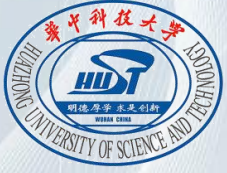


Miller Oscillator

Oscillators Classification

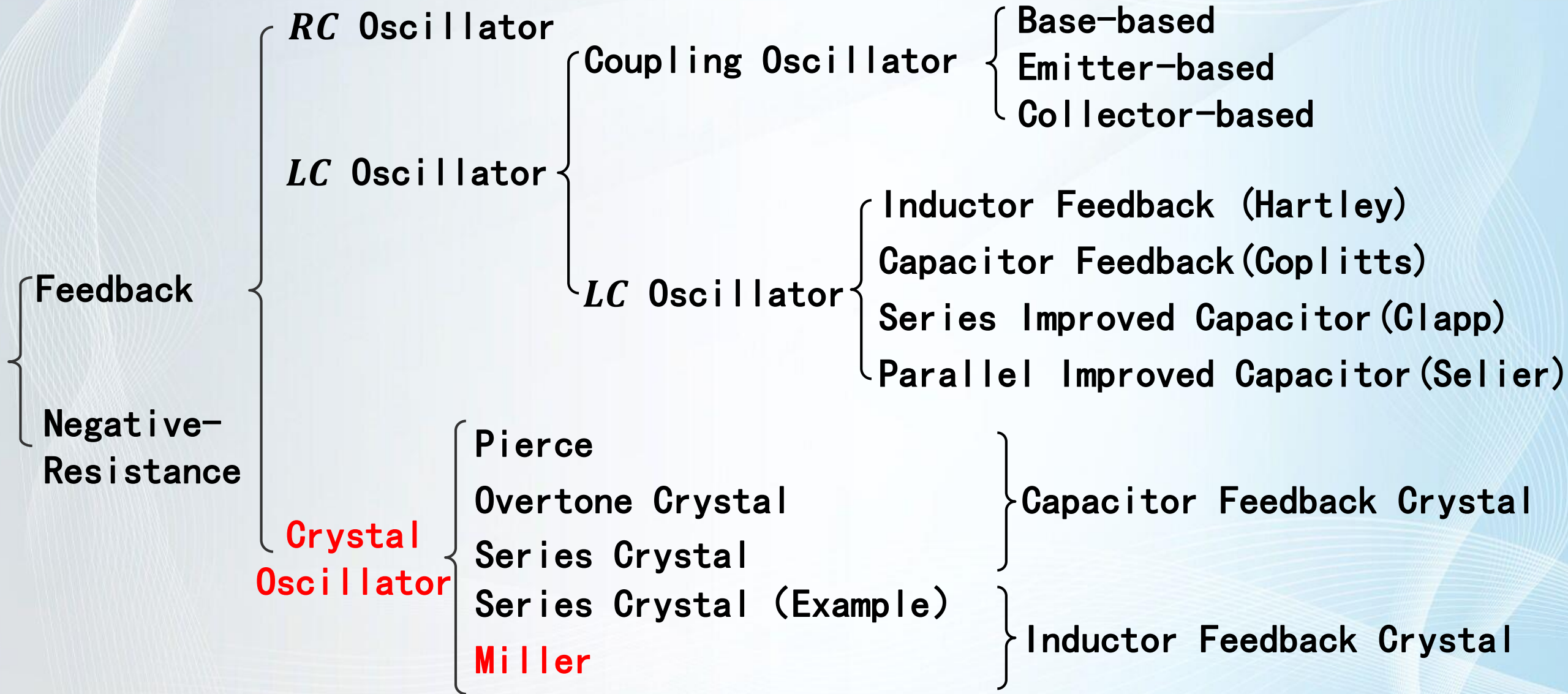


Miller Oscillator

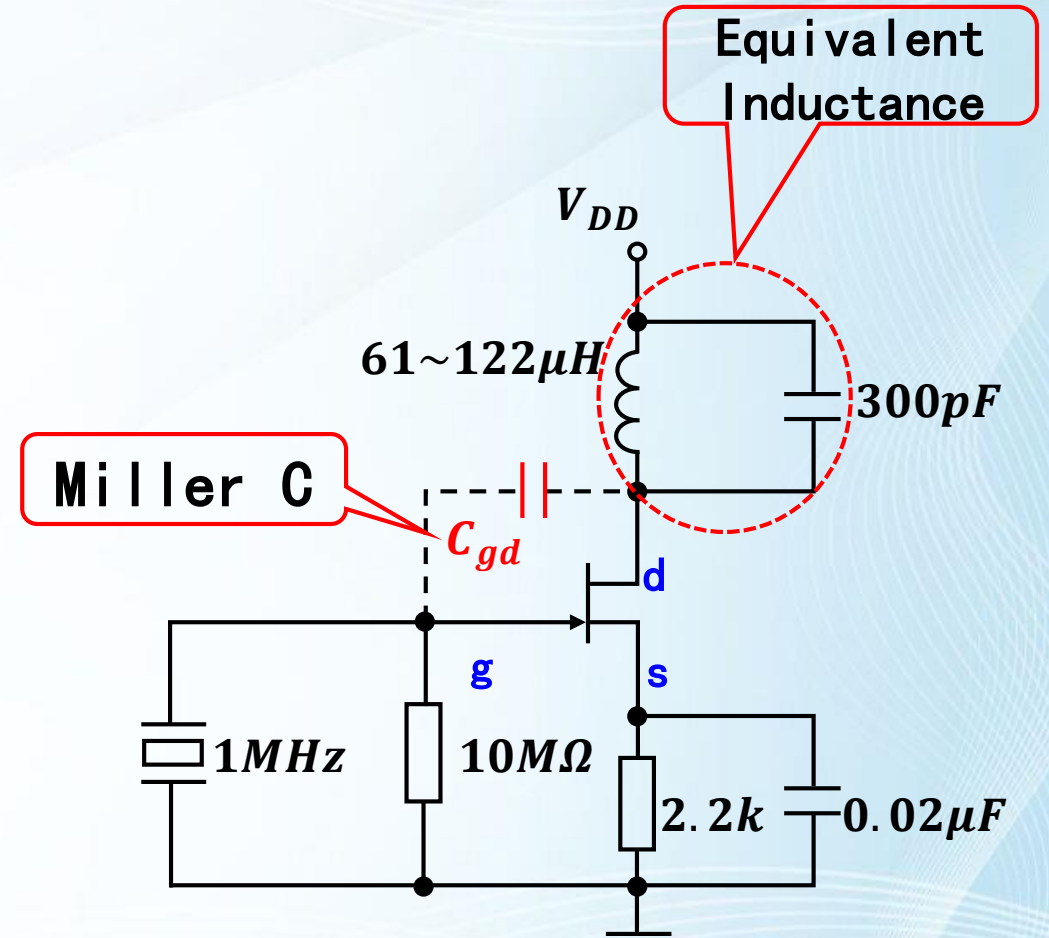- Inductance Feedback Oscillator
 - Crystal \rightarrow Inductor
 - LC Parallel Resonance \rightarrow Inductor
 - $C_{gd} \rightarrow$ Capacitor
- Reason using MOS FET:
 - R_i high, Stable




Miller Oscillator

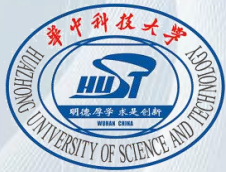

Overtone Crystal Oscillator

Oscillators Classification

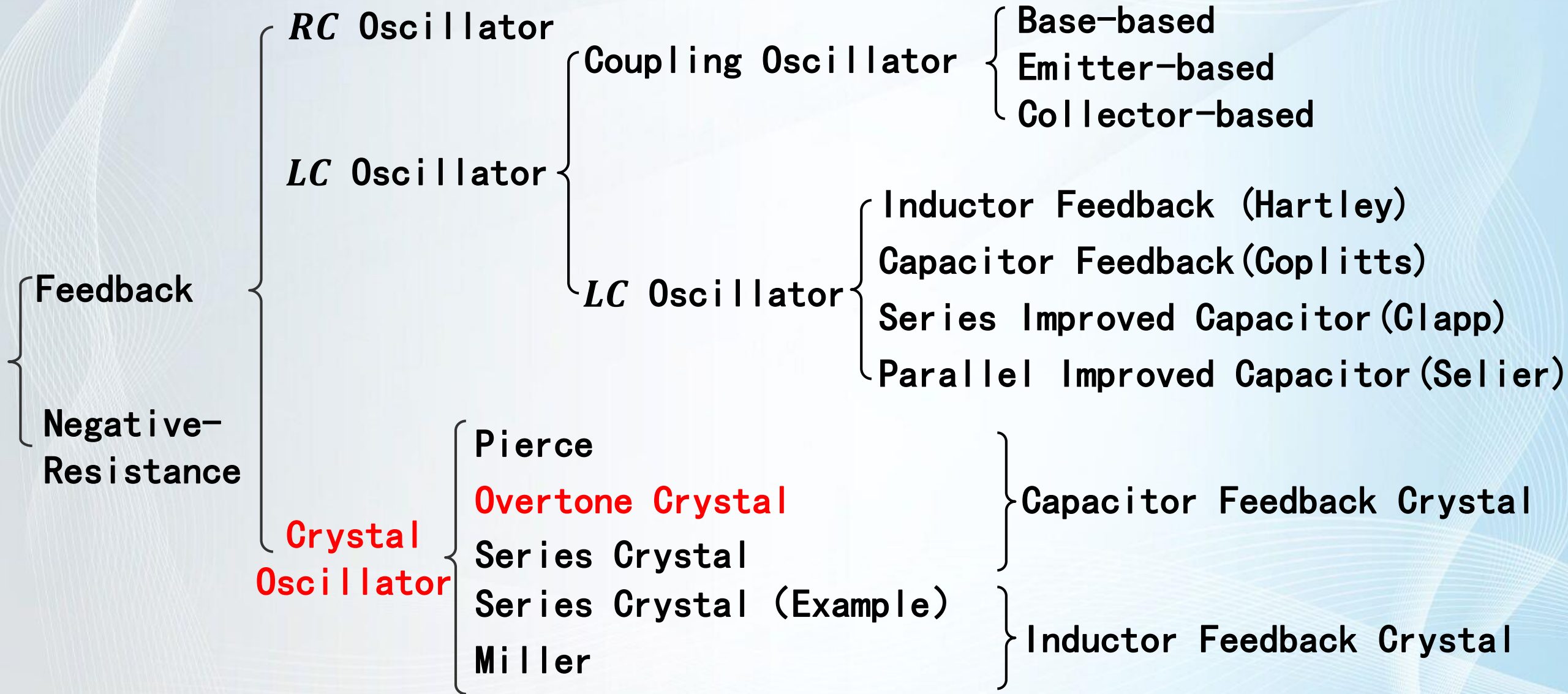



Overtone Crystal Oscillator

➤ C_2 Capacitive $\rightarrow LC_1$ Capacitive

✗ 1M & 3M Overtone: LC_1 Inductive \rightarrow no startup

✗ $\geq 7M$ Overtone: LC_1 Capacitive, Capacitance \downarrow , gain \downarrow , no startup

✓ 5MHz: LC_1 Capacitive, can startup

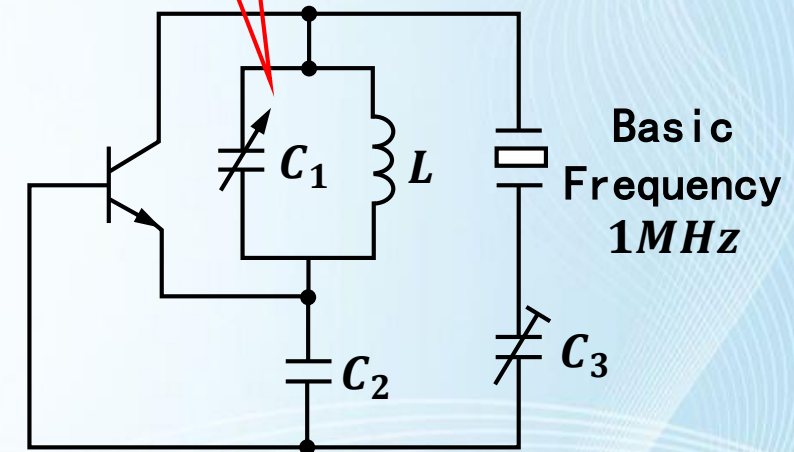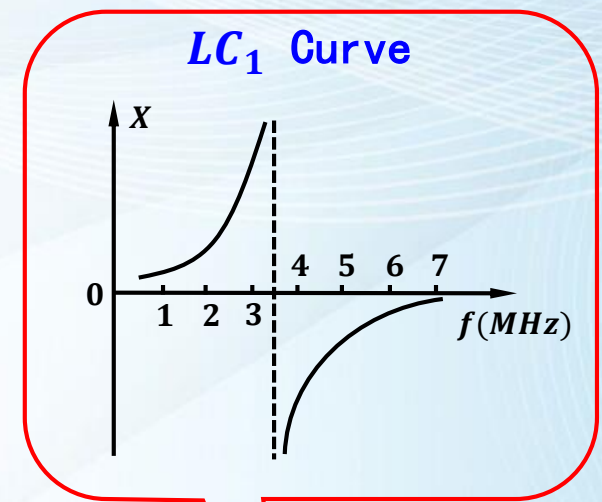


Overtone Crystal Oscillator





Series Crystal Oscillator

Oscillators Classification

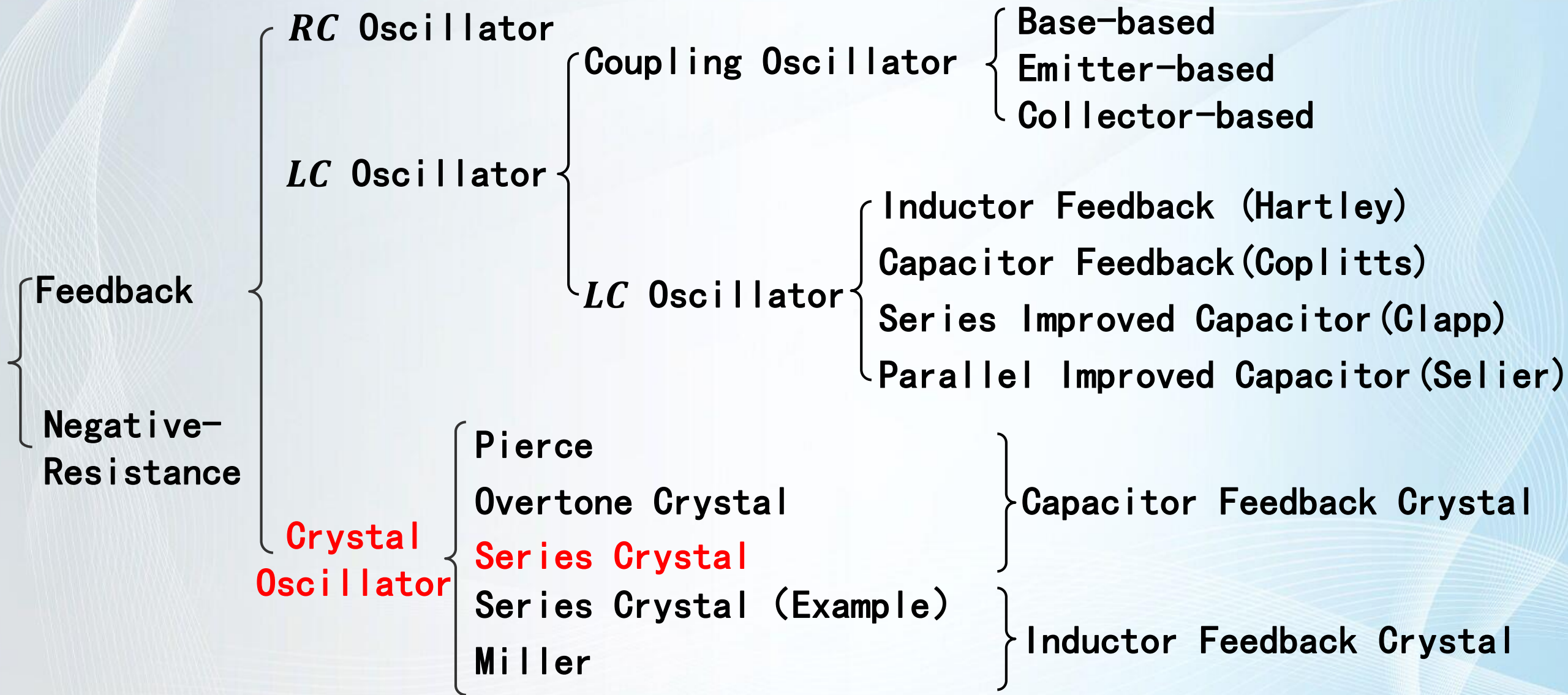

Series Crystal Oscillator

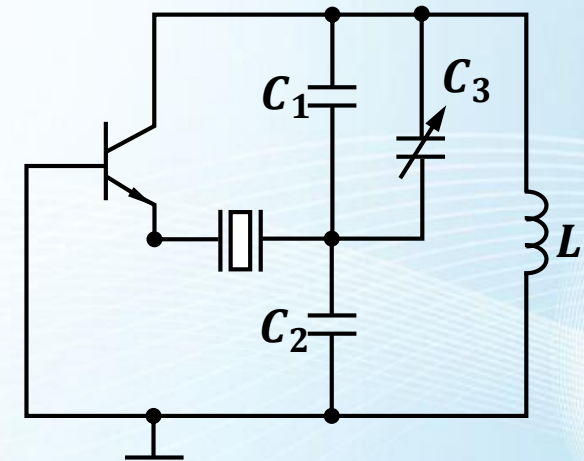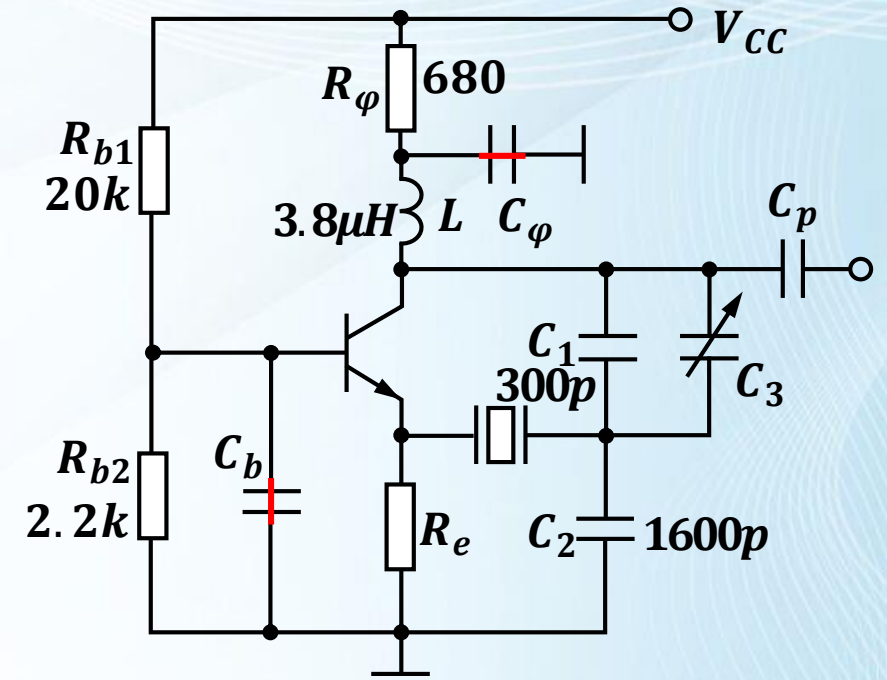- RF AC Equivalent Circuit Principle
 - Resistor Open: R_{b1} 、 R_{b2} 、 R_e 、 R_ϕ
 - Inductor Open: No RF Choke
 - Capacitor Short:
 - Bypass Capacitor: None
 - Coupling Capacitor: C_b
 - Power Filter Capacitor: C_ϕ





Series Crystal Oscillator

➤ Quartz Crystal: Short (f_q)

➤ Capacitive Feedback Oscillator


Q : Inductive Feedback Oscillator?

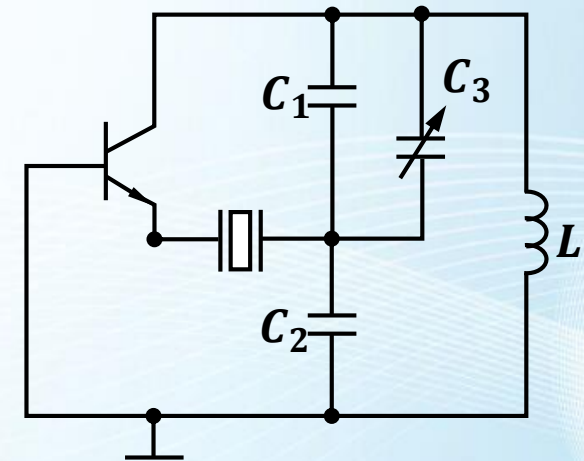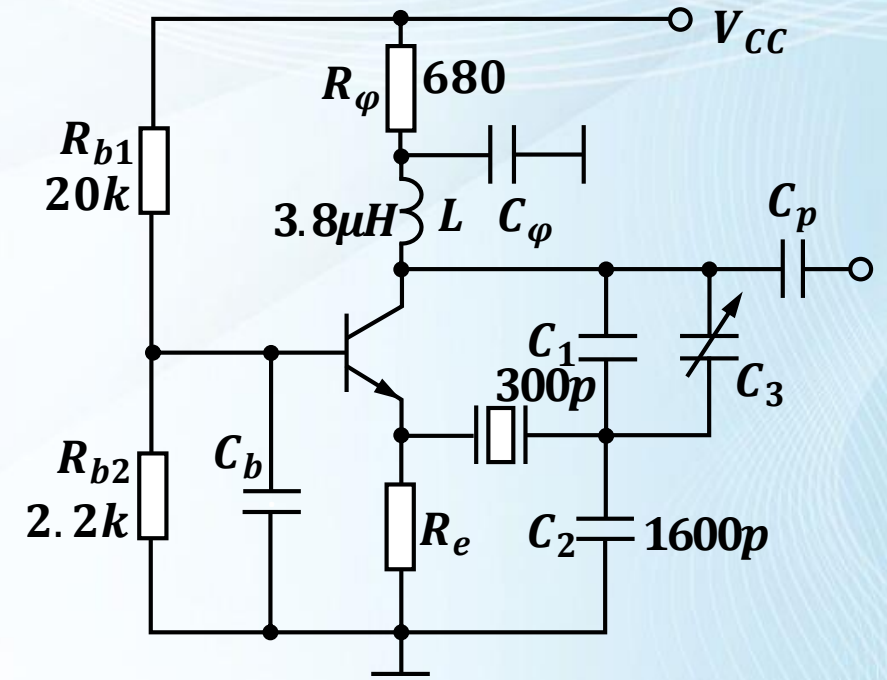



Example


Oscillators Classification

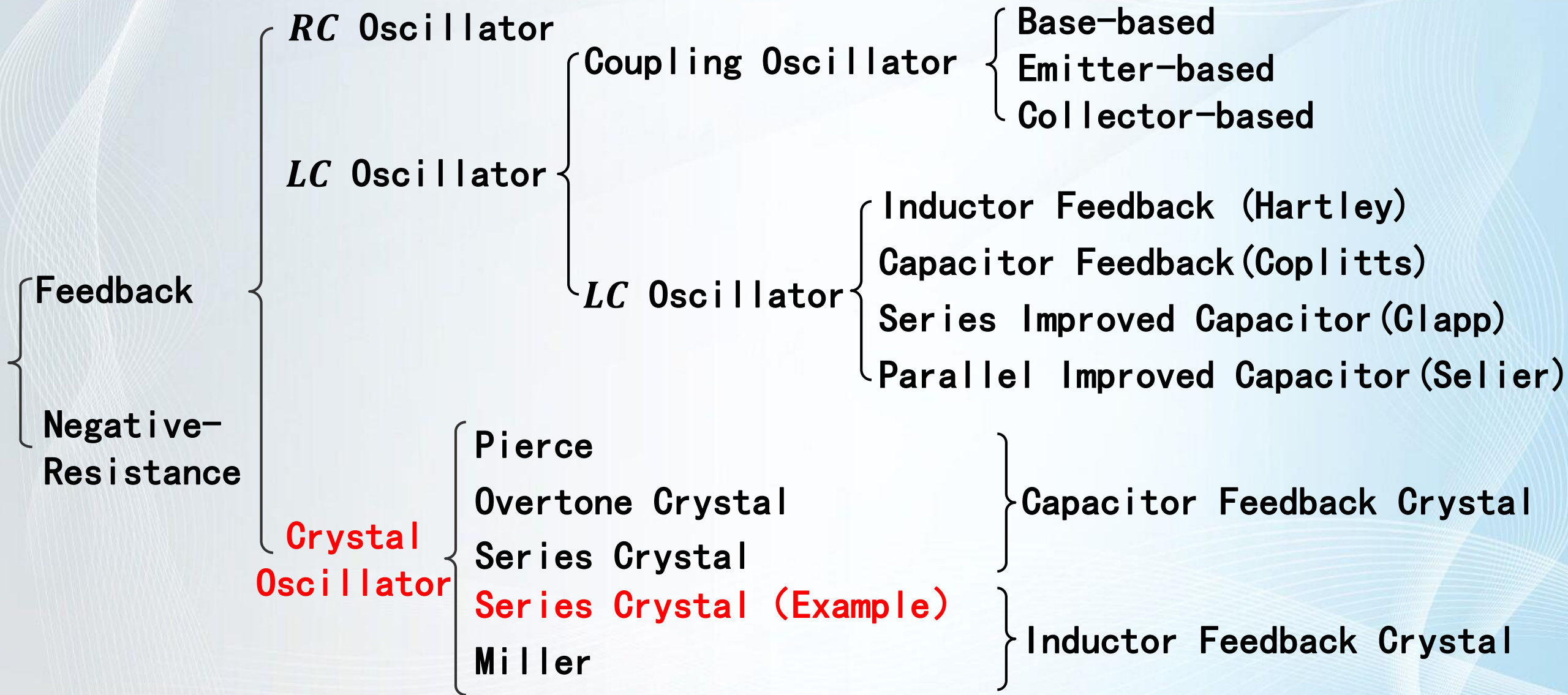

Exp.

The crystal oscillator is as figure. $J_T = 5\text{MHz}$

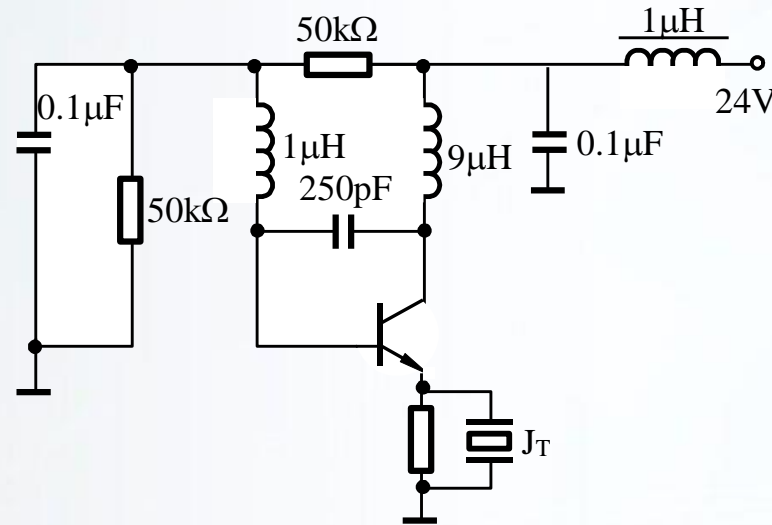- (1) Draw the equivalent circuit & determine the classification.
- (2) Compute the oscillator frequency.
- (3) Analyze the crystal function.





Exp.

The crystal oscillator is as figure. $J_T = 5\text{MHz}$

(1) Draw the equivalent circuit & determine the classification.

(2) Compute the oscillator frequency. $f_0 = 5\text{MHz}$

(3) Analyze the crystal function.

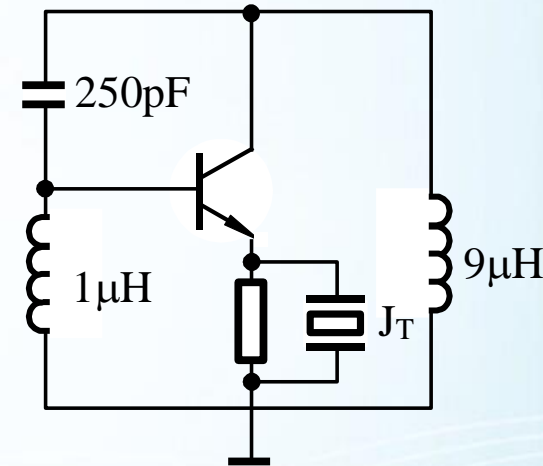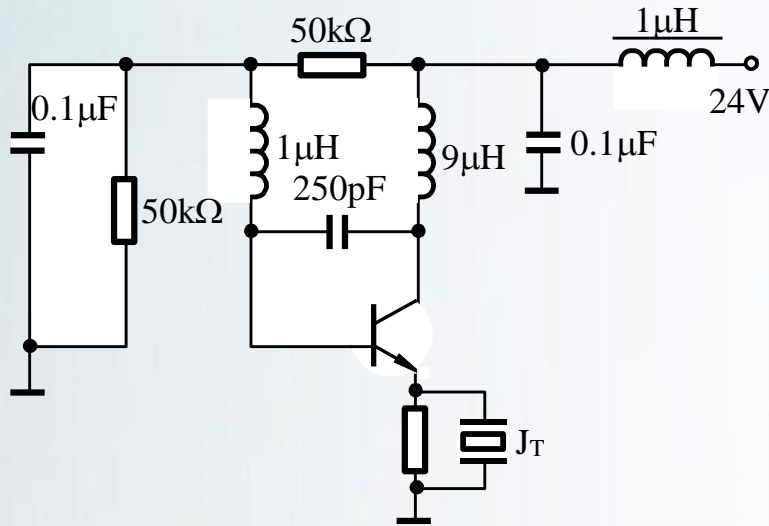

Inductive Feedback Crystal Oscillator
In Series Mode