



Huazhong University of Science and Technology
The Department of Electronics and Information Engineering



Electronic Circuit Analysis and Design

Dr. Tianping Deng


Email: dengtp@hust.edu.cn

Contents

PART 1 SEMICONDUCTOR DEVICES AND BASIC APPLICATIONS

- Chapter 1 Semiconductor Materials and Diodes
- Chapter 2 Diode Circuits
- Chapter 3 The Field-Effect Transistor
- Chapter 4 Basic FET Amplifiers
- Chapter 5 The Bipolar Junction Transistor
- Chapter 6 Basic BJT Amplifiers
- Chapter 7 Frequency Response
- Chapter 8 Output Stages and Power Amplifiers

PART 2 ANALOG ELECTRONICS

- Chapter 9 Ideal Operational Amplifiers and Op-Amp Circuits
-  **Chapter 10 Integrated Circuit Biasing and Active Loads**
- Chapter 11 Differential and Multistage Amplifiers
- Chapter 12 Feedback and Stability
- Chapter 13 Operational Amplifier Circuits
- Chapter 14 Nonideal Effects in Operational Amplifier Circuits
- Chapter 15 Applications and Design of Integrated Circuits



10.1 Bipolar Transistor Current Source

10.2 FET Current Source

10.3 Circuit with Active Loads

10.4 Small-Signal Analysis: Active Load Circuits

10.1.1 Two-Transistor Current Source

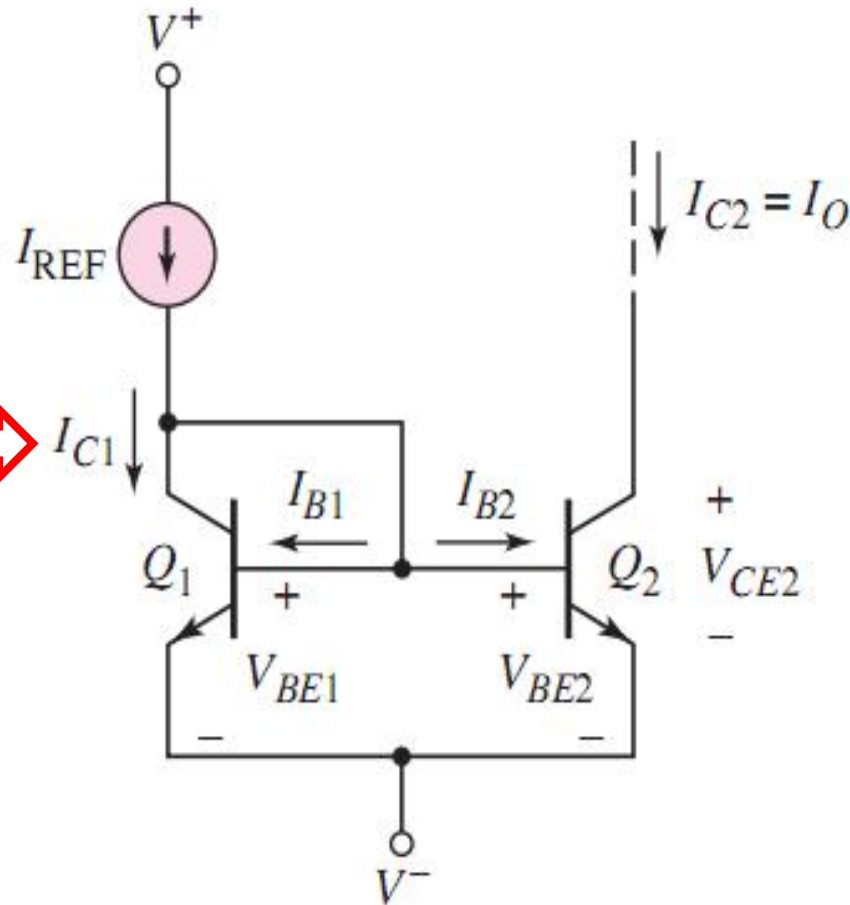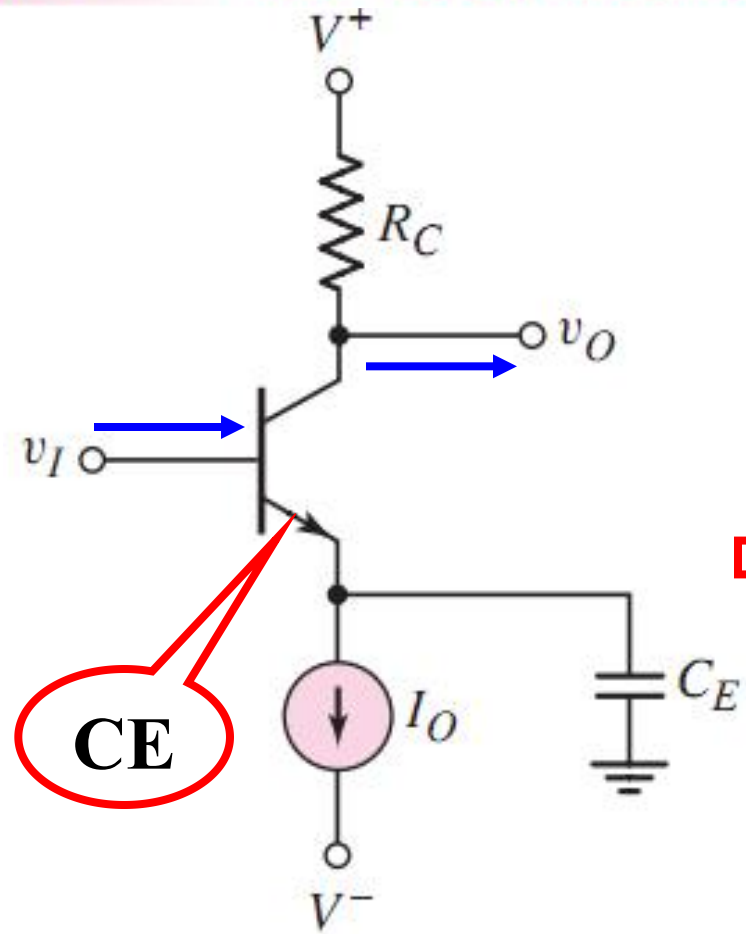

Which Region?

Forward active region

10.1 Bipolar Transistor Current Sources


10.1.1 Basic Current Source (Current Mirror)

- T_1, T_2 are identical transistors.

$$V_{BE2} = V_{BE1} \quad I_{E2} = I_{E1}$$

$$I_{REF} = I_{C1} + 2I_{B1} = I_{C1} + 2I_{C1} / \beta$$
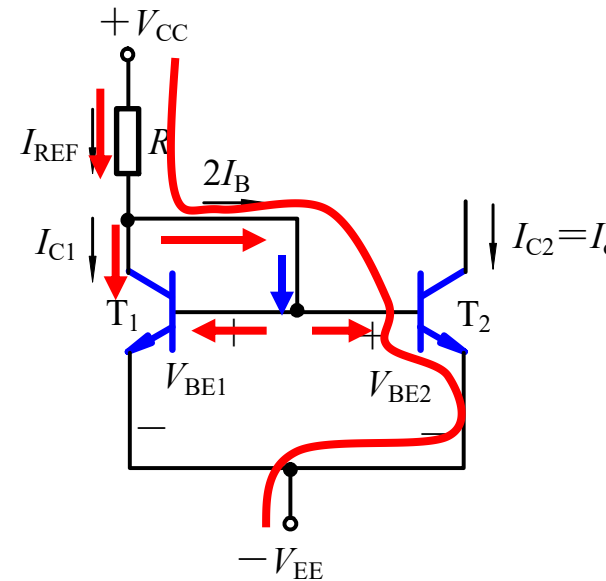
$$I_{C2} = I_{C1} = \frac{I_{REF}}{1 + 2/\beta} \quad (1)$$



If $\beta \gg 2$ $I_{C2} = I_{C1} \approx I_{REF} = \frac{V_{CC} - V_{BE} + V_{EE}}{R} \approx \frac{V_{CC} + V_{EE}}{R}$

- I_{C2} is the mirror image of I_{C1} .
- I_{C2} is almost constant, no matter the value of R_C .

10.1.1 Basic Current Source (Current Mirror)

- Because I_{C2} is almost constant, ac value I_T of I_{C2} is


Output Resistance

$$I_T \approx 0$$

$$r_o = \frac{V_T}{I_T} \approx \infty$$

- In general, r_o is in order of 100 k Ω .

$$r_o = r_{ce}$$

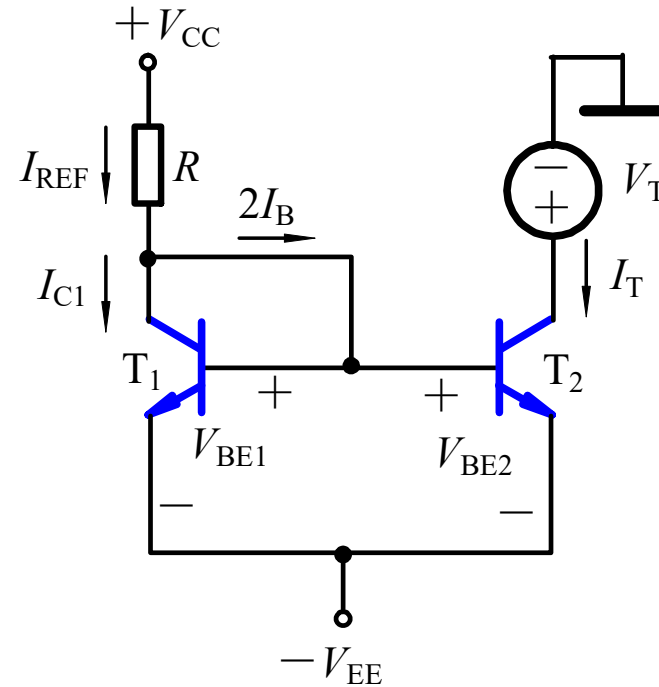

10.1.2 Improved Current Source

$$I_{E3} = I_{B1} + I_{B2} = \frac{2}{\beta} I_{C2}$$


$$I_{B3} = \frac{I_{E3}}{1 + \beta} = \frac{2}{\beta(1 + \beta)} I_{C2}$$

$$I_{REF} = I_{C1} + I_{B3} = I_{C1} + \frac{2}{\beta(1 + \beta)} I_{C2}$$

$$I_{C2} = I_{C1} \quad I_{C2} = \frac{I_{REF}}{1 + 2/(\beta^2 + \beta)} \quad (2)$$




$$I_{REF} = \frac{V_{CC} - V_{BE1} - V_{BE3} + V_{EE}}{R}$$
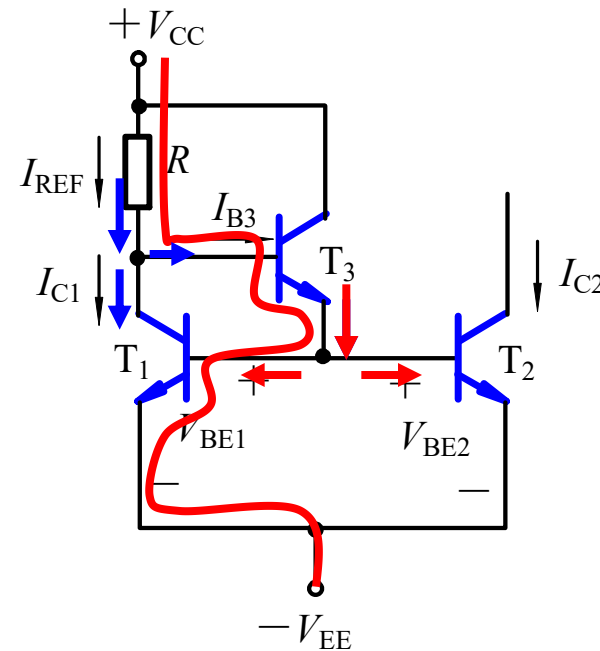
$$I_{C2} = I_{C1} = \frac{I_{REF}}{1 + 2/\beta} \quad (1)$$




- Comparing Expressions (1) and (2), when $I_{C2} \approx I_{REF}$, the error of (2) can be reduced by adding transistor T₃.

10.1.2 Improved Current Source

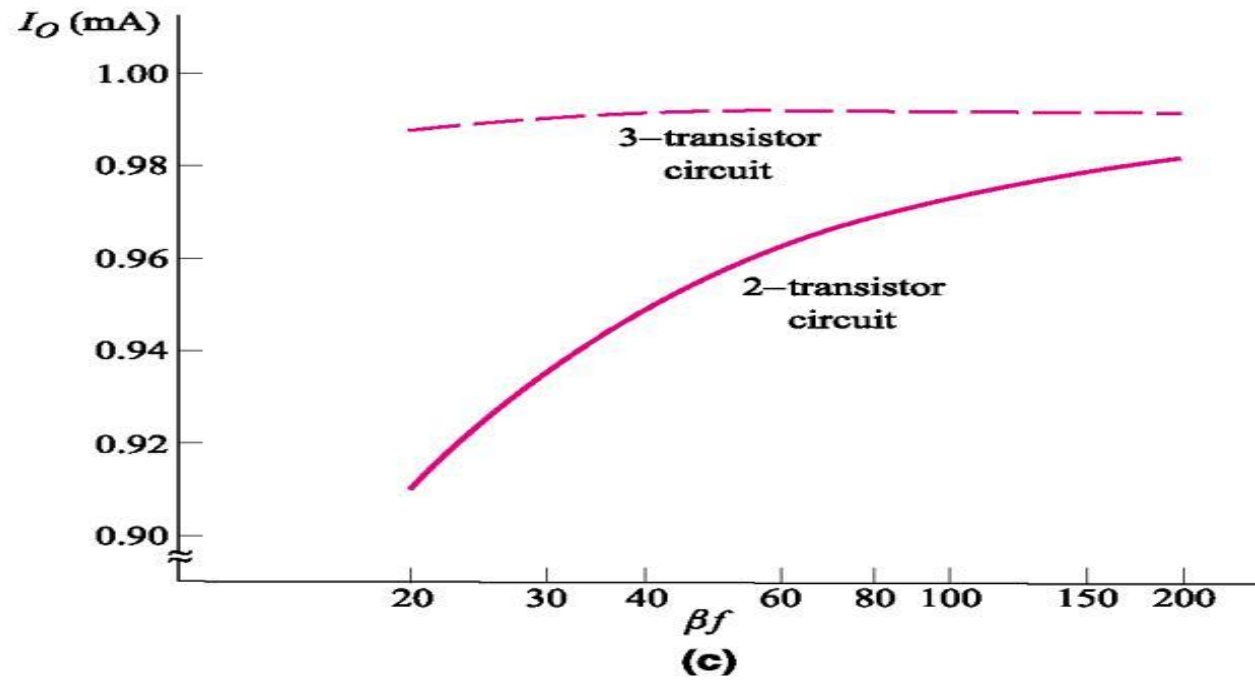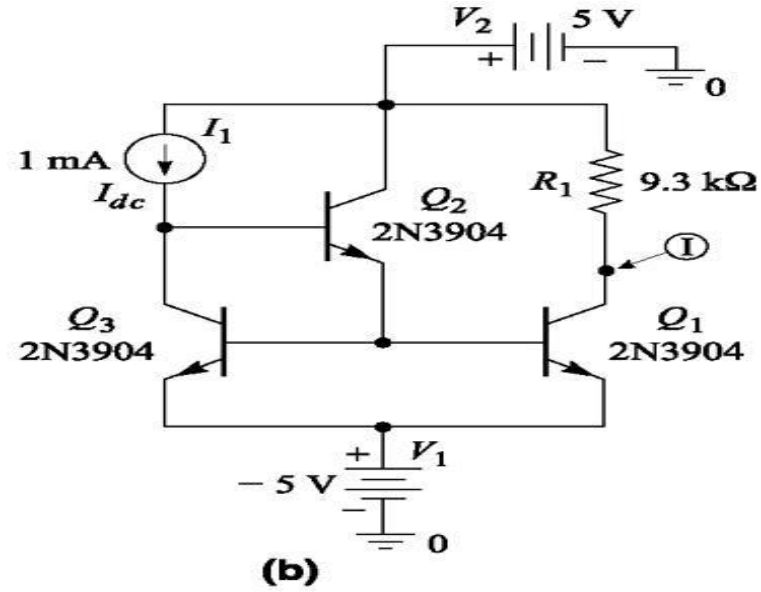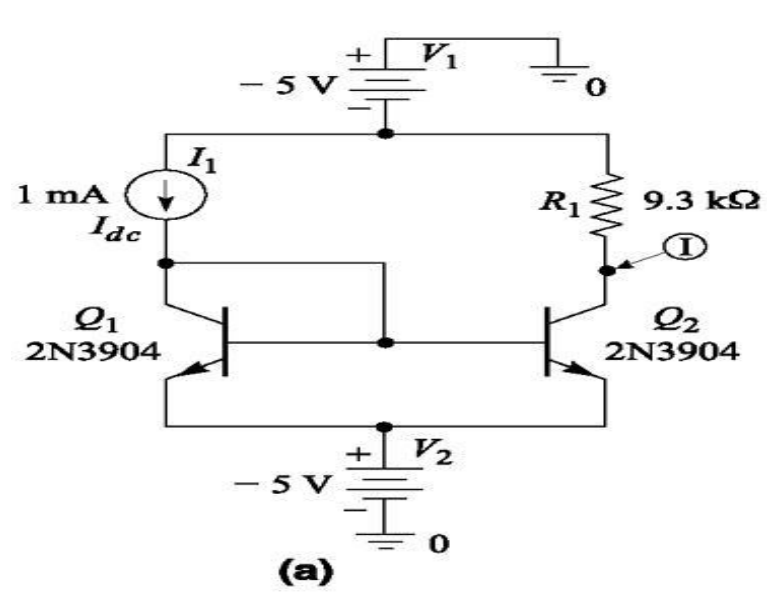

10.1.3 Widlar Current Source

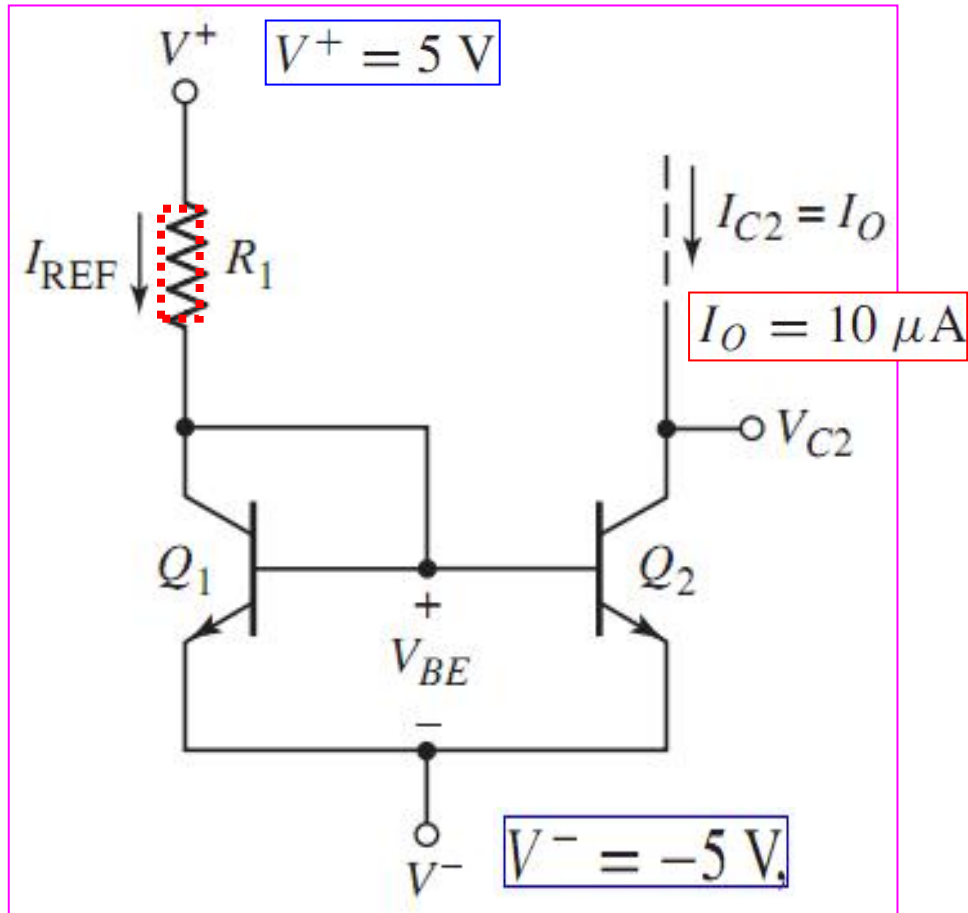


$$R_1 = \frac{V^+ - V_{BE} - V^-}{I_{\text{REF}}} \cong \frac{5 - 0.7 - (-5)}{10 \times 10^{-6}} = 930\text{ k}\Omega$$

10.1.3 Widlar Current Source

$$I_{C2} \approx I_{E2} = \frac{V_{BE1} - V_{BE2}}{R_{E2}} = \frac{\Delta V_{BE}}{R_{E2}}$$

- Because ΔV_{BE} is very small, I_{C2} is very small.
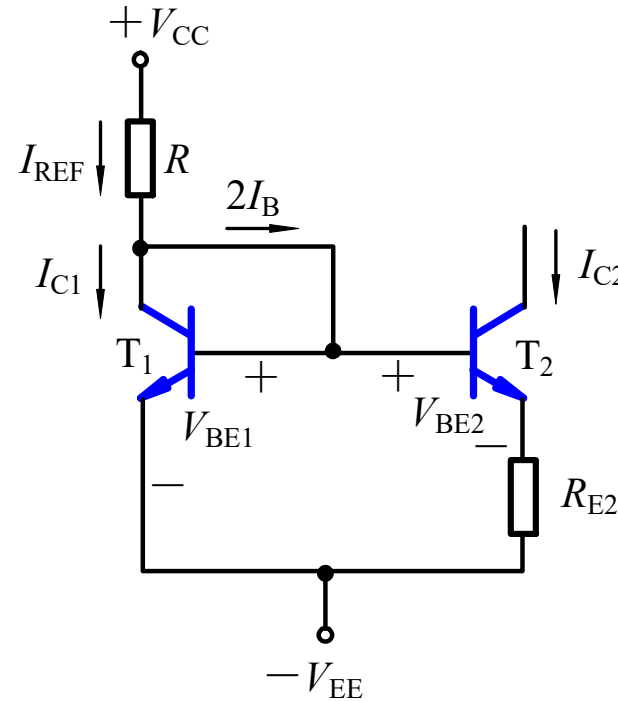
$$\text{and } I_{C2} R_{E2} = V_T \ln \left(\frac{I_{REF}}{I_{C2}} \right)$$



(The process of derivation on page 81).


$$r_o \approx r_{ce2} \left(1 + \frac{\beta R_{e2}}{r_{\pi 2} + R_{e2}} \right)$$

10.1.4 Multi-transistor Current Source

- T and R serve as the reference for all output transistors.
- T_R supplies the total base currents.
- T_R makes $I_{REF} \approx I_C$.


$$I_{C1} = I_{C2} = I_{C3} = \dots = I_{REF}$$

- There are N output transistors.

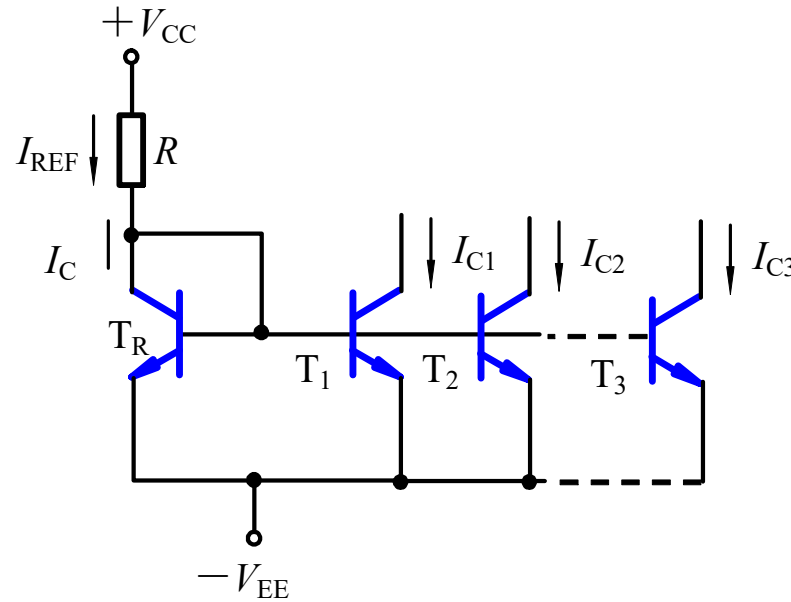


10.1 Bipolar Transistor Current Sources

$I_{\text{REF}} = ?$

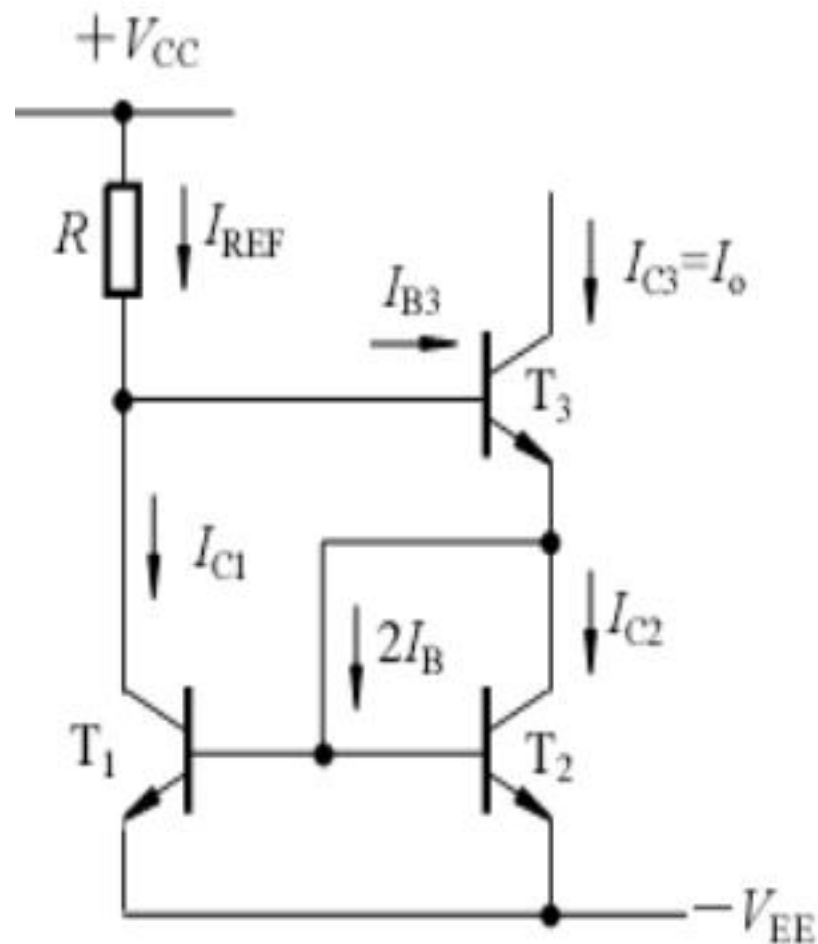

$$I_{\text{REF}} = \frac{V_{CC} - V_{BE3} - V_{BE2} + V_{EE}}{R}$$

10.1.4 Multi-transistor Current Source

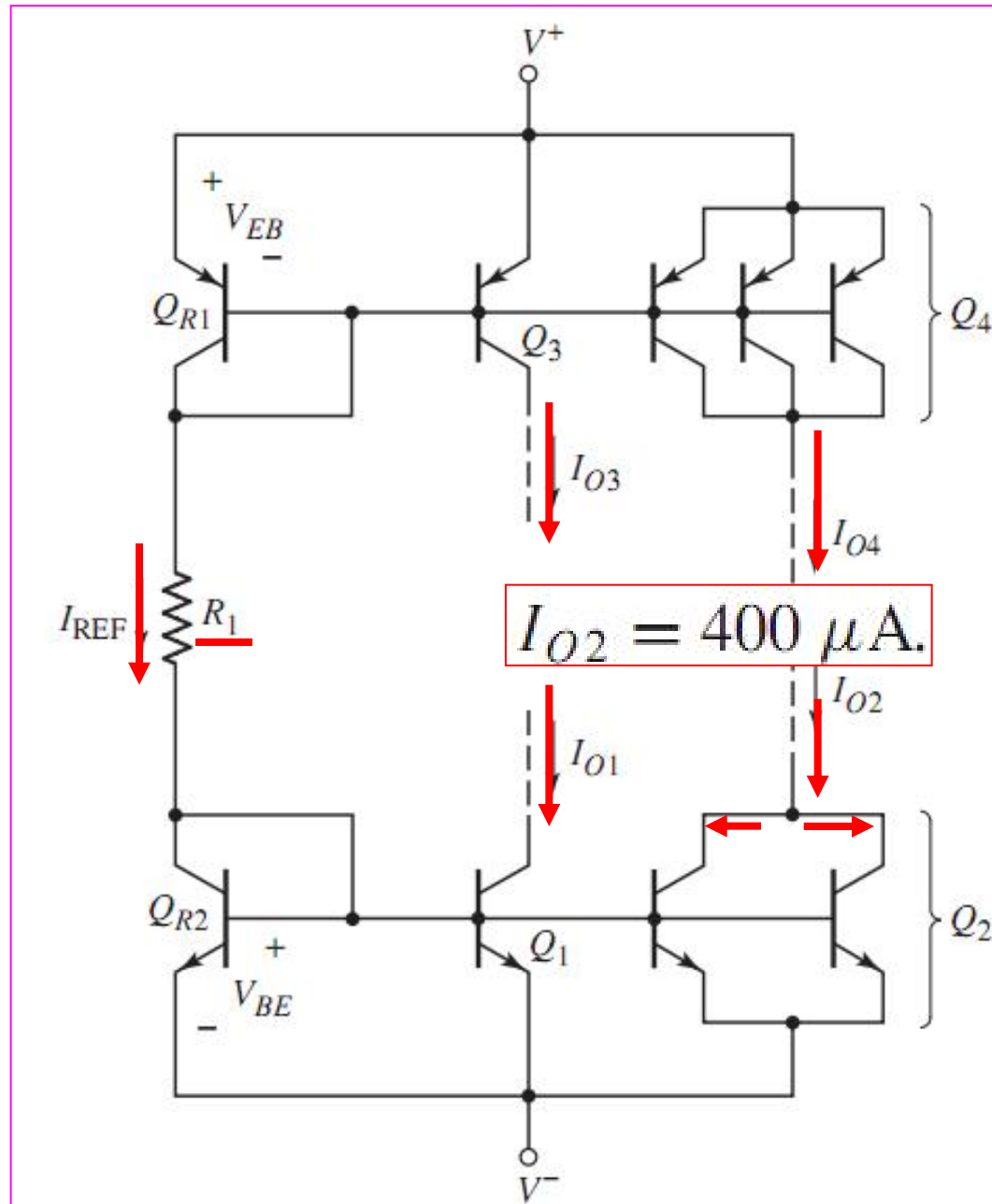

$$V^+ = +5 \text{ V}$$

$$V^- = -5 \text{ V.}$$

Neglect base currents

$$V_{BE} = V_{EB} = 0.6 \text{ V.}$$

$$I_{O2} = 400 \mu A.$$

$$I_{REF} = I_{O1} = I_{O3} = 200 \mu A$$


$$I_{O4} = 600 \mu A$$

$$R_1 = \frac{V^+ - V_{EB}(Q_{R1}) - V_{BE}(Q_{R2}) - V^-}{I_{REF}}$$

$$= \frac{5 - 0.6 - 0.6 - (-5)}{0.2}$$


$$R_1 = 44 \text{ k}\Omega$$

10.1 Bipolar Transistor Current Sources

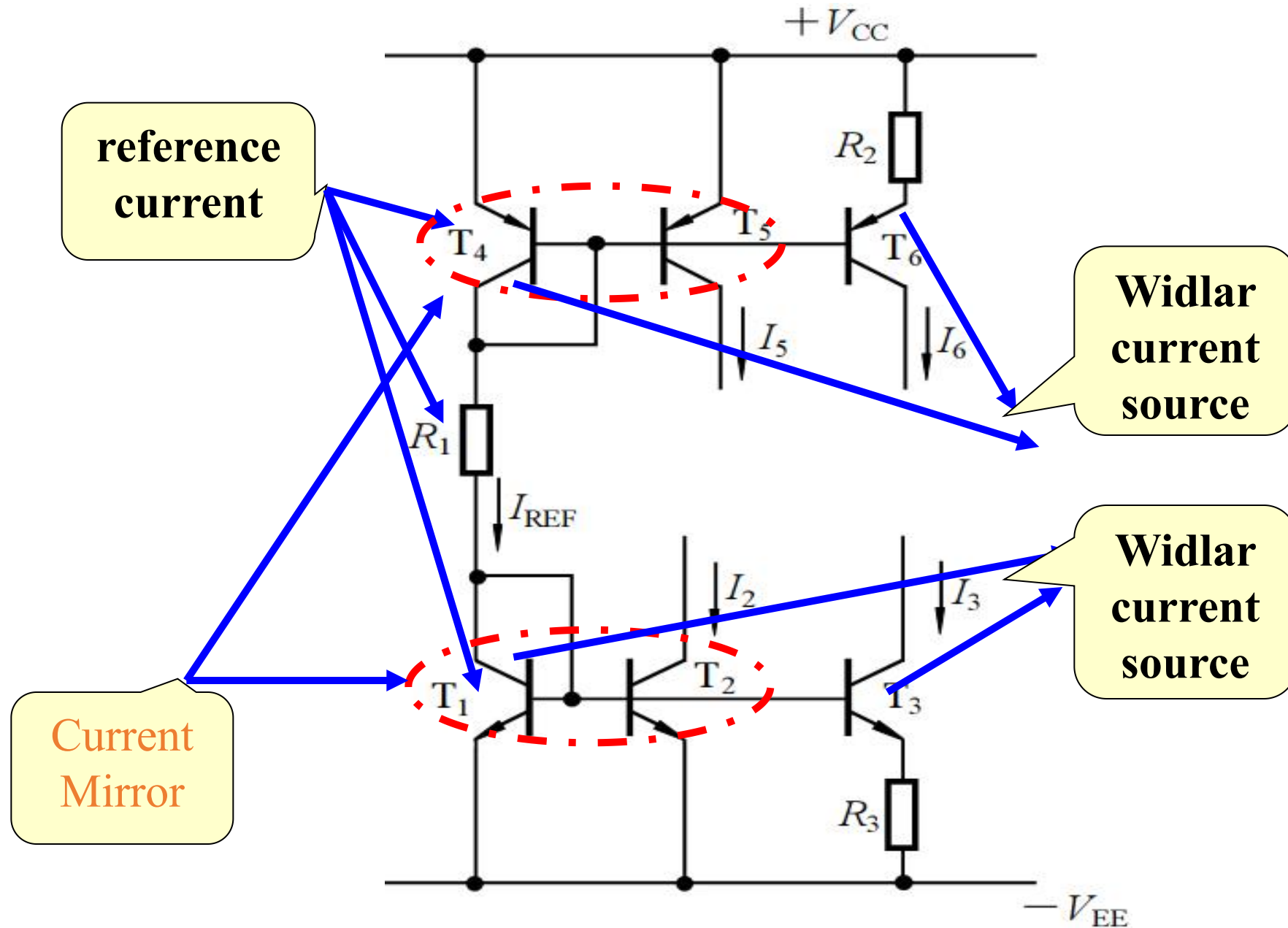


$I_{\text{REF}}=?$
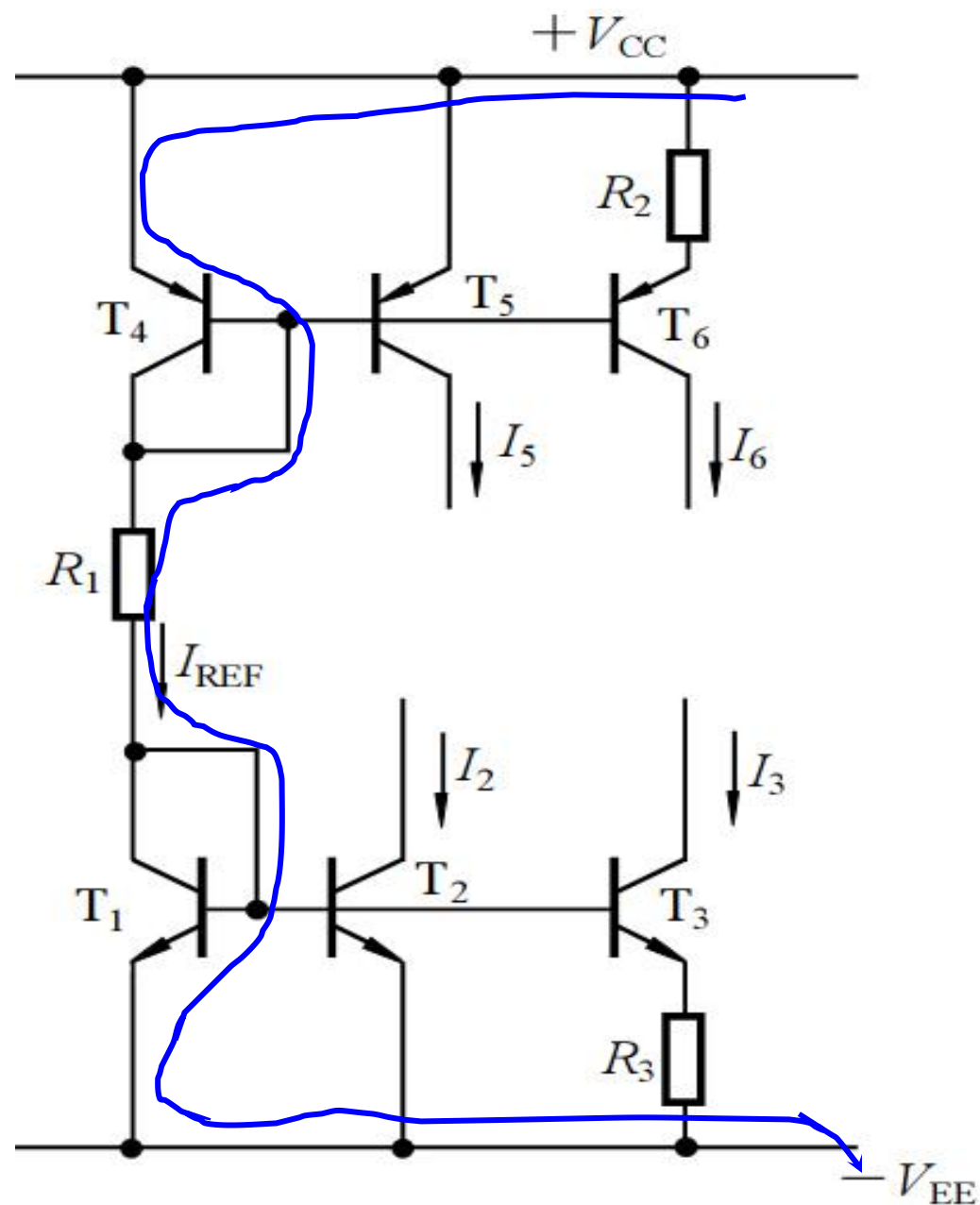
$$I_{\text{REF}} = \frac{V_{\text{CC}} + V_{\text{EE}} - V_{\text{BE1}} - V_{\text{EB4}}}{R_1}$$



Example

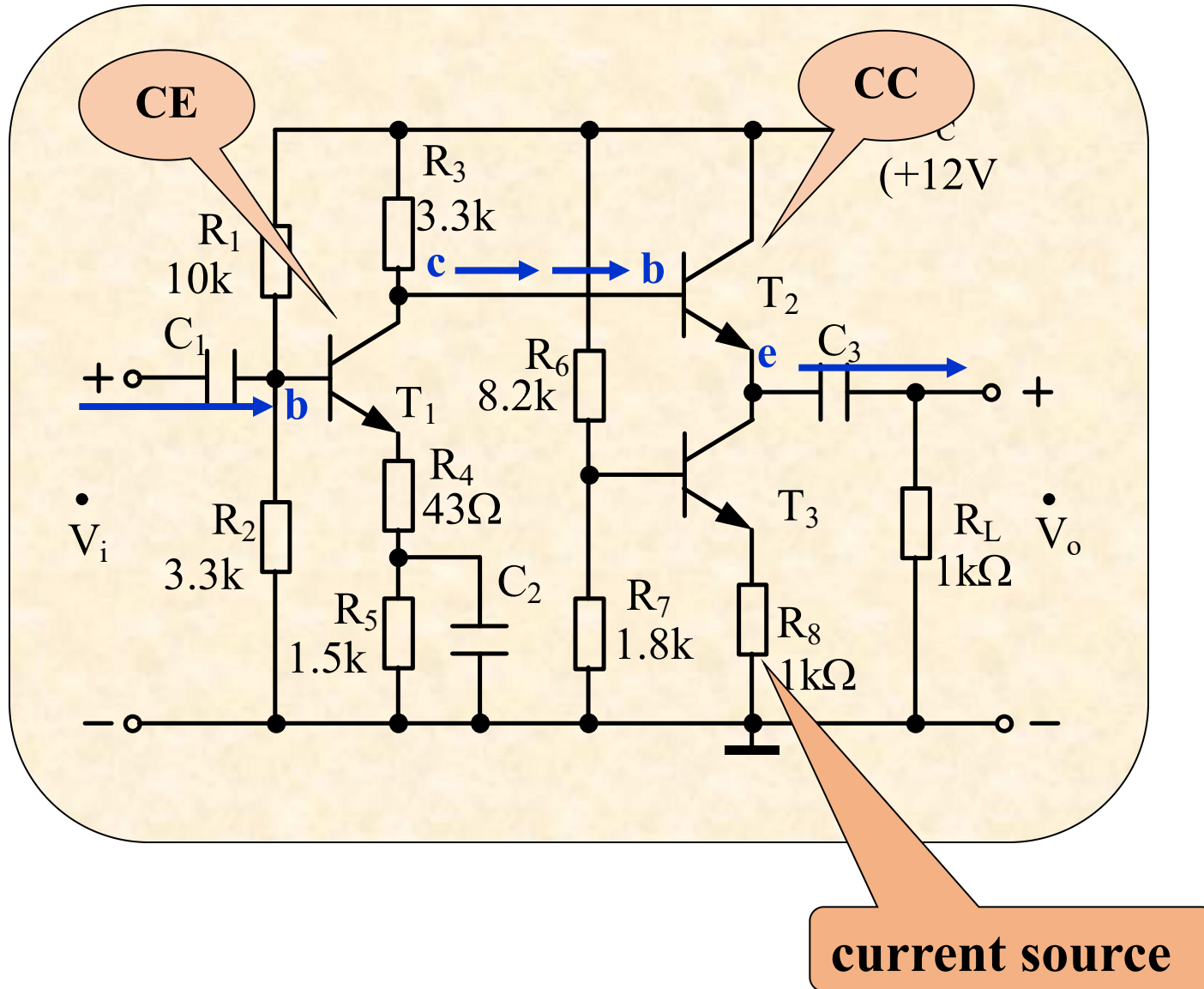


Contents

PART 1 SEMICONDUCTOR DEVICES AND BASIC APPLICATIONS

- Chapter 1 Semiconductor Materials and Diodes
- Chapter 2 Diode Circuits
- Chapter 3 The Field-Effect Transistor
- Chapter 4 Basic FET Amplifiers
- Chapter 5 The Bipolar Junction Transistor
- Chapter 6 Basic BJT Amplifiers
- Chapter 7 Frequency Response
- Chapter 8 Output Stages and Power Amplifiers

PART 2 ANALOG ELECTRONICS

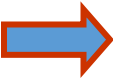- Chapter 9 Ideal Operational Amplifiers and Op-Amp Circuits
-  **Chapter 10 Integrated Circuit Biasing and Active Loads**
- Chapter 11 Differential and Multistage Amplifiers
- Chapter 12 Feedback and Stability
- Chapter 13 Operational Amplifier Circuits
- Chapter 14 Nonideal Effects in Operational Amplifier Circuits
- Chapter 15 Applications and Design of Integrated Circuits

10.1 Bipolar Transistor Current Source


10.2 FET Current Source

10.3 Circuit with Active Loads

10.4 Small-Signal Analysis: Active Load Circuits

10.2 FET Current Sources

10.2.1 Basic Current Source

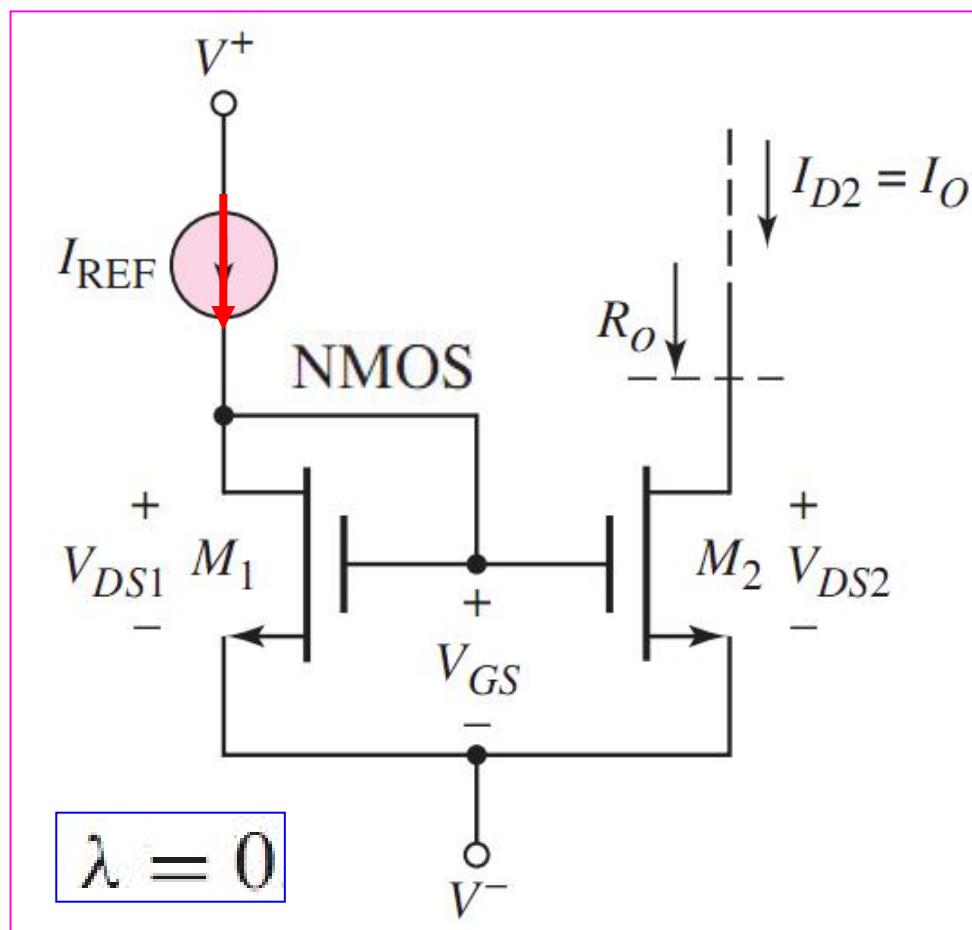

M_1

$$I_{\text{REF}} = K_{n1}(V_{GS} - V_{TN1})^2$$



$$V_{GS} = V_{TN1} + \sqrt{\frac{I_{\text{REF}}}{K_{n1}}}$$

M_2

$$I_O = K_{n2}(V_{GS} - V_{TN2})^2$$


$$I_O = K_{n2} \left[\sqrt{\frac{I_{\text{REF}}}{K_{n1}}} + V_{TN1} - V_{TN2} \right]^2$$

If M_1 and M_2 are identical transistors $V_{TN1} = V_{TN2}$ and $K_{n1} = K_{n2}$

$$I_O = I_{\text{REF}}$$

10.2 FET Current Sources

10.2.1 Basic Current Source

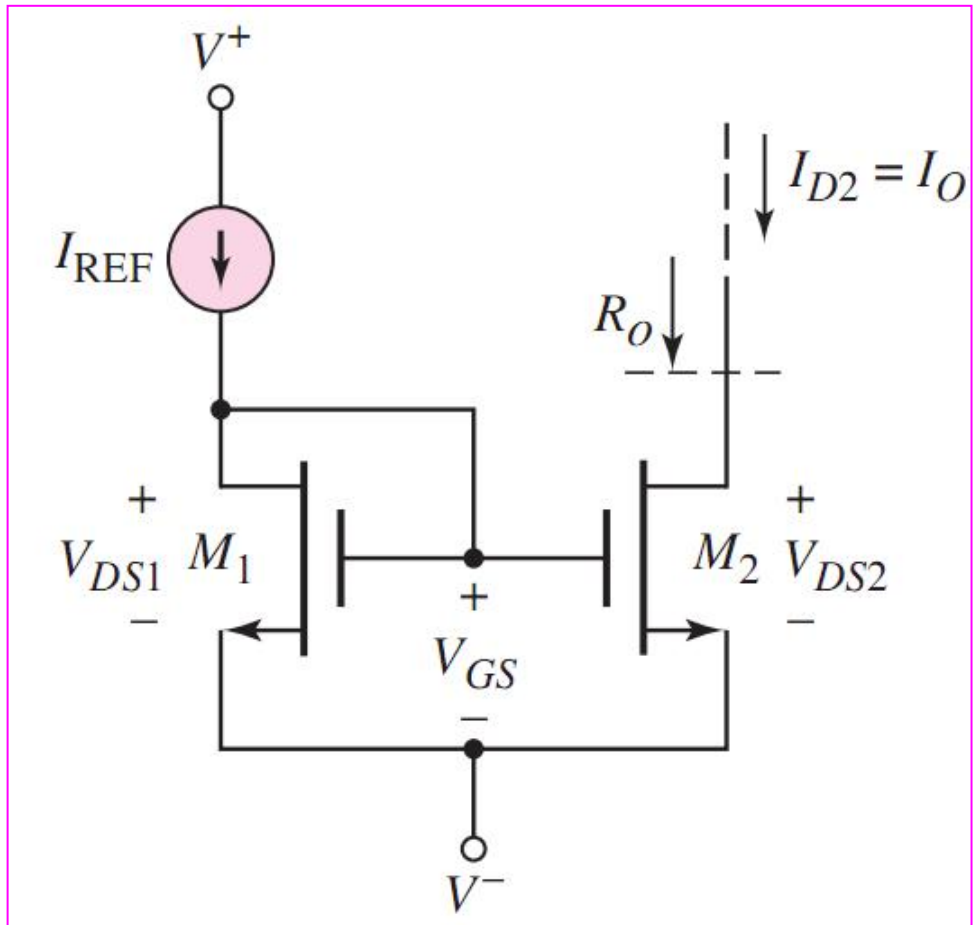

aspect ratios
width-to-length ratios

$$I_O = \frac{(W/L)_2}{(W/L)_1} \cdot I_{REF}$$

If the transistors are matched except for the aspect ratios,

10.2 FET Current Sources

10.2.1 Basic Current Source

- Load current

$$I_O = \frac{W_2 / L_2}{W_1 / L_1} I_{\text{REF}}$$


$$I_O = I_{D2} = K_{n2} (V_{GS2} - V_{T2})^2$$

$$I_O = I_{D2} = I_{\text{REF}} = \frac{V_{DD} + V_{SS} - V_{GS}}{R}$$

- Output Resistance

$$r_o = r_{ds2} \approx \infty$$

- T_3 substitute R

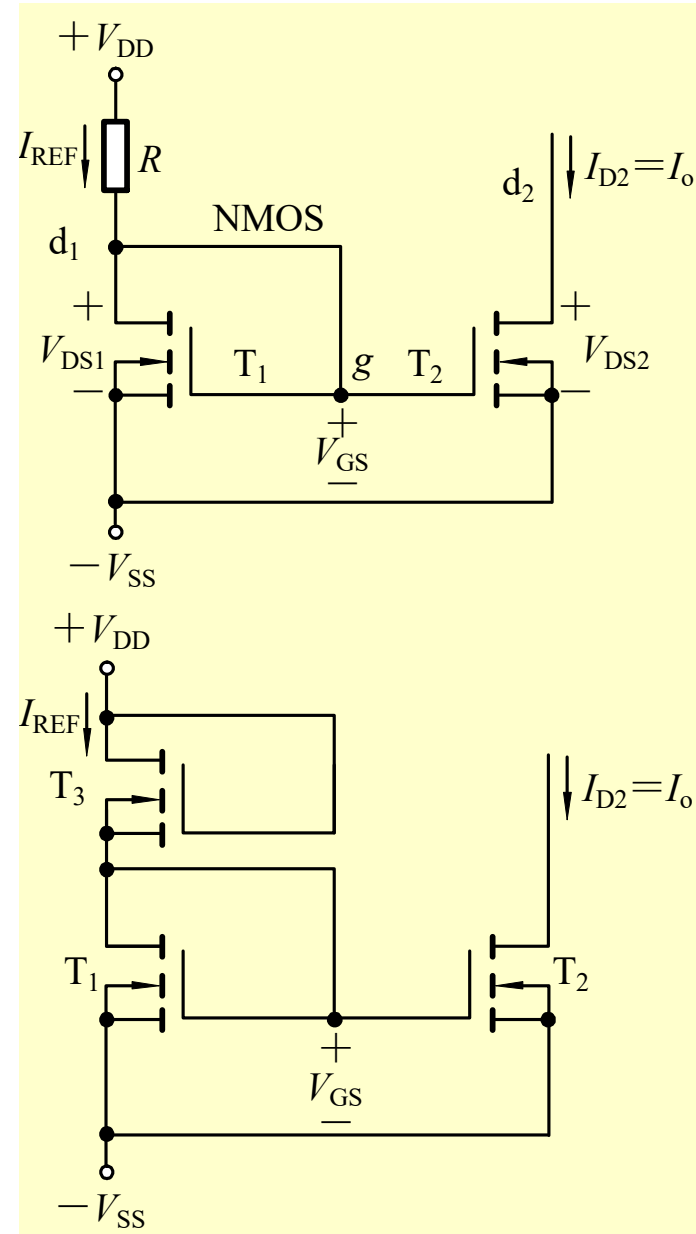


10.2 FET Current Sources

$$I_{D1} = I_{D3} = I_{REF} = K_n (V_{GS} - V_{TN})^2$$

$$V_{GS3} = V_{GS} = \frac{1}{2}(V_{DD} + V_{SS})$$

$$V_{DD} + V_{SS} > 2V_{TN}$$

$$I_{D2} = K_n (V_{GS} - V_{TN})^2$$

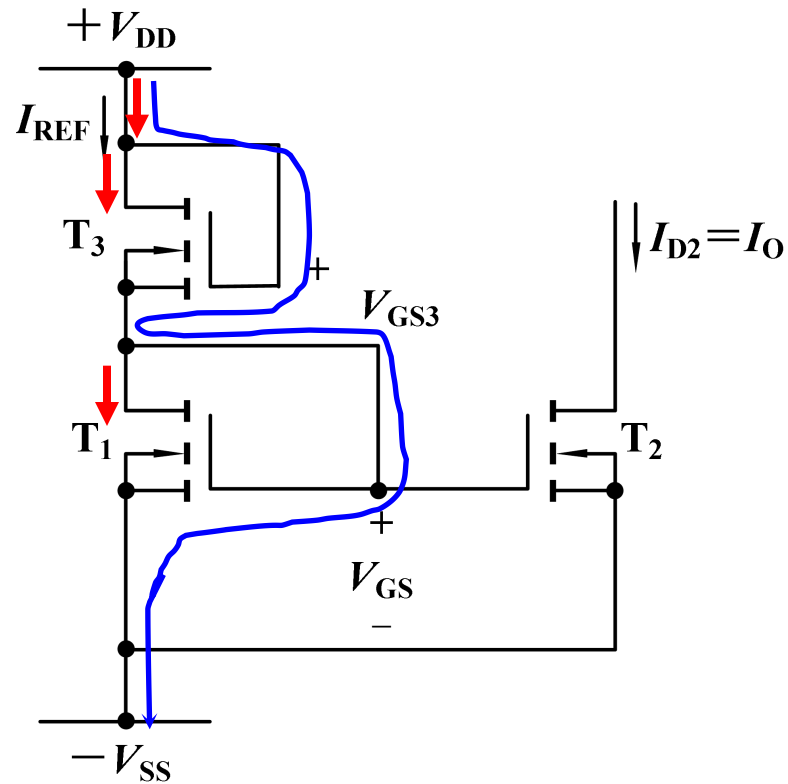

10.2 FET Current Sources

10.2.2 Multi-MOSFET Current Source


- Currents

$$I_{D2} = \frac{W_2 / L_2}{W_1 / L_1} I_{REF}$$

$$I_{D3} = \frac{W_3 / L_3}{W_1 / L_1} I_{REF}$$

$$I_{D4} = \frac{W_4 / L_4}{W_1 / L_1} I_{REF}$$
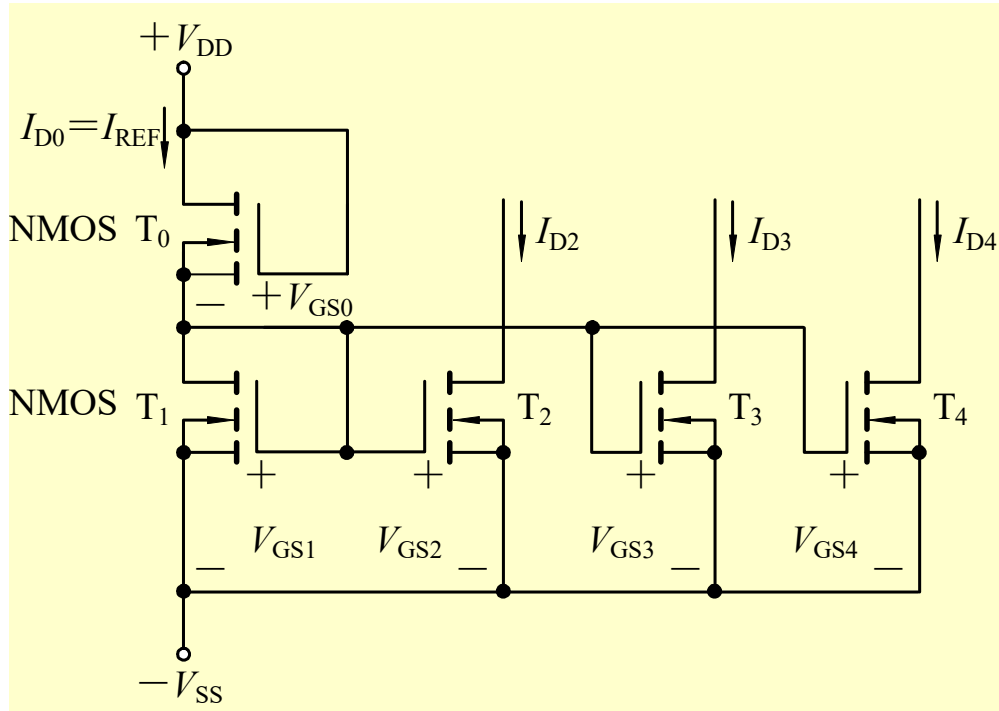
$$I_{REF} = I_{D0} = K_{n0} (V_{GS0} - V_{T0})^2$$



10.3 circuit with active loads

- T_2 , T_3 , R form active load in amplifier T_1 circuit.


- Voltage gain of CE:

$$\dot{A}_V = \frac{\dot{V}_o}{\dot{V}_i} = -\frac{\beta(R_C \parallel R_L)}{r_\pi}$$

- Equivalent ac output resistance of current source is the load for T_1 , and $R_C = r_o$


$$\dot{A}_V = -\frac{\beta R_L}{r_\pi}$$

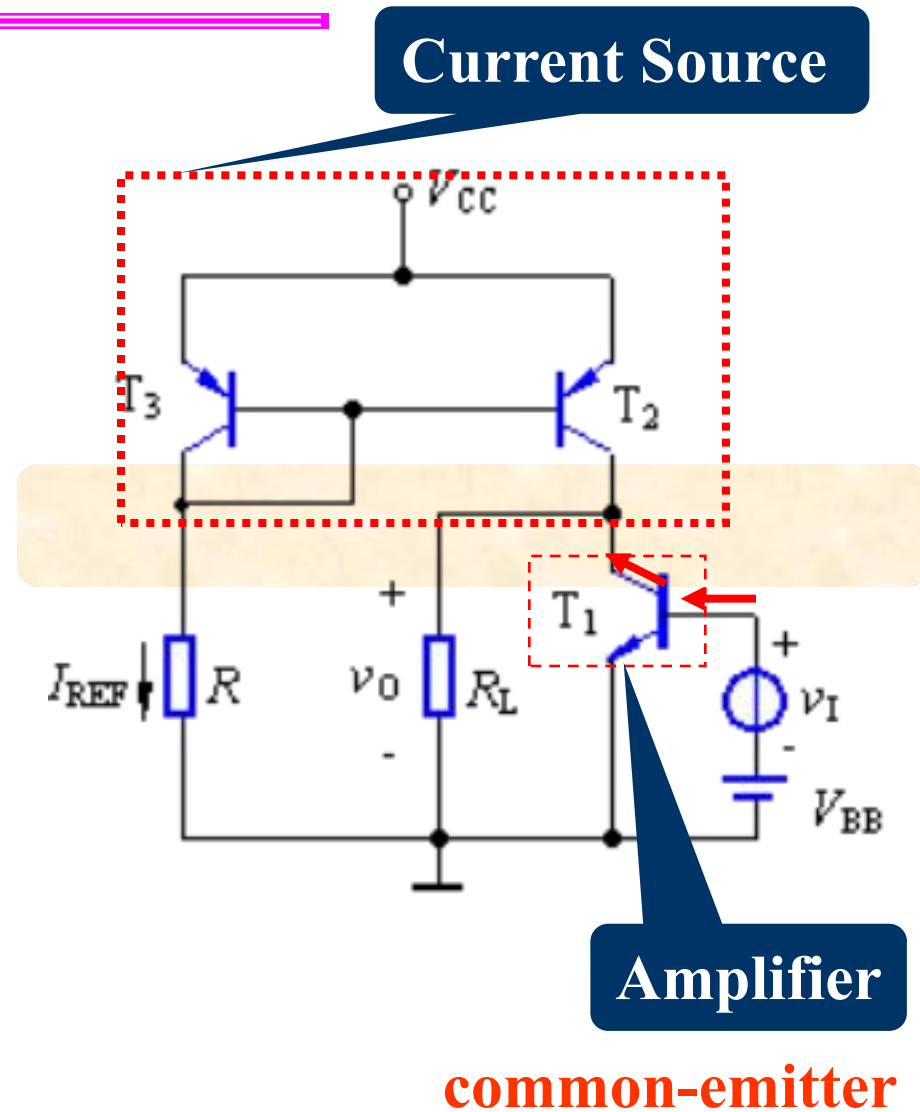Voltage gain with active load is greater than that of no active load.




10.4 Small-Signal Analysis: Active Load Circuits

Active Load

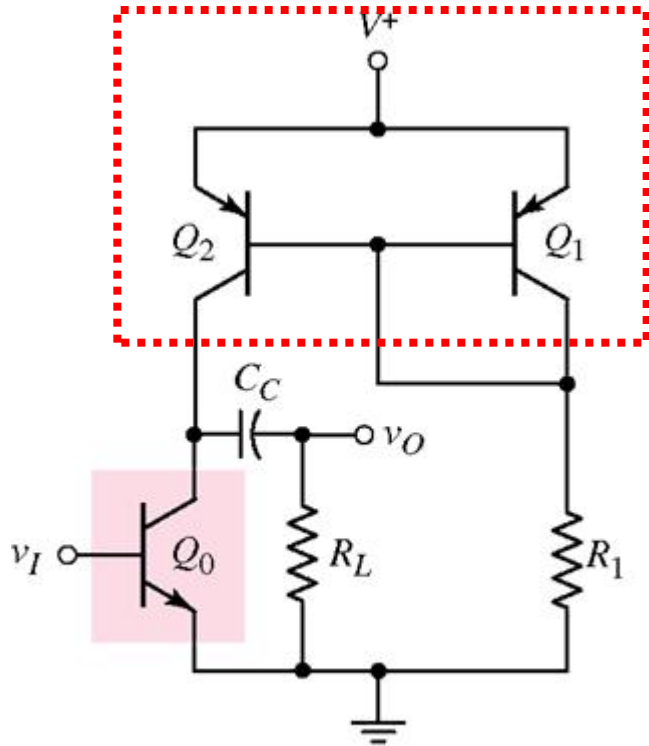

small-signal equivalent circuit

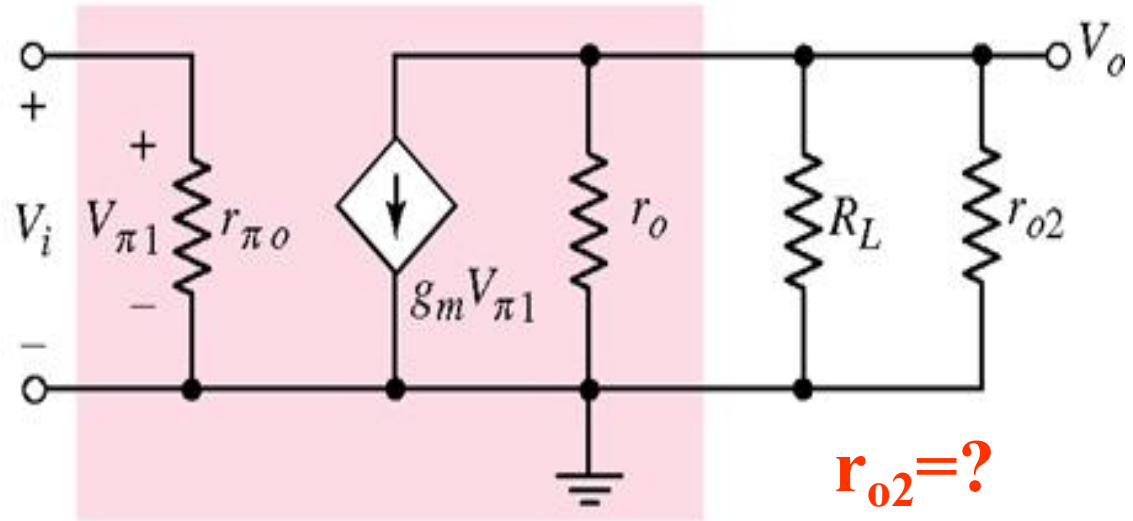

$r_{o2}=?$


$r_{o2}=r_{ce2}$

Simple BJT amplifier with active load


$$A_v = \frac{V_o}{V_i} = -g_m (r_o \parallel R_L \parallel r_{o2})$$

current source






Integrated Circuit Biasing

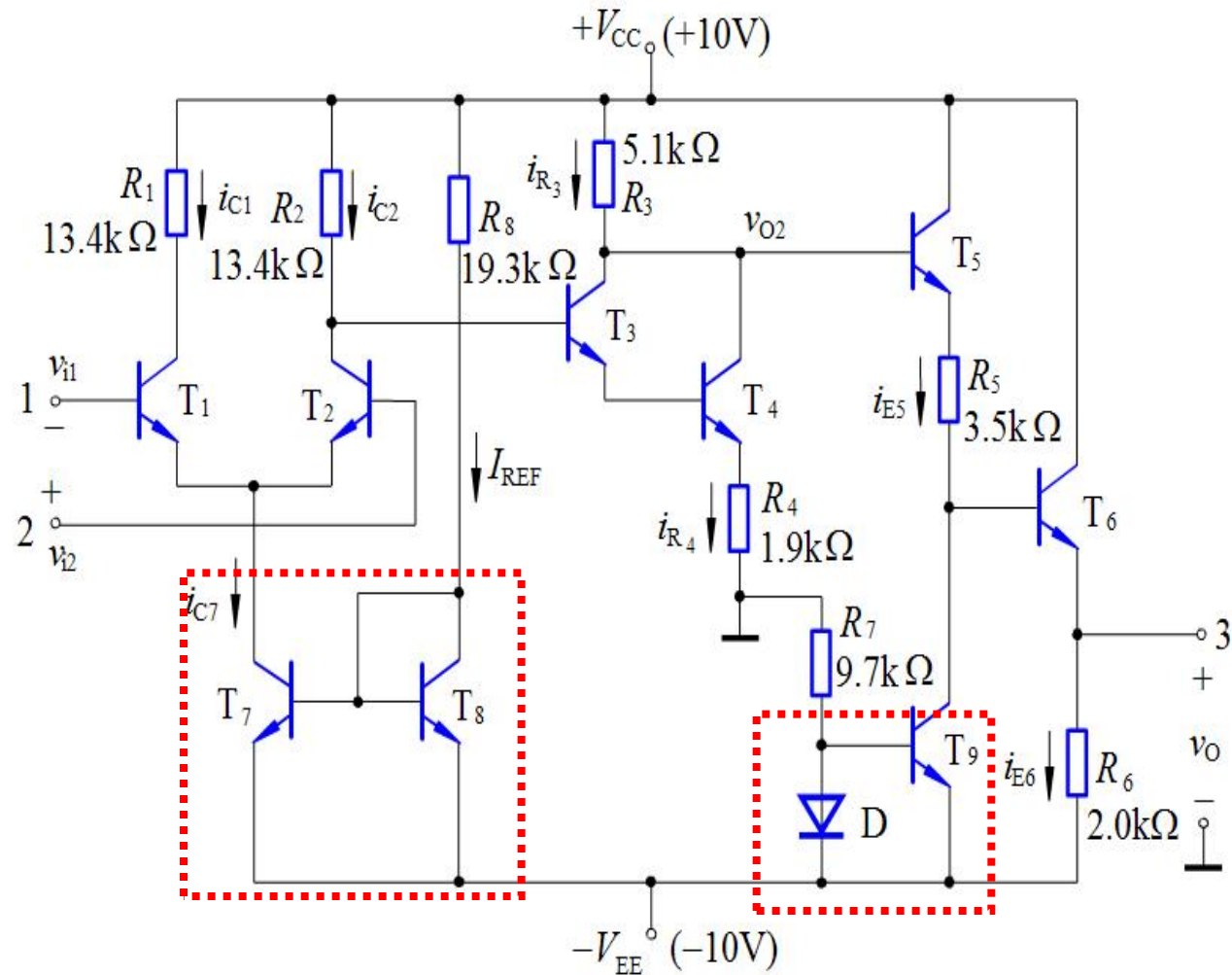

Active Loads

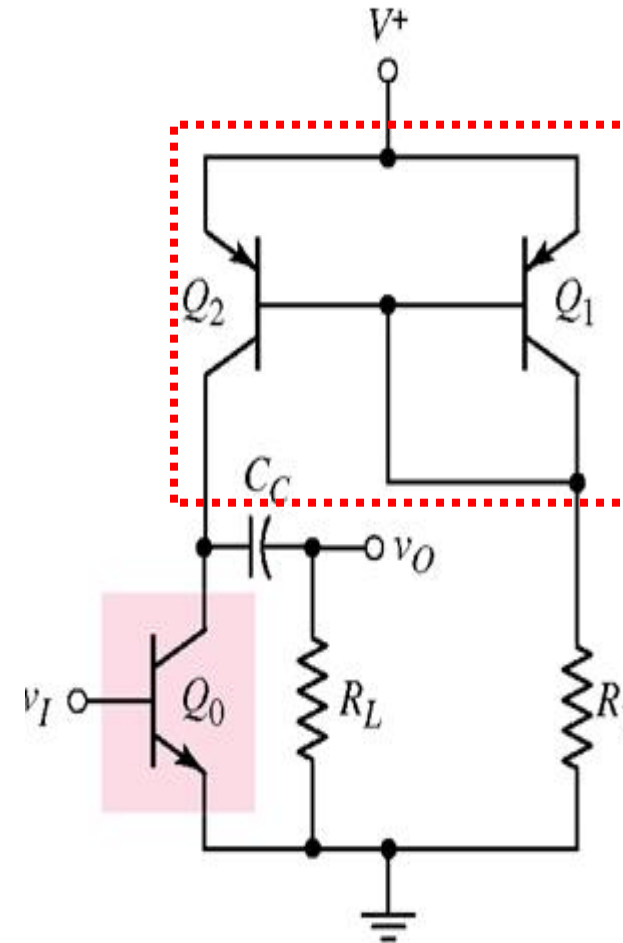

Summary

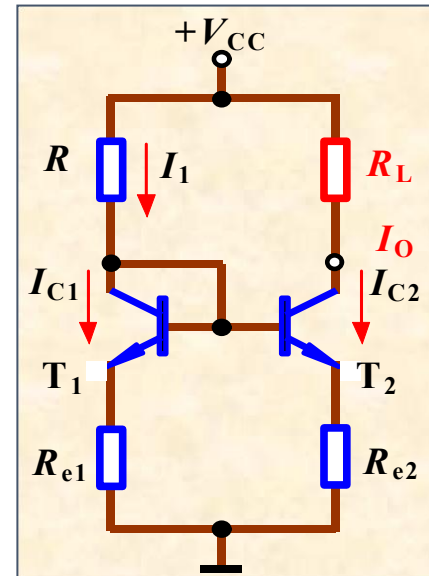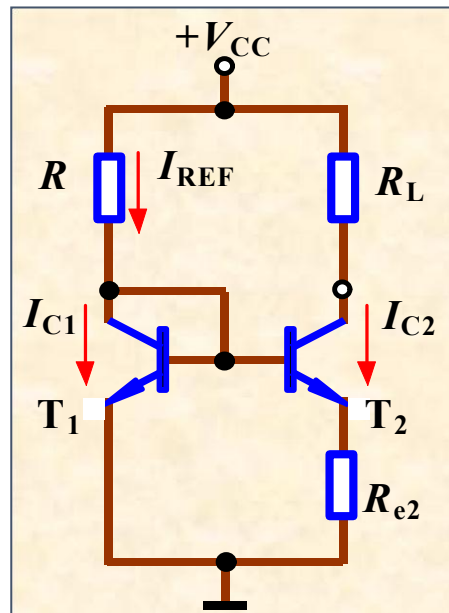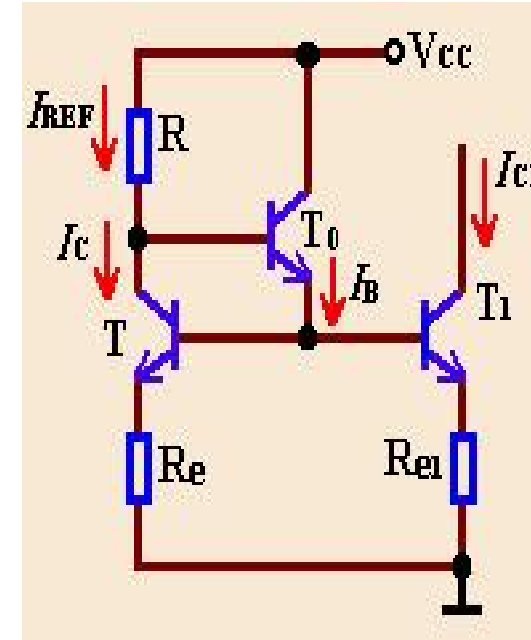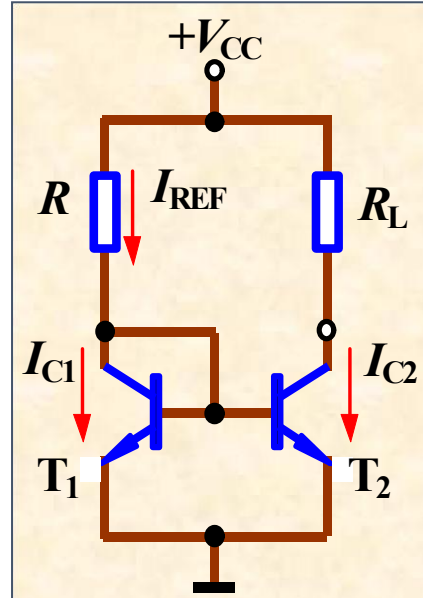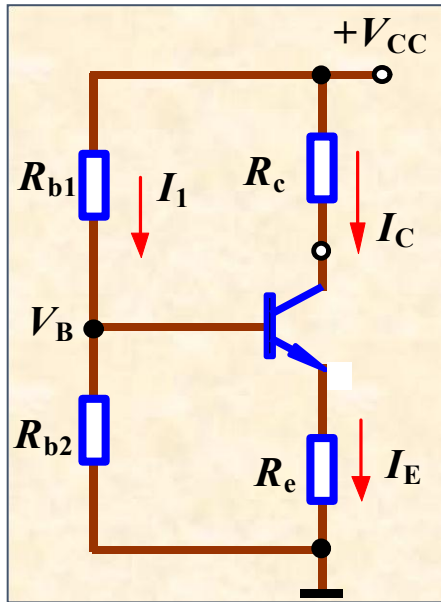

$$I_o = I_1 \frac{R_{e1}}{R_{e2}}$$