

Huazhong University of Science and Technology

The Department of Electronics and Information Engineering




Electronic Circuit Analysis and Design

Dr. Tianping Deng

Email: dengtp@hust.edu.cn

Contents

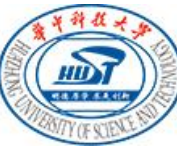

PART 1 SEMICONDUCTOR DEVICES AND BASIC APPLICATIONS

Chapter 1 Semiconductor Materials and Diodes

Chapter 2 Diode Circuits

Chapter 3 The Field-Effect Transistor

 **Chapter 4 Basic FET Amplifiers**

Chapter 5 The Bipolar Junction Transistor

Chapter 6 Basic BJT Amplifiers

Chapter 7 Frequency Response

Chapter 8 Output Stages and Power Amplifiers

PART 2 ANALOG ELECTRONICS

Chapter 9 Ideal Operational Amplifiers and Op-Amp Circuits

Chapter 10 Integrated Circuit Biasing and Active Loads


Chapter 11 Differential and Multistage Amplifiers

Chapter 12 Feedback and Stability

Chapter 13 Operational Amplifier Circuits

Chapter 14 Nonideal Effects in Operational Amplifier Circuits

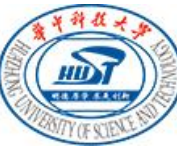Chapter 15 Applications and Design of Integrated Circuits



Ch4 Basic FET Amplifiers

4.1 The MOSFET Amplifier

4.2 Basic Transistor Amplifier Configurations

4.3 The Common Source Amplifier

4.4 The Common Drain (Source Follower) Amplifier


4.5 The Common Gate Configuration

4.5.1 Small voltage and current gains

4.5.2 Input and output Impedance

4.6 The Three Basic Amplifier Configuration: Summary and comparison

Ch4 Basic FET Amplifiers

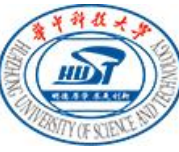


4.1 The MOSFET Amplifier

4.1.1 Graphical Analysis, Load line, and small signal parameters

4.1.2 small signal equivalent circuit


4.1 The MOSFET Amplifier

signals sound


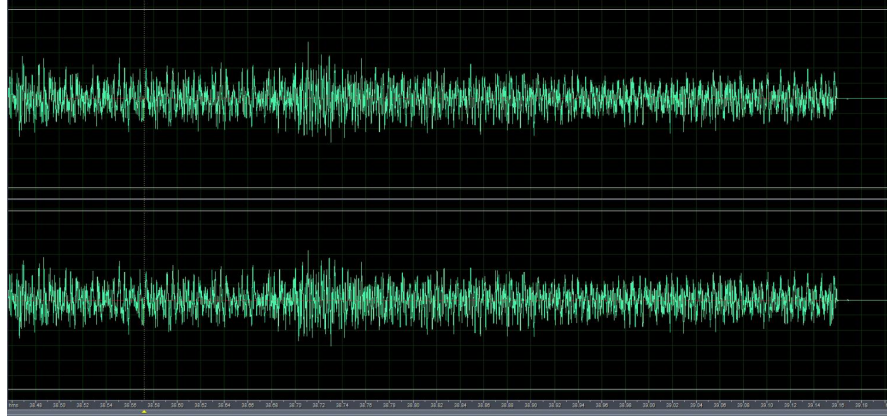


Analog circuits




amplifiers

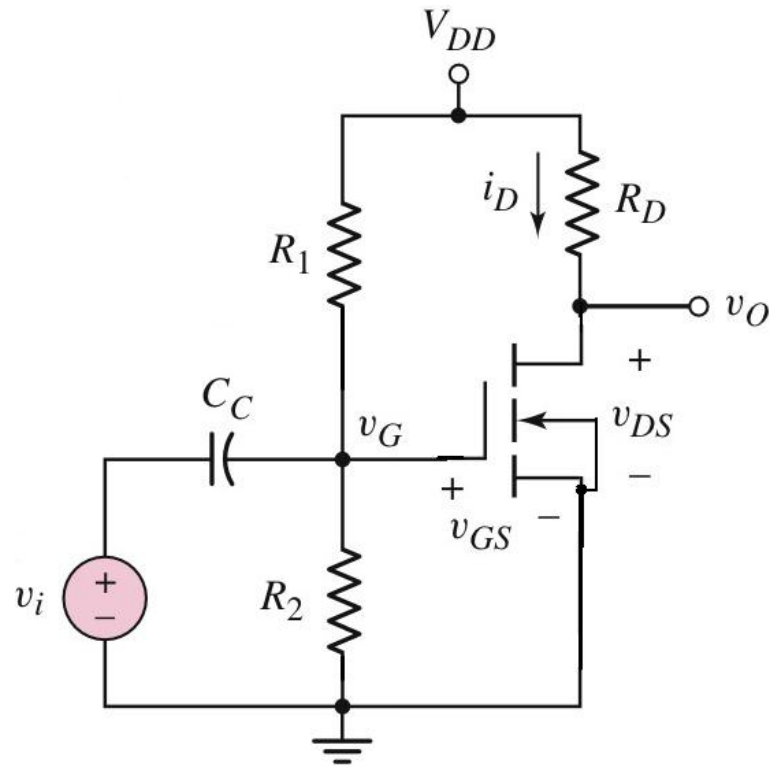

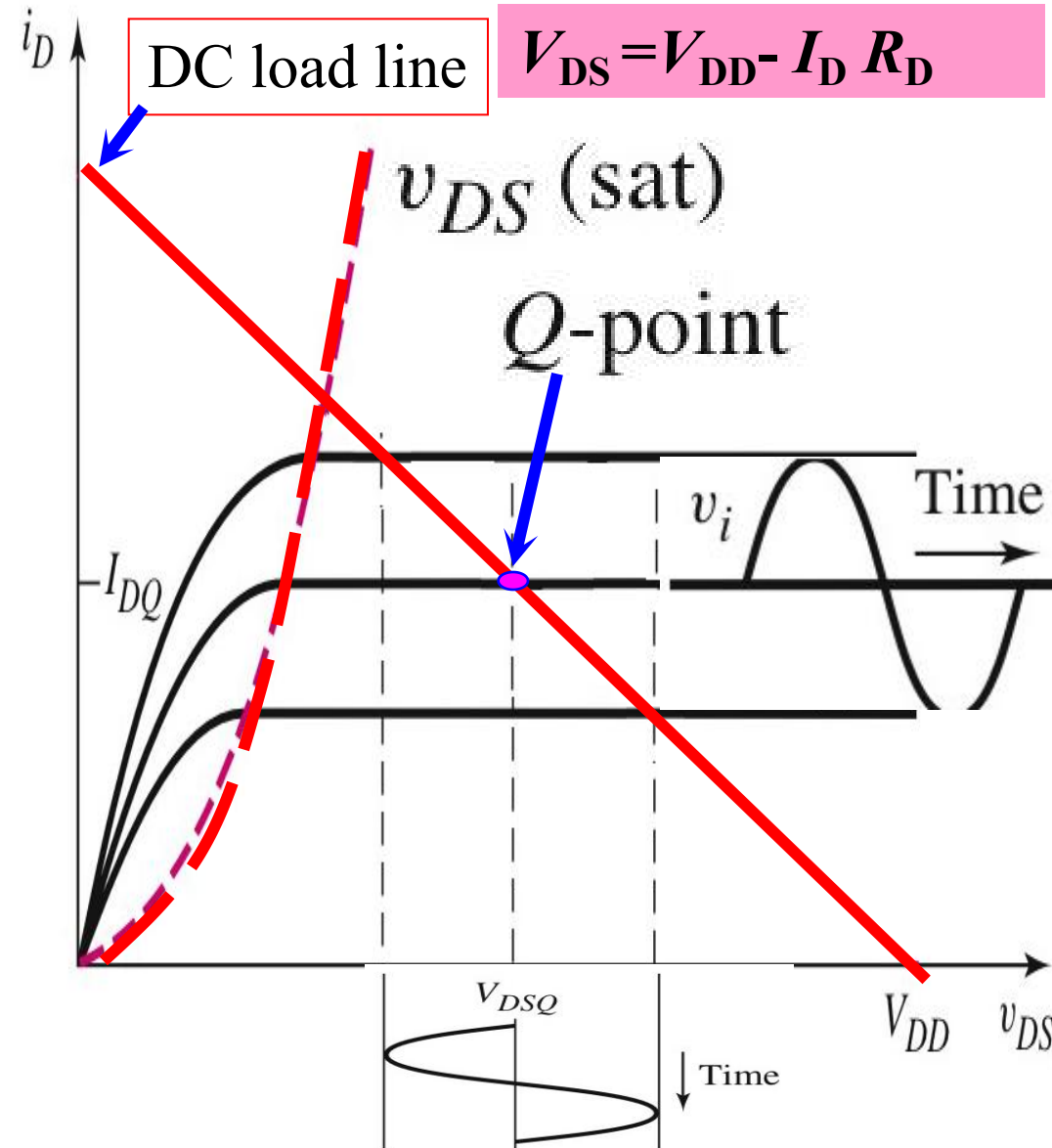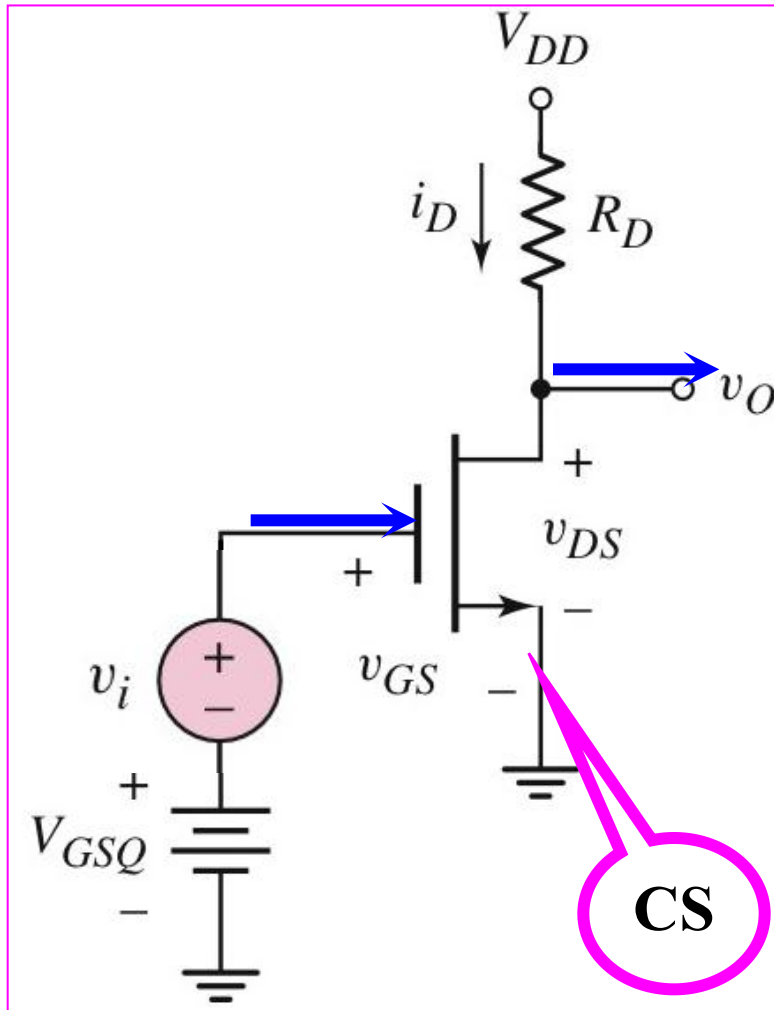4.1.1 Graphical Analysis, Load line, and small signal parameters



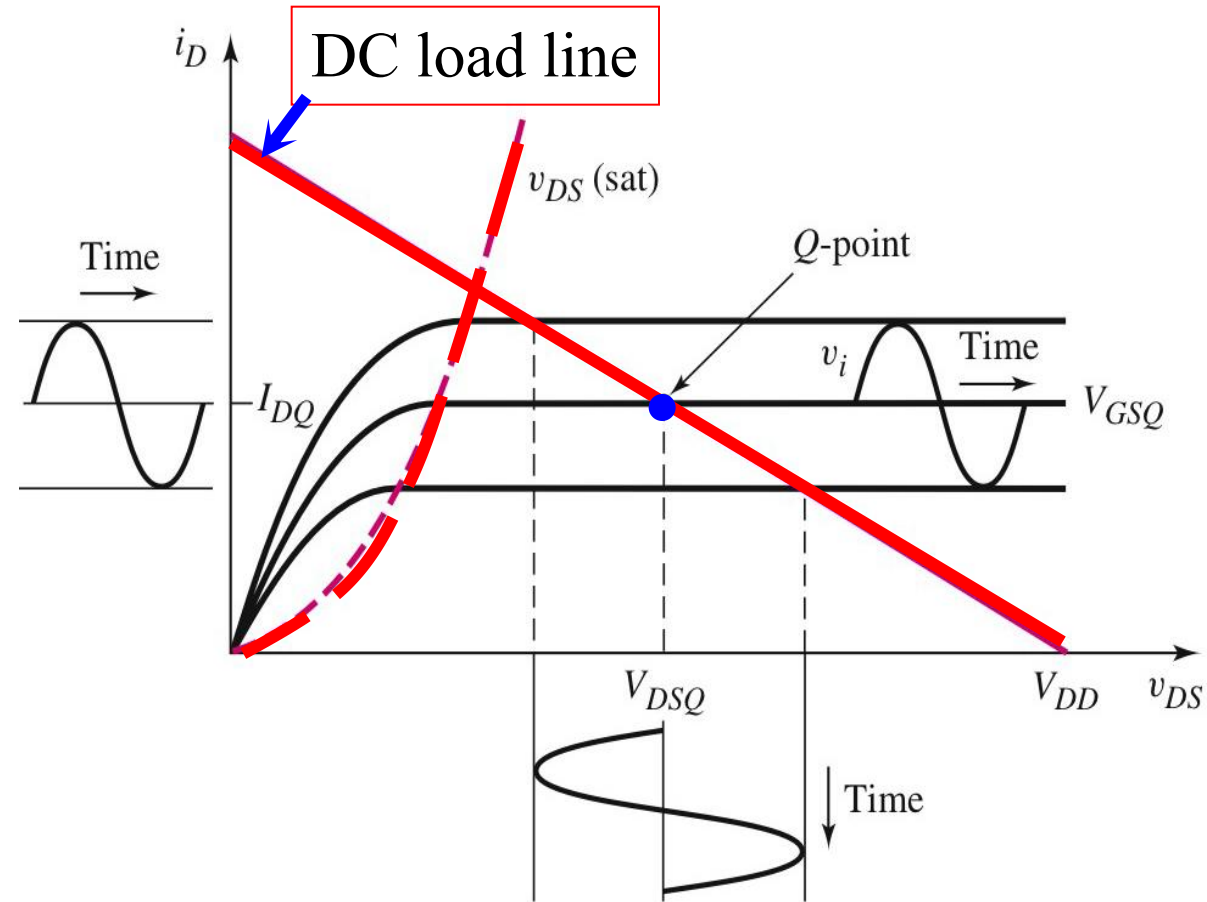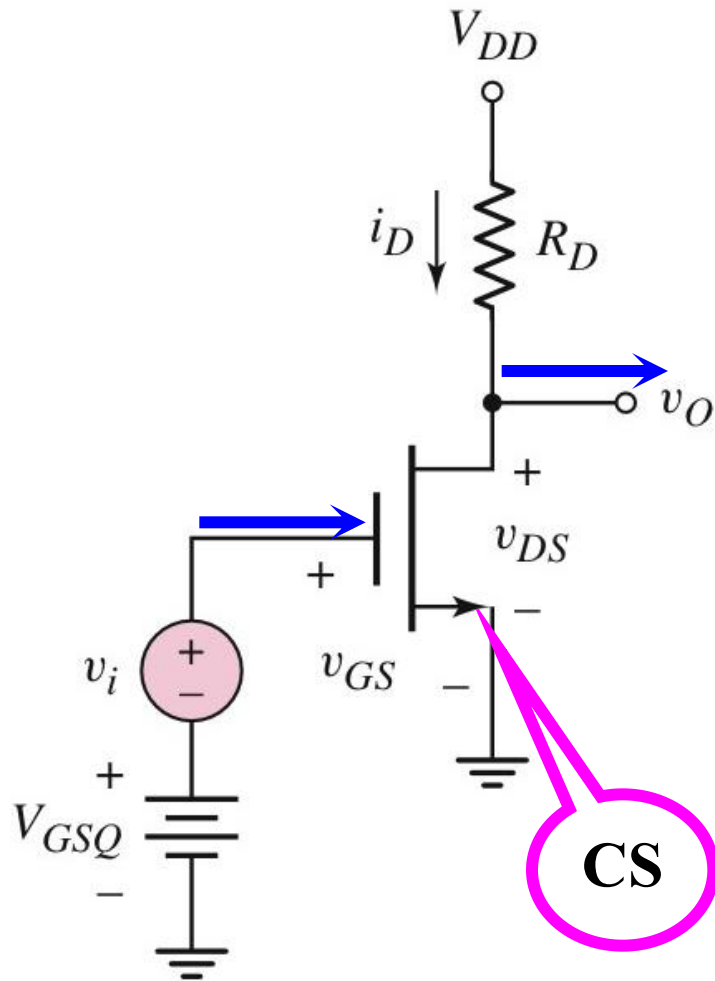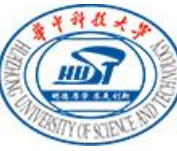4.1.1 Graphical Analysis, Load line, and small signal parameters



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

4.1.1 Graphical Analysis, Load line, and small signal parameters

Summary of notation	
Variable	Meaning
i_D, v_{GS}	Total instantaneous values
I_D, V_{GS}	DC values
i_d, v_{gs}	instantaneous ac values
I_d, V_{gs}	Phase values

4.1.1 Graphical Analysis, Load line, and small signal parameters


$$v_{GS} = V_{GSQ} + v_i = V_{GSQ} + v_{gs}$$

$$\begin{aligned} i_D &= K_n (V_{GS} - V_T)^2 \\ &= K_n (V_{GSQ} + v_{gs} - V_T)^2 \\ &= K_n (V_{GSQ} - V_T)^2 \\ &\quad + 2K_n (V_{GSQ} - V_T) v_{gs} + K_n v_{gs}^2 \\ &= I_{DQ} + g_m v_{gs} + \cancel{K_n v_{gs}^2} \end{aligned}$$

$$v_{gs} \ll 2(V_{GSQ} - V_T)$$

$$i_D = I_{DQ} + g_m v_{gs} = I_{DQ} + i_d$$



$$i_d = g_m v_{gs}$$

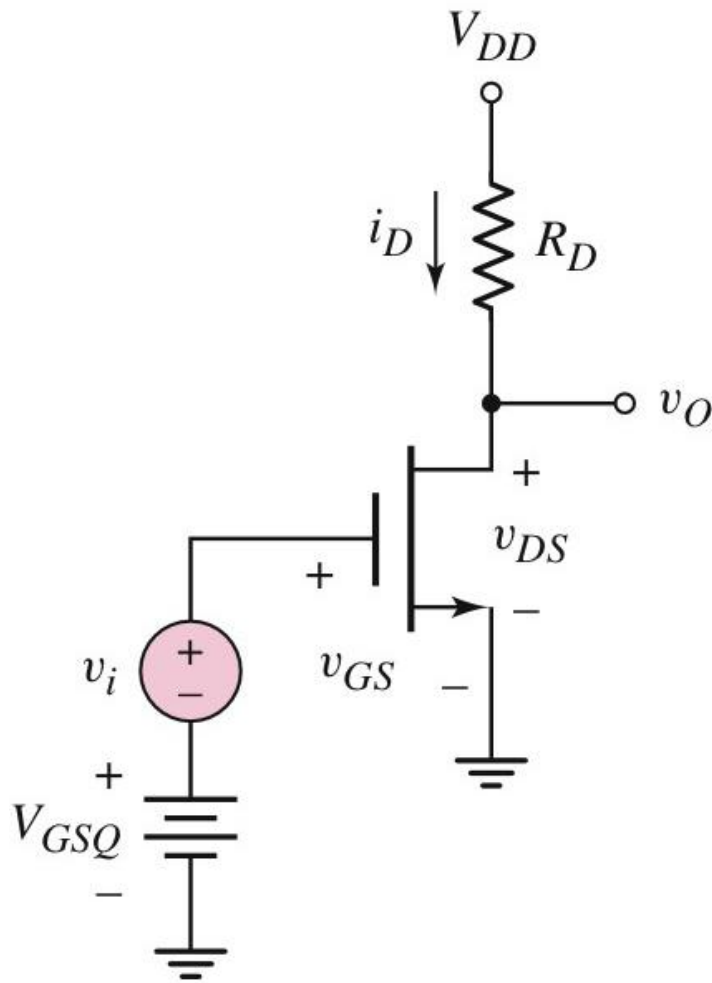

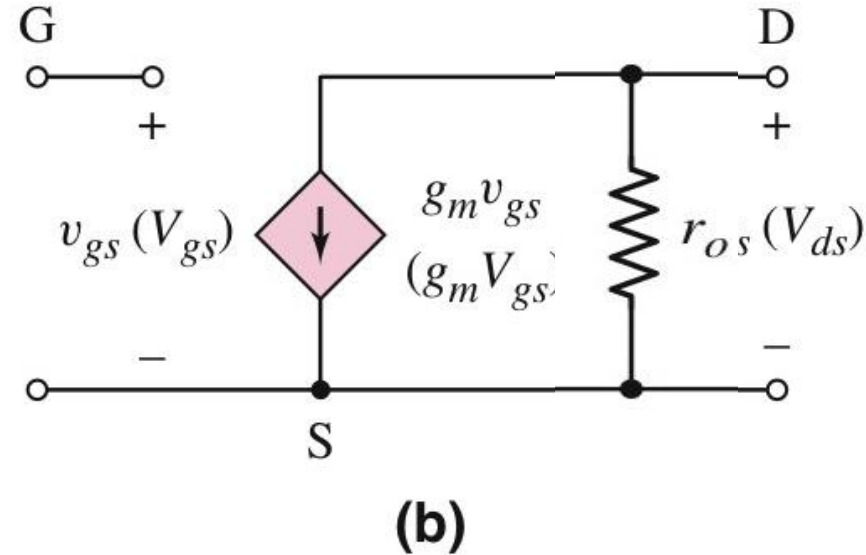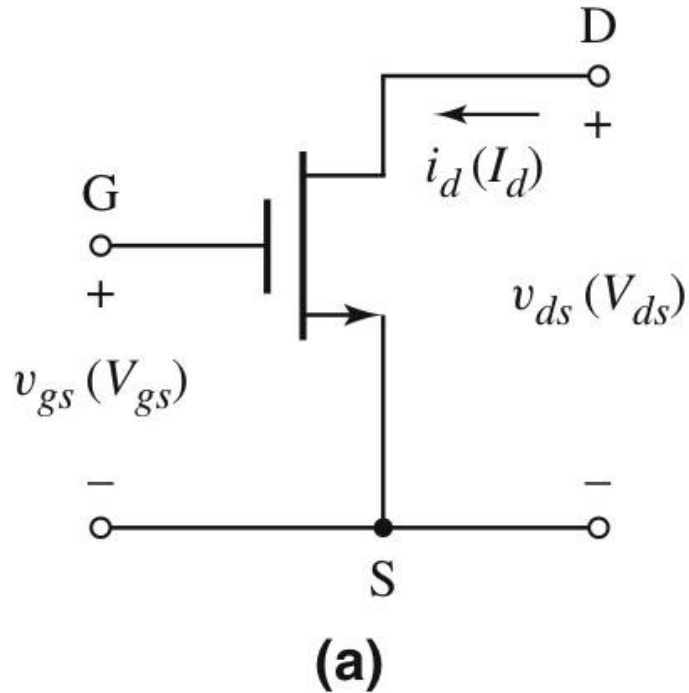4.1.2 small signal equivalent circuit



$$i_d = g_m v_{gs} \quad \lambda \neq 0$$



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$g_m = 2K_n (V_{GSQ} - V_{TN}) = 2\sqrt{K_n I_{DQ}}$$

4.1.1 Graphical Analysis, Load line, and small signal parameters

- Values depends on Q-point


$$g_m = \frac{\partial i_D}{\partial v_{GS}} = \frac{i_d}{v_{gs}}$$

$$g_m = 2K_n(V_{GSQ} - V_{TN}) = 2\sqrt{K_n I_{DQ}}$$


$$r_o = \left(\frac{\partial i_D}{\partial v_{DS}} \right)^{-1}$$

$$r_o = [\lambda K_n (V_{GSQ} - V_{TN})^2]^{-1} \cong [\lambda I_{DQ}]^{-1}$$

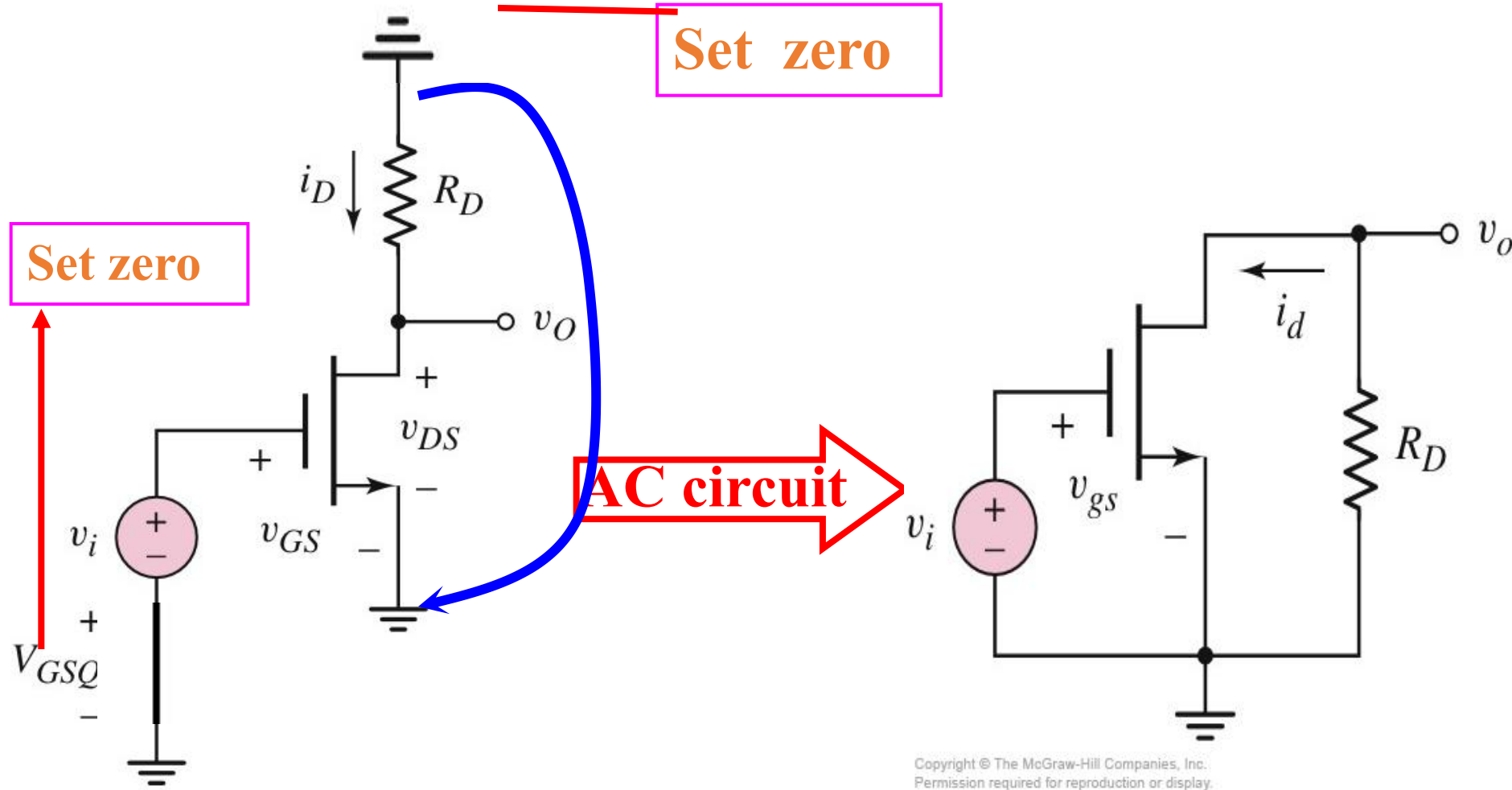4.1.1 Graphical Analysis, Load line, and small signal parameters




4.1.2 small signal equivalent circuit

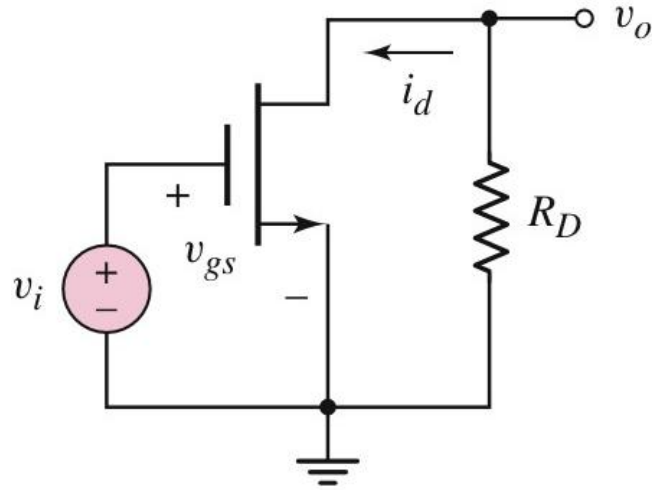


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

small signal equivalent circuit

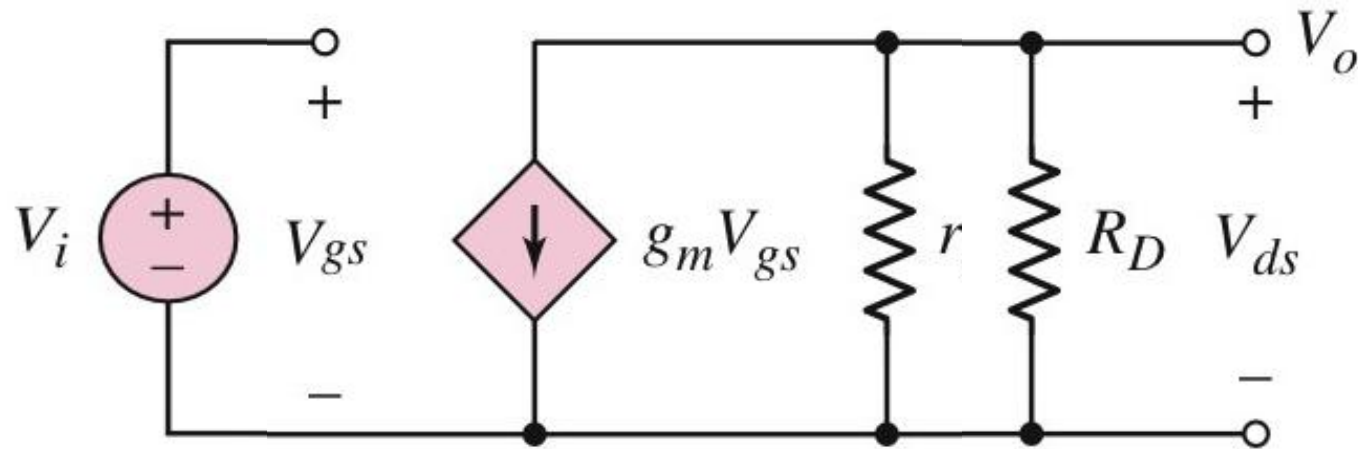

4..1.2 small signal equivalent circuit

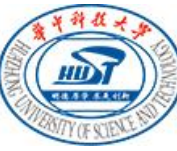

$$V_{GSQ}=2.12V$$


$$V_{DD}=5V$$

$$R_D=2.5k\Omega$$

$$V_{TN}=1V$$

$$K_n=0.80mA/V^2$$

$$\lambda=0.02V^{-1}$$

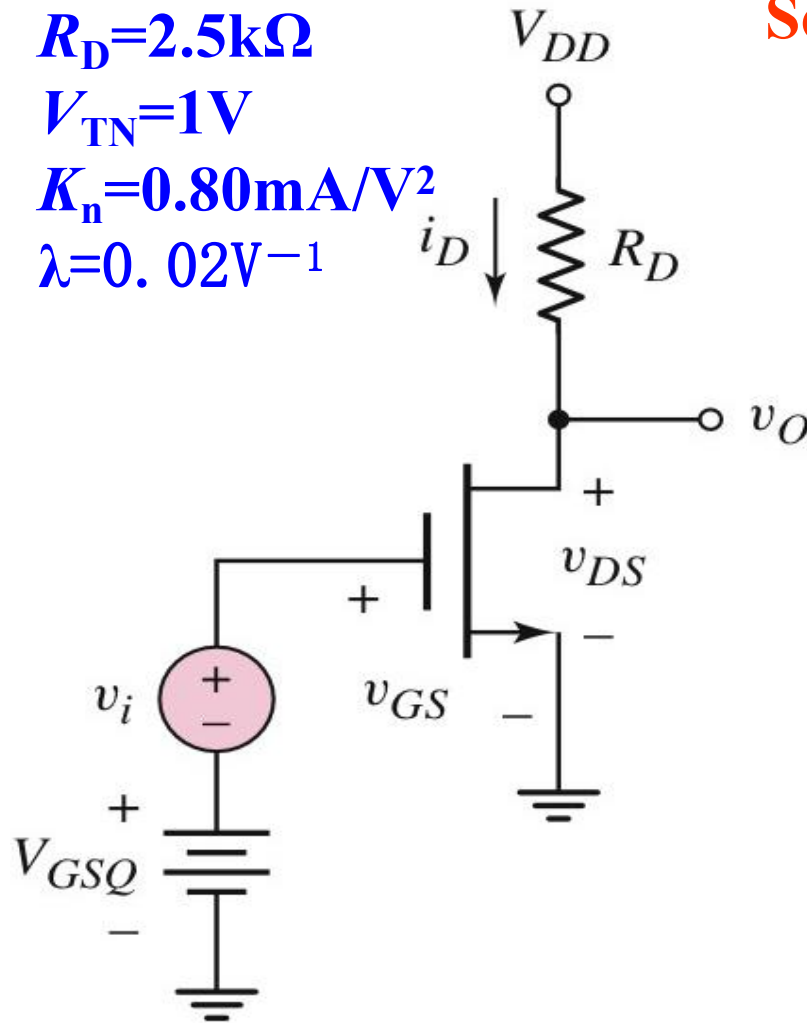

Determine small voltage gain.

Sol:
$$I_D = K_n (V_{GS} - V_{TN})^2$$
$$= 0.8(2.12 - 1)^2 = 1mA$$

$$V_{DS} = V_{DD} - I_D R_D = 5 - 1 \times 2.5 = 2.5V$$

$$V_{DSQ} = 2.5V > V_{GS} - V_{TN}$$
$$= 2.12 - 1 = 1.12V$$

Which region? Saturation region

$$g_m = 2K_n (V_{GSQ} - V_{TN})$$
$$= 2 \times 0.8(2.12 - 1) = 1.79mS$$

4.1.2 small signal equivalent circuit

Determine small voltage gain.

$$V_{GSQ}=2.12V$$


$$V_{DD}=5V$$

$$R_D=2.5k\Omega$$


$$V_{TN}=1V$$

$$K_n=0.80mA/V^2$$

$$\lambda=0.02V^{-1}$$

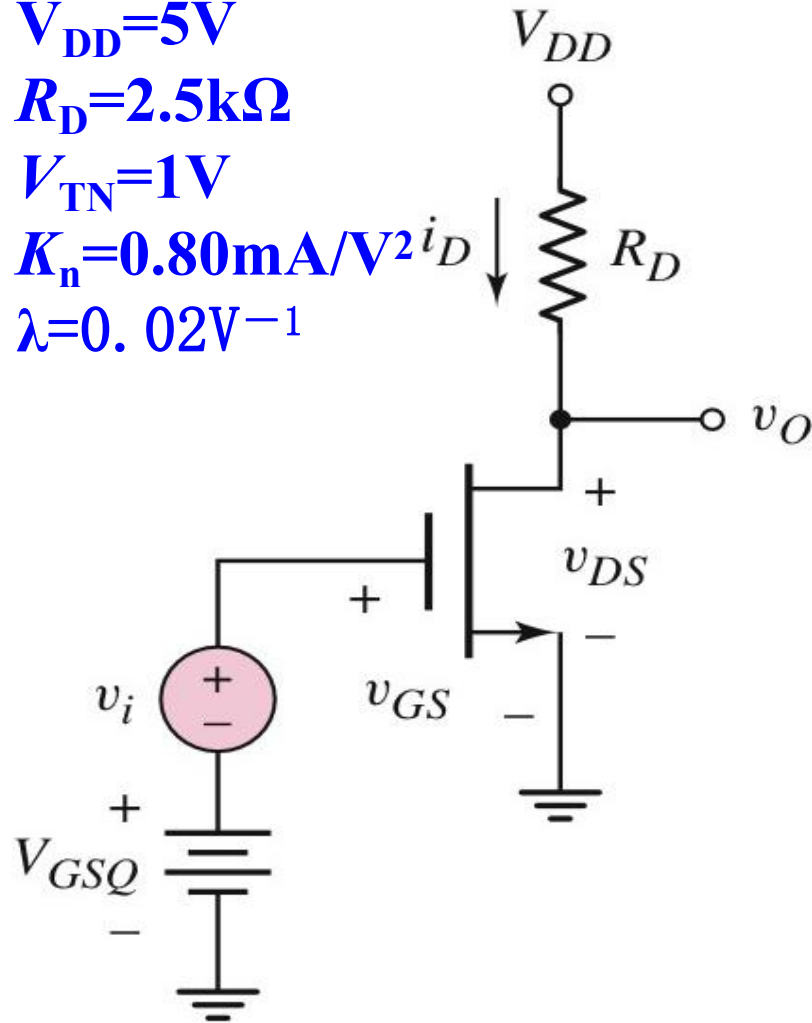

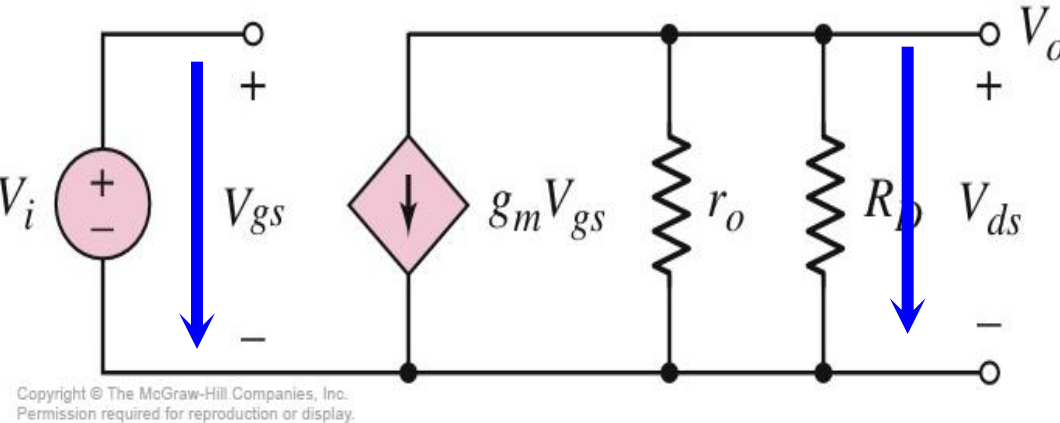
Sol: $r_o \cong [\lambda I_{DQ}]^{-1} = 50k\Omega$



$$V_i = V_{gs}$$

$$V_o = -g_m \cdot V_{gs} \cdot (r_o \parallel R_D)$$

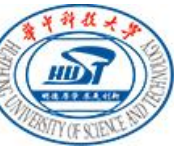
$$A_v = V_o / V_i = -g_m (r_o \parallel R_D) = -4.26$$



4..1.2 small signal equivalent circuit

Problem-Solving Technique: MOSFET AC Analysis

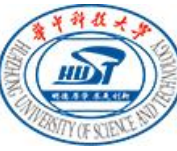- 1. Analyze circuit with only the dc sources to find quiescent solution.
Transistor must be biased in saturation region for linear amplifier.**
- 2. Replace elements with small-signal model.**
- 3. Analyze small-signal equivalent circuit, setting dc sources to zero,
to produce the circuit to the time-varying input signals only.**



Ch4 Basic FET Amplifiers

4.1 The MOSFET Amplifier

4.2 Basic Transistor Amplifier Configurations

4.3 The Common Source Amplifier

4.4 The Common Drain (Source Follower) Amplifier

4.5 The Common Gate Configuration

4.5.1 Small voltage and current gains


4.5.2 Input and output Impedance

4.6 The Three Basic Amplifier Configuration: Summary and comparison


4.2 Basic Transistor Amplifier Configurations

Common source

Common Drain

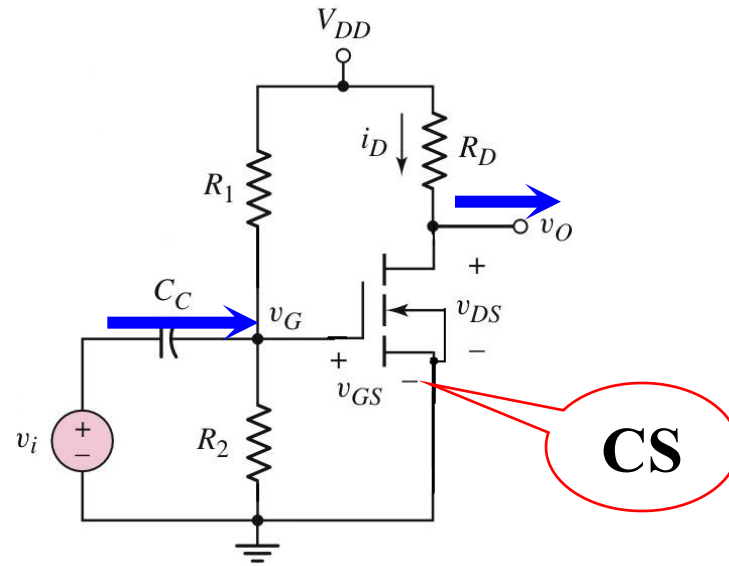

Common gate

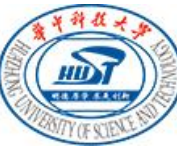

Ch4 Basic FET Amplifiers

4.1 The MOSFET Amplifier

4.2 Basic Transistor Amplifier Configurations

4.3 The Common Source Amplifier

4.4 The Common Drain (Source Follower) Amplifier

4.5 The Common Gate Configuration

4.5.1 Small voltage and current gains

4.5.2 Input and output Impedance

4.6 The Three Basic Amplifier Configuration: Summary and comparison

4.3 The Common Source Amplifier

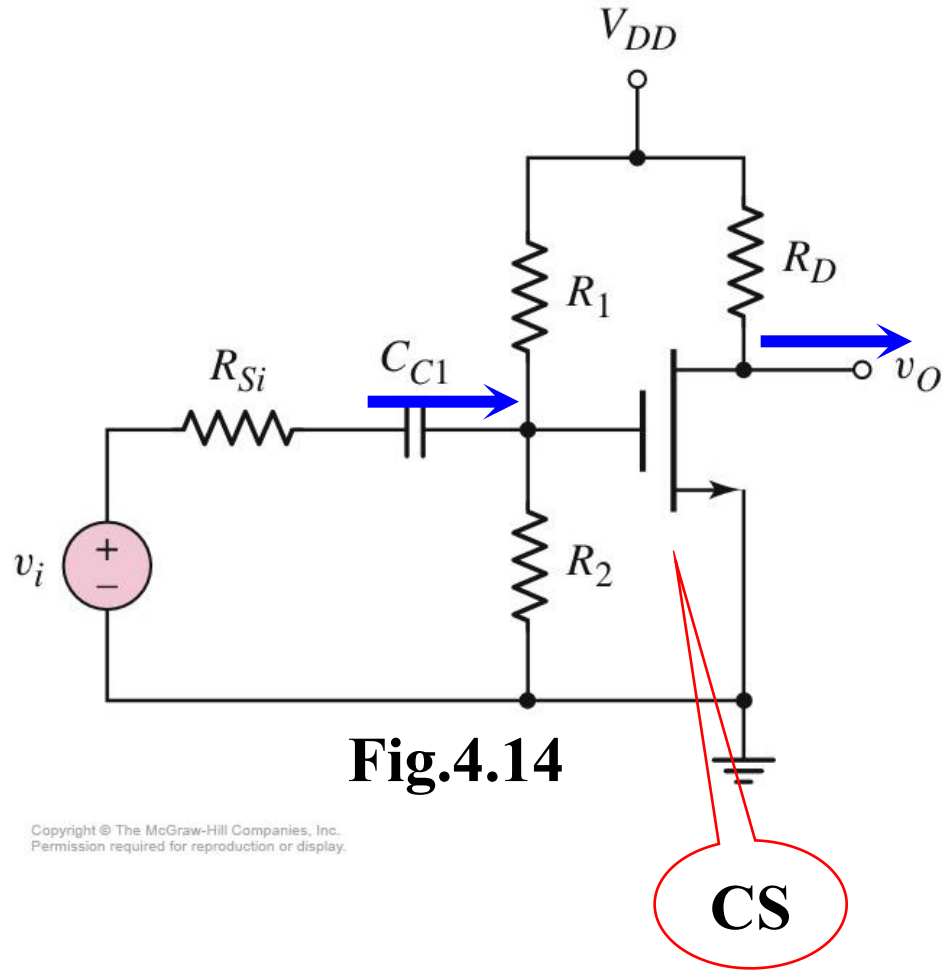
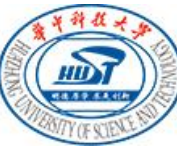


Fig.4.14

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

DC analysis:

Coupling capacitor is assumed to be open.

AC analysis:

Coupling capacitor is assumed to be a short.

DC voltage supply is set to zero volts.

4.3 The Common Source Amplifier



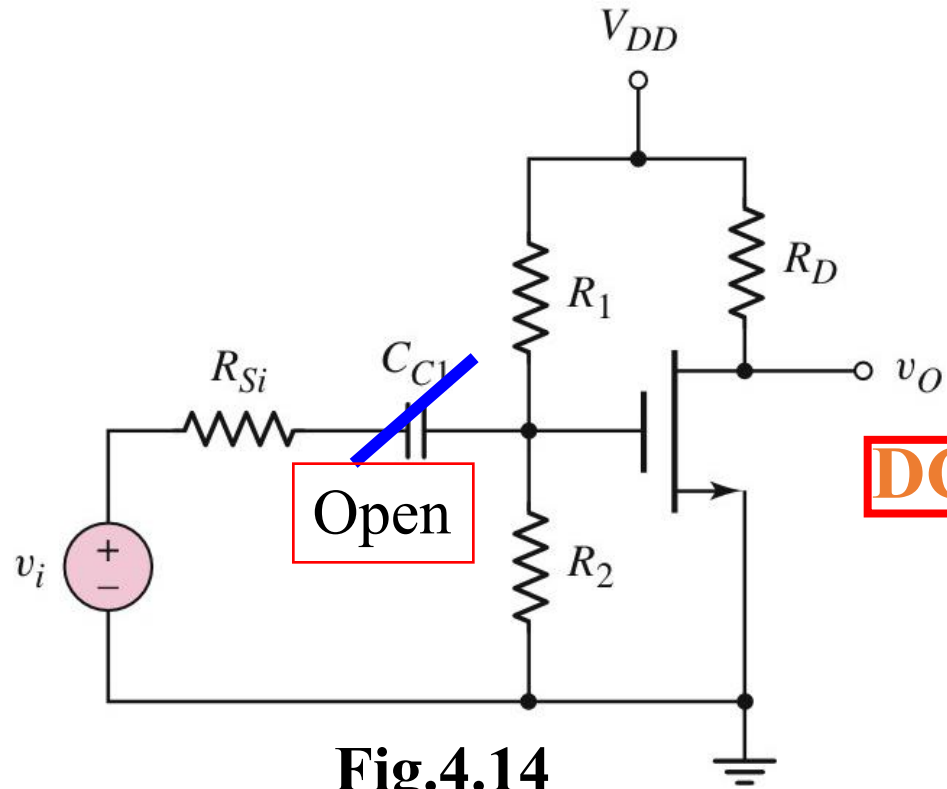
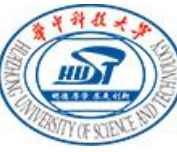


Fig.4.14

DC circuit

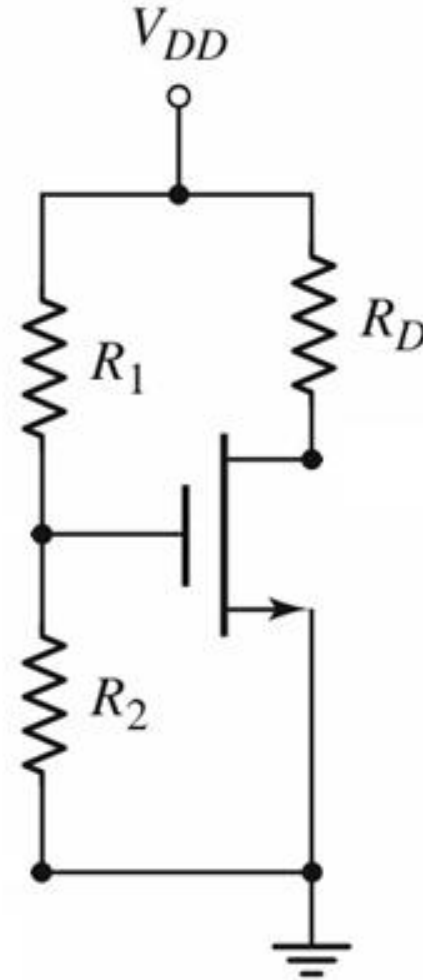

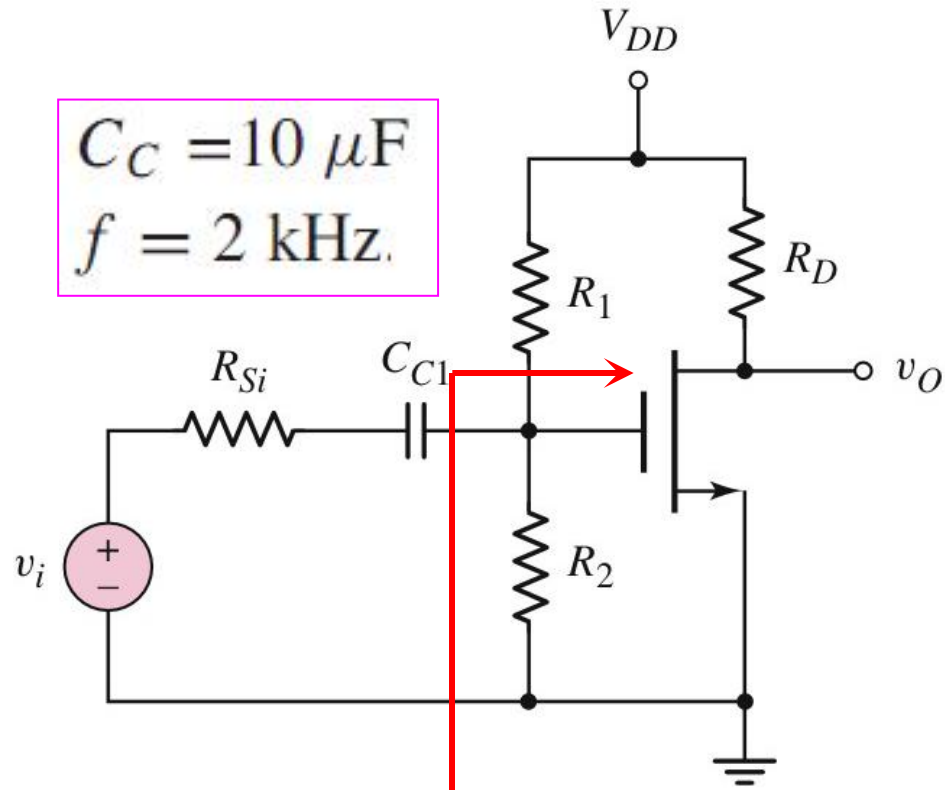4.3.1 A Basic Common Source Configuration



$$C_C = 10 \mu\text{F}$$

$$f = 2 \text{ kHz}$$

$$|Z_c| = \frac{1}{2\pi f C_C}$$

$$= \frac{1}{2\pi (2 \times 10^3) (10 \times 10^{-6})} \cong 8 \Omega$$

2-port Networks equivalent
input impedance

$$R_1 \parallel R_2$$

$$|Z_c| \ll R_1 \parallel R_2$$

Fig.4.14

capacitor is essentially a short circuit to signals with frequencies greater than 2 kHz.

4.3.1 A Basic Common Source Configuration



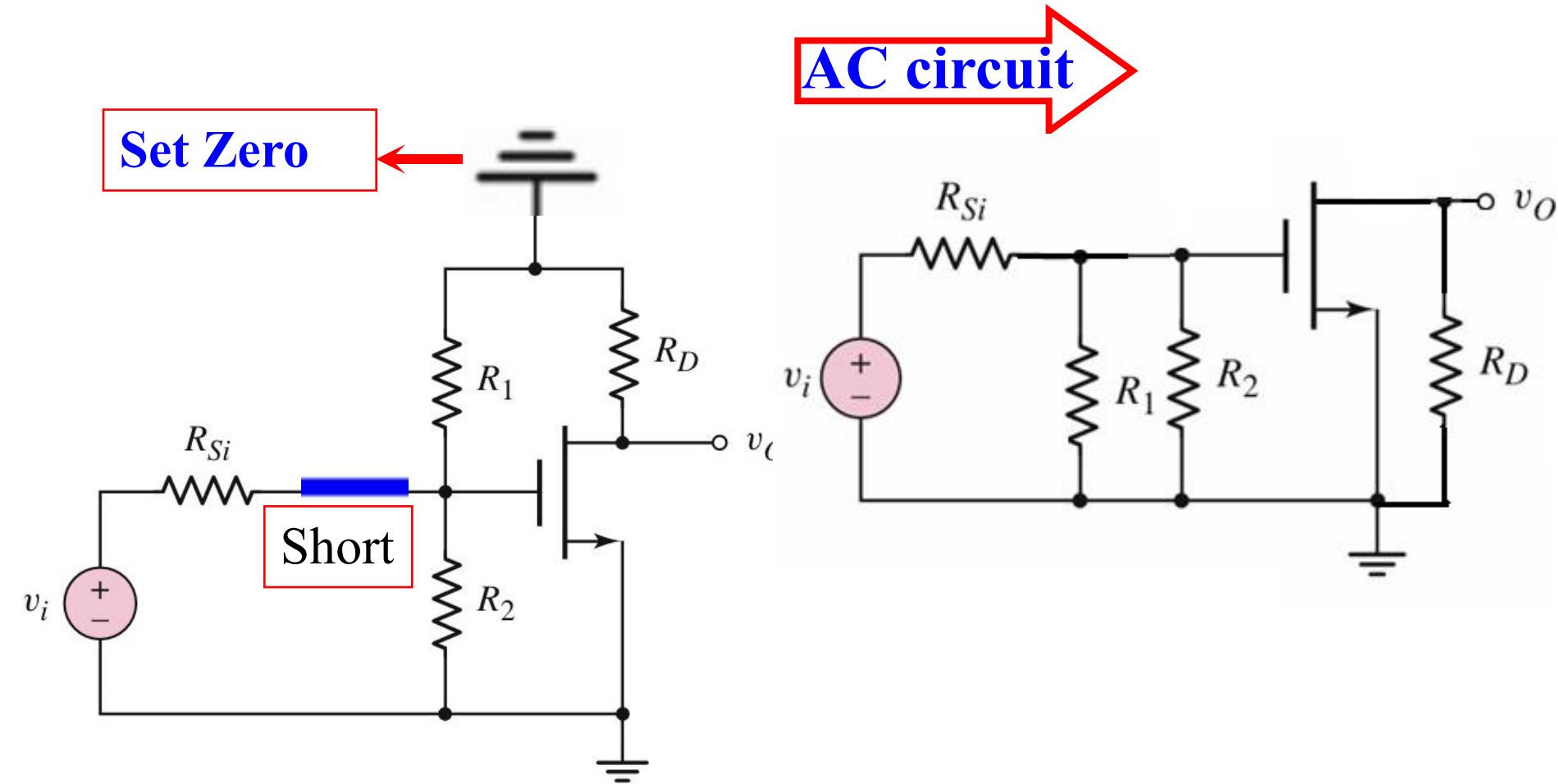
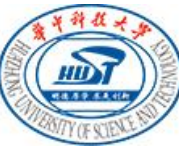


Fig.4.14

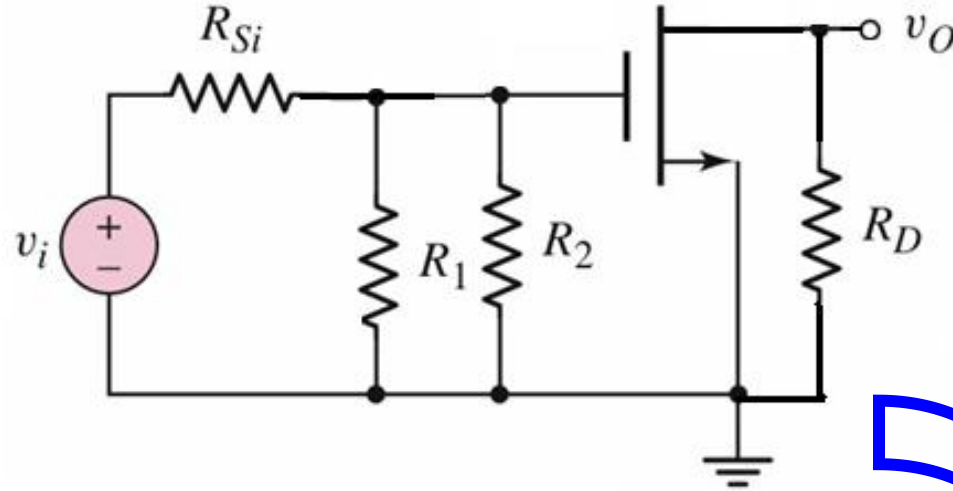
4.3.1 A Basic Common Source Configuration





AC circuit

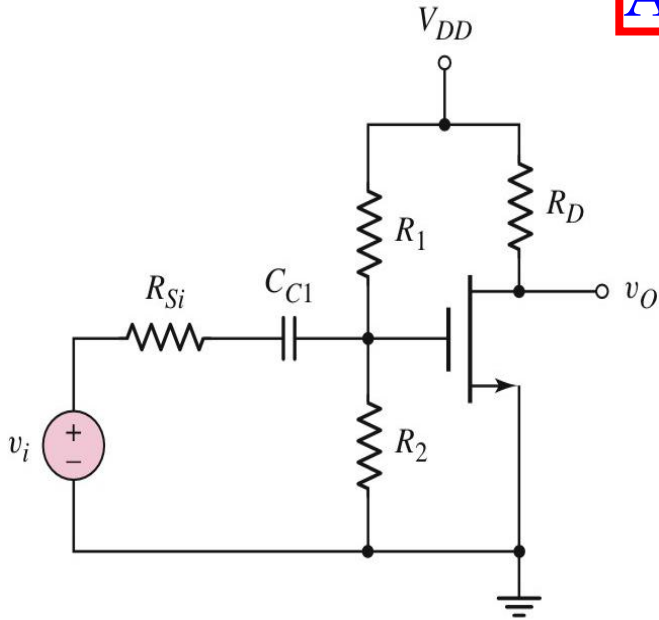

Small-Signal Equivalent Circuit

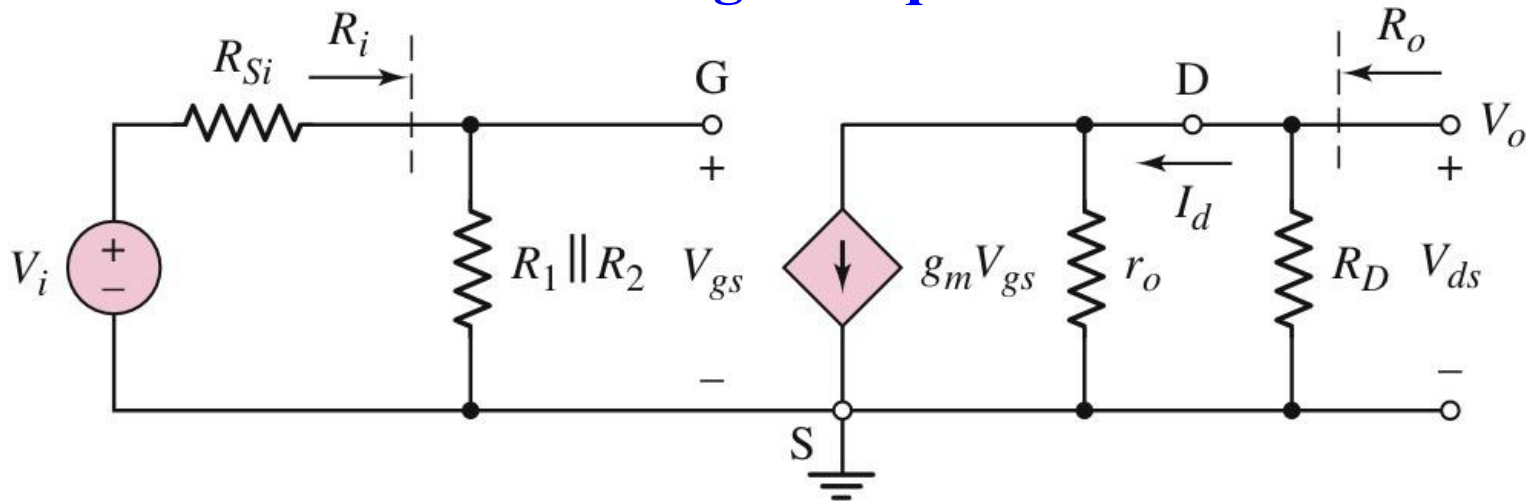

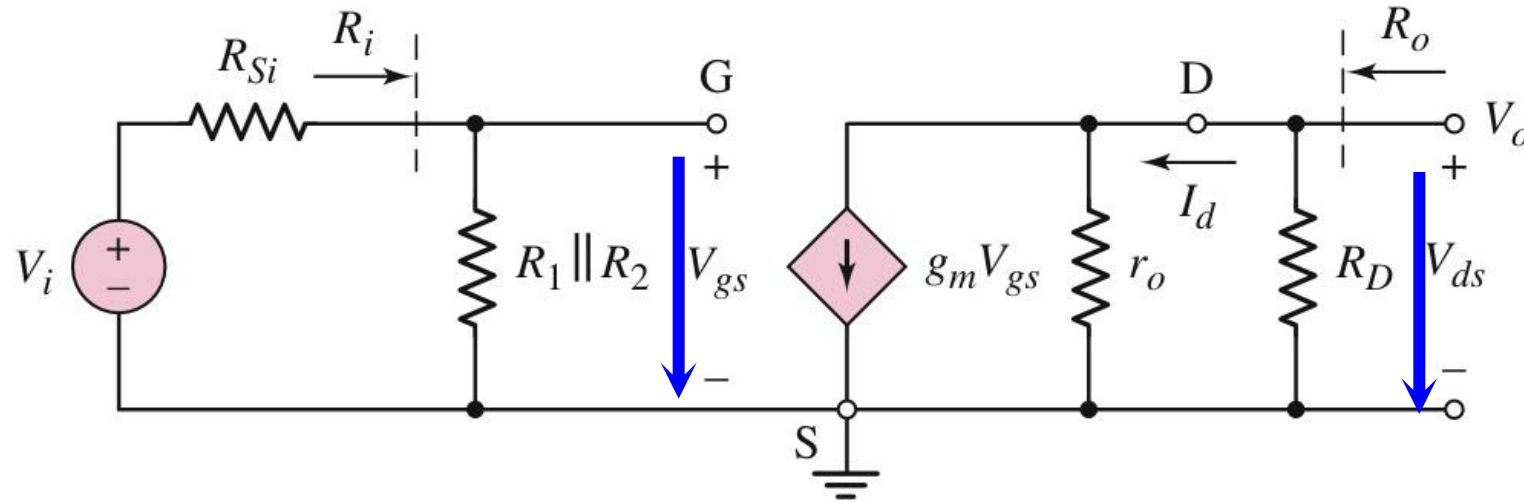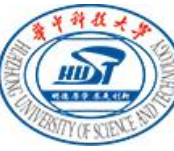4.3.1 A Basic Common Source Configuration




Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$V_{gs} = V_i \cdot \left(\frac{R_i}{R_i + R_{Si}} \right) \quad V_o = -g_m \cdot V_{gs} \cdot (r_o \parallel R_D)$$

$$A_v = V_o / V_i = -g_m (r_o \parallel R_D) \left(\frac{R_i}{R_i + R_{Si}} \right)$$

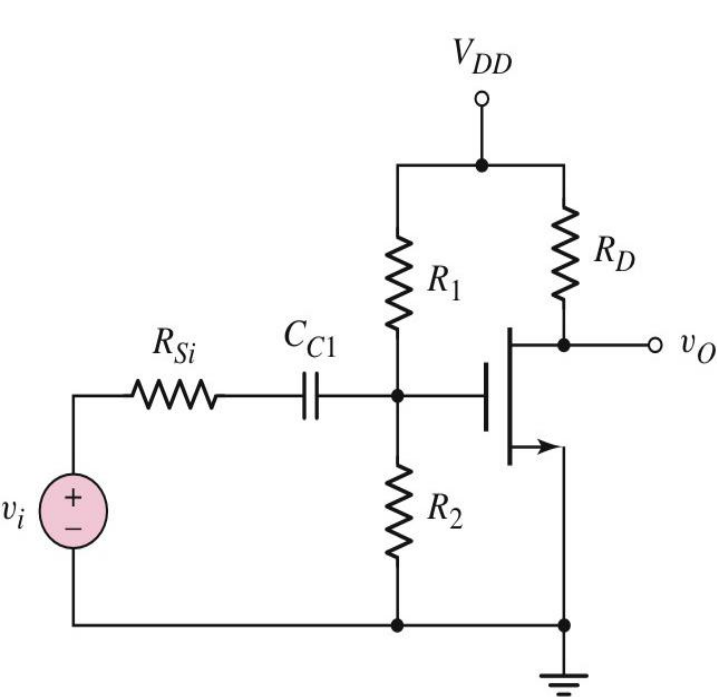4.3.1 A Basic Common Source Configuration



Q-point near the middle of the saturation region for maximum symmetrical output voltage swing.

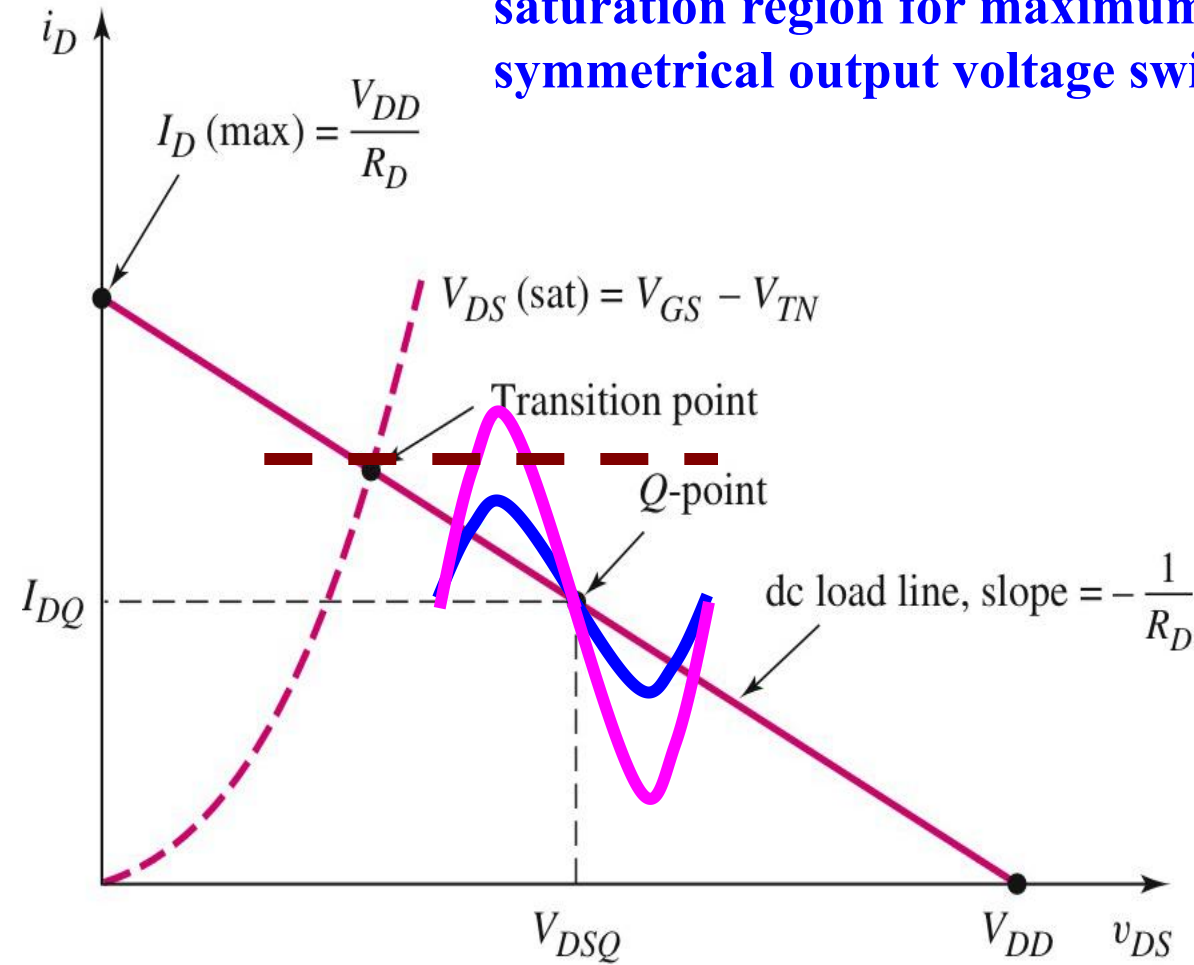


Fig.4.14

Small AC input signal for output response to be linear.

4.3.1 A Basic Common Source Configuration

$$V_{DD}=10V$$

$$R_1=70.9k\Omega, R_2=29.1k\Omega$$


$$R_D=2.5k\Omega$$

$$V_{TN}=1.5V$$

$$K_n=0.50mA/V^2$$


$$\lambda=0.01V^{-1}$$

$$R_{Si}=2.5k\Omega$$

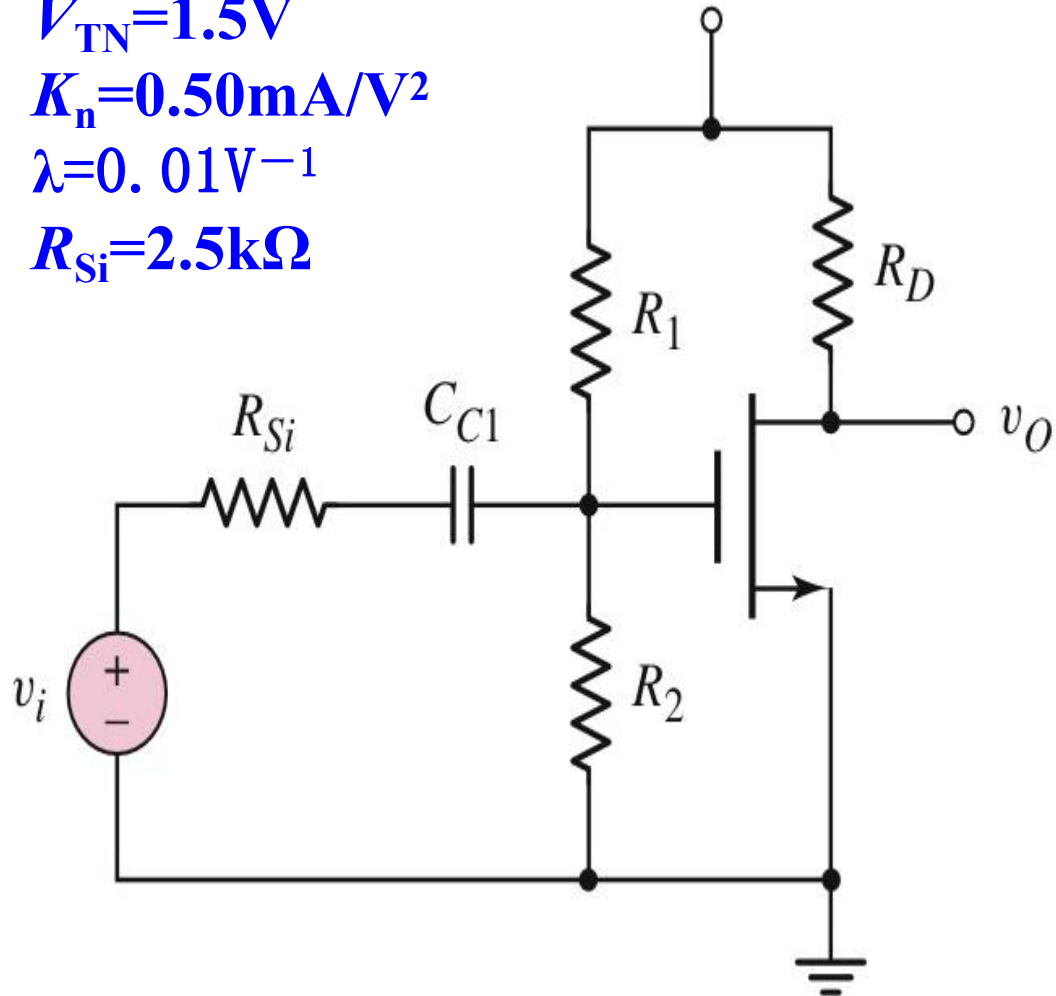


SOL:

DC Analysis

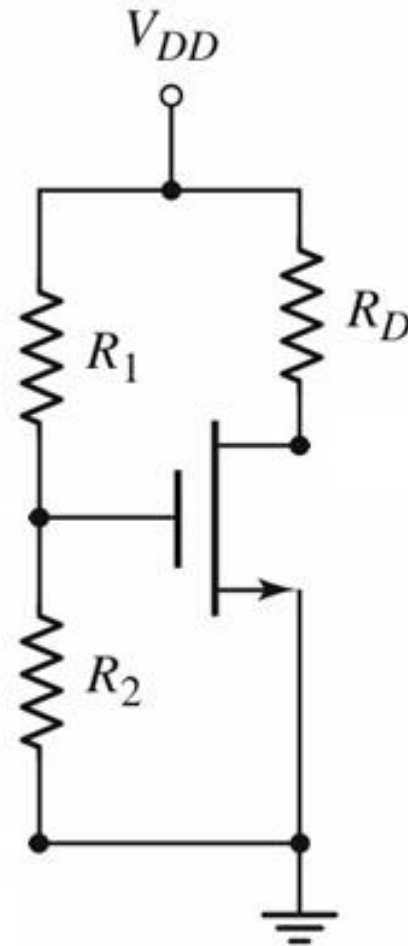

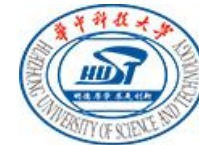4.3.1 A Basic Common Source Configuration



$$V_{DD}=10V$$

$$R_1=70.9k\Omega$$

$$R_2=29.1k\Omega$$


$$R_D=5k\Omega$$

$$V_{TN}=1.5V$$

$$K_n=0.50mA/V^2$$

$$\lambda=0.01V^{-1}$$

$$R_{Si}=4k\Omega$$

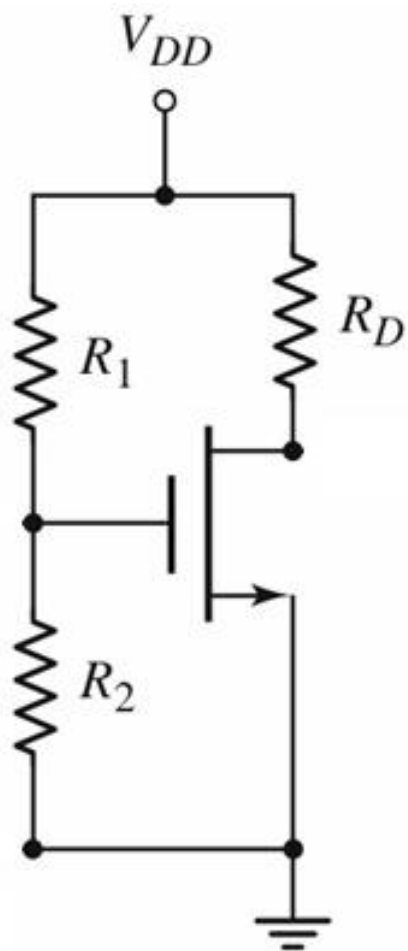

SOL:

DC Analysis

$$V_{GSQ} = \frac{R_2}{R_1 + R_2} V_{DD}$$

$$= \frac{29.1}{70.9 + 29.1} 10 = 2.91V$$

$$I_D = K_n (V_{GS} - V_{TN})^2$$

$$= 0.5(2.91 - 1.5)^2 = 1mA$$

$$V_{DSQ} = 5V > V_{GS} - V_{TN}$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$= 10 - (1)(5) = 5V$$

Saturation region

$$= 2.91 - 1.5 = 1.41V$$

4.3.1 A Basic Common Source Configuration

$$V_{DD}=10V$$

$$R_1=70.9k\Omega, R_2=29.1k\Omega$$

$$R_D=2.5k\Omega$$

$$V_{TN}=1.5V$$


$$K_n=0.50mA/V^2$$

$$\lambda=0.01V^{-1}$$


$$R_{Si}=2.5k\Omega$$

$$\begin{aligned} g_m &= 2K_n(V_{GSQ} - V_{TN}) \\ &= 2 \times 0.5(2.91 - 1.5) \\ &= 1.41mS \end{aligned}$$
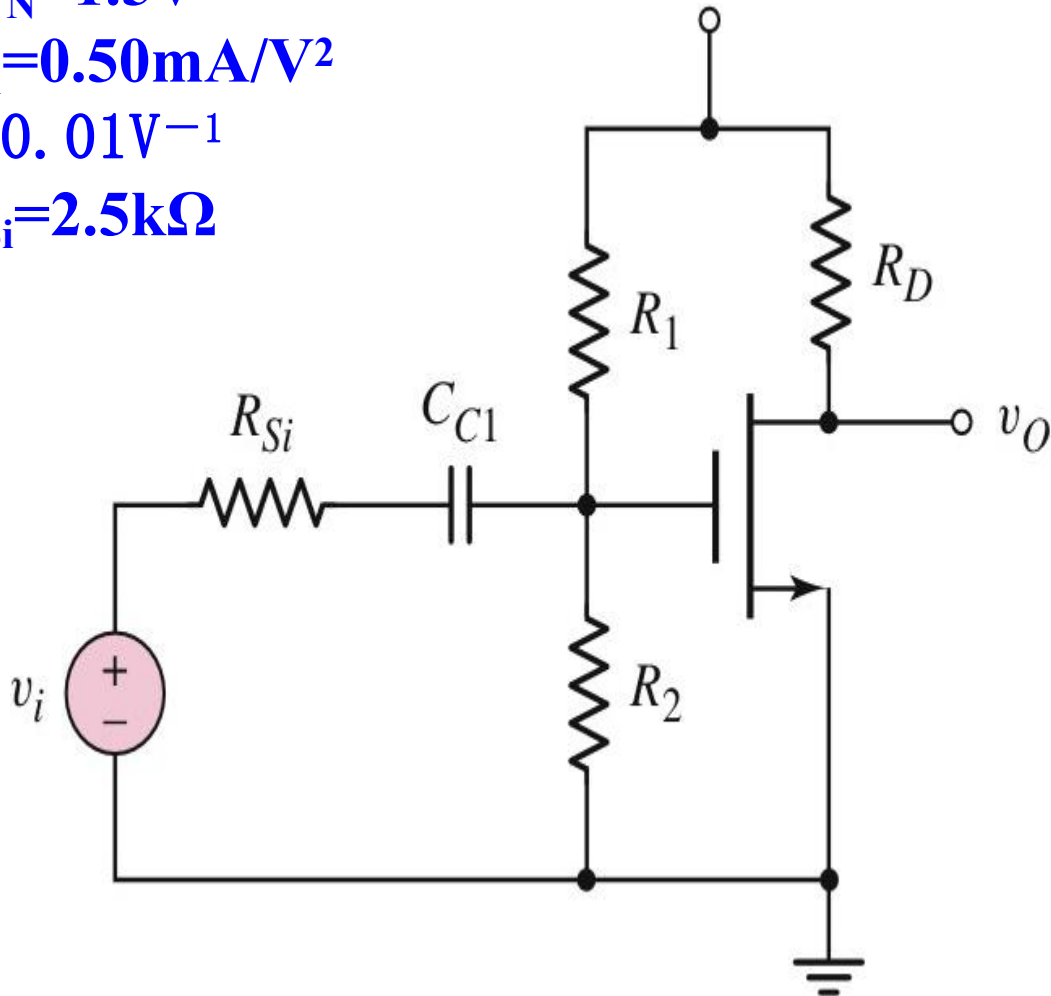
$$r_o \cong [\lambda I_{DQ}]^{-1} = 100k\Omega$$



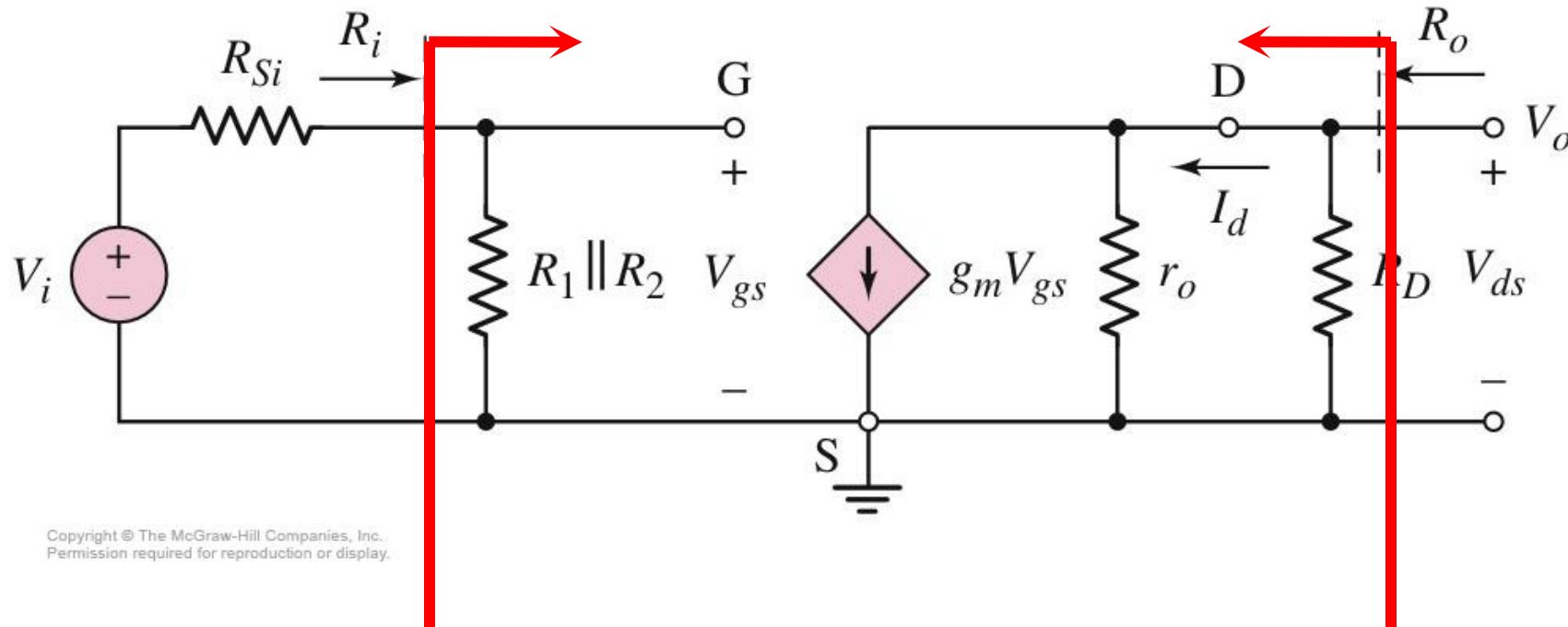
4.3.1 A Basic Common Source Configuration



$$R_i = R_1 // R_2 = 70.9 // 29.1 = 20.6 \text{ k}\Omega \quad ?$$

$$R_o = R_D // r_o = 5 // 100 = 4.76 \text{ k}\Omega \quad ?$$

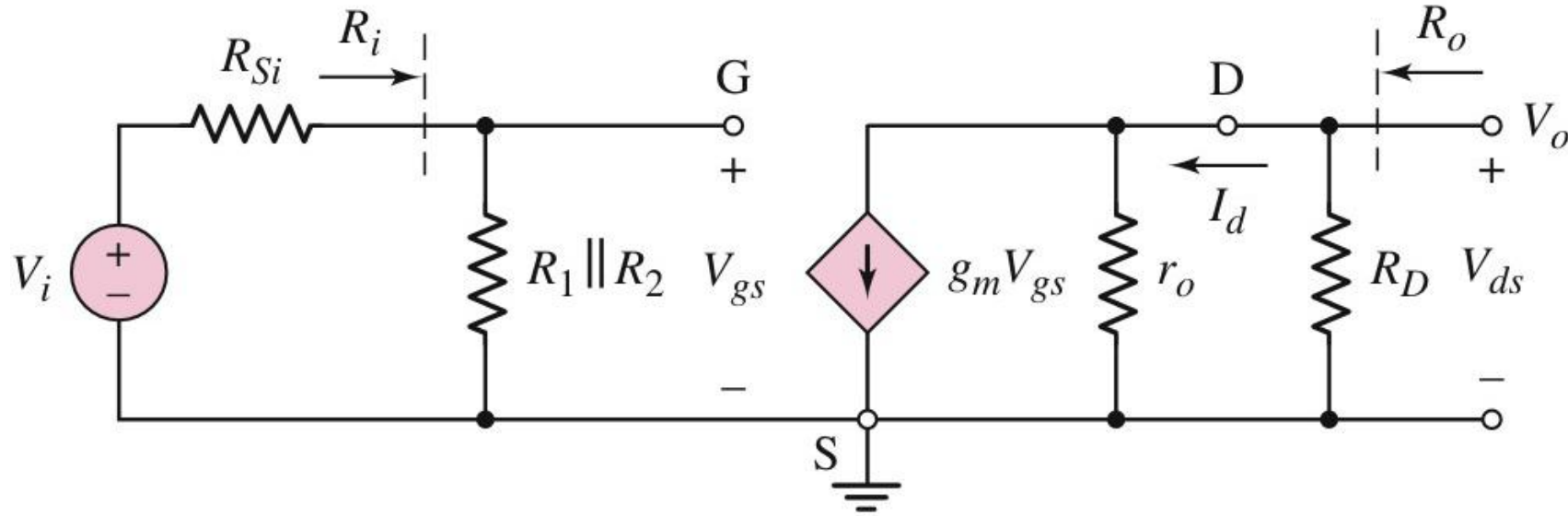4.3.1 A Basic Common Source Configuration



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$V_{gs} = V_i \cdot \left(\frac{R_i}{R_i + R_{Si}} \right) \quad V_o = -g_m \cdot V_{gs} \cdot (r_o \parallel R_D)$$

$$A_v = V_o / V_i = -g_m (r_o \parallel R_D) \left(\frac{R_i}{R_i + R_{Si}} \right) = -5.62$$

4.3.2 Common Source Amplifier with Source resistor

SOL:

DC Analysis


$$V_{GSQ} = 1.50\text{V}$$

$$I_D = 0.50\text{mA}$$

$$V_{DS} = 6.25\text{V}$$

$$g_m = 2K_n(V_{GSQ} - V_{TN}) = 1.4\text{mS}$$
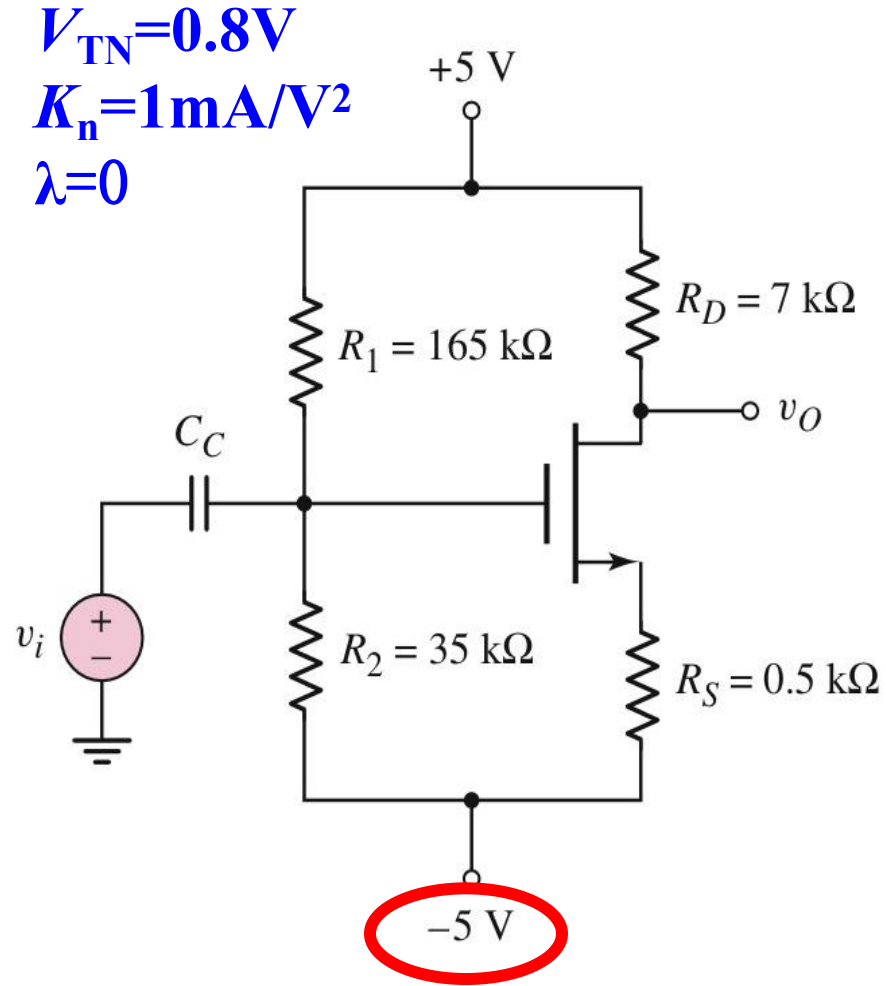
$$r_o \cong [\lambda I_{DQ}]^{-1} = \infty$$




Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.


Fig.4.19

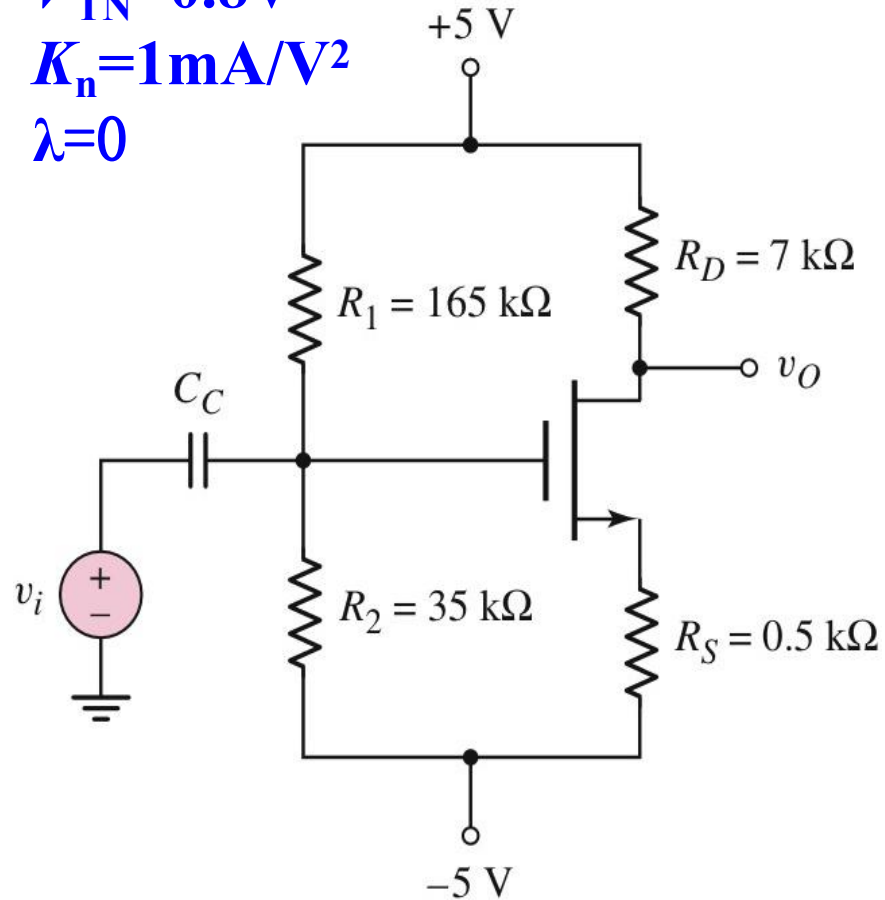4.3.2 Common Source Amplifier with Source resistor

$V_{TN}=0.8V$
 $K_n=1mA/V^2$
 $\lambda=0$



Small-Signal Equivalent Circuit

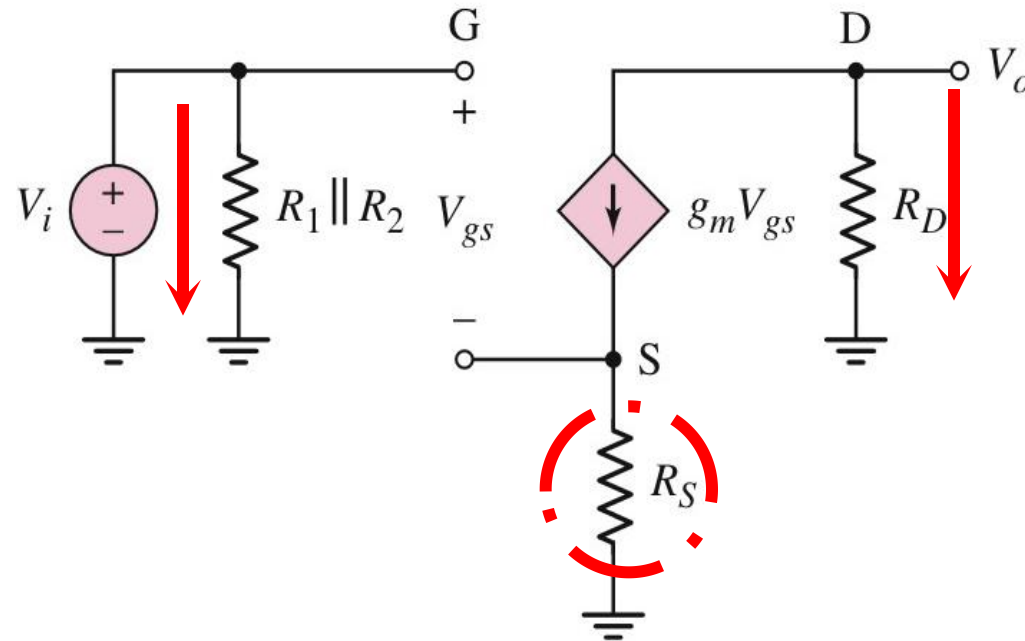

$$V_o = -g_m \cdot V_{gs} \cdot R_D$$

$$V_i = V_{gs} + g_m \cdot V_{gs} \cdot R_S$$


$$A_v = \frac{-g_m R_D}{1 + g_m R_S}$$

4.3.3 Common Source Circuit with Source bypass Capacitor

$$V_{TN} = 0.8V$$

$$K_n = 1\text{mA/V}^2$$

$$\lambda = 0$$

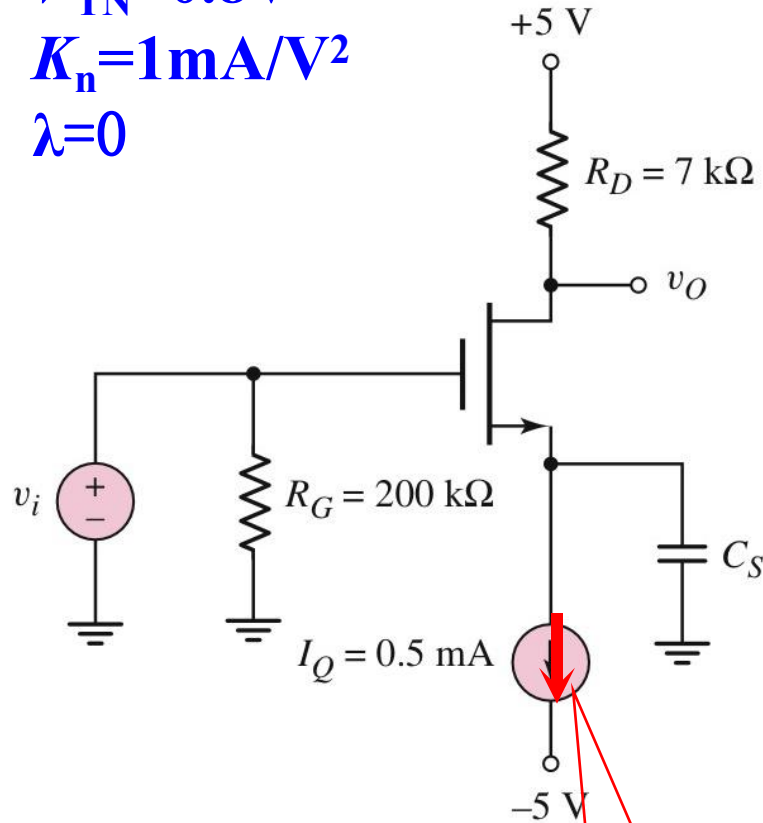

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

SOL:
DC Analysis

$$I_D = K_n (V_{GS} - V_{TN})^2 = 0.5\text{mA}$$

$$V_{GSQ} = -V_S = 1.51V$$

$$V_{DS} = V_{DD} - I_D R_D - V_S = 3.01V$$

$$V_{DSQ} = 3.01V > 1.51 - 0.8$$

$$= 0.71V$$

$$g_m = 2K_n (V_{GSQ} - V_{TN})$$

$$= 2 \cdot 1(1.51 - 0.8)$$

$$= 1.42\text{mS}$$



4.3.3 Common Source Circuit with Source bypass Capacitor

$$V_{TN} = 0.8V$$

$$K_n = 1 \text{ mA/V}^2$$

$$\lambda = 0$$

Small-signal equivalent circuit

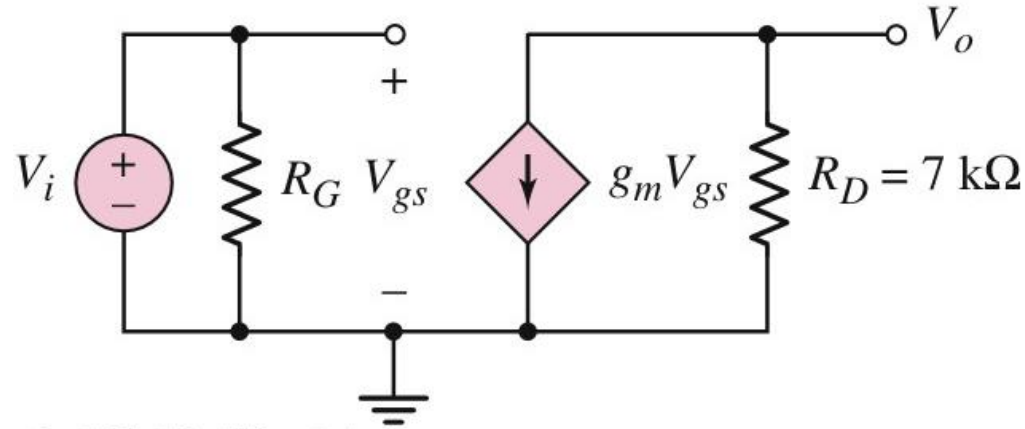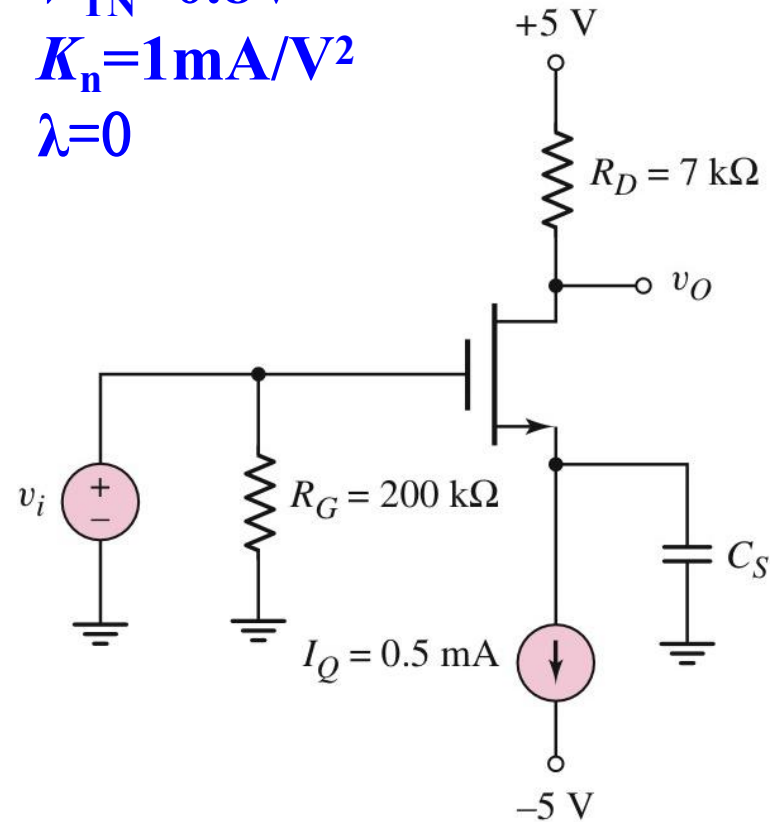


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$V_o = -g_m \cdot V_{gs} \cdot R_D$$

$$A_v = -g_m R_D = -9.9$$

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Contents

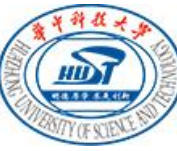

PART 1 SEMICONDUCTOR DEVICES AND BASIC APPLICATIONS

Chapter 1 Semiconductor Materials and Diodes

Chapter 2 Diode Circuits

Chapter 3 The Field-Effect Transistor

 **Chapter 4 Basic FET Amplifiers**

Chapter 5 The Bipolar Junction Transistor

Chapter 6 Basic BJT Amplifiers

Chapter 7 Frequency Response

Chapter 8 Output Stages and Power Amplifiers

PART 2 ANALOG ELECTRONICS

Chapter 9 Ideal Operational Amplifiers and Op-Amp Circuits

Chapter 10 Integrated Circuit Biasing and Active Loads


Chapter 11 Differential and Multistage Amplifiers

Chapter 12 Feedback and Stability

Chapter 13 Operational Amplifier Circuits

Chapter 14 Nonideal Effects in Operational Amplifier Circuits

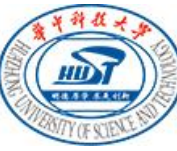Chapter 15 Applications and Design of Integrated Circuits



Ch4 Basic FET Amplifiers

4.1 The MOSFET Amplifier

4.2 Basic Transistor Amplifier Configurations

4.3 The Common Source Amplifier

4.4 The Common Drain (Source Follower) Amplifier




4.5 The Common Gate Configuration


4.5.1 Small voltage and current gains

4.5.2 Input and output Impedance

4.6 The Three Basic Amplifier Configuration: Summary and comparison

Review

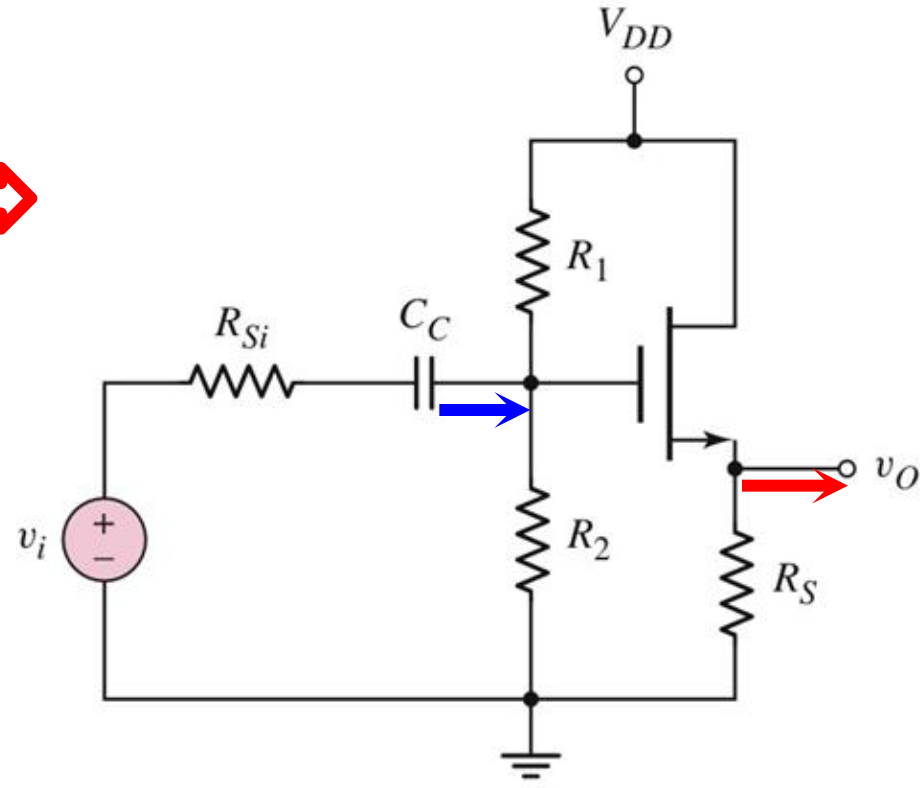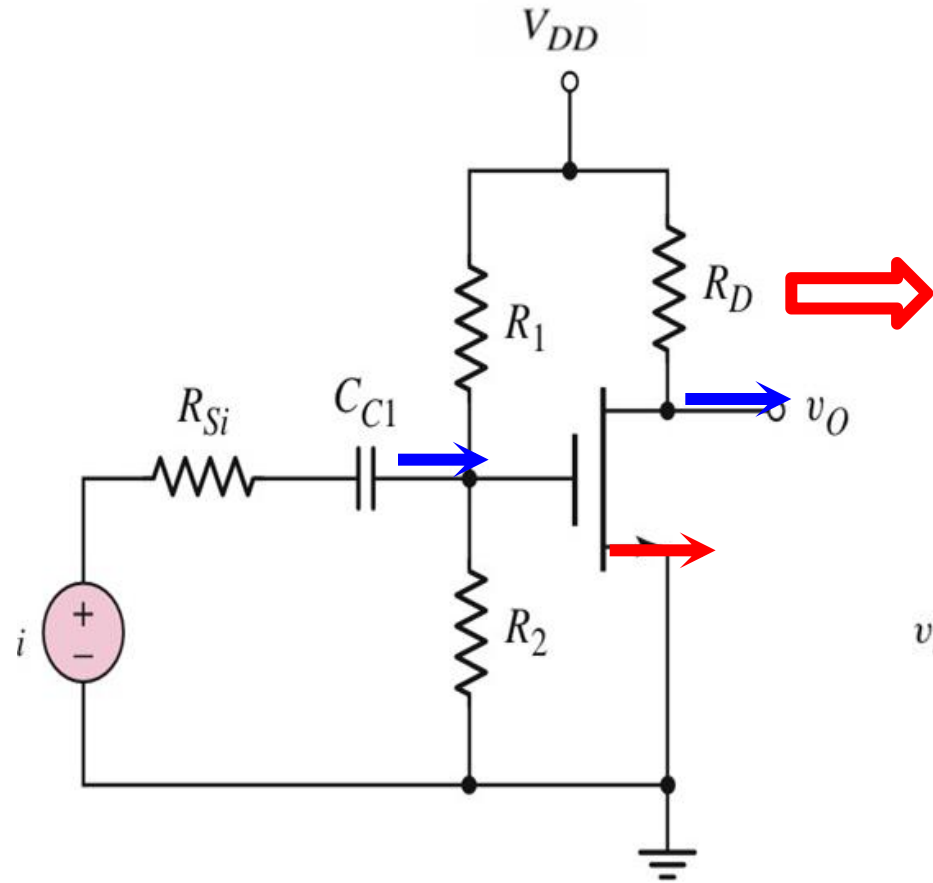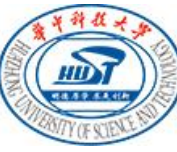

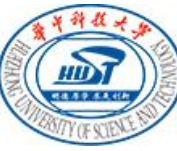

Ch4 Basic FET Amplifiers

4.1 The MOSFET Amplifier

4.2 Basic Transistor Amplifier Configurations


4.3 The Common Source Amplifier

4.4 The Common Drain (Source Follower) Amplifier

4.4.1 Small-signal voltage gain

4.4.2 Input and Output Impedance

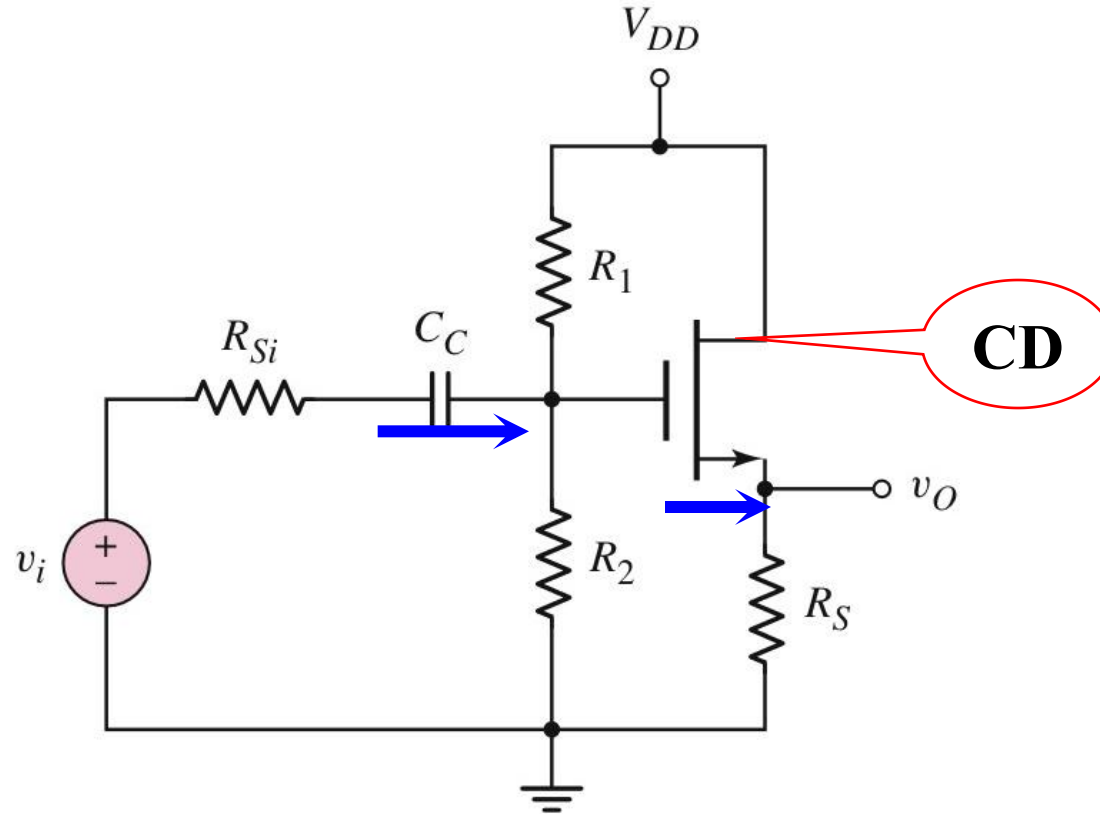4.4 The Common Drain (Source Follower) Amplifier





Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.


Source Follower

4.4.1 Small-signal voltage gain


Small-Signal Equivalent Circuit

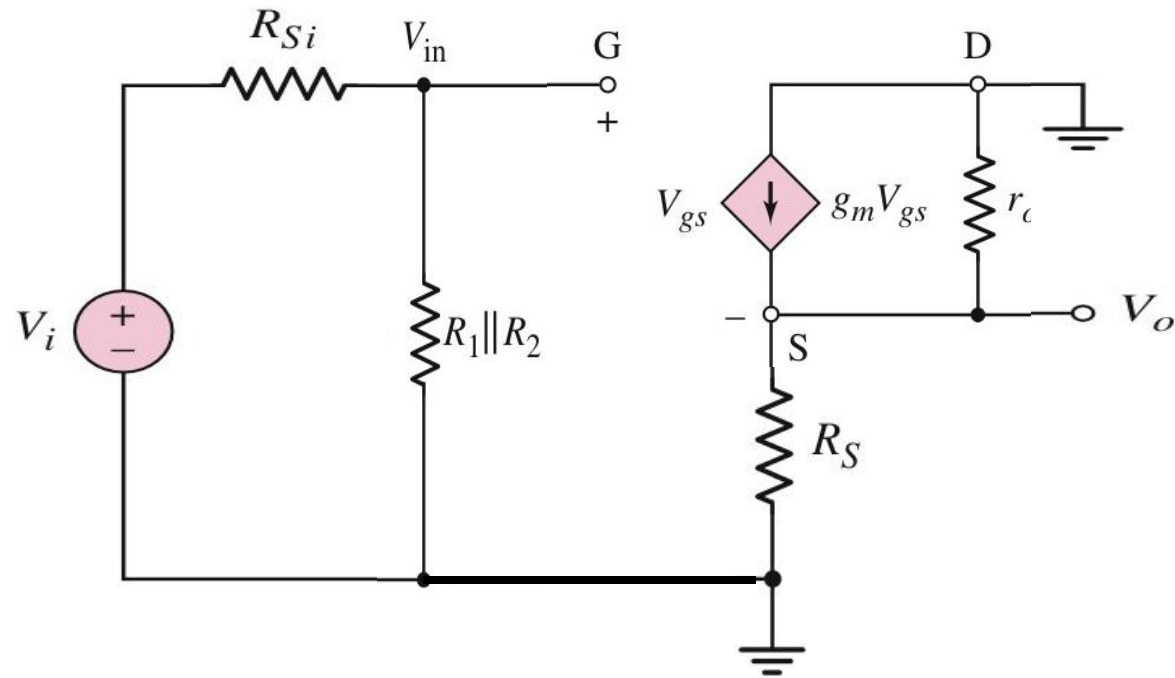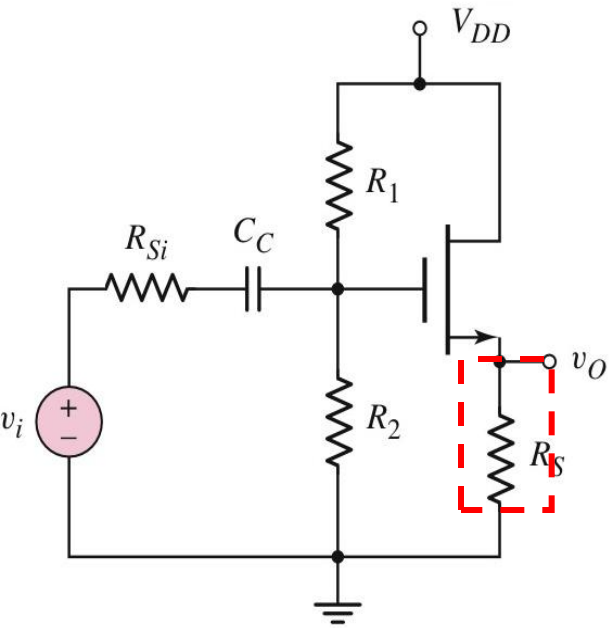

4.4.1 Small-signal voltage gain

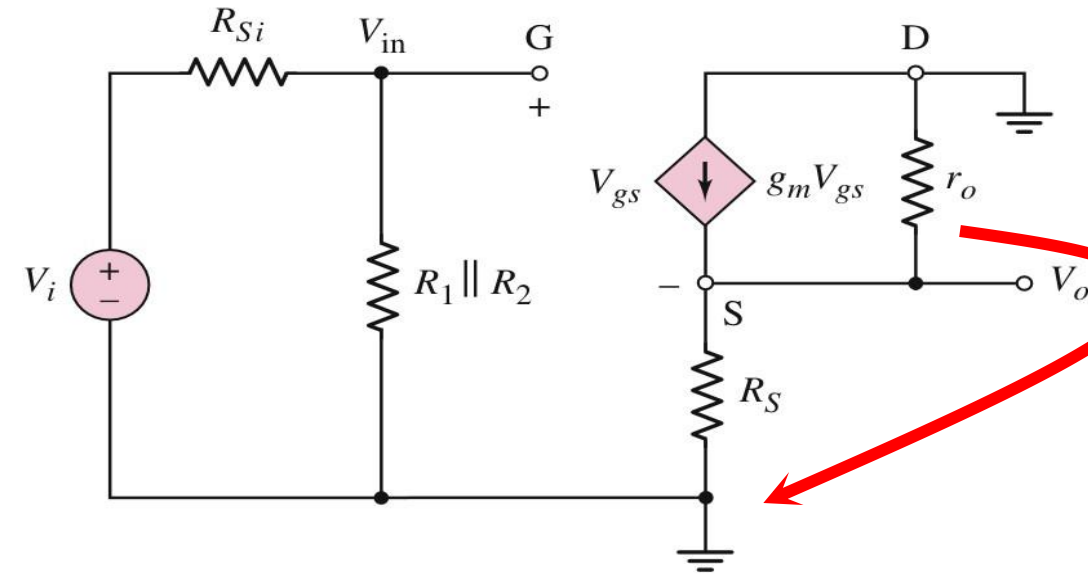

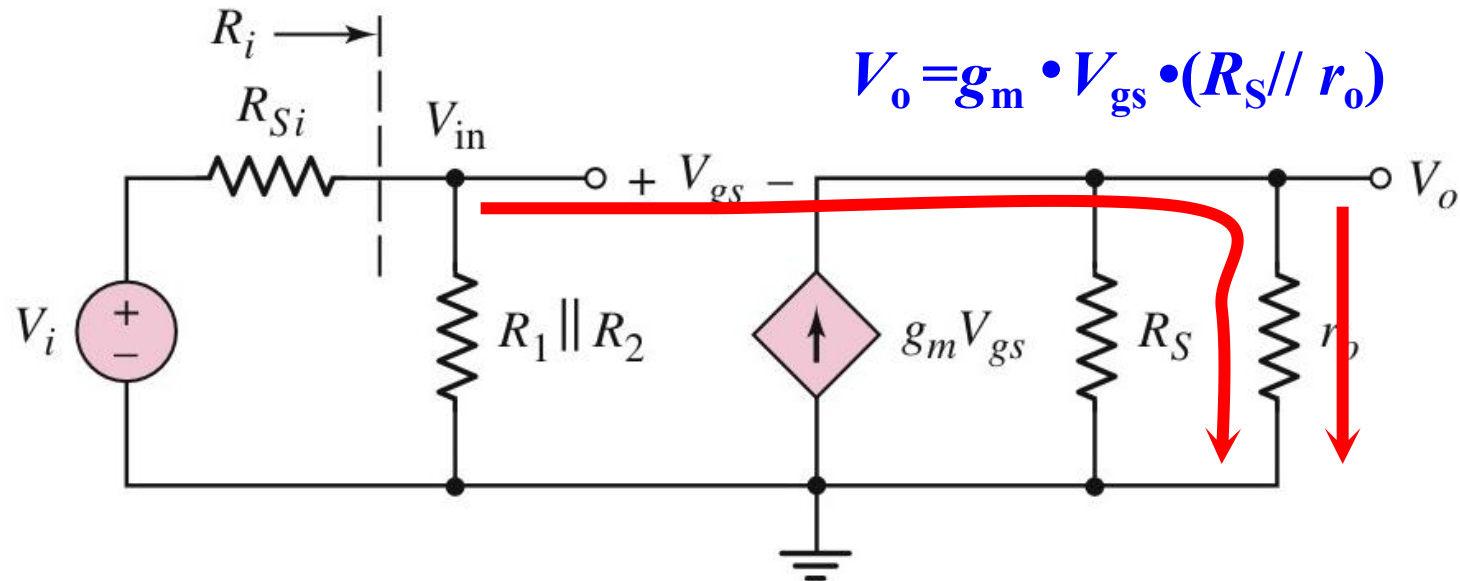
$$A_v = \frac{R_S \parallel r_o}{\frac{1}{g_m} + R_S \parallel r_o} \left(\frac{R_i}{R_i + R_{Si}} \right)$$



$$V_o = g_m \cdot V_{gs} \cdot (R_S \parallel r_o)$$


$$V_{in} = V_{gs} + V_o = V_{gs} + g_m \cdot V_{gs} \cdot (R_S \parallel r_o)$$

4.4.2 Input and Output Impedance

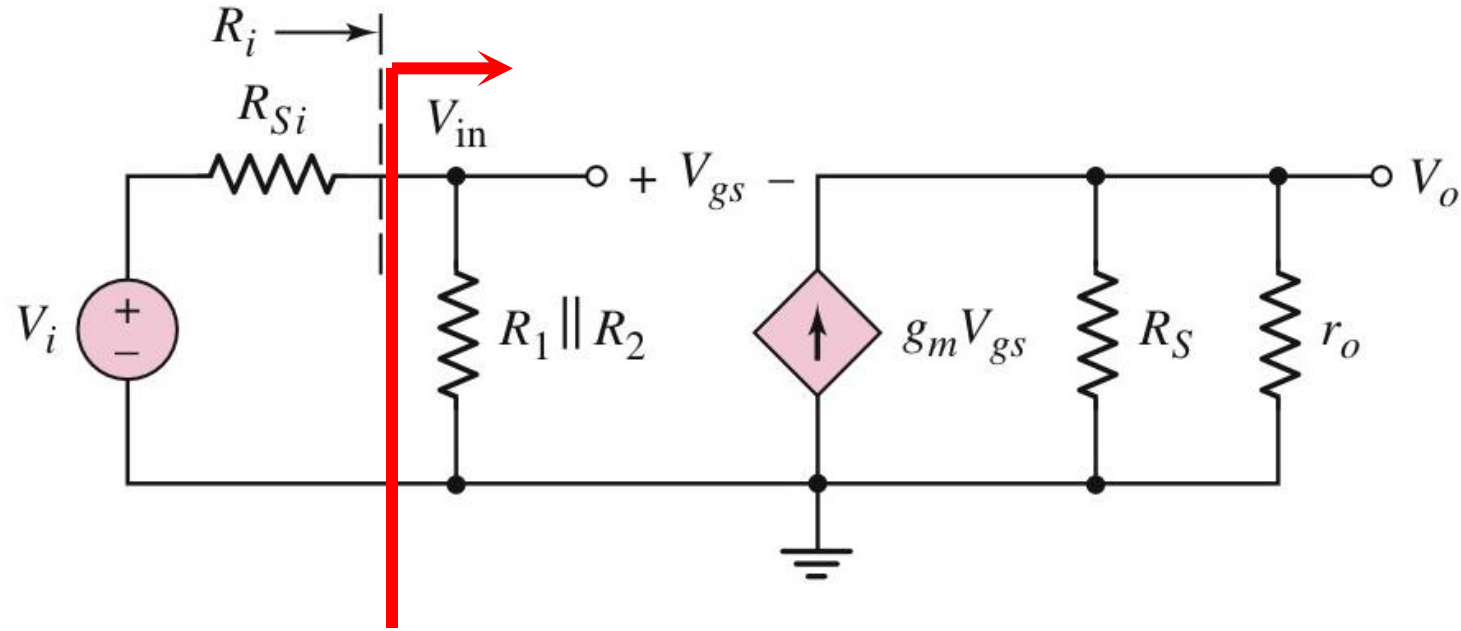


$$R_i = R_1 // R_2$$

4.4.2 Input and Output Impedance

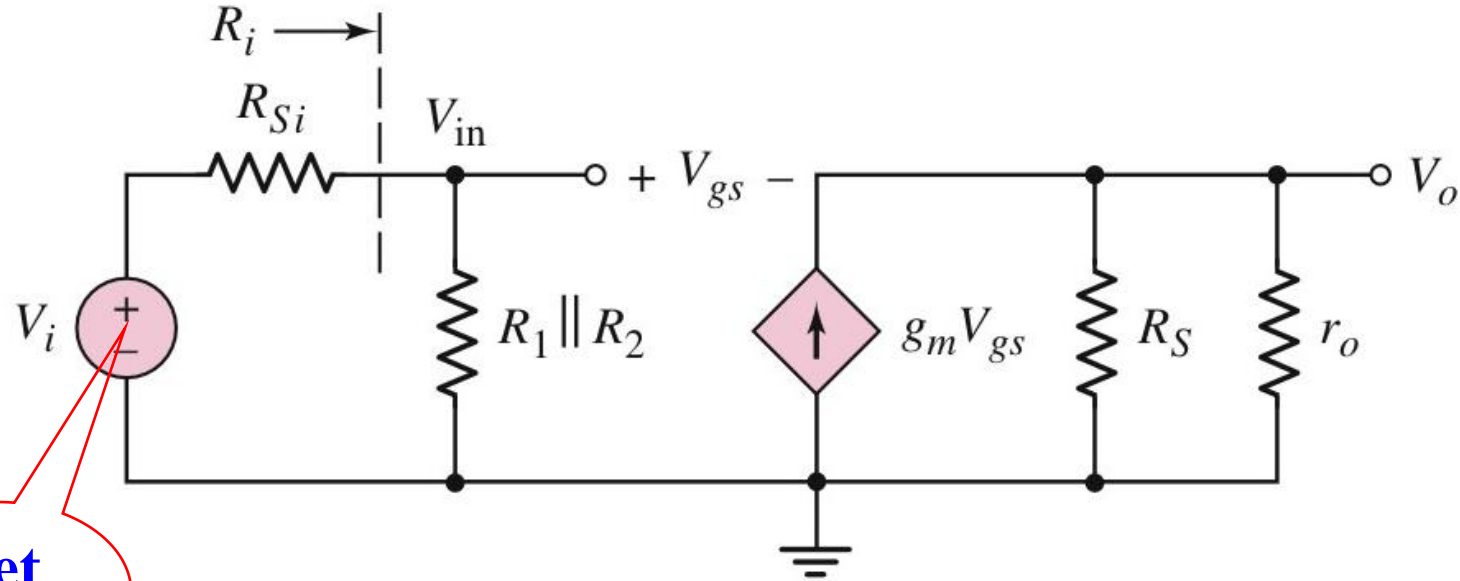


Set
zero

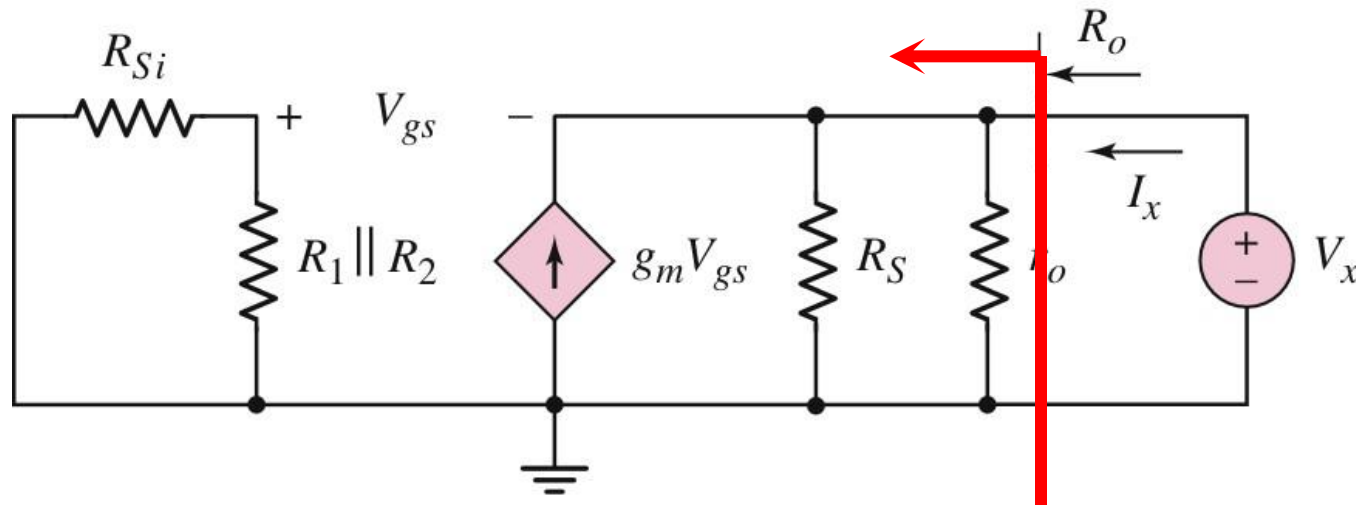

$$R_o = \frac{V_x}{I_x}$$

4.4.2 Input and Output Impedance

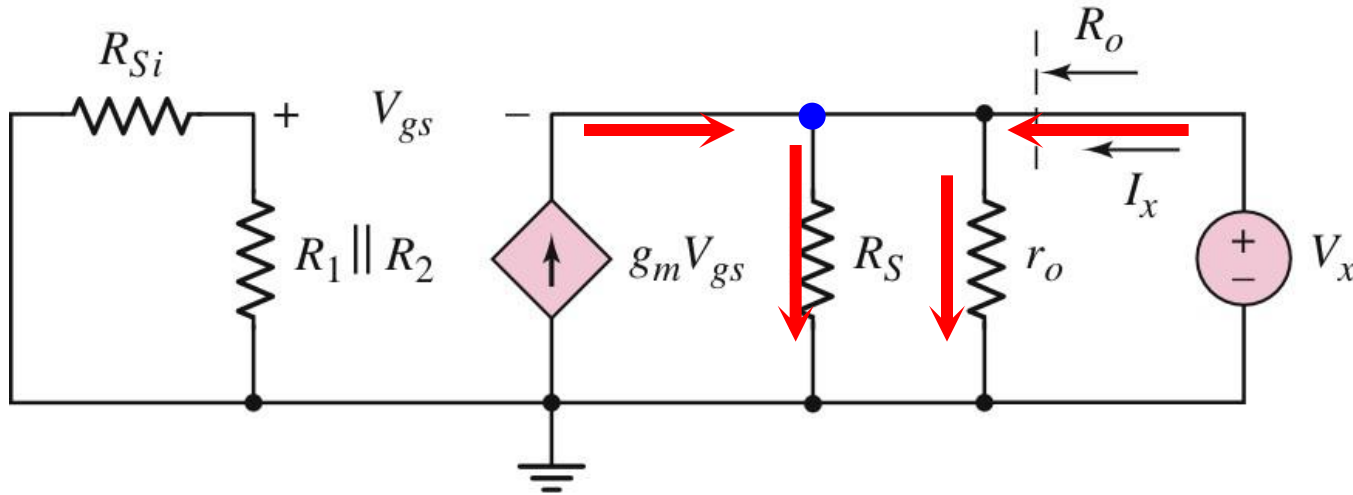

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$I_x + g_m V_{gs} = \frac{V_x}{R_S} + \frac{V_x}{r_o}$$

$$R_O = \frac{V_x}{I_x} = \frac{1}{g_m} \parallel R_S \parallel r_o$$

Output Resistance is very low.

Without significant loading effects.

Example

Calculate the small-signal voltage gain


$$\begin{aligned} V_{DD} &= 12 \text{ V} \\ R_1 &= 162 \text{ k}\Omega, \\ R_2 &= 463 \text{ k}\Omega, \\ R_S &= 0.75 \text{ k}\Omega, \end{aligned}$$

Solution: dc analysis


$$I_{DQ} = 7.97 \text{ mA} \quad V_{GSQ} = 2.91 \text{ V}$$

$$g_m = 2K_n(V_{GSQ} - V_{TN}) = 2(4)(2.91 - 1.5) = 11.3 \text{ mA/V}$$
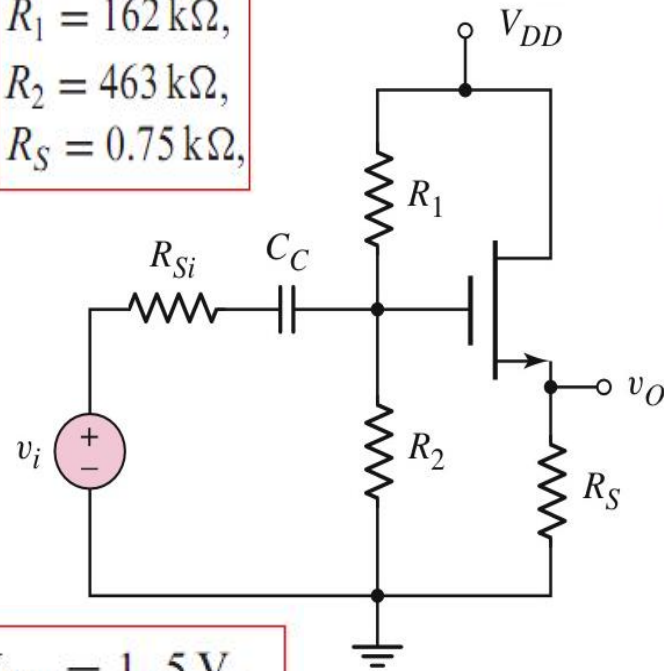
$$r_o \cong [\lambda I_{DQ}]^{-1} = [(0.01)(7.97)]^{-1} = 12.5 \text{ k}\Omega$$



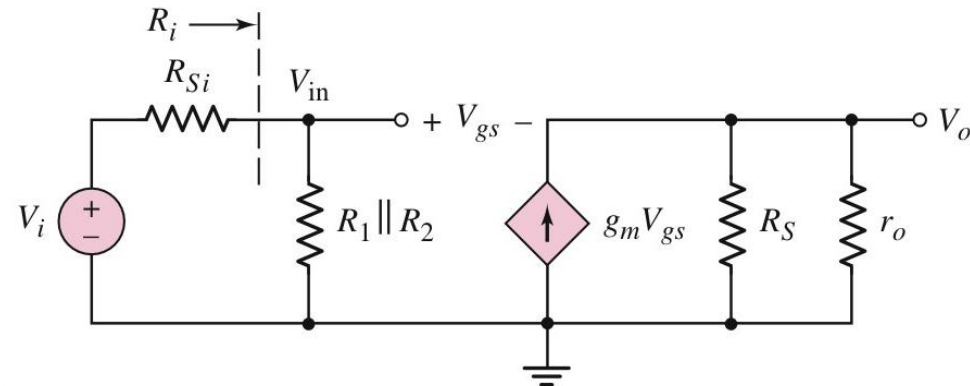
$$\begin{aligned} V_{TN} &= 1.5 \text{ V}, \\ K_n &= 4 \text{ mA/V}^2, \\ \lambda &= 0.01 \text{ V}^{-1} \\ R_{Si} &= 4 \text{ k}\Omega. \end{aligned}$$



$$R_i = R_1 \parallel R_2 = 162 \parallel 463 = 120 \text{ k}\Omega$$

$$A_v = \frac{g_m(R_S \parallel r_o)}{1 + g_m(R_S \parallel r_o)} \cdot \frac{R_i}{R_i + R_{Si}} = \frac{(11.3)(0.75 \parallel 12.5)}{1 + (11.3)(0.75 \parallel 12.5)} \cdot \frac{120}{120 + 4} = +0.860$$

Contents

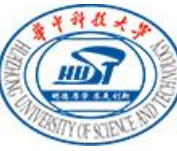

PART 1 SEMICONDUCTOR DEVICES AND BASIC APPLICATIONS

Chapter 1 Semiconductor Materials and Diodes

Chapter 2 Diode Circuits

Chapter 3 The Field-Effect Transistor

 **Chapter 4 Basic FET Amplifiers**

Chapter 5 The Bipolar Junction Transistor

Chapter 6 Basic BJT Amplifiers

Chapter 7 Frequency Response

Chapter 8 Output Stages and Power Amplifiers

PART 2 ANALOG ELECTRONICS

Chapter 9 Ideal Operational Amplifiers and Op-Amp Circuits

Chapter 10 Integrated Circuit Biasing and Active Loads


Chapter 11 Differential and Multistage Amplifiers

Chapter 12 Feedback and Stability

Chapter 13 Operational Amplifier Circuits

Chapter 14 Nonideal Effects in Operational Amplifier Circuits

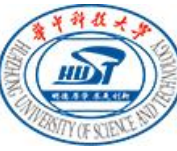Chapter 15 Applications and Design of Integrated Circuits



Ch4 Basic FET Amplifiers

4.1 The MOSFET Amplifier

4.2 Basic Transistor Amplifier Configurations

4.3 The Common Source Amplifier

4.4 The Common Drain (Source Follower) Amplifier


4.5 The Common Gate Configuration

4.5.1 Small voltage and current gains


4.5.2 Input and output Impedance

4.6 The Three Basic Amplifier Configuration: Summary and comparison


4.5 The Common Gate Configuration

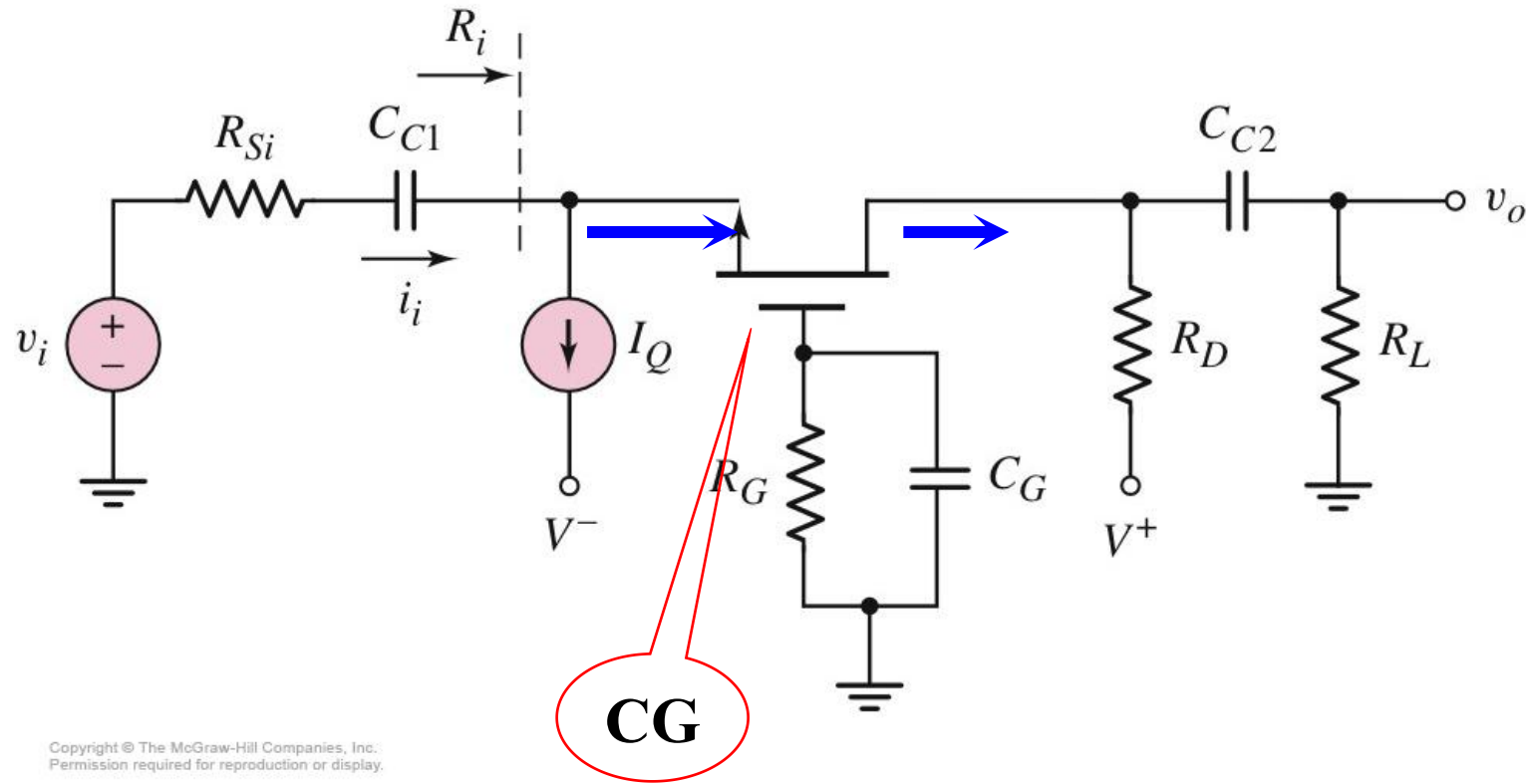


4.5.1 Small voltage and current gains

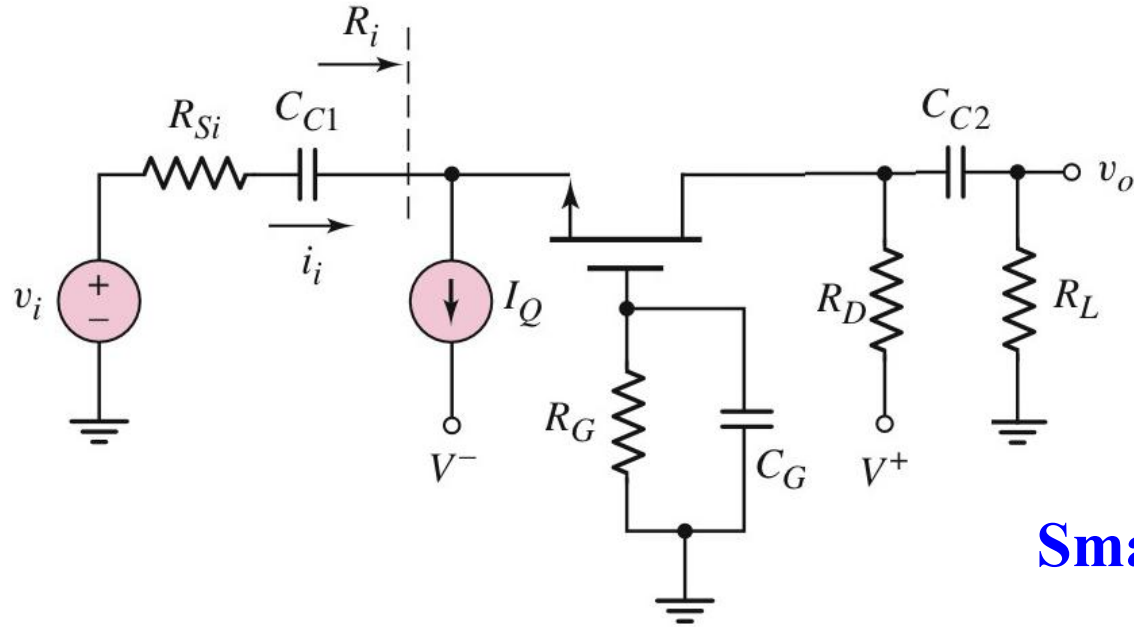

Small-Signal Equivalent Circuit

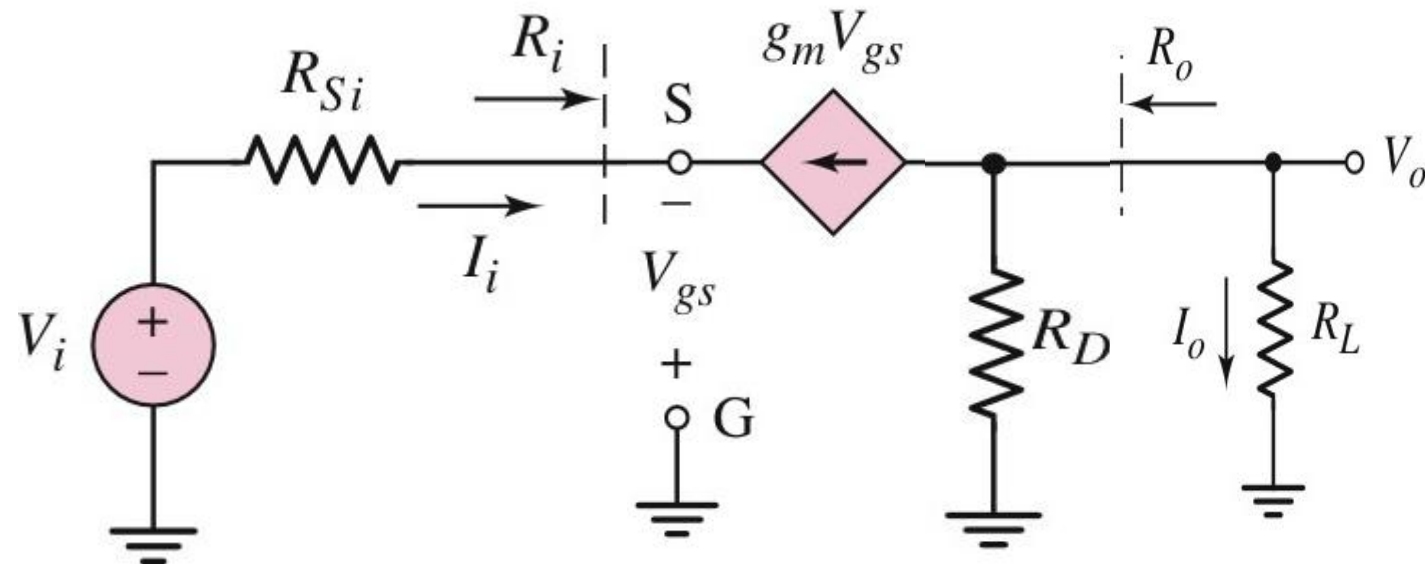

4.5.1 Small voltage and current gains

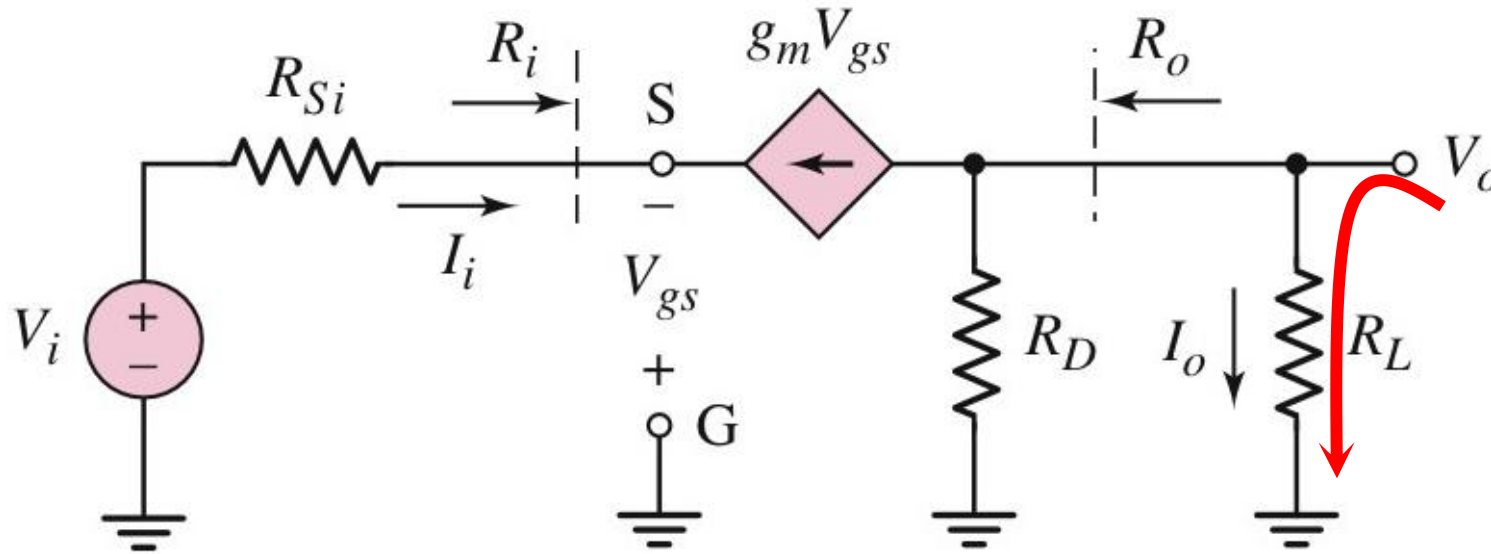


$$V_o = -g_m \cdot V_{gs} \cdot (R_D \parallel R_L)$$

$$V_i = I_i \cdot R_{Si} - V_{gs}$$

$$I_i = -g_m \cdot V_{gs}$$

$$A_v = \frac{g_m (R_D \parallel R_L)}{1 + g_m R_{Si}}$$


4.5.1 Small voltage and current gains

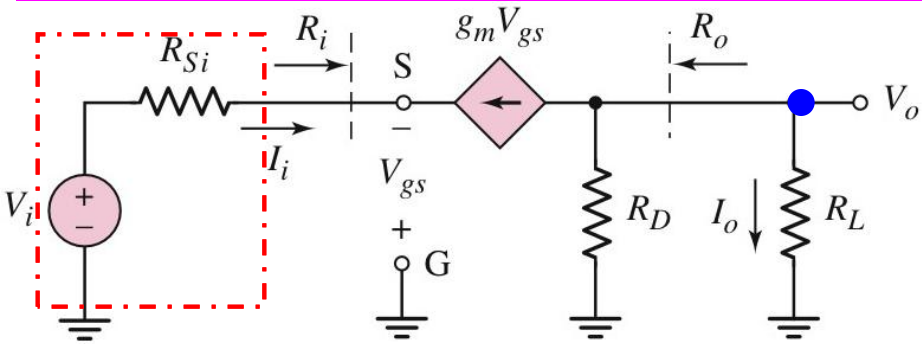

Norton equivalent circuit


$$I_o = \frac{R_D}{R_D + R_L} (-g_m V_{gs})$$
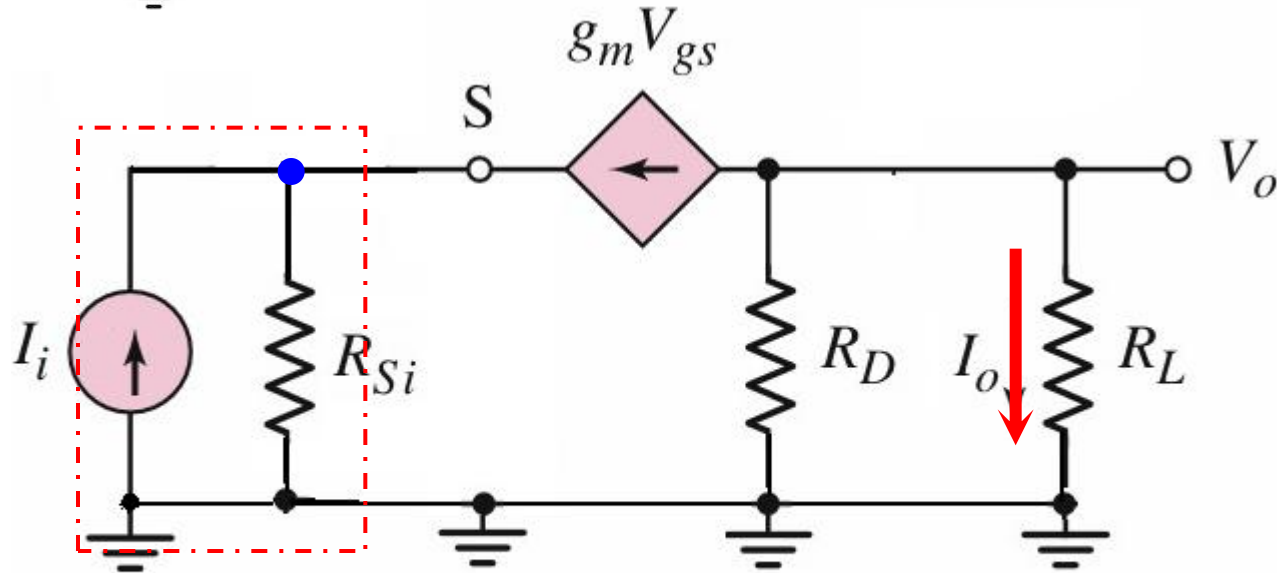
$$I_i + g_m V_{gs} + \frac{V_{gs}}{R_{Si}} = 0$$



$$A_i = \frac{I_o}{I_i} = \left(\frac{R_D}{R_D + R_L} \right) \left(\frac{g_m R_{Si}}{1 + g_m R_{Si}} \right)$$

4.5.1 Small voltage and current gains

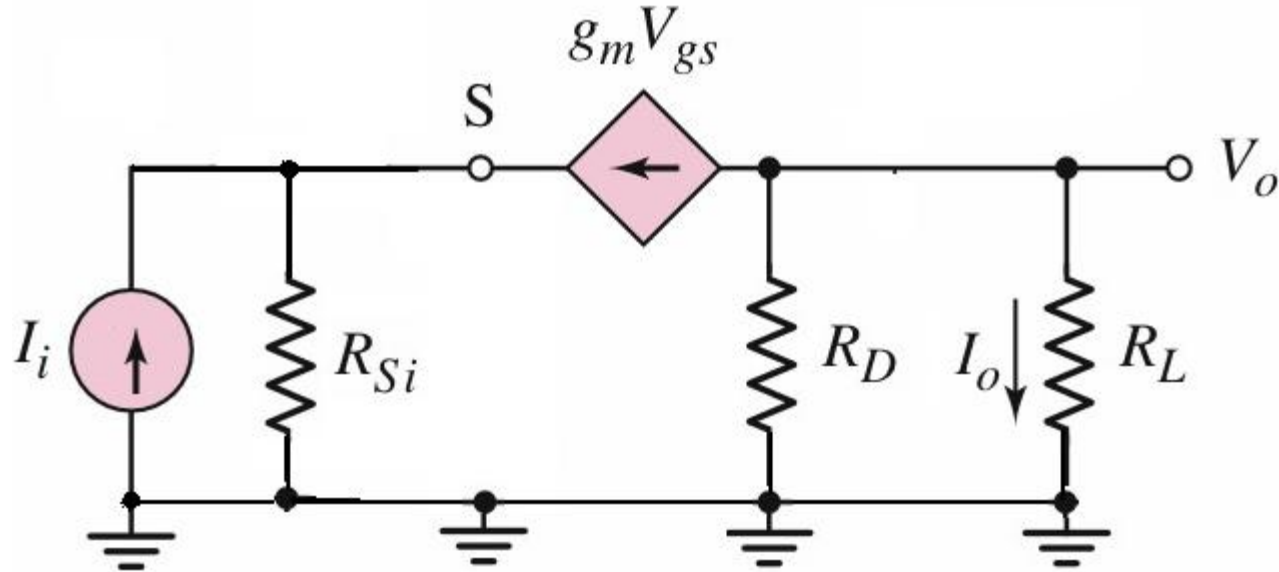

$$A_i = \frac{I_o}{I_i} = \left(\frac{R_D}{R_D + R_L} \right) \left(\frac{g_m R_{Si}}{1 + g_m R_{Si}} \right)$$


$$R_D \gg R_L$$

$$g_m R_{Si} \gg 1$$

$$A_i = 1$$

Current follower


4.5.2 Input and output Impedance

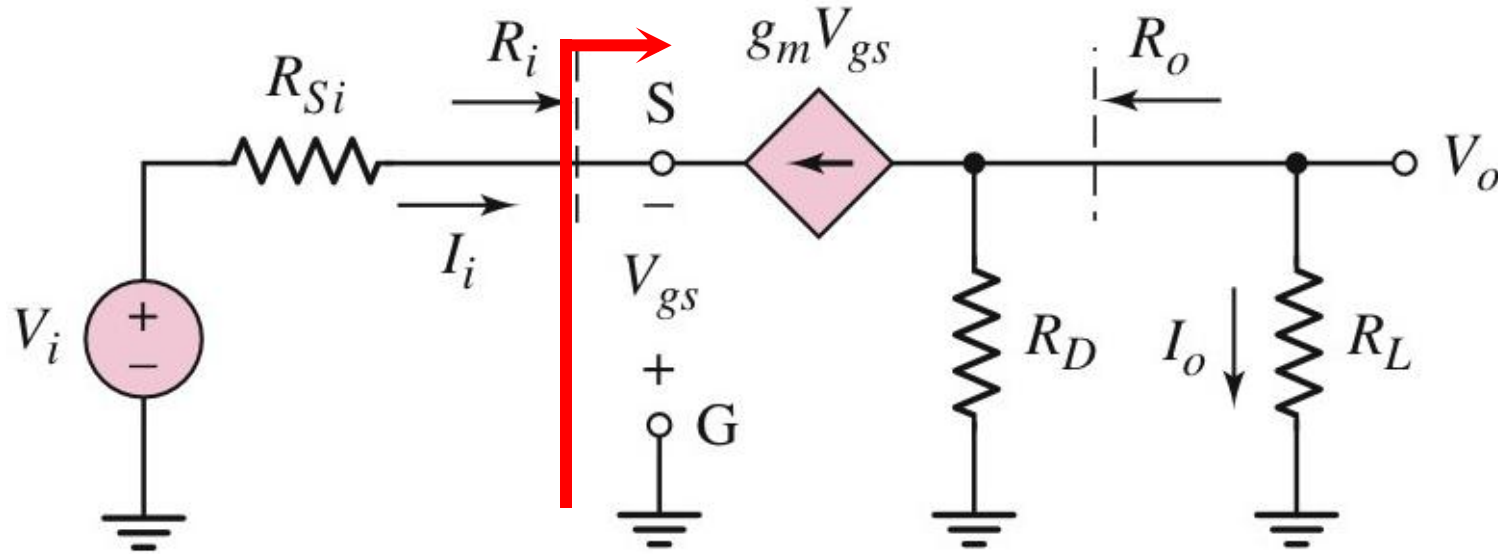

$$R_i = \frac{-V_{gs}}{I_i} = \frac{-V_{gs}}{-g_m V_{gs}} = \frac{1}{g_m}$$



Input Impedance is very low

4.5.2 Input and output Impedance

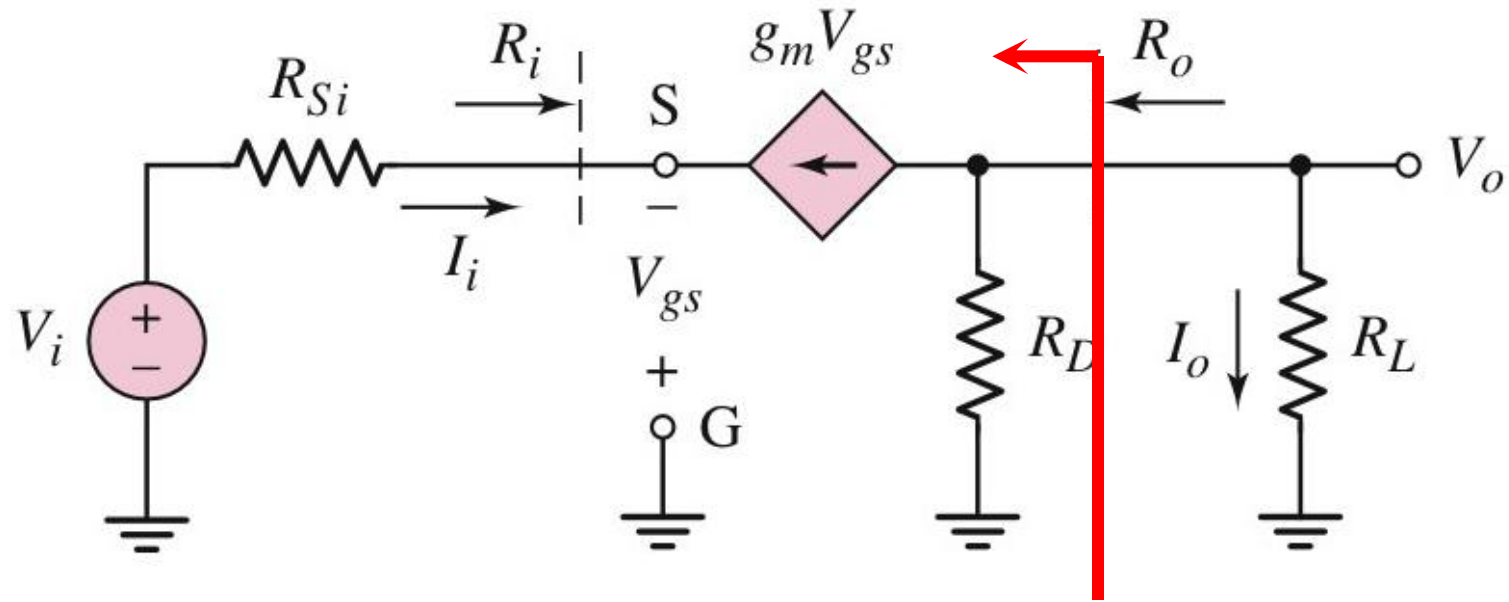


$$R_o = R_D$$

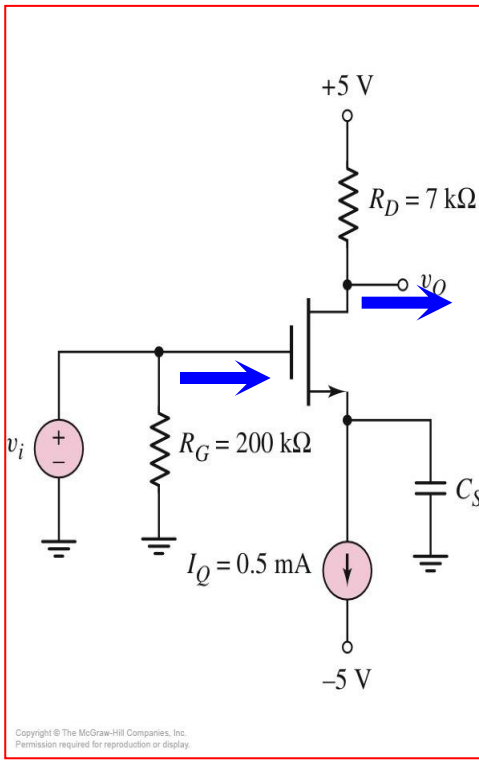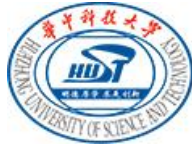
4.6 The Three Basic Amplifier Configuration:Summary and comparison



CS

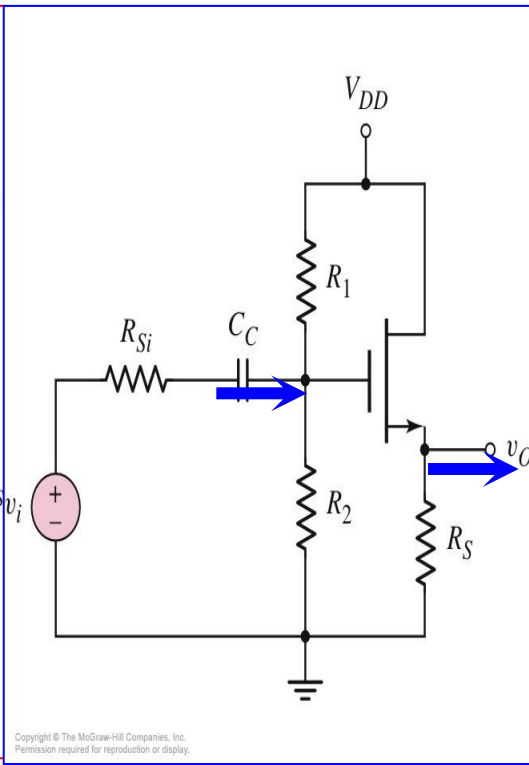


CD

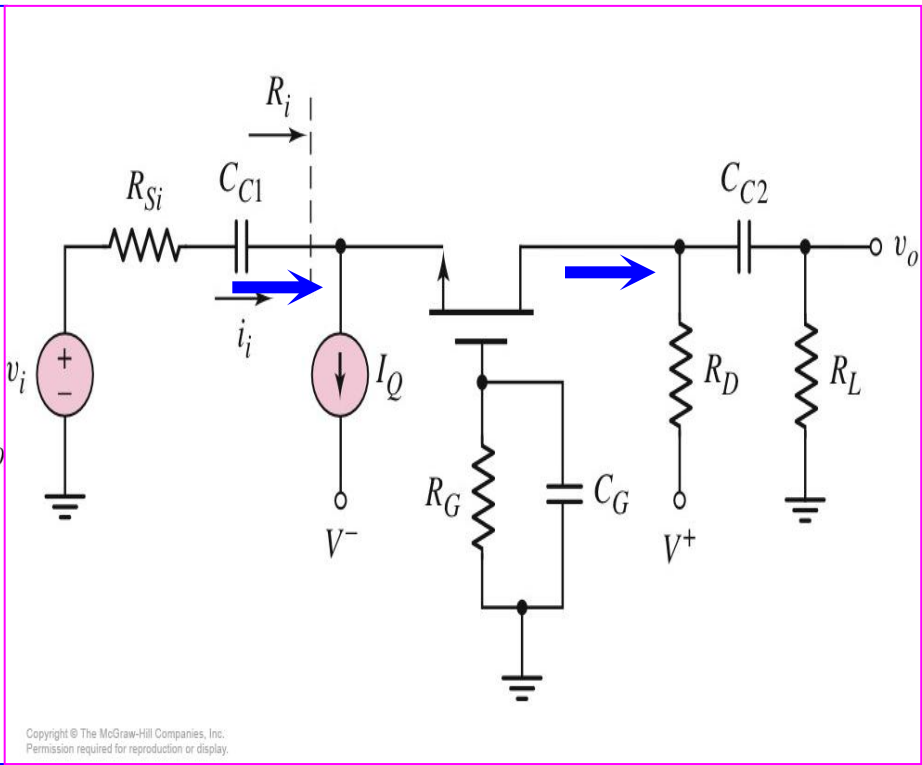

CG

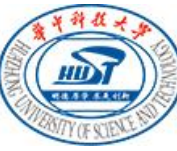Comparing three basic circuit of field effect transistor




	Common-source	Common-drain	Common-gate
Circuit			
Voltage-gain	$A_V = -g_m (R_d // r_o)$	$A_V = \frac{g_m (R_d // r_o)}{1 + g_m (R_d // r_o)}$	$A_V = \frac{(g_m + 1/r_o) R_D}{1 + (R_D / r_o)} \approx g_m R_D$
Input resistor	$R_i = R_{g1} // R_{g2}$	$R_i = R_{g1} // R_{g2}$	$R_i = \frac{1}{g_m} // R$
Output resistor	$R_o = R_d // r_o$	$R_o = \frac{1}{g_m} // R // r_o$	$R_o = R_d // r_o$
Features	<ul style="list-style-type: none"> 1. Voltage gain is large 2. Input and output voltage have opposing phase 3. Input resistance is large 	<ul style="list-style-type: none"> 1. Voltage gain is less than 1 and similar to 1 2. Input and output voltages have same phase 3. Input resistance is large 4. Output resistance is small 	<ul style="list-style-type: none"> 1. Voltage gain is large 2. Input and output voltages have same phase 3. Input resistance is small

Comparing three basic circuit of field effect transistor

Configuration	Voltage Gain	Current Gain	Input Resistance	Output Resistance
Common Source	$A_v > 1$	—	R_{TH}	Moderate to high
Source Follower	$A_v \approx 1$	—	R_{TH}	Low
Common Gate	$A_v > 1$	$A_i \approx 1$	Low	Moderate to high



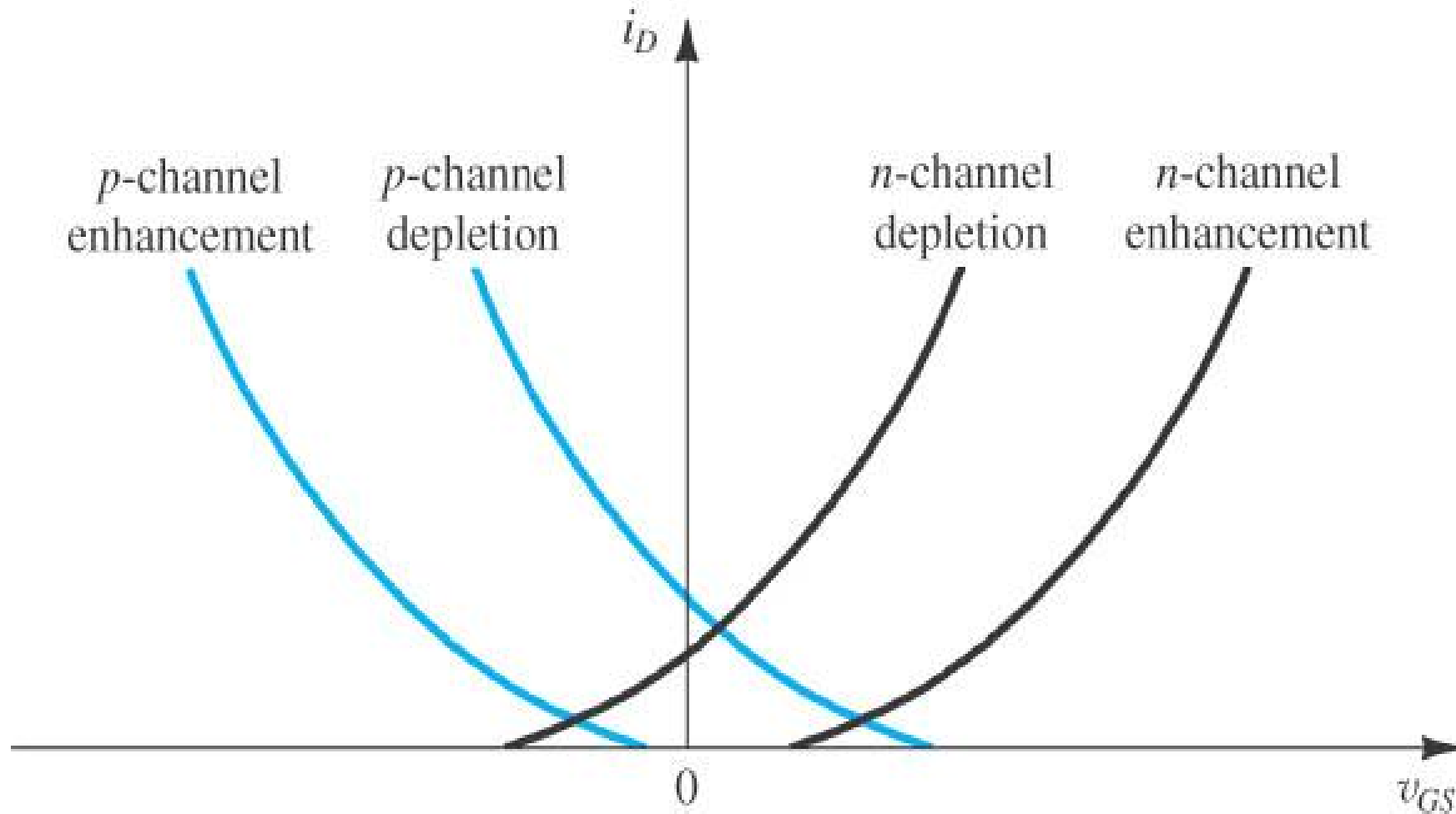
The i_D - v_{GS} Characteristic in Saturation















Overview

For chapter 3 and chapter 4:

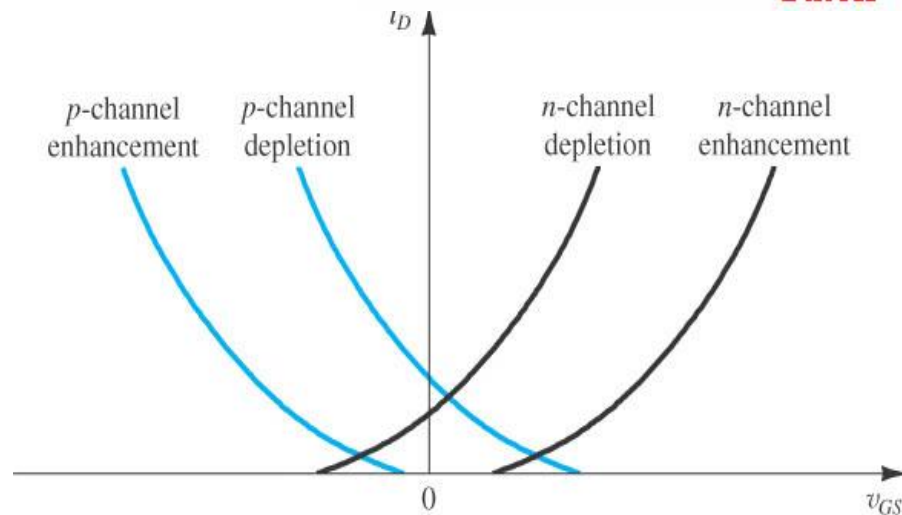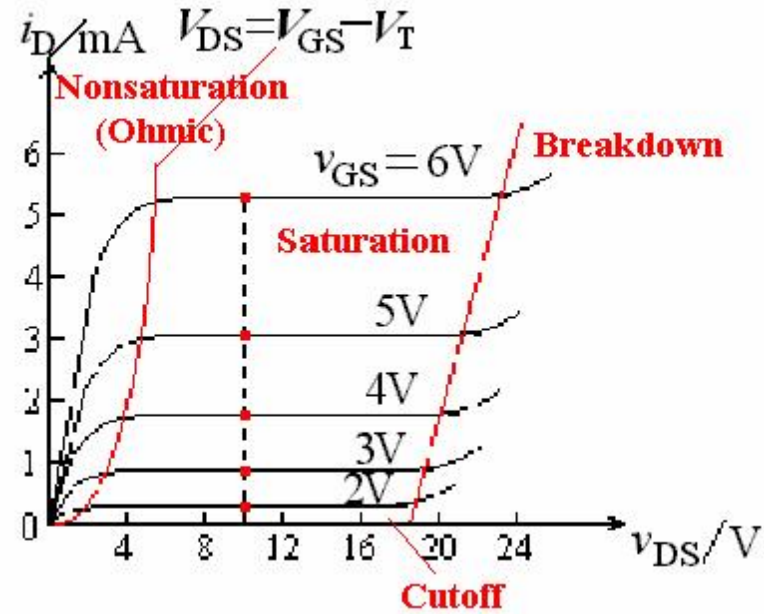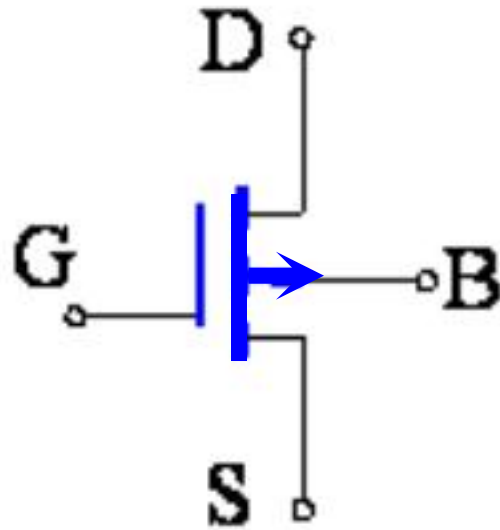1、MOSFET structure, feature, i-v characteristic



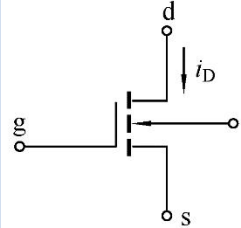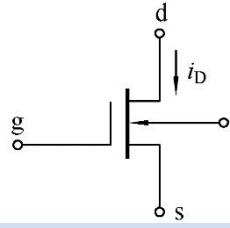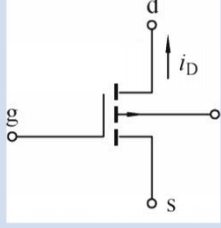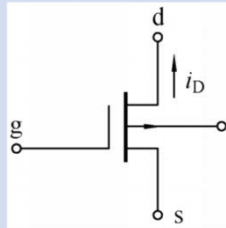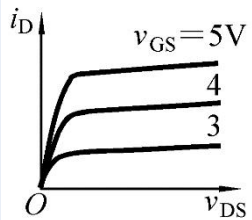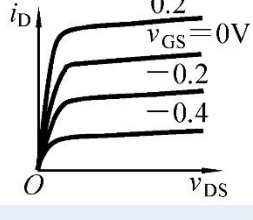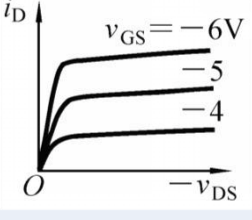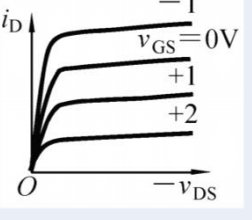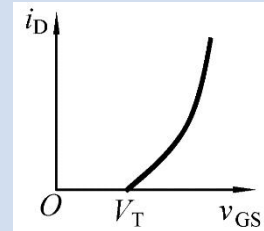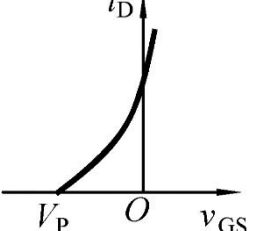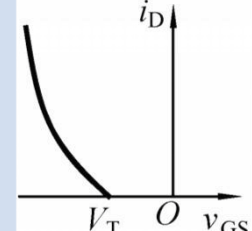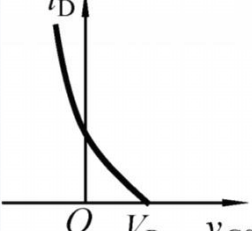	NMOS E-Mode	NMOS D-Mode	PMOS E-Mode	NMOS D-Mode
Circuit Symbol				
Output Characteristic				
Transfer Characteristic				
V_{GS} (Saturation Reg.)	$V_{GS} > V_{TN} > 0$	$V_{GS} > V_P$	$V_{GS} < V_{TP} < 0$	$V_{GS} < V_P$
V_{DS} (Saturation Reg.)	$V_{DS} > V_{GS} - V_{TN} > 0$	$V_{DS} > 0$	$V_{DS} < V_{GS} - V_{TP} < 0$	$V_{DS} < 0$

Overview

2、DC analysis

Calculate V_{GS} 、 I_D 、 V_{DS}

A、 For enhancement NMOS

Saturation region

$$I_D = K_n (V_{GS} - V_T)^2$$

$$V_{DS} = 2V_{DD} - I_D(R_d + R)$$

Non-saturation region







$$I_D = 2K_n (V_{GS} - V_T) V_{DS}$$

$$V_{DS} = 2V_{DD} - I_D(R_d + R)$$

B、 For depletion NMOS

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2 \quad (V_P \leq V_{GS})$$

3、AC analysis

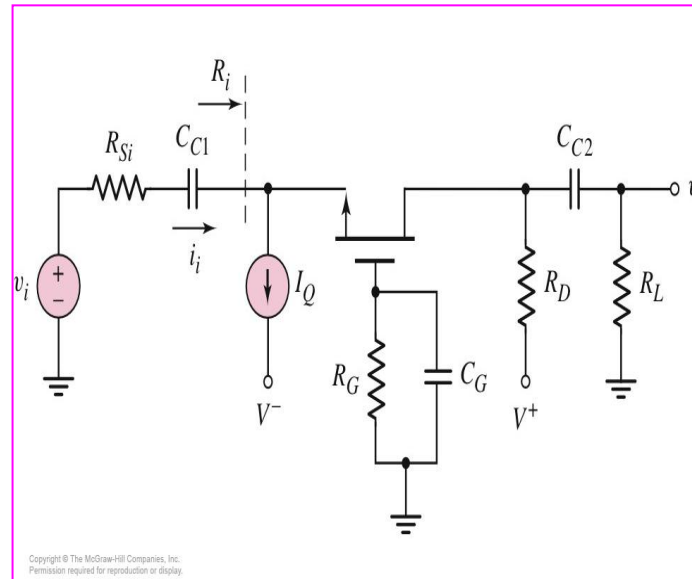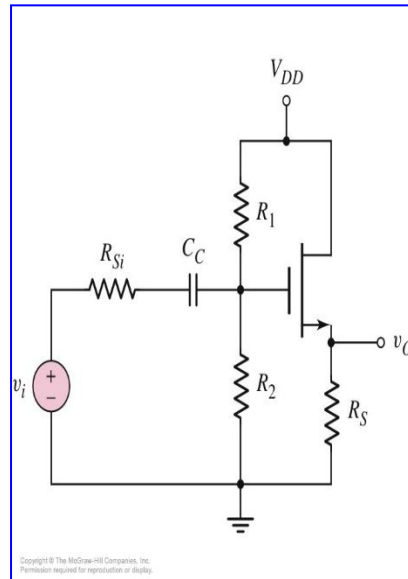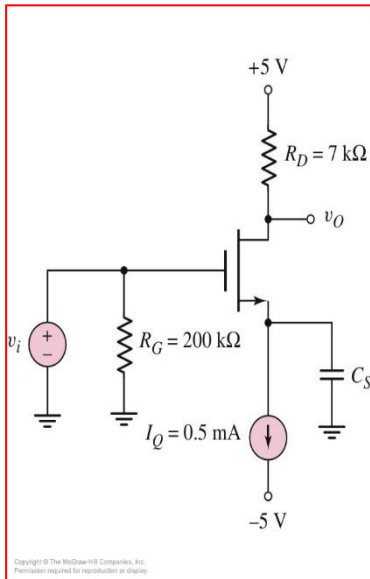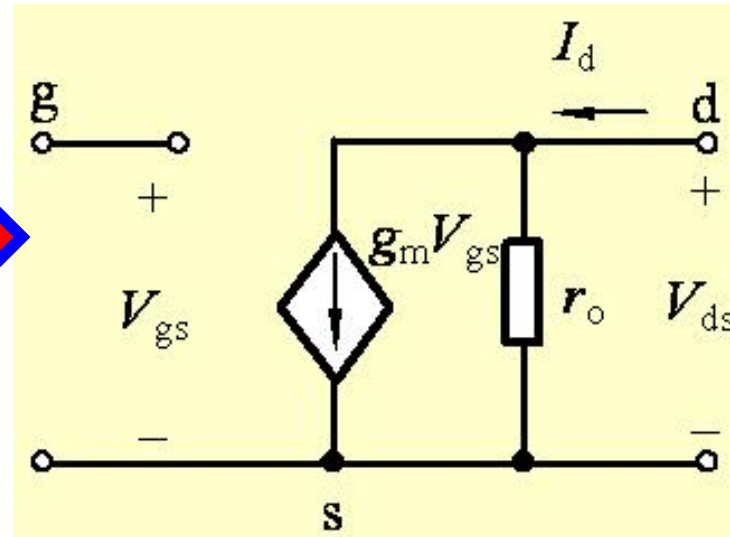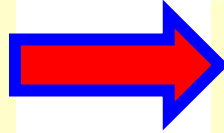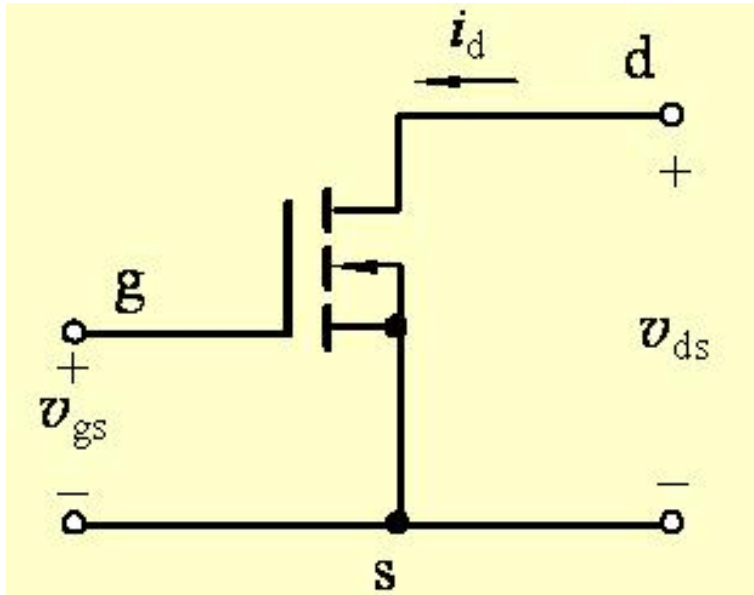



(1) The Reason of Using Multistage Circuit

A single transistor amplifier will not be able to meet the combined specifications of a given amplification factor, input resistance, and output resistance.

(2) Cascade Configuration

3 circuits are connected in series, or cascaded. Each circuit can be CE, CC, or CB configuration

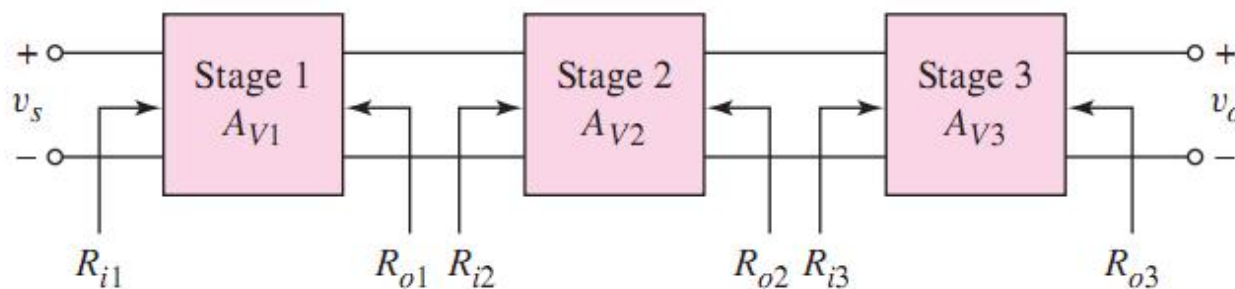


Figure 6.68 A generalized three-stage amplifier



(3) Loading effect

E.g. R_{i2} is the load of stage 1.

$$R_{i2} = R_{L1}$$

$$R_{o1} = R_{S2}$$


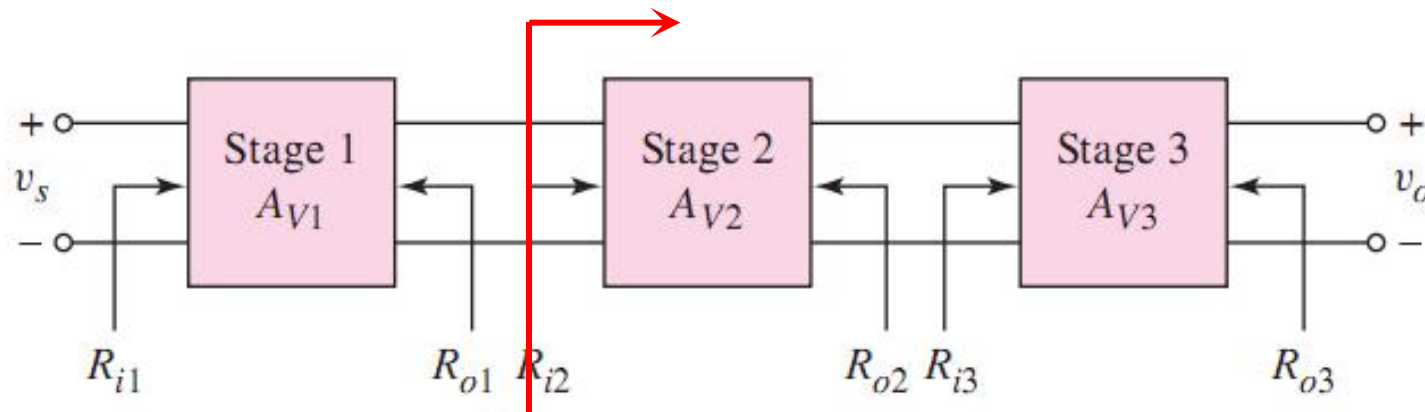


Figure 6.68 A generalized three-stage amplifier

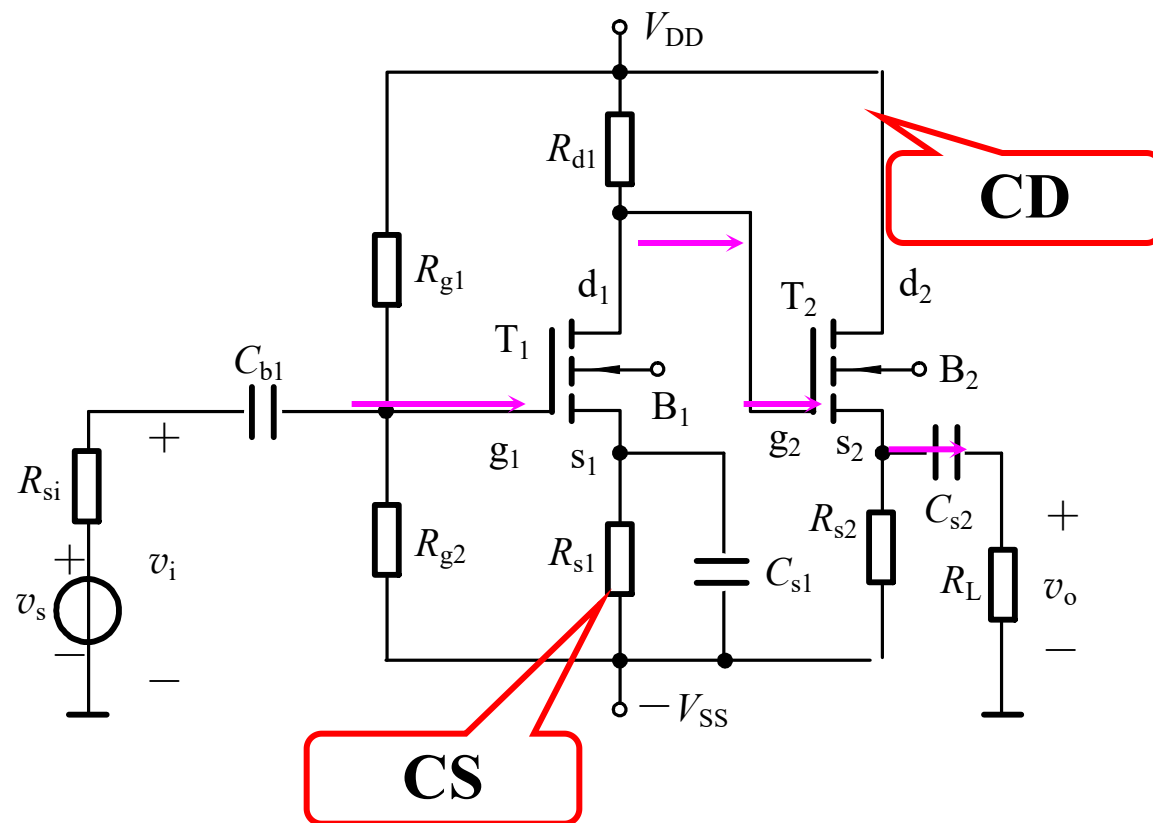

CS-CD




$$K_{n1} = 0.5 \text{ mA/V}^2, K_{n2} = 0.2 \text{ mA/V}^2, V_{TN1} = V_{TN2} = 1.2 \text{ V}, \lambda_1 = \lambda_2 = 0$$

$$R_{d1} = 16 \text{ k}\Omega, R_{s1} = 3.9 \text{ k}\Omega, R_{g1} = 390 \text{ k}\Omega, R_{g2} = 140 \text{ k}\Omega,$$

$$R_{si} = 5 \text{ k}\Omega, R_{s2} = 8.2 \text{ k}\Omega, R_L = 4 \text{ k}\Omega, V_{DD} = V_{SS} = 5 \text{ V}$$

Determine Q-point, A_v

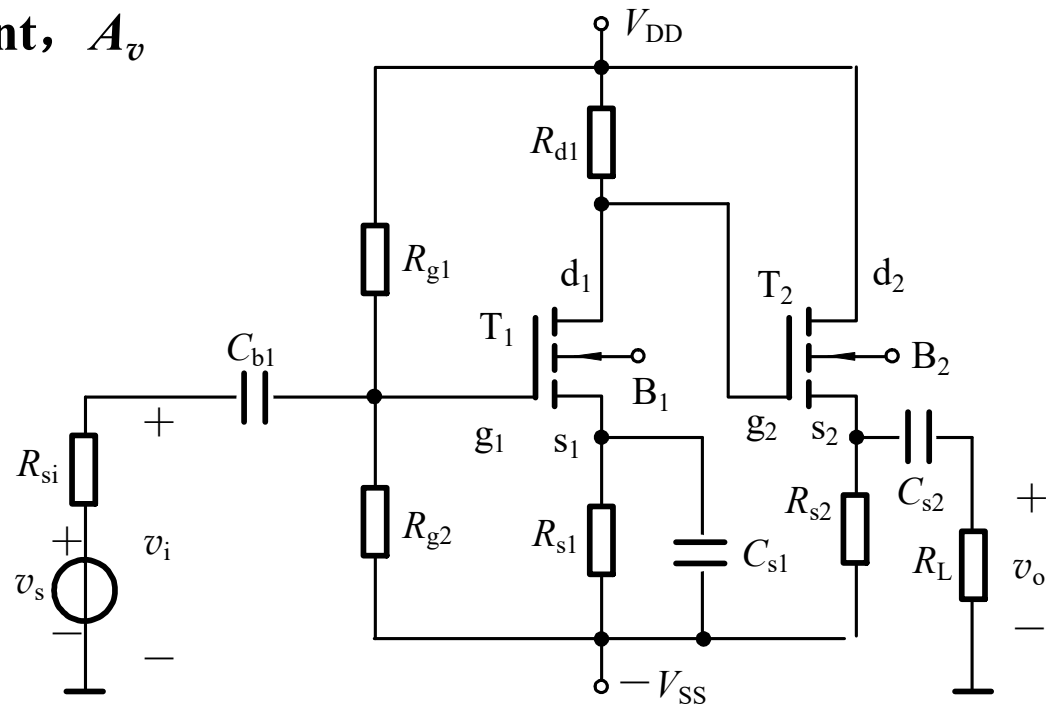

**SOL: 1.Q-point****DC Circuit**

$$V_{GSQ1} = V_{G1} - V_{S1} = \frac{R_{g2}}{R_{g1} + R_{g2}}(V_{DD} + V_{SS}) - I_{DQ1}R_{S1}$$

$$= \frac{140}{390 + 140} \times 10 - 3.9I_{DQ1} = 2.64 - 3.9I_{DQ1}$$

In sat.

$$I_{DQ1} = K_{n1}(V_{GSQ1} - V_{TN1})^2 = 0.5(V_{GSQ1} - 1.2)^2$$


$$V_{GSQ1} = 2.64 - 3.9 \times 0.5(V_{GSQ1} - 1.2)^2$$

$$V_{GSQ1} = \frac{3.68 \pm \sqrt{3.68^2 - 4 \times 1.95 \times 0.168}}{2 \times 1.95} \text{ V}$$

$$= \frac{3.68 \pm 3.497}{3.9} \text{ V} \quad \text{get } V_{GSQ1} = 1.84 \text{ V}$$

$$I_{DQ1} = 0.5(V_{GSQ1} - V_{TN1})^2 = 0.2 \text{ mA}$$
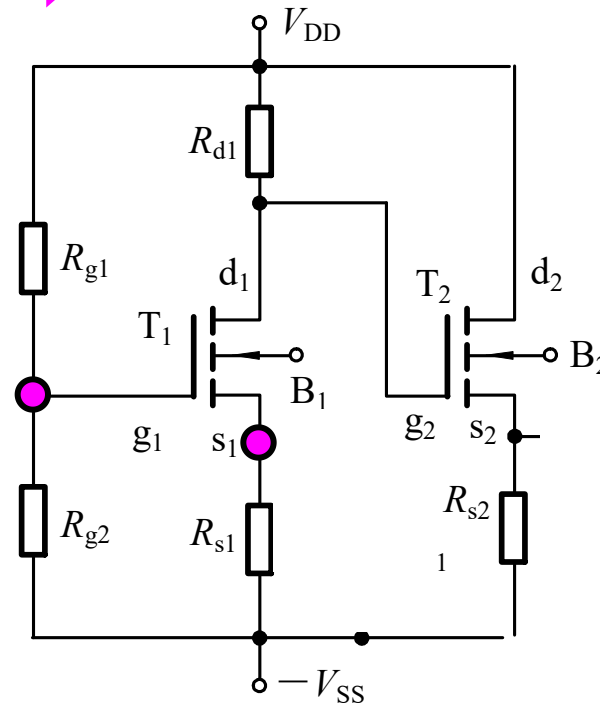
$$V_{DSQ1} = V_{DD} + V_{SS} - I_{DQ1}(R_{d1} + R_{S1}) = 6.02 \text{ V}$$





For T_2

$$V_{G2} = V_{D1} = V_{DD} - I_{DQ1} R_{d1} = (5 - 0.2 \times 16) \text{V} = 1.8 \text{V}$$

$$V_{GSQ2} = V_{G2} - V_{S2} = 1.8 - I_{DQ2} R_{S2} + V_{SS}$$

$$\begin{aligned} I_{DQ2} &= K_{n2} (V_{GSQ2} - V_{TN2})^2 \\ &= 0.2 (1.8 - I_{DQ2} \times 8.2 + 5 - 1.2)^2 \\ &= 0.2 (5.6 - 8.2 I_{DQ2})^2 \end{aligned}$$


$$I_{DQ2}^2 - 1.44 I_{DQ2} + 0.466 = 0$$


$$I_{DQ2} = \frac{1.44 \pm \sqrt{1.44^2 - 4 \times 0.466}}{2} \text{mA} = \frac{1.44 \pm 0.458}{2} \text{mA}$$

$$\text{get } I_{DQ2} = \frac{(1.44 - 0.458)}{2} \approx 0.49 \text{mA}$$

$$V_{GSQ2} = (1.8 + 5 - 0.49 \times 8.2) \text{V} = 2.78 \text{V}$$
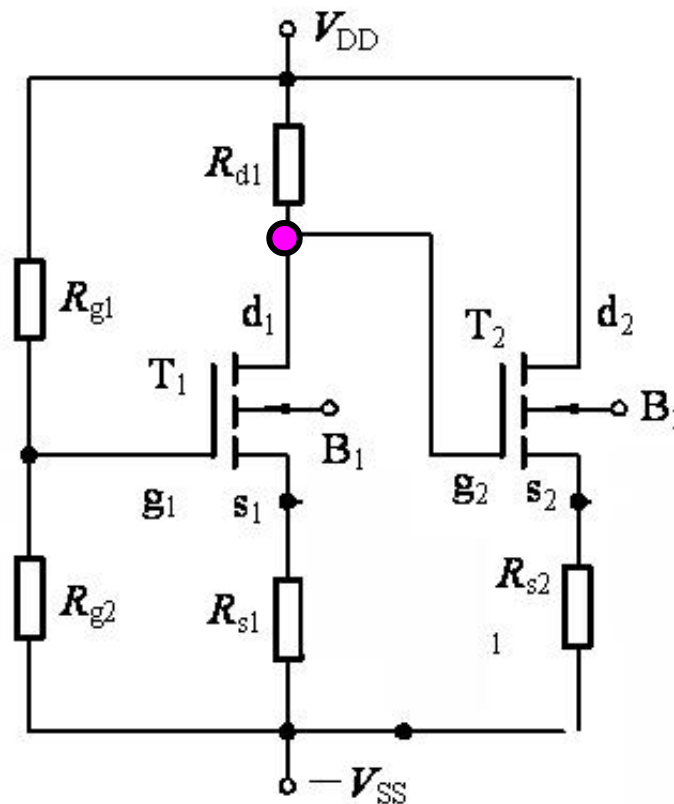
$$V_{DSQ2} = V_{DD} + V_{SS} - I_{DQ2} R_{S2} = (10 - 8.2 \times 0.49) \text{V} = 5.98 \text{V}$$




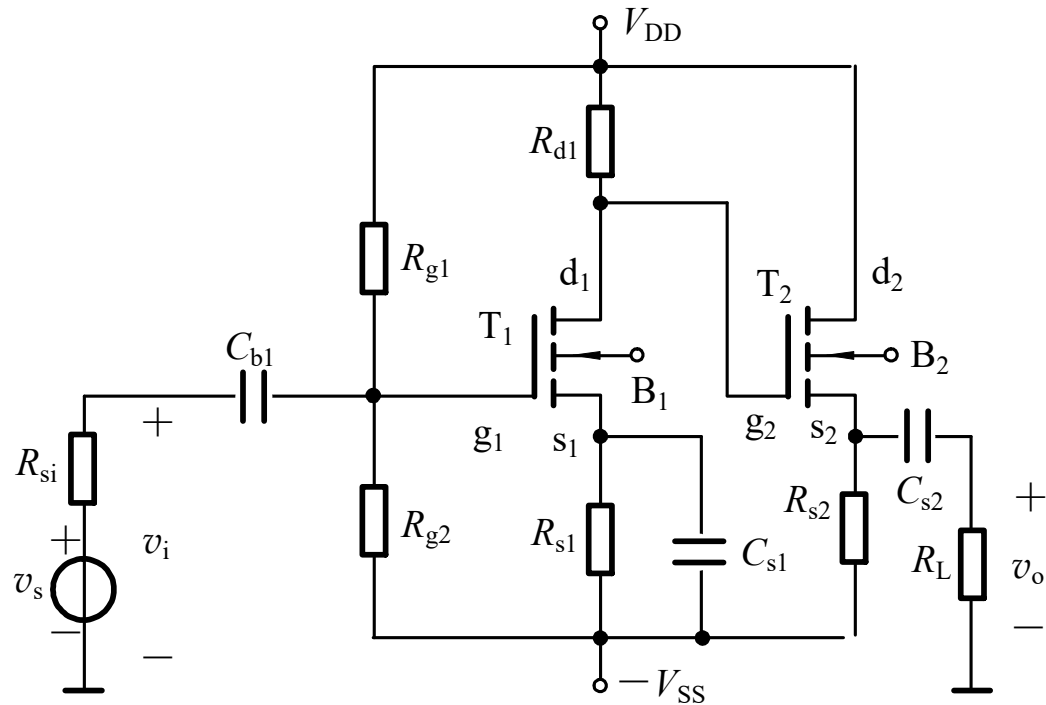2. A_v 

Small signal Eq.

$$g_{m1} = 2K_{n1}(V_{GSQ1} - V_{TN1}) = 2 \times 0.5(1.84 - 1.2)\text{mA} \cdot \text{V}^{-1} = 0.64\text{mA} \cdot \text{V}^{-1}$$
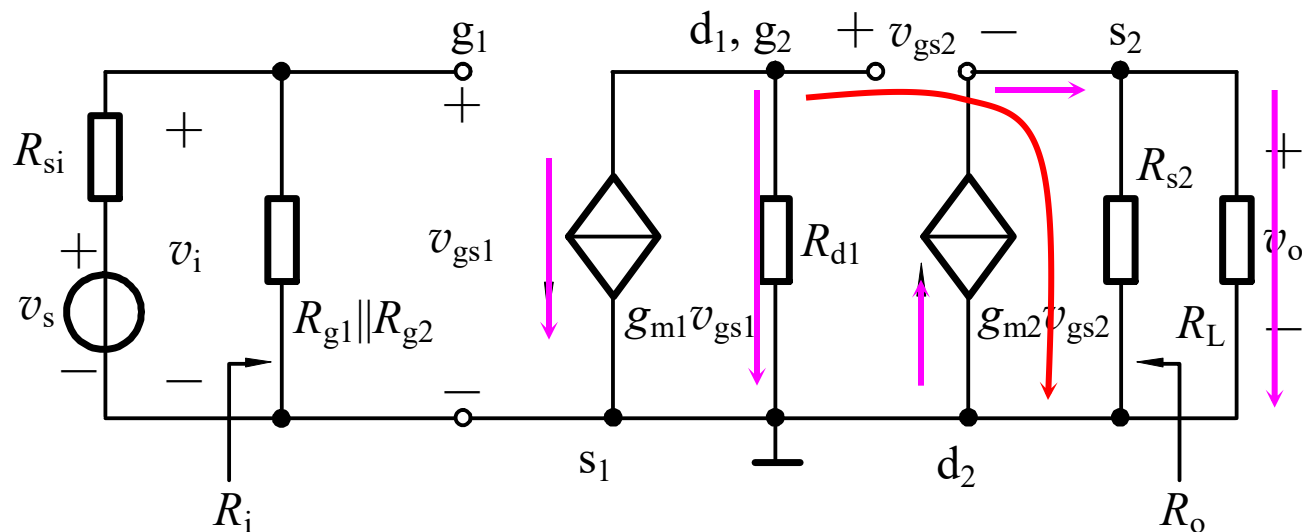
$$g_{m2} = 2K_{n2}(V_{GSQ2} - V_{TN2}) = 2 \times 0.2(2.78 - 1.2)\text{mA} \cdot \text{V}^{-1} = 0.632\text{mA} \cdot \text{V}^{-1}$$




$$v_o = g_{m2} v_{gs2} (R_{S2} // R_L)$$

$$v_{gs2} + v_o = -g_{m1} v_{gs1} R_{d1}$$

$$A_v = \frac{v_o}{v_i} = \frac{v_o}{v_{gs1}} = -\frac{g_{m1} g_{m2} R_{d1} (R_{S2} // R_L)}{1 + g_{m2} (R_{S2} // R_L)}$$

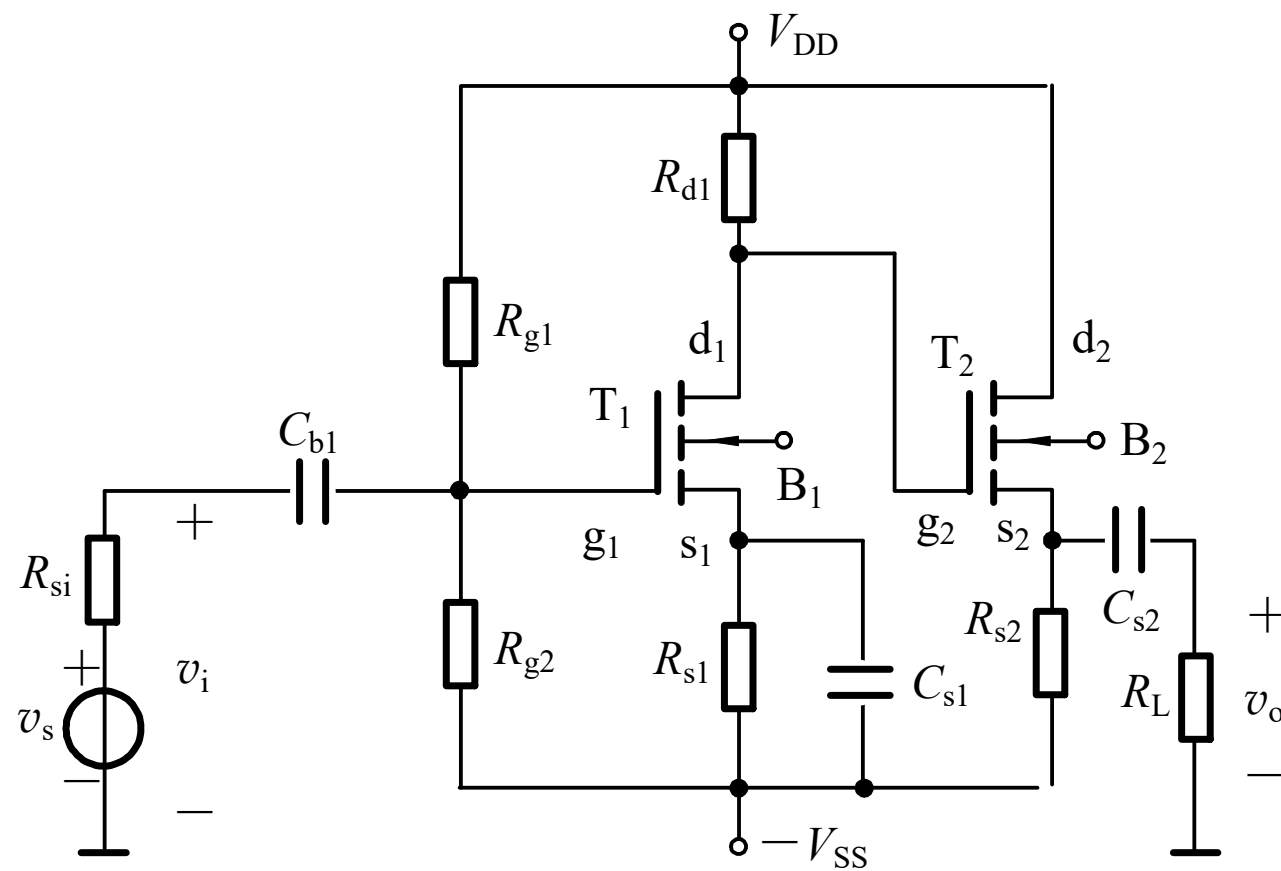If not sketch this small signal circuit, how to get this?



1 、 (12 points)

For the NMOS amplifier in Figure 1, the circuit parameters are:

$$K_n = 1 \text{ mA/V}^2, \lambda = 0; V_T = 2 \text{ V}, g_m = 2K_n(V_{GSQ} - V_T) = 2\sqrt{K_n I_{DQ}},$$

In the saturation region, the drain current is $i_D = K_n (v_{GS} - V_T)^2$,

In the nonsaturation region, the drain current is $i_D \approx 2K_n (v_{GS} - V_T) v_{DS}$,

- (1) Find the Q-point;
- (2) Sketch the Small-Signal Equivalent Circuit;
- (3) Find $A_v = v_o / v_i$;
- (4) Find R_i and R_o

