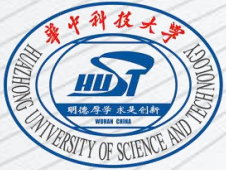


Huazhong University  
of Science & Technology

# Electronic Circuit of Communications

School of Electronic Information  
and Communications

Jiaqing Huang



# Non-linear Analysis

# Devices Classification

(1) Linear

Resistor, Capacitor, Air Core Inductor

No relationship with Voltage/Current

(2) Non-linear

Diode, Transistor, Core Inductor

No relationship with Voltage/Current



(3) Linear Time-varying

Mixer (Trans-Conductance)

Time-varying parameters, no relationship with Voltage/Current
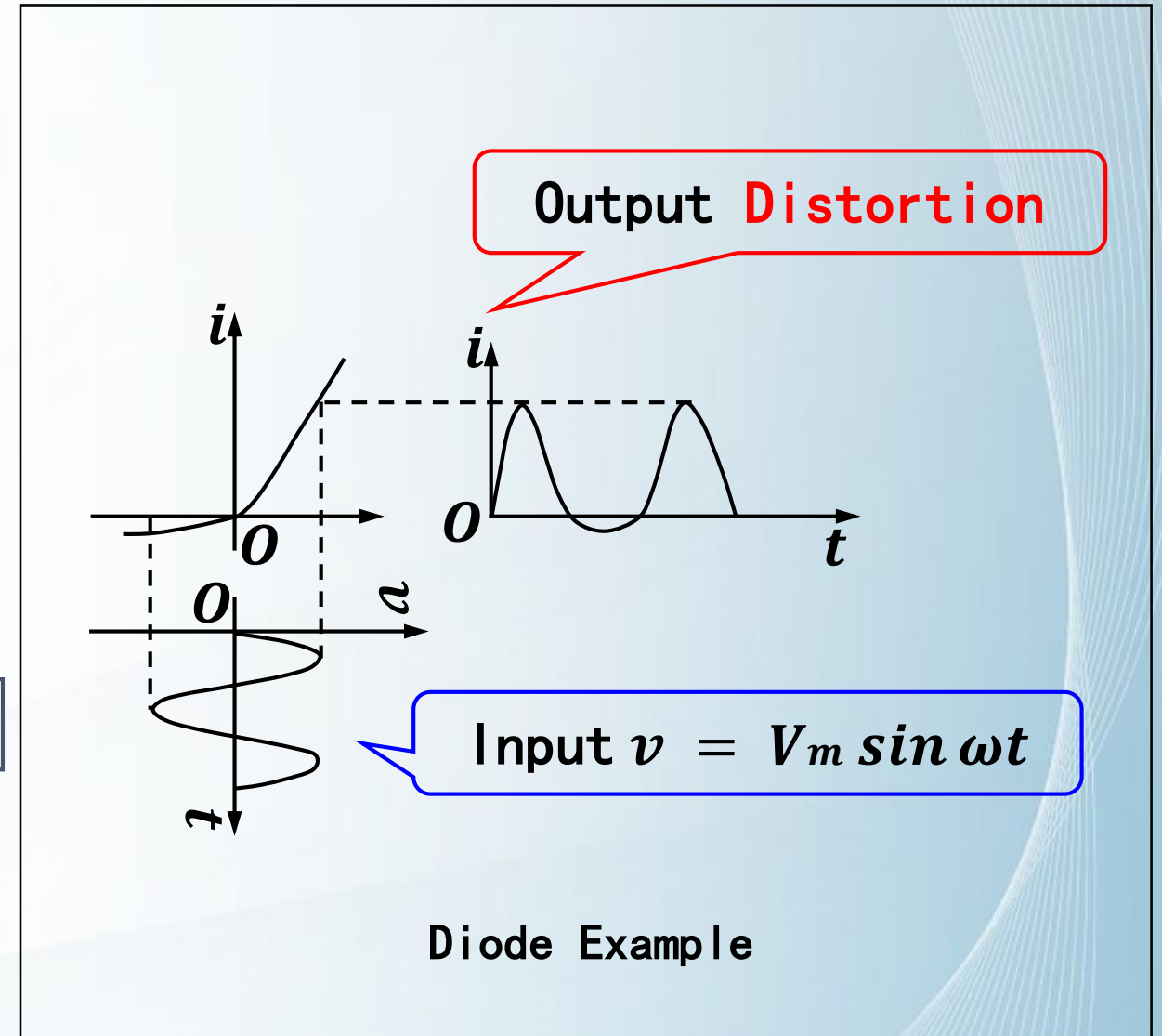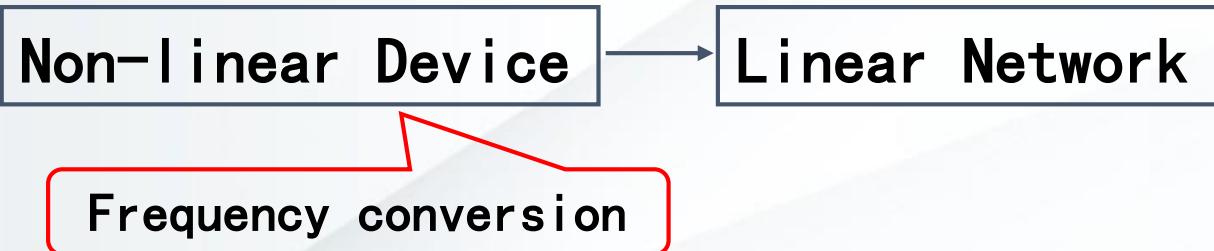
# Non-linear Devices

- Frequency Conversion
- Absolute vs. Relative



## **Non-linear Analysis**

1

**Power  
Series  
Analysis**

2

**Polygonal  
Line  
Analysis**


3

**Linear  
Time-  
varying  
Analysis**
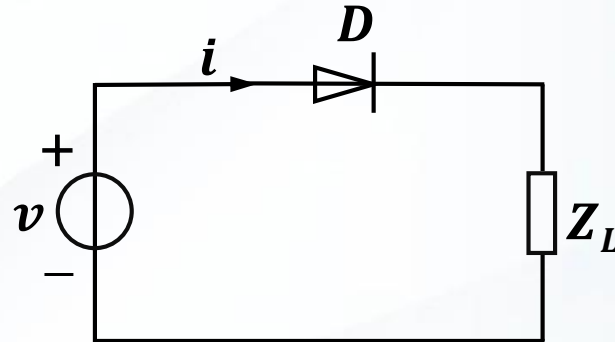
## (1) Power Series Analysis

➤ Eg. Diode,

$$i = a_0 + a_1(v - V_0) + a_2(v - V_0)^2 + a_3(v - V_0)^3 + \dots$$



➤ Cons

Signal is big, it will be complicated

## (2) Polygonal Line Analysis

- Curve  $\approx$  Multiple Line Segment

Example:  $OC$  Curve  $\approx OB + BC$


$$\begin{cases} i_c = 0 & (v_B < V_{BZ}) \\ i_c = g_c (v_B - V_{BZ}) & (v_B \geq V_{BZ}) \end{cases}$$

- Pros

Simplify

- Cons

Big signals, Eg, Power amplifier

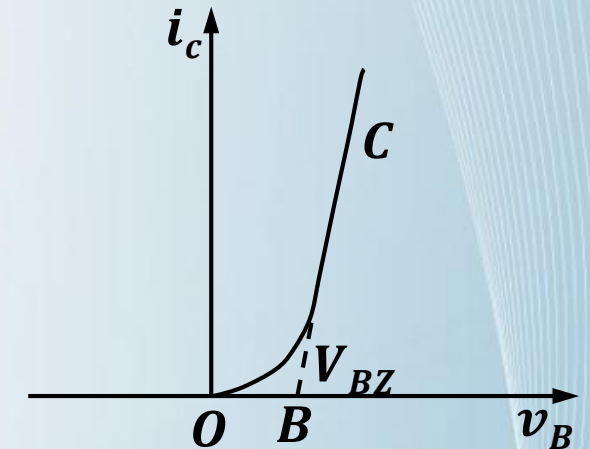

Transfer Curve



### (3) Linear Time-varying Analysis

➤ Big  $v_1$ : Quiescent Point Change

Small  $v_2$ , Linear

➤ Example:

Mixer=Time-varying Transconductance

