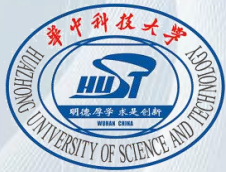


Huazhong University
of Science & Technology

Electronic Circuit of Communications

School of Electronic Information
and Communications

Jiaqing Huang




5 Oscillators

Classifications of Oscillators

- Comparison:
- RF Oscillator *vs.* RF Small Signal Amplifier & RF Power Amplifier?

Non-input *vs.* Has input

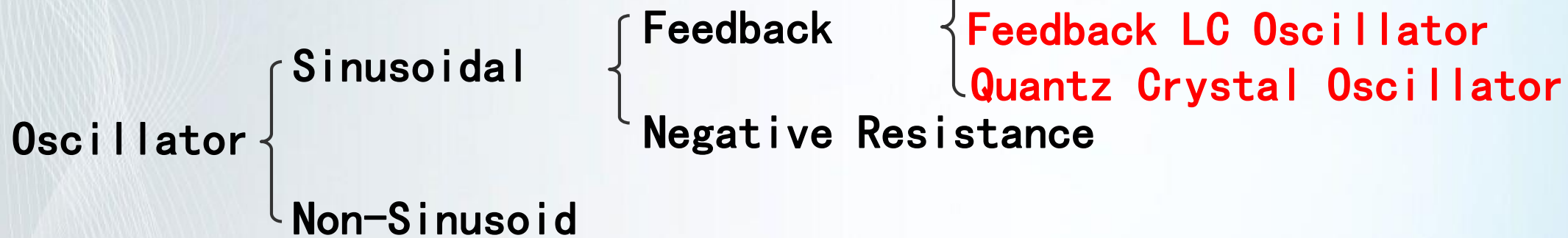

RC Oscillator *vs.* *LC* Oscillator?



Feedback LC Oscillator – Principle

➤ Why?

$L\&C$, Positive Feedback

➤ How?


➤ How to start? “0→1”

➤ Non-linear (Amplitude cannot be ∞)

➤ How to maintain?

➤ $K = “1”$, Resonant Amplifier, For $\dot{V}_f = \dot{V}_i$ by adjusting M

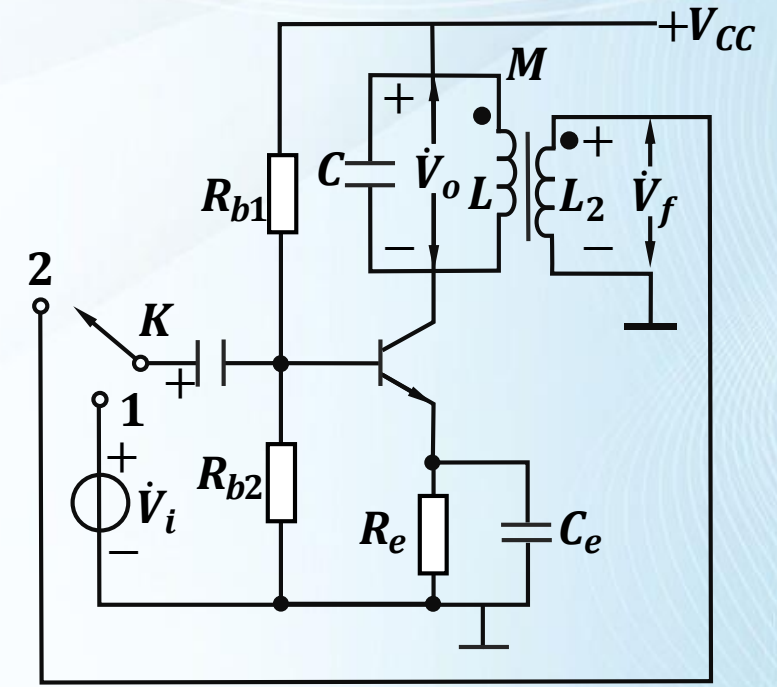➤ $K = “2”$, Resonant Amplifier → Oscillator



Feedback *LC* Oscillator – Essential Elements

- Resonant circuits

L & C

- Energy for compensating loss of L

V_{cc}

- Energy to active devices on right time

Positive Feedback + Active Devices

Feedback *LC* Oscillator – Conditions

- **Startup Condition**
- **Balance Condition**
- **Stability Condition for Balance**




Startup Condition

Startup Condition of Oscillator

- Idea: Amplifier $\dot{A}_f \rightarrow \infty \Rightarrow \text{Oscillator}$

$$\left\{ \begin{array}{l} \text{Open-loop Gain: } \dot{A}_o = \left. \frac{\dot{V}_o}{\dot{V}_i} \right|_{\dot{V}_f=0} \\ \text{Close-loop Gain: } \dot{A}_f = \frac{\dot{A}_o}{1 - \dot{A}_o \cdot \dot{F}} \end{array} \right. \quad \dot{F} = \frac{\dot{V}_f}{\dot{V}_o}$$

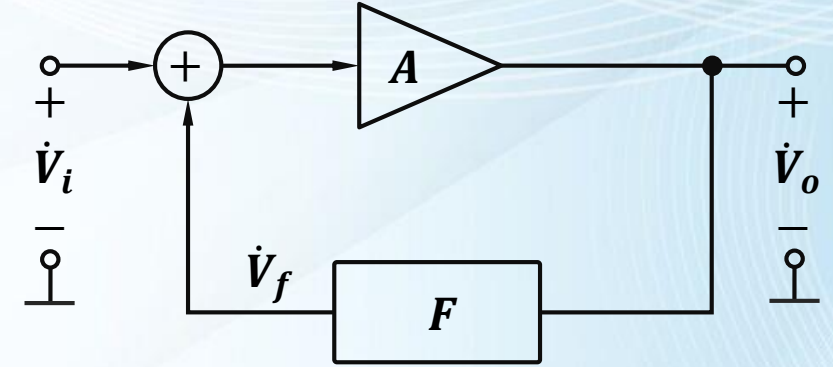

- $1 - \dot{A}_o \cdot \dot{F} = 0 \Rightarrow \dot{A}_f \rightarrow \infty$. Non-input, Amplifier \Rightarrow Oscillator
- If $\dot{A}_o \cdot \dot{F} = 1$, amplitude may not be strong
- F Should be big $\Rightarrow \dot{A}_o \cdot \dot{F} > 1$ In general $\frac{1}{8} \sim \frac{1}{2}$

Startup Condition of Oscillator

$$\triangleright \dot{A}_o \cdot \dot{F} > 1 \quad \begin{cases} A_o \cdot F > 1 \\ \varphi_A + \varphi_F = 2n\pi \quad (n = 0, \pm 1, \dots) \end{cases}$$


$$A_o > \frac{1}{F}$$

Amplitude Startup Condition
Phase Startup Condition

Startup A_0

Average A

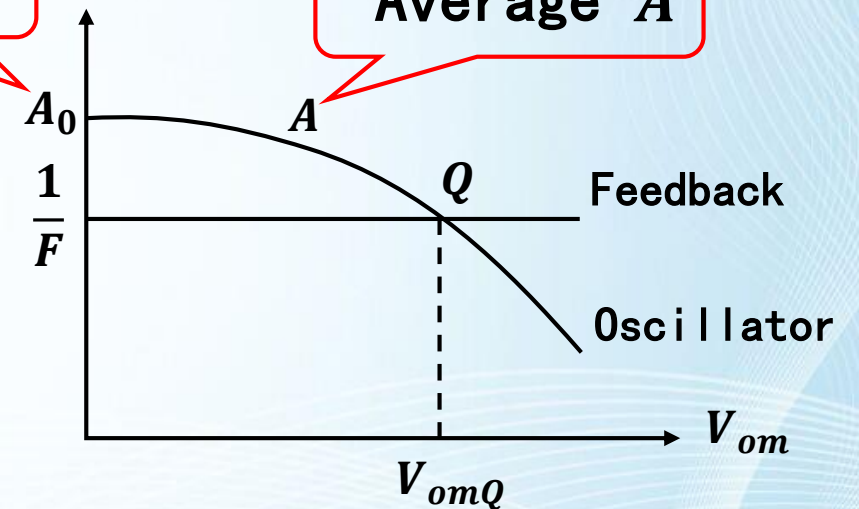- Oscillator Characteristics: A vs. V_o
- Feedback Characteristics : F vs. V_o



Soft-prompting

$$A = \frac{A_o}{\tau}, \quad \tau = 2 \sim 4$$


Startup Condition of Oscillator

$$A_o > \frac{1}{F}$$


$$\triangleright \dot{A}_o \cdot \dot{F} > 1 \quad \begin{cases} A_o \cdot F > 1 \\ \varphi_A + \varphi_F = 2n\pi \quad (n = 0, \pm 1, \dots) \end{cases}$$

Amplitude Startup Condition
Phase Startup Condition


A_0 is Small,
cannot
auto-startup

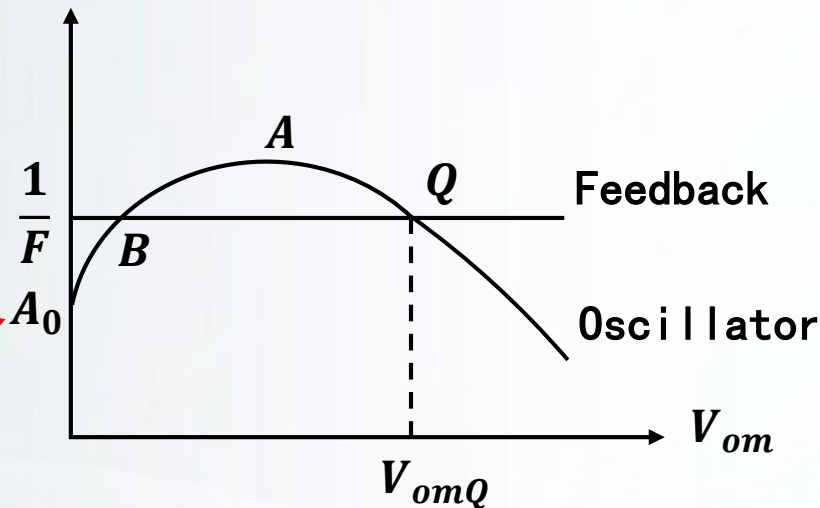

Hard-prompting

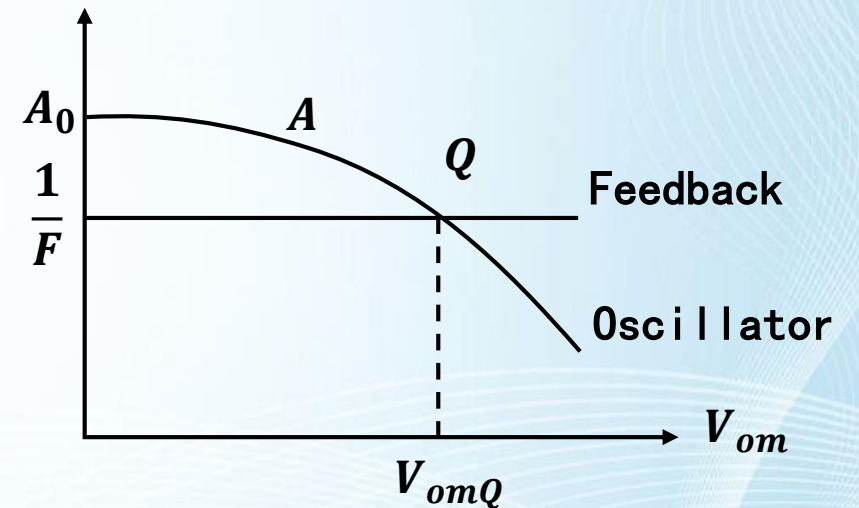

Soft-prompting

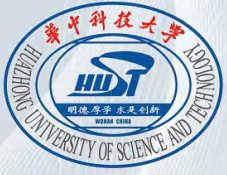



Balance Condition

Balance Condition of Oscillator

➤ $\dot{A} \cdot \dot{F} = 1$ $\begin{cases} A \cdot F = 1 \\ \varphi_A + \varphi_F = 2n\pi \end{cases} \quad (n = 0, 1, 2, 3 \dots)$ Amplitude Condition
Phase Condition

➤ Physical Significance:

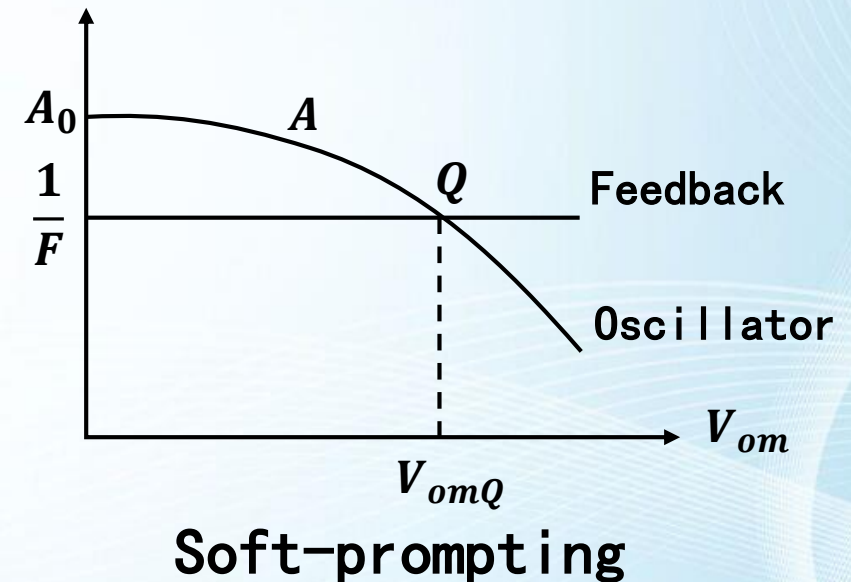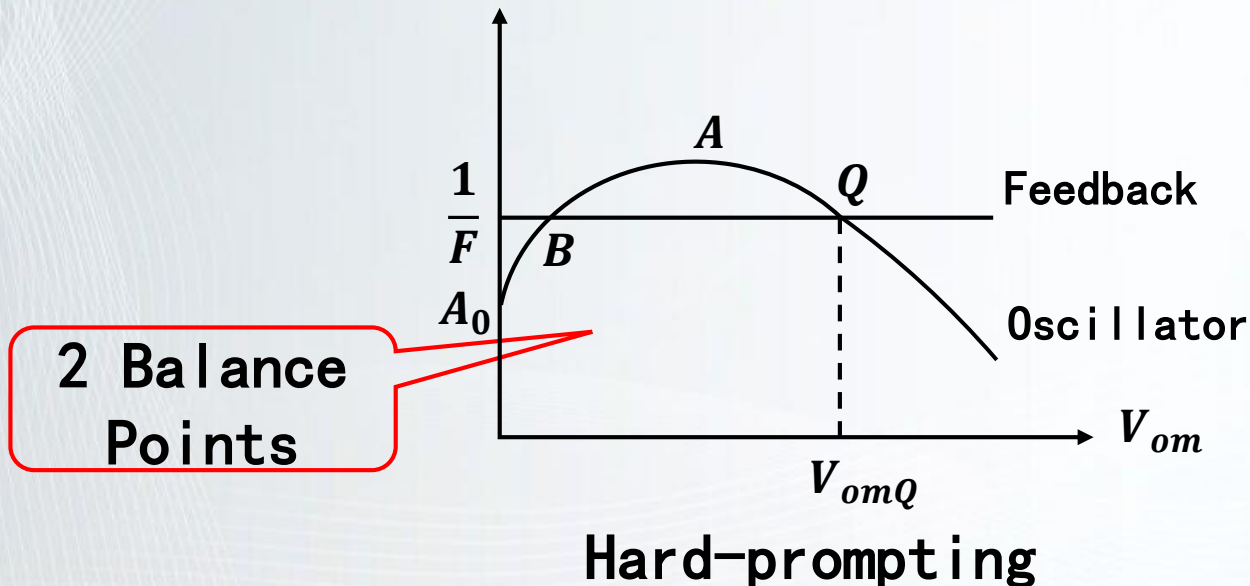$\dot{V}_f = \dot{V}_i$, Maintain Oscillator



Balance Condition of Oscillator (Circuit Parameters)

➤ $\dot{A} \cdot \dot{F} = 1$, To decompose $A = \text{Transistor} + \text{Parallel Resonance}$

$$\left\{ \begin{array}{l} \dot{A} \cdot \dot{F} = 1 \\ \dot{A} = \frac{\dot{V}_c}{\dot{V}_i} = \frac{\dot{I}_{c1} Z_{p1}}{\dot{V}_i} = \overline{y_{fe}} \cdot Z_{p1} \end{array} \right\} \overline{y_{fe}} \cdot Z_{p1} \cdot \dot{F} = 1$$

Parallel Resonance


Average forward y_{fe}

Circuit Parameters

➤ $\overline{y_{fe}} \cdot Z_{p1} \cdot \dot{F} = 1$ $\left\{ \begin{array}{l} |\overline{y_{fe}}| \cdot |Z_{p1}| \cdot F = 1 \\ \varphi_Y + \varphi_Z + \varphi_F = 2n\pi \end{array} \right. \quad \begin{array}{l} \text{Amplitude Condition} \\ \text{Phase Condition} \end{array} \quad (n = 0, 1, 2, 3 \dots)$

Summary


- Balance: $A \cdot F = 1,$ $\varphi_A + \varphi_F = 2n\pi$
- Balance (Circuit) : $|\overline{y_{fe}}| \cdot |Z_{p1}| \cdot F = 1,$ $\varphi_Y + \varphi_Z + \varphi_F = 2n\pi$
- Transistor
- Parallel Resonance

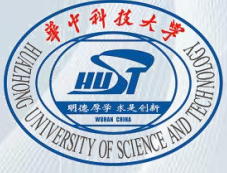

Stability Condition


Balance Stability Condition of Oscillator

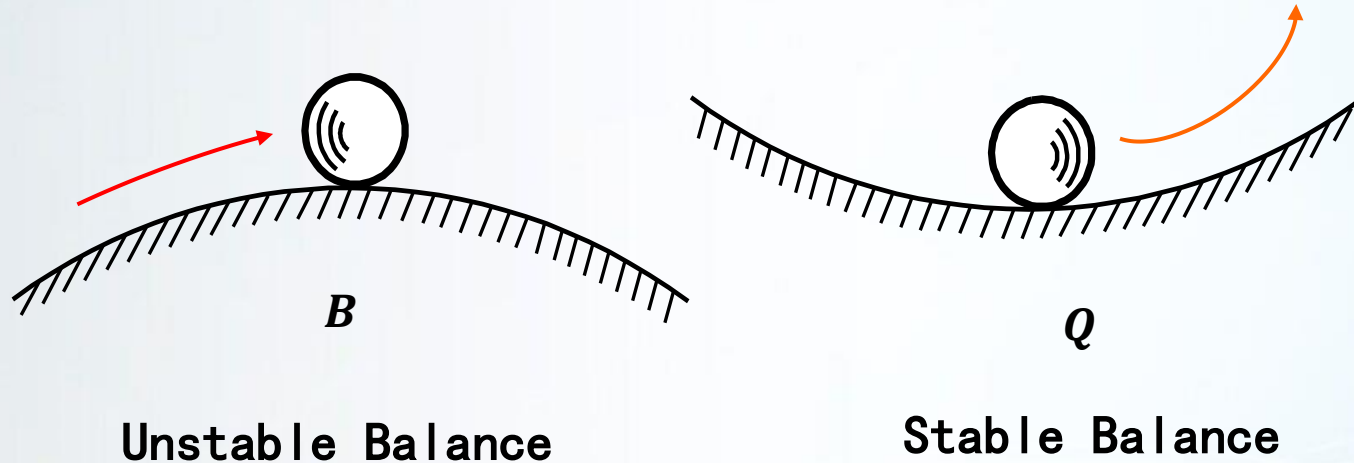- **Stability Condition of Balance:**
ability to recover automatically to balance status



Balance Stability Condition – Amplitude

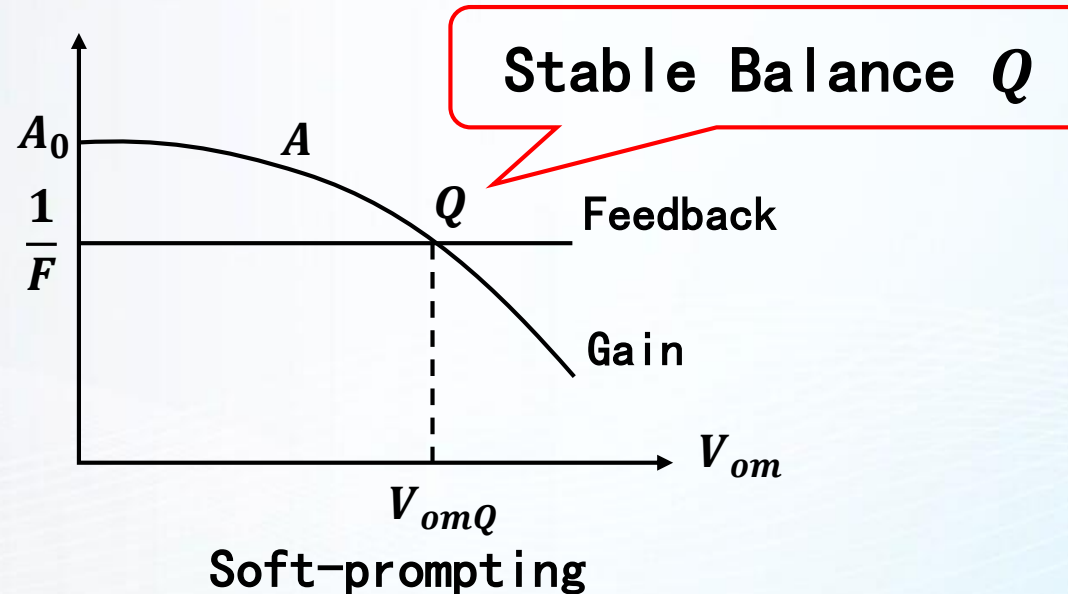
- ① If $V_{om} \uparrow (> V_{omQ})$, $A \downarrow$, $V_{om} \downarrow$, back to Q
- ② If $V_{om} \downarrow (< V_{omQ})$, $A \uparrow$, $V_{om} \uparrow$, back to Q



Balance Stability Condition – Amplitude

① If $V_{om} \uparrow (> V_{omB})$, $A \uparrow$, $V_{om} \uparrow$, far away from B

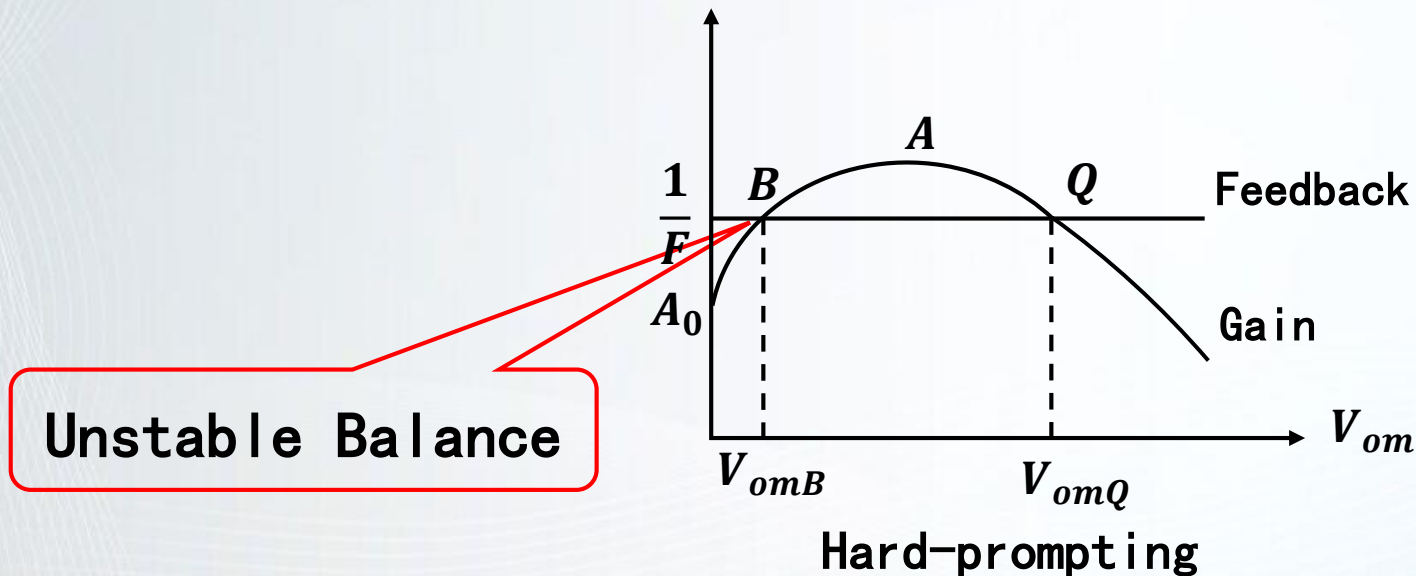② If $V_{om} \downarrow (< V_{omB})$, $A \downarrow$, $V_{om} \downarrow$, far away from B




Balance Stability Condition – Amplitude

- Condition: Gain A has negative slope around Q

$$\left. \frac{\partial A}{\partial V_{om}} \right|_{V_{om}=V_{omQ}} < 0 \quad \text{Stability Amplitude Condition}$$

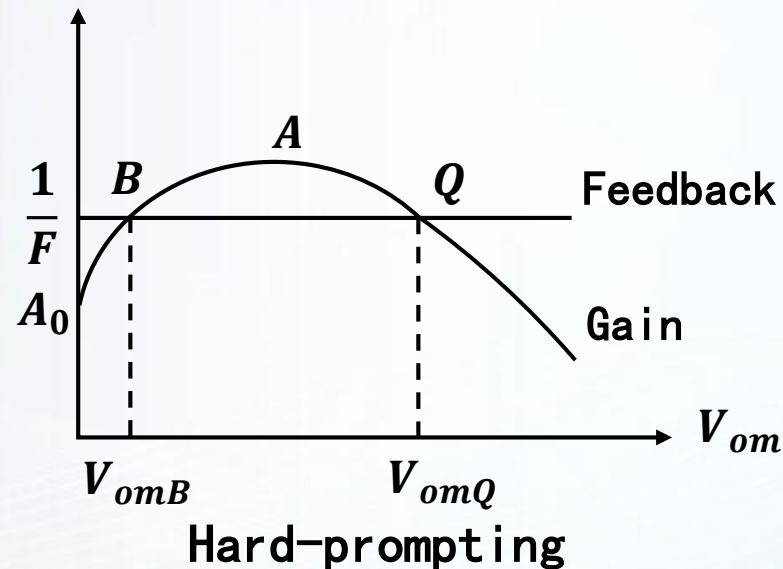- **Active devices** (Transistors) have this property, which can help stable amplitude



Balance Stability Condition – Phase

- Phase leads by external reasons \rightarrow Frequency \uparrow $\frac{\Delta\omega}{\Delta\varphi} > 0$
- To compensate $\Delta\varphi$: $\frac{\Delta\varphi}{\Delta\omega} < 0$
- Partial Differential Form: $\frac{\partial\varphi}{\partial\omega} < 0$ or $\frac{\partial(\varphi_Y + \varphi_Z + \varphi_F)}{\partial\omega} < 0$
- φ_Z dominates frequency changing

$$\left| \frac{\partial\varphi_Y}{\partial\omega} \right| \ll \left| \frac{\partial\varphi_Z}{\partial\omega} \right| \quad \left| \frac{\partial\varphi_F}{\partial\omega} \right| \ll \left| \frac{\partial\varphi_Z}{\partial\omega} \right|$$


Stability Phase Condition $\frac{\partial\varphi}{\partial\omega} \approx \frac{\partial\varphi_Z}{\partial\omega} < 0$

Balance Stability Condition – Phase

- Condition: Phase–frequency curve has negative slope

$$\frac{\partial \varphi}{\partial \omega} \approx \frac{\partial \varphi_Z}{\partial \omega} < 0 \quad \text{Stability Phase Condition}$$

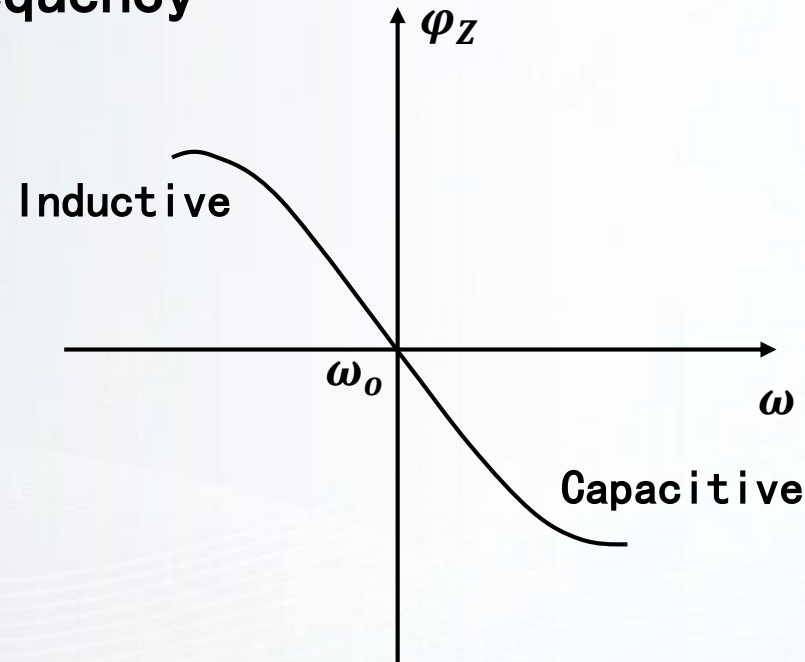- **LC** parallel resonance circuits have this property, which can help stable phase. Meanwhile, **LC** parallel resonance circuits determine frequency




Phase–Frequency Curve of Parallel Resonance

Balance Stability Condition – Phase

➤ To decrease $\Delta\omega$:

➤ $\varphi_{YF} \rightarrow 0$ (Resonant) \Rightarrow Stability \uparrow

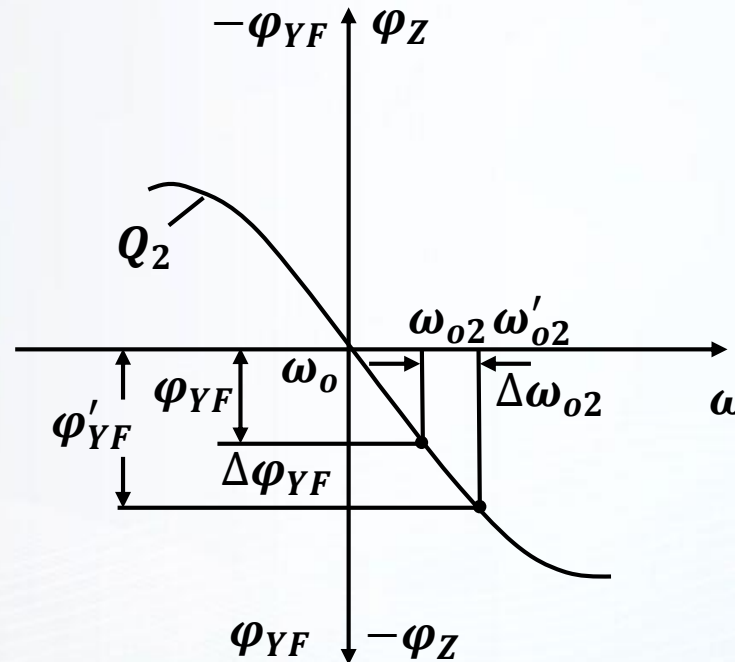➤ $\Delta\varphi_{YF} \downarrow \Rightarrow \Delta\omega \downarrow$



$$\varphi_Y + \varphi_Z + \varphi_F = 0$$

$$\varphi_Z = -(\varphi_Y + \varphi_F)$$

$$= -\varphi_{YF}$$

Balance Stability Condition – Phase

➤ To decrease $\Delta\omega$:

➤ $\varphi_{YF} \rightarrow 0$ (Resonant) \Rightarrow Stability \uparrow

➤ $\Delta\varphi_{YF} \downarrow \Rightarrow \Delta\omega \downarrow$

➤ Increase Q

