


Huazhong University  
of Science & Technology

# Electronic Circuit of Communications

School of Electronic Information  
and Communications

Jiaqing Huang

# Oscillators Classification

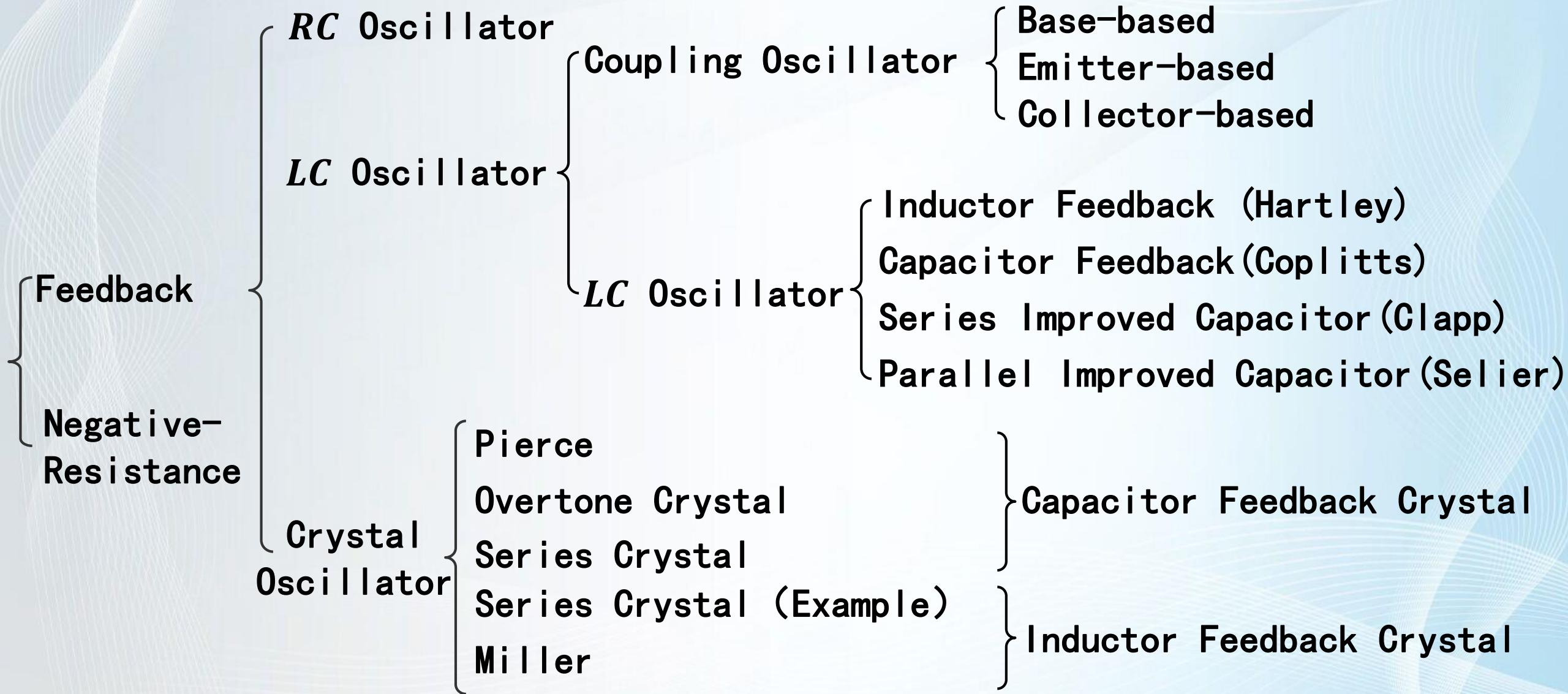




# Coupling Oscillators




# Oscillators Classification

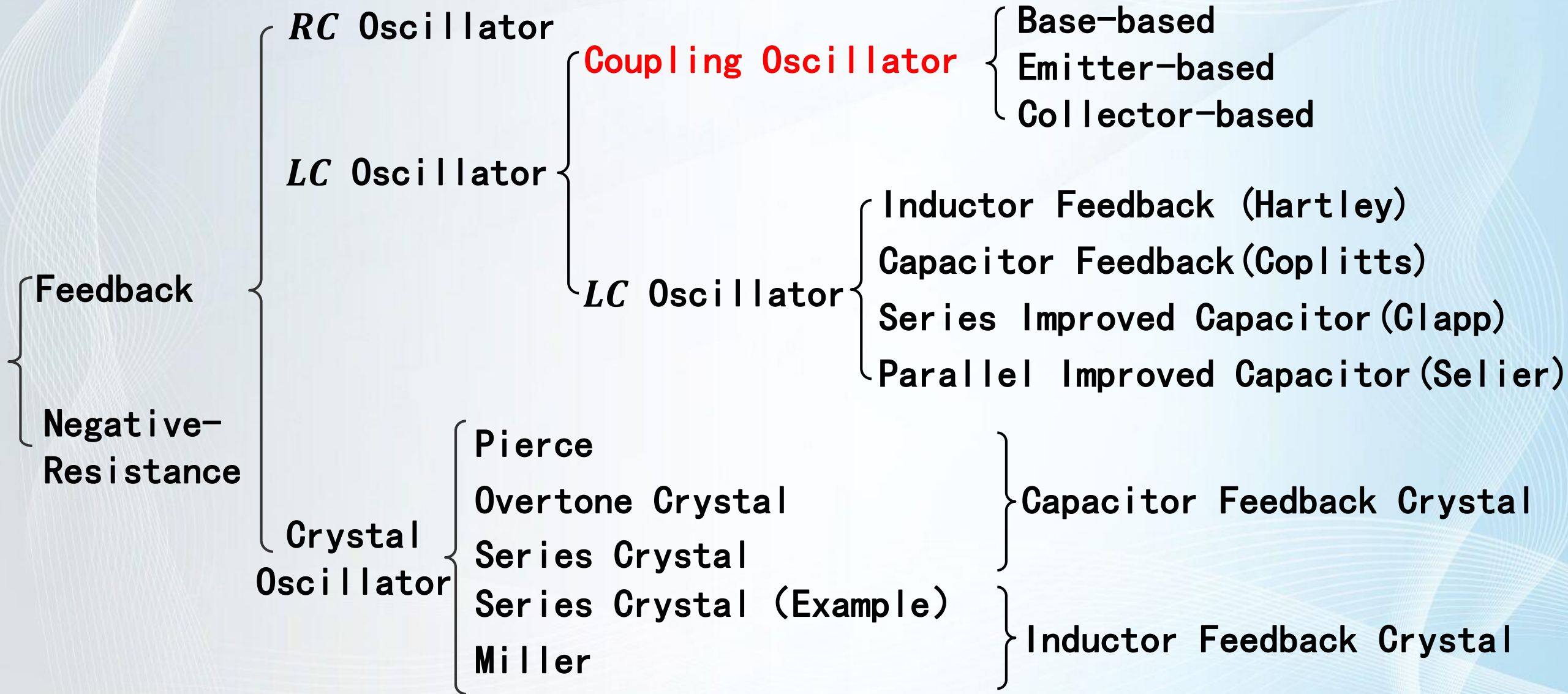

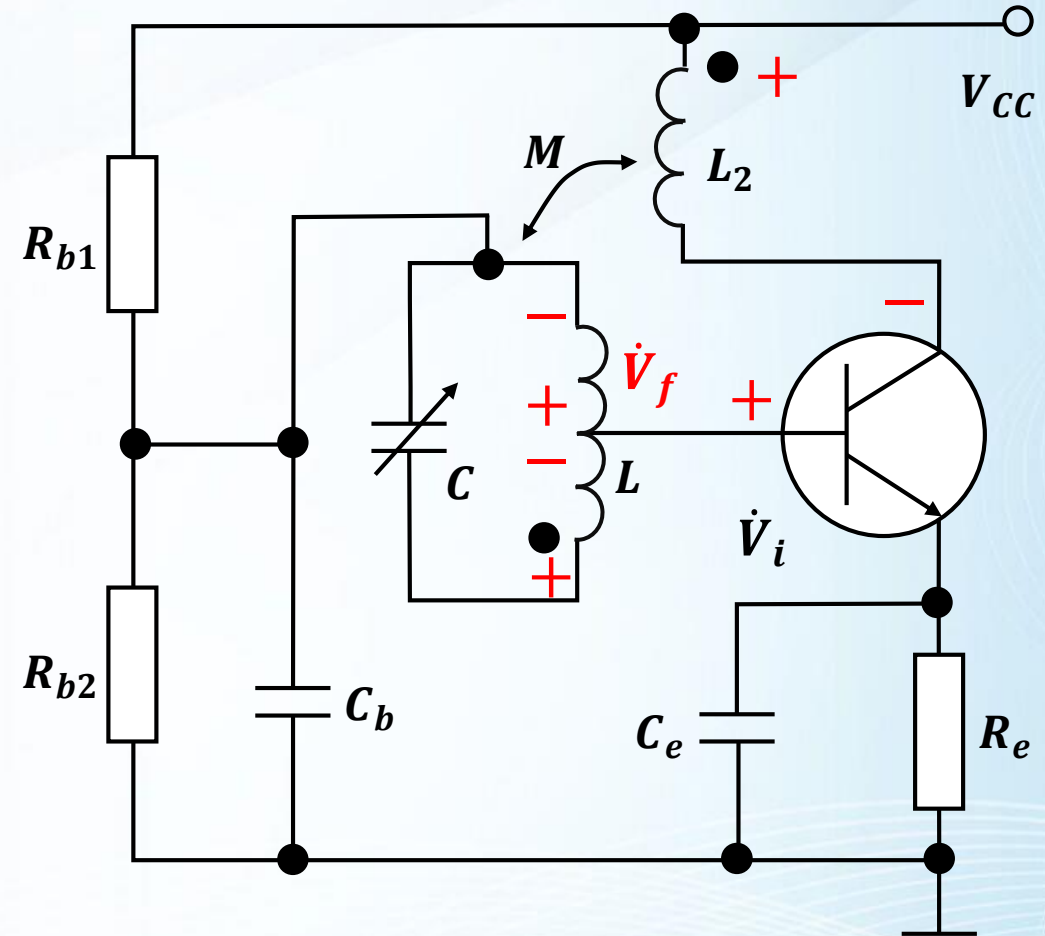
# Coupling Oscillator (Base)

- $R_i$  of b-e  $\downarrow \Rightarrow Q \downarrow$
- Tap-connected between Transistor & LC Oscillator
- Key: Determine  $\dot{V}_f$  ( $\dot{V}_f = \dot{V}_i$ )



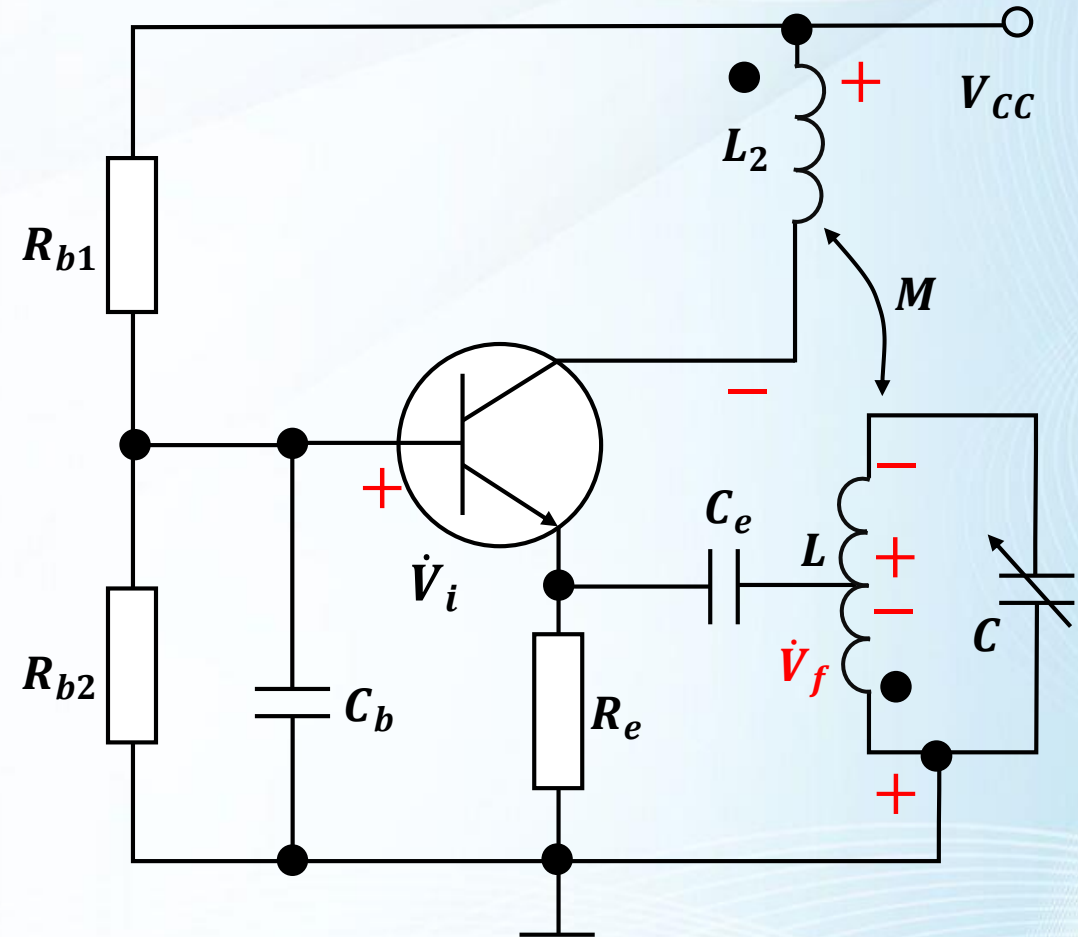
# Coupling Oscillator (Emitter)

- $R_i$  of b-e  $\downarrow \Rightarrow Q \downarrow$
- Tap-connected between Transistor & LC Oscillator
- Key: Determine  $\dot{V}_f$  ( $\dot{V}_f = \dot{V}_i$ )



# Coupling Oscillator (Collector)

➤ Stable output when radio frequency

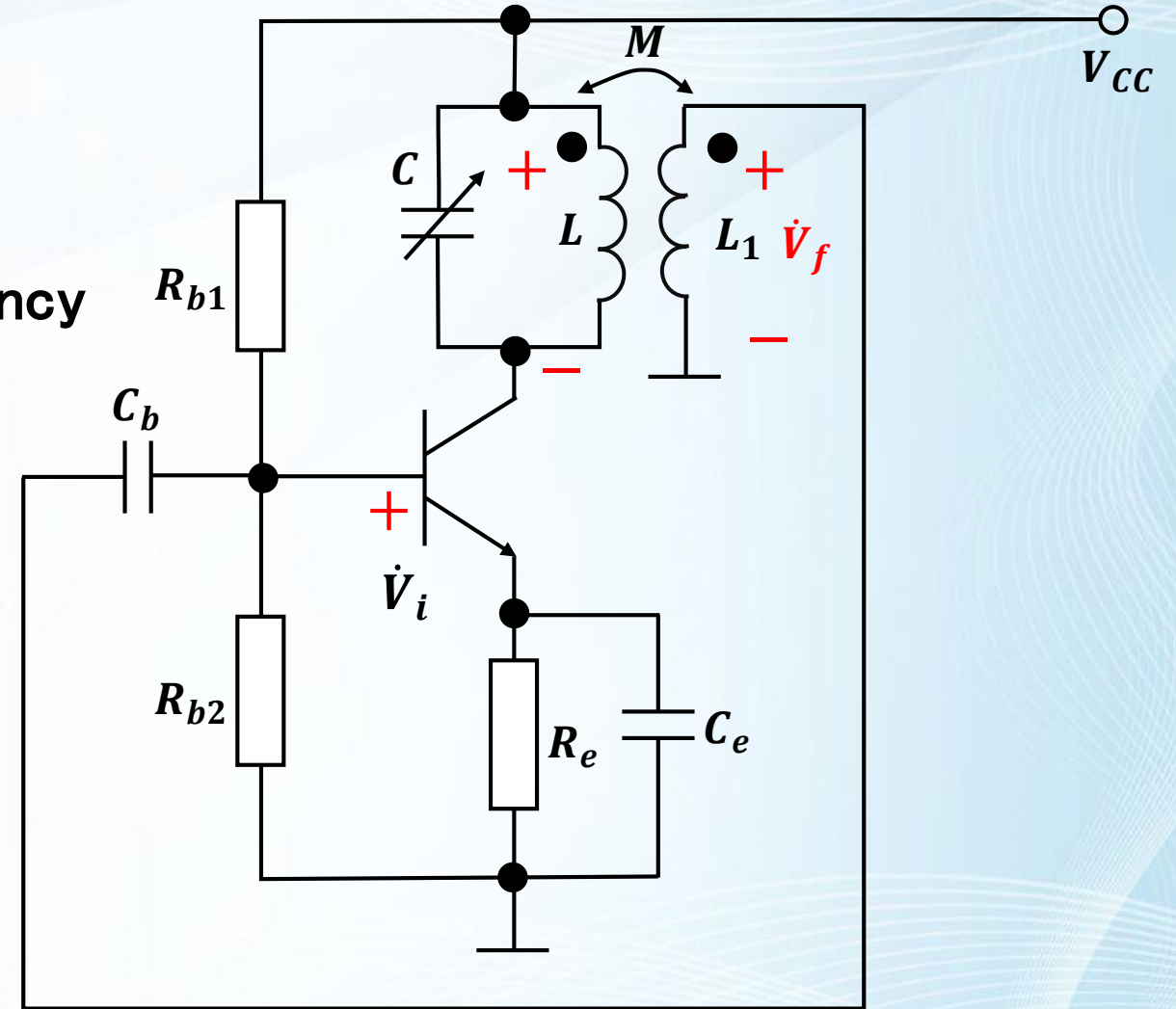


➤ Key: Determine  $\dot{V}_f$  ( $\dot{V}_f = \dot{V}_i$ )


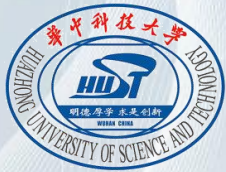
# Coupling Oscillator


- Oscillation Frequency:  $f_0 = \frac{1}{2\pi\sqrt{LC}}$
- Advantage:
  - Adjust  $F$  (by  $M$ )  $\nRightarrow f_0$
- Disadvantage:
  - Upper-bound frequency can not be high  
Reason: Distributed capacitance of transformer, unstable






# Inductor Feedback Oscillators


# Oscillators Classification

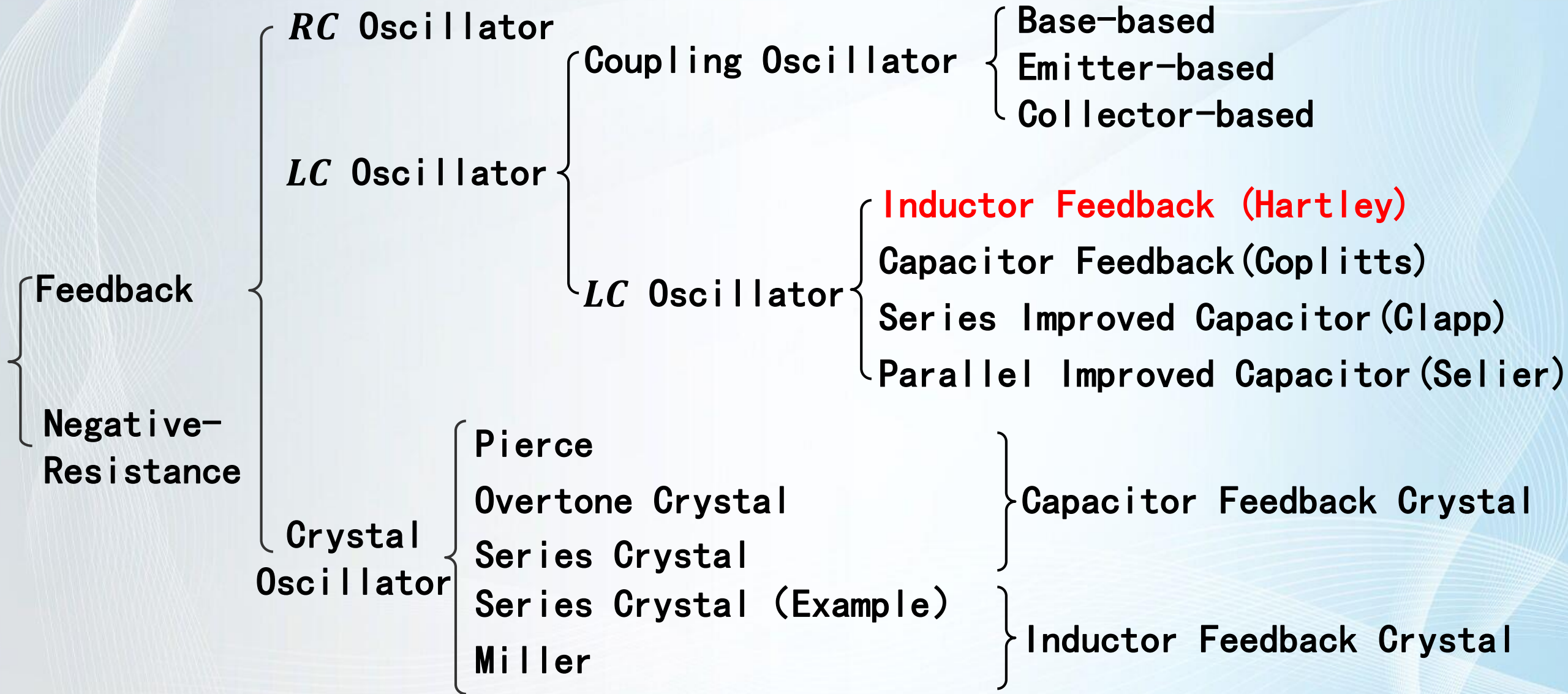

# Inductor Feedback Oscillator (Hartley)

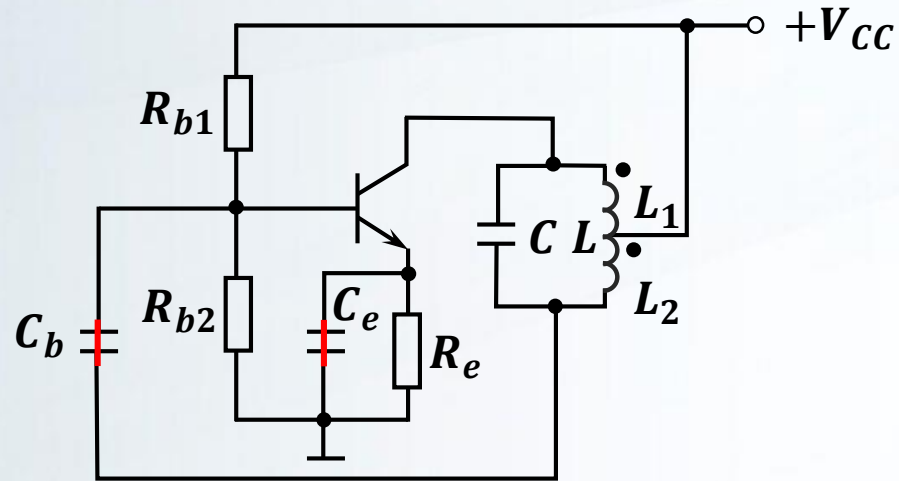

Inductor Feedback Oscillator

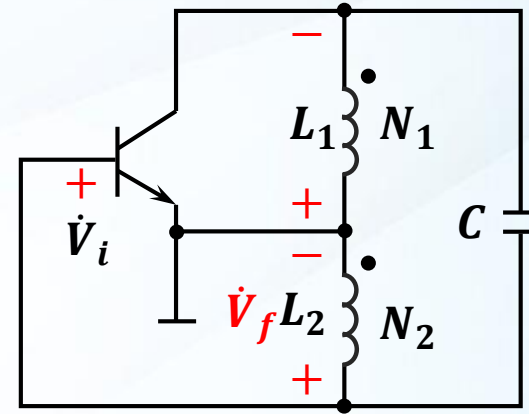


Equivalent Circuit

## ➤ RF Equivalent Circuit Principle


- Resistor Open:  $R_{b1}$ ,  $R_{b2}$ ,  $R_e$
- Inductor Open: No RF Choke
- Capacitor Short:
  - Bypass Capacitor:  $C_e$
  - Coupling Capacitor:  $C_b$
  - Power Filter Capacitor: None



# Inductor Feedback Oscillator (Hartley)

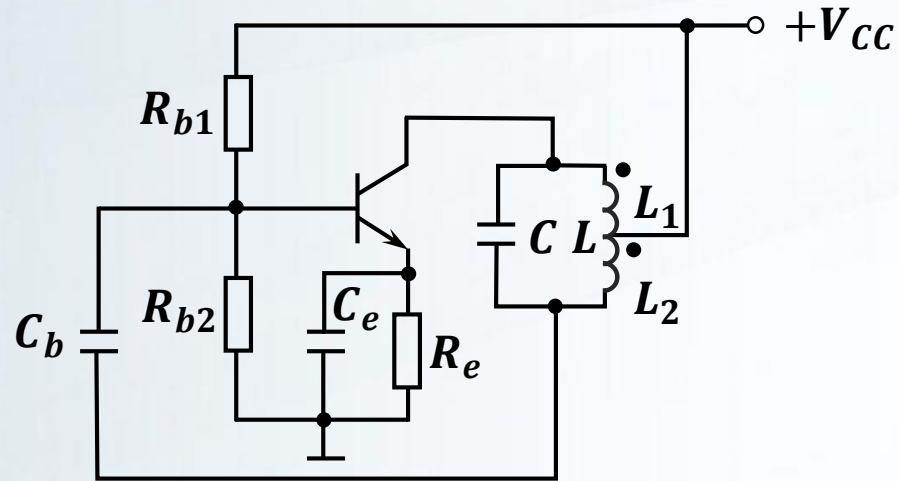

Inductor Feedback Oscillator

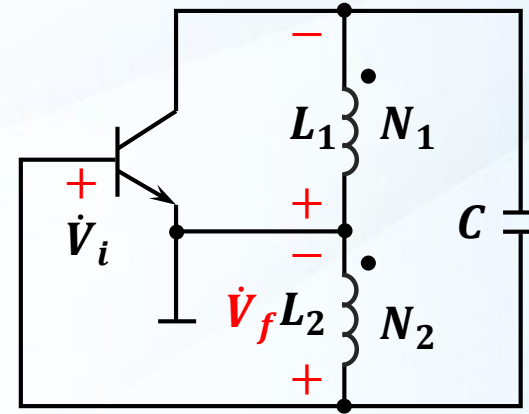


Equivalent Circuit

**Oscillation Frequency:**  $f_0 \approx \frac{1}{2\pi\sqrt{LC}}$        $L = L_1 + L_2 + 2M$


**Feedback Coefficient:**  $F = \frac{L_2 + M}{L_1 + M}$



# Inductor Feedback Oscillator (Hartley)

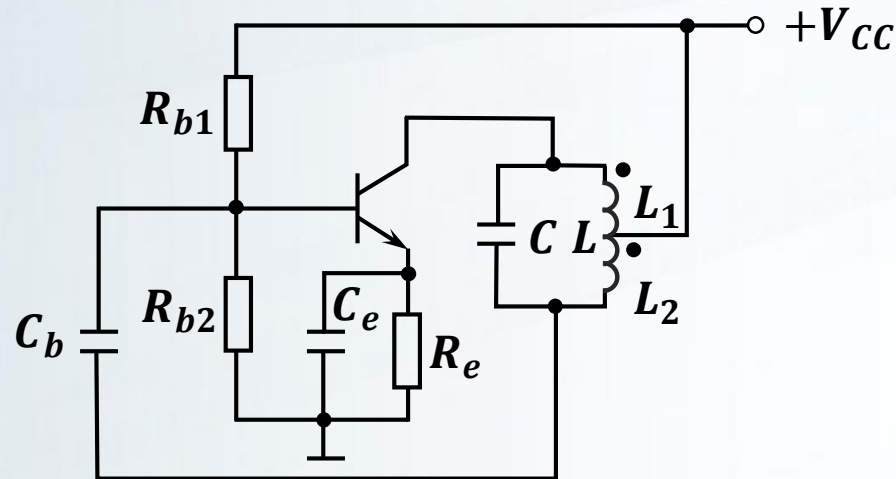


Inductor Feedback Oscillator

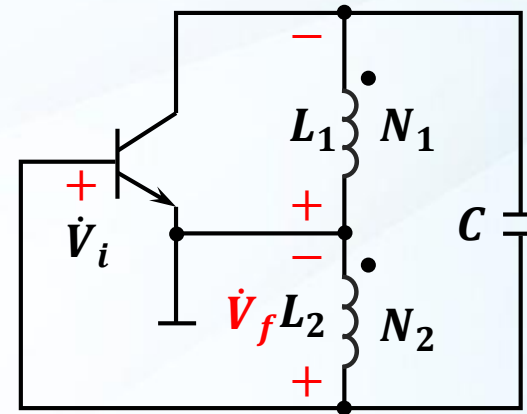

Equivalent Circuit


- Advantage:**
- 1)  $M$  between  $L_1$  &  $L_2$  is strong to start oscillation easily
  - 2) Adjust frequency by  $C$  conveniently
  - 3)  $C \neq F$

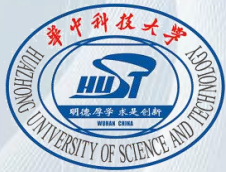- Disadvantage:**
- 1) Distorted oscillation waveform  
Reason: high feedback/impedance of Inductors
  - 2) Upper-bound frequency is not high  
Reason: distributed capacitance





# Capacitor Feedback Oscillators

# Oscillators Classification

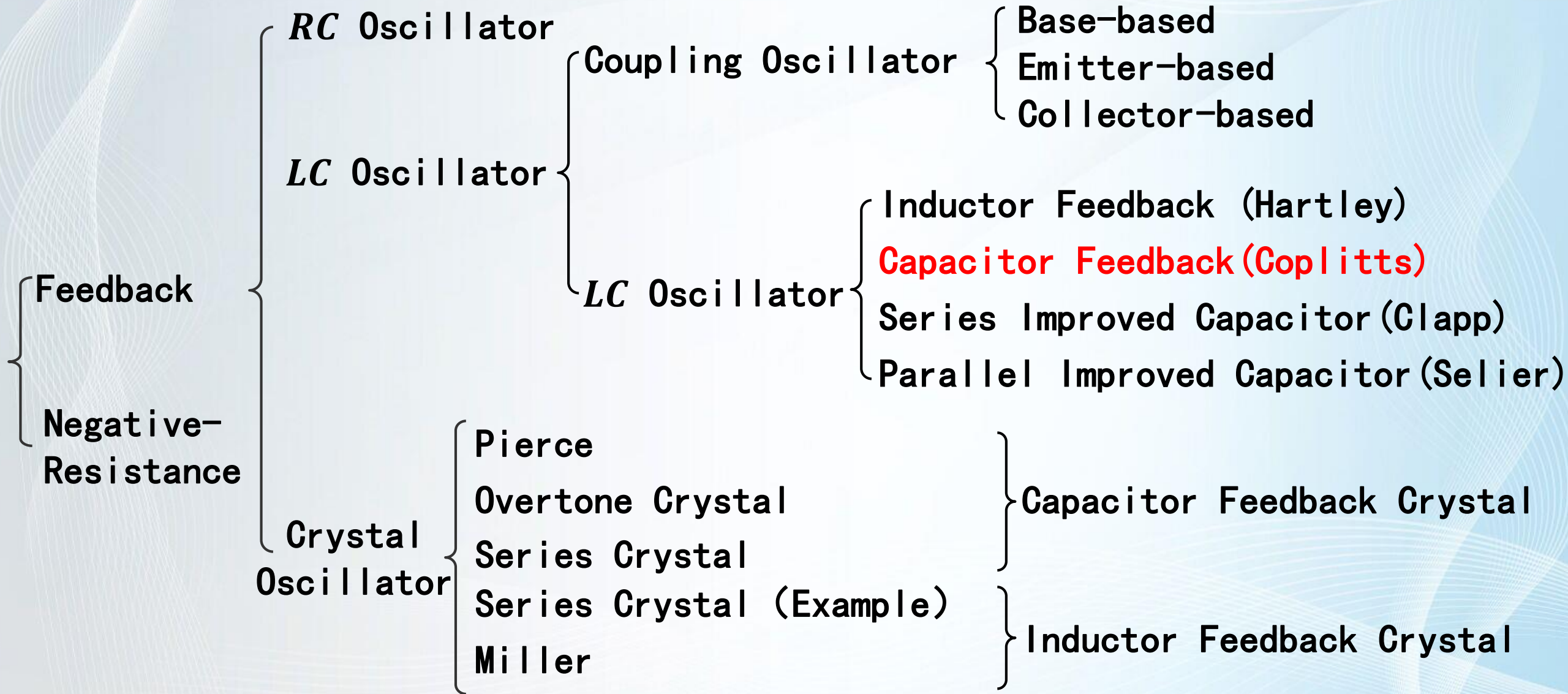


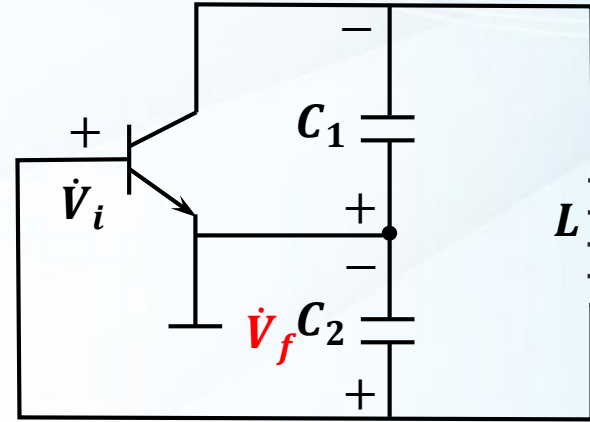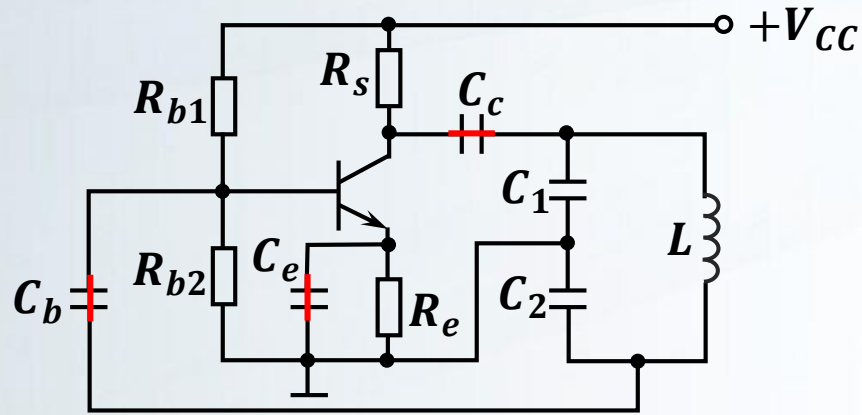
# Capacitor Feedback Oscillator (Coplitts)





## ➤ RF Equivalent Circuit Principle

- Resistor Open:  $R_{b1}$ 、 $R_{b2}$ 、 $R_e$ 、 $R_s$
- Inductor Open: No RF Choke
- Capacitor Short:
  - Bypass Capacitor:  $C_e$
  - Coupling Capacitor:  $C_b$ 、 $C_c$
  - Power Filter Capacitor: None



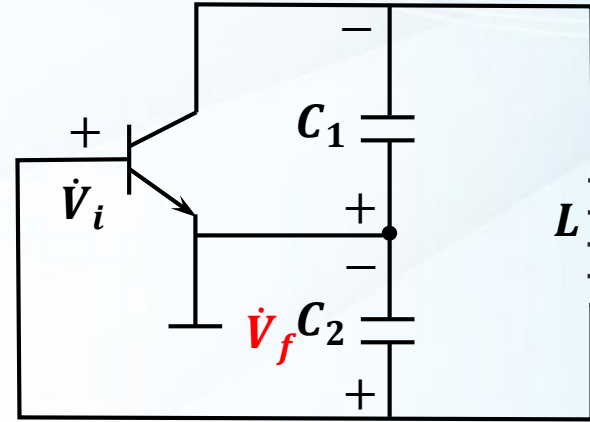
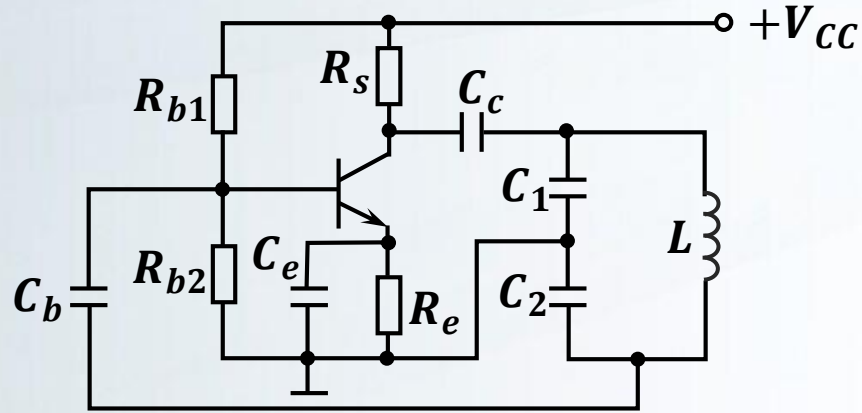
# Capacitor Feedback Oscillator (Coplitts)



## ➤ Advantage:

- Better oscillation waveform
- Better stability
- Higher frequency
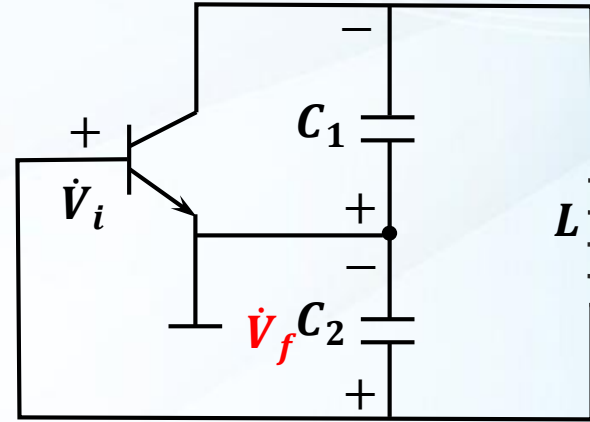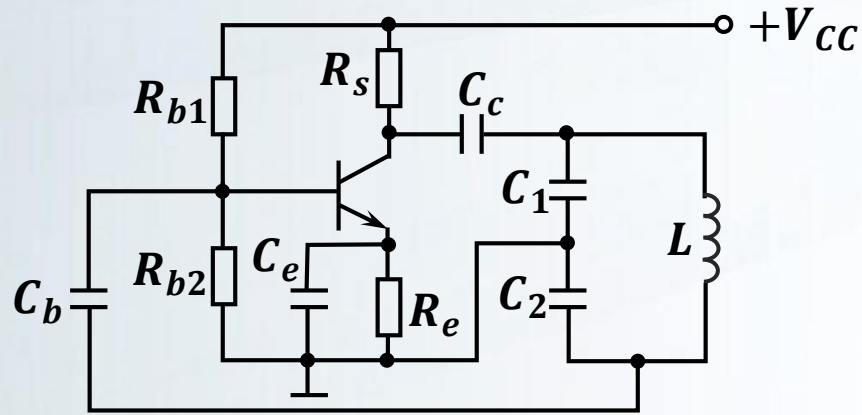
# Capacitor Feedback Oscillator (Coplitts)




$$\left\{ \begin{array}{l} \text{Frequency } f_0 \approx \frac{1}{2\pi\sqrt{LC}} \\ \text{Feedback } F = \frac{C_1}{C_2} \end{array} \right. \quad C = \frac{C_1 C_2}{C_1 + C_2}$$

## ➤ Disadvantage:

➤ Adjust  $f_0$  by  $C_1$  or  $C_2 \Rightarrow F$  (Solution:  $L //$  a capacitor)


➤  $F \Rightarrow f_0$

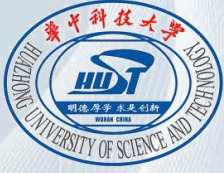

# Series Improved Capacitor Feedback Oscillators




# Oscillators Classification

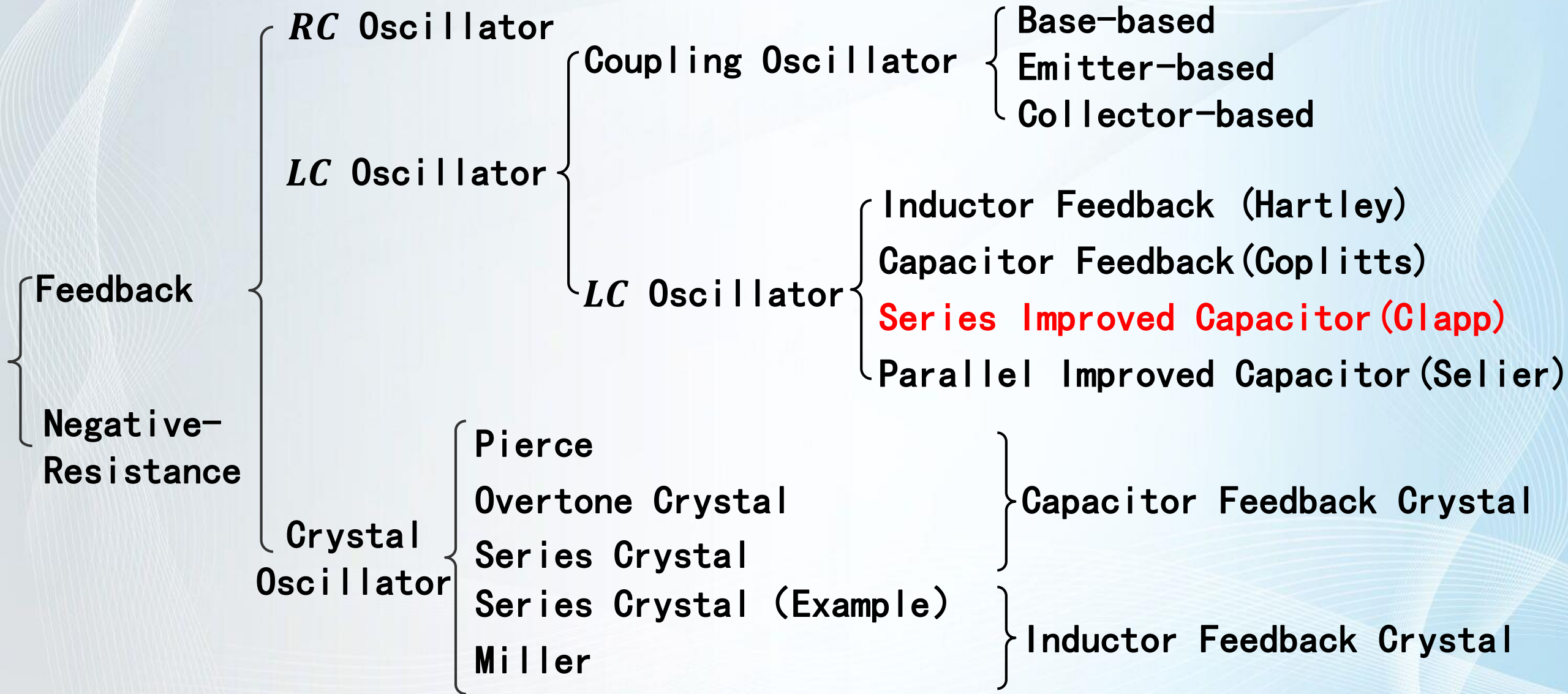




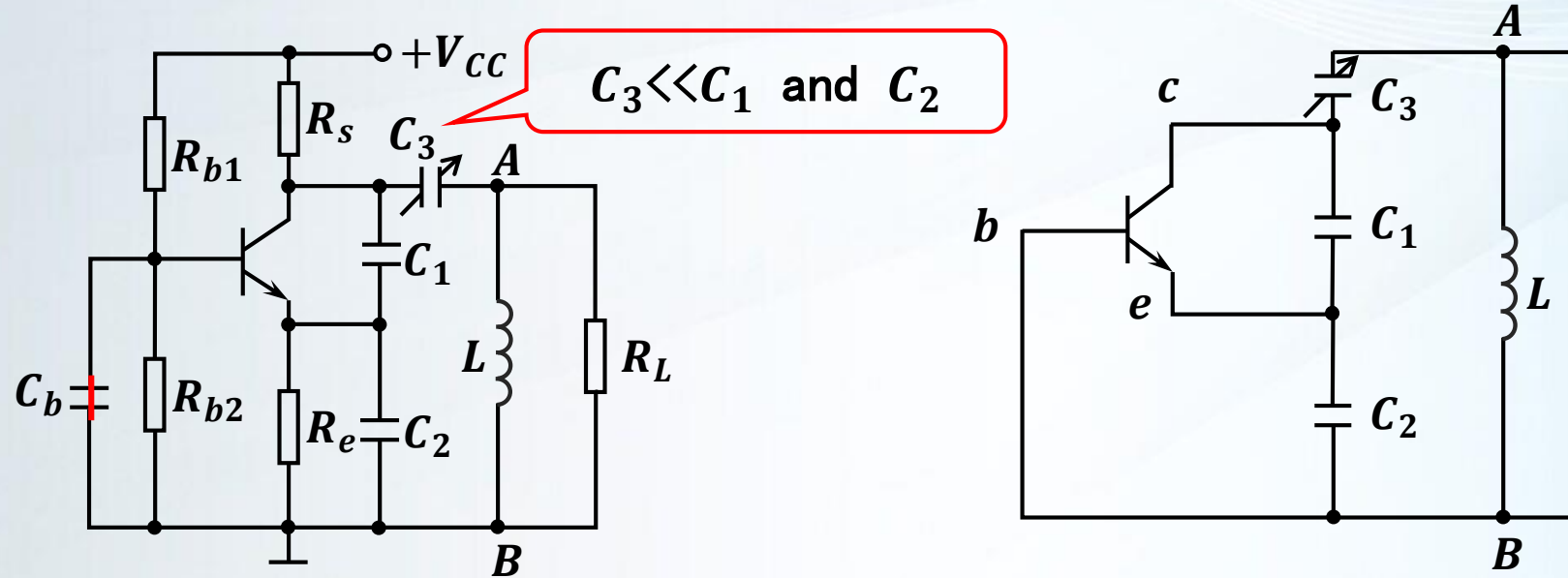
# Series Improved Capacitor Feedback Oscillator (Clapp)



## ➤ Equivalent Circuit Principle

- Resistor Open:  $R_{b1}$ 、 $R_{b2}$ 、 $R_e$ 、 $R_s$ 、 $R_L$
- Inductor Open: No RF Choke
- Capacitor Short:
  - Bypass Capacitor:  $C_b$
  - Coupling Capacitor: None
  - Power Filter Capacitor: None
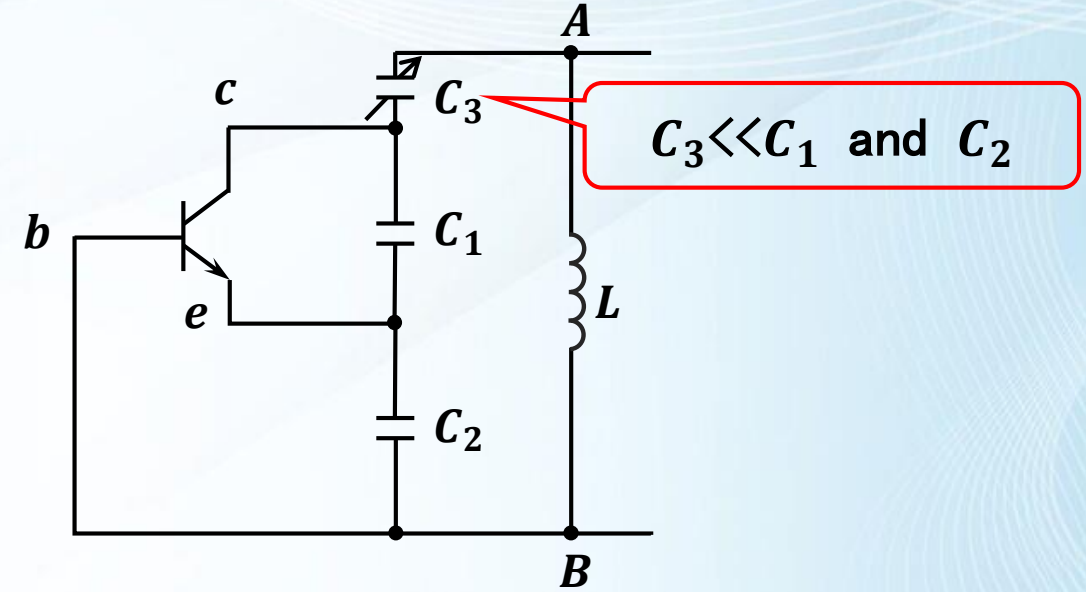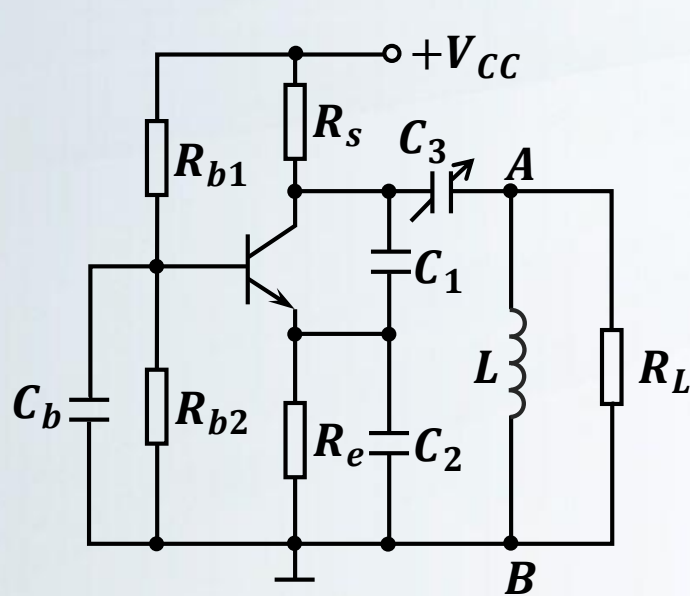
# Series Improved Capacitor Feedback Oscillator (Clapp)




$$\left\{ \begin{array}{l} \text{Frequency } f_0 \approx \frac{1}{2\pi\sqrt{LC}} \approx \frac{1}{2\pi\sqrt{LC_3}} \\ \text{Feedback } F = \frac{C_1}{C_2} \end{array} \right.$$

$$f_0 \Leftrightarrow F$$

$$\begin{aligned} \text{Total } C &= C_1 + C_2 + C_3 \\ C &= \frac{C_1 C_2 C_3}{C_1 C_2 + C_2 C_3 + C_1 C_3} = \frac{C_3}{1 + \frac{C_3}{C_1} + \frac{C_3}{C_2}} \approx C_3 \end{aligned}$$

# Series Improved Capacitor Feedback Oscillator (Clapp)

- **Stability?** (input output capacitance)
  - **Clue:** tap-connected

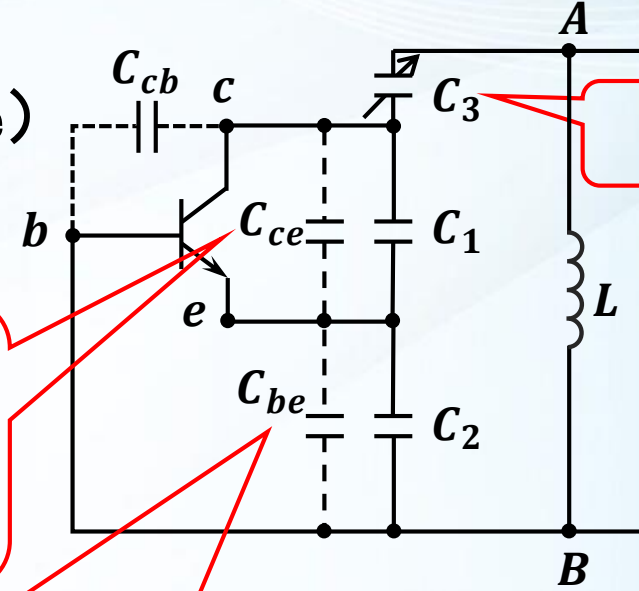
$$C_3 \ll C_1 \text{ and } C_2$$

**Access Factor:  $p'_{ce} \approx \frac{C_3}{C_1} \ll 1$**   
**Equivalent impedance of  $C_{ce} \downarrow \downarrow$**   
**Stability  $\uparrow \uparrow$**

**Access Factor:  $p'_{be} \approx \frac{C_3}{C_2} \ll 1$**   
**Equivalent impedance of  $C_{be} \downarrow \downarrow$**   
**Stability  $\uparrow \uparrow$**

## Better frequency stability



# Series Improved Capacitor Feedback Oscillator (Clapp)

Key:  $C_3 \ll C_1$  and  $C_2$

## ➤ Advantage

- Loose coupling ( $C_{ce}$ 、 $C_{be}$  with small access factor)
- Adjust  $F$  by  $C_1$ 、 $C_2 \Rightarrow f_0$
- Adjust  $f_0$  by  $C_3 \Rightarrow F$

## ➤ Disadvantage


- Narrow wave range (Cover factor =  $\frac{f_{0max}}{f_{0min}} = 1.2 \sim 1.3$ )
- Output amplitudes vary with frequencies






# Parallel Improved Capacitor Feedback Oscillators

# Oscillators Classification

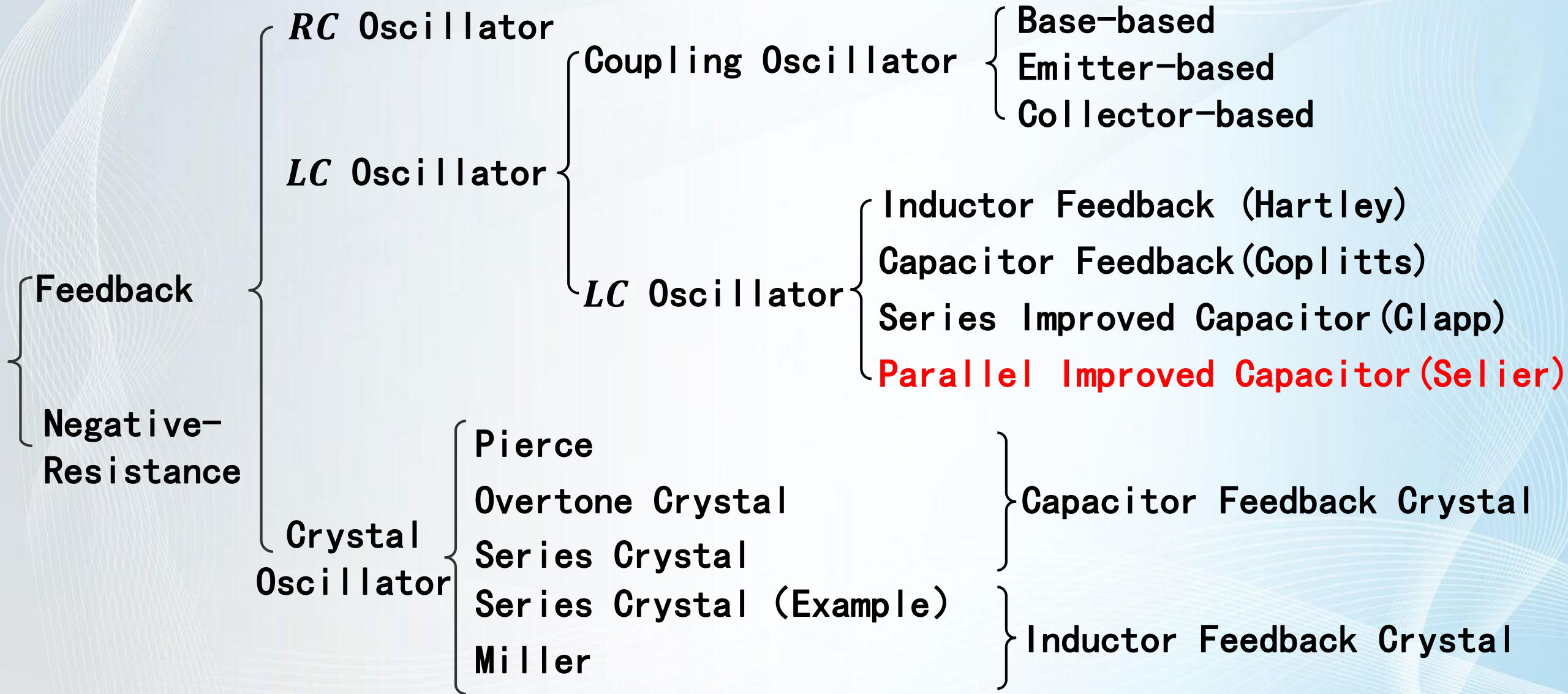

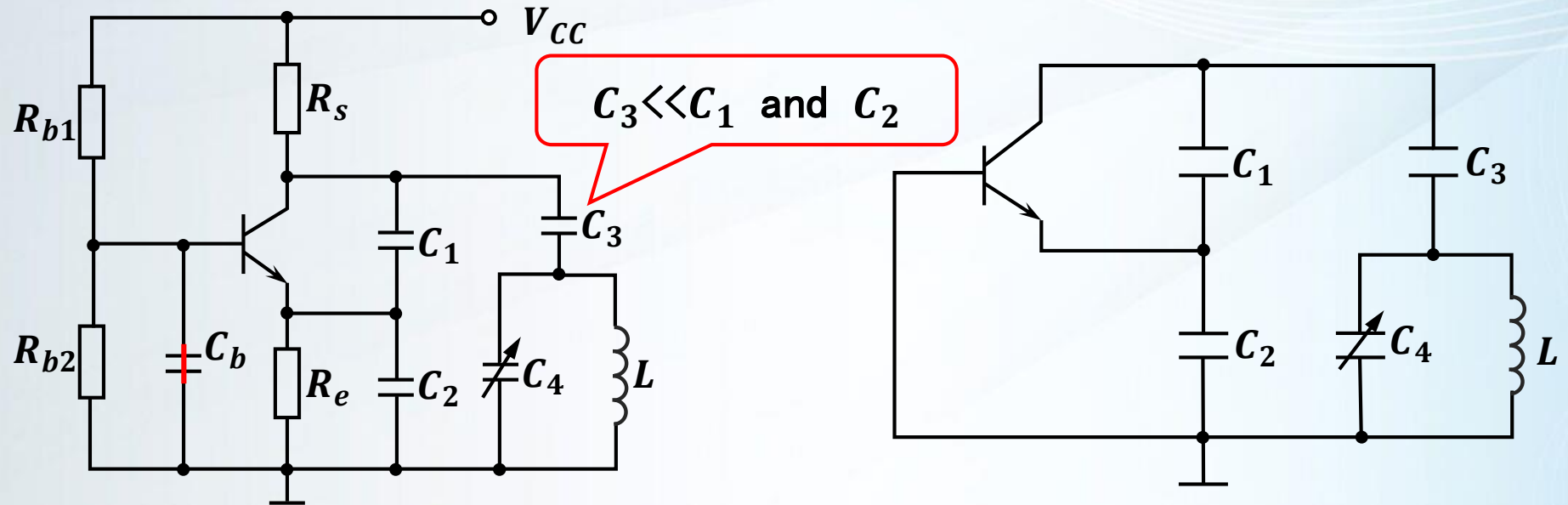
# Parallel Improved Capacitor Feedback Oscillator (Seiler)



- RF Equivalent Circuit Principle
  - Resistor Open:  $R_{b1}$ 、 $R_{b2}$ 、 $R_e$ 、 $R_s$
  - Inductor Open: No RF Choke
  - Capacitor Short:
    - Bypass Capacitor:  $C_b$
    - Coupling Capacitor: None
    - Power Filter Capacitor: None


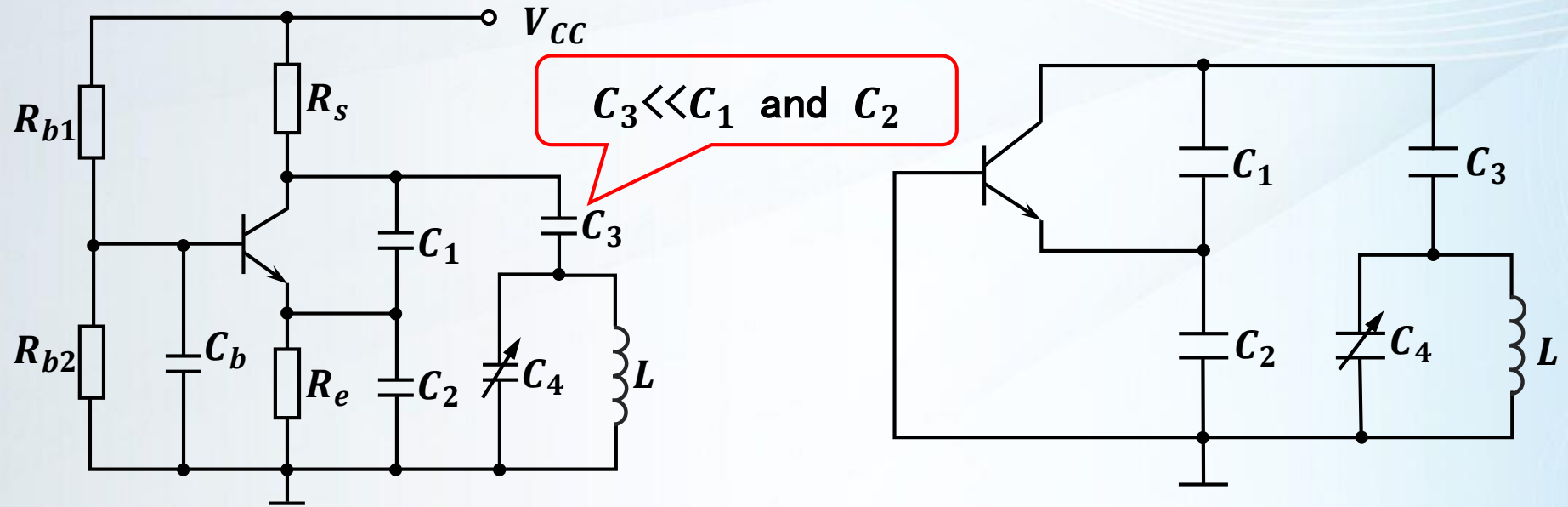
# Parallel Improved Capacitor Feedback Oscillator (Seiler)



Frequency  $f_0 \approx \frac{1}{2\pi\sqrt{LC}} \approx \frac{1}{2\pi\sqrt{L(C_3 + C_4)}}$


Feedback  $F = \frac{C_1}{C_2}$

$f_0 \Leftrightarrow F$

Total  $C = (C_1 + C_2 + C_3) // C_4$

$$C = \frac{C_1 C_2 C_3}{C_1 C_2 + C_2 C_3 + C_1 C_3} + C_4 \approx C_3 + C_4$$

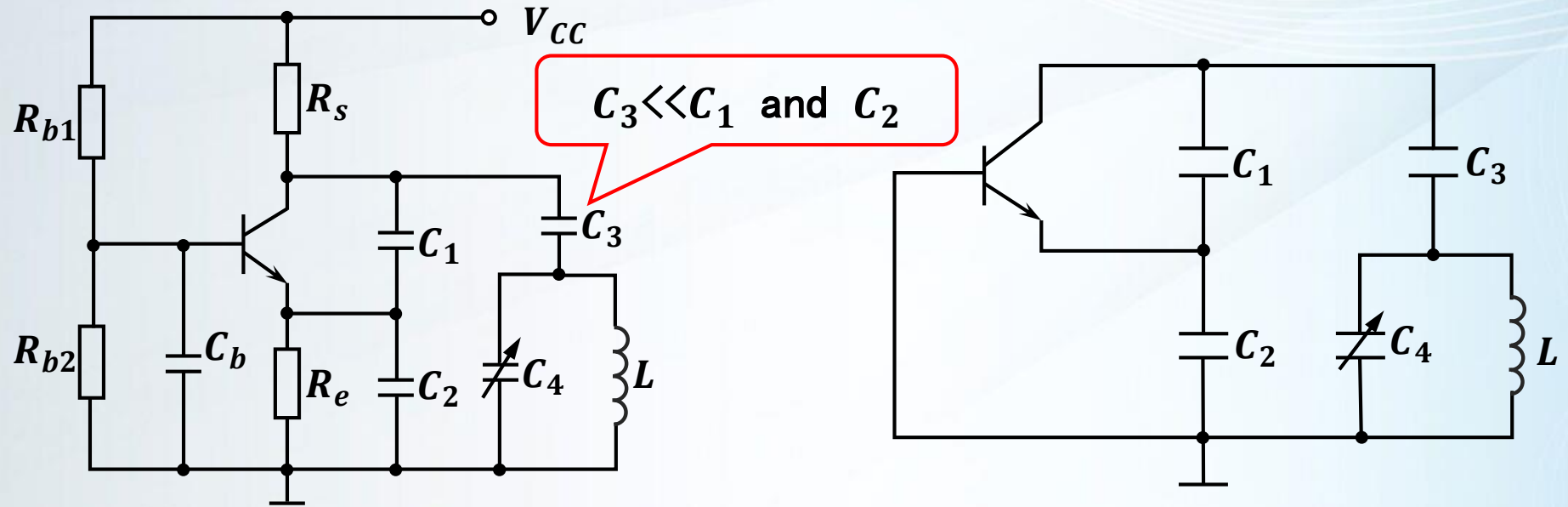
# Parallel Improved Capacitor Feedback Oscillator (Seiler)



## ➤ Selection of $C_3$

- $C_3$  too small, loosely coupling, not easy to start
- $C_3$  too big, stability ↓
- In general, decrease  $C_3$  as much as possible when startup condition is satisfied

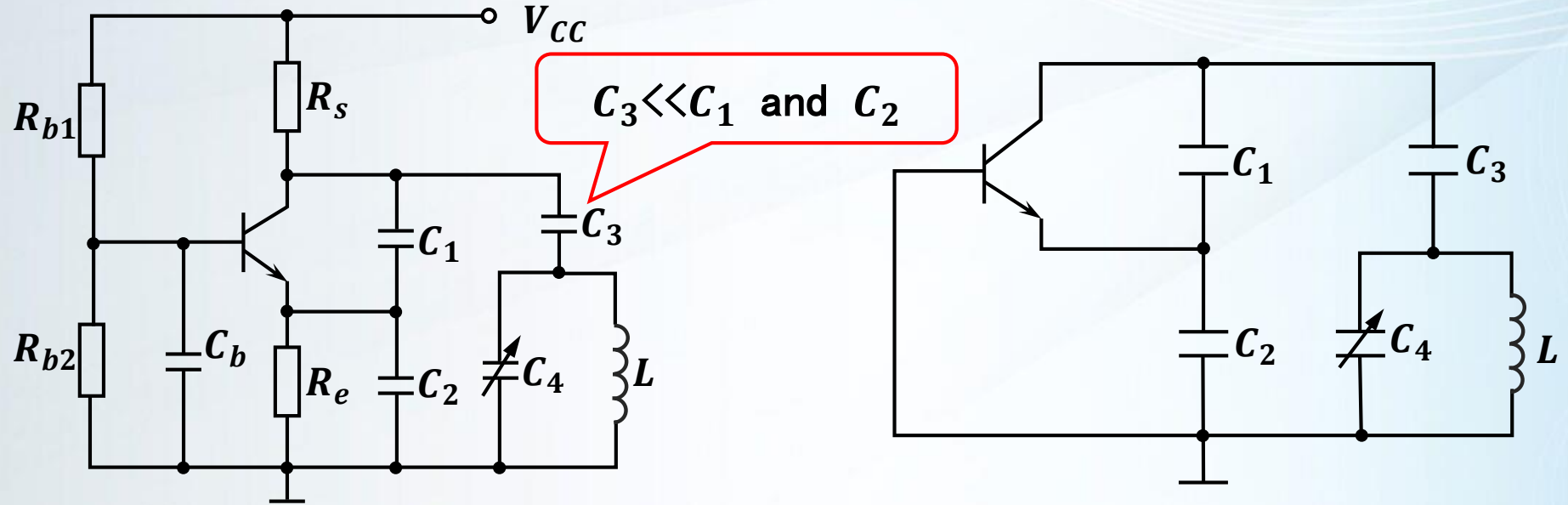
# Parallel Improved Capacitor Feedback Oscillator (Seiler)


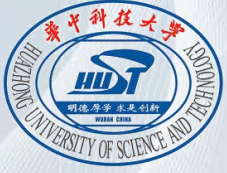
## ➤ Advantage

- Wide wave range (Cover factor =  $\frac{f_{0max}}{f_{0min}} = 1.6 \sim 1.8$ )
- Output amplitudes are stable







# Criteria of LC Composition
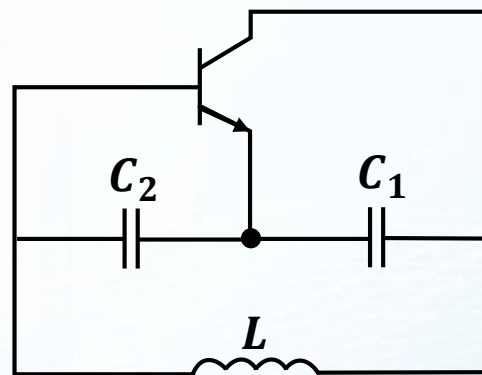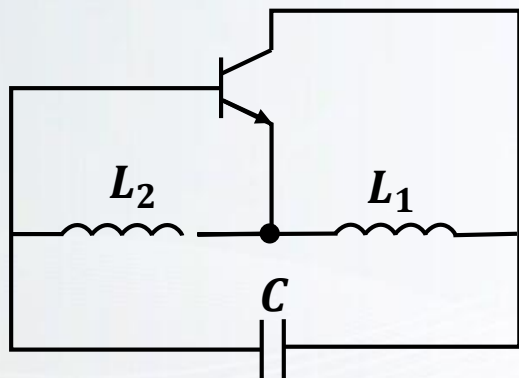
# Criteria of $LC$ Oscillator Composition

➤ General case?

- ①  $c - e$  and  $b - e$  are same
- ②  $b - c$  is different



# Criteria of $LC$ Oscillator Composition

- Suppose 3 reactance

$$Z_1 = jX_{ce} \quad Z_2 = jX_{be} \quad Z_3 = jX_{cb}$$

- Purely resistive when resonant


$$X_{be} + X_{ce} + X_{cb} = 0$$

- $AF = 1$ ,  $F = 1/A > 0$

- $F = X_{be}/X_{ce} > 0$ ,  $X_{be}$  and  $X_{ce}$  are the same type



- Thus:

- $X_{be}$  and  $X_{ce}$  are the same type (both inductive or both capacitive)
- They are different with  $X_{cb}$

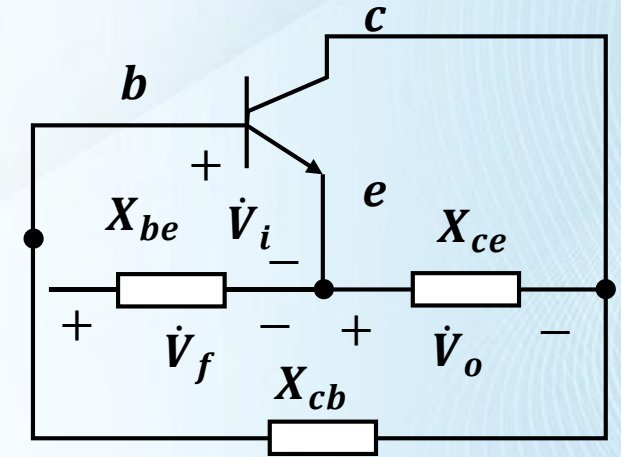



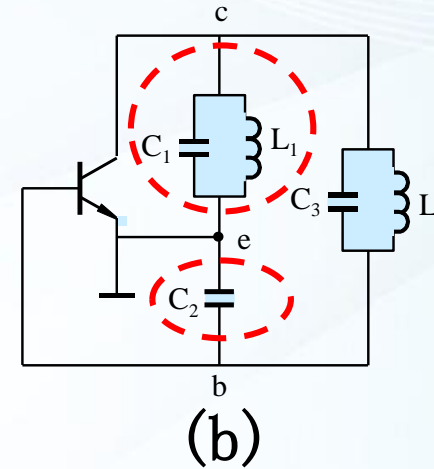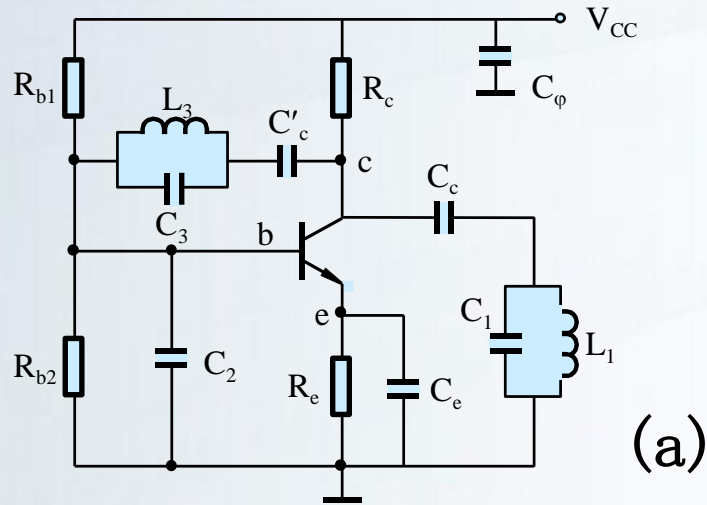**Exp 5-1 Draw AC equivalent circuit of the oscillator, determine when to start oscillation and classification.**



**Solution: 1) AC Equivalent circuit**

**2) Criteria of LC composition:**

$x_{be}$  Capacitive,  $x_{ce}$  Capacitive

$x_{cb}$  Inductive

- $L_1C_1$  Capacitive  $\rightarrow f_0 > f_1$  ( $L_1C_1$  natural frequency)
- $L_3C_3$  Inductive  $\rightarrow f_0 < f_3$
- **Classification: Capacitor Feedback LC Oscillator**

$$\frac{1}{2\pi\sqrt{L_1C_1}} < \frac{1}{2\pi\sqrt{L_3C_3}}$$

$$L_1C_1 > L_3C_3$$