

Basic Concepts

`jqhuang@mail.hust.edu.cn`

Outlines

- Resistor、 Inductor、 Capacitor: Lead vs. Lag
- Impedance vs. Admittance
- Quality Factor (Q) of Inductor
 - vs. Quality Factor (Q) of resonance circuit


1 Resistor

$$u = \sqrt{2} U \sin \omega t$$

$$i = \frac{u}{R} = \sqrt{2} \frac{U}{R} \sin \omega t = \sqrt{2} I \sin \omega t$$


$$U = IR$$

Vector relation

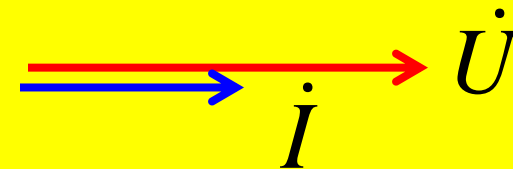

2 Inductor

$$u = L \frac{di}{dt}$$

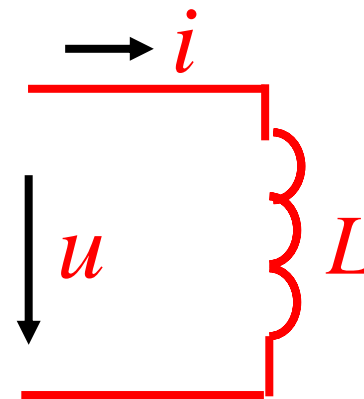

If $i = \sqrt{2} I \sin \omega t$

Then $u = L \frac{di}{dt} = \sqrt{2} I \cdot \omega L \cos \omega t$

$$= \sqrt{2} I \omega L \sin(\omega t + 90^\circ)$$

$$= \sqrt{2} U \sin(\omega t + 90^\circ)$$


2 Inductor Voltage leads Current

$$i = \sqrt{2}I \sin \omega t$$


$$\begin{aligned} u &= \sqrt{2} \underline{I \omega L} \sin(\omega t + 90^\circ) \\ &= \sqrt{2} \underline{U} \sin(\omega t + 90^\circ) \end{aligned}$$

1. Frequency is same

2. Phase diff 90° (u leads i 90°)

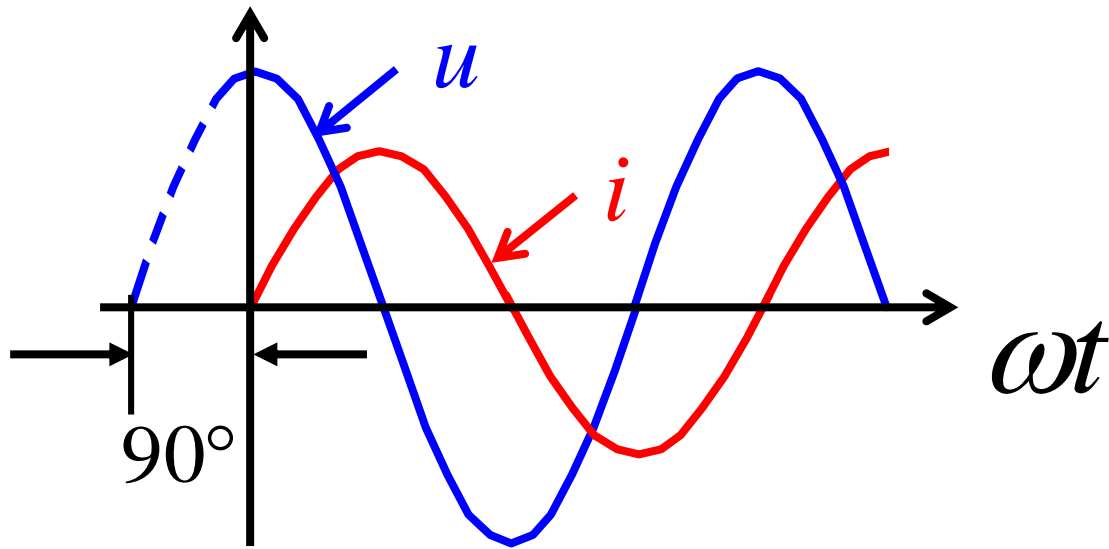

\dot{U} Lead!

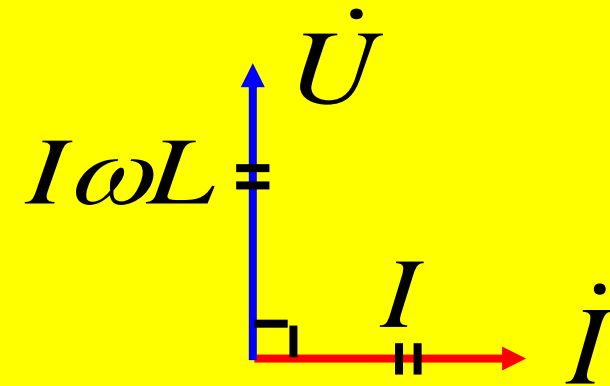

Inductance


$$\begin{aligned} u &= \sqrt{2} I \omega L \sin(\omega t + 90^\circ) \\ &= \sqrt{2} U \sin(\omega t + 90^\circ) \end{aligned}$$


Root-Mean-Square(RMS) $U = I \omega L$

Def:




$$X_L = \omega L$$

(Ω)

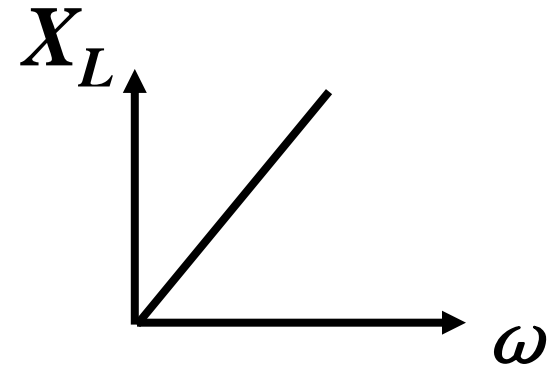

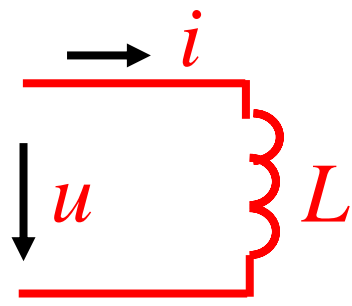

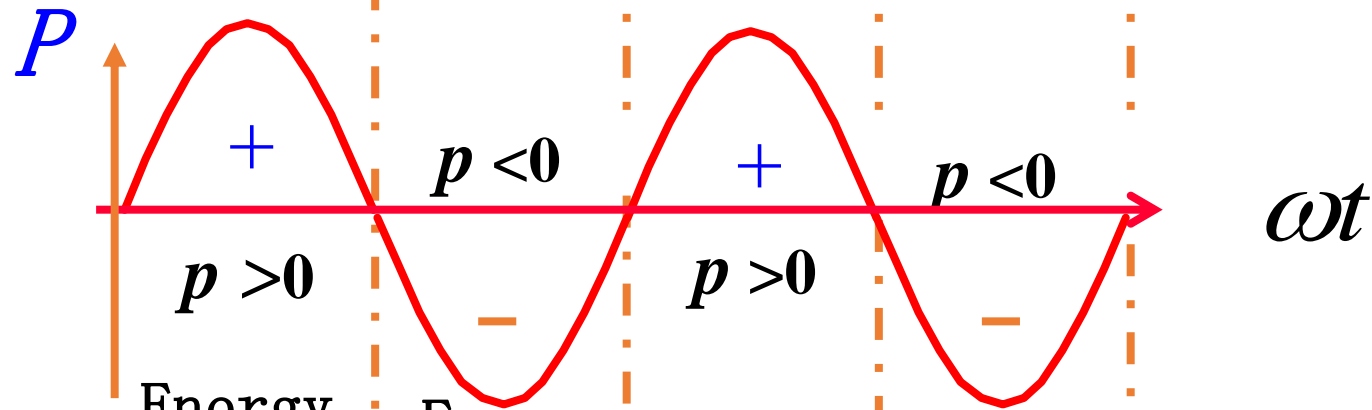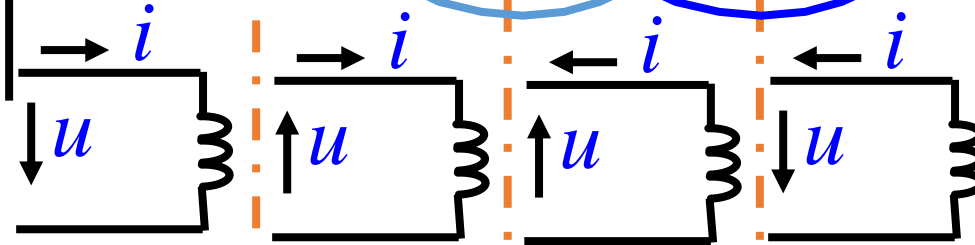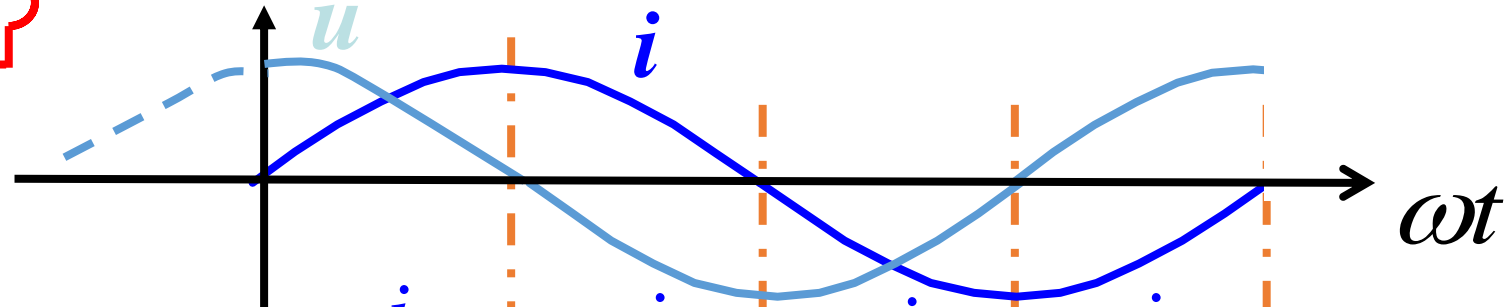
Power $p = i \cdot u = UI \sin 2\omega t$



Energy transforming

Energy Storage
Release

3 Capacitor

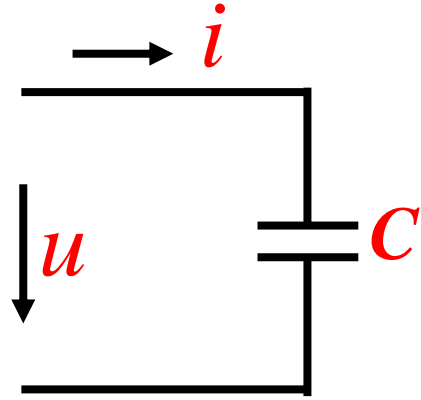

$$i = C \frac{du}{dt}$$

If $u = \sqrt{2}U \sin \omega t$

Then

$$\begin{aligned} i &= C \frac{du}{dt} = \sqrt{2}UC\omega \cos \omega t \\ &= \sqrt{2}U\omega C \cdot \sin(\omega t + 90^\circ) \end{aligned}$$


3 Capacitor Voltage lags Current

$$\begin{cases} u = \sqrt{2}U \sin \omega t \\ i = \sqrt{2}U \omega C \cdot \sin(\omega t + 90^\circ) \end{cases}$$


I

1. Frequency is same

2. Phase diff 90° (u lags i 90°)

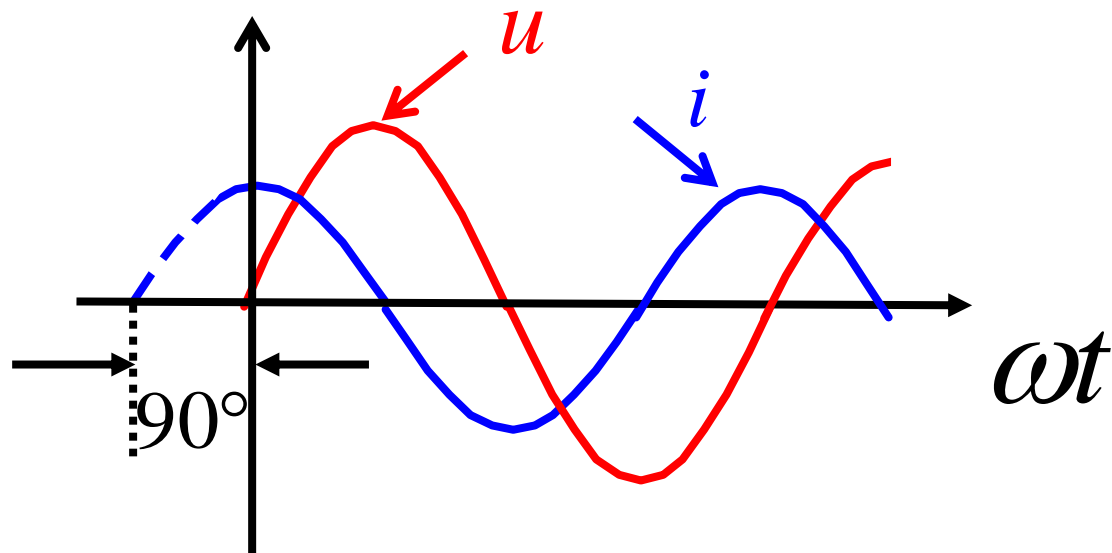

***i* leads !**

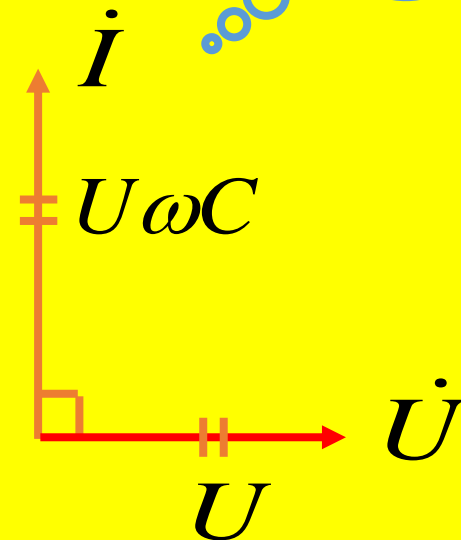

Captance


$$\begin{cases} u = \sqrt{2}U \sin \omega t \\ i = \sqrt{2} \underline{U \omega C} \cdot \sin(\omega t + 90^\circ) \end{cases}$$

I


Root-Mean-Square(RMS) $U = \frac{1}{\omega C} I$

Def:
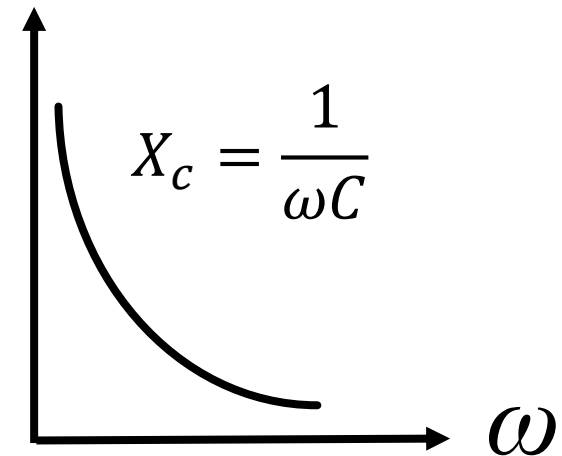
$$X_c = \frac{1}{\omega C} \quad (\Omega)$$




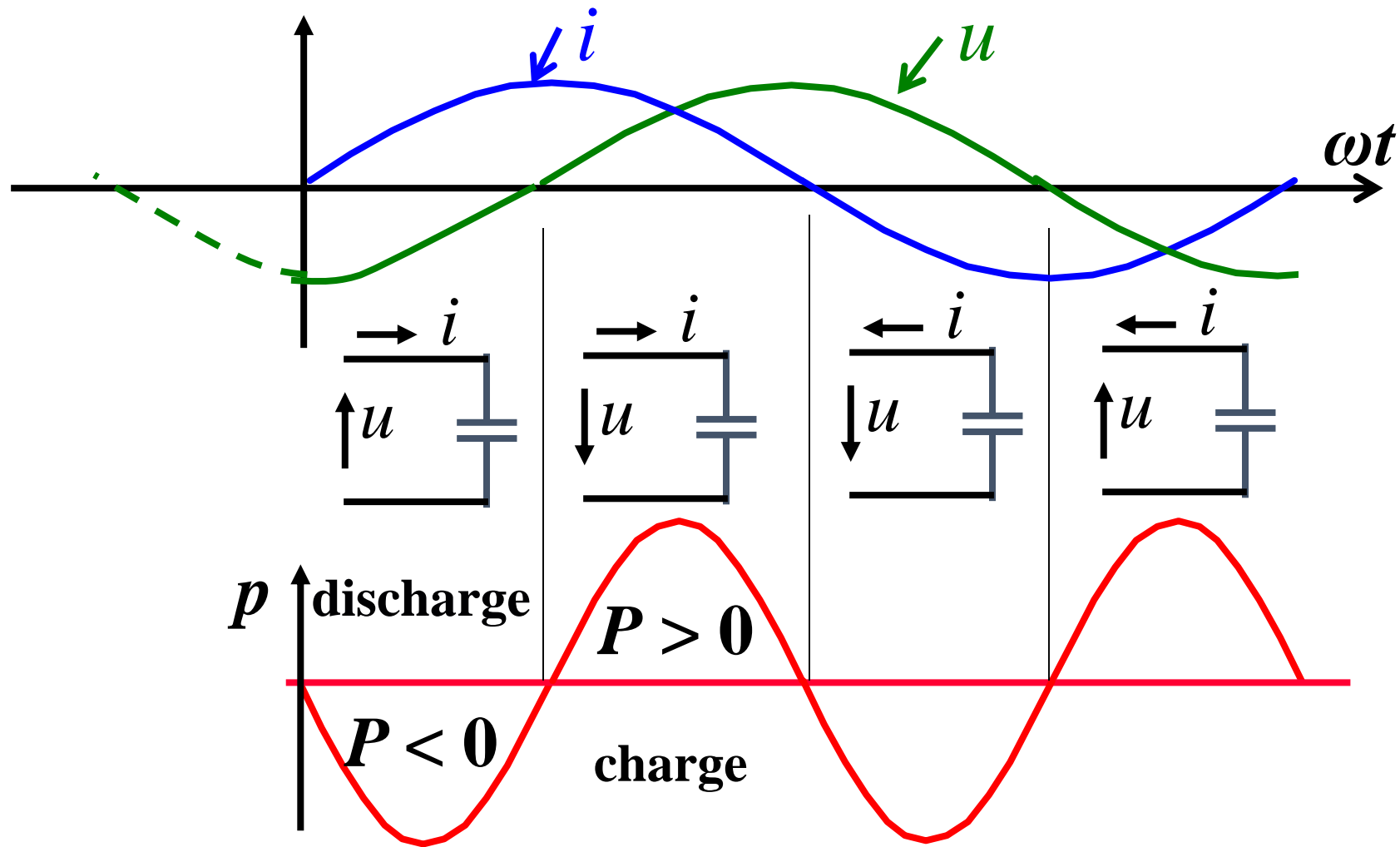Power $p = i \cdot u = -U I \sin 2\omega t$



Impedance vs. Admittance

Impedance vs. Admittance

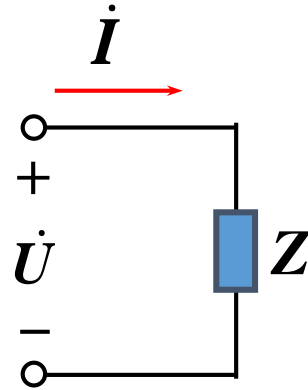


Impedance $Z = \frac{\dot{U}}{\dot{I}} = R + jX$

Unit: Ω

Resistance

Reactance

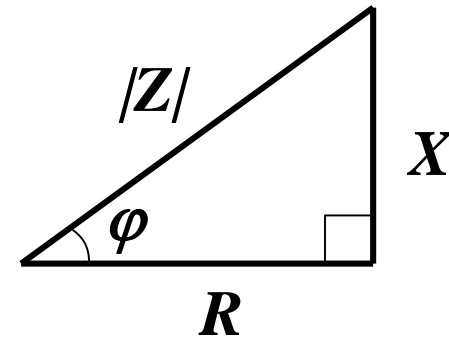

Impedance Triangle

Impedance vs. Admittance


Admittance

Unit: S

$$Y = \frac{\dot{I}}{\dot{U}} = G + jB$$

Conductance

Susceptance

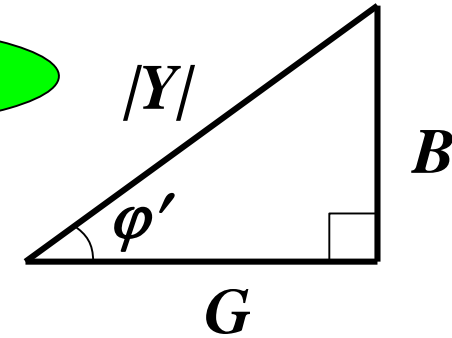

Admittance Triangle

$$Y = \frac{1}{Z}$$


Impedance

Unit: Ω

$$Z = \frac{\dot{U}}{\dot{I}} = R + jX$$

Resistance

Reactance

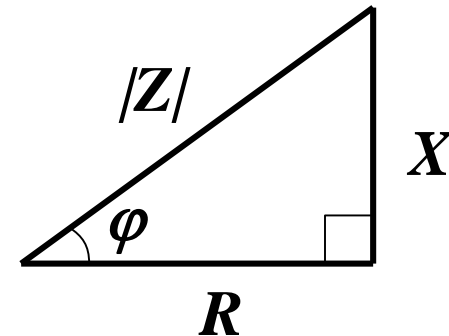

Impedance Triangle

Inductor Q vs. Resonator Q

Inductor Quality Factor (Q)

➤ Definition



$$Q = \frac{\omega L}{R}$$

Physical Significance

- Q reflects energy loss of inductor
- The bigger Q , the less loss, the higher efficiency
- Compared with resonator Q (see Chapter 2)

Q & A