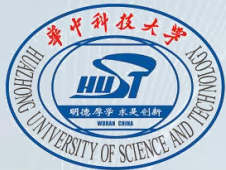


Huazhong University
of Science & Technology

Electronic Circuit of Communications

School of Electronic Information
and Communications

Jiaqing Huang




RF Power Amplifier

Radio Frequency Power Amplifier

➤ Objectives



- ① P_o ↑
- ② η_c ↑

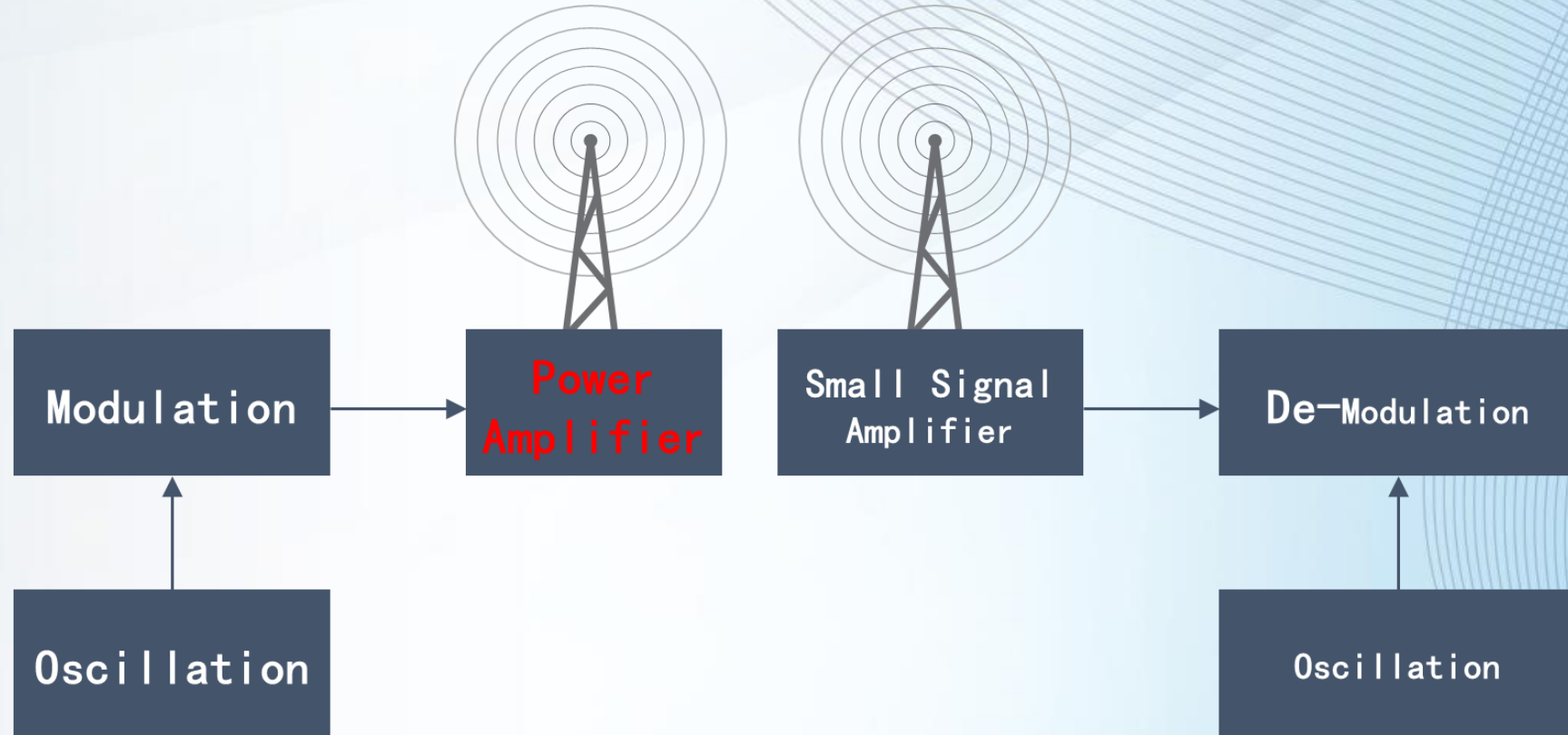

➤ Comparison

- ◆ RF Power Amplifier *vs.* RF Small Signal Amplifier?
- ◆ RF Power Amplifier *vs.* Audio Power Amplifier?




RF Power Amplifier — Principle

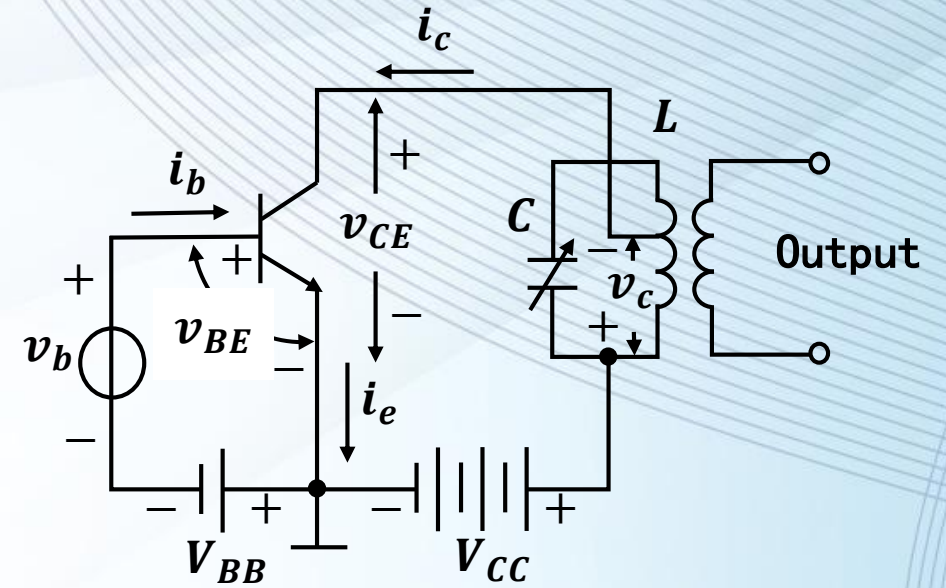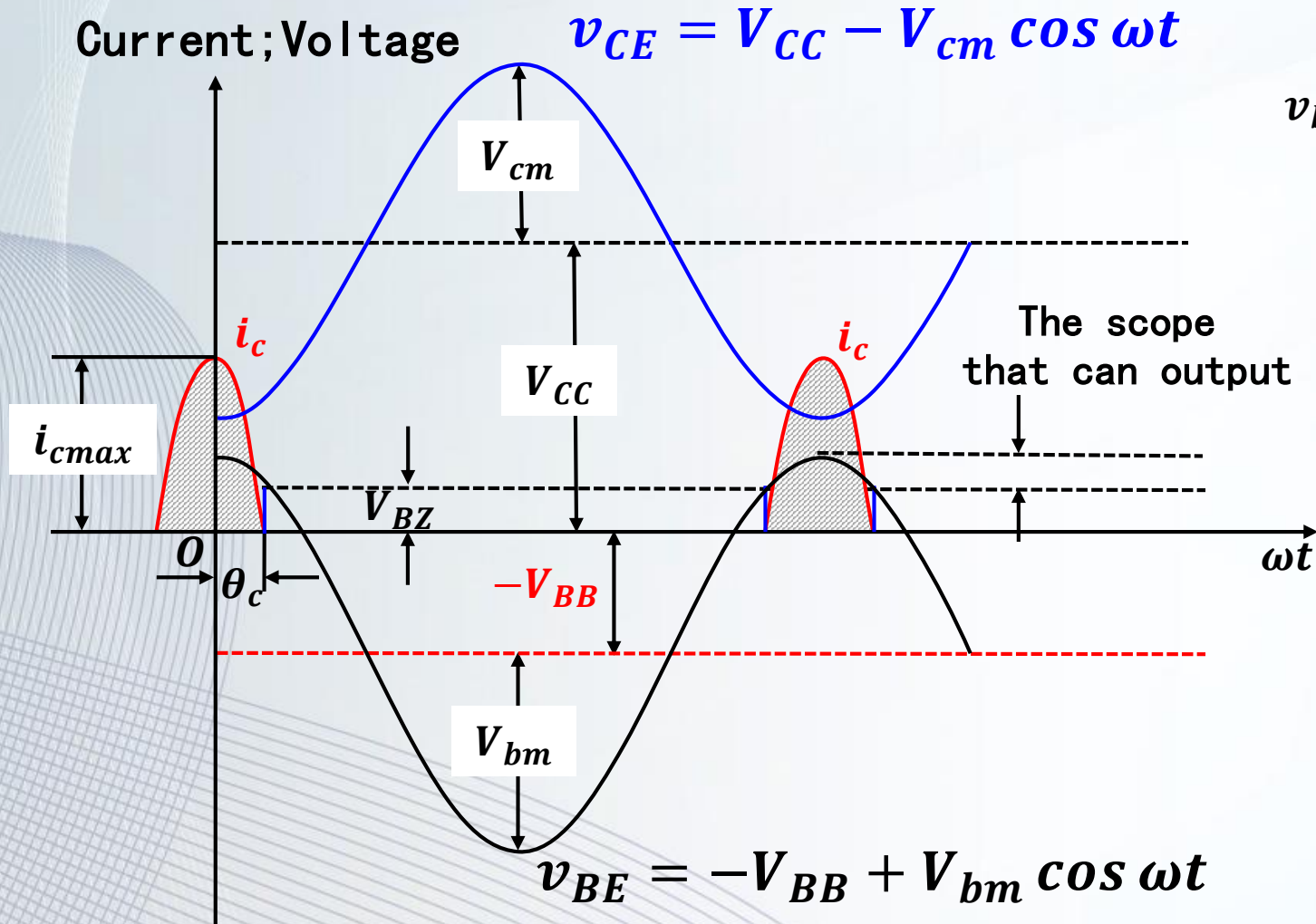

Key Concepts

- **Reversely Biased**
- $\theta_c < 90^\circ$ (**Class C**)
- **Cosine Pulses** i_c
- **Nonlinear** + Linear

RF Power Amplifier — Time & Frequency

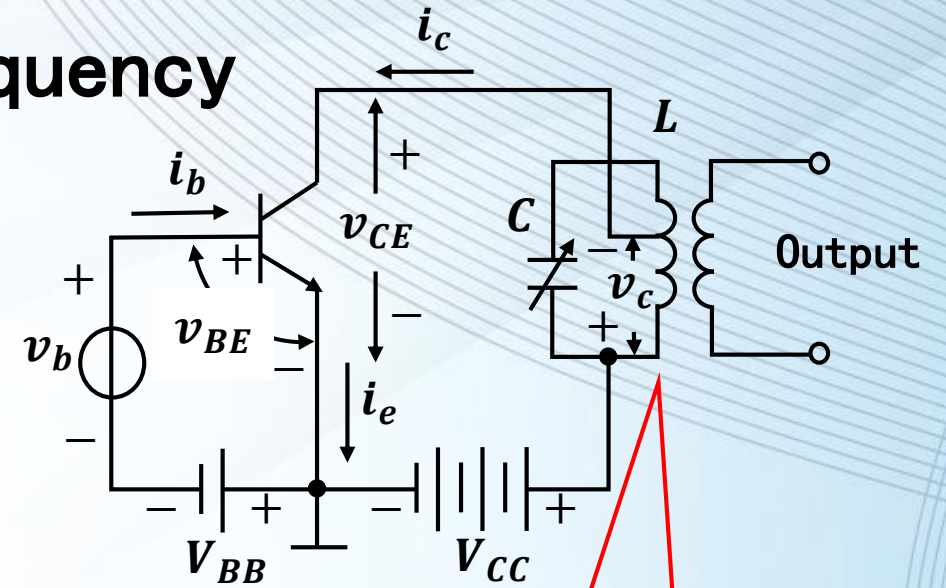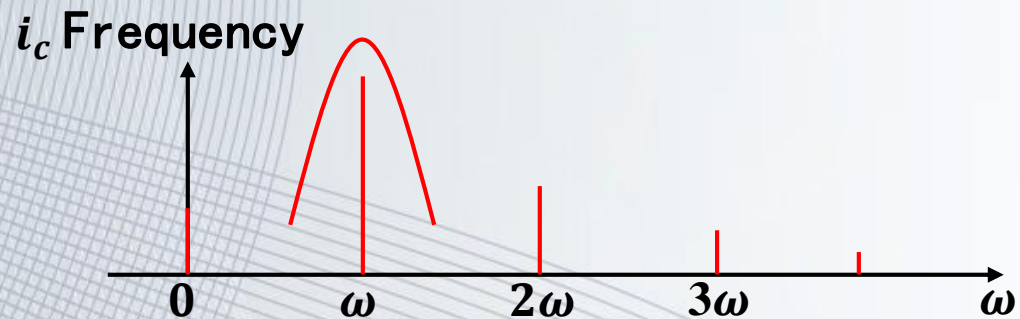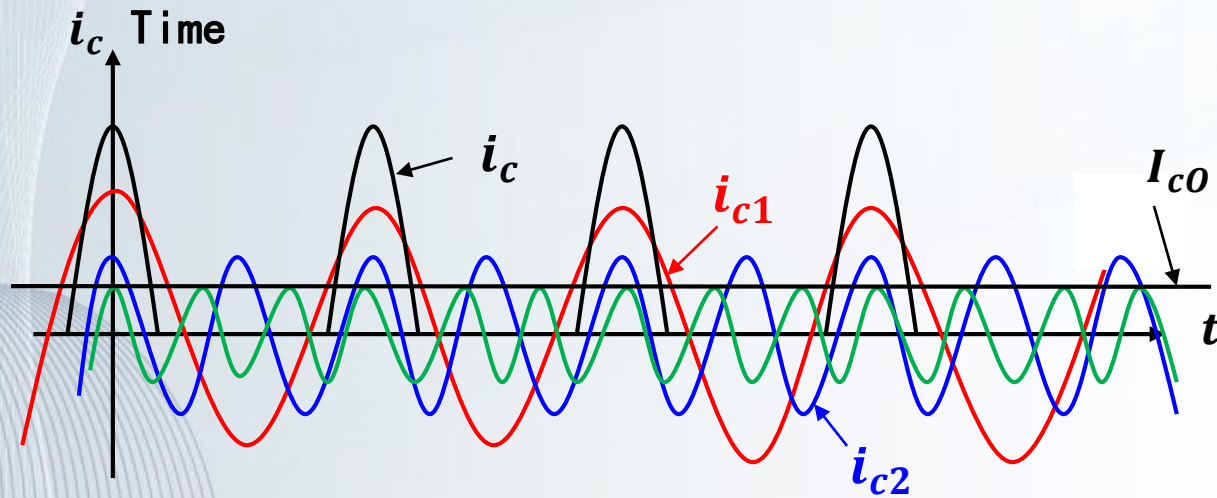

$$\begin{aligned} v_c &= i_{c1} \cdot R_P \\ &= I_{cm1} \cos \omega t \cdot R_P \\ &= V_{cm} \cos \omega t \end{aligned}$$

RF Power Amplifier *vs.* RF Small Signal Amplifier


➤ Similarity

- ◆ Radio frequency
- ◆ Load is resonance


➤ Difference

- ◆ Amplitude of input
- ◆ Quiescent point of Transistor
- ◆ Dynamic range

Non-linear

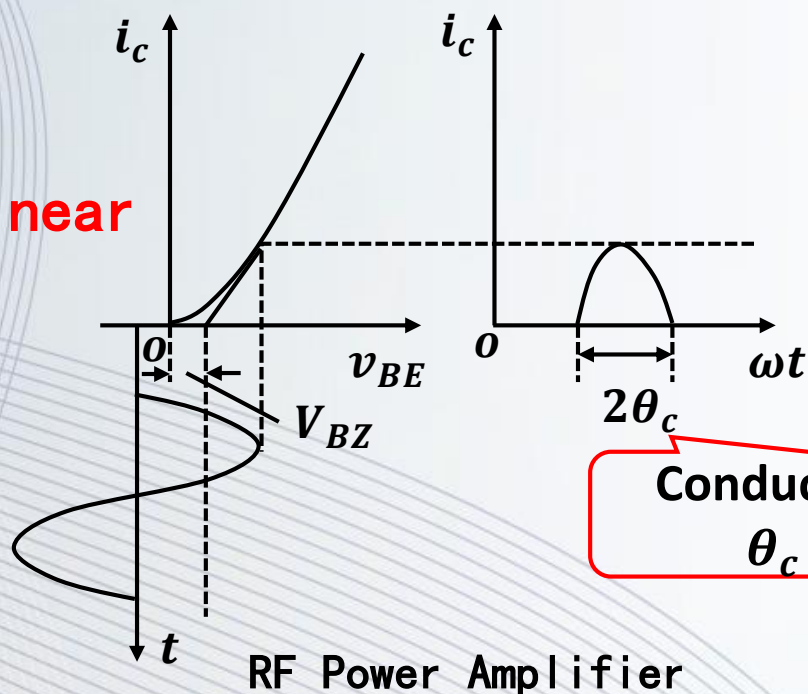

Linear

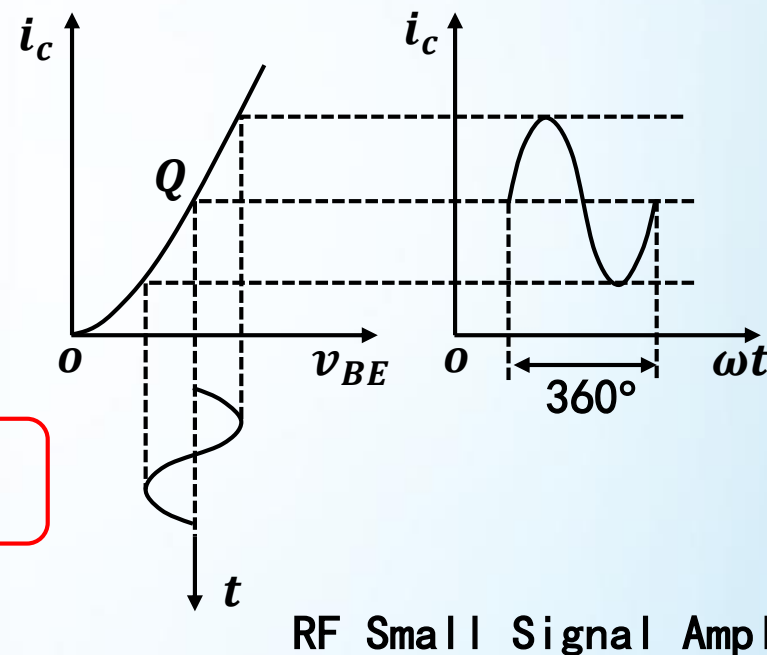


RF Power Amplifier *vs.* Audio Power Amplifier

➤ Similarity

- ◆ High Power
- ◆ High Efficiency

➤ Difference

	RF Power Amplifier	Audio Power Amplifier
Load	Parallel Resonance	Resistance
Status	Class C	Class A / B
Relative Bandwidth	Radio Narrowband	Audio Wideband

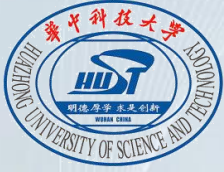

Output Power and Efficiency


RF Power Amplifier — Power & Efficiency

Power: $\boxed{\text{Output Power } P_o \uparrow} = \boxed{\text{DC Power } P_{DC}} - \boxed{\text{Collector Dissipation Power } P_c \downarrow}$


Efficiency: Collector $\eta_c \uparrow = \frac{P_o}{P_{DC}} = \frac{P_o}{P_o + P_c \downarrow}$

$$P_c = \frac{1}{T} \int_0^T i_c \cdot v_{CE} dt$$

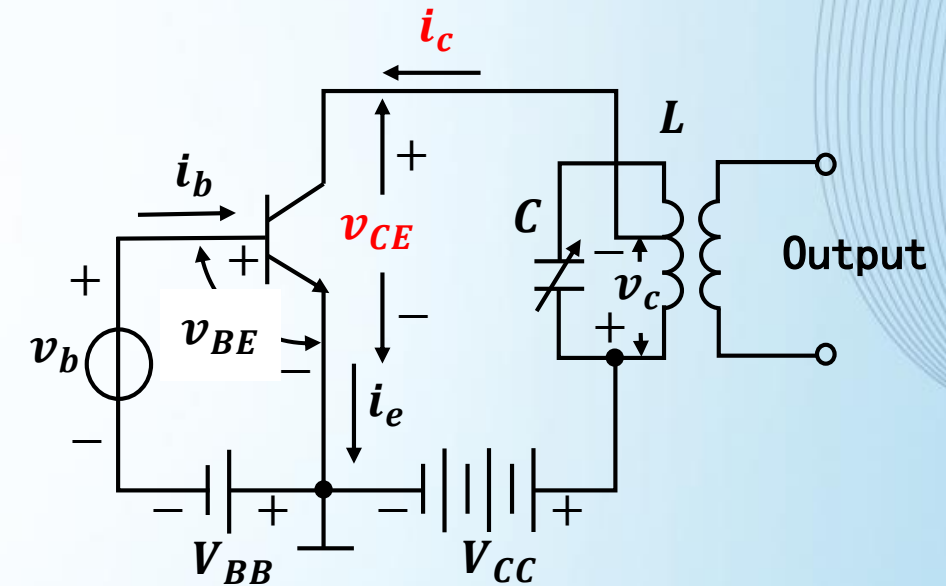➤ $P_c \downarrow$ $P_o \uparrow$ $\eta_c \uparrow$
How to decrease P_c ?



RF Power Amplifier — Decrease P_c

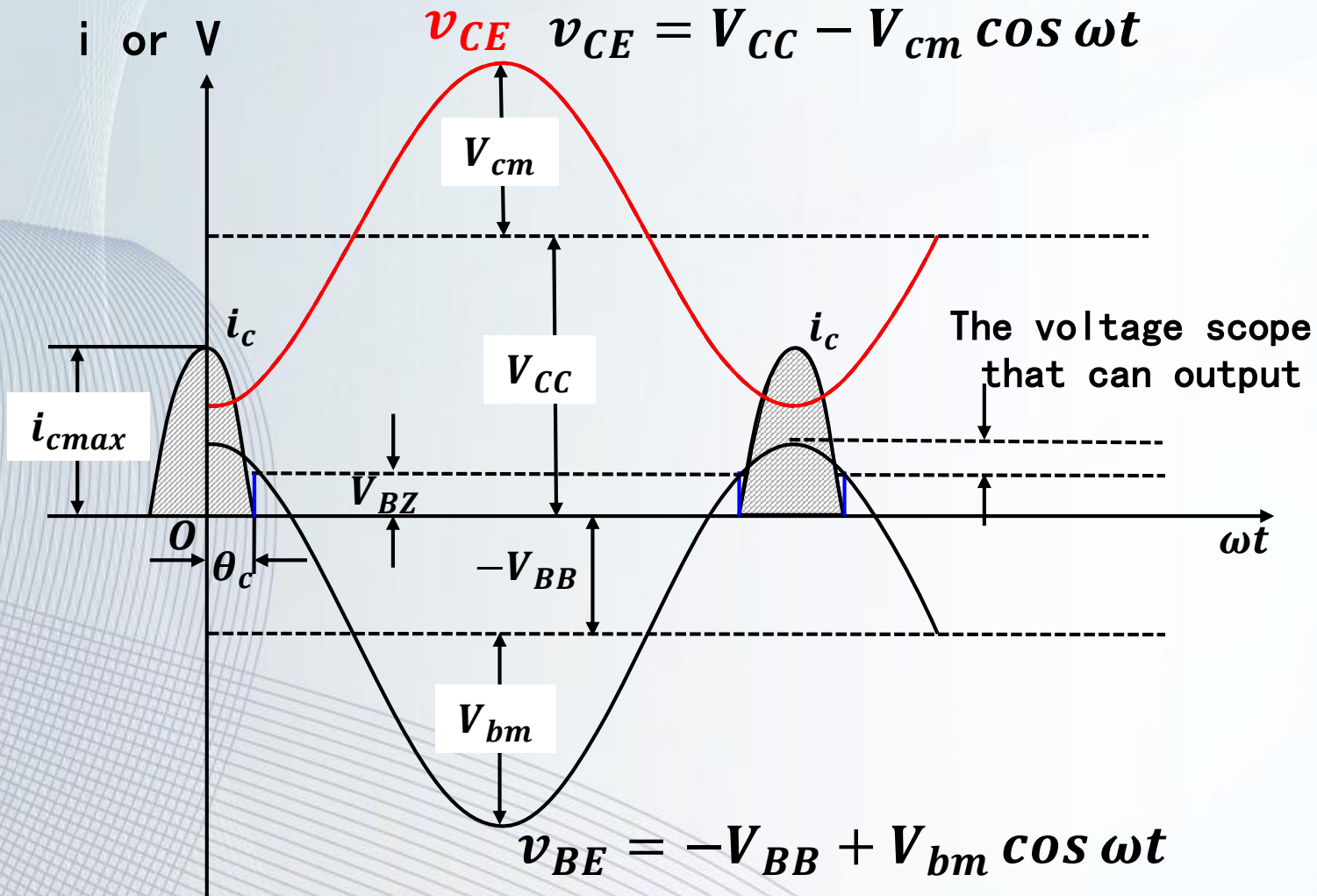

$$P_c = \frac{1}{T} \int_0^T i_c \cdot v_{CE} dt$$


How to decrease P_c :

➤ LC Resonant on ω

$$i_{cmax} \Leftrightarrow v_{CEmin}$$

➤ Decrease θ_c

RF Power Amplifier — Decrease P_c

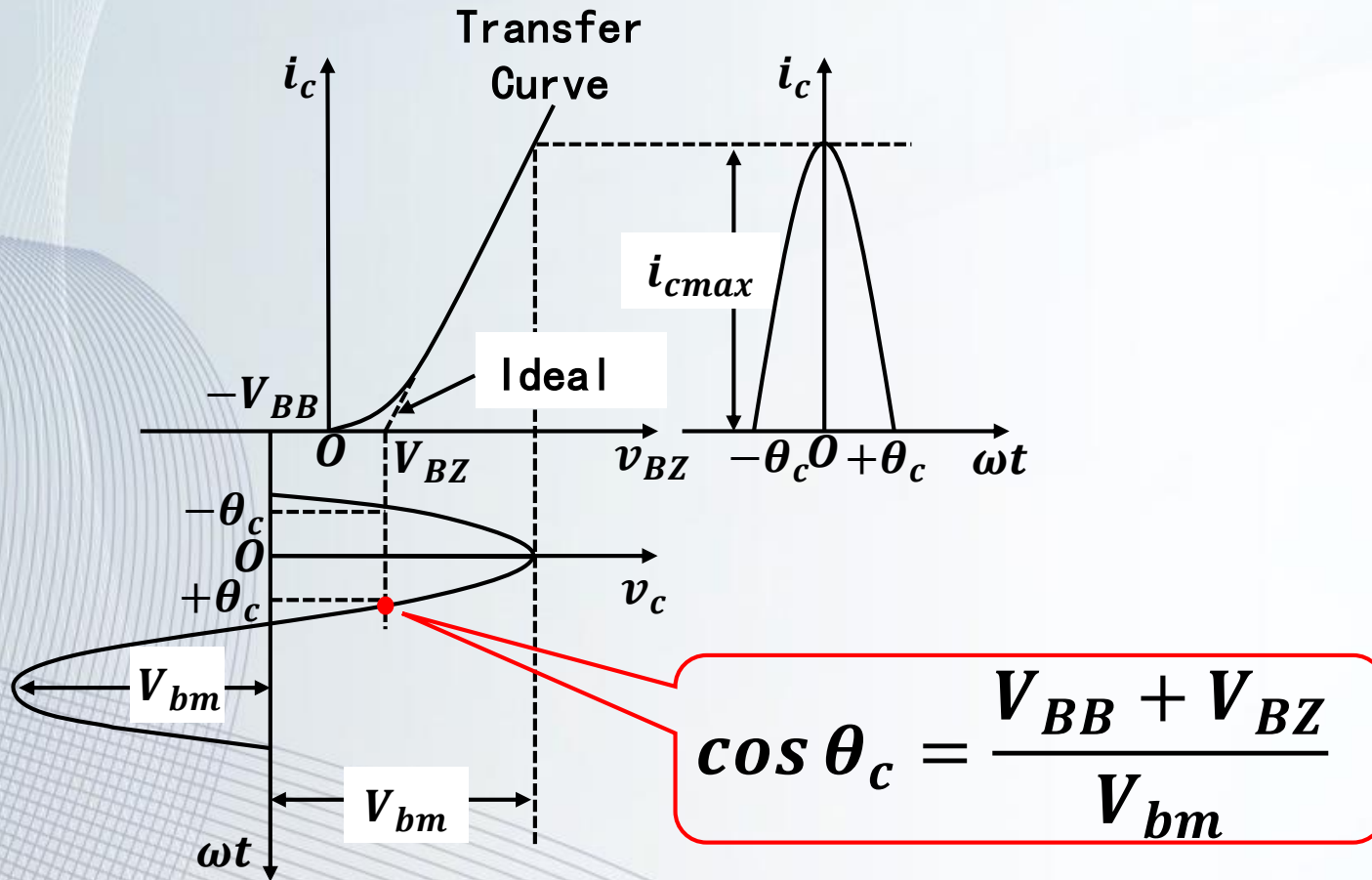

$$P_c = \frac{1}{T} \int_0^T i_c \cdot v_{CE} dt$$

How to decrease P_c :

➤ *LC* Resonant on ω

$$i_{cmax} \Leftrightarrow v_{CEmin}$$

➤ Decrease θ_c

RF Power Amplifier—Detailed Definition

$$i_c = I_{c0} + I_{cm1} \cos \omega t + I_{cm2} \cos 2\omega t + \dots + I_{cmn} \cos n\omega t + \dots$$

Output Power $P_o = \frac{1}{2} V_{cm} \cdot I_{cm1} = \frac{1}{2} \frac{V_{cm}^2}{R_p} = \frac{1}{2} I_{cm1}^2 R_p$



Parallel Resonant Resistance

Voltage Utilization Factor ξ

Collector Efficiency $\eta_c = \frac{P_o}{P_{dc}} = \frac{\frac{1}{2} V_{cm} \cdot I_{cm1}}{V_{CC} \cdot I_{c0}} = \frac{1}{2} \xi g_1(\theta_c)$


DC Power $P_{dc} = V_{CC} \cdot I_{c0}$


Utilization Factor $g_1(\theta_c)$

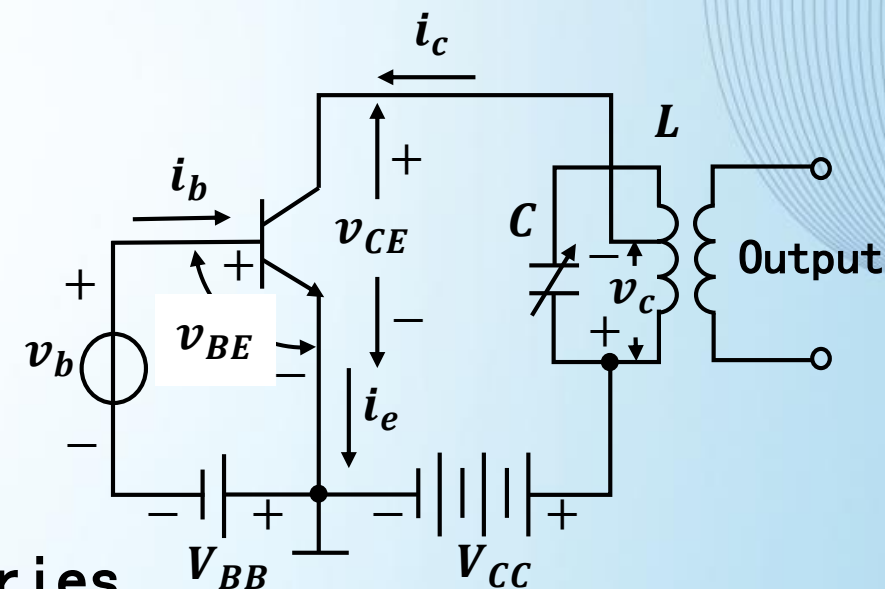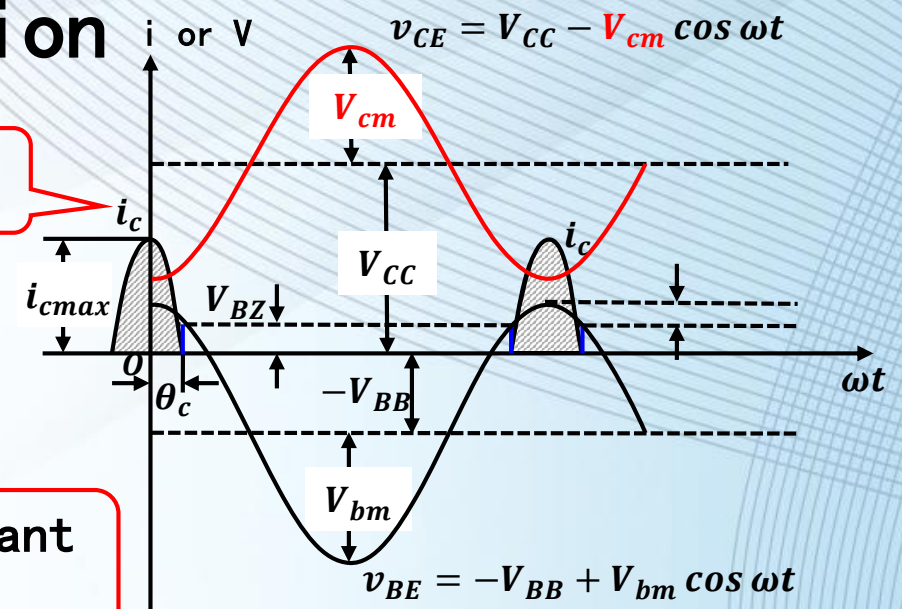

☆ Compute I_{cm1} & $I_{c0} \Leftarrow$ Analyze i_c by Fourier Series


Summary—Output Power & Efficiency

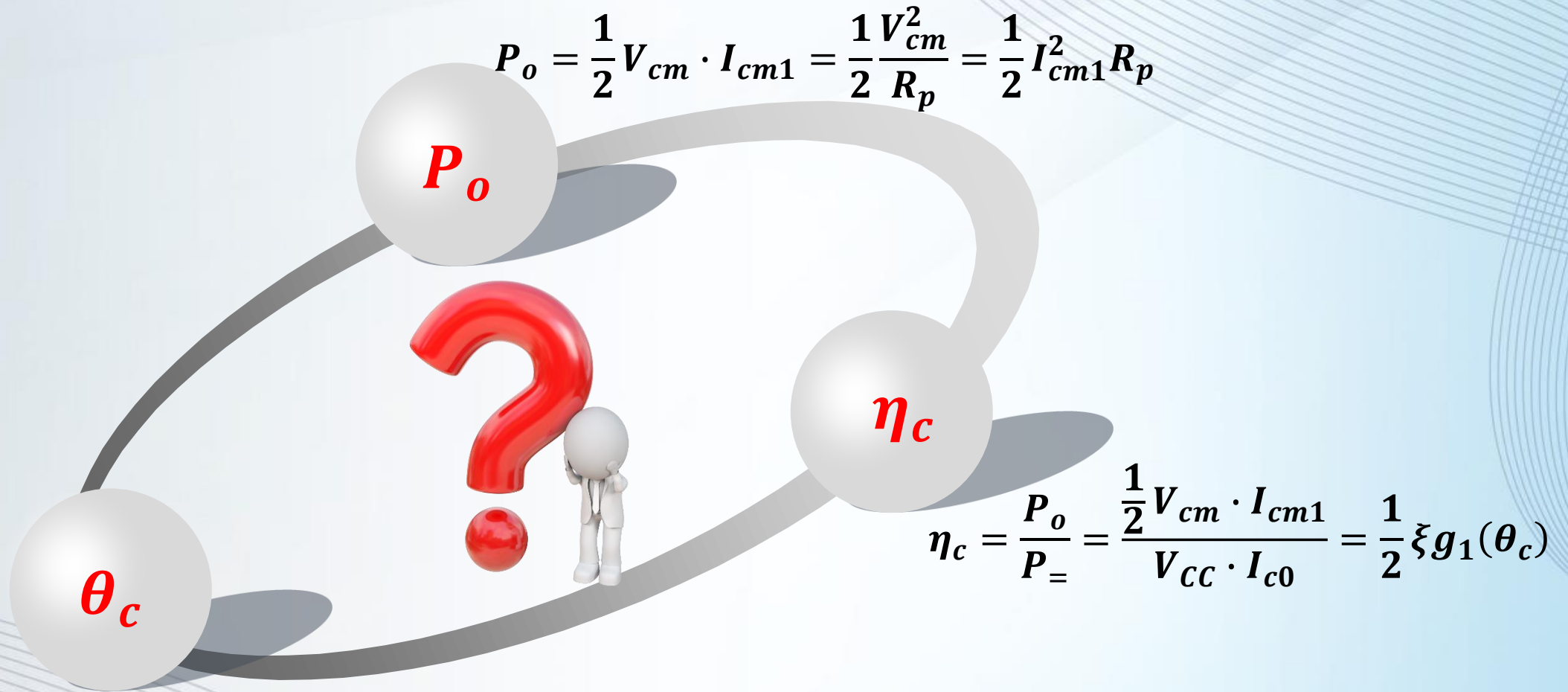

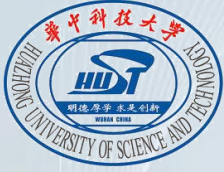

RF Power Amplifier Computation

RF Power Amplifier — Clue

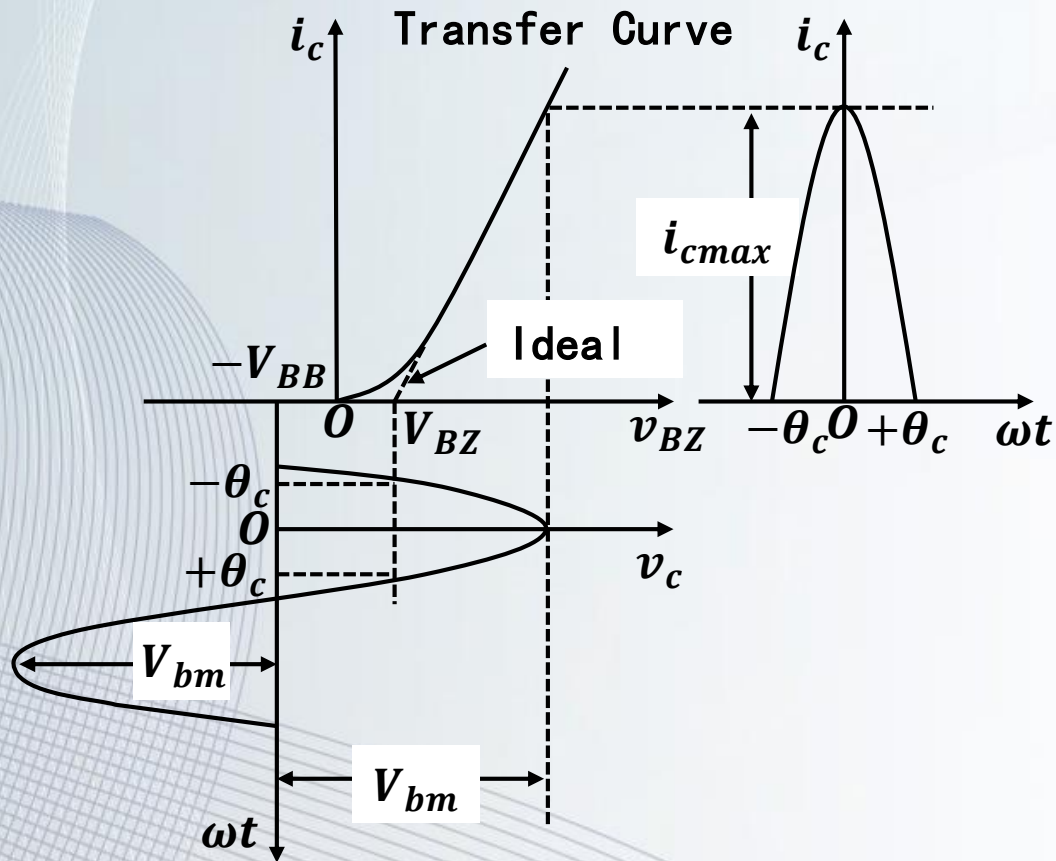

$$\begin{cases} P_o = \frac{1}{2} V_{cm} \cdot I_{cm1} = \frac{V_{cm}^2}{2R_p} = \frac{1}{2} I_{cm1}^2 R_p \\ \eta_c = \frac{P_o}{P_{cc}} = \frac{\frac{1}{2} V_{cm} \cdot I_{cm1}}{V_{cc} \cdot I_{c0}} = \frac{1}{2} \xi g_1(\theta_c) \end{cases}$$

➤ Key: compute I_{c0} & I_{cm1}

⇐ Analyze Cosine Pulse i_c

➤ $i_c = ?$ ($\theta_c = ?$ $i_{cmax} = ?$)


➤ By Fourier Series

⇐ Piecewise Linear Approximation


(Transfer Curve, Output Curve)

RF Power Amplifier — Piecewise Linear Approximation

Transfer Curve

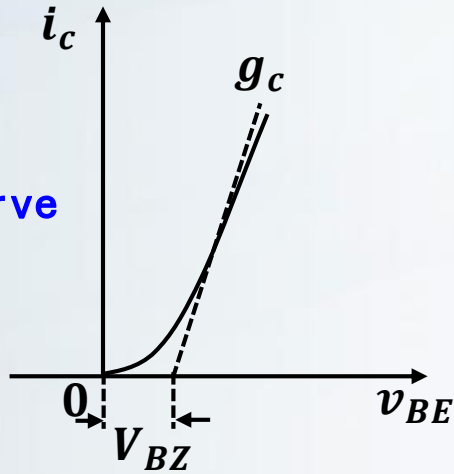

Output Curve

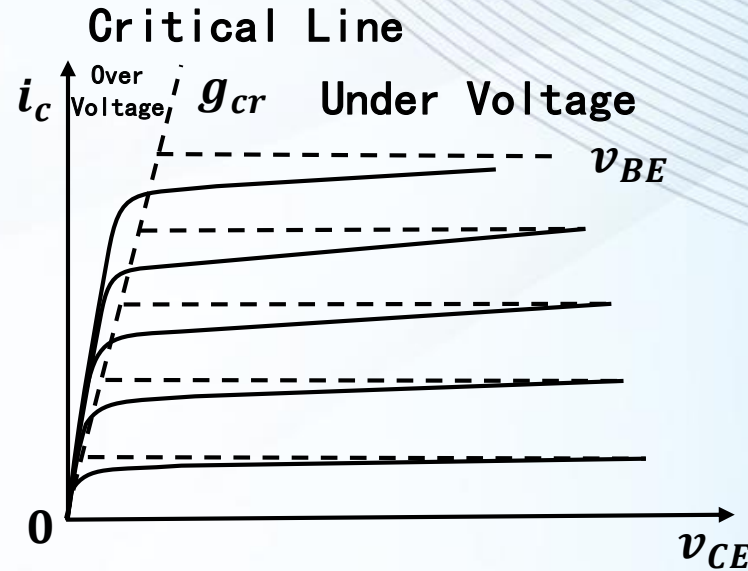

Trans-conductance

$$i_c = g_c(v_{BE} - V_{BZ}) \quad (v_{BE} > V_{BZ}) \quad (1)$$

Critical Line Equation:

$$i_c = g_{cr} v_{CE} \quad (2)$$

Critical Line Gradient

Periodic Cosine Pulses

$$\left\{ \begin{array}{l} \text{Transfer Equation: } i_c = g_c(v_{BE} - V_{BZ}) \end{array} \right. \quad (1)$$

$$\left\{ \begin{array}{l} \text{Base Equation : } v_{BE} = -V_{BB} + V_{bm} \cos \omega t \end{array} \right. \quad (3)$$


Substitute (3) into (1),

$$i_c = g_c(-V_{BB} + V_{bm} \cos \omega t - V_{BZ}) \quad (4)$$


If $\omega t = \theta_c$, $i_c = 0$, Substitute into (4),

$$0 = g_c(-V_{BB} + V_{bm} \cos \theta_c - V_{BZ}) \quad (5)$$

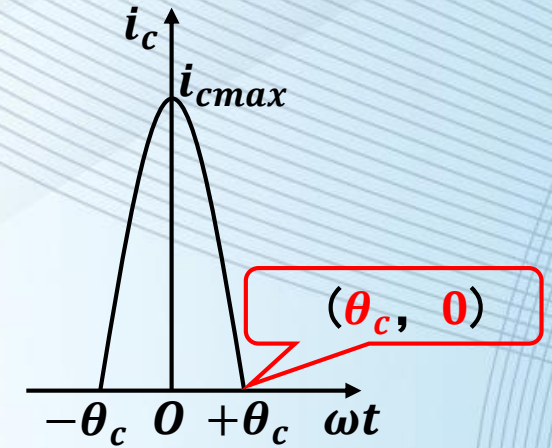Obtain $\cos \theta_c = \frac{V_{BB} + V_{BZ}}{V_{bm}}$


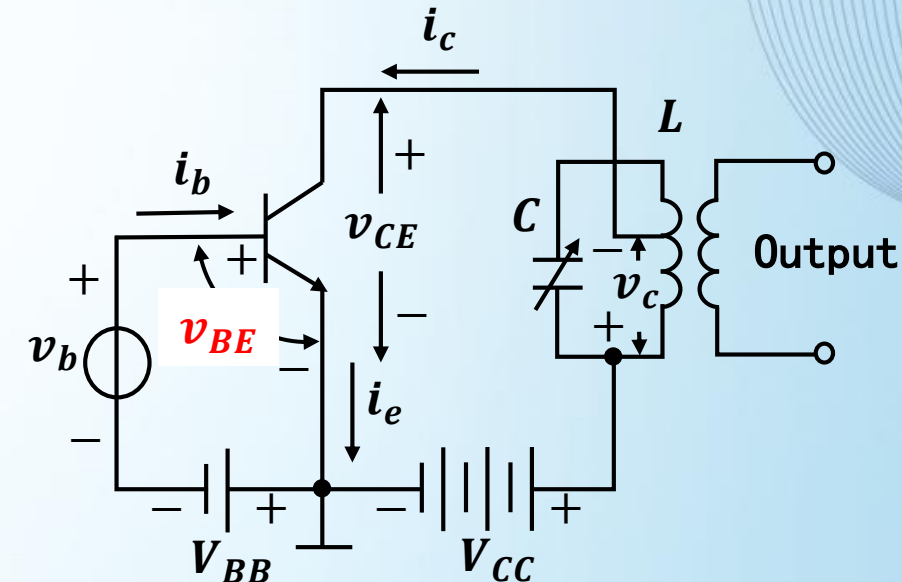
$$\cos \theta_c = \frac{V_{BB} + V_{BZ}}{V_{bm}}$$



Periodic Cosine Pulses

$$\begin{cases} i_c = g_c(-V_{BB} + V_{bm} \cos \omega t - V_{BZ}) \end{cases} \quad (4)$$

$$\begin{cases} 0 = g_c(-V_{BB} + V_{bm} \cos \theta_c - V_{BZ}) \end{cases} \quad (5)$$

(4) - (5), 得

$$i_c = g_c V_{bm} (\cos \omega t - \cos \theta_c) \quad (6)$$

If $\omega t = 0$, $i_c = i_{cmax}$, Substitute into (6)


$$i_{cmax} = g_c V_{bm} (1 - \cos \theta_c) \quad (7)$$

$$(6) \div (7), \quad i_c = i_{cmax} \left(\frac{\cos \omega t - \cos \theta_c}{1 - \cos \theta_c} \right)$$

Cosine Pulse Formula

$$i_c = i_{cmax} \left(\frac{\cos \omega t - \cos \theta_c}{1 - \cos \theta_c} \right)$$
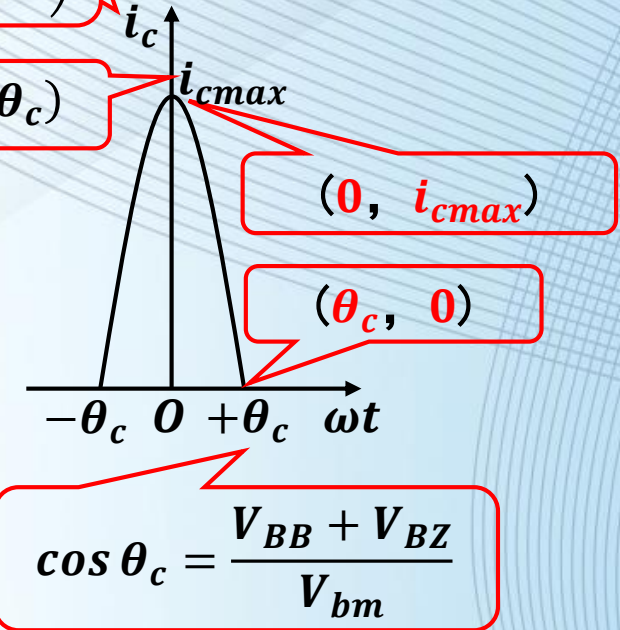
$$i_{cmax} = g_c V_{bm} (1 - \cos \theta_c)$$



Periodic Cosine Pulses-Decompose

$$i_c = i_{cmax} \left(\frac{\cos \omega t - \cos \theta_c}{1 - \cos \theta_c} \right)$$

$$i_{cmax} = g_c V_{bm} (1 - \cos \theta_c)$$

➤ By Fourier Series

$$i_c = I_{c0} + I_{cm1} \cos \omega t + I_{cm2} \cos 2 \omega t + \dots + I_{cmn} \cos n \omega t + \dots$$

➤ Compute Coefficients

DC Power

$$I_{c0} = \frac{1}{2\pi} \int_{-\theta_c}^{+\theta_c} i_c d\omega t = i_{cmax} \cdot \alpha_0(\theta_c)$$

$$\alpha_0(\theta_c) = \frac{\sin \theta_c - \theta_c \cos \theta_c}{\pi(1 - \cos \theta_c)}$$

Output Power


$$I_{cm1} = \frac{1}{2\pi} \int_{-\theta_c}^{+\theta_c} i_c \cos \omega t d\omega t = i_{cmax} \cdot \alpha_1(\theta_c)$$

$$\alpha_1(\theta_c) = \frac{\theta_c - \cos \theta_c \sin \theta_c}{\pi(1 - \cos \theta_c)}$$


⋮

$$I_{cmn} = \frac{1}{2\pi} \int_{-\theta_c}^{+\theta_c} i_c \cos n \omega t d\omega t = i_{cmax} \cdot \alpha_n(\theta_c)$$
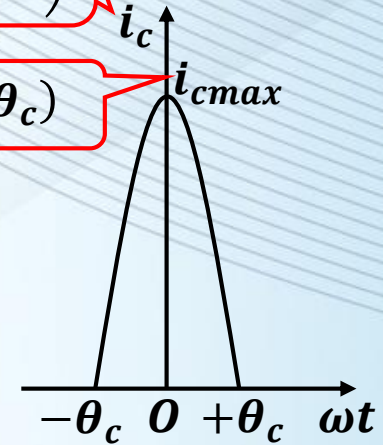
$$\alpha_n(\theta_c) = \frac{2}{\pi} \cdot \frac{\sin n \theta_c \cos \theta_c - n \cos n \theta_c \sin \theta_c}{n(n^2 - 1)(1 - \cos \theta_c)}$$


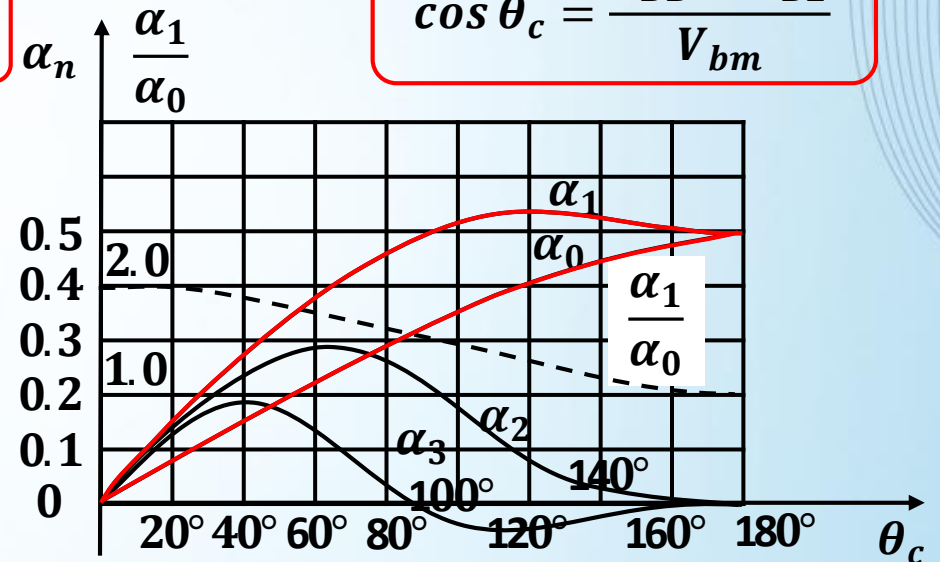
$$\cos \theta_c = \frac{V_{BB} + V_{BZ}}{V_{bm}}$$



Fourier Coefficients

Periodic Cosine Pulses—Decompose

➤ By Fourier Series

$$i_c = I_{c0} + I_{cm1} \cos \omega t + I_{cm2} \cos 2 \omega t + \cdots + I_{cmn} \cos n \omega t + \cdots$$

➤ Compute Coefficients


$$\begin{cases} I_{c0} = \frac{1}{2\pi} \int_{-\theta_c}^{+\theta_c} i_c d\omega t = i_{cmax} \cdot \alpha_0(\theta_c) \\ I_{cm1} = \frac{1}{2\pi} \int_{-\theta_c}^{+\theta_c} i_c \cos \omega t d\omega t = i_{cmax} \cdot \alpha_1(\theta_c) \end{cases}$$

$$\eta_c = \frac{P_o}{P_{cc}} = \frac{\frac{1}{2} V_{cm} \cdot I_{cm1}}{V_{cc} \cdot I_{c0}} = \frac{1}{2} \xi \cdot g_1(\theta_c)$$

$$g_1(\theta_c) = \frac{I_{cm1}}{I_{c0}} = \frac{\alpha_1(\theta_c)}{\alpha_0(\theta_c)}$$


$$i_c = i_{cmax} \left(\frac{\cos \omega t - \cos \theta_c}{1 - \cos \theta_c} \right)$$
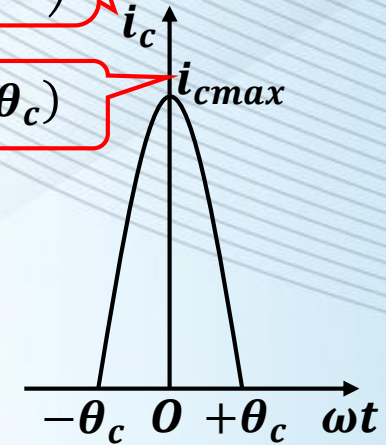
$$i_{cmax} = g_c V_{bm} (1 - \cos \theta_c)$$



Efficiency

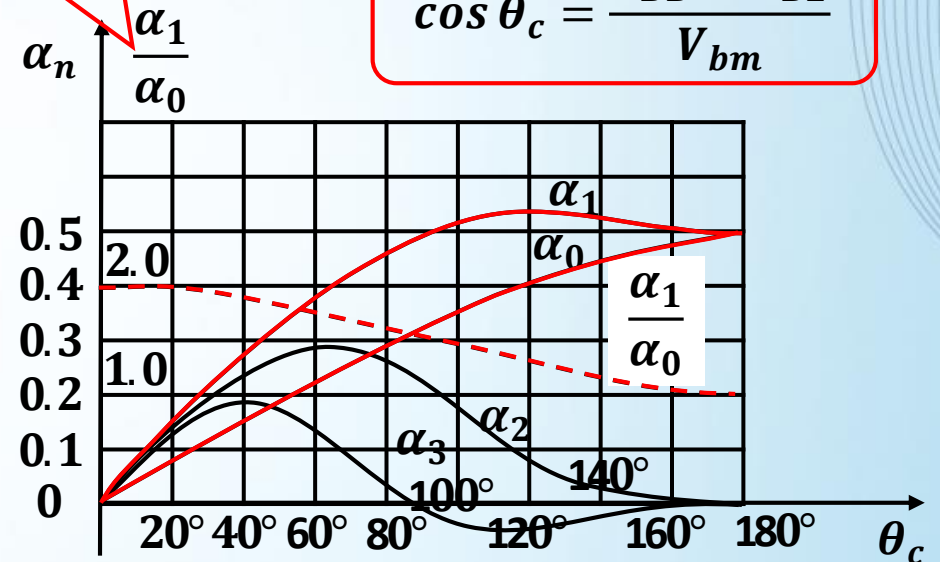
$$\cos \theta_c = \frac{V_{BB} + V_{BZ}}{V_{bm}}$$



Fourier Coefficients

➤ Tradeoff between Power & Efficiency, Optimal θ_c around 70°

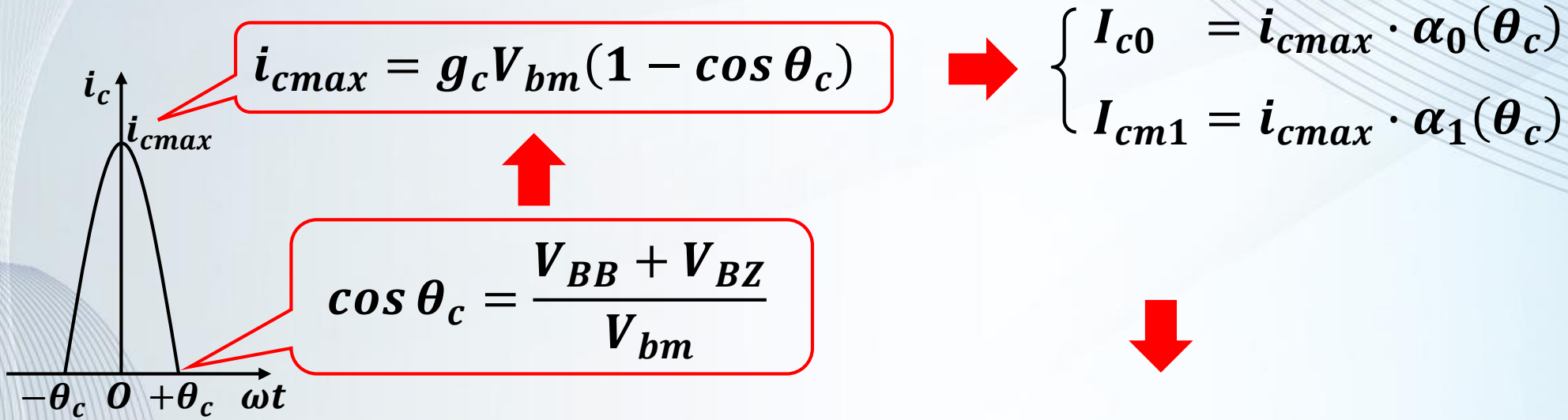Summary—Computation of RF Power Amplifier



$$\begin{cases} P_o = \frac{1}{2} V_{cm} \cdot I_{cm1} = \frac{1}{2} \frac{V_{cm}^2}{R_p} = \frac{1}{2} I_{cm1}^2 R_p \\ \eta_c = \frac{P_o}{P_{cc}} = \frac{\frac{1}{2} V_{cm} \cdot I_{cm1}}{V_{cc} \cdot I_{c0}} = \frac{1}{2} \xi \cdot g_1(\theta_c) \end{cases}$$

$$g_1(\theta_c) = \frac{\alpha_1(\theta_c)}{\alpha_0(\theta_c)}$$

Exp 4-1 The transfer characteristic of a RF power amplifier is as figure. The parameters of transistor are : $f_T \geq 150\text{MHz}$, $A_p \geq 13\text{dB}$, $I_{cmax} = 3\text{A}$, $P_{cmax} = 5\text{W}$. $V_{BZ} = 0.6\text{V}$, $V_{BB} = 1.4\text{V}$, $\theta_c = 70^\circ$, $V_{CC} = 24\text{V}$, $\xi = 0.9$. Compute all metrics.

$$\text{Figure} \Rightarrow g_c = \frac{1\text{A}}{(2.6-0.6)\text{V}} = 0.5\text{A/V}$$

$$\cos \theta_c = \frac{V_{BB}+V_{BZ}}{V_{bm}}, \Rightarrow V_{bm} = \frac{1.4+0.6}{\cos 70^\circ} = 5.8\text{V}$$

Solution: $\therefore i_{cmax} = g_c V_{bm}(1 - \cos \theta_c)$, Compute I_{cm1} , I_{c0}

$$i_{cmax} = \frac{1}{2} \times 5.8 \times (1 - \cos 70^\circ) = 2\text{A} < I_{cmax} \text{ (Safe)}$$

$$\Rightarrow \begin{cases} I_{cm1} = i_{cmax} \cdot \alpha_1(70^\circ) = 2 \times 0.436 = 0.872\text{A} \\ I_{c0} = i_{cmax} \cdot \alpha_0(70^\circ) = 2 \times 0.253 = 0.506\text{A} \end{cases}$$

$$\Rightarrow \begin{cases} P_o = \frac{1}{2} I_{cm1} \cdot V_{cm} = \frac{1}{2} I_{cm1} \cdot (\xi V_{CC}) = \frac{1}{2} \times 0.872 \times 0.9 \times 24 = 9.4\text{W} \\ P_{=} = V_{CC} \cdot I_{c0} = 24 \times 0.506 = 12\text{W} \Rightarrow P_c = P_{=} - P_o = 2.6\text{W} < P_{cmax} \text{ (Safe)} \end{cases}$$

$$\Rightarrow \eta_c = \frac{P_o}{P_{=}} = \frac{9.4}{12} = 78\%$$

