



Huazhong University of Science and Technology
The Department of Electronics and Information Engineering

Electronic Circuit Analysis and Design

Dr. Tianping Deng

Email: dengtp@hust.edu.cn

Contents

PART 1 SEMICONDUCTOR DEVICES AND BASIC APPLICATIONS

Chapter 1 Semiconductor Materials and Diodes

Chapter 2 Diode Circuits

Chapter 3 The Field-Effect Transistor

Chapter 4 Basic FET Amplifiers

Chapter 5 The Bipolar Junction Transistor

 **Chapter 6 Basic BJT Amplifiers**

Chapter 7 Frequency Response

Chapter 8 Output Stages and Power Amplifiers

PART 2 ANALOG ELECTRONICS

Chapter 9 Ideal Operational Amplifiers and Op-Amp Circuits

Chapter 10 Integrated Circuit Biasing and Active Loads

Chapter 11 Differential and Multistage Amplifiers

Chapter 12 Feedback and Stability

Chapter 13 Operational Amplifier Circuits

Chapter 14 Nonideal Effects in Operational Amplifier Circuits

Chapter 15 Applications and Design of Integrated Circuits

Ch6. Basic BJT Amplifiers

6.0 Preview

6.1 Analog Signals and Linear Amplifiers

6.2 The Bipolar Linear Amplifier

6.3 Basic Transistor Amplifier Configurations

6.4 Common-Emitter Amplifiers

6.5 AC Load Line Analysis

6.6 Common-Collector (Emitter-Follower) Amplifier

6.7 Common-Base Amplifier


6.8 The Three Basic Amplifiers: Summary and Comparison

6.9 Multistage Amplifiers

6.10 Power Considerations

6.11 Design Application



6.12 Summary

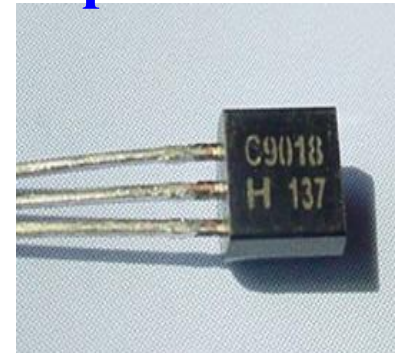

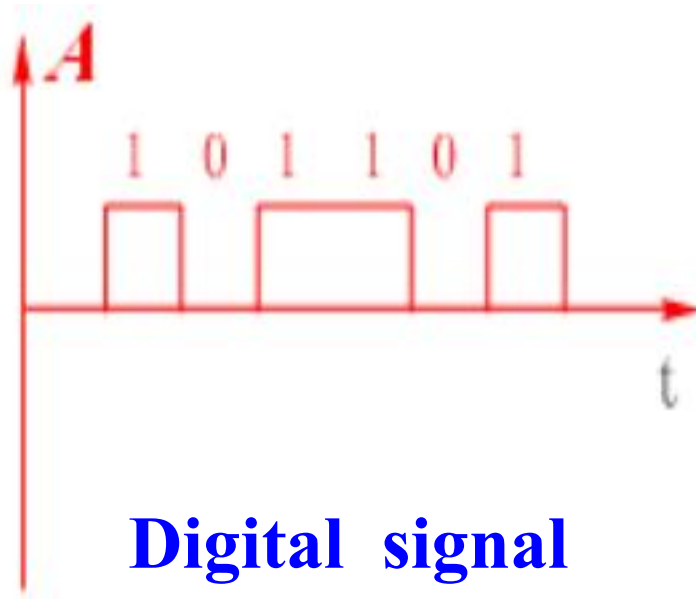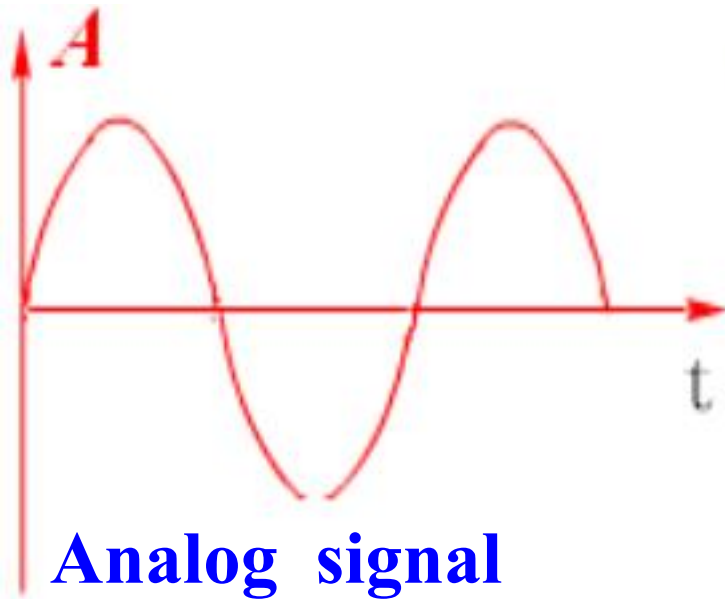6.1 Analog Signals and Linear Amplifiers

Signals

- A signal contains some type of information. There are two kinds of signals: analog and digital.



6.1 Analog Signals and Linear Amplifiers

Amplifiers



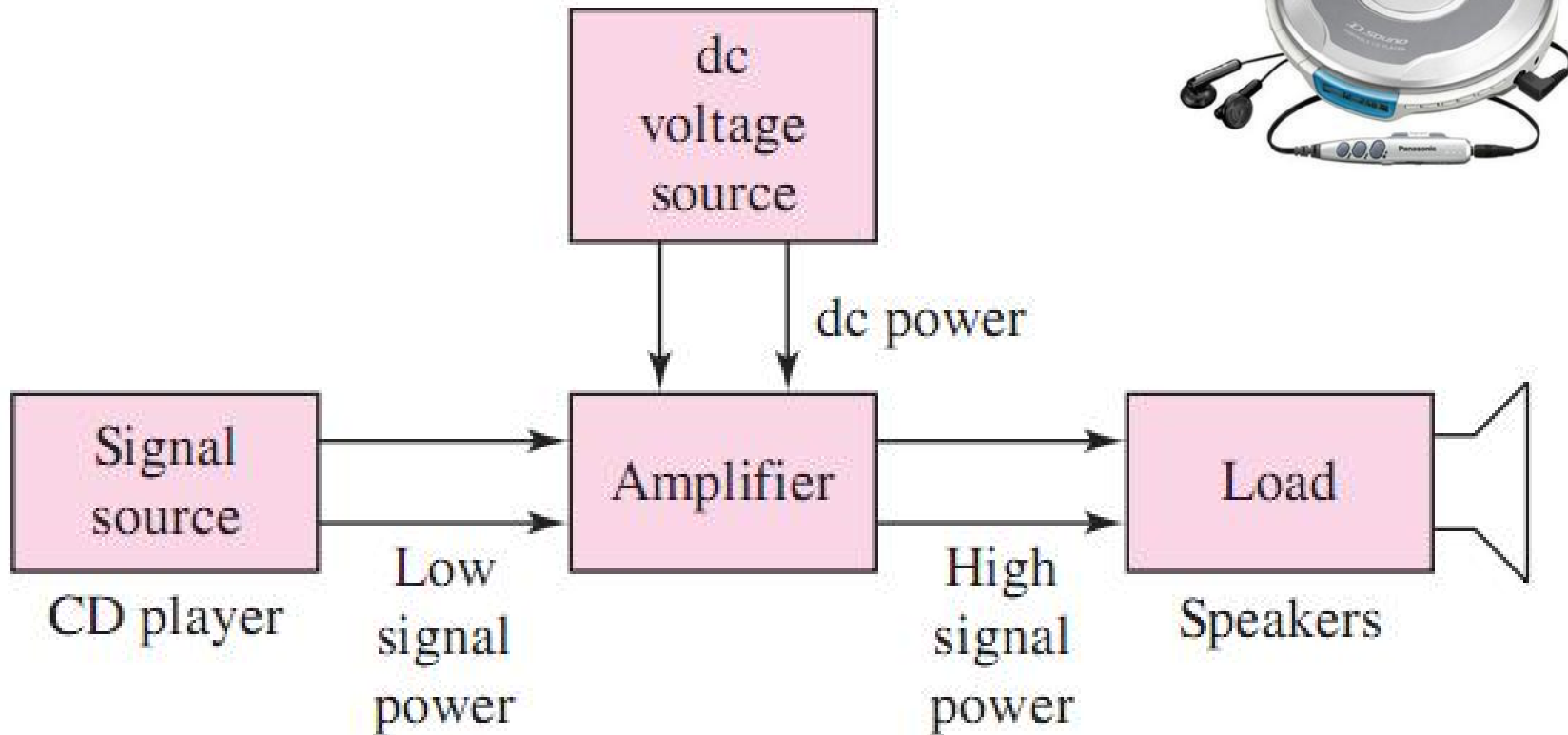


Figure 6.1 Block diagram of a compact disc player system


6.2 The Bipolar Linear Amplifier

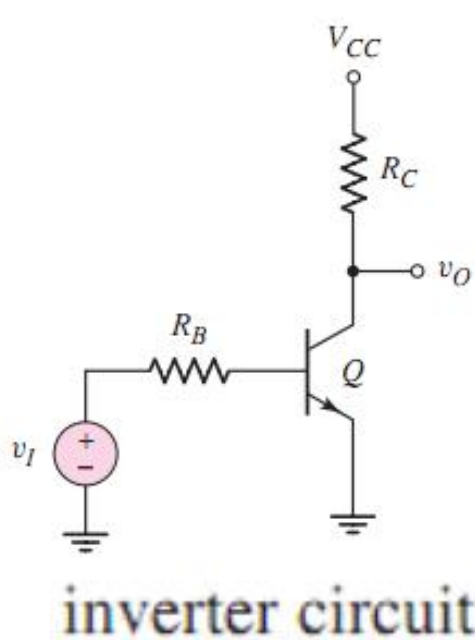

which region ?

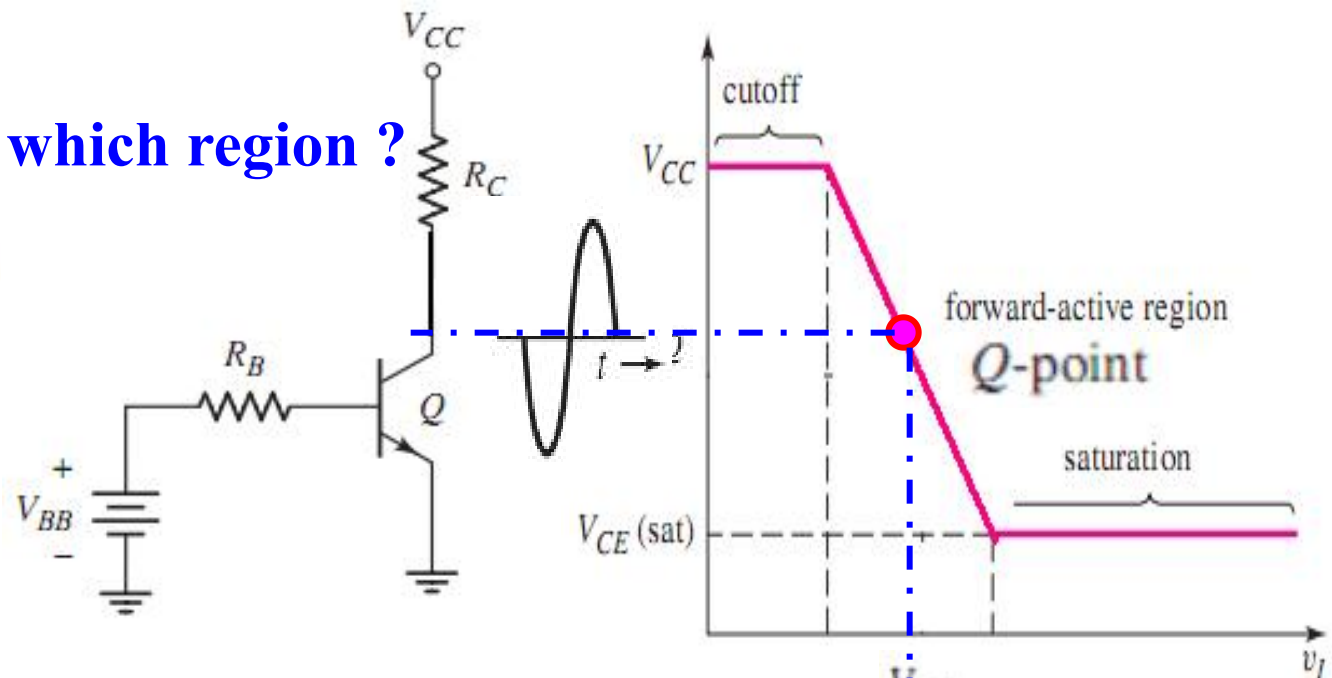


Forward active region

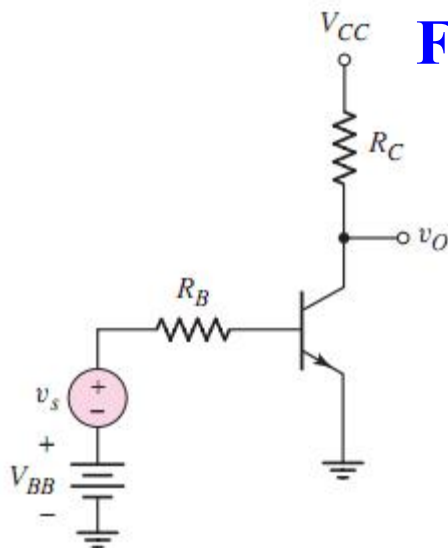


6.2 The Bipolar Linear Amplifier

Q-point

DC analysis

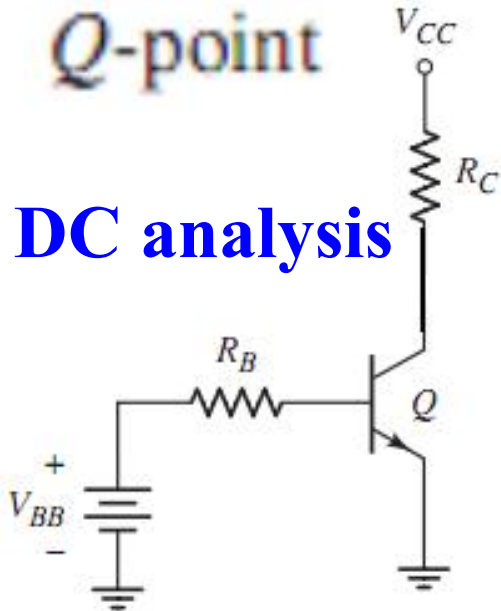

$$v_O = ?$$

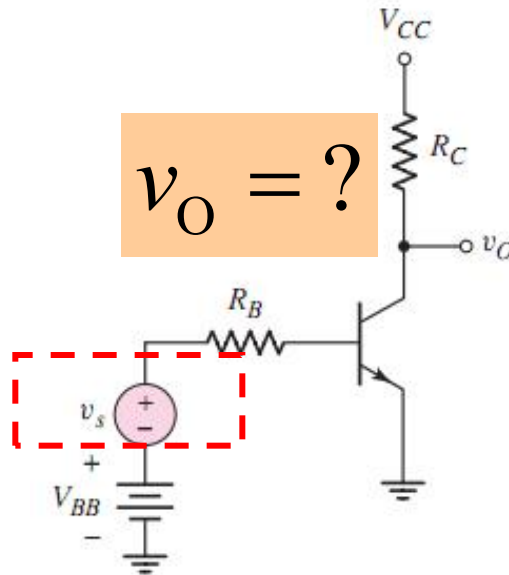

DC

AC

$$v_O = V_O + v_o$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$I_C = \beta I_B$$

$$V_{CE} = V_{CC} - I_C R_C$$

Table 6.1

Summary of notation

Variable

Meaning

i_B, v_{BE}

Total instantaneous values

I_B, V_{BE}

DC values


i_b, v_{be}

Instantaneous ac values


I_b, V_{be}

Phasor values

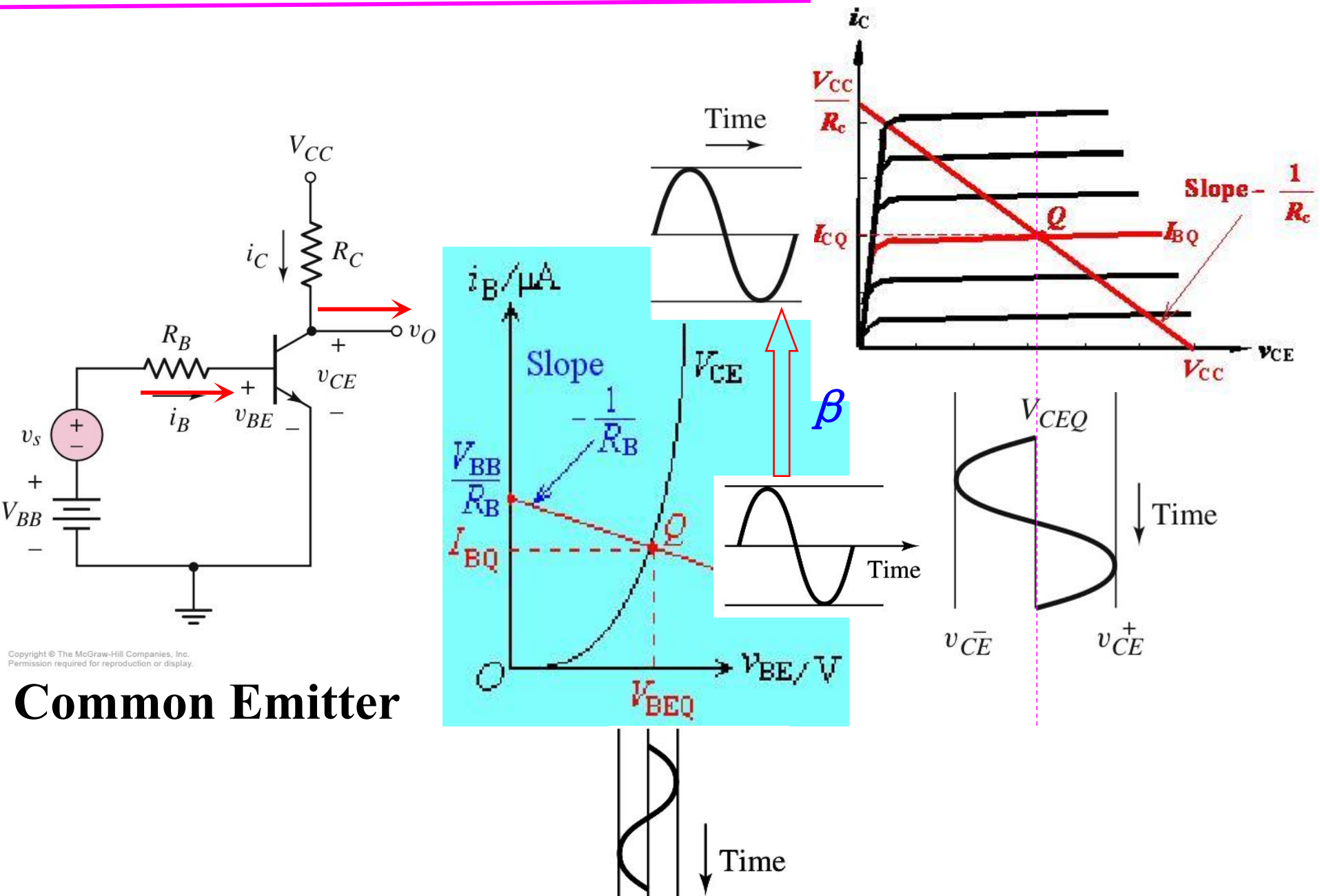
6.2.1 Graphical Analysis and ac Equivalent Circuit



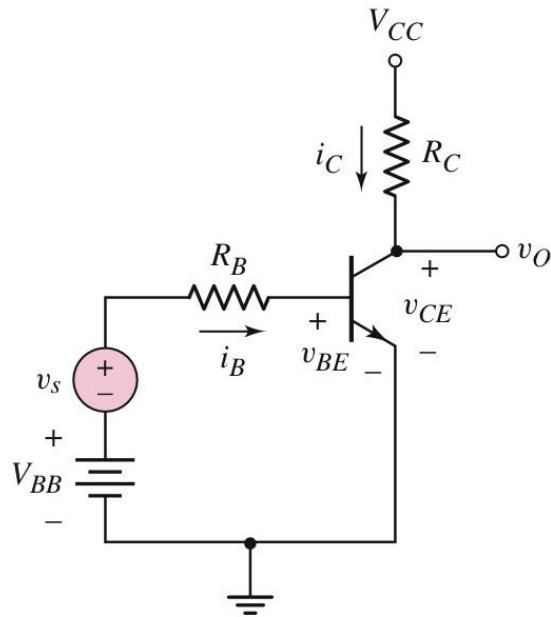6.2.1 Graphical Analysis and ac Equivalent Circuit



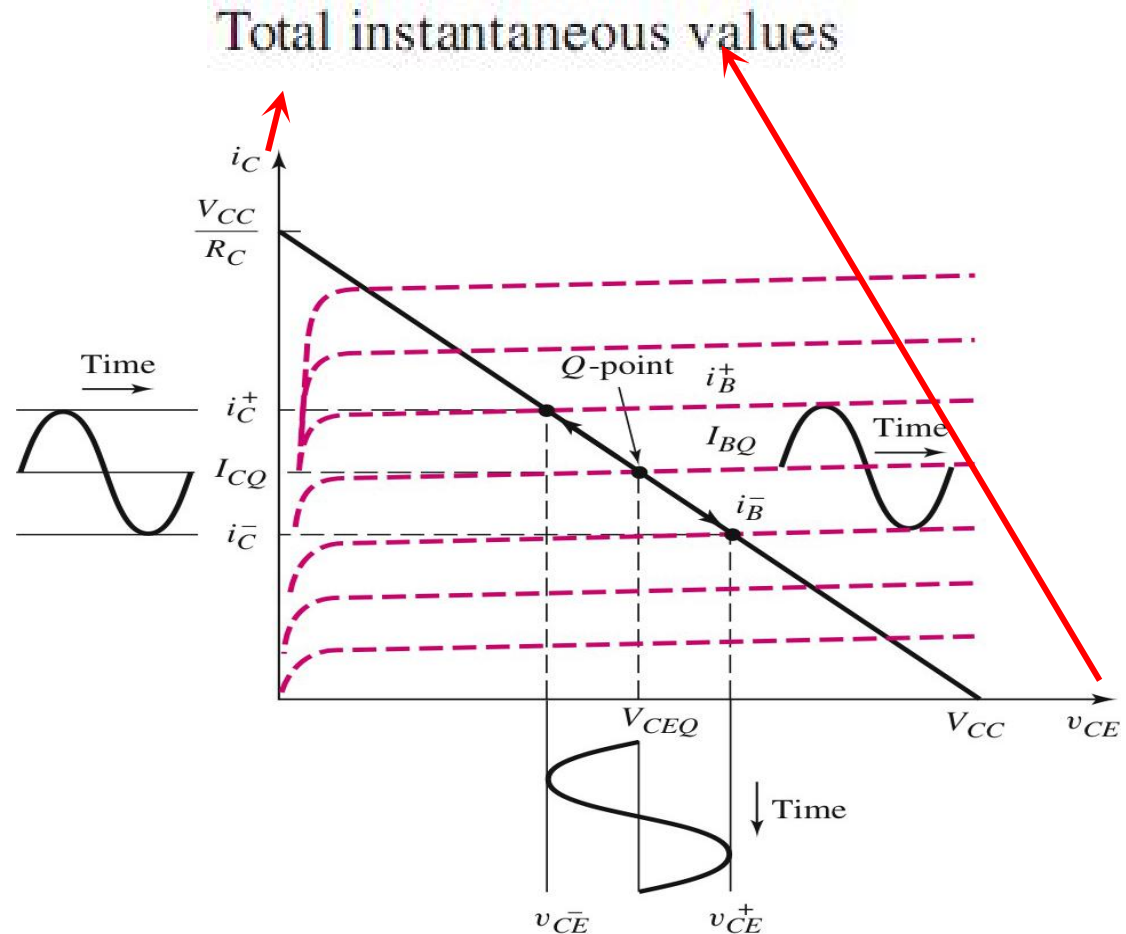Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

How to get the small signal model?

6.2.1 Graphical Analysis and ac Equivalent Circuit

i_B Versus v_{BE} Characteristic

$$i_B = \frac{i_C}{\beta} = \frac{I_S e^{\frac{v_{BE}}{V_T}}}{\beta}$$

$$v_{BE} = V_{BE} + v_{be}$$


$$i_B = \frac{I_S}{\beta} e^{\frac{V_{BE} + v_{be}}{V_T}} = \frac{I_S}{\beta} e^{\frac{V_{BE}}{V_T} + \frac{v_{be}}{V_T}}$$

$$= \frac{I_S}{\beta} \cdot e^{\frac{V_{BE}}{V_T}} \cdot e^{\frac{v_{be}}{V_T}} = I_{BQ} \cdot e^{\frac{v_{be}}{V_T}}$$

$$v_{be} \ll V_T$$

Taylor series
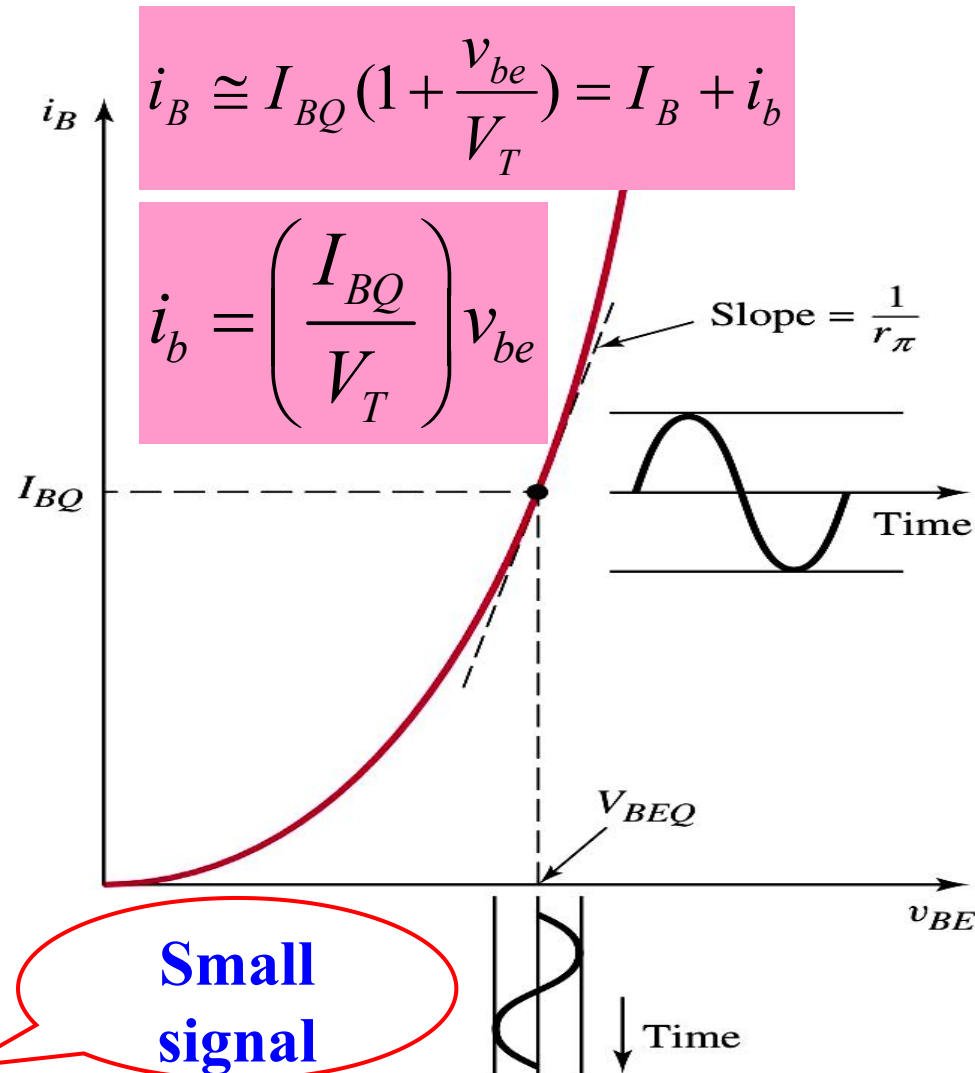
$$e^{\frac{v_{be}}{V_T}} = 1 + \frac{v_{be}}{V_T}$$



6.2.2 Small signal Hybrid- Π Equivalent Circuit


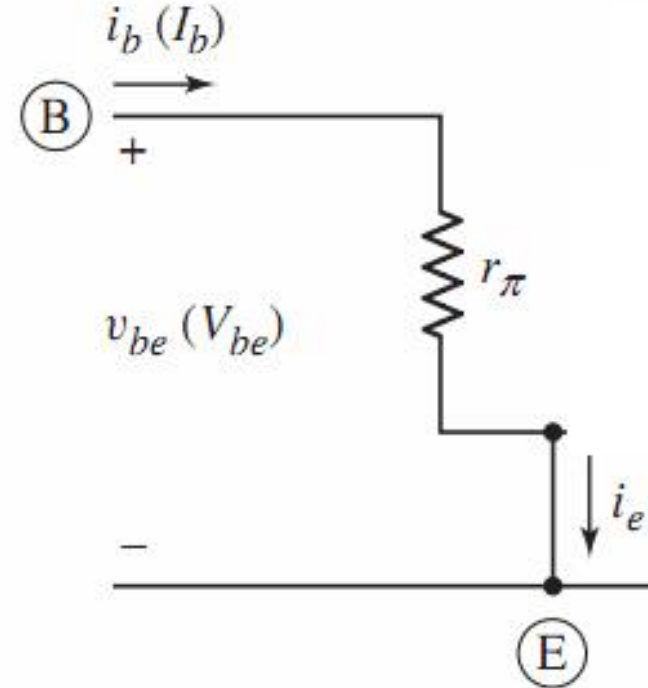
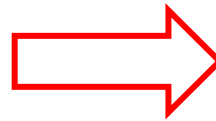
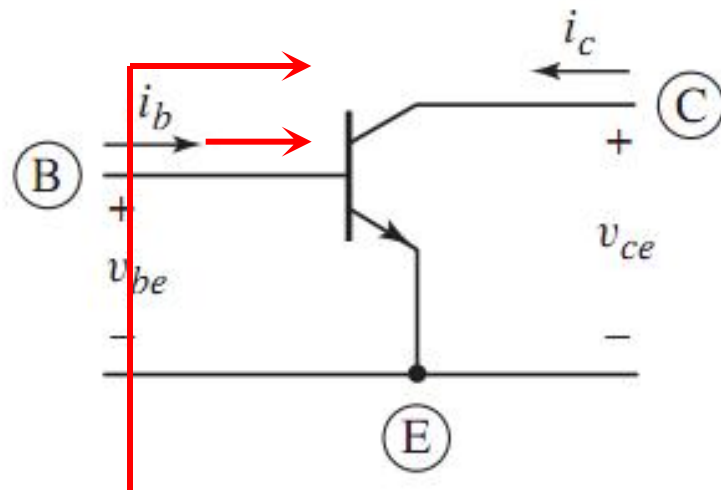


Figure 6.8 The BJT as a small-signal, two-port network


$$v_{be} = i_b r_\pi \quad i_b = \left(\frac{I_{BQ}}{V_T} \right) v_{be}$$
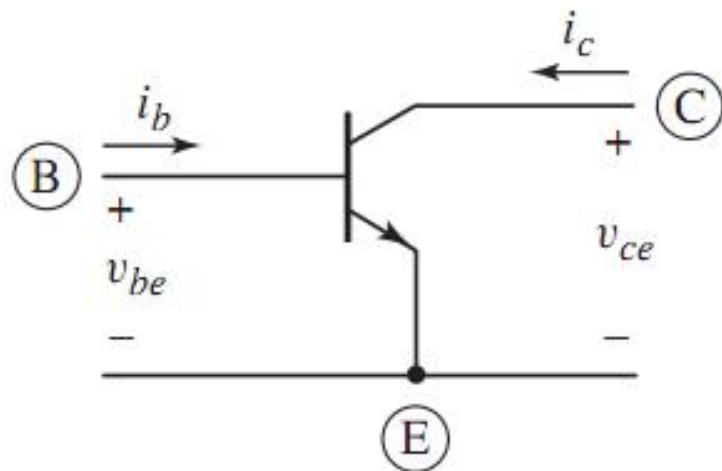
$$r_\pi = \frac{V_T}{I_{BQ}} = \frac{\beta V_T}{I_{CQ}}$$



$$i_C = I_S \exp\left(\frac{v_{BE}}{V_T}\right)$$

Figure 6.8 The BJT as a small-signal, two-port network

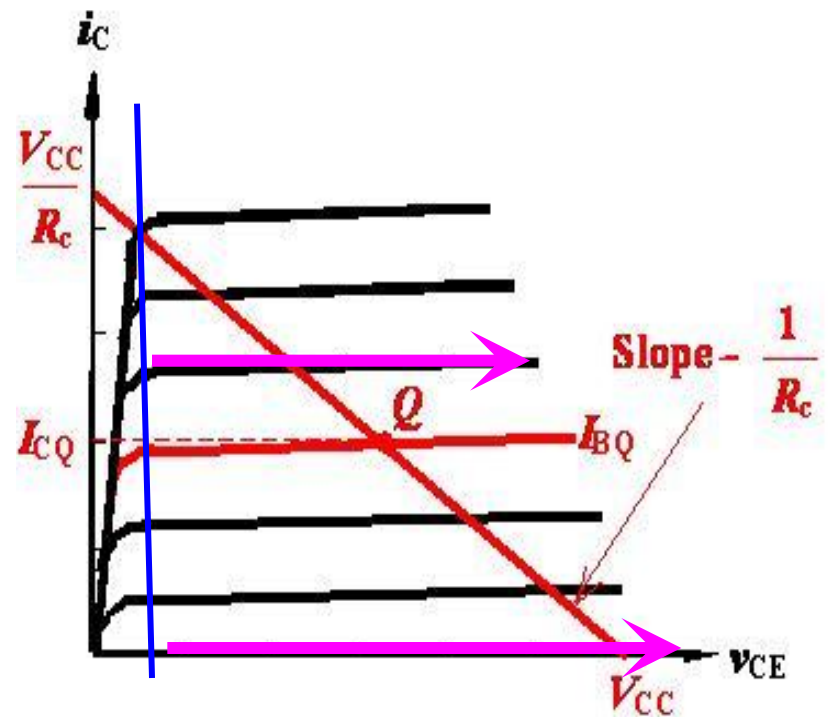

6.2.2 Small signal Hybrid- Π Equivalent Circuit

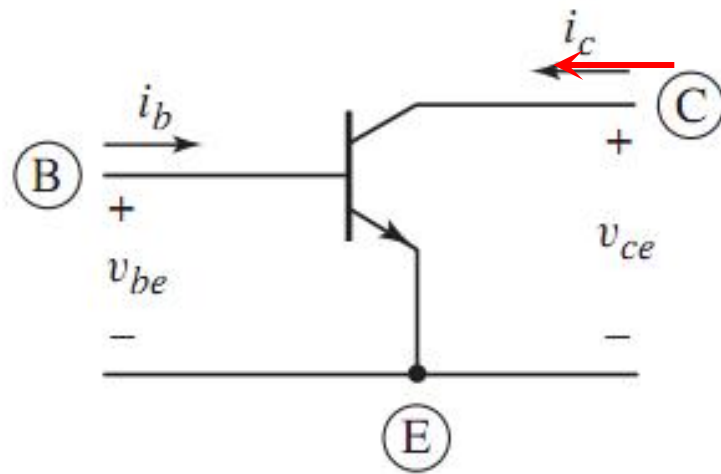


Figure 6.8 The BJT as a small-signal, two-port network

Transconductance

$$\Delta i_C = \left. \frac{\partial i_C}{\partial v_{BE}} \right|_{Q-pt} \cdot \Delta v_{BE}$$

$$i_c = \left. \frac{\partial i_C}{\partial v_{BE}} \right|_{Q-pt} \cdot v_{be}$$

$$i_C = I_S \exp\left(\frac{v_{BE}}{V_T}\right)$$

$$\left. \frac{\partial i_C}{\partial v_{BE}} \right|_{Q-pt} = \frac{1}{V_T} \cdot I_S \exp\left(\frac{v_{BE}}{V_T}\right) \Big|_{Q-pt}$$

$$= \frac{I_{CQ}}{V_T}$$

$$g_m = \frac{I_{CQ}}{V_T}$$

$$i_c = g_m \cdot v_{be}$$

6.2.2 Small signal Hybrid- Π Equivalent Circuit



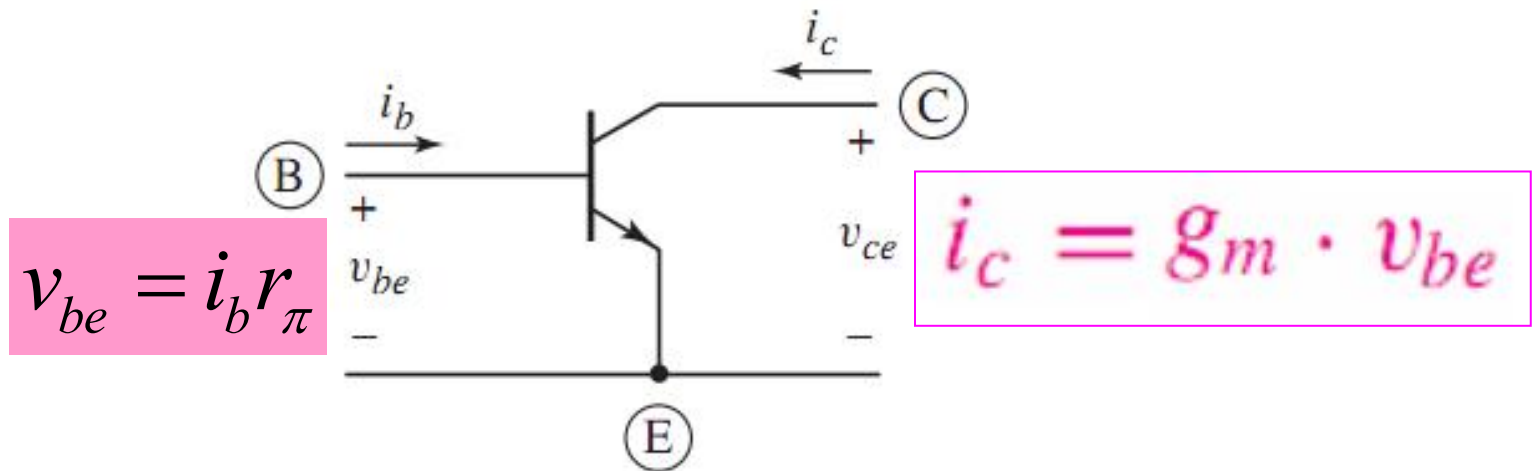


Figure 6.8 The BJT as a

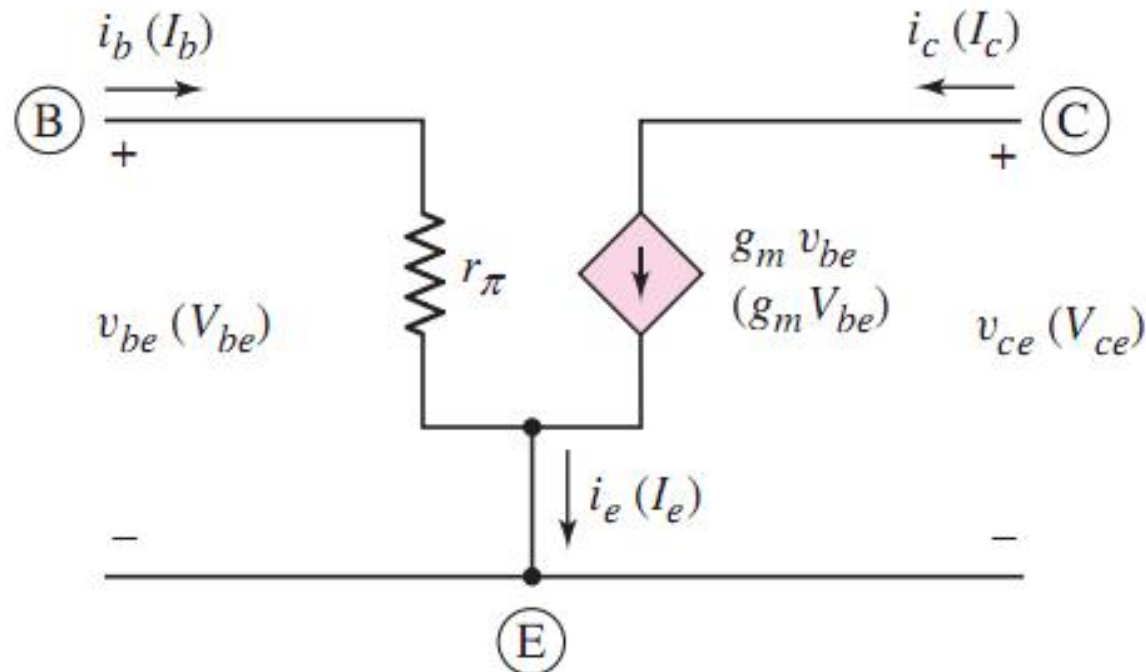


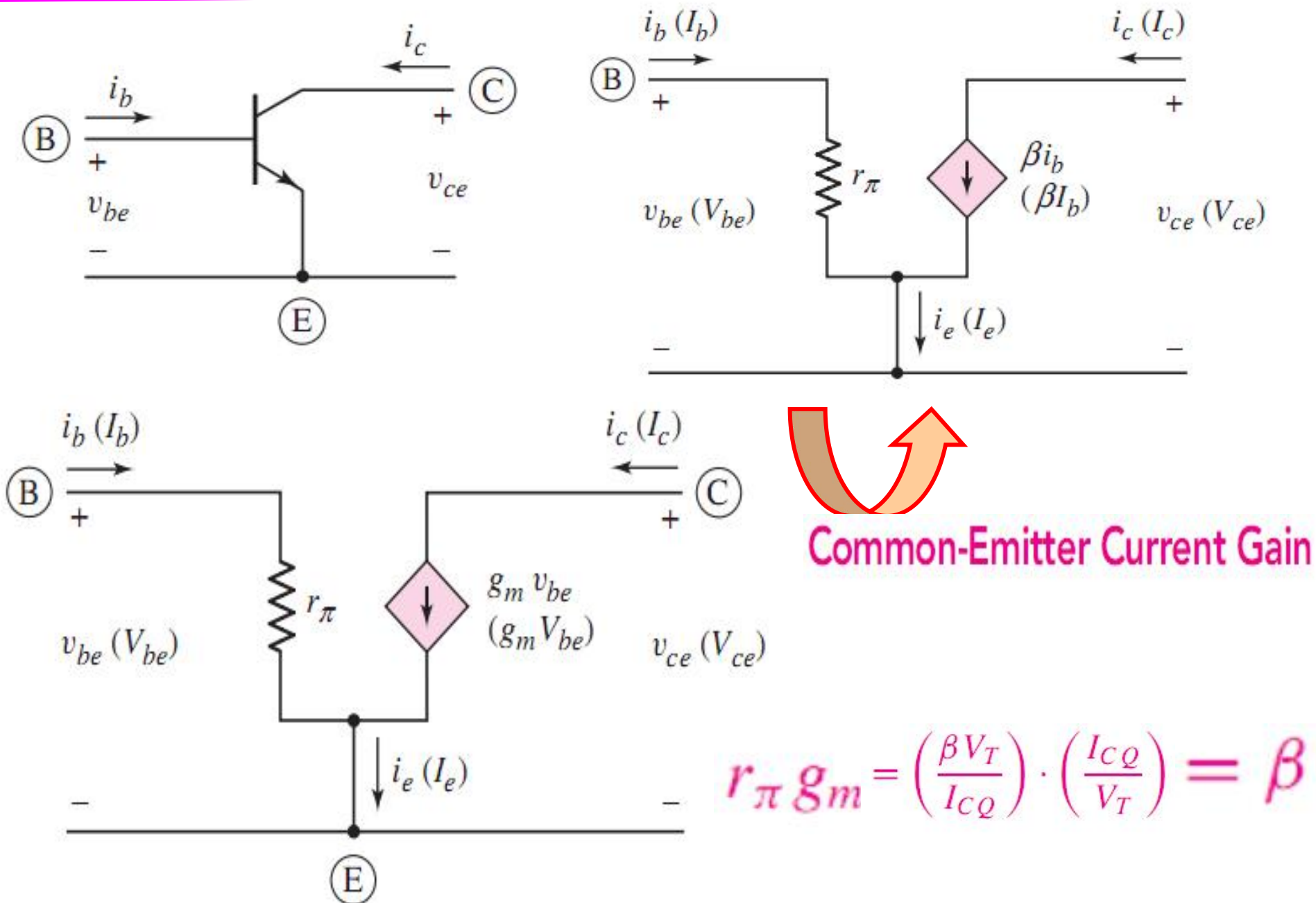
6.2.2 Small signal Hybrid- Π Equivalent Circuit



6.2.2 Small signal Hybrid- Π Equivalent Circuit


Small signal voltage gain

AC circuit

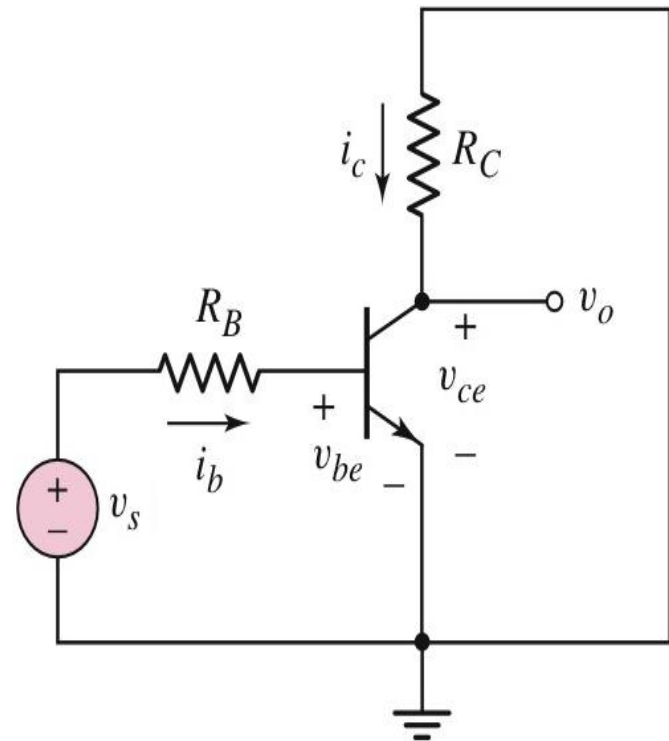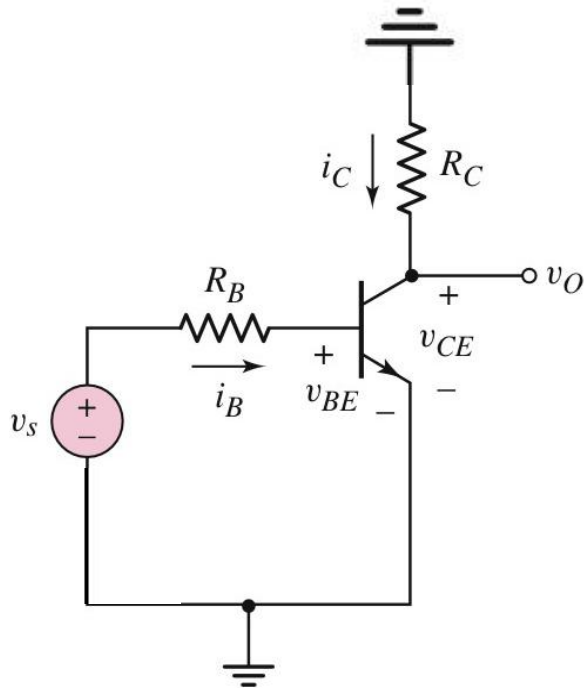


6.2.2 Small signal Hybrid- Π Equivalent Circuit

Small signal voltage gain

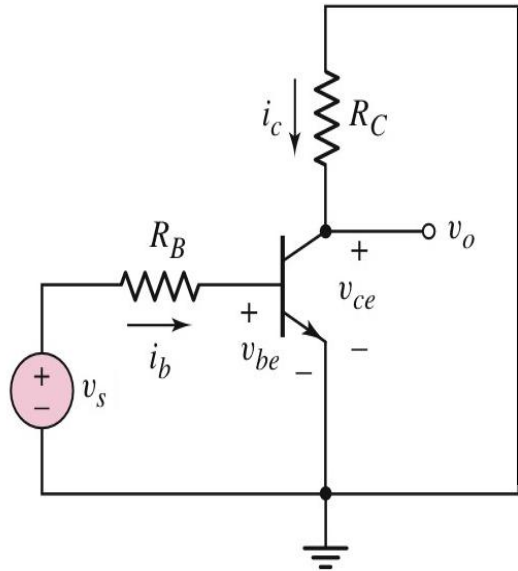

Small-Signal Equivalent Circuit

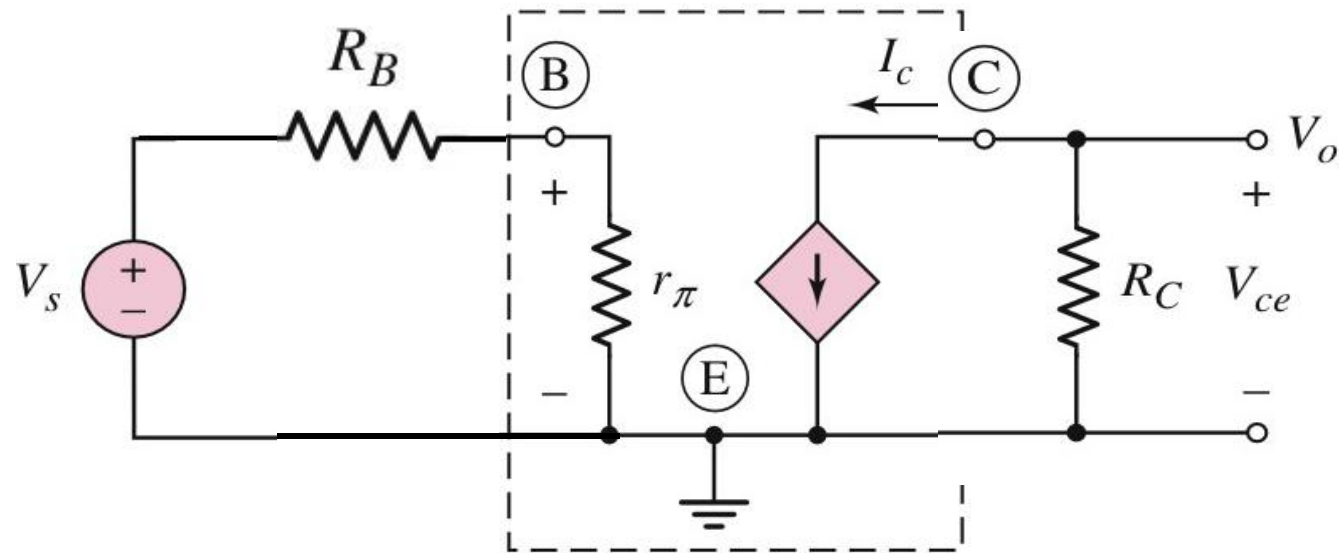


6.2.2 Small signal Hybrid- Π Equivalent Circuit

Small signal voltage gain

$$A_v = \frac{V_o}{V_\pi} = ?$$

$$- g_m R_C \parallel R_L$$

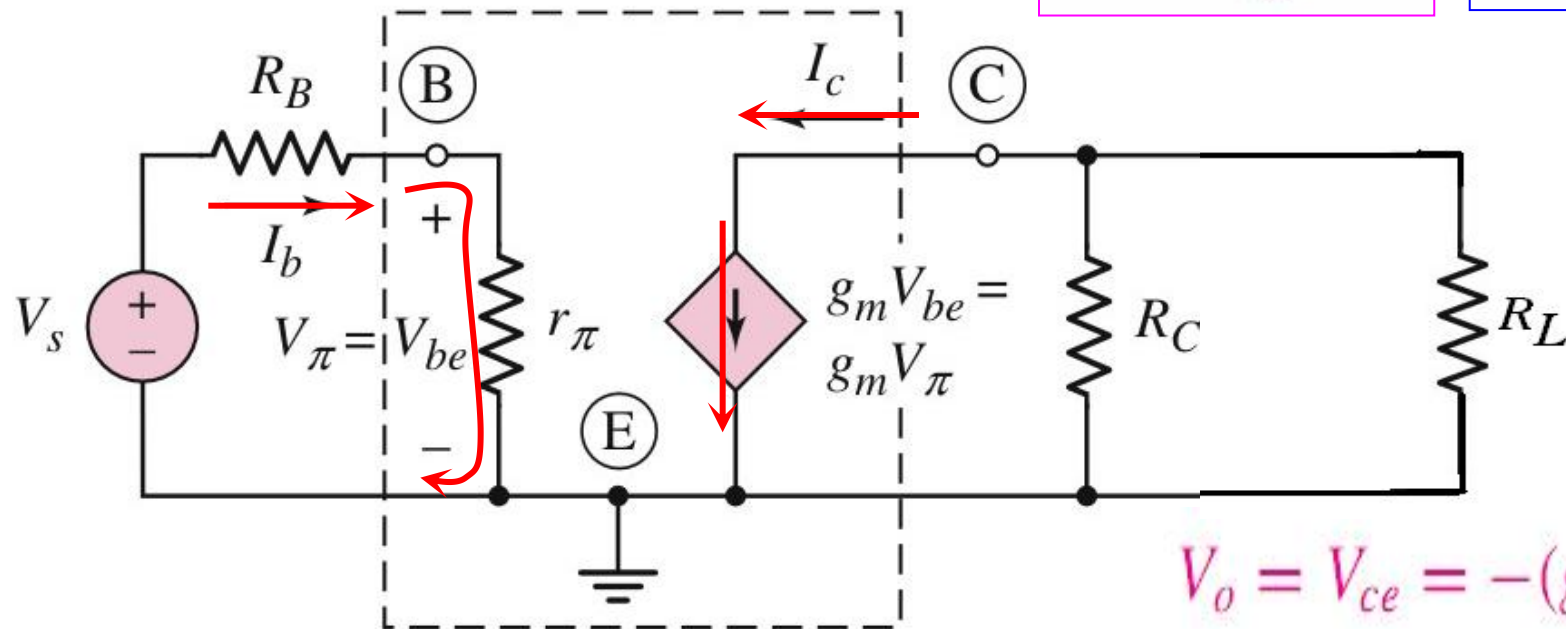

$$V_o = V_{ce} = -(g_m V_\pi) R_C$$

$$V_\pi = \left(\frac{r_\pi}{r_\pi + R_B} \right) \cdot V_s$$

$$A_v = \frac{V_o}{V_\pi} :$$


$$A_{us} = \frac{V_o}{V_s} = -(g_m R_C) \cdot \left(\frac{r_\pi}{r_\pi + R_B} \right)$$

$$A_v = \frac{V_o}{V_\pi} = - g_m R_C$$

6.2.2 Small signal Hybrid- Π Equivalent Circuit

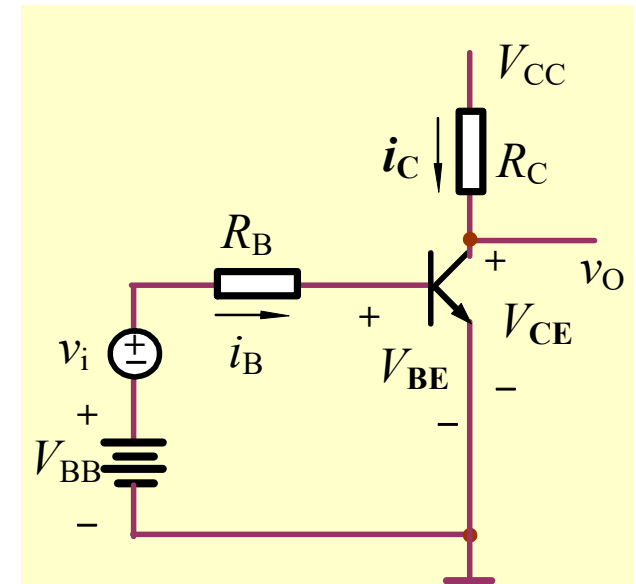Example 1

Calculate the small-signal voltage gain of the bipolar transistor circuit shown in Fig. Assume $\beta=100$, $V_{CC}=12\text{V}$, $V_{BE}=0.7\text{V}$, $R_C=6\text{k}\Omega$, $R_B=50\text{k}\Omega$, $V_{BB}=1.2\text{V}$. If $v_i=0.25\sin\omega t\text{ V}$, find v_o .



Sol: (1) Find the Q-point values

$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{1.2 - 0.7}{50} = 10\text{ uA}$$

$$I_C = \beta I_B = 100 \times 10\text{ uA} = 1\text{mA}$$

$$V_{CE} = V_{CC} - I_C R_C = 12 - 1\text{mA} \times 6\text{k}\Omega = 6\text{V}$$

Which region?

6.2.2 Small signal Hybrid- Π Equivalent Circuit

Example 1

(2) Find the small-signal parameters

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = \frac{100 \times 0.026}{1} = 2.6 \text{ k}\Omega$$



and $g_m = \frac{I_{CQ}}{V_T} = \frac{1}{0.026} = 38.5 \text{ mA/V}$

(3) Find AC parameters

$$A_{vs} = \frac{V_o}{V_i} = -g_m R_C \frac{r_{\pi}}{r_{\pi} + R_B}$$

$$= -38.5 \times 6 \times \frac{2.6}{2.6 + 50}$$

$$= -11.4$$

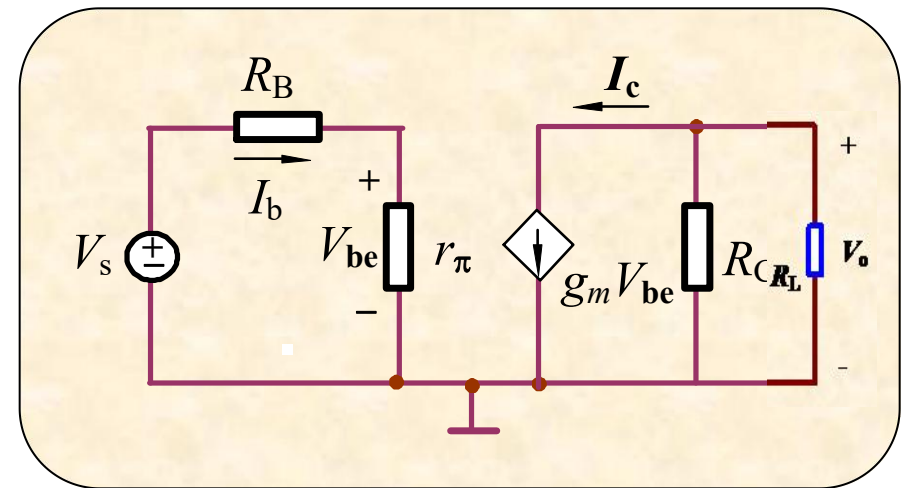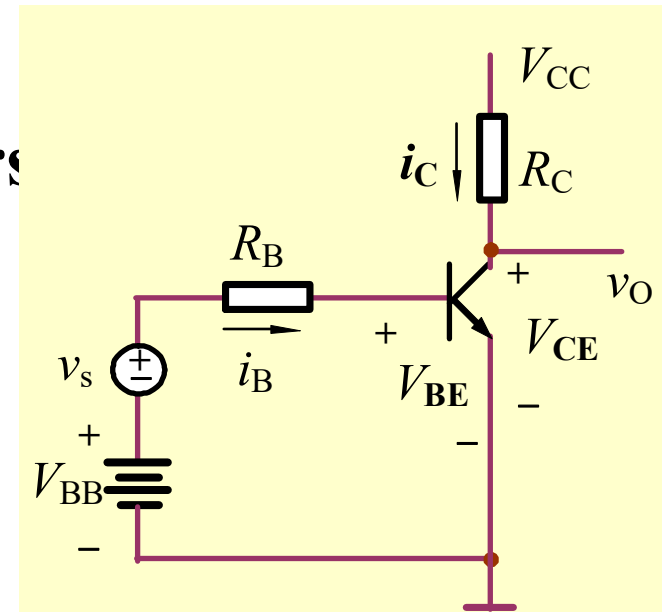

6.2.2 Small signal Hybrid- Π Equivalent Circuit


Example 1

(3) In small-signal circuit, ac base current is given by

$$i_b = \frac{v_i}{R_B + r_\pi} = \frac{0.25 \sin \omega t}{50 + 2.6} = 4.75 \sin \omega t (\mu A)$$

$$i_c = \beta i_b = 100 \times 4.75 \sin \omega t = 0.475 \sin \omega t (mA)$$


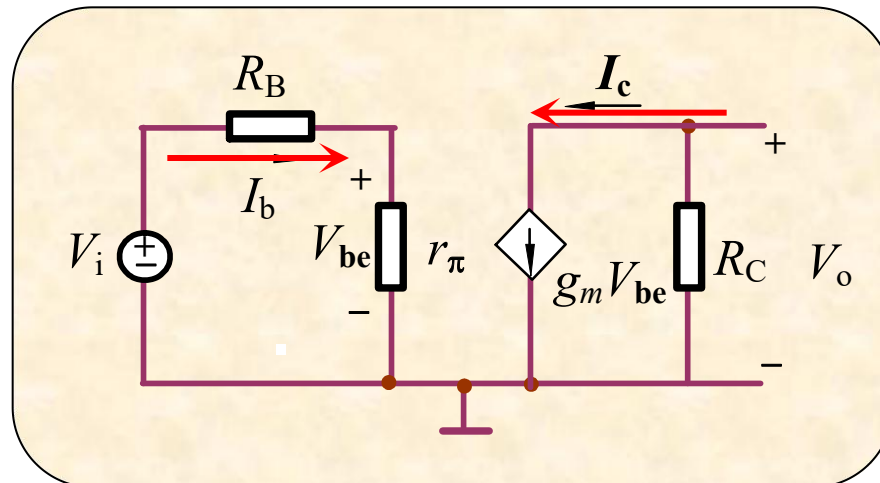
$$v_o = -i_c R_c = -(0.475 \sin \omega t) \times 6 = -2.85 \sin \omega t (V)$$



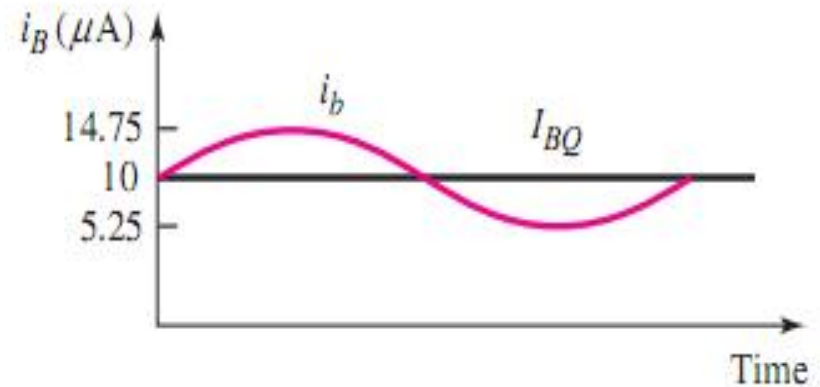
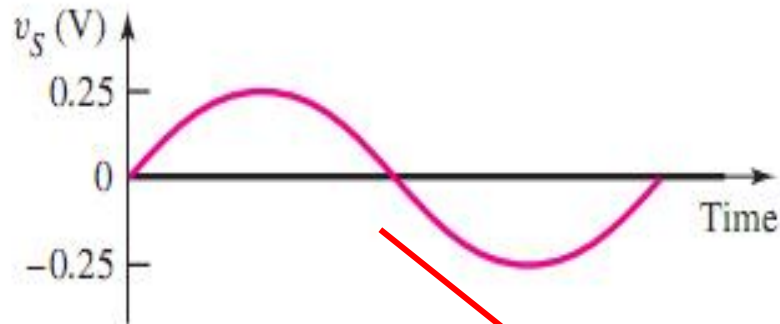
6.2.2 Small signal Hybrid- Π Equivalent Circuit

$$v_s = 0.25 \sin \omega t \text{ V}$$

$$i_b = 4.75 \sin \omega t (\mu\text{A})$$



180-degree phase shift

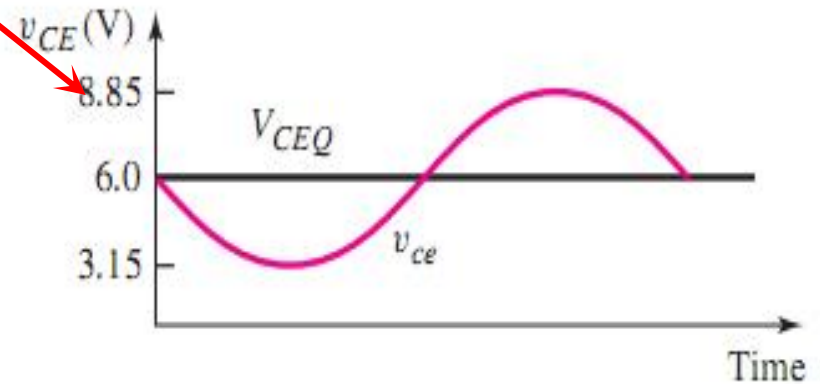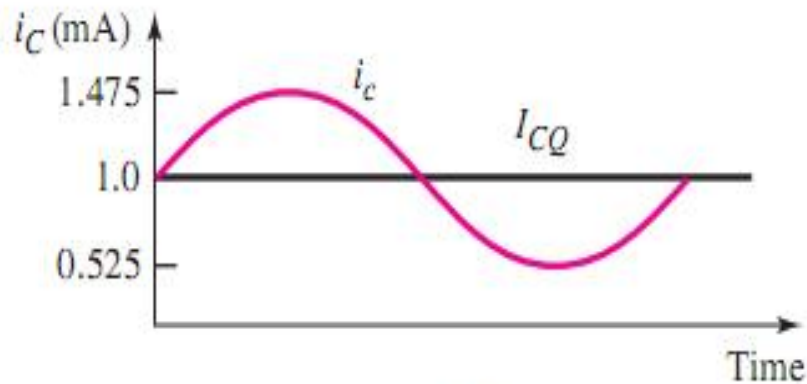

$$i_c = 0.475 \sin \omega t (mA)$$

$$v_o = -2.85 \sin \omega t (V)$$

6.2.2 Small signal Hybrid- π Equivalent Circuit









Problem-Solving Technique: BJT AC Analysis

- 1. Analyze circuit with only dc sources to find Q point.**
- 2. Replace each element in circuit with small-signal model, including the hybrid π model for the transistor.**
- 3. Analyze the small-signal equivalent circuit after setting dc source components to zero.**


6.2.2 Small signal Hybrid- Π Equivalent Circuit

Table 6.2

Transformation of elements in dc and small-signal analysis

Element	I - V relationship	DC model	AC model
Resistor	$I_R = \frac{V}{R}$	R	R
Capacitor	$I_C = sC V$	Open 	C
Inductor	$I_L = \frac{V}{sL}$	Short 	L
Diode	$I_D = I_S(e^{v_D/V_T} - 1)$	$+V_\gamma - r_f$ 	$r_d = V_T/I_D$ 
Independent voltage source	$V_S = \text{constant}$	$+V_S -$ 	Short 
Independent current source	$I_S = \text{constant}$	I_S 	Open 

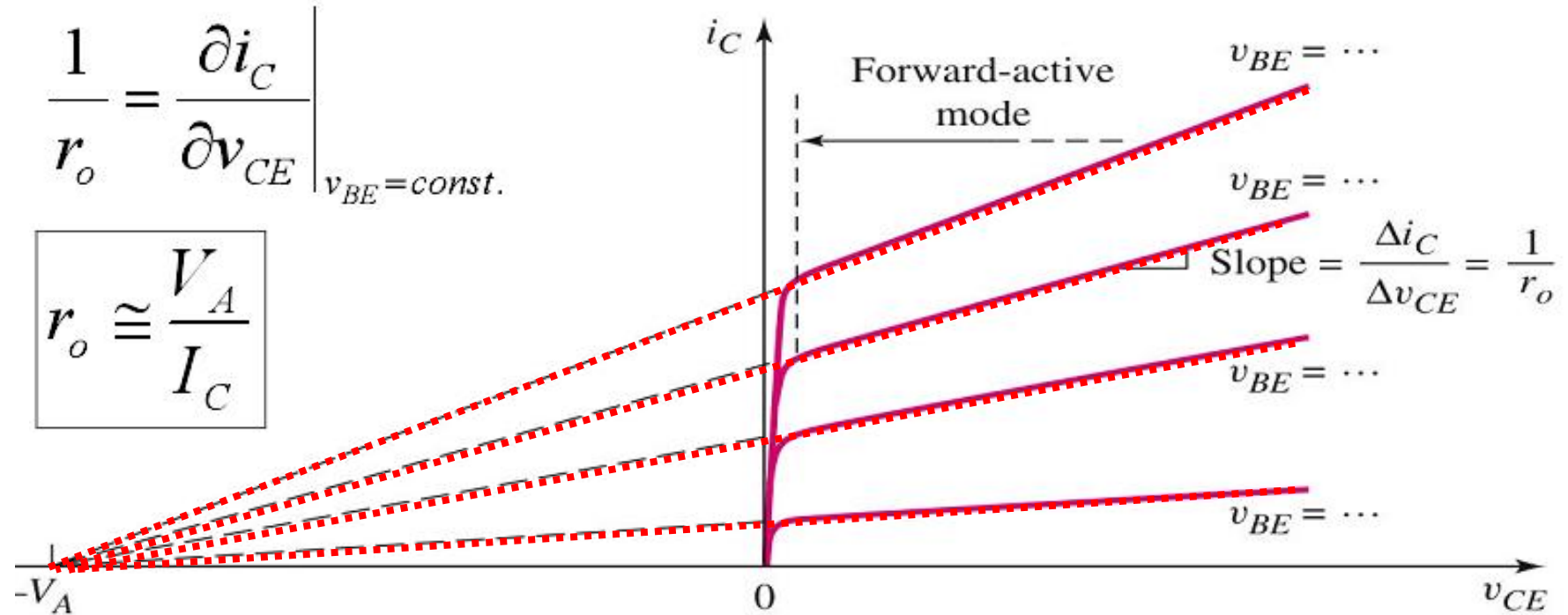6.2.3 Hybrid- π Equivalent Circuit , Including the Early Effect





- V_A : Early voltage : a point at negative voltage axis where all curves meet

$$r_o = \frac{V_A}{I_{CQ}} \quad \text{small-signal transistor output resistance}$$

6.2.3 Hybrid- π Equivalent Circuit , Including the Early Effect

Hybrid π Model for npn with Early Effect

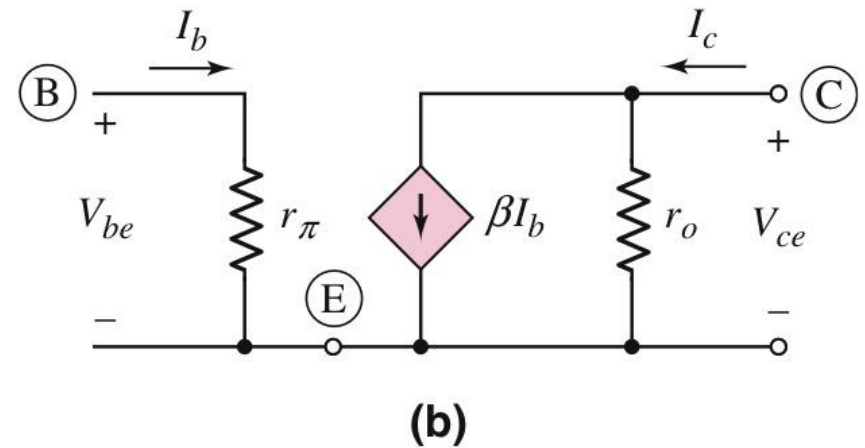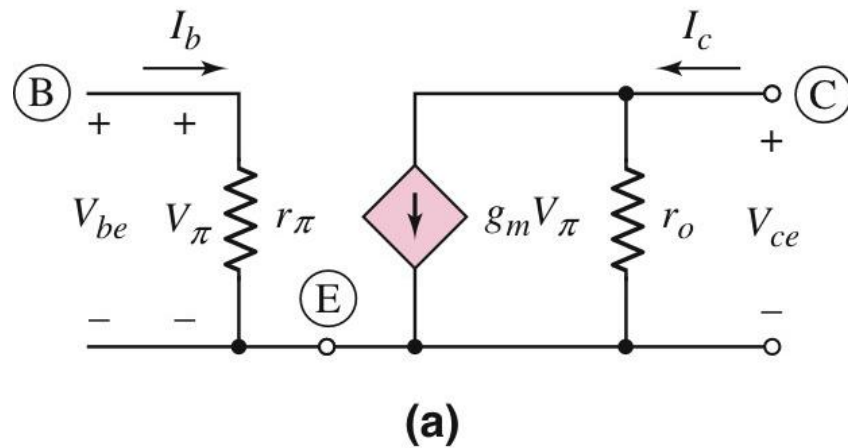


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$r_o = \frac{V_A}{I_{CQ}}$$

6.2.3 Hybrid- Π Equivalent Circuit , Including the Early Effect

$$V_A = 50 \text{ V.}$$

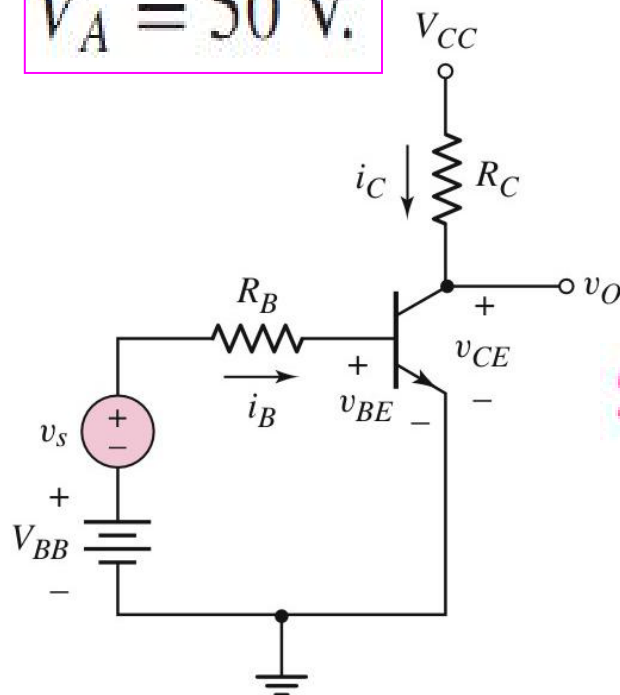


Calculate the small-signal voltage gain of the bipolar transistor circuit shown in Fig.

Assume $\beta=100$, $V_{CC}=12\text{V}$, $V_{BE}=0.7\text{V}$, $R_C=6\text{k}\Omega$, $R_B=50\text{k}\Omega$, $V_{BB}=1.2\text{V}$.

Solution:
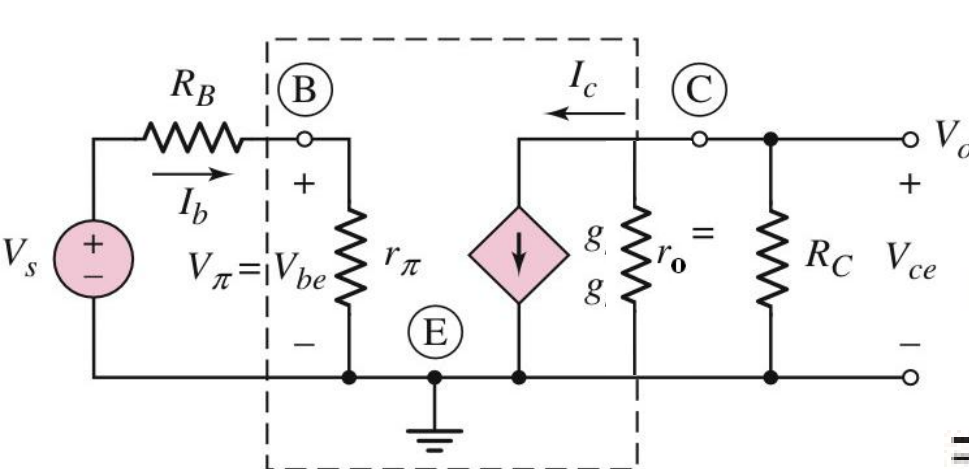
$$r_o = \frac{V_A}{I_{CQ}} = \frac{50}{1 \text{ mA}} = 50 \text{ k}\Omega$$







$$A_v = \frac{V_o}{V_s}$$


$$= -g_m (R_C \parallel \underline{r_o}) \left(\frac{r_\pi}{r_\pi + R_B} \right)$$

$$= -10.2 \quad \mathbf{-11.4}$$

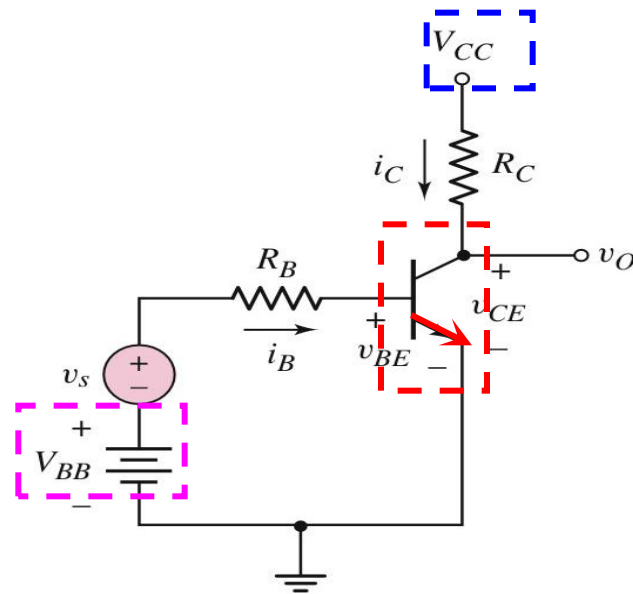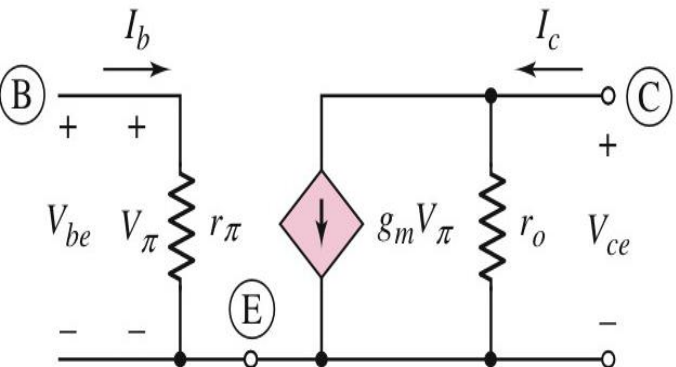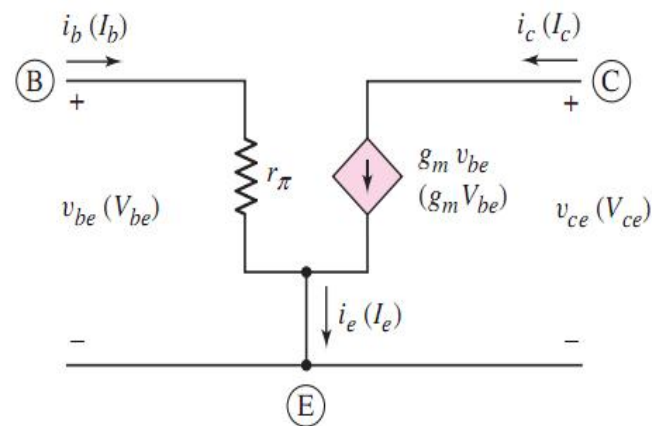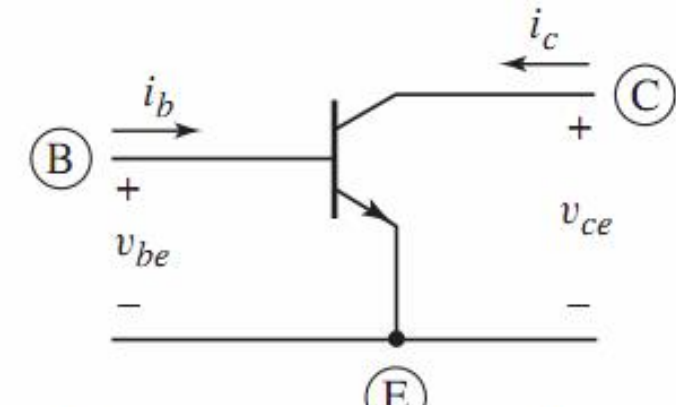6.2.3 Hybrid- Π Equivalent Circuit , Including the Early Effect



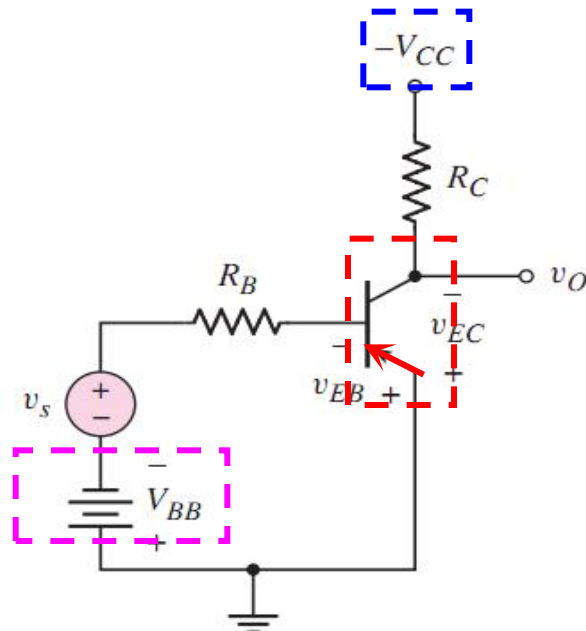Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.



small-signal
equivalent circuit





is the same

P389-396
Teach
yourself!

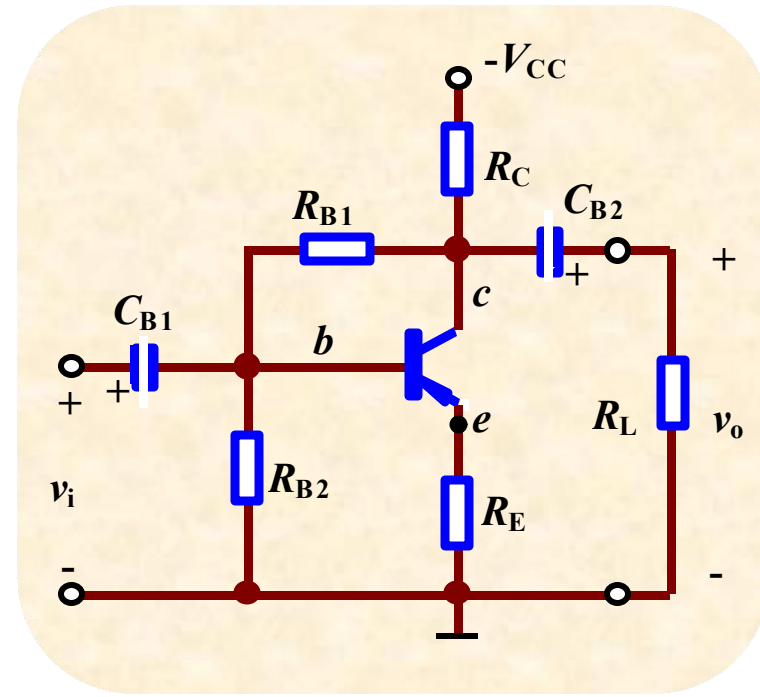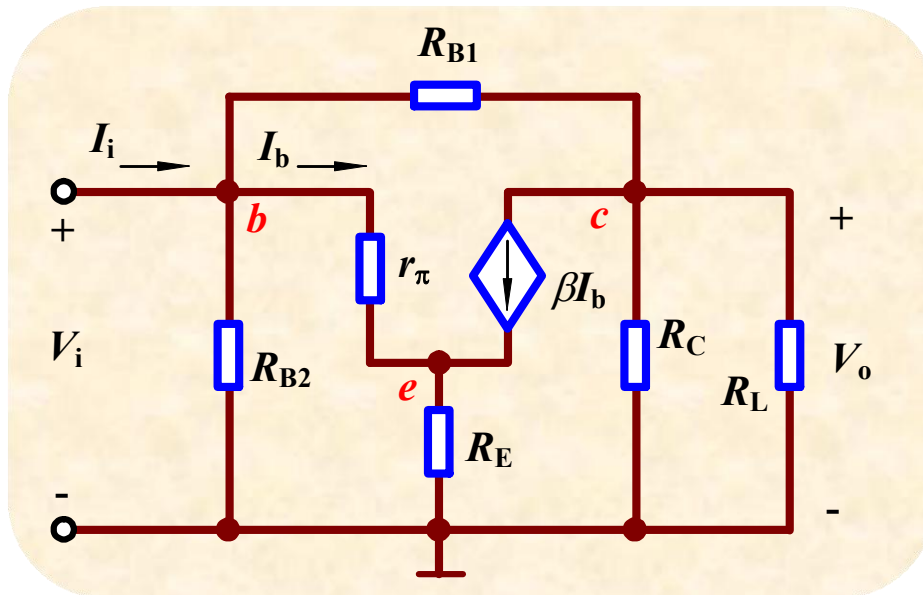Example

The circuit shown in Fig.

Draw its small-signal equivalent circuit.



Contents

PART 1 SEMICONDUCTOR DEVICES AND BASIC APPLICATIONS

Chapter 1 Semiconductor Materials and Diodes

Chapter 2 Diode Circuits

Chapter 3 The Field-Effect Transistor

Chapter 4 Basic FET Amplifiers

Chapter 5 The Bipolar Junction Transistor

 **Chapter 6 Basic BJT Amplifiers**

Chapter 7 Frequency Response

Chapter 8 Output Stages and Power Amplifiers

PART 2 ANALOG ELECTRONICS

Chapter 9 Ideal Operational Amplifiers and Op-Amp Circuits

Chapter 10 Integrated Circuit Biasing and Active Loads

Chapter 11 Differential and Multistage Amplifiers

Chapter 12 Feedback and Stability

Chapter 13 Operational Amplifier Circuits

Chapter 14 Nonideal Effects in Operational Amplifier Circuits

Chapter 15 Applications and Design of Integrated Circuits

Ch6. Basic BJT Amplifiers

6.0 Preview

6.1 Analog Signals and Linear Amplifiers

6.2 The Bipolar Linear Amplifier

6.3 Basic Transistor Amplifier Configurations

6.4 Common-Emitter Amplifiers

6.5 AC Load Line Analysis

6.6 Common-Collector (Emitter-Follower) Amplifier

6.7 Common-Base Amplifier


6.8 The Three Basic Amplifiers: Summary and Comparison

6.9 Multistage Amplifiers

6.10 Power Considerations


6.11 Design Application

6.12 Summary

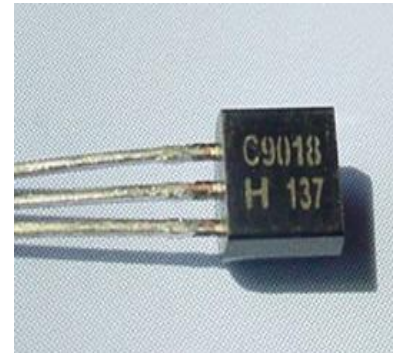

6.3 Basic Transistor Amplifier Configurations

Review

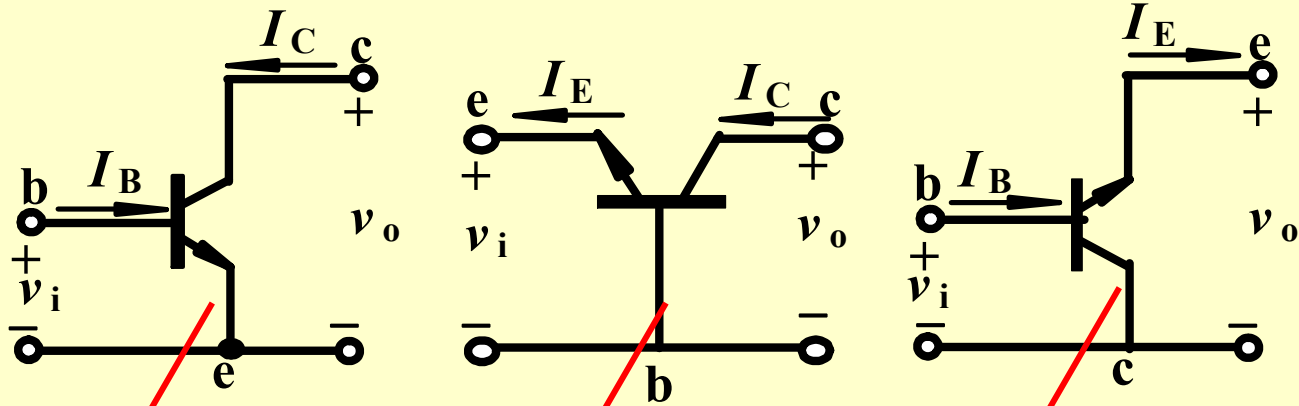

$$I_C = \beta I_B$$

$$I_C = \alpha I_E$$

$$I_E = I_B / (1 - \alpha)$$

CE


CB

Circuit Conf

CC

ns

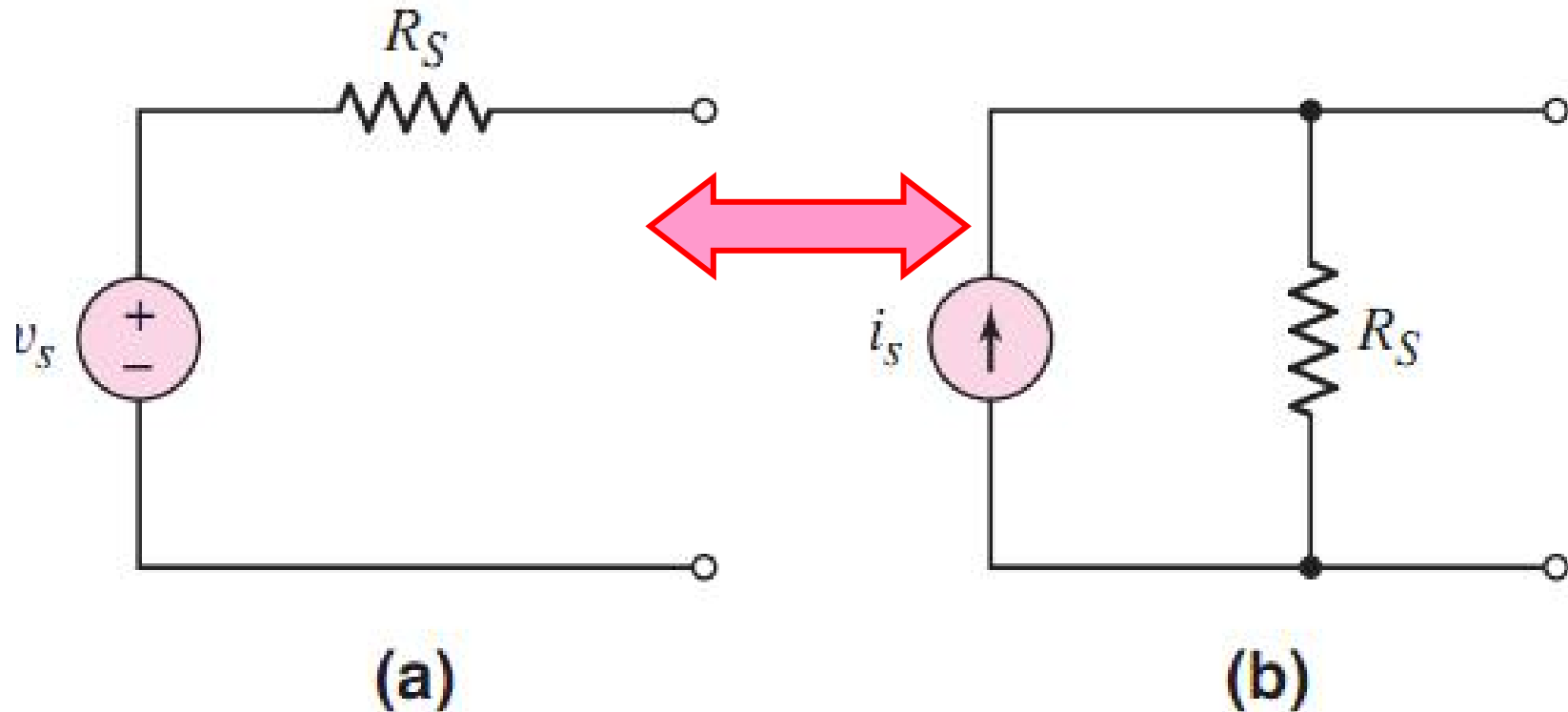
6.3 Basic Transistor Amplifier Configurations



Thevenin equivalent source Norton equivalent source

6.3 Basic Transistor Amplifier Configurations


Voltage Amplifier

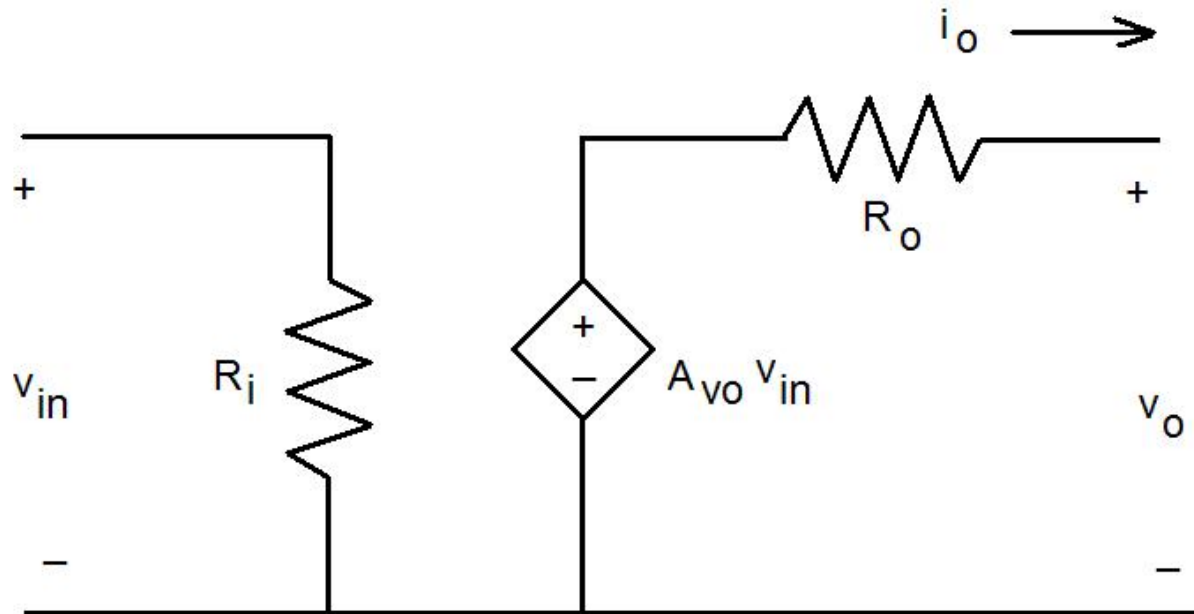

Output voltage proportional to
input voltage

6.3 Basic Transistor Amplifier Configurations


Current Amplifier

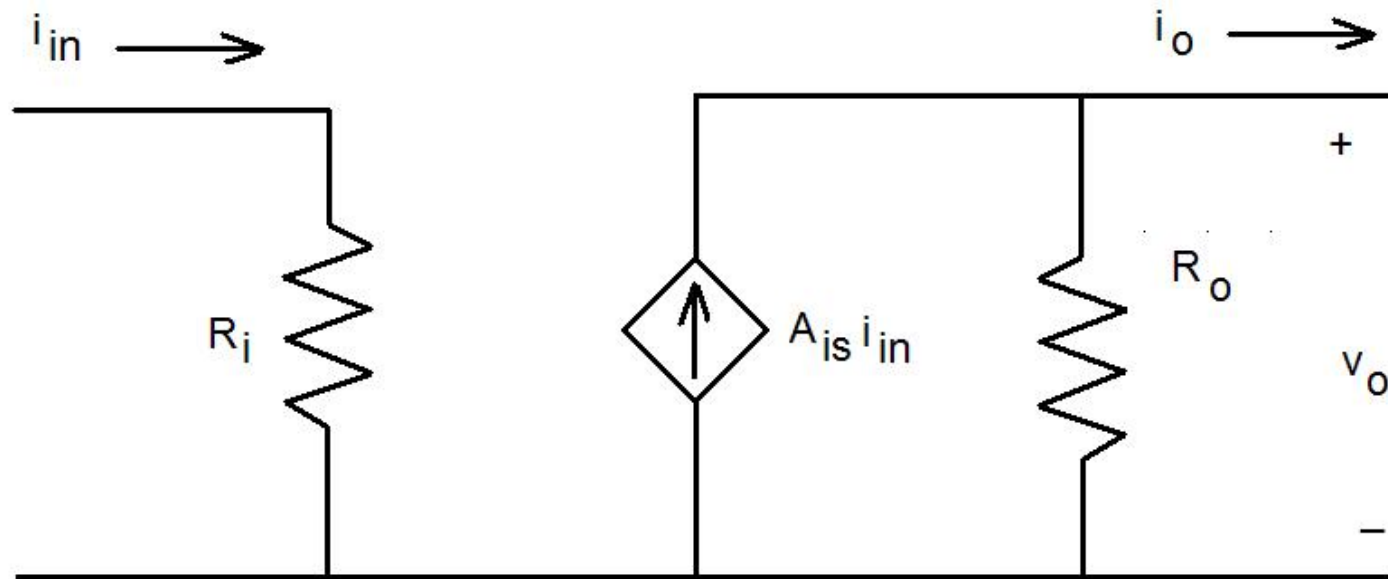

Output current proportional to
input current

6.3 Basic Transistor Amplifier Configurations


Transconductance Amplifier

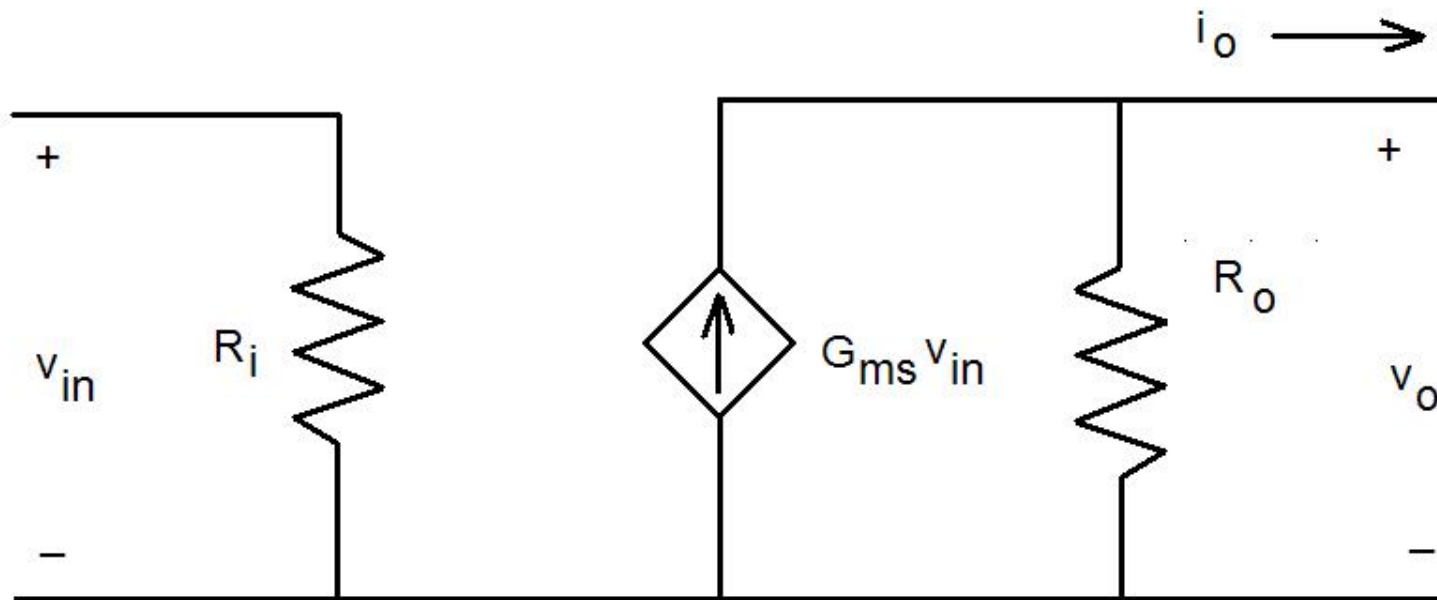

Output current proportional to
input voltage

6.3 Basic Transistor Amplifier Configurations





Transresistance Amplifier

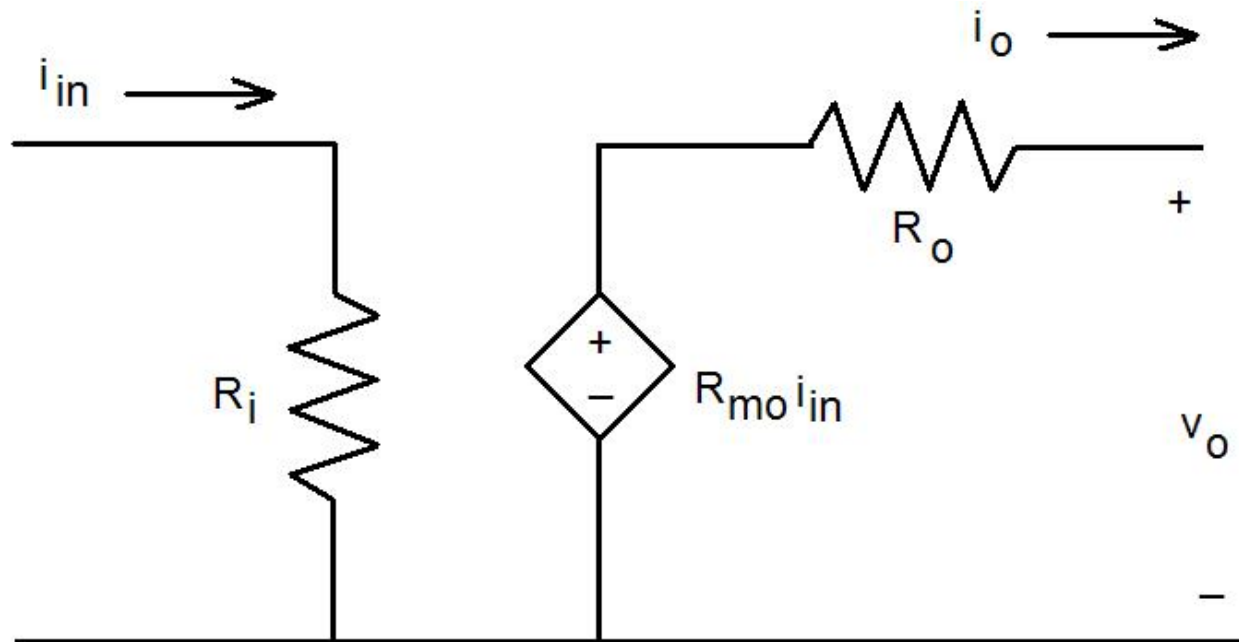

Output voltage proportional to
input current


6.3 Basic Transistor Amplifier Configurations

Table 6.3 Four equivalent two-port networks

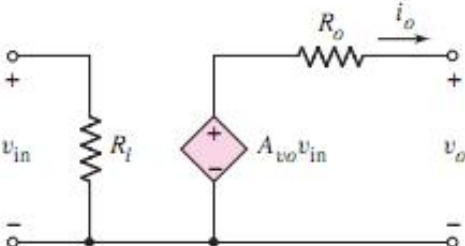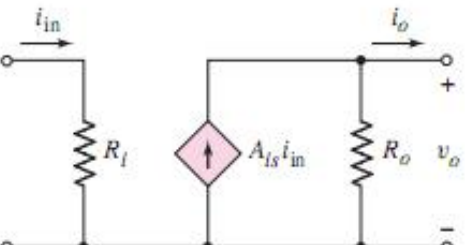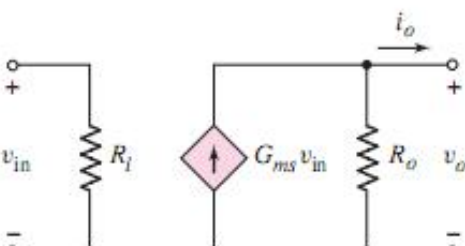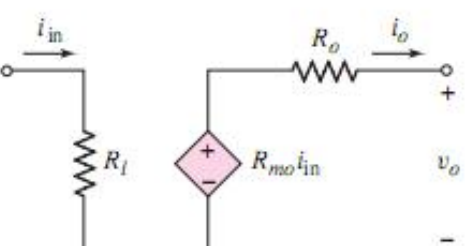Type	Equivalent circuit	Gain property
Voltage amplifier		Output voltage proportional to input voltage
Current amplifier		Output current proportional to input current
Transconductance amplifier		Output current proportional to input voltage
Transresistance amplifier		Output voltage proportional to input current

6.3 Basic Transistor Amplifier Configurations

Voltage Amplifier

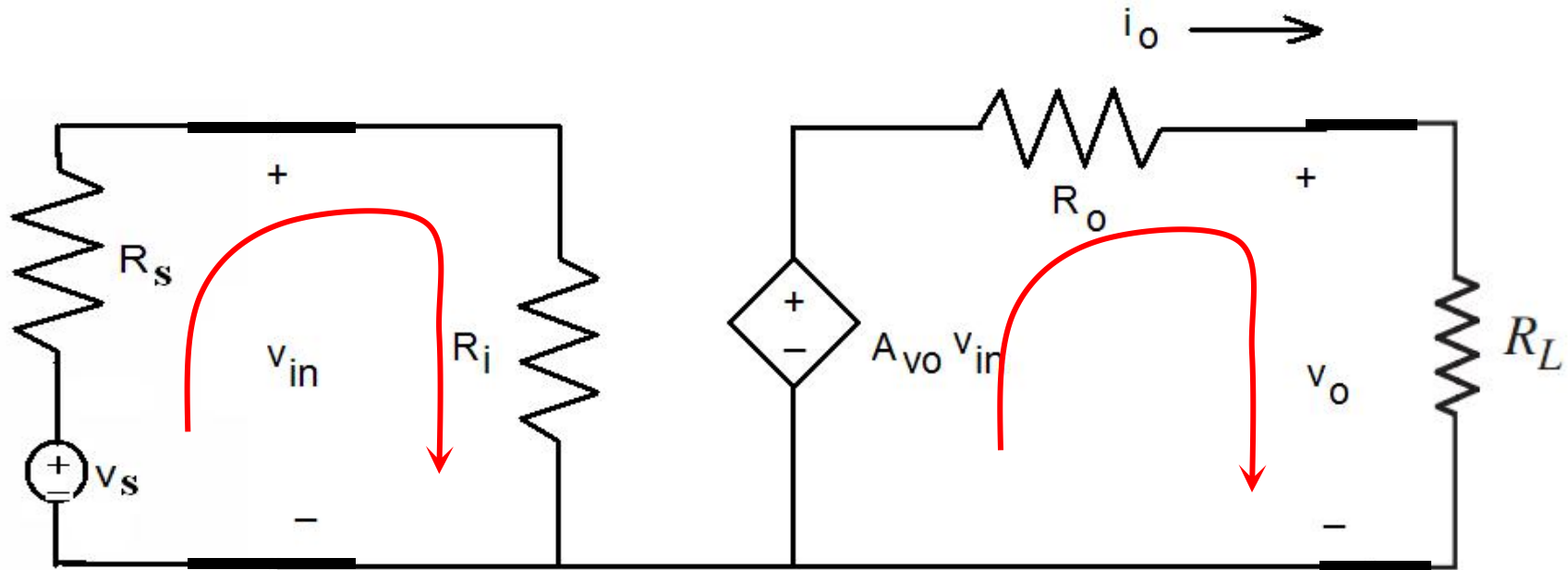


$$v_{in} = \frac{R_i}{R_i + R_s} \cdot v_s \qquad v_o = \frac{R_L}{R_L + R_o} \cdot A_{vo} v_{in}$$

$$R_i \gg R_s$$

$$R_o \ll R_L$$

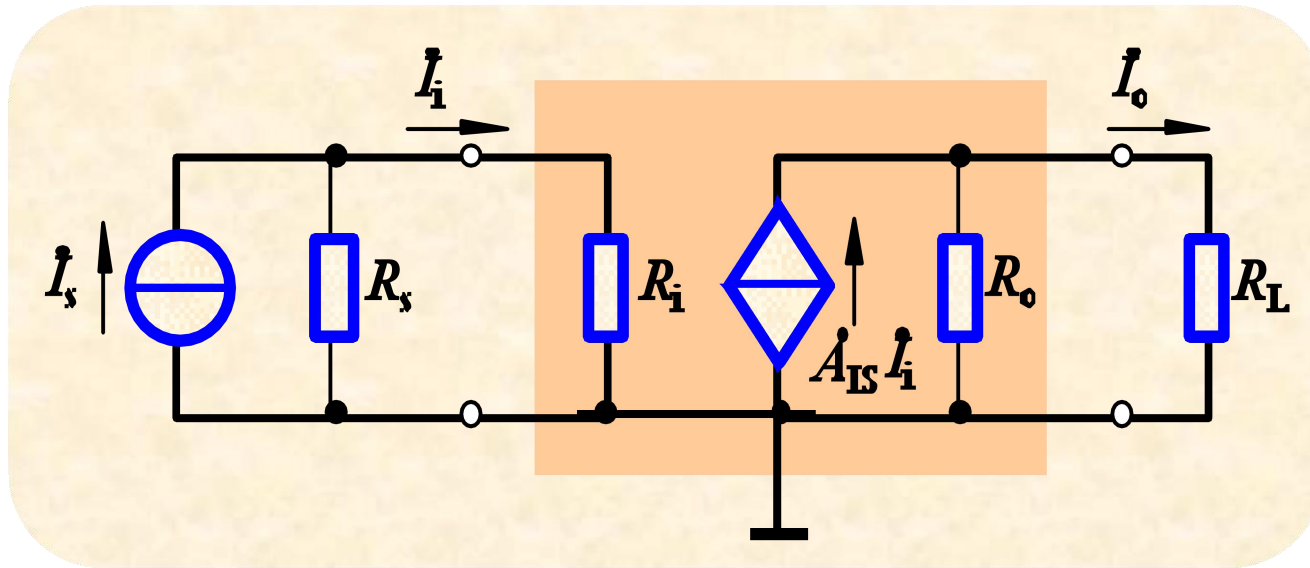6.3 Basic Transistor Amplifier Configurations



$$\dot{I}_i = \dot{I}_s \frac{R_s}{R_s + R_i}$$

C u r r e n t
a m p l i f i e r

$$R_i \ll R_s$$

$$R_o \gg R_L$$

Contents

PART 1 SEMICONDUCTOR DEVICES AND BASIC APPLICATIONS

Chapter 1 Semiconductor Materials and Diodes

Chapter 2 Diode Circuits

Chapter 3 The Field-Effect Transistor

Chapter 4 Basic FET Amplifiers

Chapter 5 The Bipolar Junction Transistor

 **Chapter 6 Basic BJT Amplifiers**

Chapter 7 Frequency Response

Chapter 8 Output Stages and Power Amplifiers

PART 2 ANALOG ELECTRONICS

Chapter 9 Ideal Operational Amplifiers and Op-Amp Circuits

Chapter 10 Integrated Circuit Biasing and Active Loads

Chapter 11 Differential and Multistage Amplifiers

Chapter 12 Feedback and Stability

Chapter 13 Operational Amplifier Circuits

Chapter 14 Nonideal Effects in Operational Amplifier Circuits

Chapter 15 Applications and Design of Integrated Circuits

Ch6. Basic BJT Amplifiers

6.0 Preview

6.1 Analog Signals and Linear Amplifiers

6.2 The Bipolar Linear Amplifier

6.3 Basic Transistor Amplifier Configurations

6.4 Common-Emitter Amplifiers

6.5 AC Load Line Analysis

6.6 Common-Collector (Emitter-Follower) Amplifier

6.7 Common-Base Amplifier


6.8 The Three Basic Amplifiers: Summary and Comparison

6.9 Multistage Amplifiers

6.10 Power Considerations


6.11 Design Application

6.12 Summary

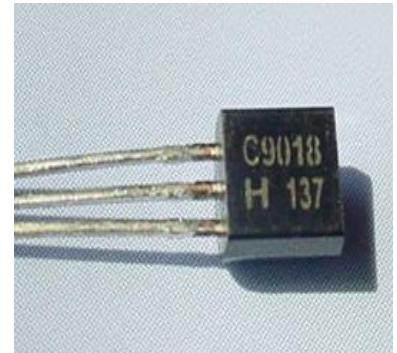

6.4 Common-Emitter Amplifiers

6.4.1 Common-Emitter Amplifier Circuit

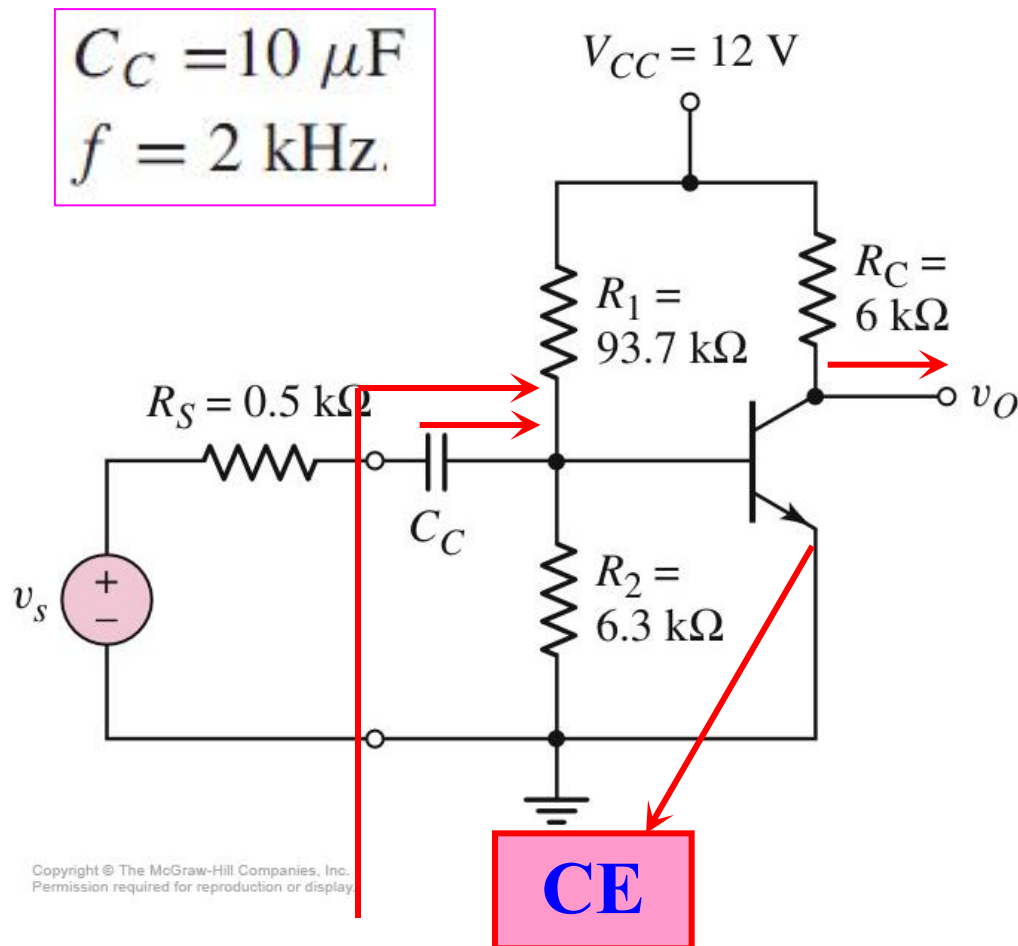

$$|Z_c| = \frac{1}{2\pi f C_C}$$
$$= \frac{1}{2\pi (2 \times 10^3)(10 \times 10^{-6})} \cong 8 \Omega$$

**2-port Networks equivalent
input impedance**



$$R_1 \parallel R_2 \parallel r_\pi$$

$$|Z_c| \ll R_1 \parallel R_2 \parallel r_\pi$$

capacitor is essentially a short circuit to signals with frequencies greater than 2 kHz.


6.4 Common-Emitter Amplifiers

6.4.1 Common-Emitter Amplifier Circuit

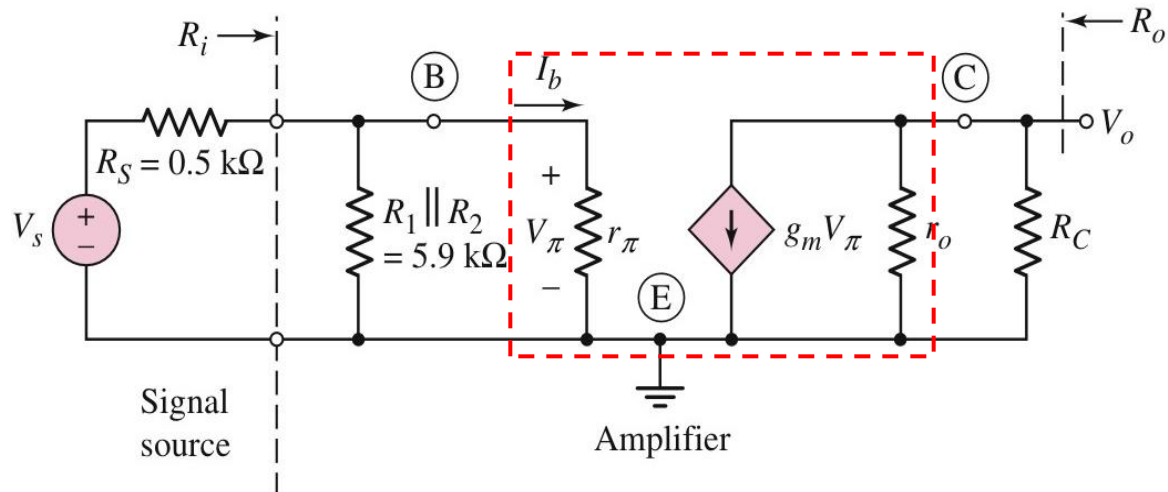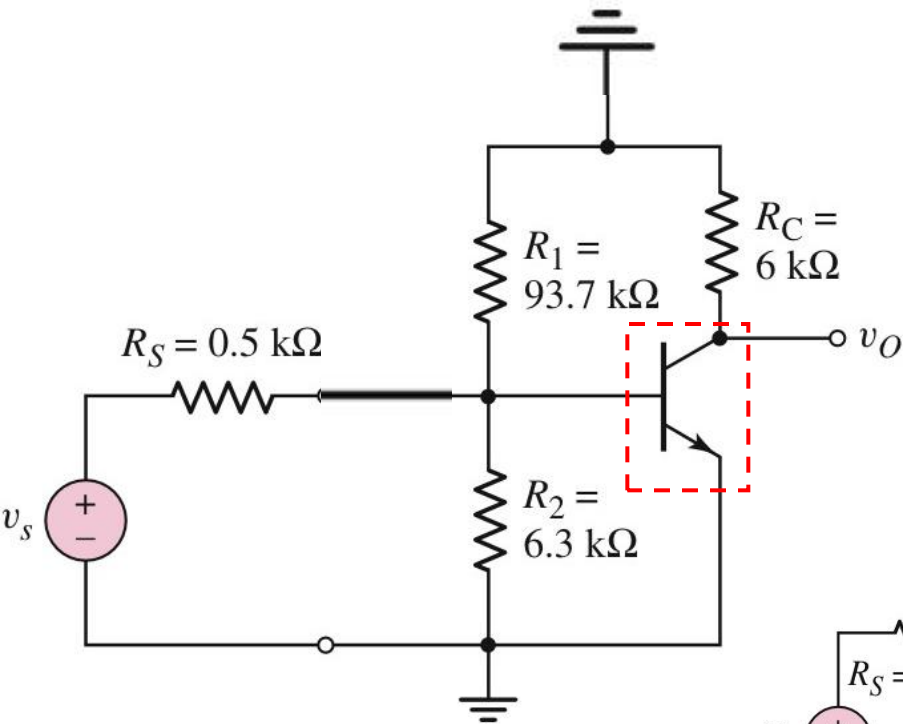

6.4 Common-Emitter Amplifiers

6.4.1 Common-Emitter Amplifier Circuit

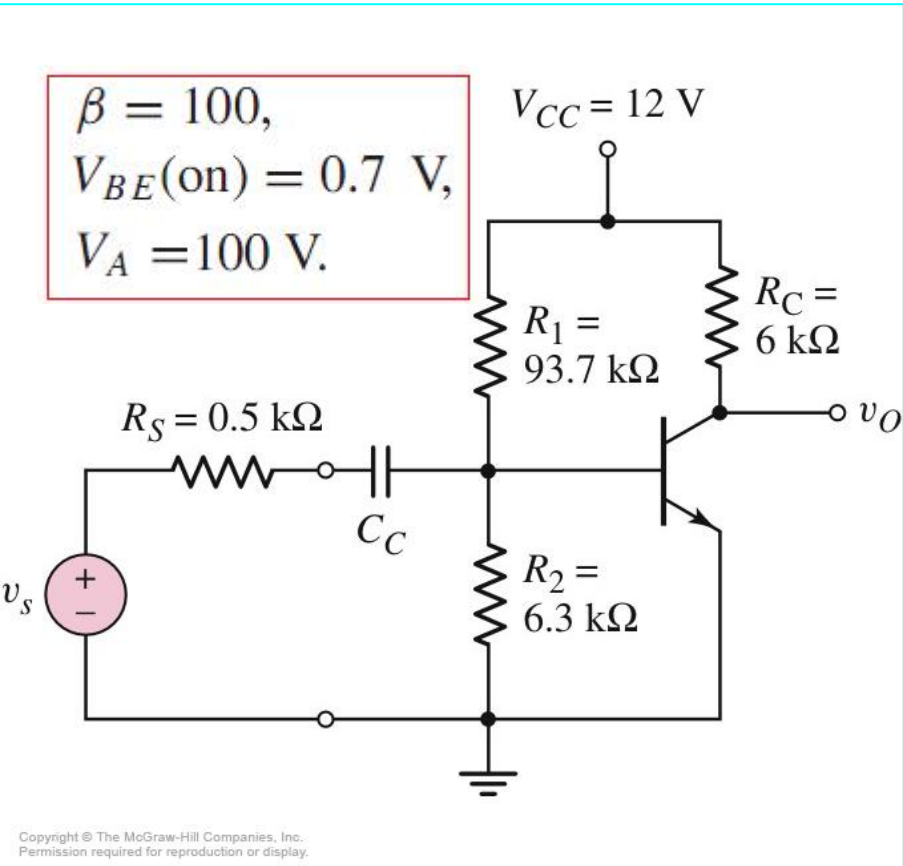

$$I_{CQ} = 0.95 \text{ mA}$$

$$V_{CEQ} = 6.31 \text{ V},$$

forward-active mode

$$r_{\pi} = \frac{V_T \beta}{I_{CQ}} = \frac{(0.026)(100)}{(0.95)} = 2.74 \text{ k}\Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.95}{0.026} = 36.5 \text{ mA/V}$$

$$r_o = \frac{V_A}{I_{CQ}} = \frac{100}{0.95} = 105 \text{ k}\Omega$$


DC Solution:



6.4 Common-Emitter Amplifiers

6.4.1 Common-Emitter Amplifier Circuit

Find $A_{v_s} = v_o/v_s$, R_i , R_o

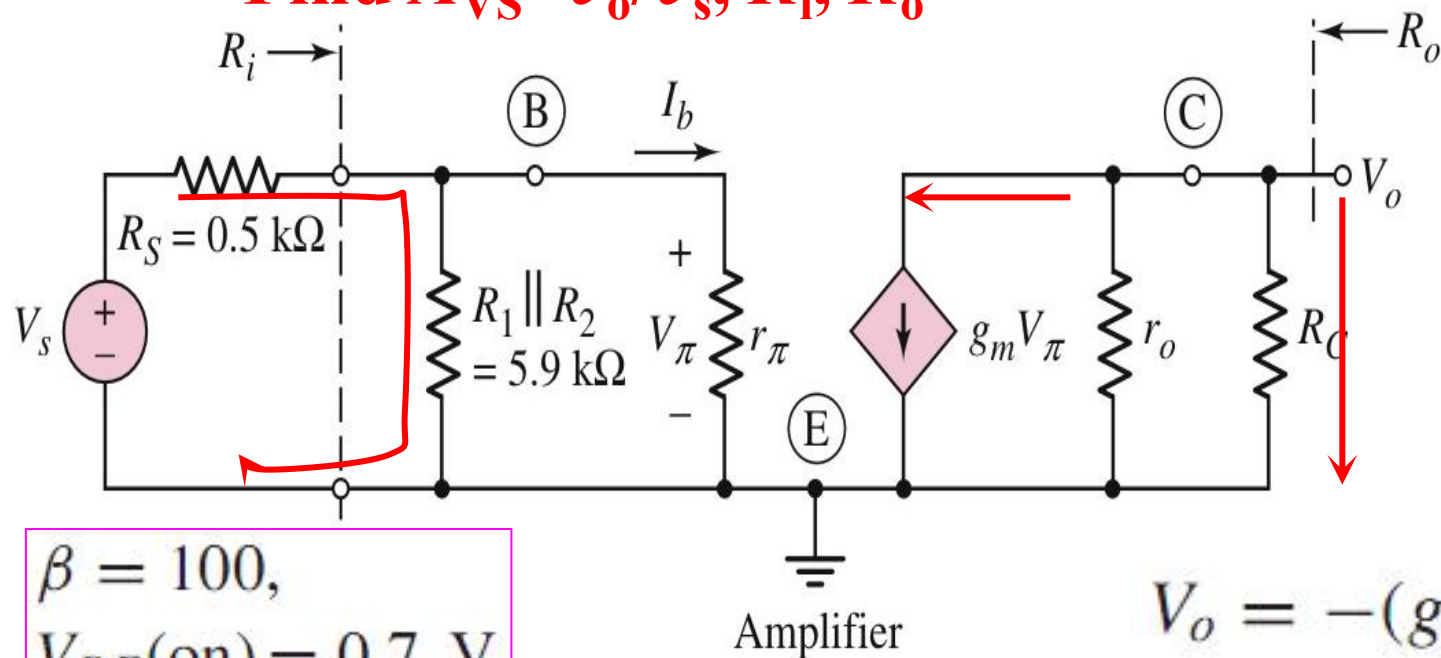


$$\begin{aligned}\beta &= 100, \\ V_{BE(\text{on})} &= 0.7 \text{ V}, \\ V_A &= 100 \text{ V}.\end{aligned}$$

$$V_o = -(g_m V_\pi)(r_o \parallel R_C)$$

$$\begin{aligned}V_\pi &= \left(\frac{R_1 \parallel R_2 \parallel r_\pi}{R_1 \parallel R_2 \parallel r_\pi + R_S} \right) \cdot V_s \\ A_v &= \frac{V_o}{V_s} = -g_m \left(\frac{R_1 \parallel R_2 \parallel r_\pi}{R_1 \parallel R_2 \parallel r_\pi + R_S} \right) (r_o \parallel R_C) \\ &= -163\end{aligned}$$

6.4 Common-Emitter Amplifiers

6.4.1 Common-Emitter Amplifier Circuit

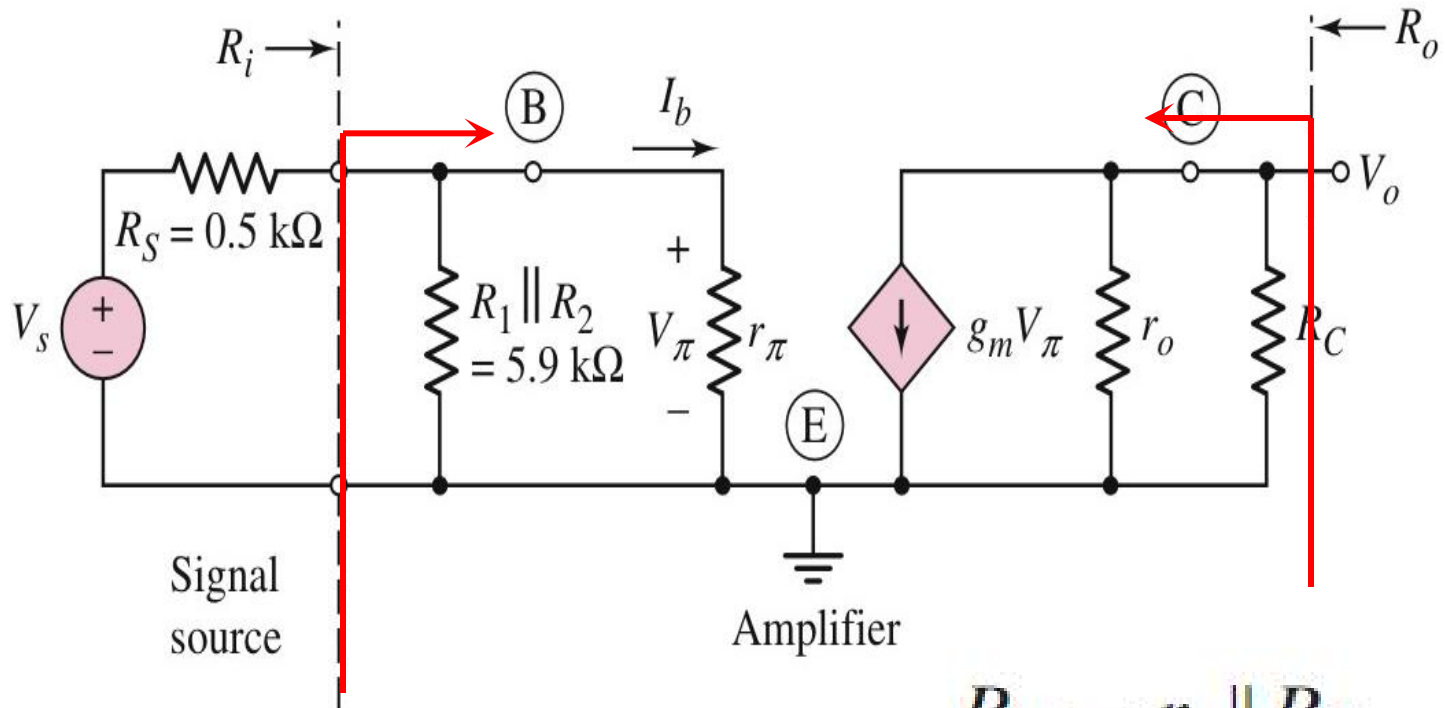


$$R_i = R_1 \parallel R_2 \parallel r_\pi$$
$$= 5.9 \parallel 2.74 = 1.87 \text{ k}\Omega$$


$$R_o = r_o \parallel R_C$$
$$= 105 \parallel 6 = 5.68 \text{ k}\Omega$$

6.4 Common-Emitter Amplifiers

6.4.2 Circuit with Emitter Resistor

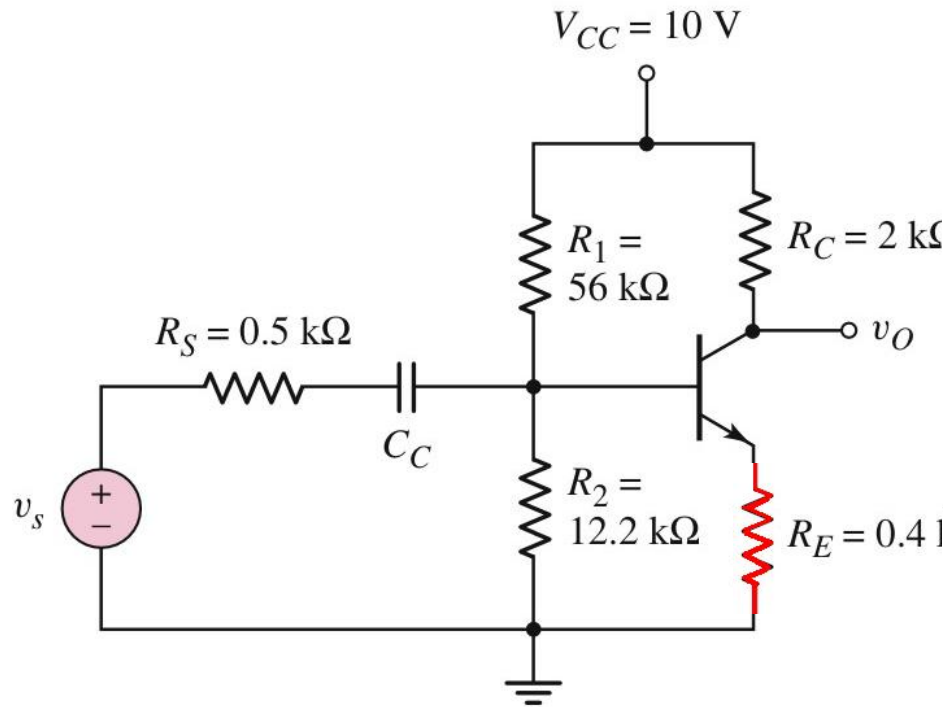

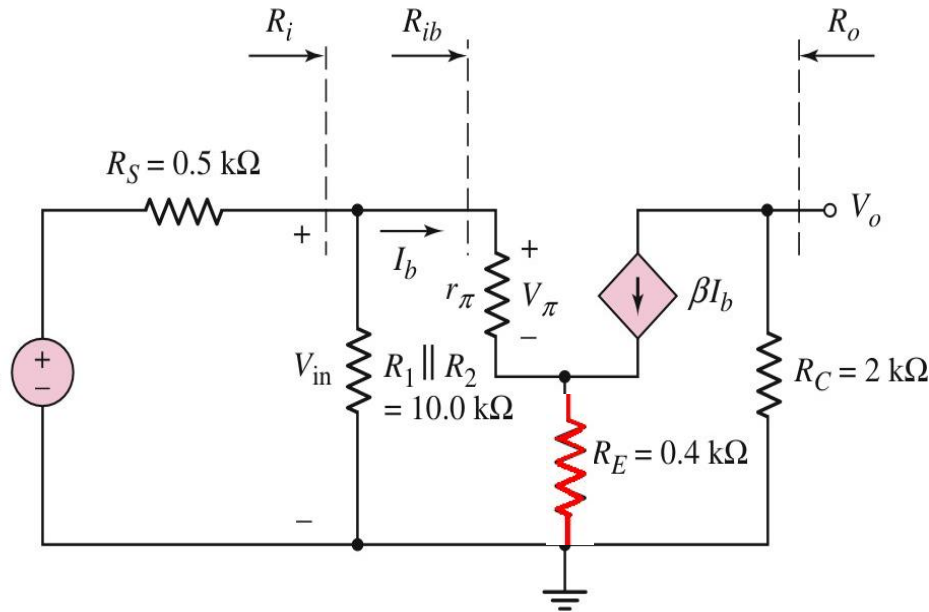Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.


small-signal equivalent circuit

$$A_v = v_o / v_{in}, R_i, R_o$$

Become smaller or larger?

6.4 Common-Emitter Amplifiers

6.4.2 Circuit with Emitter Resistor

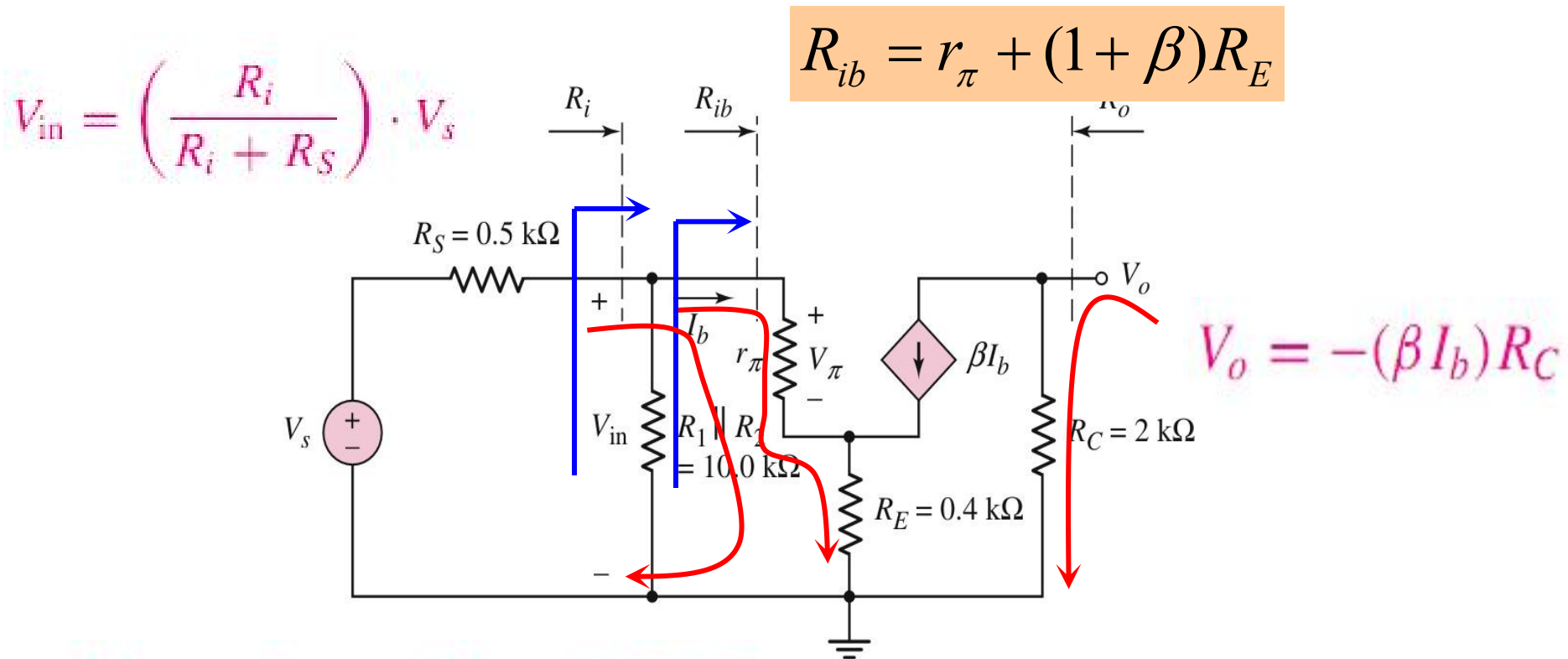

$$V_{in} = I_b r_{\pi} + (I_b + \beta I_b) R_E$$

$$R_i = R_1 \parallel R_2 \parallel R_{ib}$$

$$A_{vS} = \frac{V_o}{V_s}$$

$$= \frac{-\beta R_C}{r_{\pi} + (1 + \beta) R_E} \left(\frac{R_i}{R_i + R_S} \right)$$


6.4 Common-Emitter Amplifiers

6.4.2 Circuit with Emitter Resistor

$$\beta = 100$$

$$V_{BE}(\text{on}) = 0.7 \text{ V}$$

$$V_A = \infty$$

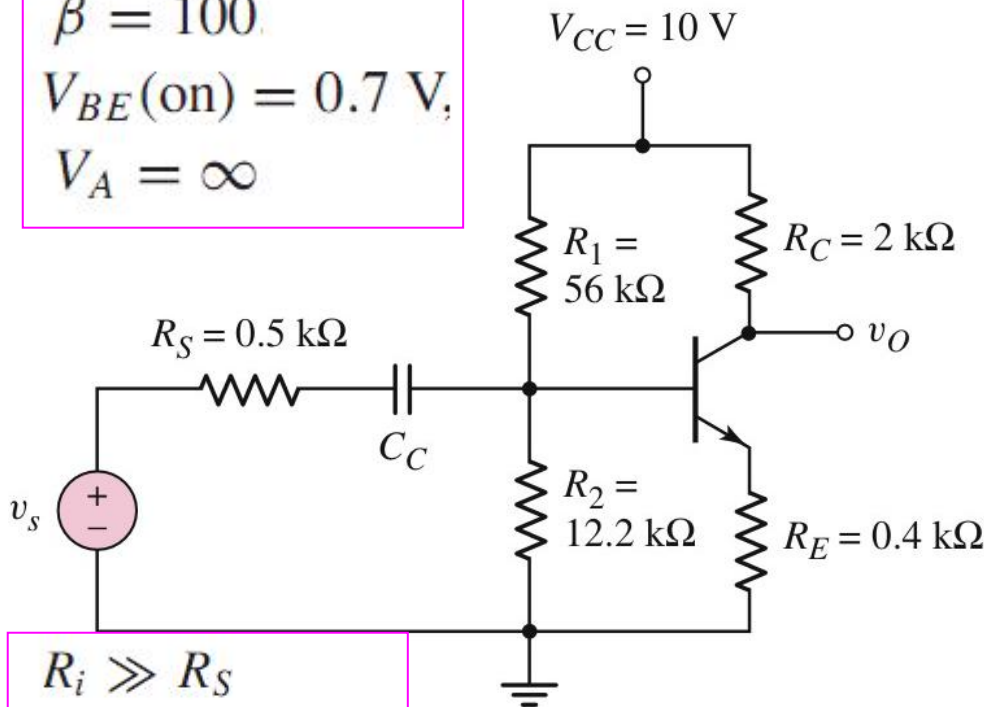

$$R_i \gg R_S$$

$$(1 + \beta)R_E \gg r_\pi$$

Voltage-divider biasing stabilizes Q, but degrades ac voltage gain, how can we improve it?

$$A_{vs} = \frac{-R_C}{R_E} = \frac{-2}{0.4} = -5.0$$



-163

$$A_{vs} = \frac{V_o}{V_s} = \frac{-\beta R_C}{r_\pi + (1 + \beta)R_E} \left(\frac{R_i}{R_i + R_S} \right) = \frac{-R_C}{R_E}$$

$$A_{vs} = -4.53$$

6.4 Common-Emitter Amplifiers


6.4.2 Circuit with Emitter Resistor

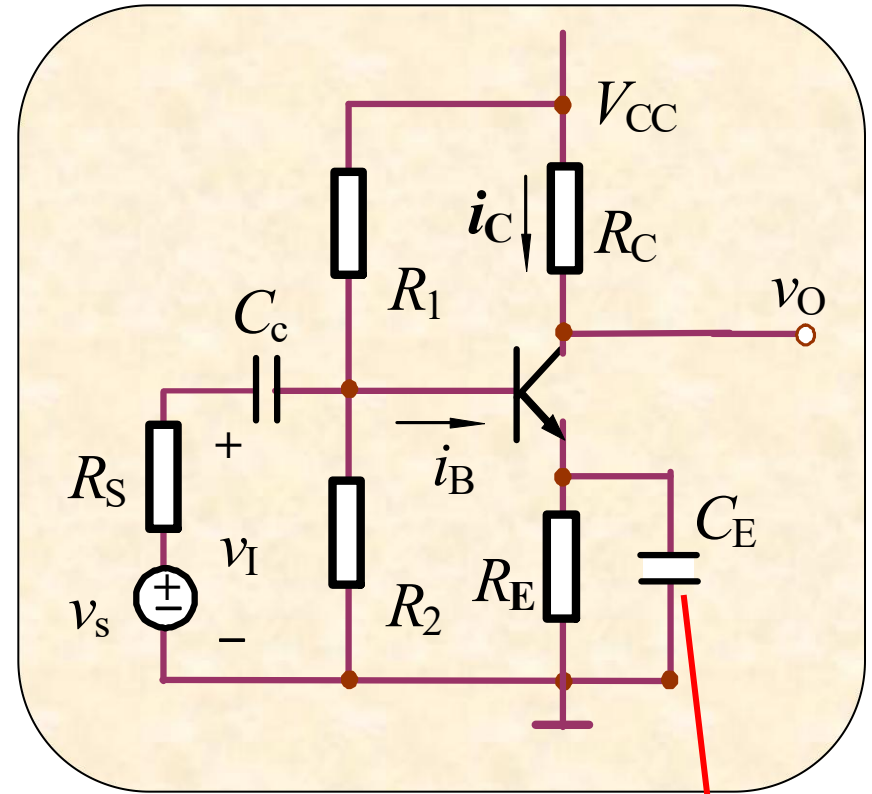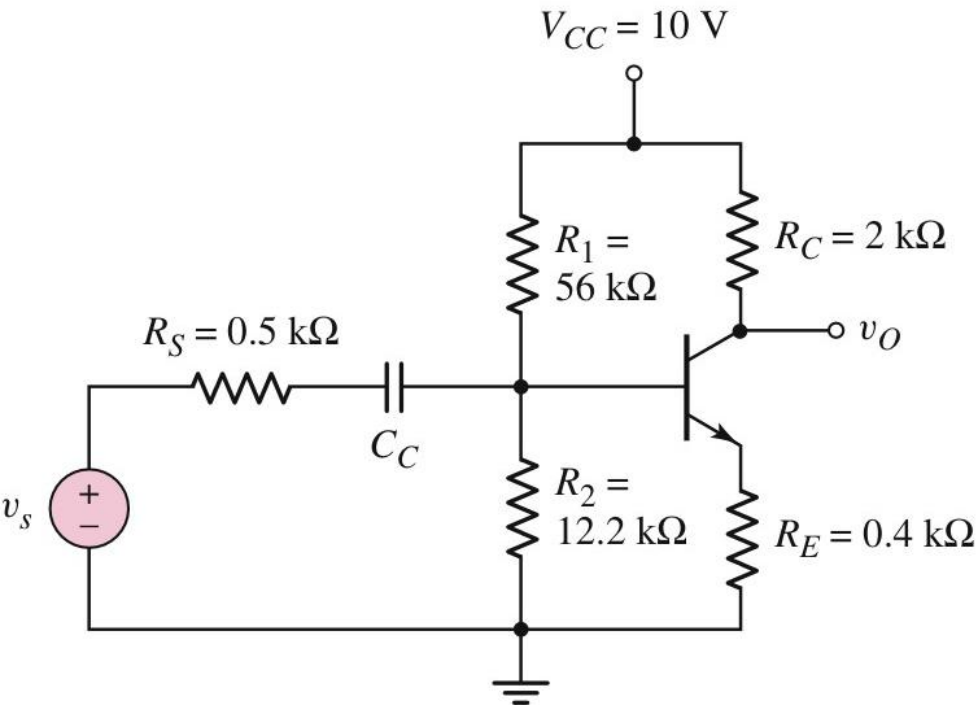

Bypass Capacitor

6.4 Common-Emitter Amplifiers

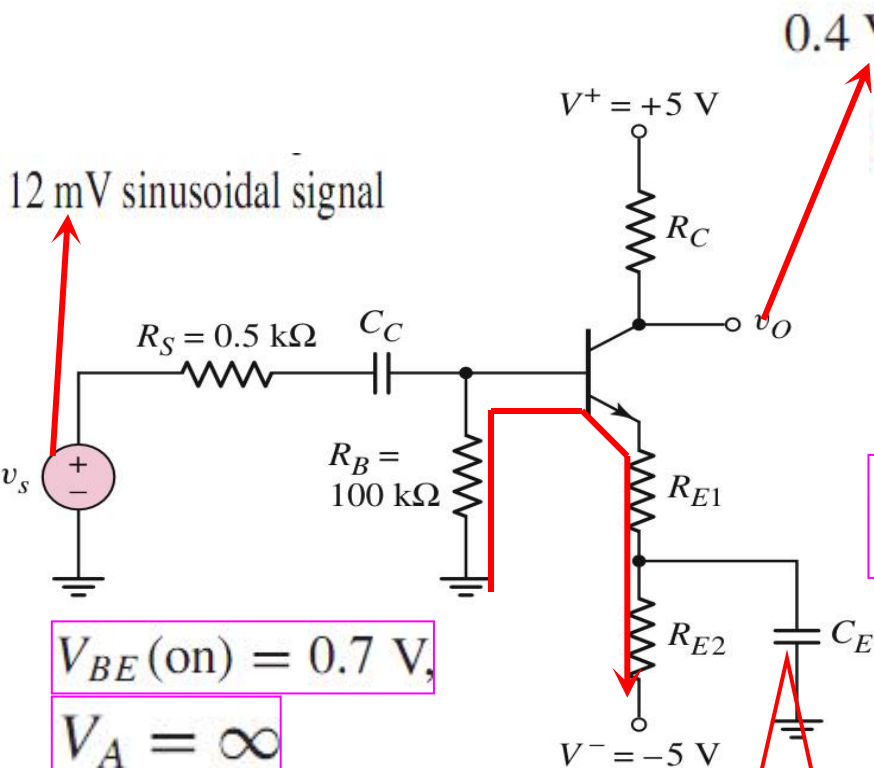6.4.3 Circuit with Emitter Bypass Capacitor



$$V_{BE(\text{on})} = 0.7 \text{ V},$$

$$V_A = \infty$$

$$75 \leq \beta \leq 125$$

$$\beta = 100$$

DC: open
AC: short

Design the bipolar amplifier

$$R_{E2} = 20.3 \text{ k}\Omega$$

Solution

$$|A_v| = \frac{0.4 \text{ V}}{12 \text{ mV}} = 33.3$$

$$|A_v| \cong \frac{R_C}{R_{E1}} \quad \text{set } R_C/R_{E1} = 40$$

$$5 = \underline{I_B} R_B + V_{BE(\text{on})} + I_E (\underline{R_{E1}} + \underline{R_{E2}})$$

$$I_E \cong I_C = 0.20 \text{ mA.}$$

$$R_{E1} + R_{E2} = 20.5 \text{ k}\Omega$$


$$V_{CEQ} = 4 \text{ V}, \quad R_C = 9.5 \text{ k}\Omega$$

$$R_{E1} = \frac{R_C}{40} = \frac{9.5}{40} = 0.238 \text{ k}\Omega$$

6.4 Common-Emitter Amplifiers

6.4.3 Circuit with Emitter Bypass Capacitor

Design the bipolar amplifier

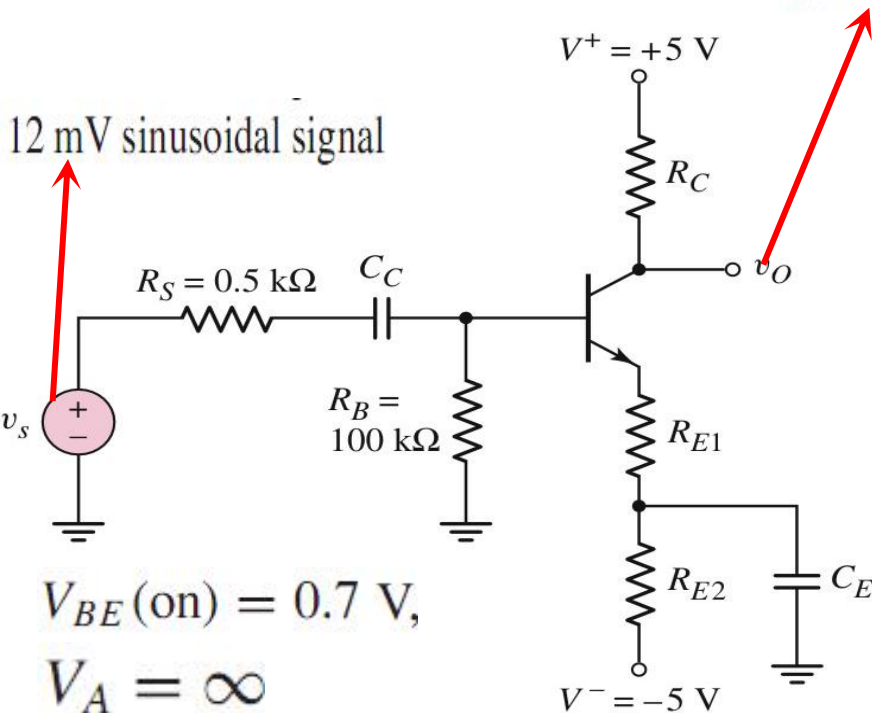

$$V_{BE(\text{on})} = 0.7 \text{ V},$$

$$V_A = \infty$$

$$75 \leq \beta \leq 125$$

$$\beta = 100$$

$$I_E \cong I_C = 0.20 \text{ mA.}$$

$$V_{CEQ} = 4 \text{ V.}$$

$$R_C = 9.5 \text{ k}\Omega$$

$$R_{E1} = \frac{R_C}{40} = \frac{9.5}{40} = 0.238 \text{ k}\Omega$$

$$R_{E2} = 20.3 \text{ k}\Omega$$




pick standard resistor values

$$R_{E1} = 240 \text{ }\Omega$$

$$R_{E2} = 20 \text{ k}\Omega$$

$$R_C = 10 \text{ k}\Omega$$

6.4 Common-Emitter Amplifiers

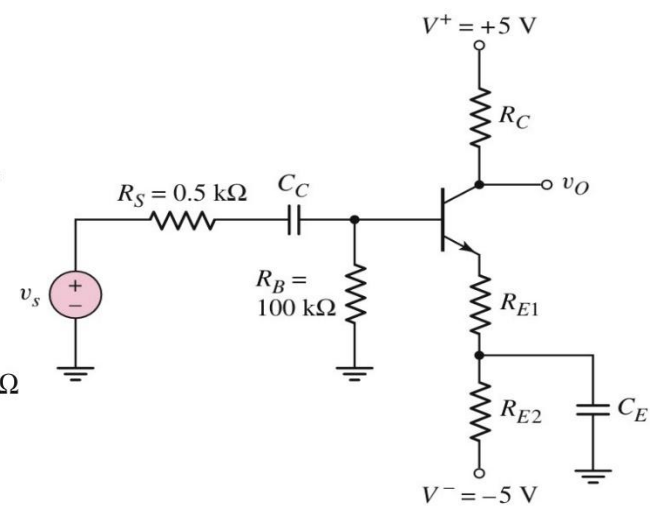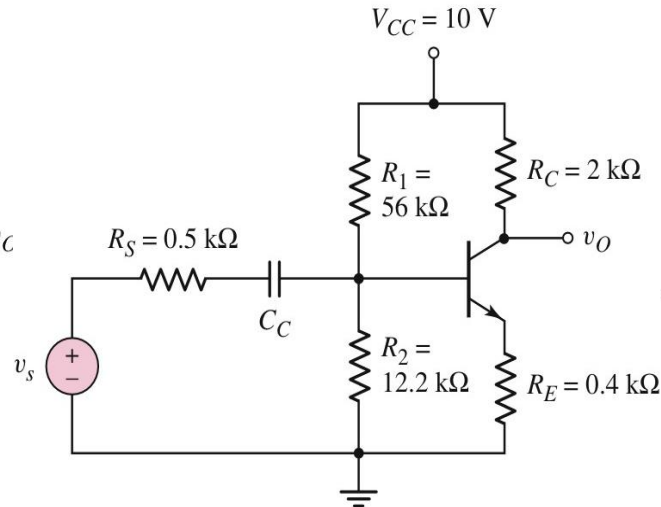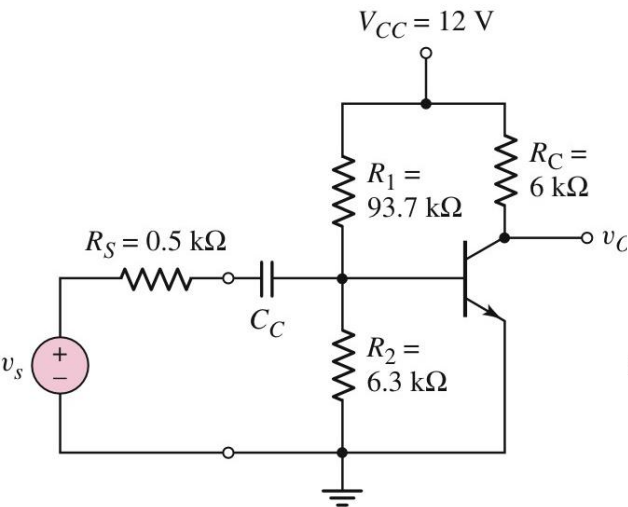

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

**Small Signal
Voltage Gain**

$$-g_m R_C // r_o$$

$$= \frac{-\beta [R_C // r_o]}{r_\pi + (1 + \beta) R_E}$$

$$= \frac{-\beta [R_C // r_o]}{r_\pi + (1 + \beta) R_{E1}}$$

**Input
impedance** $R_1 // R_2 // r_\pi$

$$R_1 // R_2 // [r_\pi + (1 + \beta) R_E]$$


$$R_1 // R_2 // [r_\pi + (1 + \beta) R_{E1}]$$

**Output
impedance**


$$\approx R_c$$

$$\approx R_c$$

$$\approx R_c$$

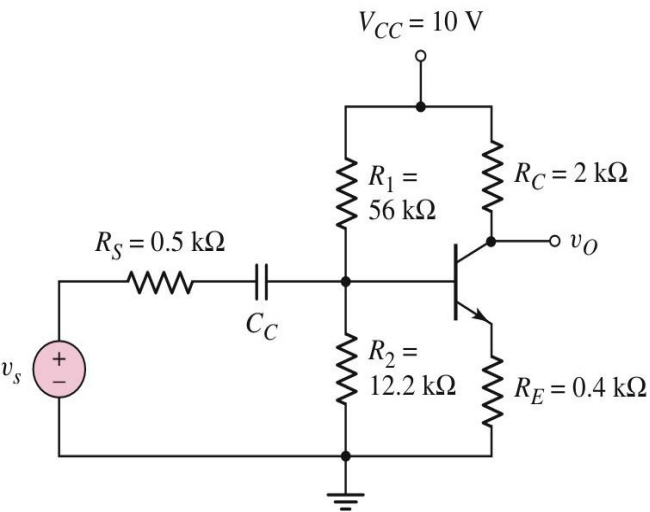


Find R_o

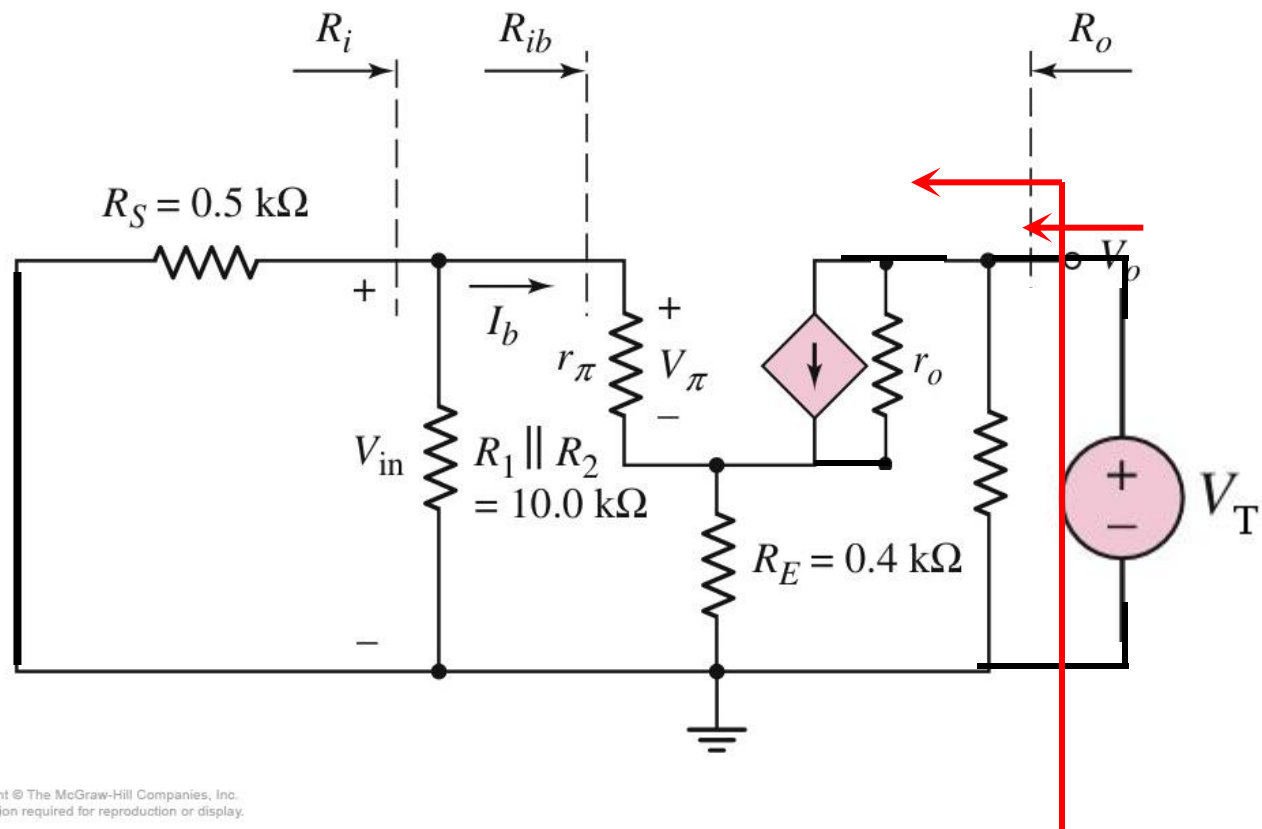



$$R'_o = r_o \left(1 + \frac{\beta \cdot R_E}{r_\pi + R'_s + R_E} \right)$$
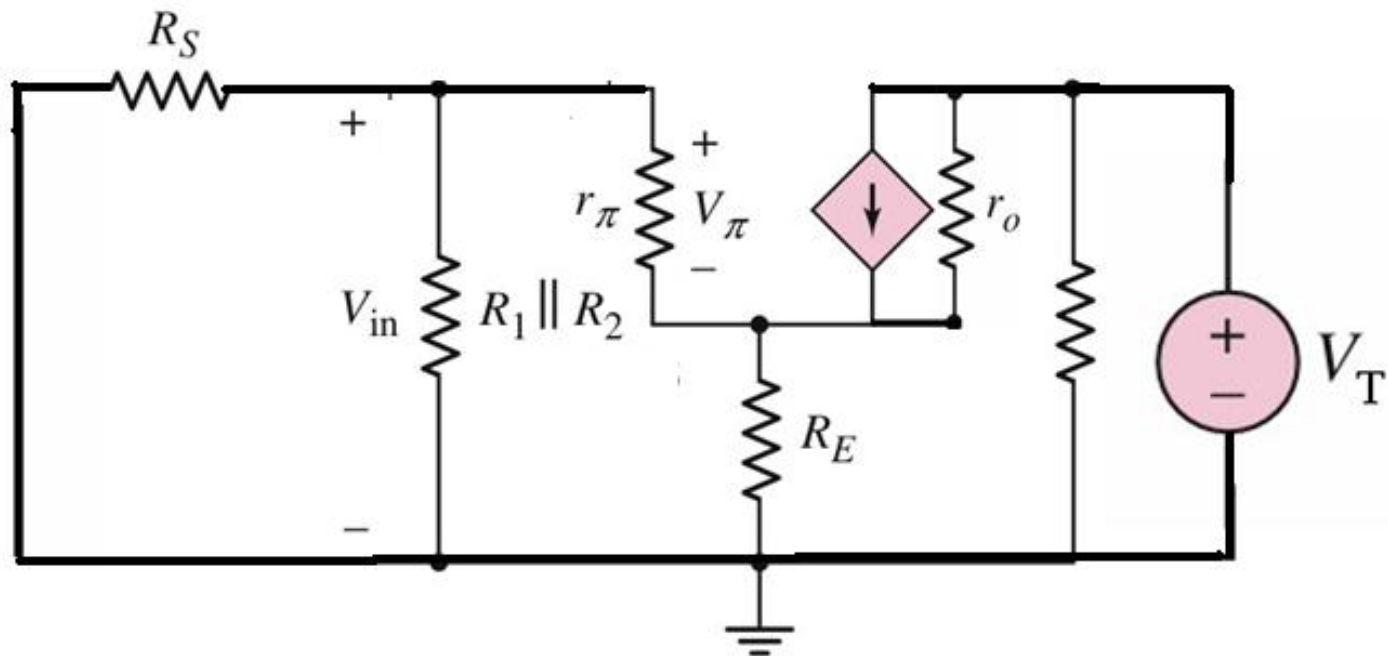
$$\dot{V}_T - (\dot{I}_c - \beta \cdot \dot{I}_b) r_o - (\dot{I}_c + \dot{I}_b) R_E = 0$$



$$R_o = R_c // R'_o$$

$$R'_o = r_o \left(1 + \frac{\beta \cdot R_E}{r_\pi + R'_s + R_E} \right)$$

$$R'_o \gg R_c$$

$$R_o \approx R_c$$


6.4 Common-Emitter Amplifiers

Summary of CE amplifier

- Large voltage gain $-g_m R_C / / r_o$
- Inverting amplifier
- Large current gain $I_C = \beta I_B$
- Input resistance is relatively low. $R_1 || R_2 || r_\pi$
- Output resistance is relatively high. R_C


$$\beta = 50 \quad ,$$

$$V_{BE} = 0.7V;$$

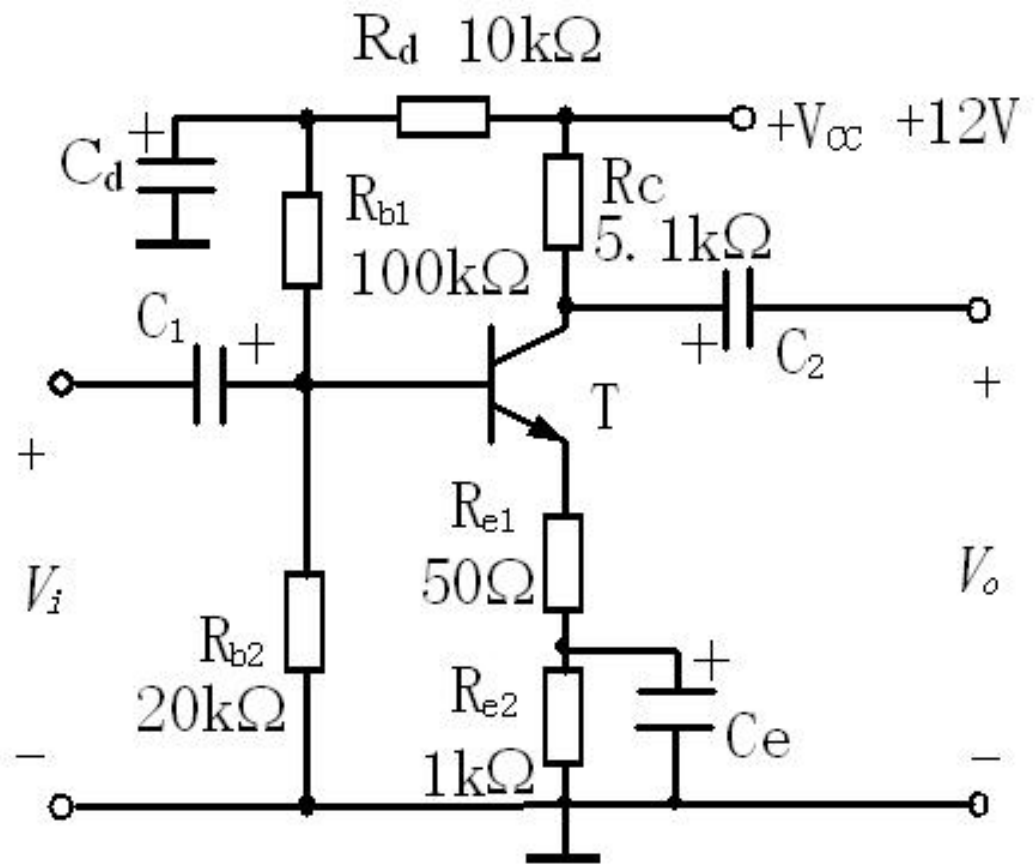

- 1、 Calculate (I_B, I_C, V_{CE}) ;
- 2、 Sketch the small signal equivalent circuit;
- 3、 Find R_i and R_o ;
- 4、 Find $A_v = V_o / V_i$;


DC Solution:

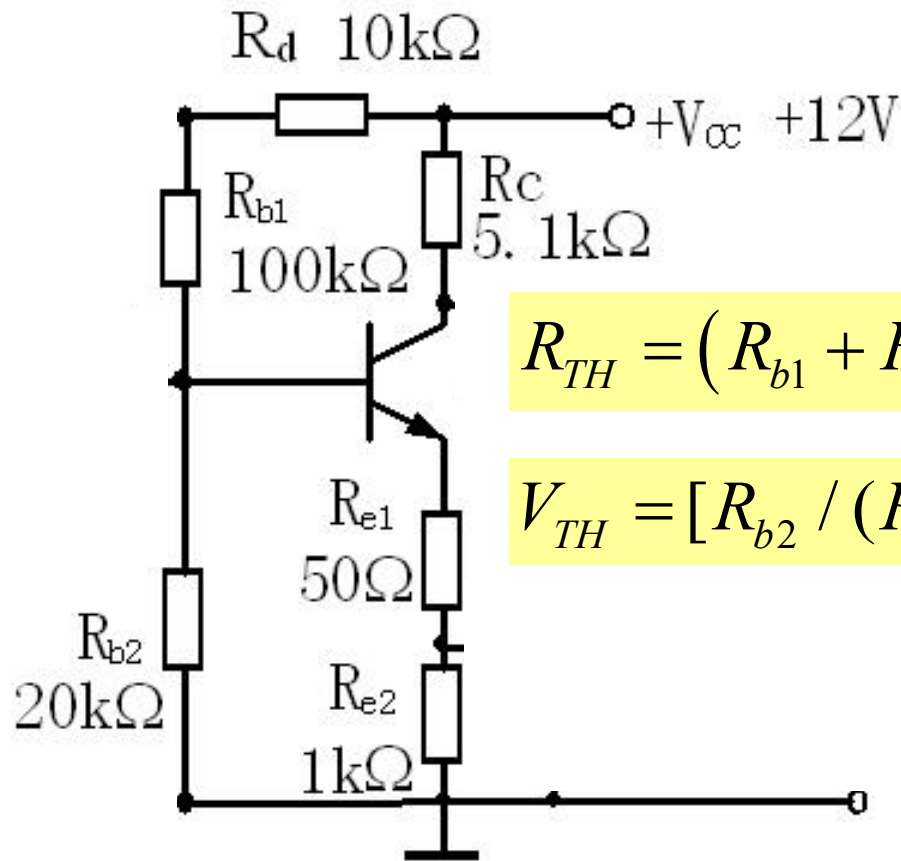


$$R_{TH} = (R_{b1} + R_d) // R_{b2} = 16.9k\Omega$$

$$V_{TH} = [R_{b2} / (R_{b1} + R_{b2} + R_d)] V_{CC}$$

$$= 1.846V$$

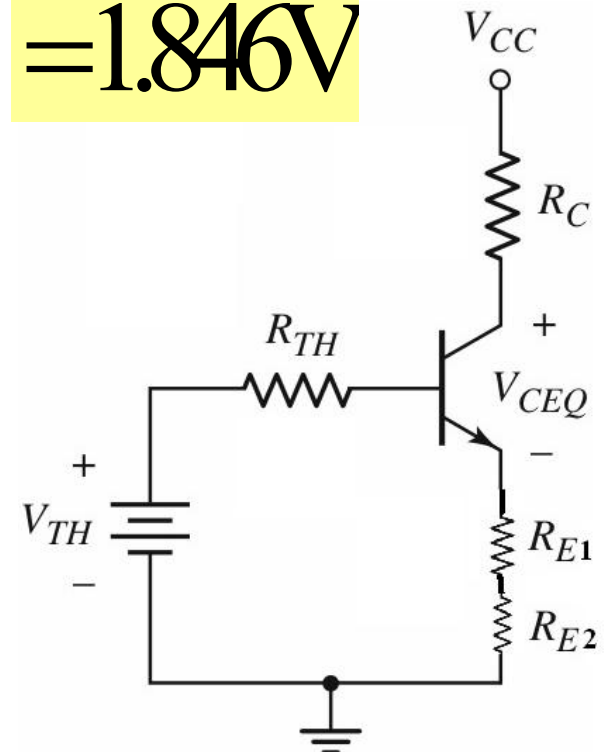

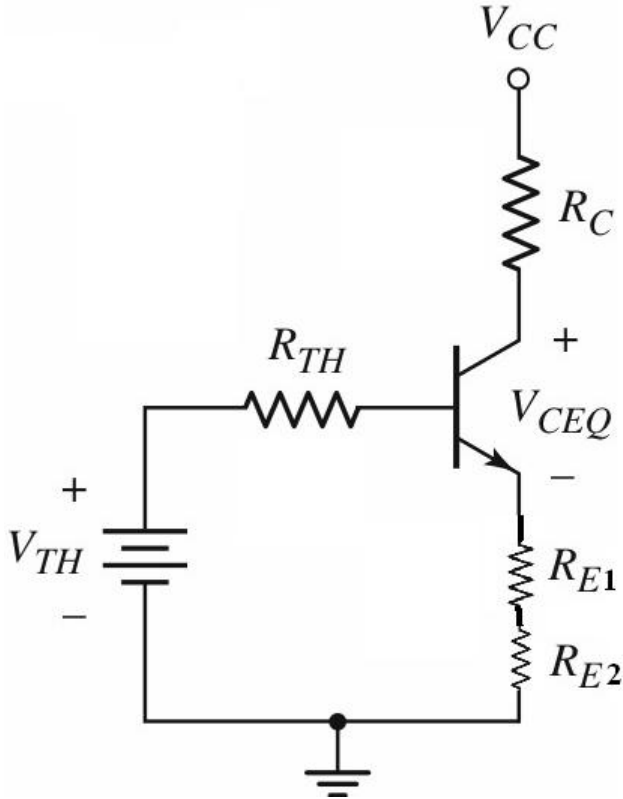

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (1 + \beta)(R_{E1} + R_{E2})}$$

$$= 16 \mu A$$


$$I_C = \beta I_B = 0.8 \text{ mA}$$

$$V_{CEQ} = V_{CC} - I_C R_C - I_E (R_{E1} + R_{E2})$$

$$= V_{CC} - I_C (R_C + R_{E1} + R_{E2})$$

$$= 7.1 \text{ V}$$

AC CIRCUIT

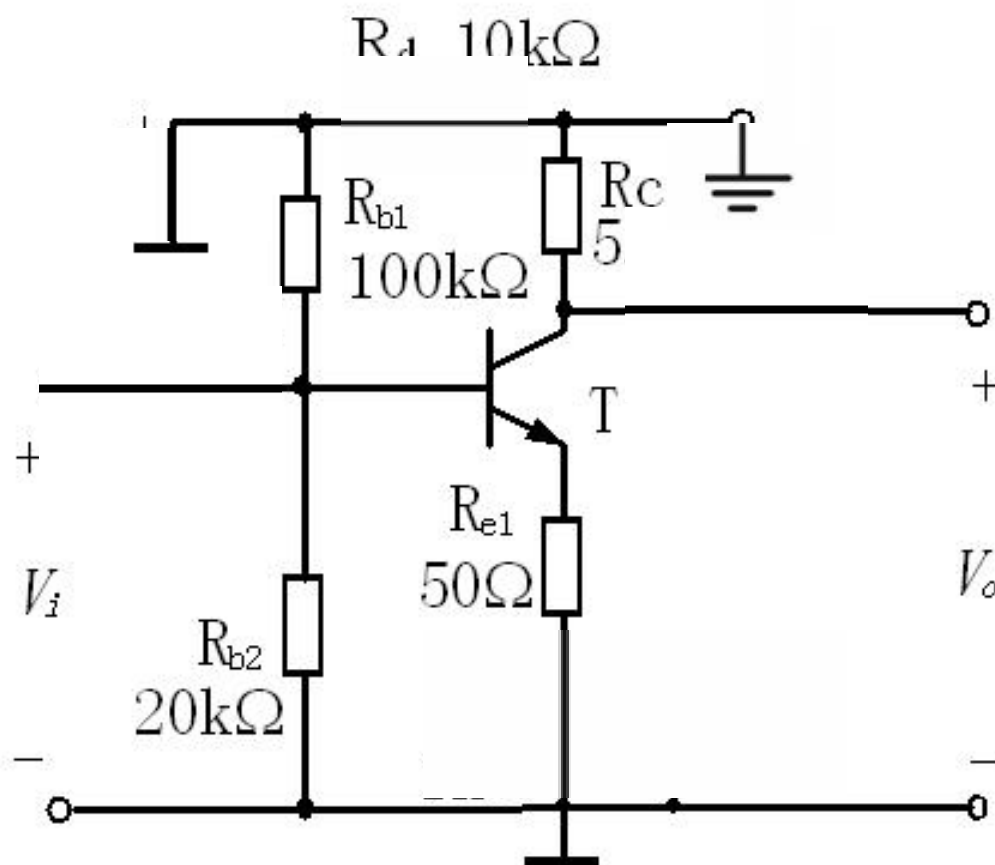

Contents

PART 1 SEMICONDUCTOR DEVICES AND BASIC APPLICATIONS

Chapter 1 Semiconductor Materials and Diodes

Chapter 2 Diode Circuits

Chapter 3 The Field-Effect Transistor

Chapter 4 Basic FET Amplifiers

Chapter 5 The Bipolar Junction Transistor

 **Chapter 6 Basic BJT Amplifiers**

Chapter 7 Frequency Response

Chapter 8 Output Stages and Power Amplifiers

PART 2 ANALOG ELECTRONICS

Chapter 9 Ideal Operational Amplifiers and Op-Amp Circuits

Chapter 10 Integrated Circuit Biasing and Active Loads

Chapter 11 Differential and Multistage Amplifiers

Chapter 12 Feedback and Stability

Chapter 13 Operational Amplifier Circuits

Chapter 14 Nonideal Effects in Operational Amplifier Circuits

Chapter 15 Applications and Design of Integrated Circuits

Ch6. Basic BJT Amplifiers

6.0 Preview

6.1 Analog Signals and Linear Amplifiers

6.2 The Bipolar Linear Amplifier

6.3 Basic Transistor Amplifier Configurations

6.4 Common-Emitter Amplifiers

6.5 AC Load Line Analysis

6.6 Common-Collector (Emitter-Follower) Amplifier

6.7 Common-Base Amplifier


6.8 The Three Basic Amplifiers: Summary and Comparison

6.9 Multistage Amplifiers

6.10 Power Considerations

6.11 Design Application

6.12 Summary

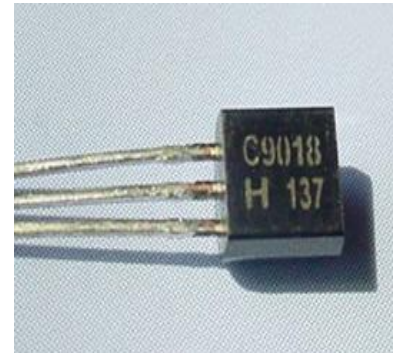


6.5 AC Load line Analysis

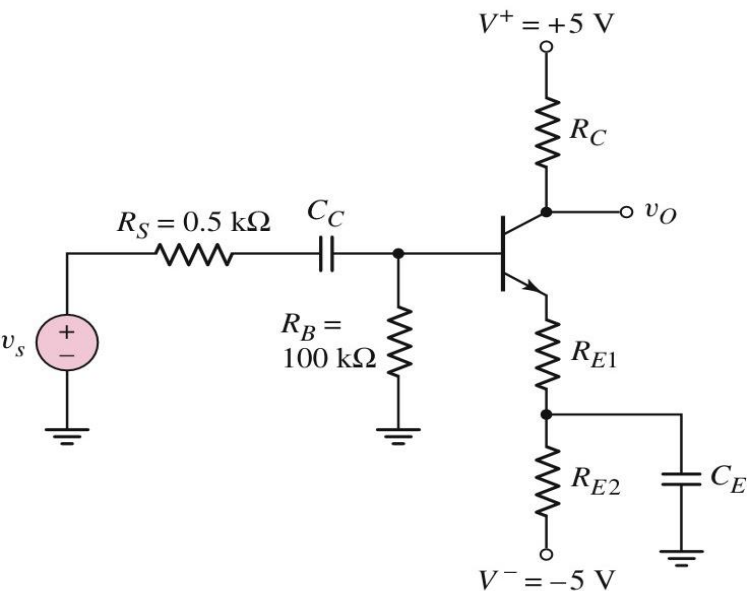
6.5.1 AC load line

Review DC load line

$$V_{CE} = V^+ - (V^-) - I_{EQ}(R_C + R_{E1} + R_{E2})$$


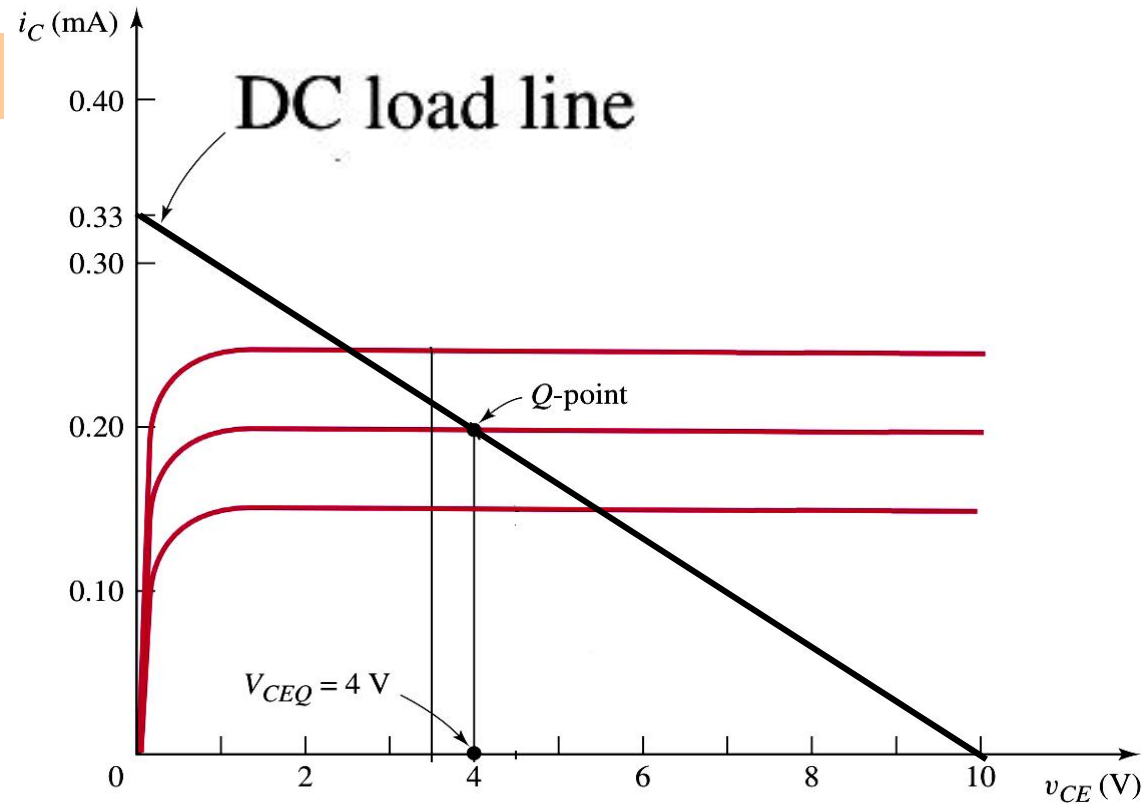
$$\text{slope} \cong \frac{-1}{R_C + R_{E1} + R_{E2}} = \frac{-1}{30.2 \text{ k}\Omega}$$




$$V_{CE} = (V^+ - V^-) - I_C [R_C + (R_{E1} + R_{E2})]$$

6.5 AC Load line Analysis

6.5.1 AC load line

The small-signal equivalent circuit

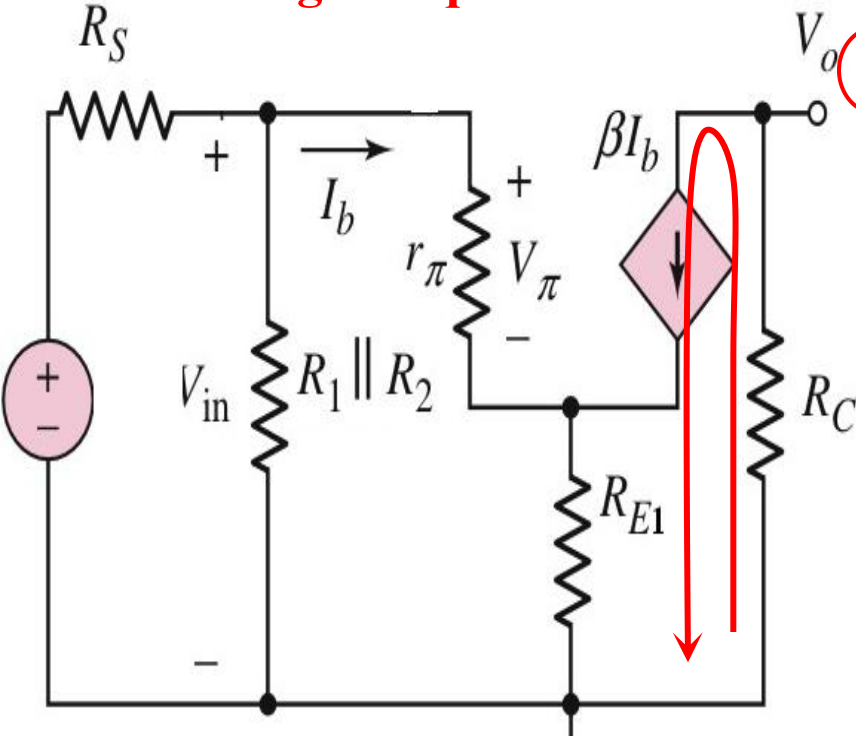


$$i_c R_C + v_{ce} + i_e R_{E1} = 0$$

$$v_{ce} = -i_c (R_C + R_{E1})$$

$$v_{ce} = v_{CE} - V_{CEQ}$$

$$i_c = i_C - I_{CQ}$$
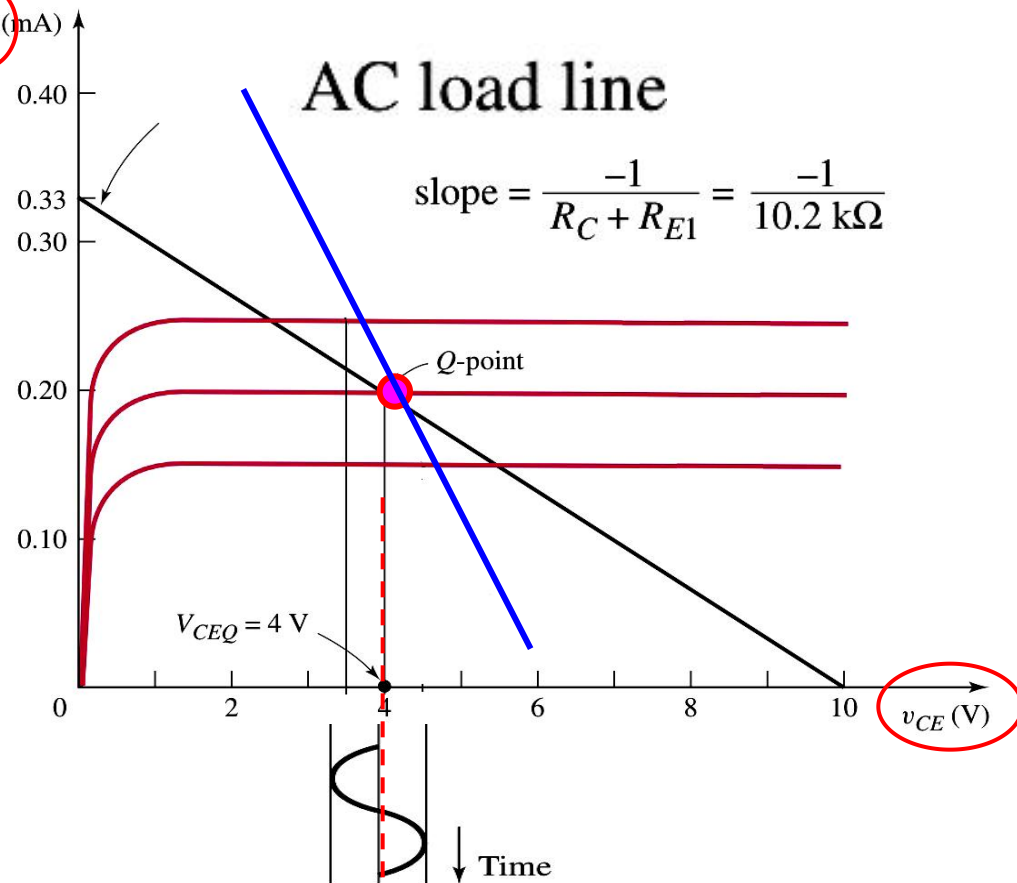
$$\text{Slope} = \frac{-1}{R_C + R_{E1}}$$




$$i_C = [-1/(R_C + R_{E1})] \cdot v_{CE} + [1/(R_C + R_{E1})] V_{CEQ} + I_{CQ}$$


6.5 AC Load line Analysis

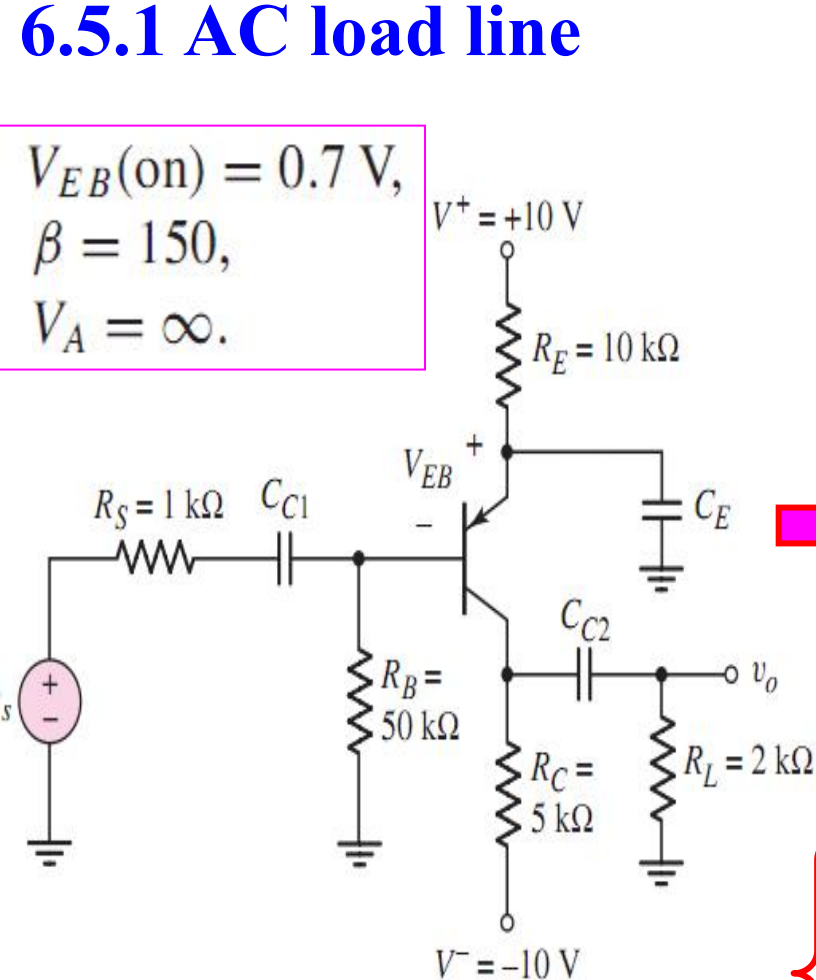6.5.1 AC load line

$$V_{EB(\text{on})} = 0.7 \text{ V},$$
$$\beta = 150,$$
$$V_A = \infty.$$



DC Circuit

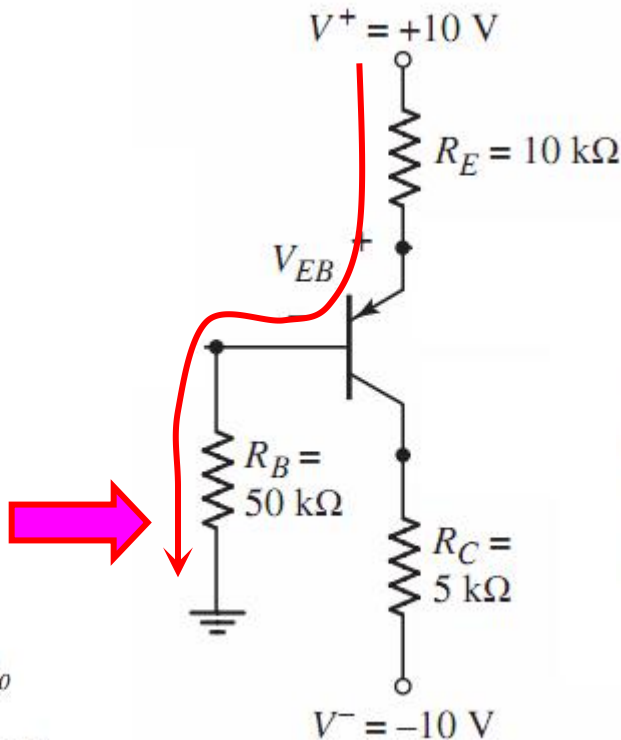

$$I_{BQ} = 5.96 \mu\text{A}$$


$$I_{CQ} = 0.894 \text{ mA}$$

$$V_{ECQ} = 6.53 \text{ V}$$

$$\left\{ \begin{aligned} V^+ &= (1 + \beta) I_{BQ} R_E + V_{EB(\text{on})} + I_{BQ} R_B \\ I_{CQ} &= \beta I_{BQ} \\ V_{ECQ} &= (V^+ - V^-) - I_{CQ} R_C - I_{EQ} R_E \end{aligned} \right.$$

6.5 AC Load line Analysis


6.5.1 AC load line

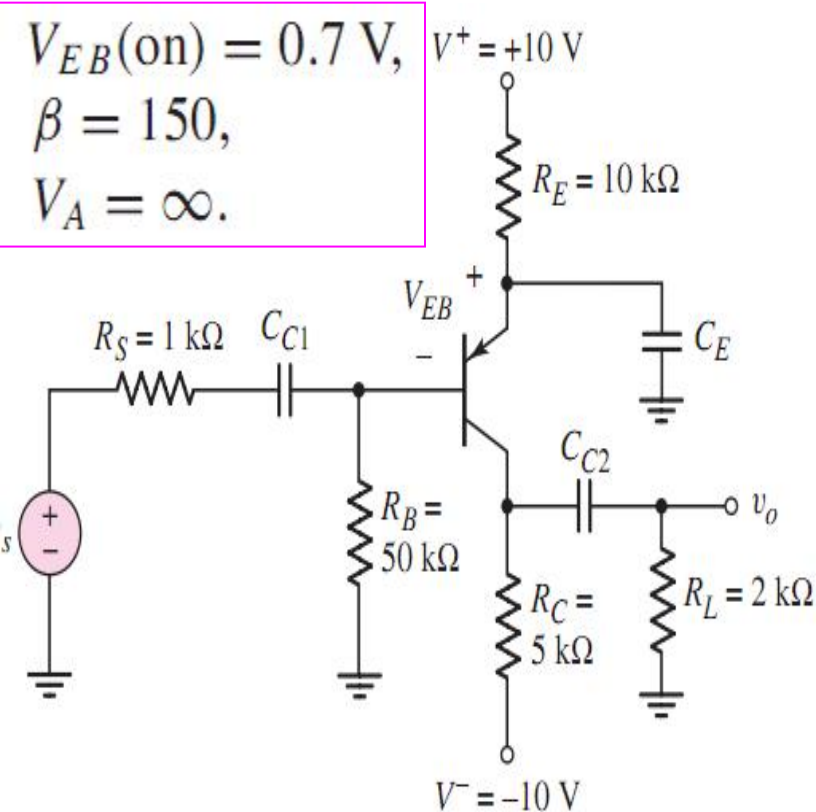

$$I_{BQ} = 5.96 \mu\text{A}$$



$$I_{CQ} = 0.894 \text{ mA}$$

$$V_{ECQ} = 6.53 \text{ V}$$

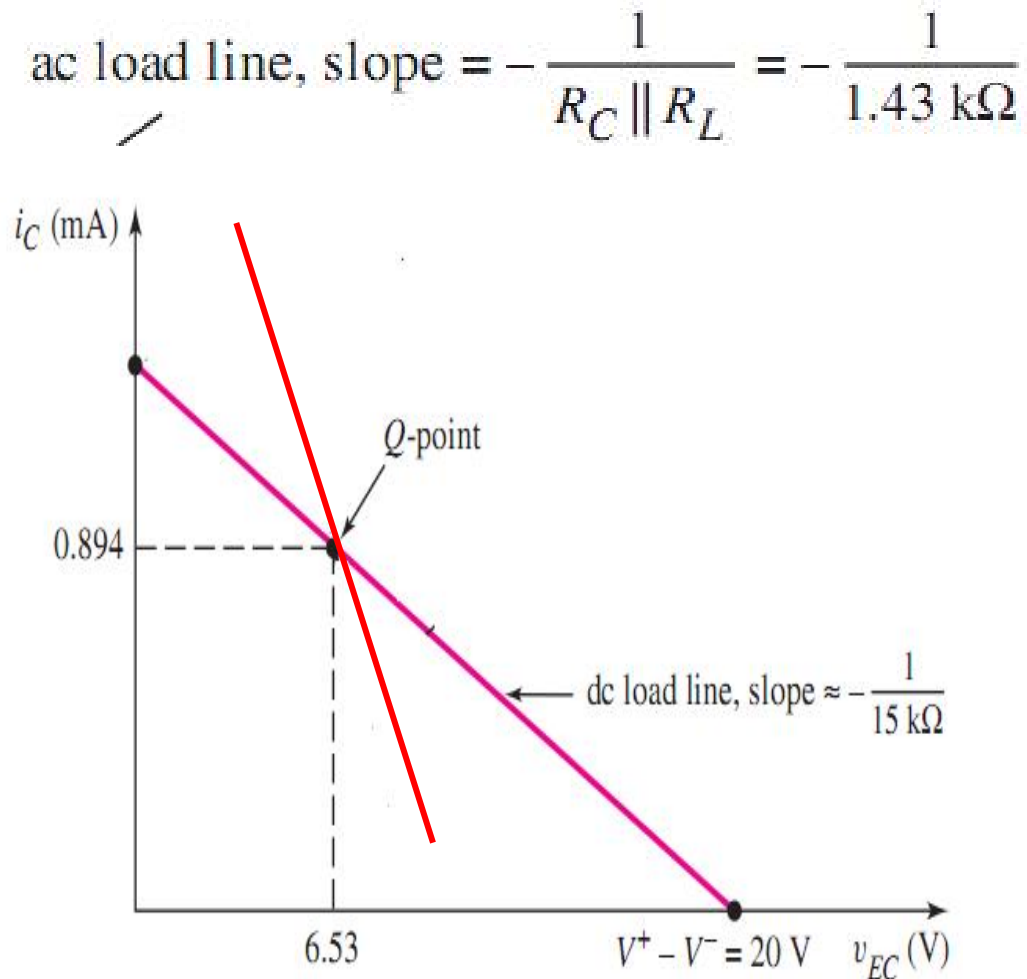


6.5 AC Load line Analysis

6.5.1 AC load line

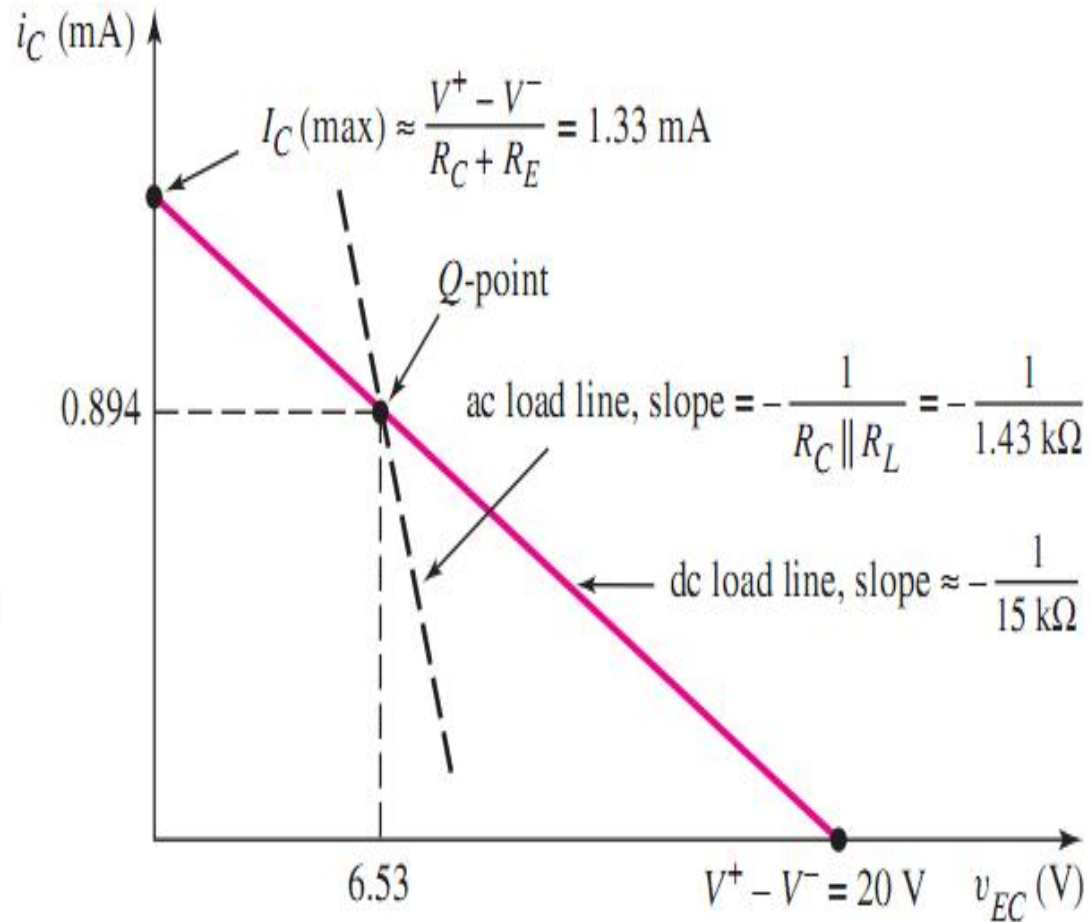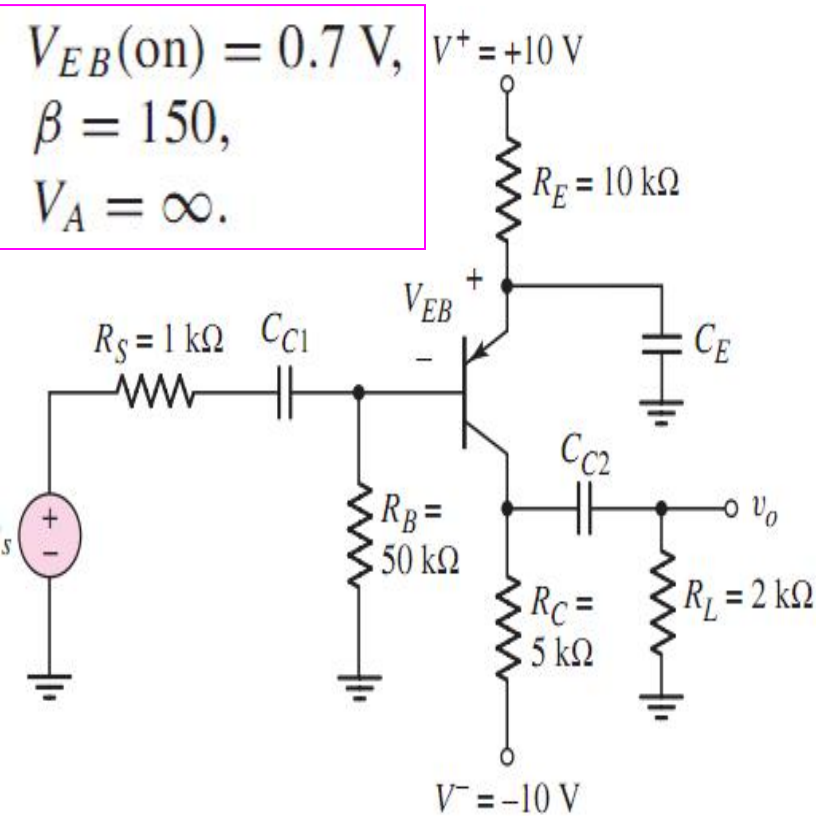

6.5 AC Load line Analysis

6.5.2 Maximum Symmetrical Swing

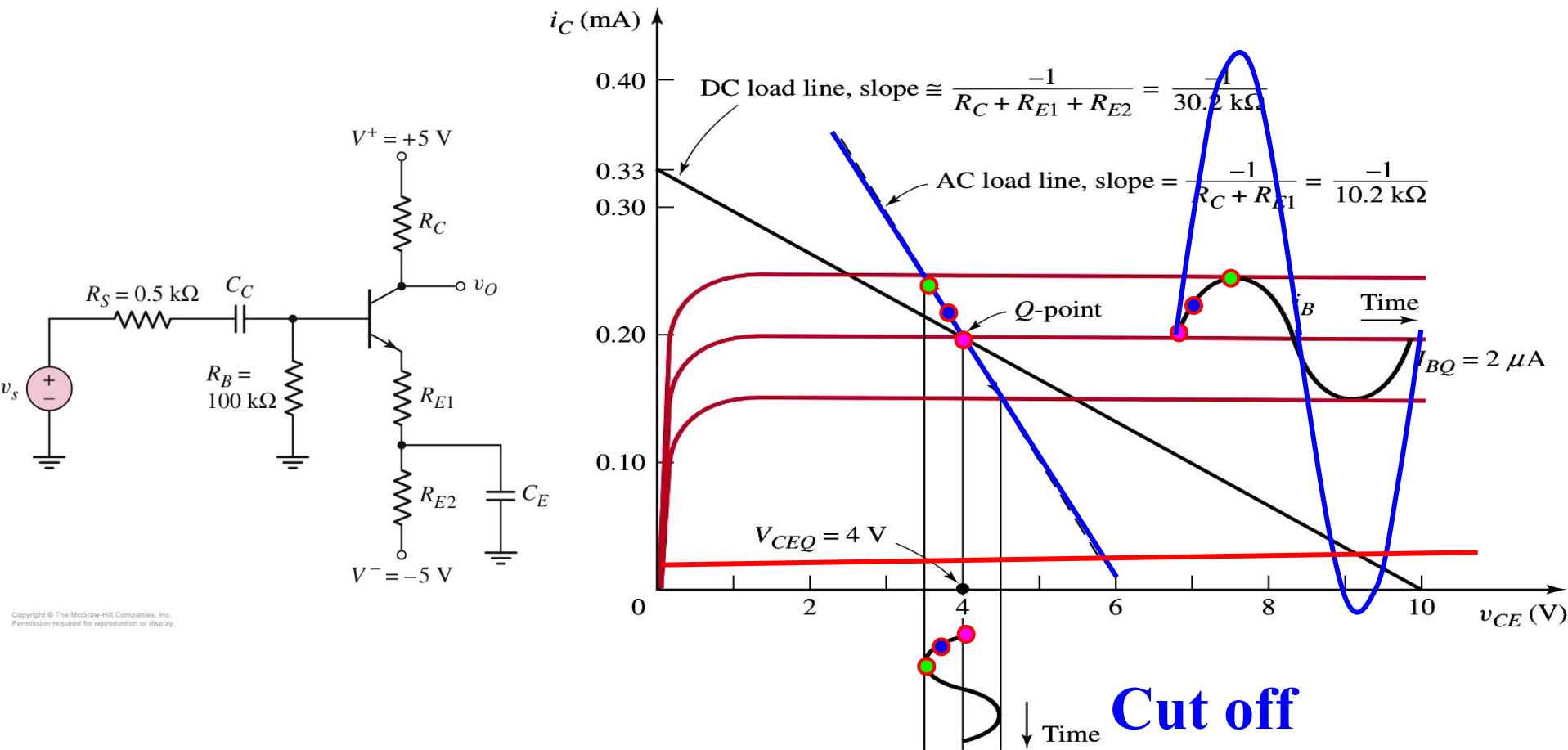

Maximum Symmetrical Swing

6.5 AC Load line Analysis

6.5.2 Maximum Symmetrical Swing


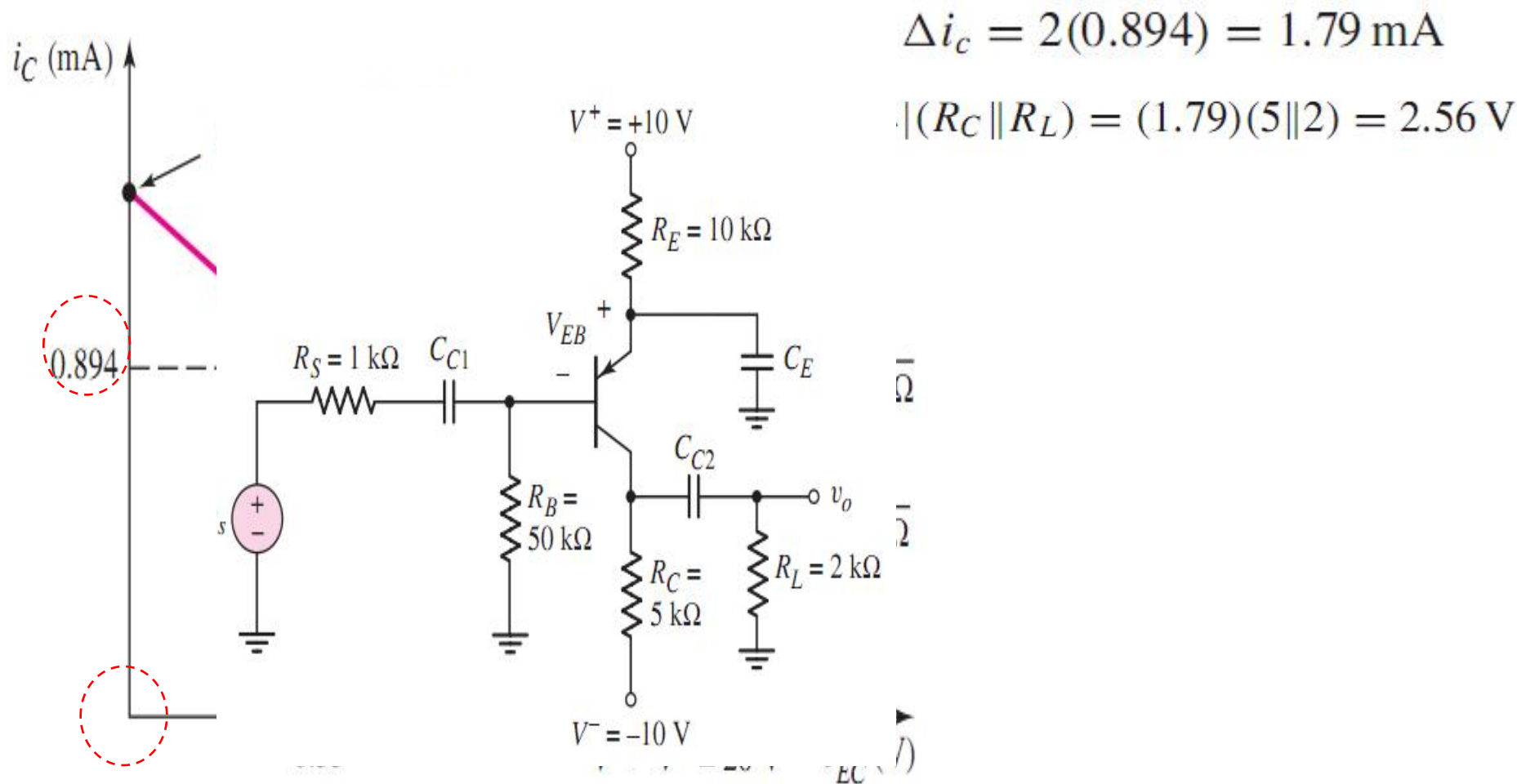


Figure 6.46

$$i_C = I_{CQ} + \frac{1}{2} |\Delta i_C| = 0.894 + 0.894 = 1.79 \text{ mA}$$

The max of v_o

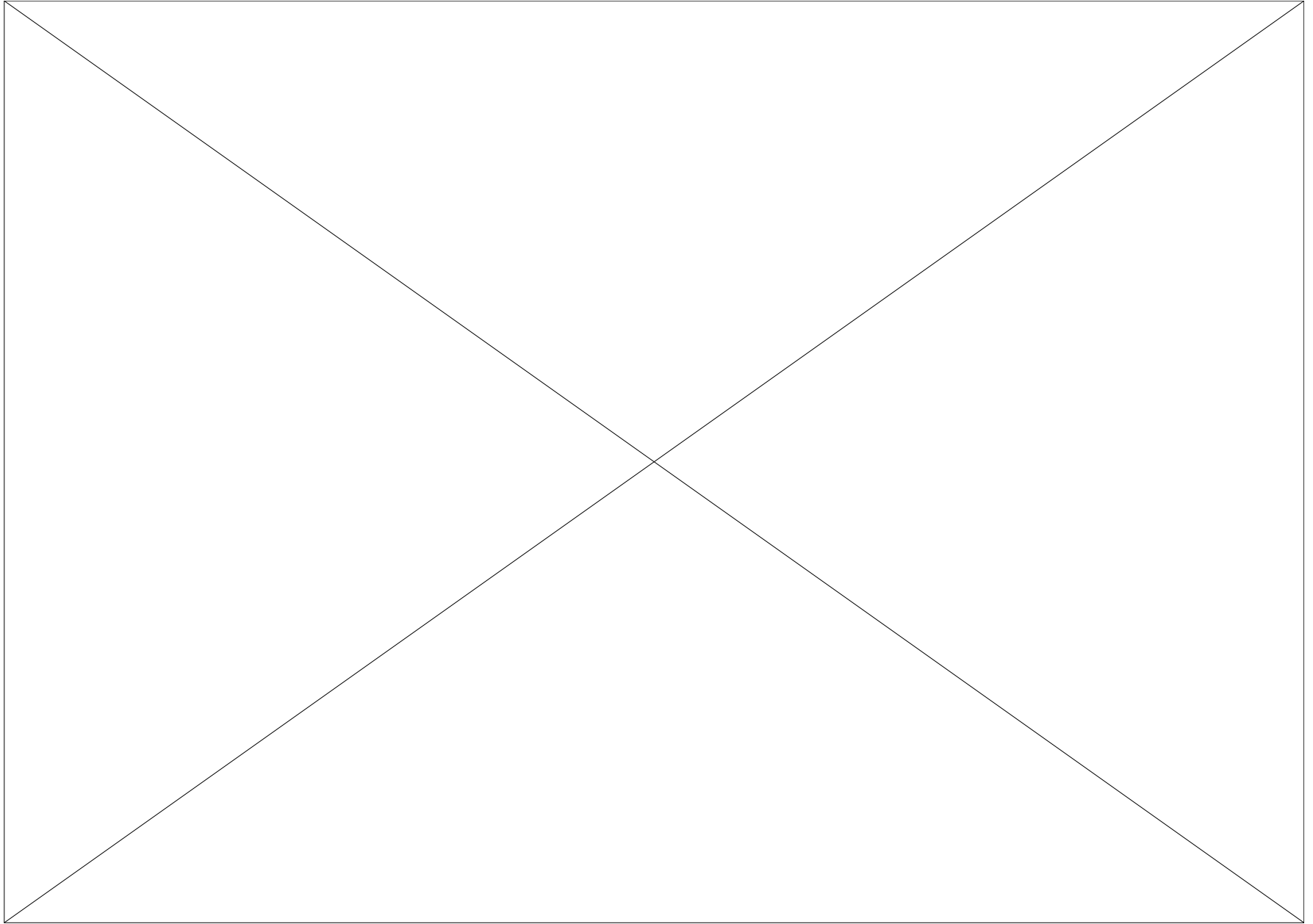

6.5 AC Load line Analysis

6.5.2 Maximum Symmetrical Swing

Problem-Solving Technique: Maximum Symmetrical Swing

1. Write dc load line equation that relates I_{CQ} and V_{CEQ} .
2. Write ac load line equations that relates i_c and v_{ce}
3. In general, $i_c = I_{CQ} - I_C(\min)$, where $I_C(\min)$ is zero or other minimum collector current.
4. In general, $v_{ce} = V_{CEQ} - V_{CE}(\min)$, where $V_{CE}(\min)$ is some specified minimum collector-emitter voltage.
5. Combine above 4 equations to find optimum I_{CQ} and V_{CEQ} .

Contents

PART 1 SEMICONDUCTOR DEVICES AND BASIC APPLICATIONS

Chapter 1 Semiconductor Materials and Diodes

Chapter 2 Diode Circuits

Chapter 3 The Field-Effect Transistor

Chapter 4 Basic FET Amplifiers

Chapter 5 The Bipolar Junction Transistor

 **Chapter 6 Basic BJT Amplifiers**

Chapter 7 Frequency Response

Chapter 8 Output Stages and Power Amplifiers

PART 2 ANALOG ELECTRONICS

Chapter 9 Ideal Operational Amplifiers and Op-Amp Circuits

Chapter 10 Integrated Circuit Biasing and Active Loads

Chapter 11 Differential and Multistage Amplifiers

Chapter 12 Feedback and Stability

Chapter 13 Operational Amplifier Circuits

Chapter 14 Nonideal Effects in Operational Amplifier Circuits

Chapter 15 Applications and Design of Integrated Circuits

Ch6. Basic BJT Amplifiers

6.0 Preview

6.1 Analog Signals and Linear Amplifiers

6.2 The Bipolar Linear Amplifier

6.3 Basic Transistor Amplifier Configurations

6.4 Common-Emitter Amplifiers

6.5 AC Load Line Analysis

6.6 Common-Collector (Emitter-Follower) Amplifier

6.7 Common-Base Amplifier


6.8 The Three Basic Amplifiers: Summary and Comparison

6.9 Multistage Amplifiers

6.10 Power Considerations


6.11 Design Application

6.12 Summary

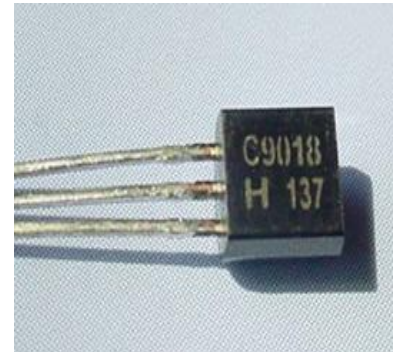

6.6 Common-Collector (Emitter-Follower) Amplifier

6.6.1 Small signal voltage gain

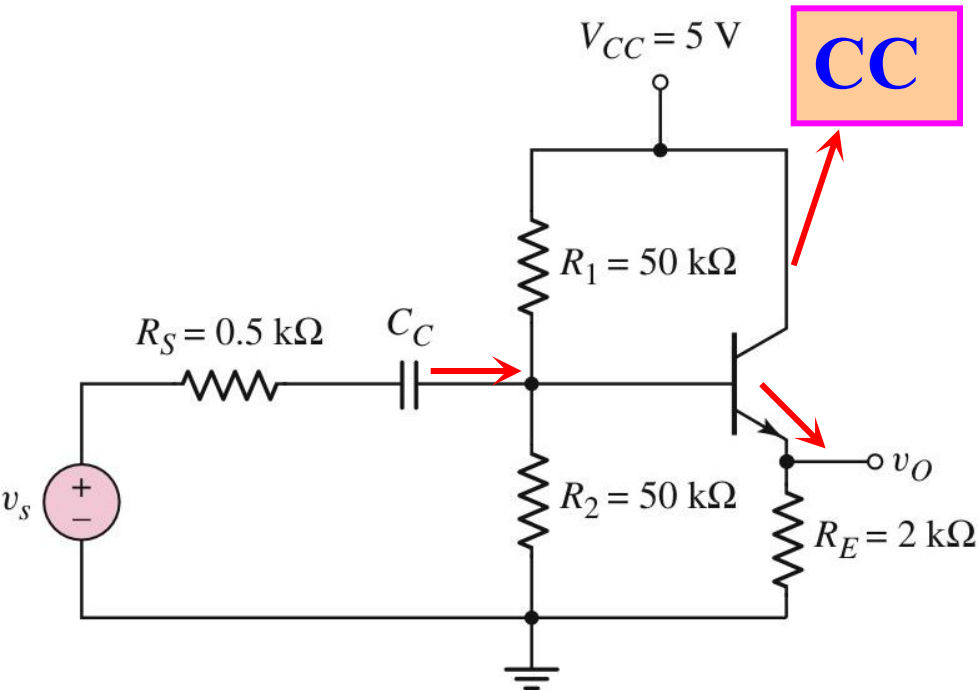


Small-signal equivalent circuit

Emitter-Follower



6.6 Common-Collector (Emitter-Follower) Amplifier

6.6.1 Small signal voltage gain

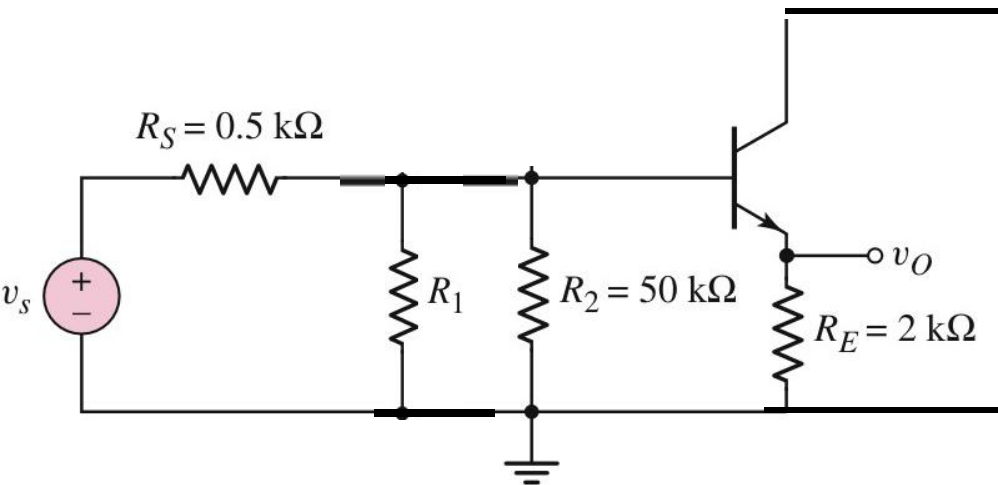


6.6 Common-Collector (Emitter-Follower) Amplifier

6.6.1 Small signal voltage gain

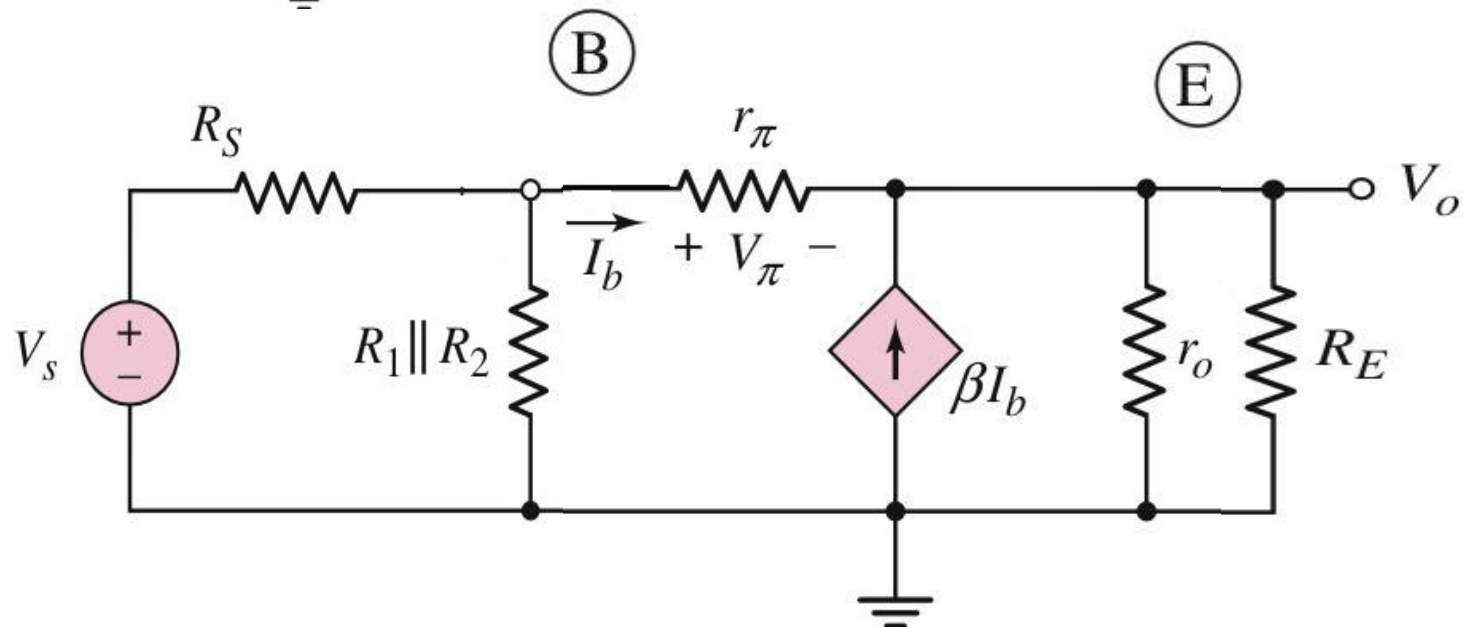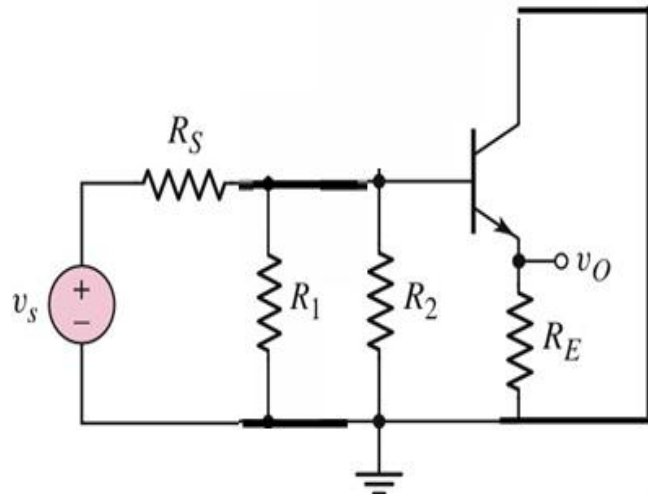

6.6 Common-Collector (Emitter-Follower) Amplifier

6.6.1 Small signal voltage gain

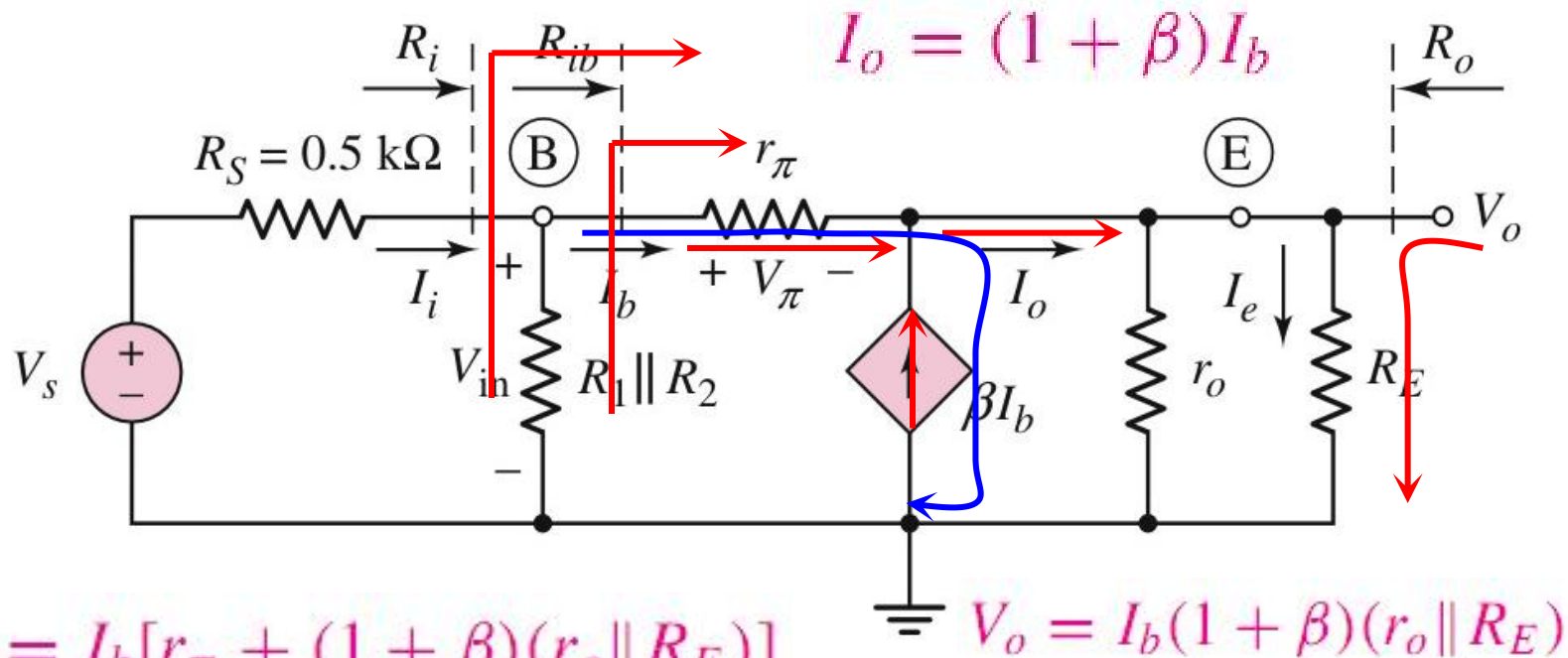


$$V_{in} = I_b [r_\pi + (1 + \beta)(r_o \parallel R_E)]$$

$$R_{ib} = \frac{V_{in}}{I_b} = r_\pi + (1 + \beta)(r_o \parallel R_E)$$

$$R_i = R_1 \parallel R_2 \parallel R_{ib} \quad V_{in} = \left(\frac{R_i}{R_i + R_S} \right) \cdot V_s$$

6.6 Common-Collector (Emitter-Follower) Amplifier

6.6.1 Small signal voltage gain

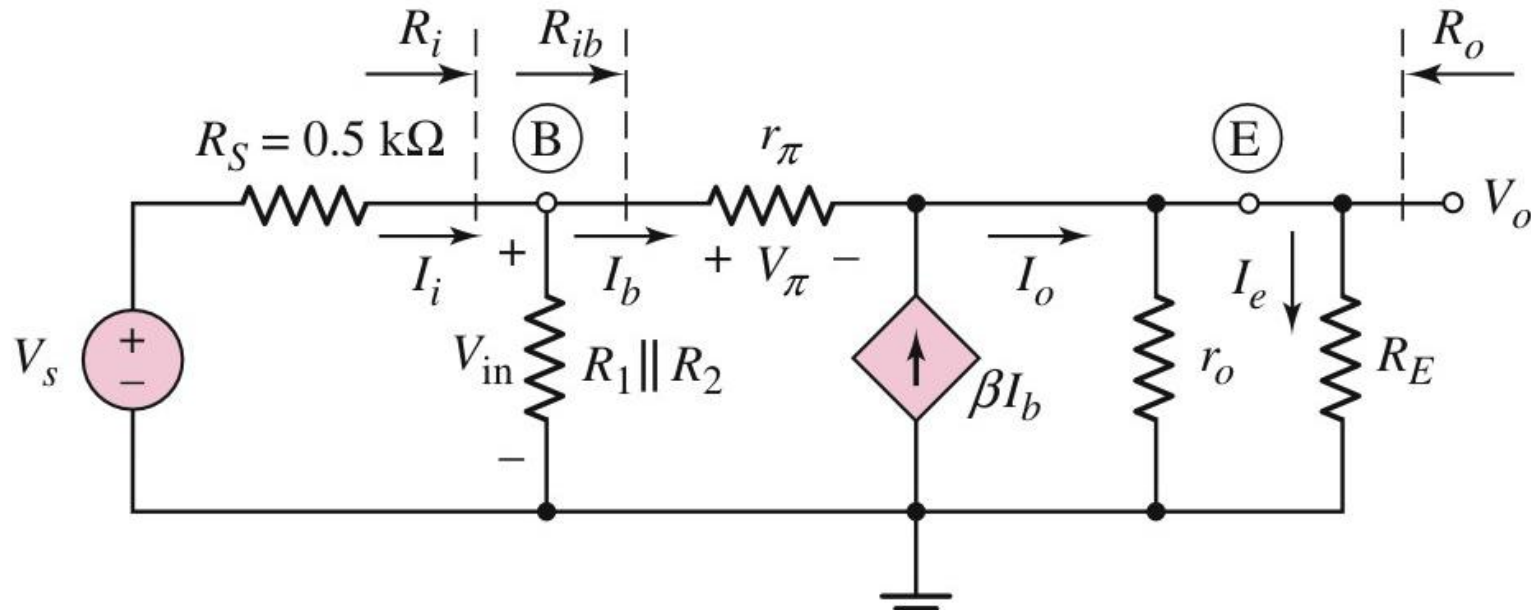


$$A_{vs} = \frac{V_o}{V_s} = \frac{(1 + \beta)(r_o \parallel R_E)}{r_\pi + (1 + \beta)(r_o \parallel R_E)} \cdot \left(\frac{R_i}{R_i + R_S} \right)$$

$$A_v = \frac{V_o}{V_i} = \frac{(1 + \beta)(r_o \parallel R_E)}{r_\pi + (1 + \beta)(r_o \parallel R_E)} < 1$$

$$(1 + \beta)(r_o \parallel R_E) \gg r_\pi$$
$$A_v = 1 \quad \textbf{Follower}$$

6.6 Common-Collector (Emitter-Follower) Amplifier

6.6.2 Input and output impedance

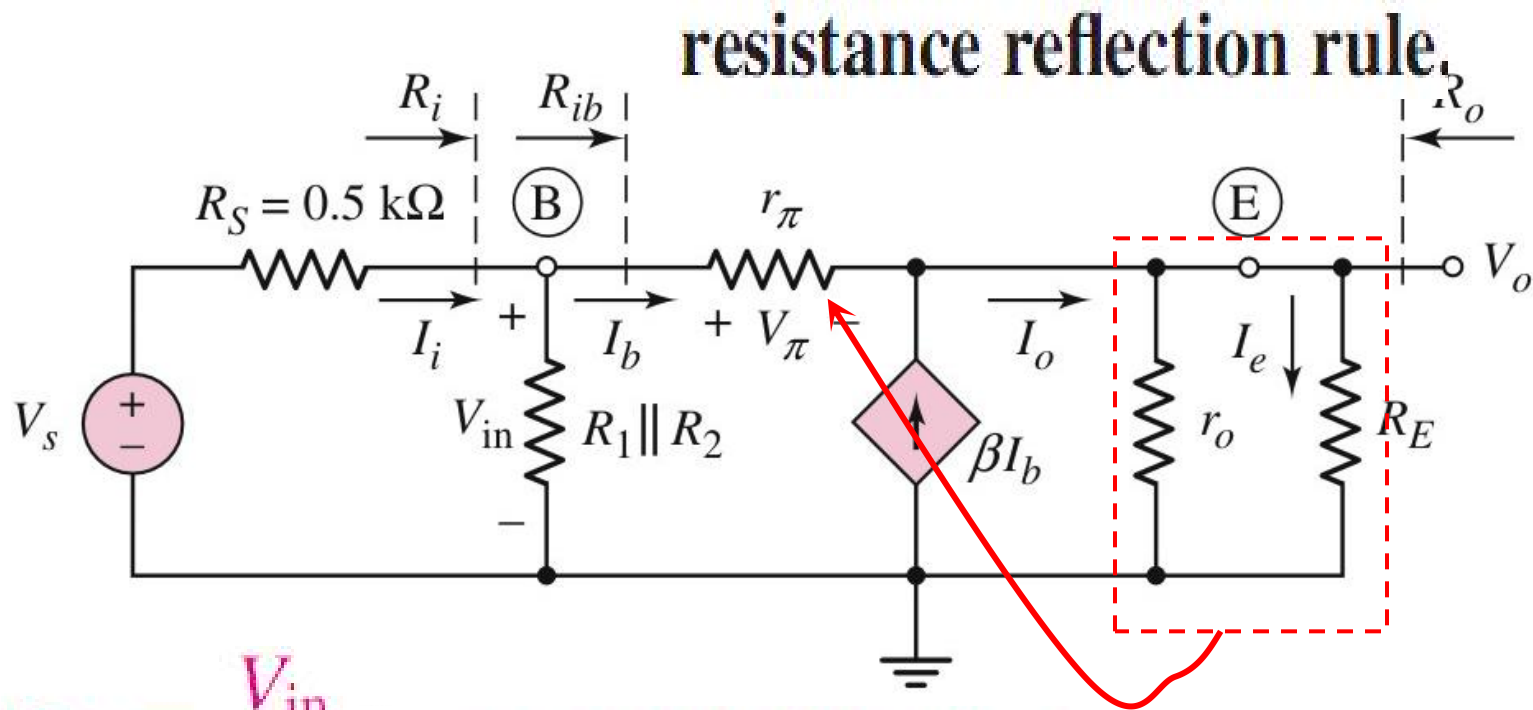


$$R_{ib} = \frac{V_{in}}{I_b} = r_\pi + \underline{(1 + \beta)(r_o \parallel R_E)}$$

$$R_i = R_1 \parallel R_2 \parallel R_{ib}$$

6.6 Common-Collector (Emitter-Follower) Amplifier


6.6.2 Input and output impedance

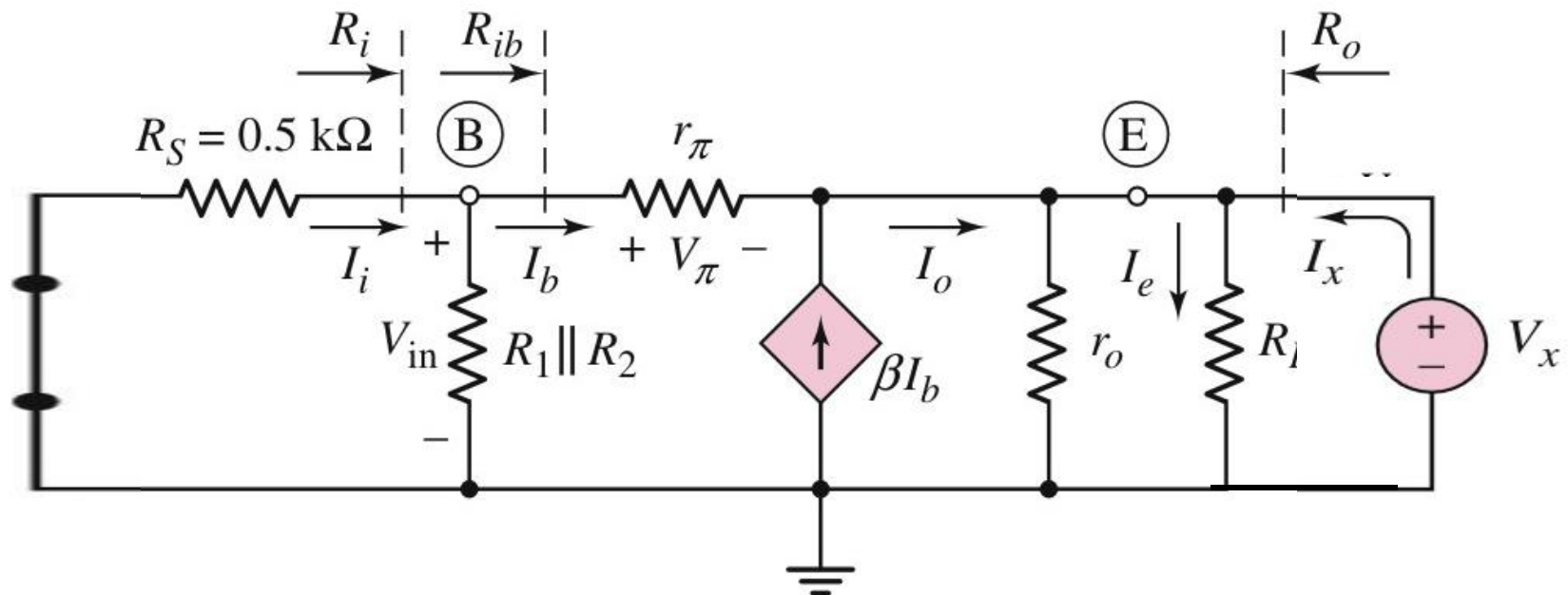

$$R_o = \frac{V_x}{I_x} \quad R_S = 0 \quad \longrightarrow$$

6.6 Common-Collector (Emitter-Follower) Amplifier

6.6.2 Input and output impedance

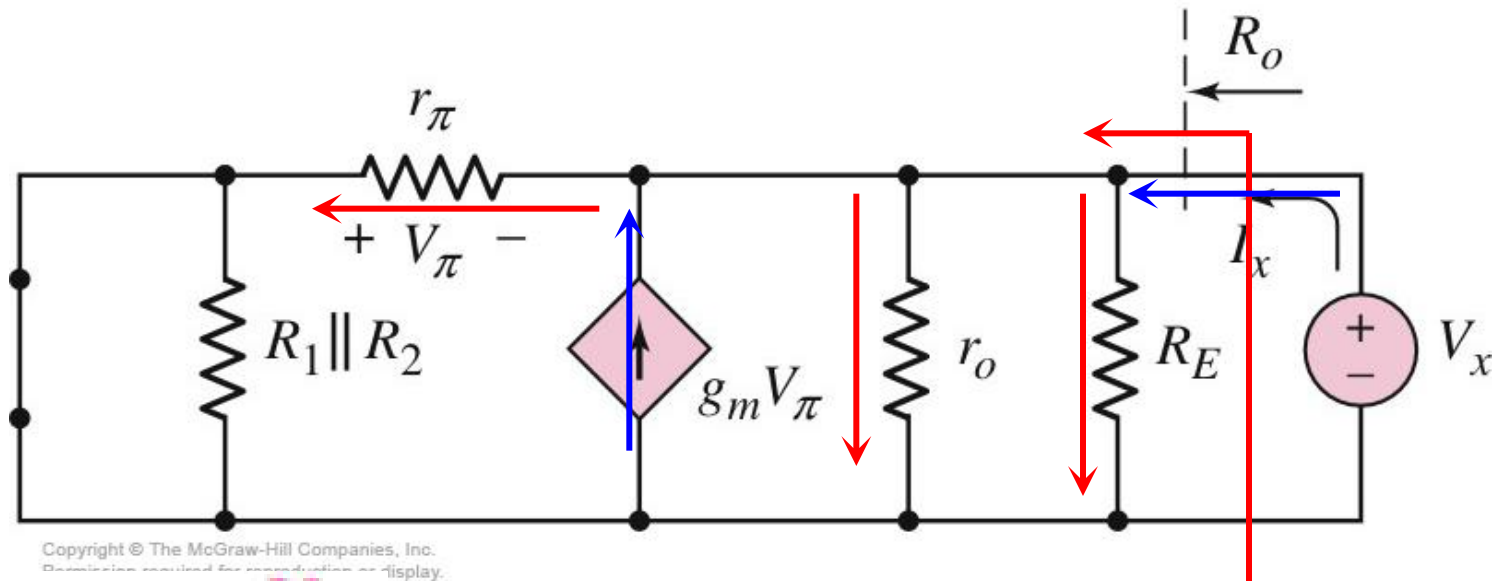

$$R_o = \frac{V_x}{I_x}$$

$$\frac{I_x}{V_x} = \frac{1}{R_o} = g_m + \frac{1}{R_E} + \frac{1}{r_o} + \frac{1}{r_\pi}$$

$$I_x + g_m V_\pi = \frac{V_x}{R_E} + \frac{V_x}{r_o} + \frac{V_x}{r_\pi}$$


$$R_o = \frac{1}{g_m} \parallel R_E \parallel r_o \parallel r_\pi$$

$$V_\pi = -V_x$$

6.6 Common-Collector (Emitter-Follower) Amplifier

6.6.2 Input and output impedance

resistance reflection rule.

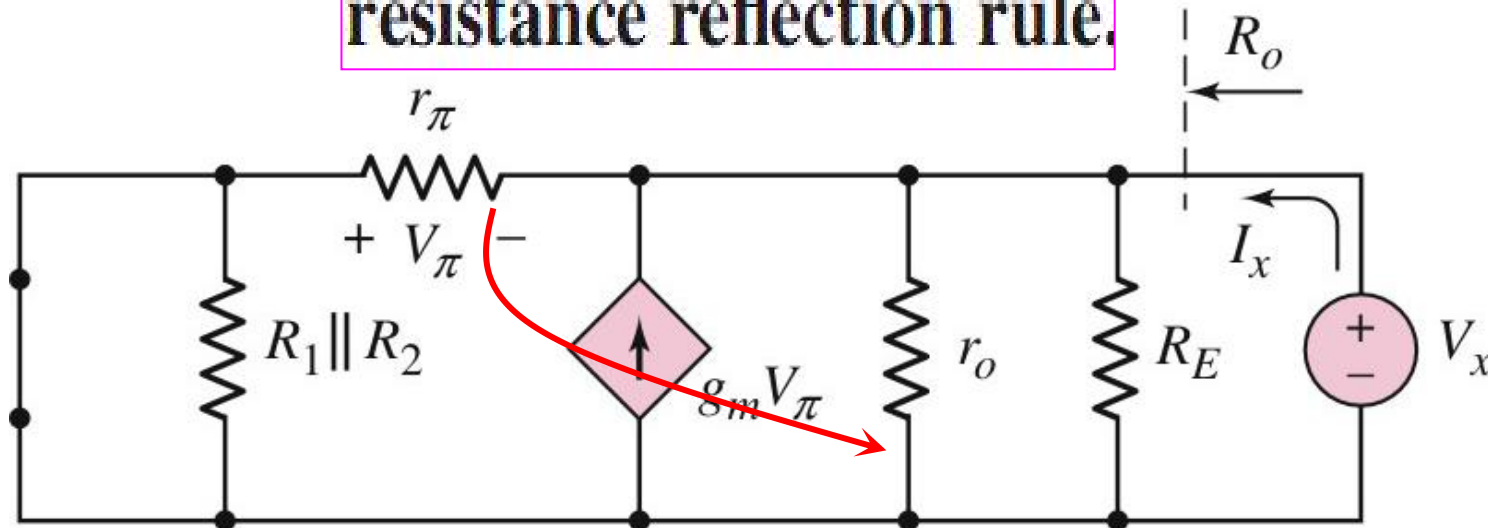

Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$R_o = \frac{1}{g_m} \parallel R_E \parallel r_o \parallel r_\pi \quad R_o = \frac{r_\pi}{1 + \beta} \parallel R_E \parallel r_o$$


$$\frac{1}{R_o} = \left(g_m + \frac{1}{r_\pi} \right) + \frac{1}{R_E} + \frac{1}{r_o} = \left(\frac{1 + \beta}{r_\pi} \right) + \frac{1}{R_E} + \frac{1}{r_o}$$

6.6 Common-Collector (Emitter-Follower) Amplifier

6.6.2 Input and output impedance

$$R_S \neq 0$$


resistance reflection rule.

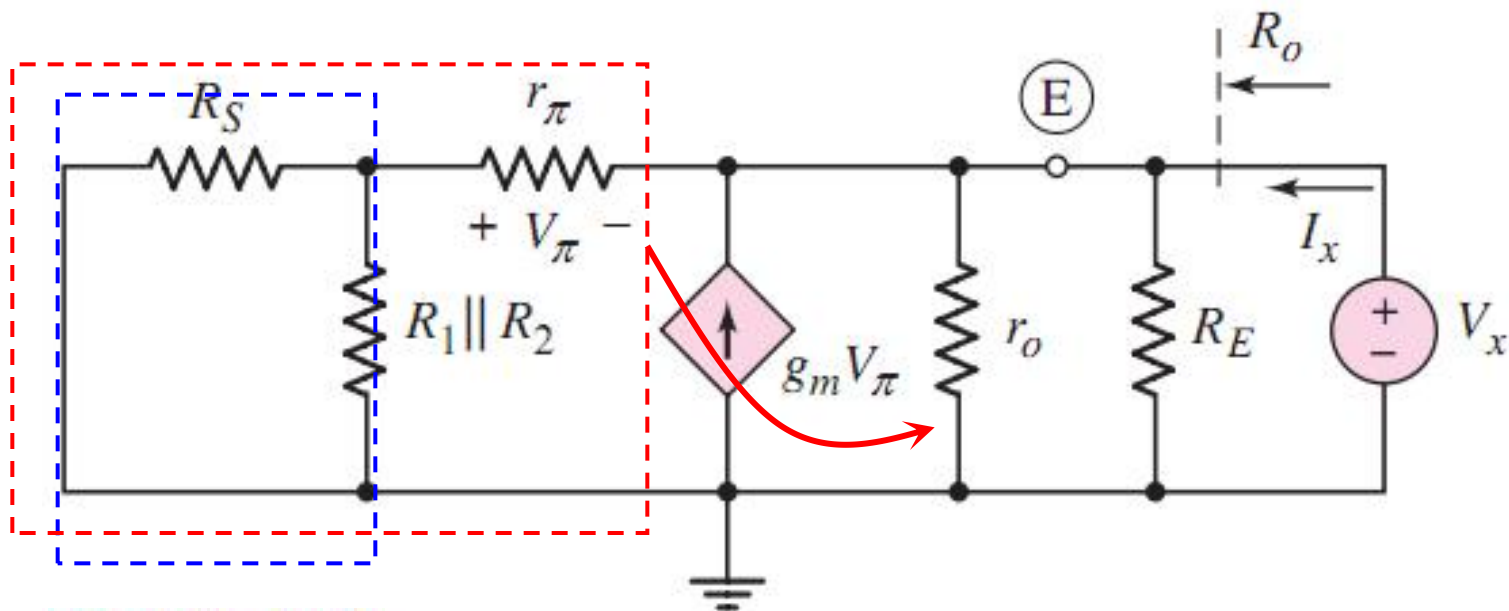

$$R_1 \parallel R_2 \parallel R_S$$
$$r_\pi + R_1 \parallel R_2 \parallel R_S \quad R_o = \left(\frac{r_\pi + R_1 \parallel R_2 \parallel R_S}{1 + \beta} \right) \parallel R_E \parallel r_o$$

6.6 Common-Collector (Emitter-Follower) Amplifier

6.6.3 Small Signal Current Gain

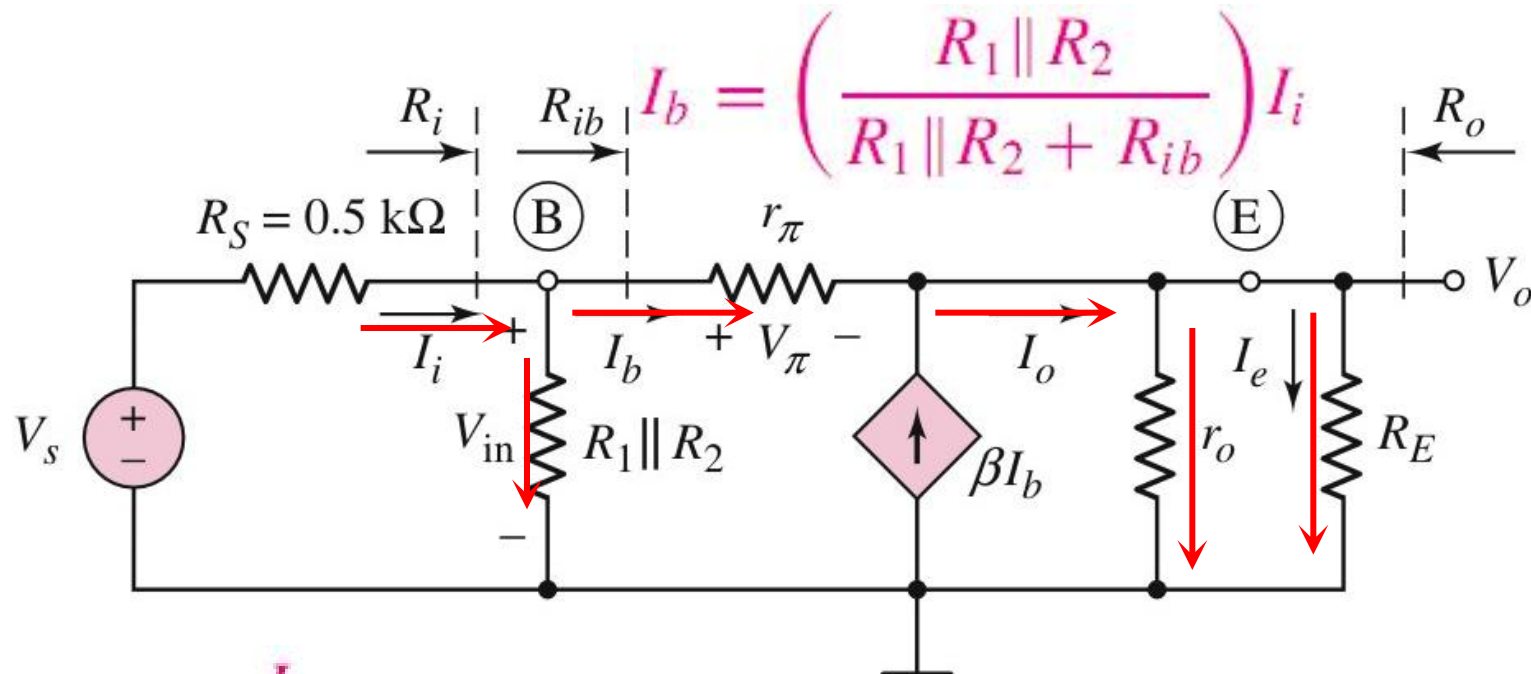


$$A_i = \frac{I_e}{I_i} \quad I_o = (1 + \beta) I_b = (1 + \beta) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{ib}} \right) I_i$$
$$I_e = \left(\frac{r_o}{r_o + R_E} \right) I_o \quad A_i = \frac{I_e}{I_i} = (1 + \beta) \left(\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{ib}} \right) \left(\frac{r_o}{r_o + R_E} \right)$$


$$R_1 \parallel R_2 \gg R_{ib} \text{ and } r_o \gg R_E$$

$$A_i \cong (1 + \beta)$$

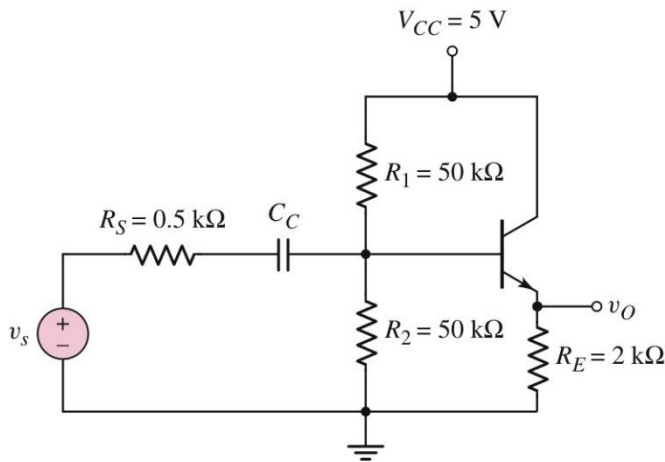6.6 Common-Collector (Emitter-Follower) Amplifier



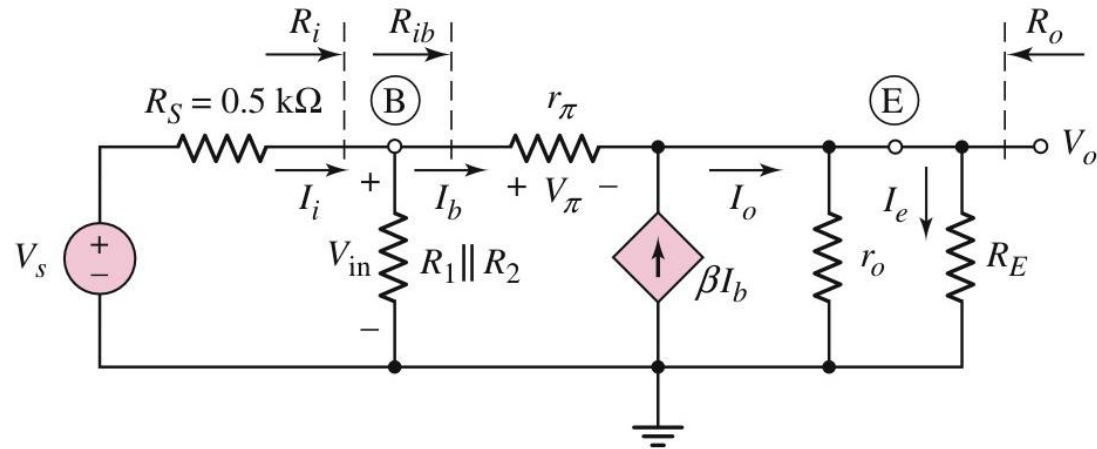Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.



Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Small signal voltage gain


$$A_v = \frac{V_o}{V_i} = \frac{(1 + \beta)(r_o \parallel R_E)}{r_\pi + (1 + \beta)(r_o \parallel R_E)}$$

Input impedance

$$R_i = R_1 \parallel R_2 \parallel [r_\pi + (1 + \beta)(r_o \parallel R_E)]$$

Output impedance
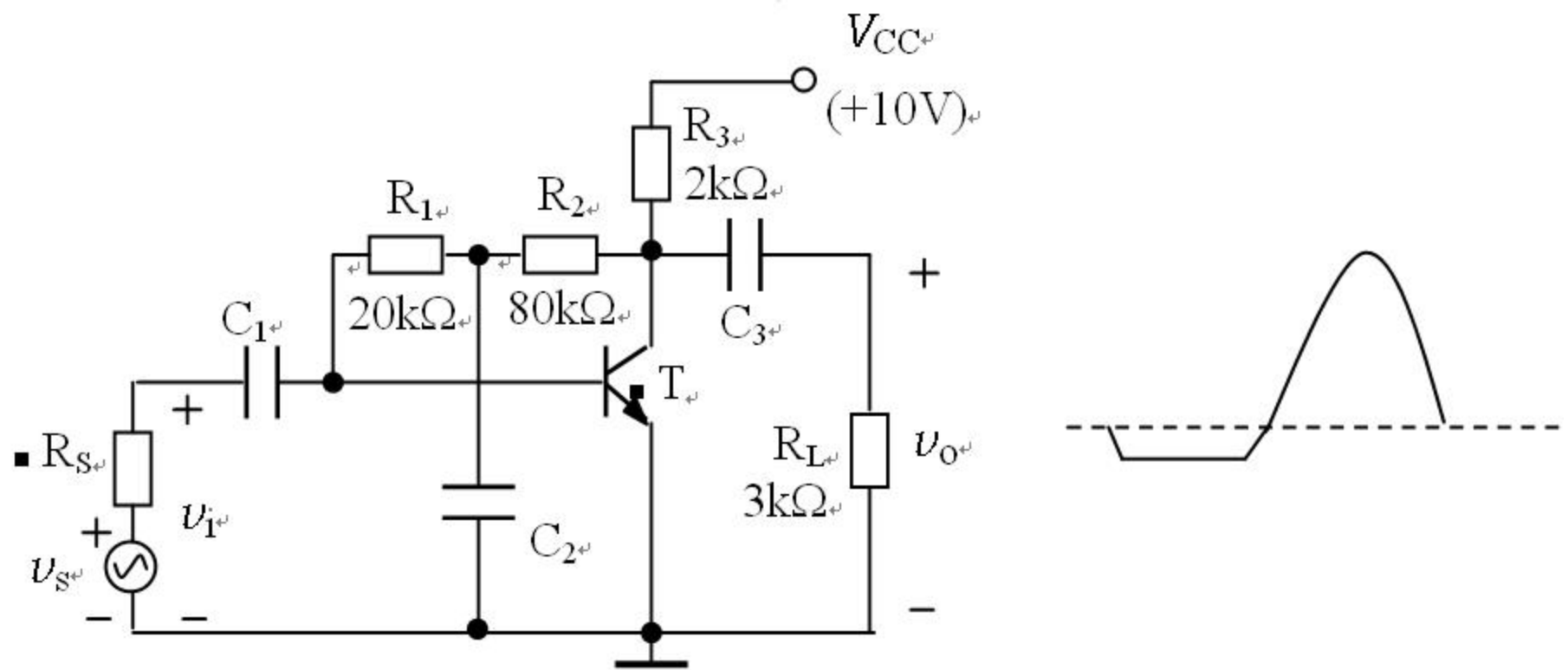
$$R_o = \left(\frac{r_\pi + R_1 \parallel R_2 \parallel R_S}{1 + \beta} \right) \parallel R_E \parallel r_o$$



- 1、 Calculate (I_B, I_C, V_{CE}) ;
- 2、 Sketch the small signal equivalent circuit;
- 3、 Find R_i and R_o ;
- 4、 Find $A_v = V_o / V_i$;
- 5、 $R_S = 200\Omega$, Find $A_{vs} = V_o / V_s$;
- 6、 The output voltage is shown as figure, which distortion?



Huazhong University of Science and Technology
The Department of Electronics and Information Engineering

Electronic Circuit Analysis and Design

Dr. Tianping Deng

Email: dengtp@hust.edu.cn

Ch6. Basic BJT Amplifiers

6.0 Preview

6.1 Analog Signals and Linear Amplifiers

6.2 The Bipolar Linear Amplifier

6.3 Basic Transistor Amplifier Configurations

6.4 Common-Emitter Amplifiers

6.5 AC Load Line Analysis

6.6 Common-Collector (Emitter-Follower) Amplifier

6.7 Common-Base Amplifier


6.8 The Three Basic Amplifiers: Summary and Comparison

6.9 Multistage Amplifiers

6.10 Power Considerations


6.11 Design Application

6.12 Summary

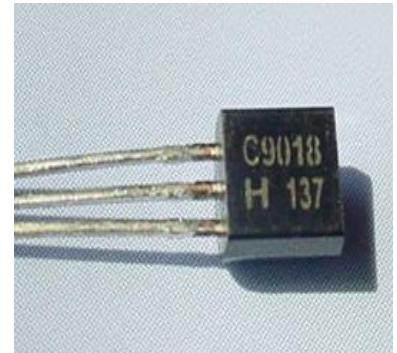


6.7 Common-Base Amplifier

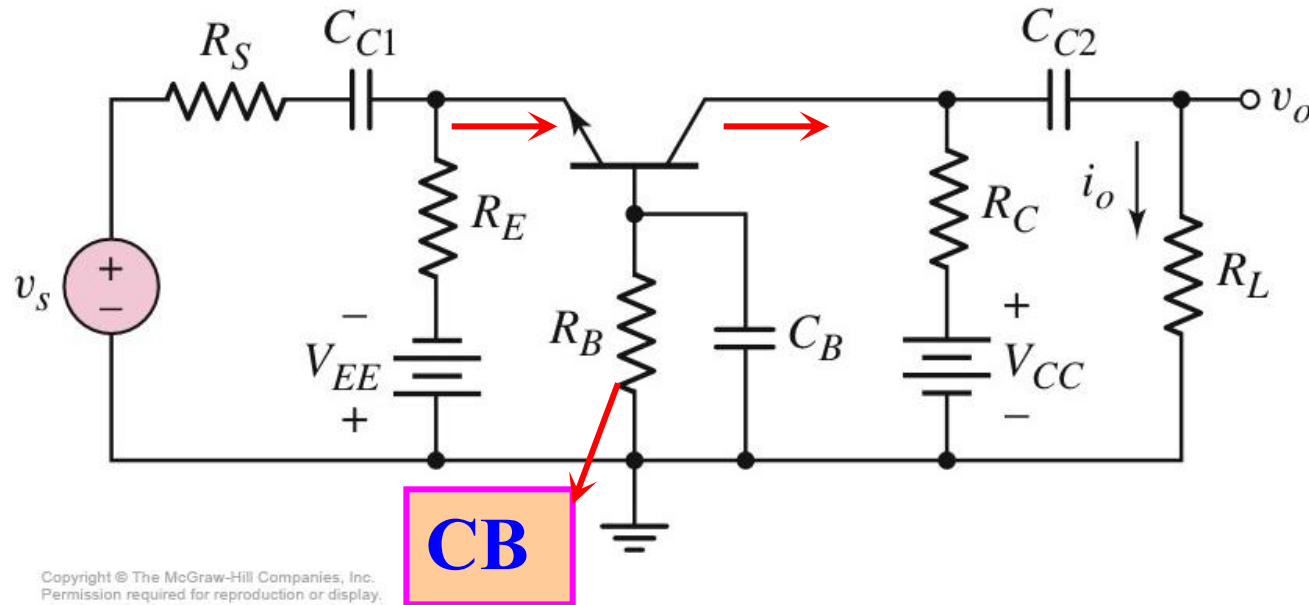6.7.1 Small Signal Voltage and Current Gains




6.7 Common-Base Amplifier

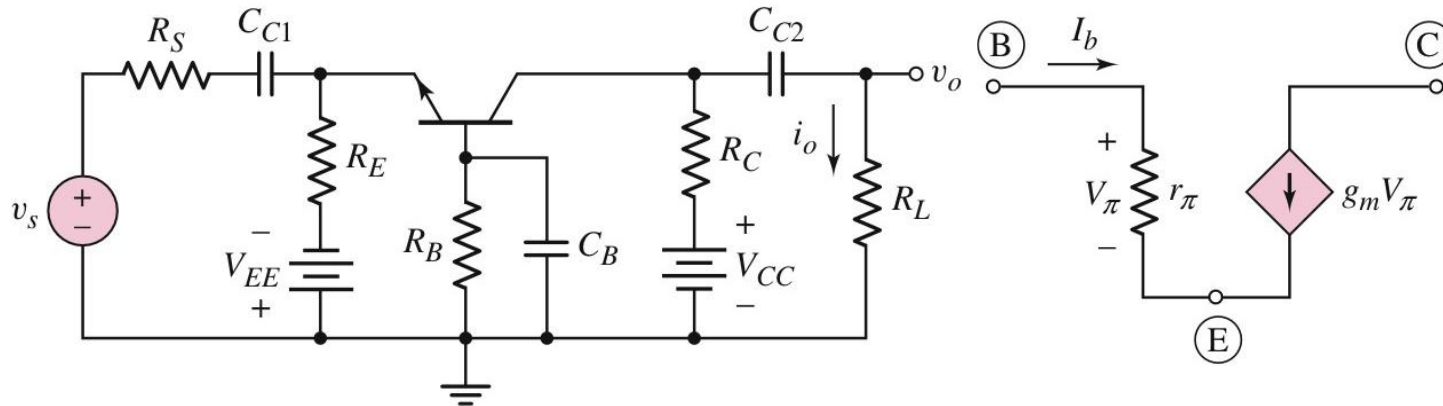6.7.1 Small Signal Voltage and Current Gains




Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

Small-signal equivalent circuit

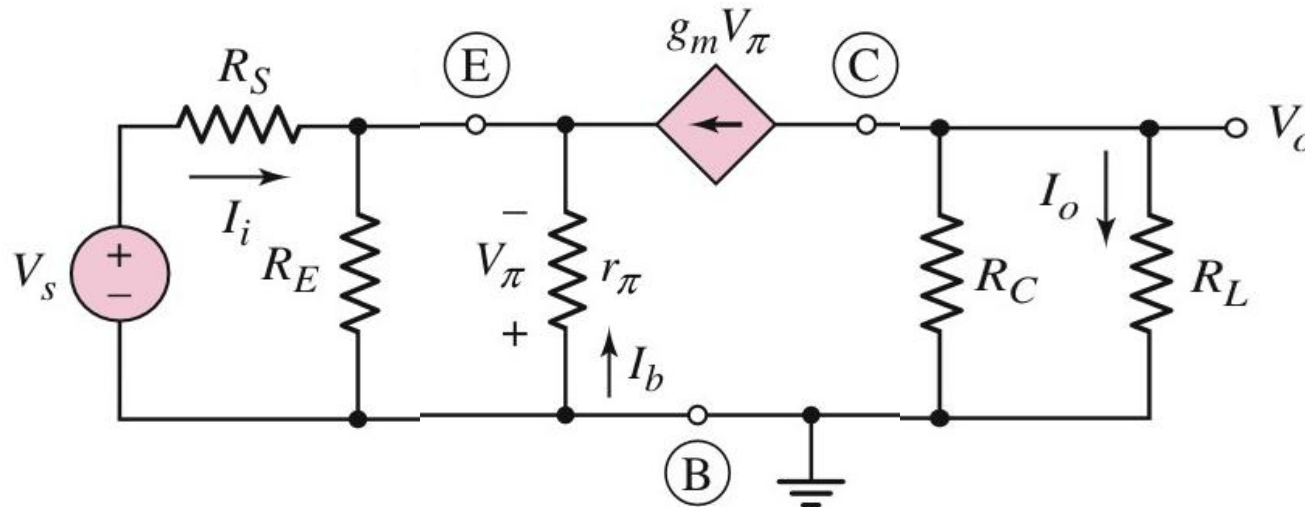

6.7 Common-Base Amplifier

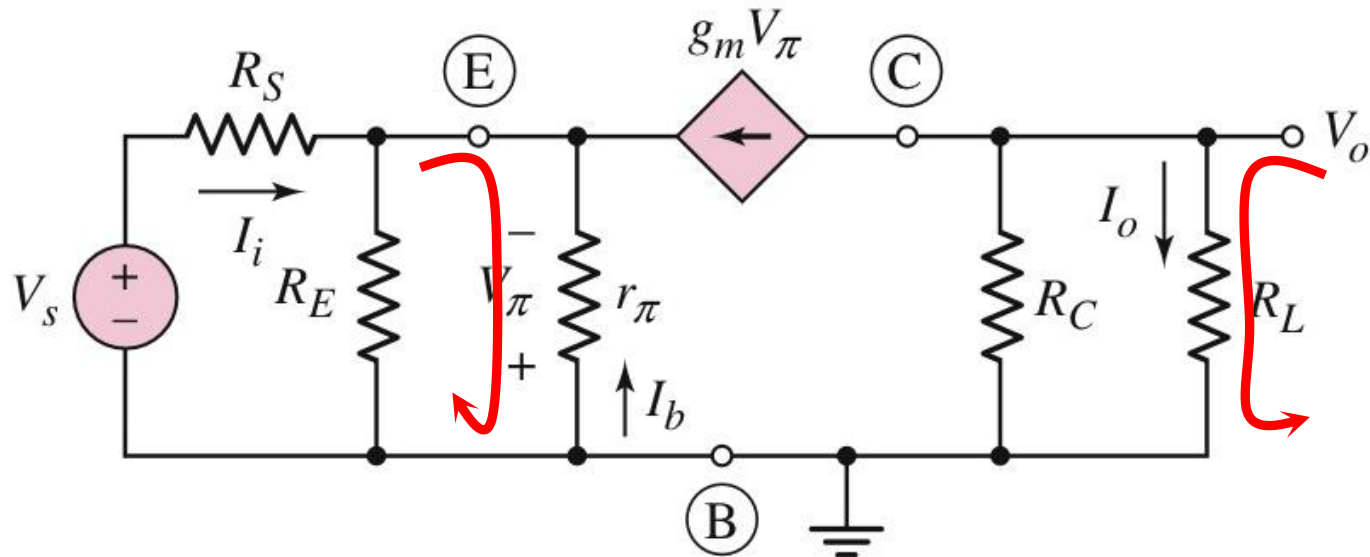6.7.1 Small Signal Voltage and Current Gains



Input loop $V_{in} = -I_b r_\pi$

Output loop $V_o = -I_c R'_L = -\beta I_b R'_L$ $R'_L = R_C \parallel R_L$


Voltage gain

$$A_v = \frac{V_o}{V_{in}} = \frac{-\beta I_b R'_L}{-I_b r_\pi} = \frac{\beta R'_L}{r_\pi}$$

$$A_{vs} = \frac{V_o}{V_s} = ?$$

6.7 Common-Base Amplifier

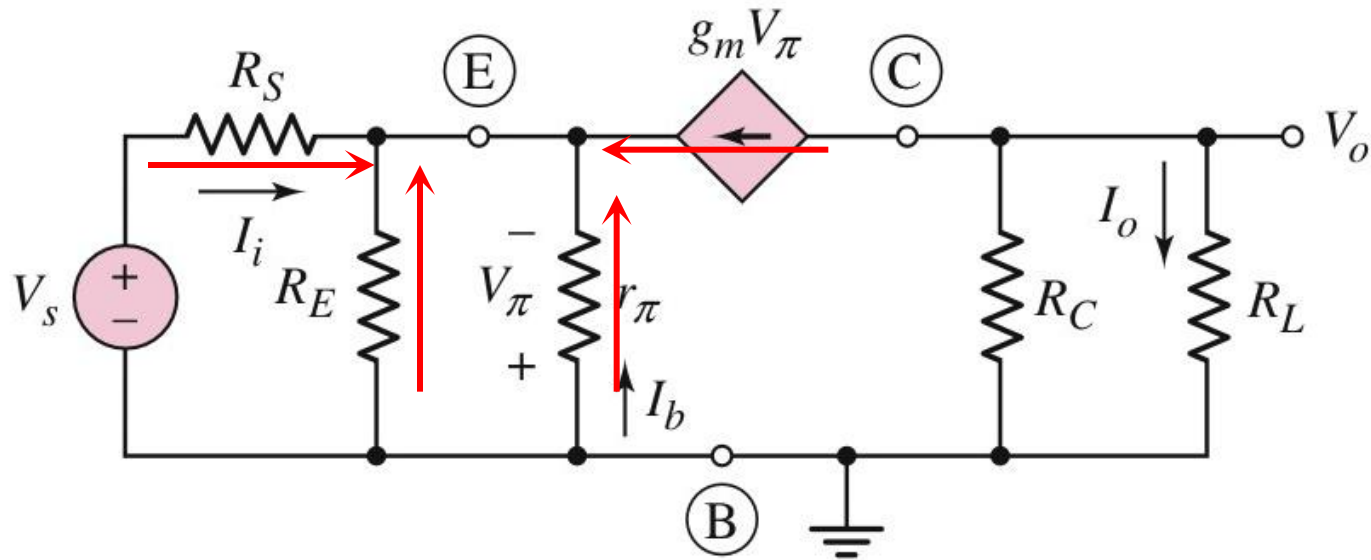
6.7.1 Small Signal Voltage and Current Gains



$$g_m V_\pi + \frac{V_\pi}{r_\pi} + \frac{V_\pi}{R_E} + \frac{V_s - (-V_\pi)}{R_S} = 0$$

$$V_\pi \left(\frac{1 + \beta}{r_\pi} + \frac{1}{R_E} + \frac{1}{R_S} \right) = -\frac{V_s}{R_S}$$

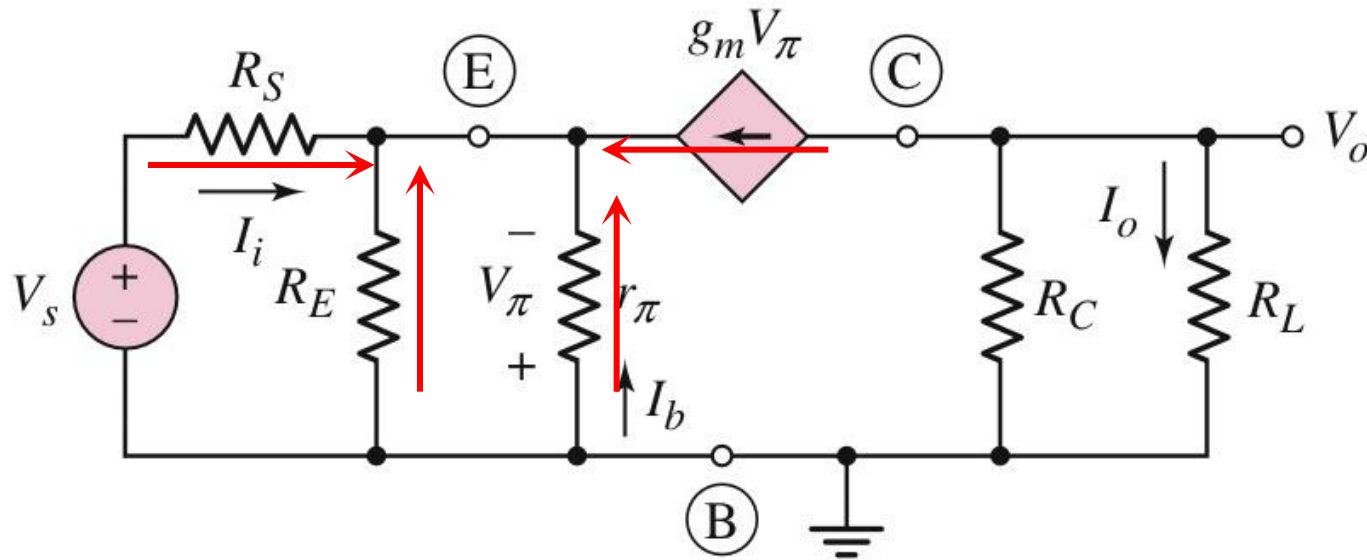6.7.1 Small Signal Voltage and Current Gains




$$A_v = \frac{V_o}{V_{in}} = \frac{\beta(R_C \parallel R_L)}{r_\pi} = g_m(R_C \parallel R_L)$$

$$V_\pi = -\frac{V_s}{R_S} \left[\left(\frac{r_\pi}{1 + \beta} \right) \parallel R_E \parallel R_S \right]$$

$$A_v = \frac{V_o}{V_s} = +g_m \left(\frac{R_C \parallel R_L}{R_S} \right) \left[\left(\frac{r_\pi}{1 + \beta} \right) \parallel R_E \parallel R_S \right]$$

6.7 Common-Base Amplifier

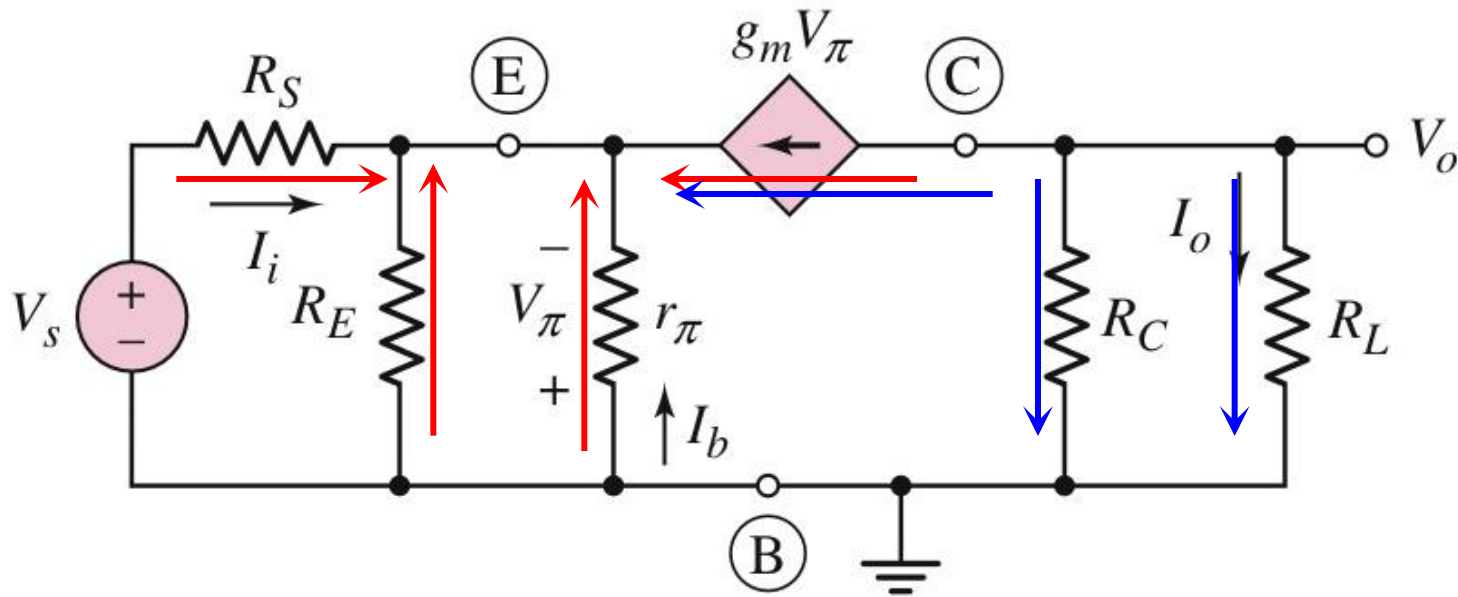6.7.1 Small Signal Voltage and Current Gains



$$I_i + \frac{V_\pi}{r_\pi} + g_m V_\pi + \frac{V_\pi}{R_E} = 0 \quad \Rightarrow \quad V_\pi = -I_i \left[\left(\frac{r_\pi}{1 + \beta} \right) \parallel R_E \right]$$


$$I_o = -(g_m V_\pi) \left(\frac{R_C}{R_C + R_L} \right)$$

$$\begin{aligned} R_E &\rightarrow \infty \\ R_L &\rightarrow 0 \end{aligned}$$

$$A_i = \frac{I_o}{I_i} = g_m \left(\frac{R_C}{R_C + R_L} \right) \left[\left(\frac{r_\pi}{1 + \beta} \right) \parallel R_E \right] \quad A_{io} = \frac{g_m r_\pi}{1 + \beta} = \frac{\beta}{1 + \beta} = \alpha$$

6.7 Common-Base Amplifier

6.7.2 Input and output impedance

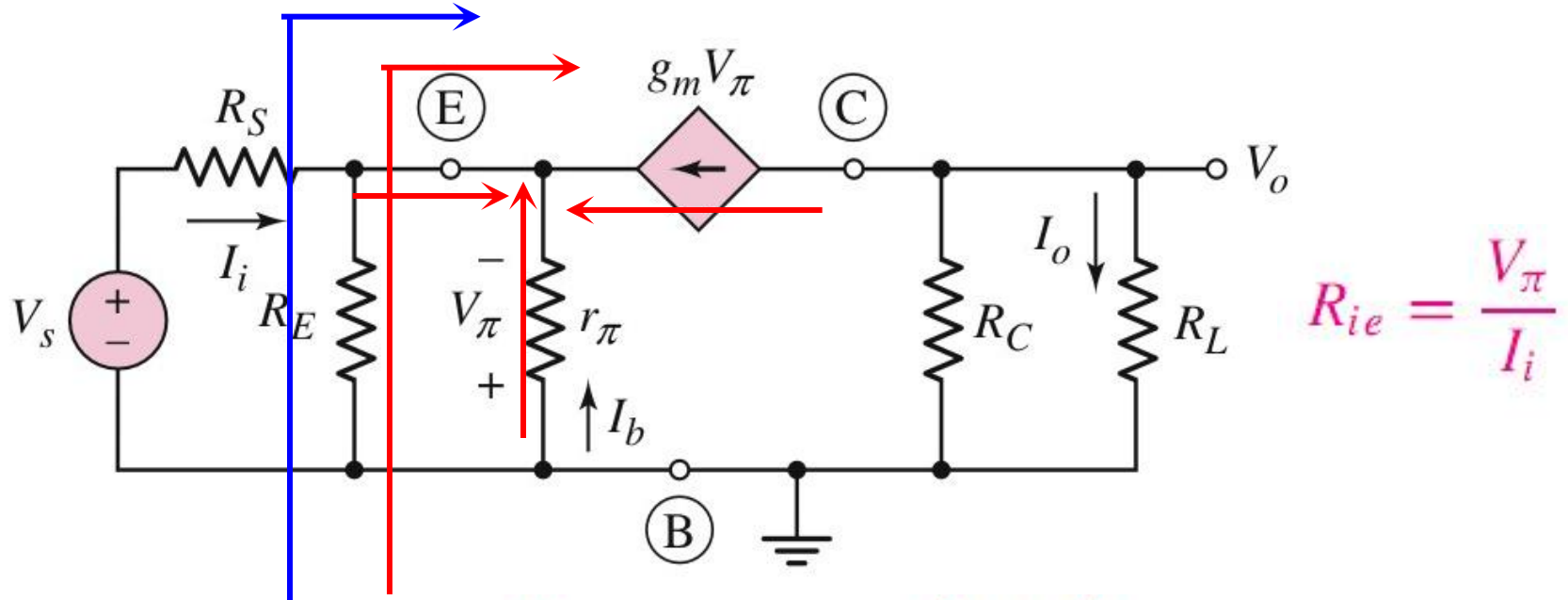

$$R_{ie} = \frac{V_\pi}{I_i}$$


$$I_i = I_b + g_m V_\pi = \frac{V_\pi}{r_\pi} + g_m V_\pi = V_\pi \left(\frac{1 + \beta}{r_\pi} \right)$$

$$R_{ie} = \frac{V_\pi}{I_i} = \frac{r_\pi}{1 + \beta} \equiv r_e$$

$$R_i = R_E // R_{ie} = R_E // \frac{r_\pi}{1 + \beta}$$



6.7 Common-Base Amplifier

6.7.2 Input and output impedance

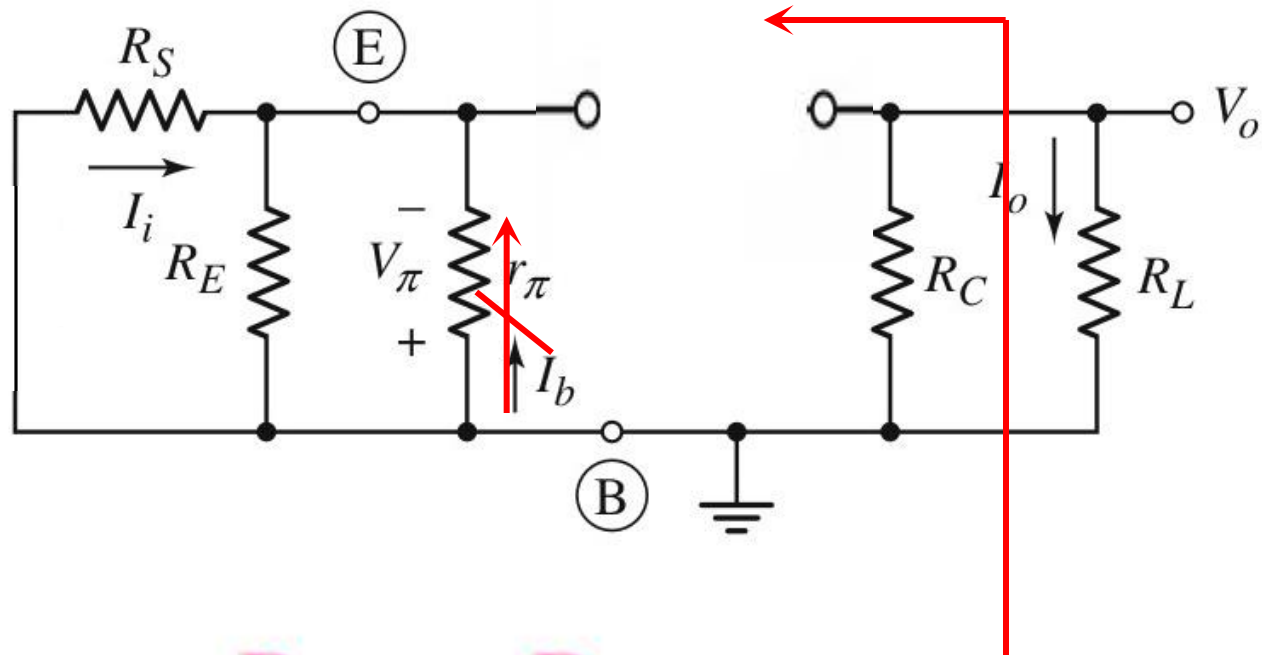

$$R_o = R_C$$

6.7 Common-Base Amplifier

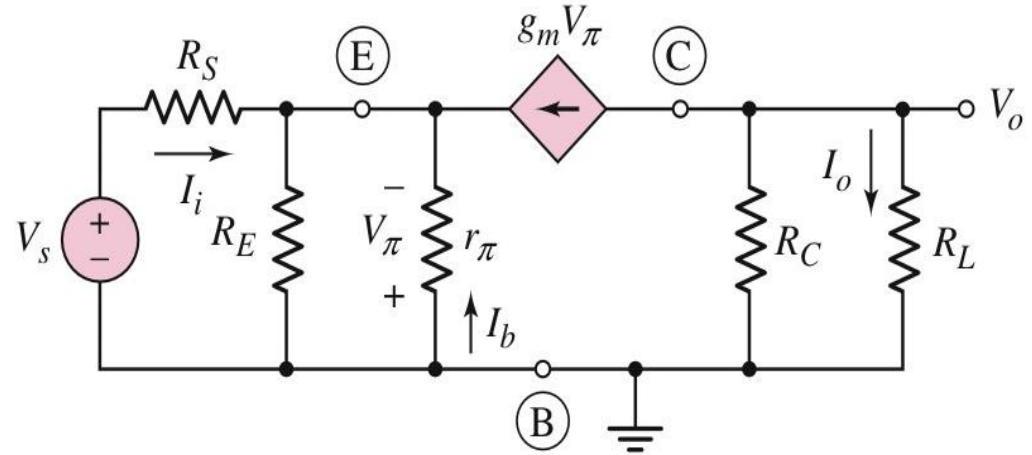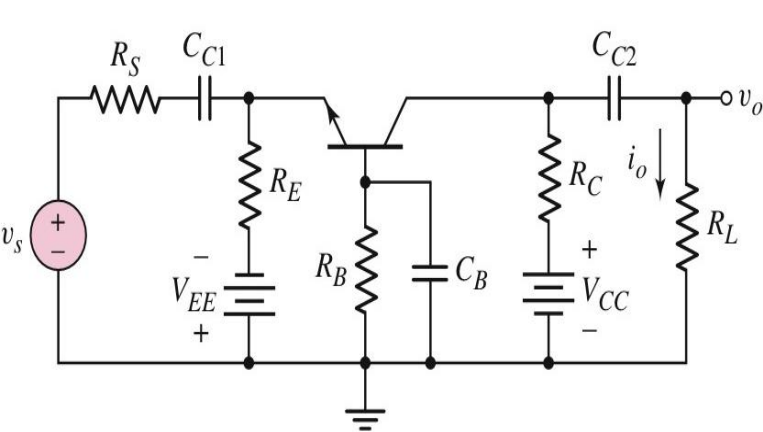

Small Signal Voltage Gain

$$A_v = \frac{V_o}{V_\pi} = \frac{\beta R'_L}{r_\pi}$$




Input impedance

$$R_i = R_E // R_{ie} = R_E // \frac{r_\pi}{1 + \beta}$$

Output impedance

$$R_o = R_C$$

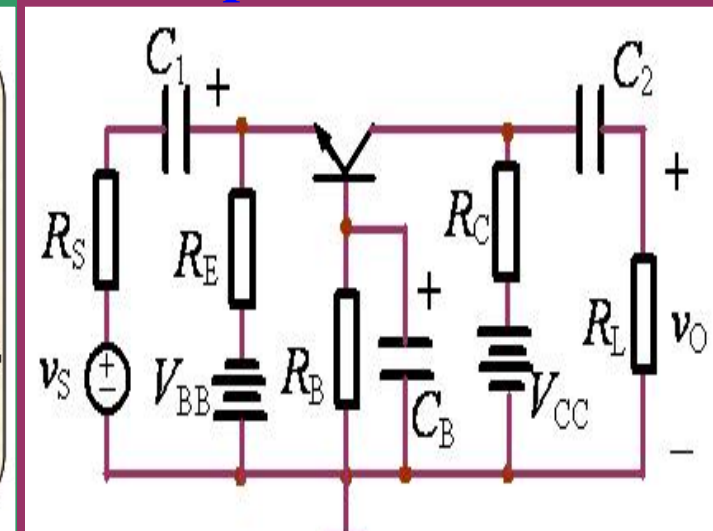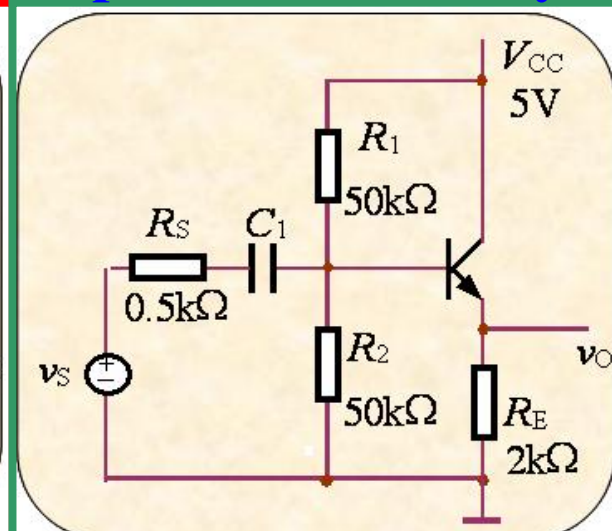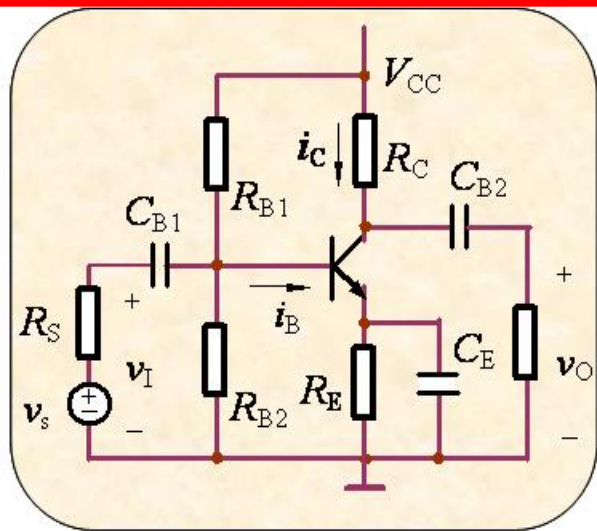6.8 The Three Basic Amplifier: Summary and Comparison



$$A_V = -\frac{\beta \cdot (R_C // R_L)}{r_\pi}$$

$$\frac{(1 + \beta)(R_E // r_o)}{r_\pi + (1 + \beta)(R_E // r_o)}$$

$$\frac{\beta \cdot (R_C // R_L)}{r_\pi}$$

$$R_i = R_{B1} // R_{B2} // r_\pi$$

$$R_1 // R_2 // [r_\pi + (1 + \beta)(R_E // r_o)]$$

Large

$$R_E // \frac{r_\pi}{1 + \beta}$$

Small

$$R_o \approx R_C$$

$$R_E // \frac{R'_S + r_\pi}{1 + \beta}$$

Small

$$R_o \approx R_C$$

6.8 The Three Basic Amplifier: Summary and Comparison

Summary of Single Stage BJT Amplifiers

	C-E ($R_E=0$)	Emitter Degenerated C-E	C-C	C-B
Terminal Voltage Gain	Inverting & large	Inverting & moderate	1	Non-inverting & Large
Terminal Current Gain	Inverting & large	Inverting & large	Non- inverting & Large	1
Input Resistance	Moderate	Large	Large	Low
Output Resistance	Moderate	Moderate	Low	Moderate

1、 The basic BJT amplifiers has:

(A) 、 CE

(B)、 CC

(C)、 CB

- 1) which has the lest input resistance (**C**)
- 2) which has the lest output resistance (**B**)
- 3) which can amplify the ac voltage (**A C**)
- 4) which can amplify the ac current (**A B**)
- 5) the input and the output has the same phase is (**B、)C**
- 6) the input and the output has the opposite phase is (**A**)

Contents

PART 1 SEMICONDUCTOR DEVICES AND BASIC APPLICATIONS

Chapter 1 Semiconductor Materials and Diodes

Chapter 2 Diode Circuits

Chapter 3 The Field-Effect Transistor

Chapter 4 Basic FET Amplifiers

Chapter 5 The Bipolar Junction Transistor

 **Chapter 6 Basic BJT Amplifiers**

Chapter 7 Frequency Response

Chapter 8 Output Stages and Power Amplifiers

PART 2 ANALOG ELECTRONICS

Chapter 9 Ideal Operational Amplifiers and Op-Amp Circuits

Chapter 10 Integrated Circuit Biasing and Active Loads

Chapter 11 Differential and Multistage Amplifiers

Chapter 12 Feedback and Stability

Chapter 13 Operational Amplifier Circuits

Chapter 14 Nonideal Effects in Operational Amplifier Circuits

Chapter 15 Applications and Design of Integrated Circuits

Ch6. Basic BJT Amplifiers

6.0 Preview

6.1 Analog Signals and Linear Amplifiers

6.2 The Bipolar Linear Amplifier

6.3 Basic Transistor Amplifier Configurations

6.4 Common-Emitter Amplifiers

6.5 AC Load Line Analysis

6.6 Common-Collector (Emitter-Follower) Amplifier

6.7 Common-Base Amplifier


6.8 The Three Basic Amplifiers: Summary and Comparison

6.9 Multistage Amplifiers

6.10 Power Considerations

6.11 Design Application

6.12 Summary

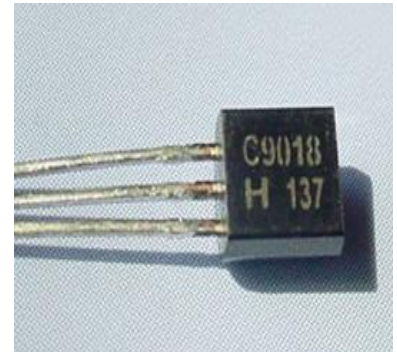

6.9 Multistage Amplifiers

(1) The Reason of Using Multistage Circuit

A single transistor amplifier will not be able to meet the combined specifications of a given amplification factor, input resistance, and output resistance.

(2) Cascade Configuration

3 circuits are connected in series, or cascaded. Each circuit can be CE, CC, or CB configuration

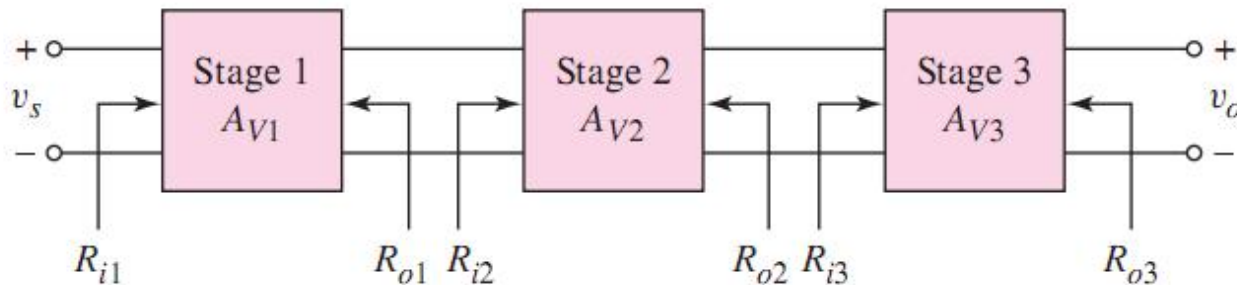


Figure 6.68 A generalized three-stage amplifier

6.9 Multistage Amplifiers

(3) Loading effect

E.g. R_{i2} is the load of stage 1.

$$R_{i2} = R_{L1}$$

$$R_{o1} = R_{S2}$$


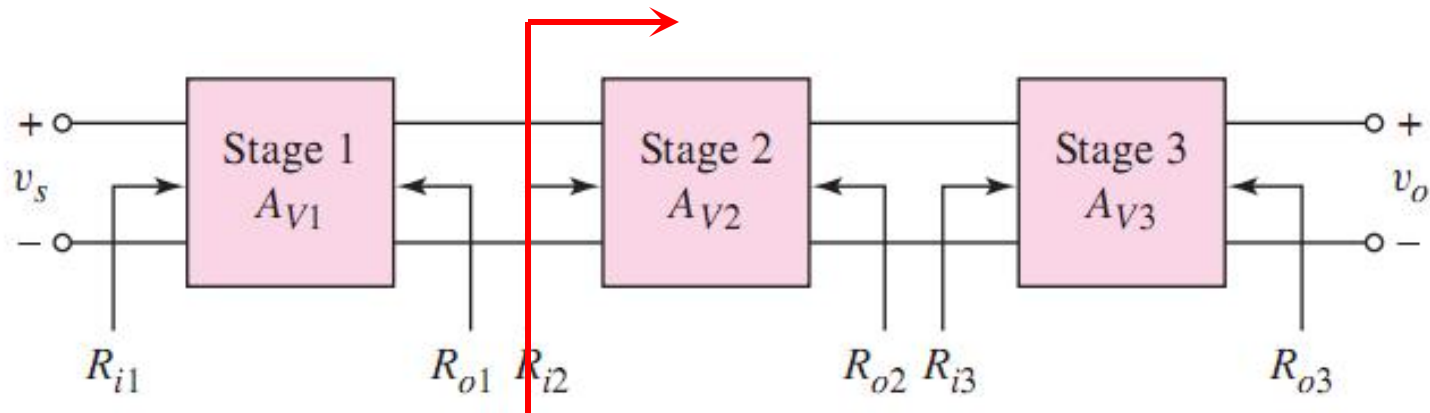
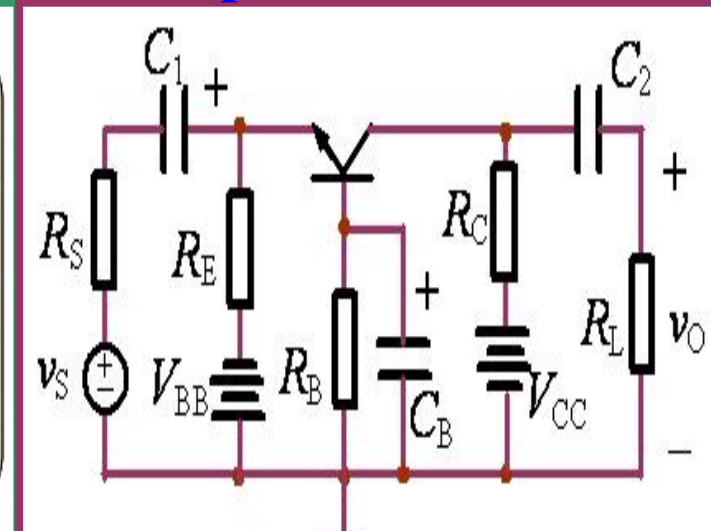
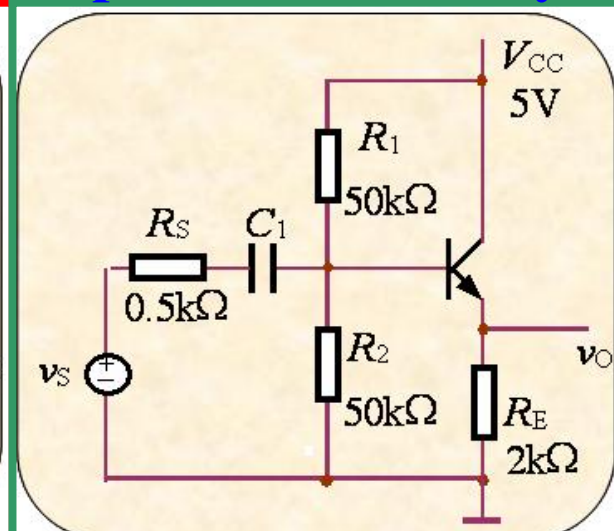


Figure 6.68 A generalized three-stage amplifier

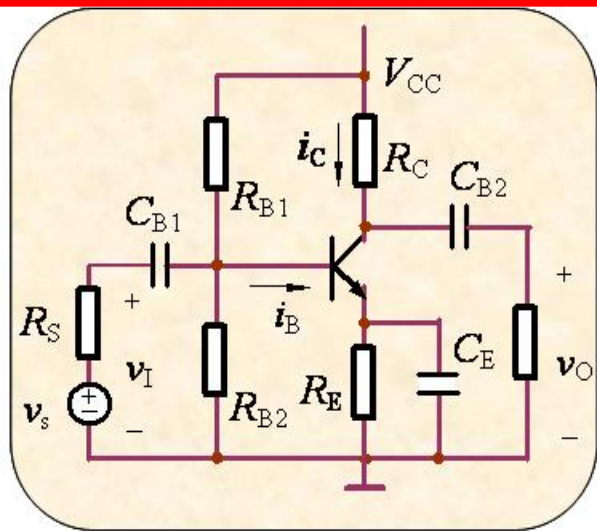6.8 The Three Basic Amplifier: Summary and Comparison



$$A_V = -\frac{\beta \cdot (R_C // R_L)}{r_\pi}$$

$$\frac{(1 + \beta)(R_E // r_o)}{r_\pi + (1 + \beta)(R_E // r_o)}$$

$$\frac{\beta \cdot (R_C // R_L)}{r_\pi}$$

$$R_i = R_{B1} // R_{B2} // r_\pi$$

$$R_1 // R_2 // [r_\pi + (1 + \beta)(R_E // r_o)]$$

Large

$$R_E // \frac{r_\pi}{1 + \beta}$$

Small

$$R_o \approx R_C$$

$$R_E // \frac{R'_S + r_\pi}{1 + \beta}$$

Small

$$R_o \approx R_C$$

6.9 Multistage Amplifiers


6.9.1 Multistage Analysis: Cascade Configuration

$$A_{v1S} = \frac{V_{o1}}{V_s} = -g_{m1}(R_C // R_{L1}) \frac{R_i}{R_i + R_s}$$

$$= -g_{m1}(R_{C1} // R_{i2}) \frac{R_i}{R_i + R_s}$$

$$= -g_{m1}(R_{C1} // r_{\pi2}) \frac{R_i}{R_i + R_s}$$

$$A_{v2} = -g_{m2}(R_{C2} // R_L)$$

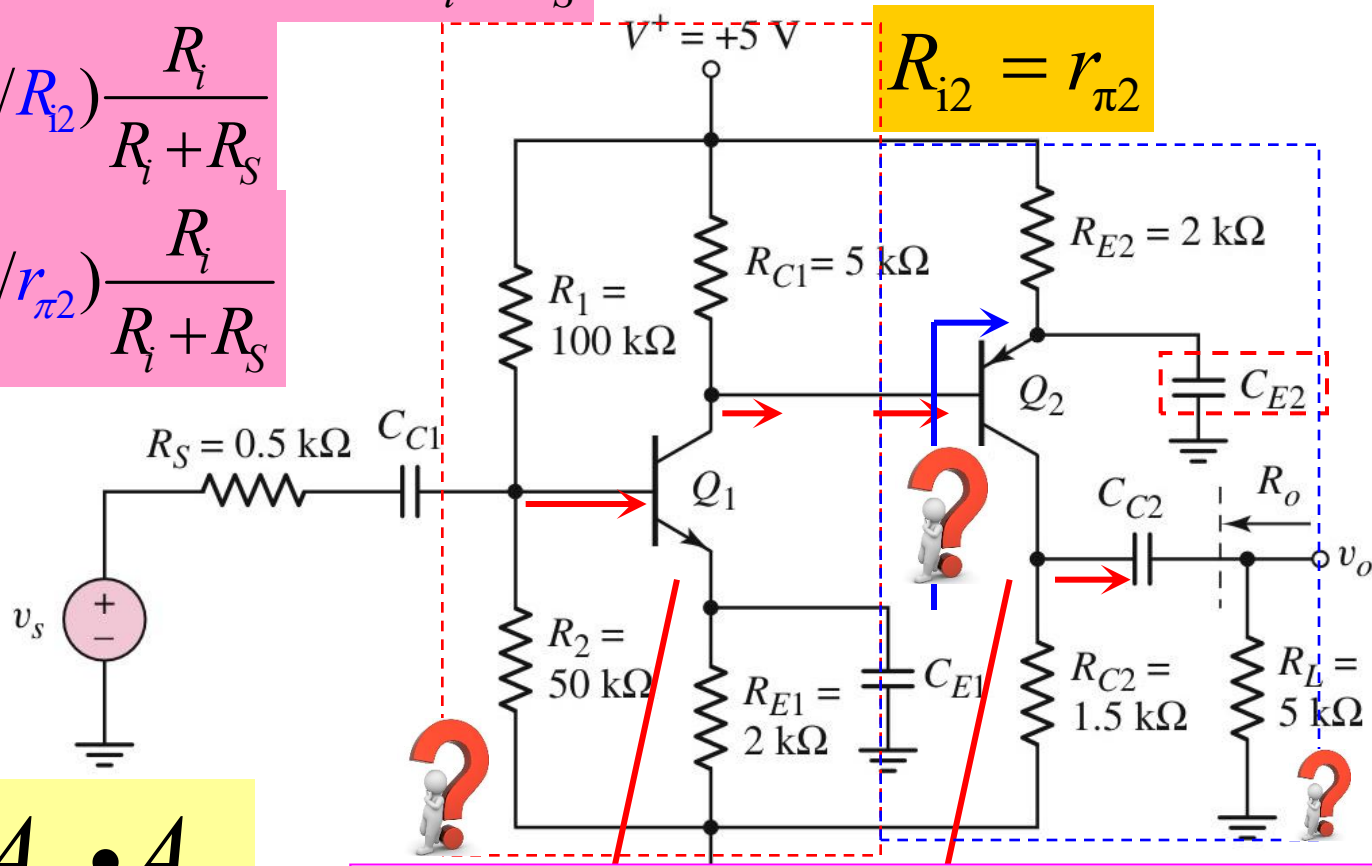


$$A_v = A_{v1} \cdot A_{v2}$$

$$A_v = \frac{V_o}{V_s} = g_{m1} g_{m2} (R_{C1} // r_{\pi2}) (R_{C2} // R_L) \left(\frac{R_i}{R_i + R_s} \right)$$

6.9 Multistage Amplifiers

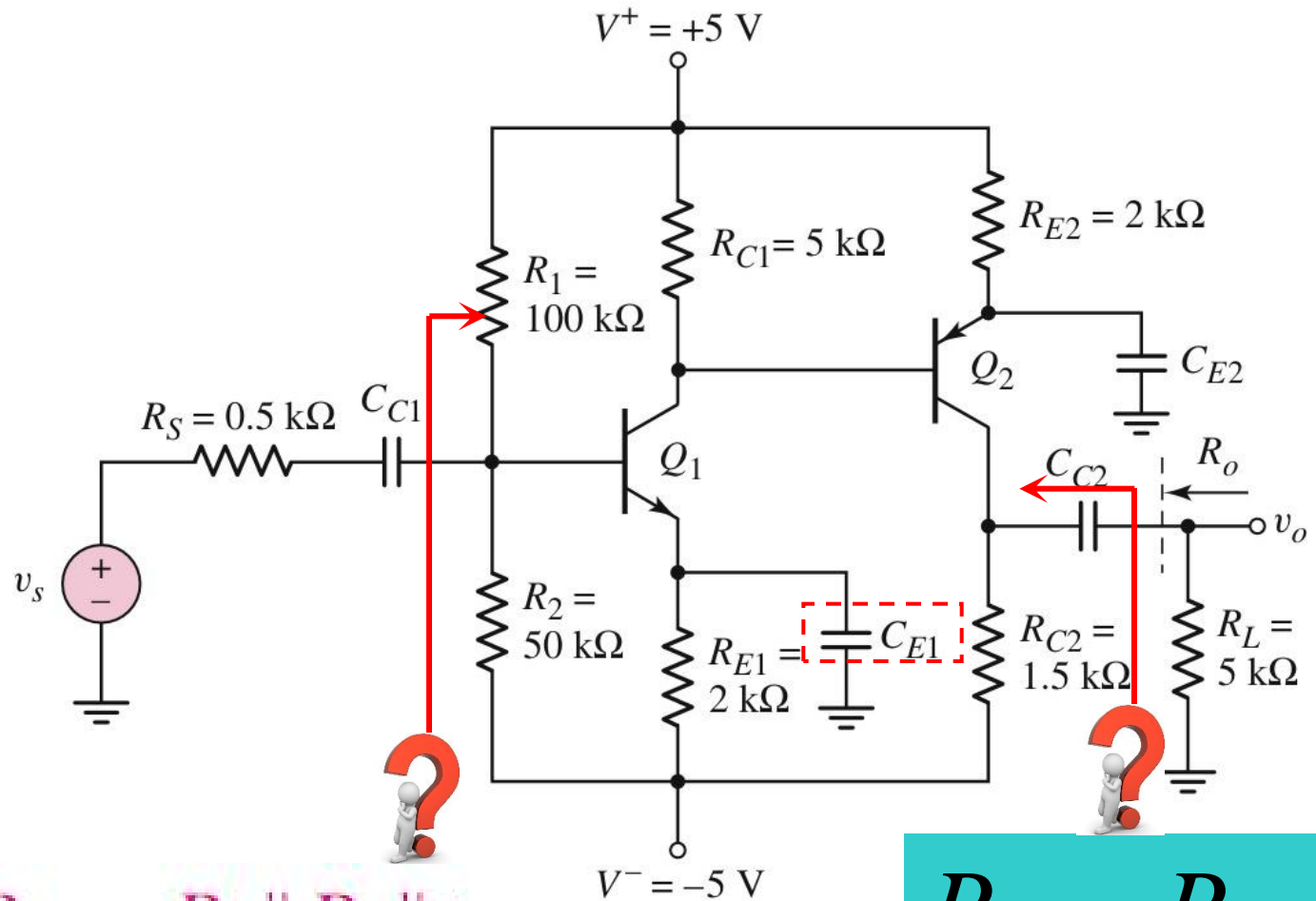6.9.1 Multistage Analysis: Cascade Configuration




$$R_i = R_1 \parallel R_2 \parallel r_{\pi 1}$$


$$R_o = R_{c2}$$

6.9 Multistage Amplifiers

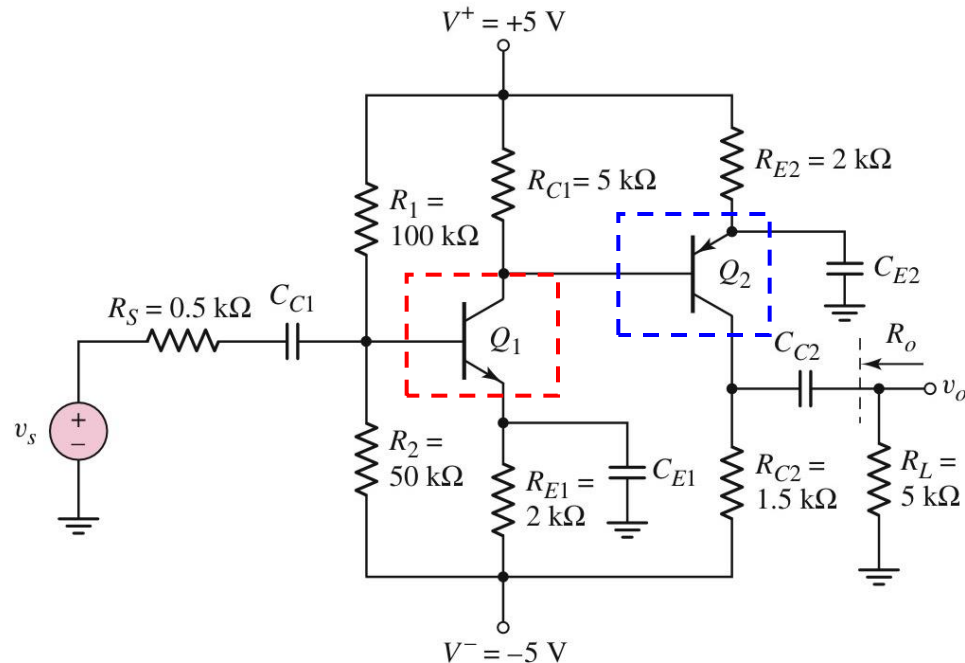6.9.1 Multistage Analysis: Cascade Configuration



Sketch small-signal circuit

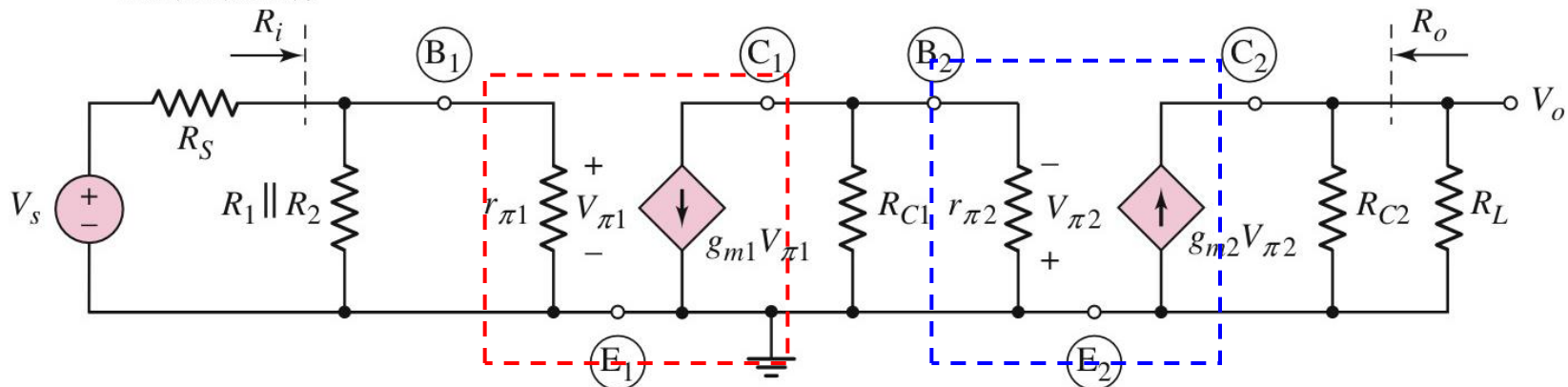


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

6.9 Multistage Amplifiers

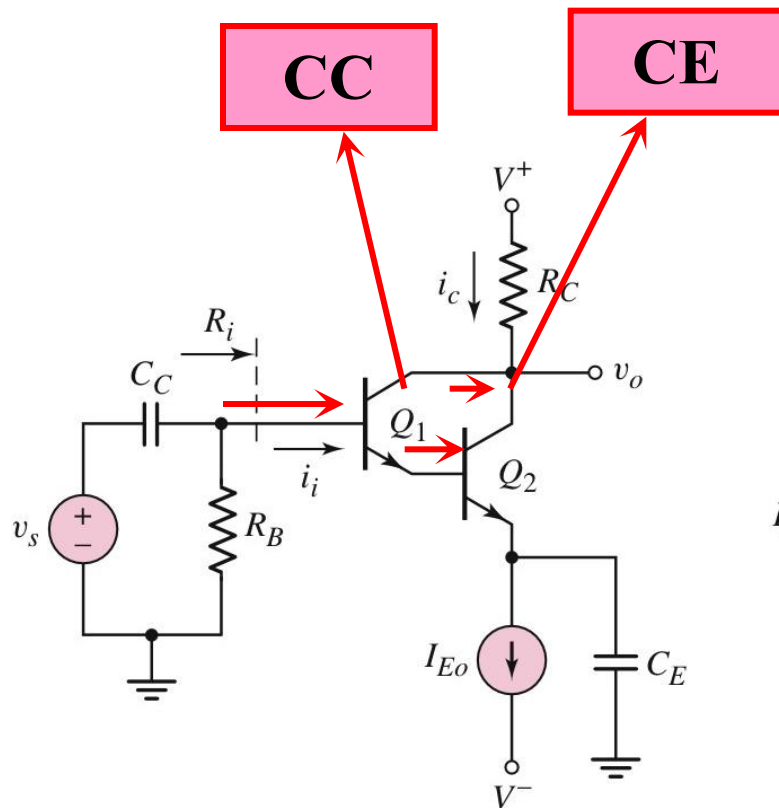6.9.2 Multistage Circuit: Darlington Pair Configuration



(a)


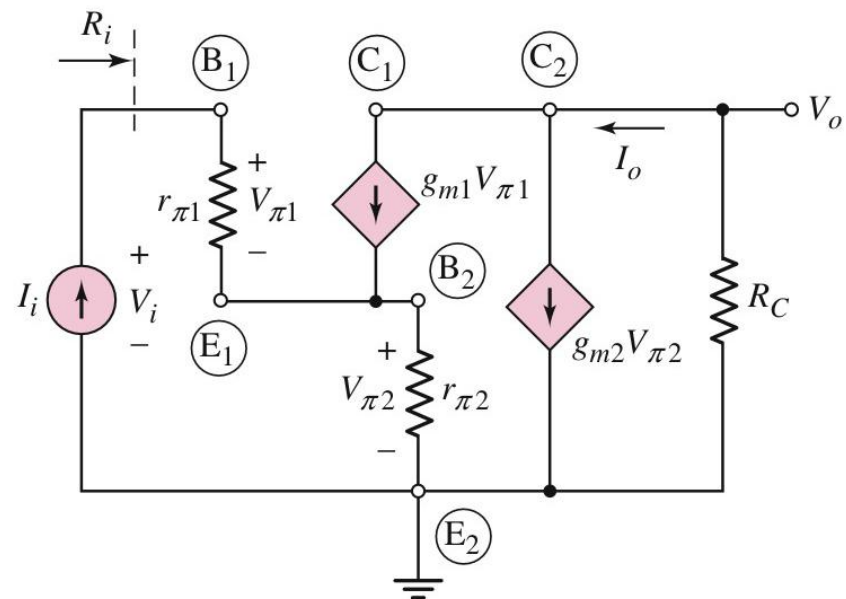


(b)

6.9 Multistage Amplifiers

6.9.2 Multistage Circuit: Darlington Pair Configuration

$$A_i \cong \beta_1 \beta_2$$

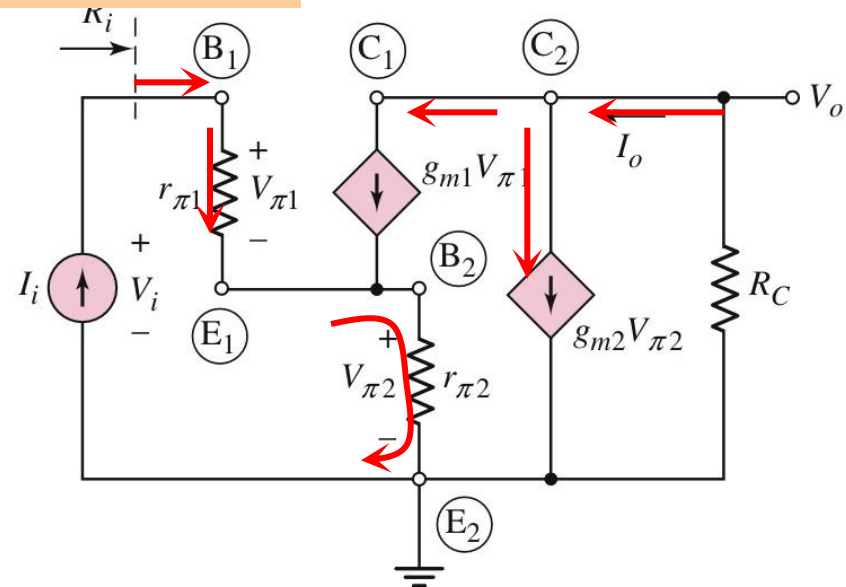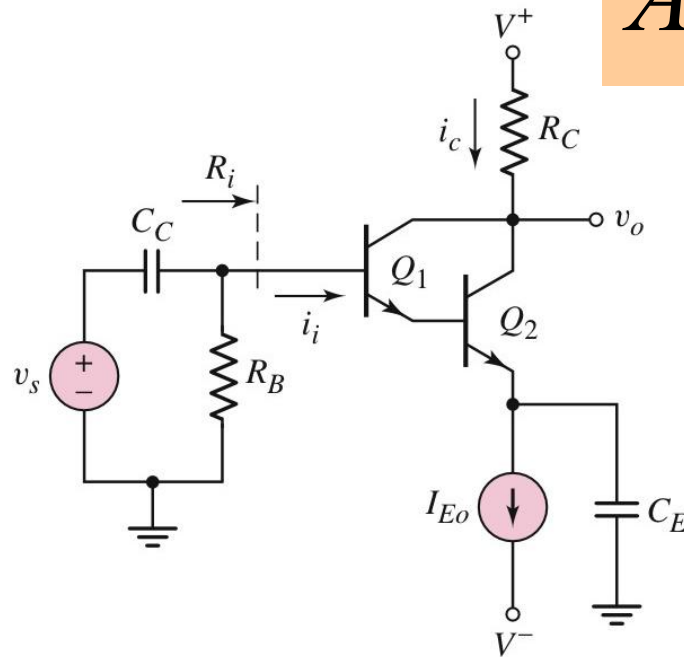

$$V_{\pi 1} = I_i r_{\pi 1}$$


$$I_o = g_{m1} V_{\pi 1} + g_{m2} V_{\pi 2} = \beta_1 I_i + \beta_2 (1 + \beta_1) I_i$$

$$g_{m1} V_{\pi 1} = g_{m1} r_{\pi 1} I_i = \beta_1 I_i$$


$$V_{\pi 2} = (I_i + \beta_1 I_i) r_{\pi 2} \quad A_i = \frac{I_o}{I_i} = \beta_1 + \beta_2 (1 + \beta_1) \cong \beta_1 \beta_2$$

6.9 Multistage Amplifiers

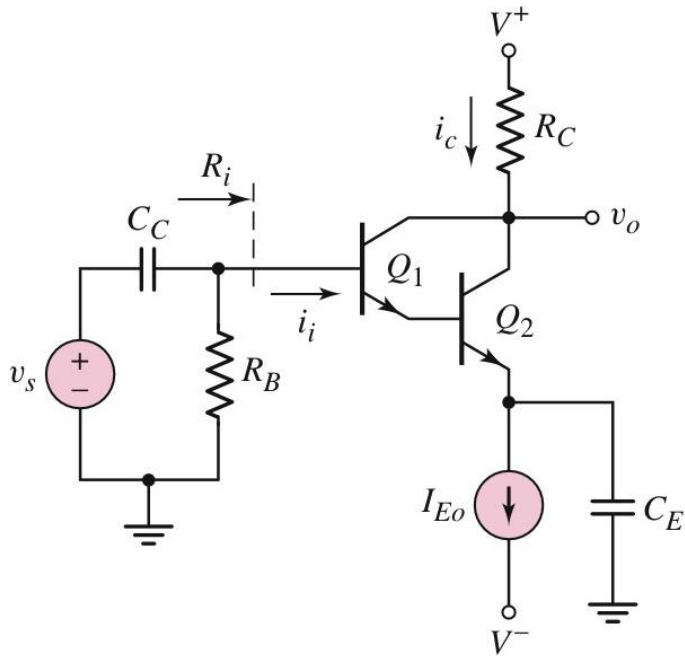6.9.2 Multistage Circuit: Darlington Pair Configuration



(a)

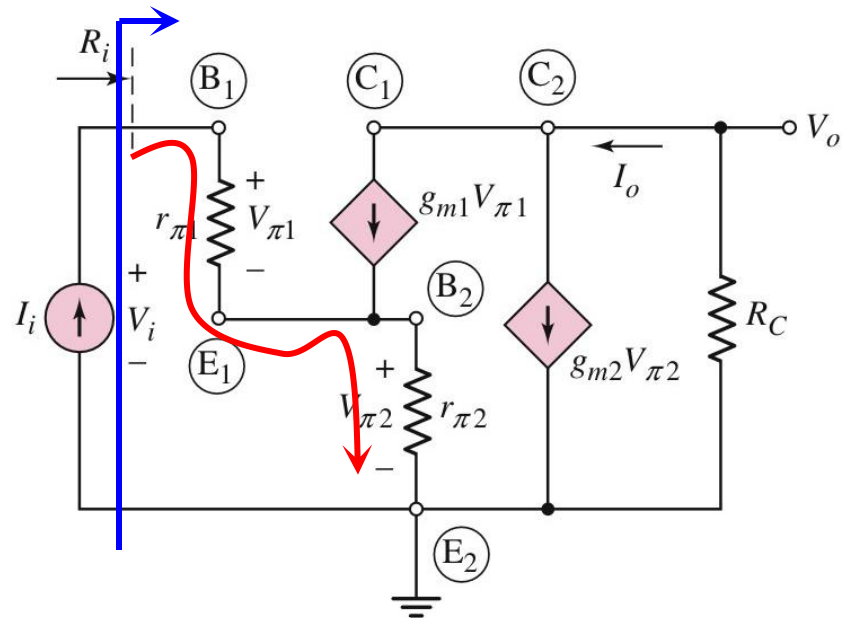

(b)


Copyright © The McGraw-Hill Companies, Inc.
Permission required for reproduction or display.

$$V_i = V_{\pi 1} + V_{\pi 2} = I_i r_{\pi 1} + I_i (1 + \beta_1) r_{\pi 2}$$

$$R_i = r_{\pi 1} + (1 + \beta_1) r_{\pi 2}$$

6.9 Multistage Amplifiers

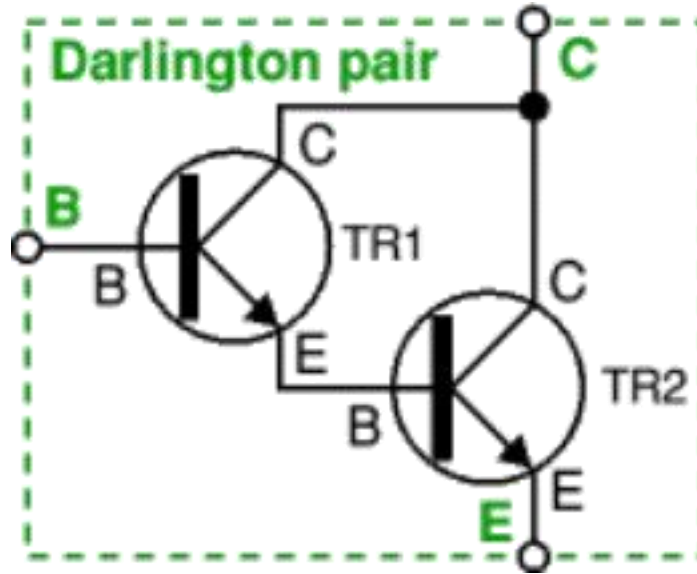6.9.2 Multistage Circuit: Darlington Pair Configuration




A Darlington pair behaves like a single transistor with a very high current gain

6.9 Multistage Amplifiers

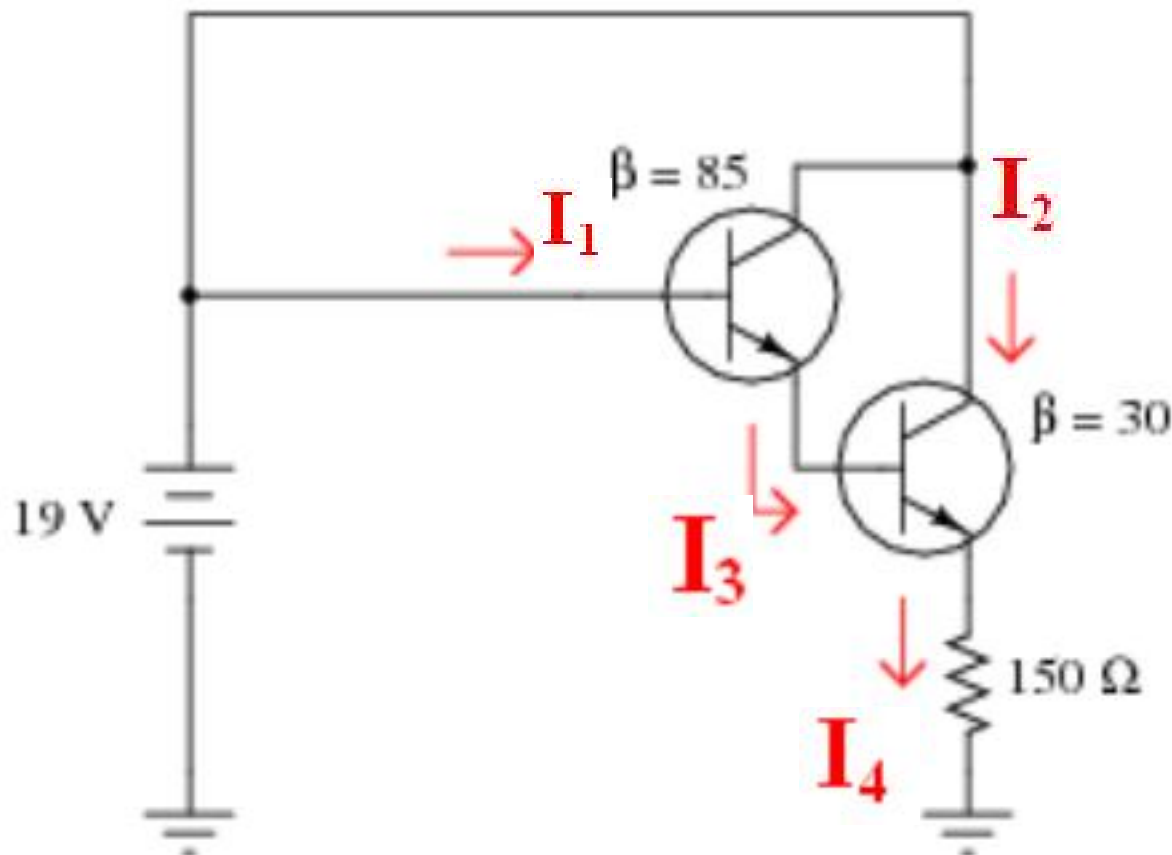6.9.2 Multistage Circuit: Darlington Pair Configuration


Calculate all labeled currents in this Darlington pair circuit, for all transistors, assuming $V_{BE}=0.7\text{ V}$



- | |
|------------------------------------|
| • $I_1 = 44.01\text{ }\mu\text{A}$ |
| • $I_2 = 113.5\text{ mA}$ |
| • $I_3 = 3.785\text{ mA}$ |
| • $I_4 = 117.3\text{ mA}$ |

6.9 Multistage Amplifiers

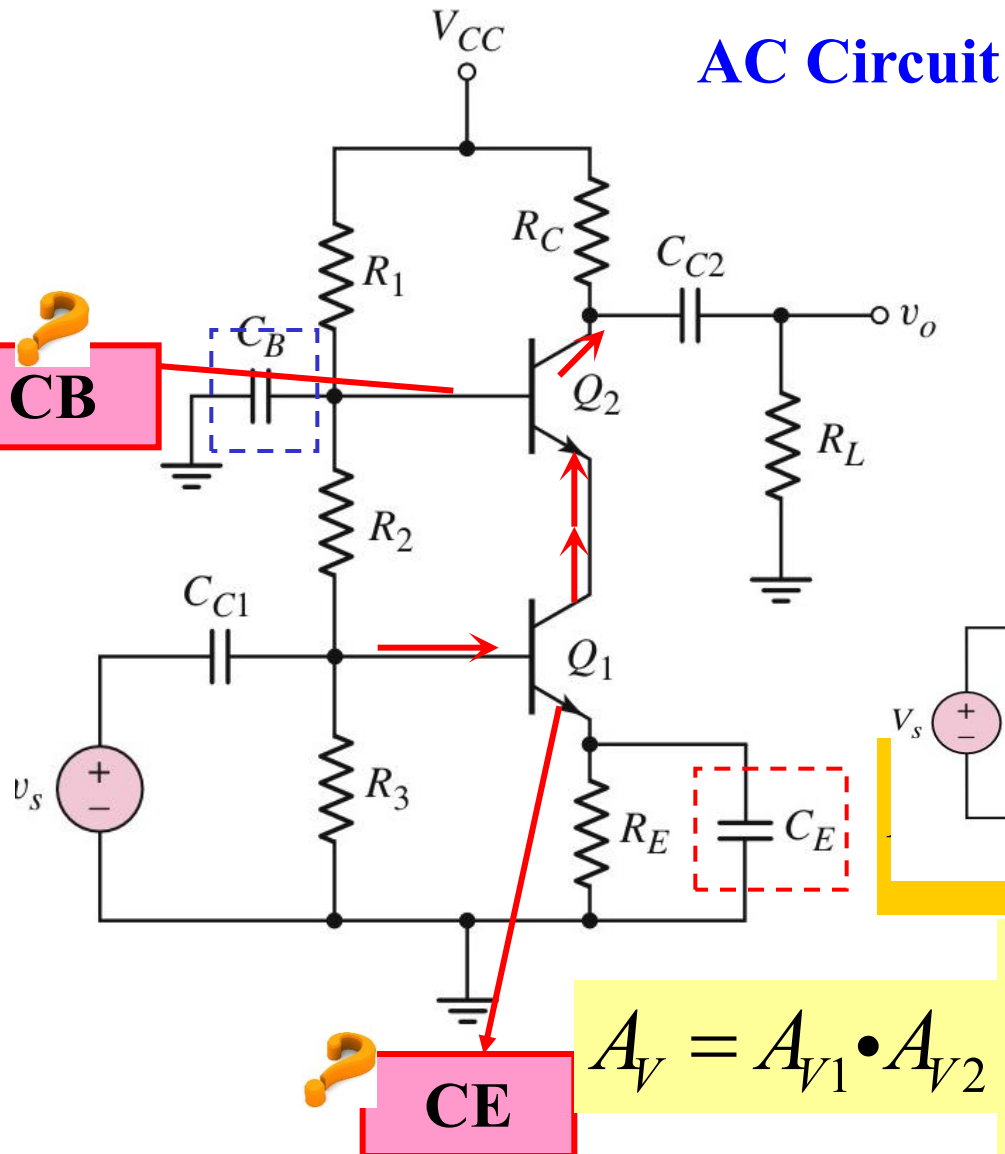
6.9.3 Multistage Circuit: Cascode Configuration



$$A_{V1} = \frac{V_{o1}}{V_i} = -g_{m1}(R_C // R_{L1})$$

$$= -g_{m1}R_{i2} = -g_{m1} \frac{r_{\pi 2}}{1 + \beta_2}$$


$$A_{V2} = g_{m2}(R_C // R_L)$$

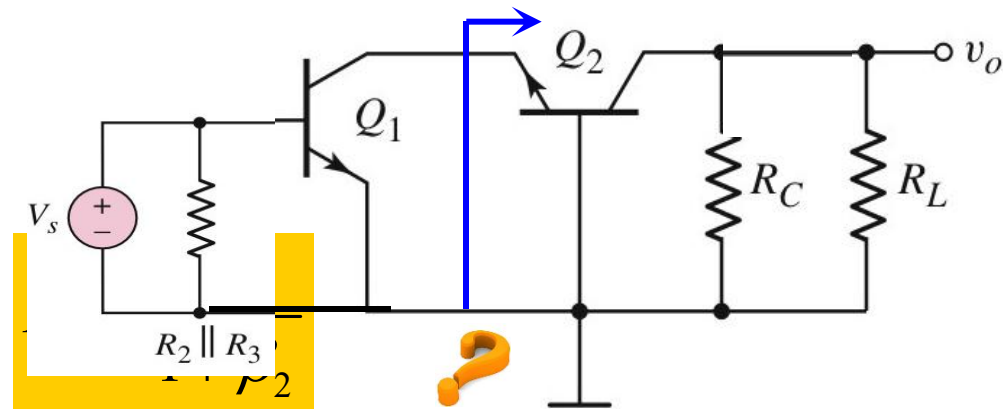

$$A_V = A_{V1} \cdot A_{V2} = -g_{m1} \frac{r_{\pi 2}}{1 + \beta_2} \cdot g_{m2}(R_C // R_L)$$

6.9 Multistage Amplifiers

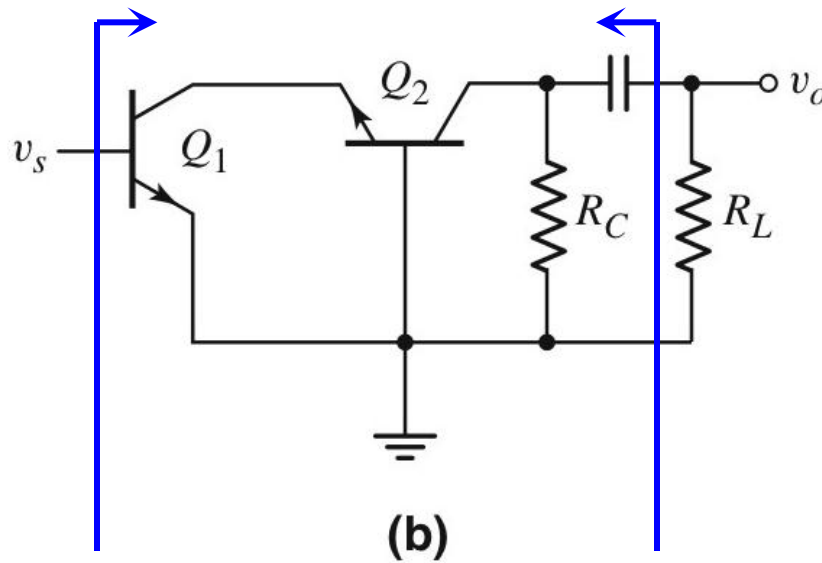6.9.3 Multistage Circuit: Cascode Configuration



$$g_{m2} \left(\frac{r_{\pi 2}}{1 + \beta_2} \right) = \frac{\beta_2}{1 + \beta_2} \cong 1$$

$$A_v \cong -g_{m1} (R_C \parallel R_L)$$



$$A_v = A_{v1} \cdot A_{v2} = -g_{m1} \frac{r_{\pi 2}}{1 + \beta_2} \cdot g_{m2} (R_C \parallel R_L)$$

$$R_i = R_2 \parallel R_3 \parallel r_{\pi 1}$$

$$R_o = R_c$$

6.9 Multistage Amplifiers

6.9.3 Multistage Circuit: Cascode Configuration

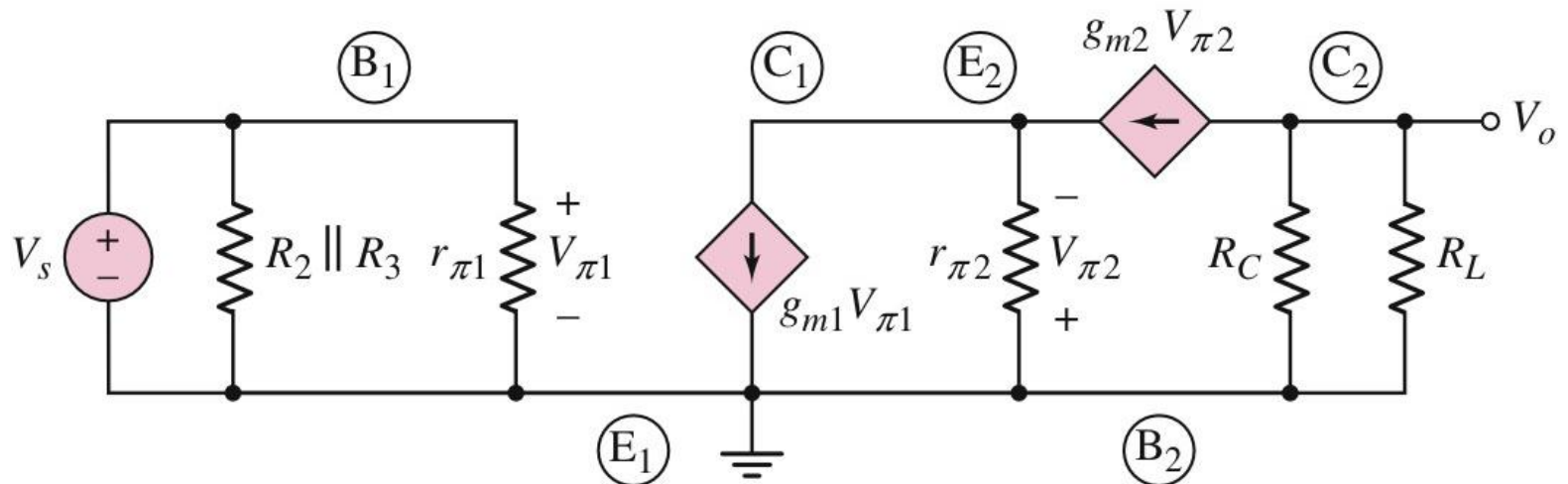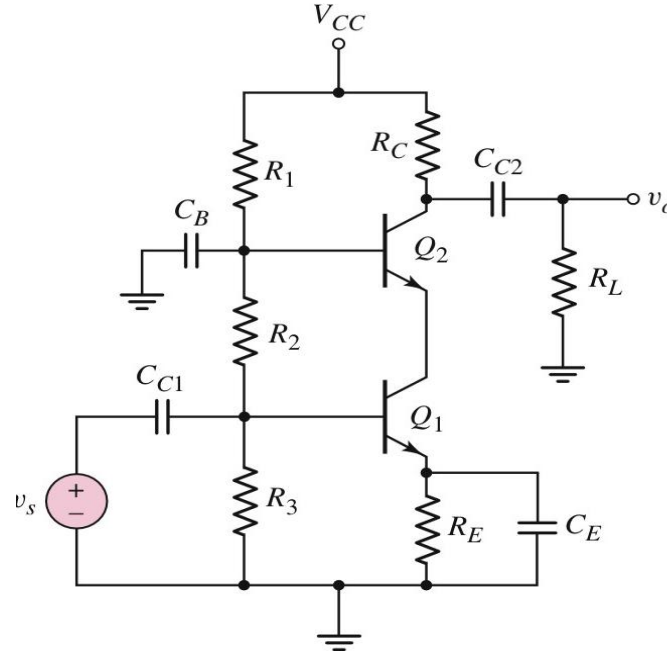

Example 2

Find $A_v = \frac{V_o}{V_i}$, $\beta=50$.

Sol:


(1) Find the Q-point values

$$I_{B1} = \frac{V_{CC} - V_{BE}}{R_{B1}} \approx 40\mu\text{A}$$

$$I_{C1} = \beta \cdot I_{B1} = 2\text{mA}$$

$$I_{B2} = \frac{V_{CC} - V_{BE}}{R_{B2} + (1 + \beta)R_E} \approx 34.3\mu\text{A}$$
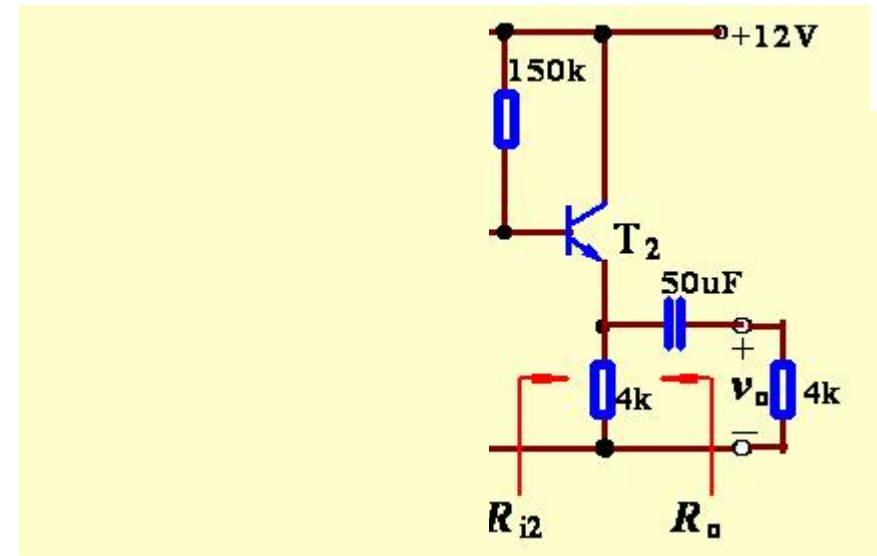
$$I_{C2} = \beta \cdot I_{B2} = 1.7\text{mA}$$



(2) Determine small-signal parameters

$$r_{\pi1} = \frac{26(\text{mV})}{I_{B1}(\text{mA})} = 650\Omega$$

$$r_{\pi2} = \frac{26(\text{mV})}{I_{B2}(\text{mA})} = 758\Omega$$

2. Multistage Amplifiers

(3) Find voltage gain

$$R_{i2} = R_{B2} // [r_{\pi2} + (1 + \beta)(R_{E2} // R_L)]$$

$$= 61k\Omega$$

$$A_{v1} = \frac{V_{o1}}{V_i} = -\frac{\beta \cdot (R_{C1} // R_{i2})}{r_{\pi1}} = -217.5$$


$$\dot{A}_{v2} = \frac{V_o}{V_{i2}} \approx 1 \quad A_v = \frac{V_o}{V_i} = \frac{V_{o1}}{V_i} \cdot \frac{V_o}{V_{o1}} = A_{v1} \cdot A_{v2} = -217.5$$

(4) Determine input and output resistances

$$R_i = R_{B1} // r_{\pi1} \approx r_{\pi1} = 650\Omega$$


$$R_o = R_{E2} // \frac{(R_{S1} // R_{B1}) + r_{\pi2}}{1 + \beta} = R_{E2} // \frac{(R_{o1} // R_{B2}) + r_{\pi2}}{1 + \beta}$$
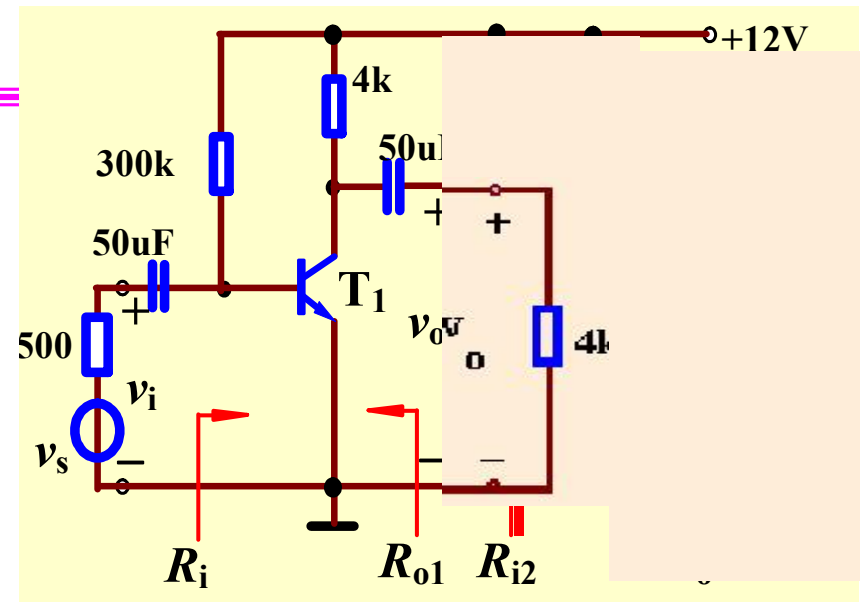
$$= 4k // \frac{(4k // 150k) + 0.758k}{1 + 50} \approx 95\Omega$$




$$\dot{A}_v = -115.87$$

More Complicated Amplifier ...

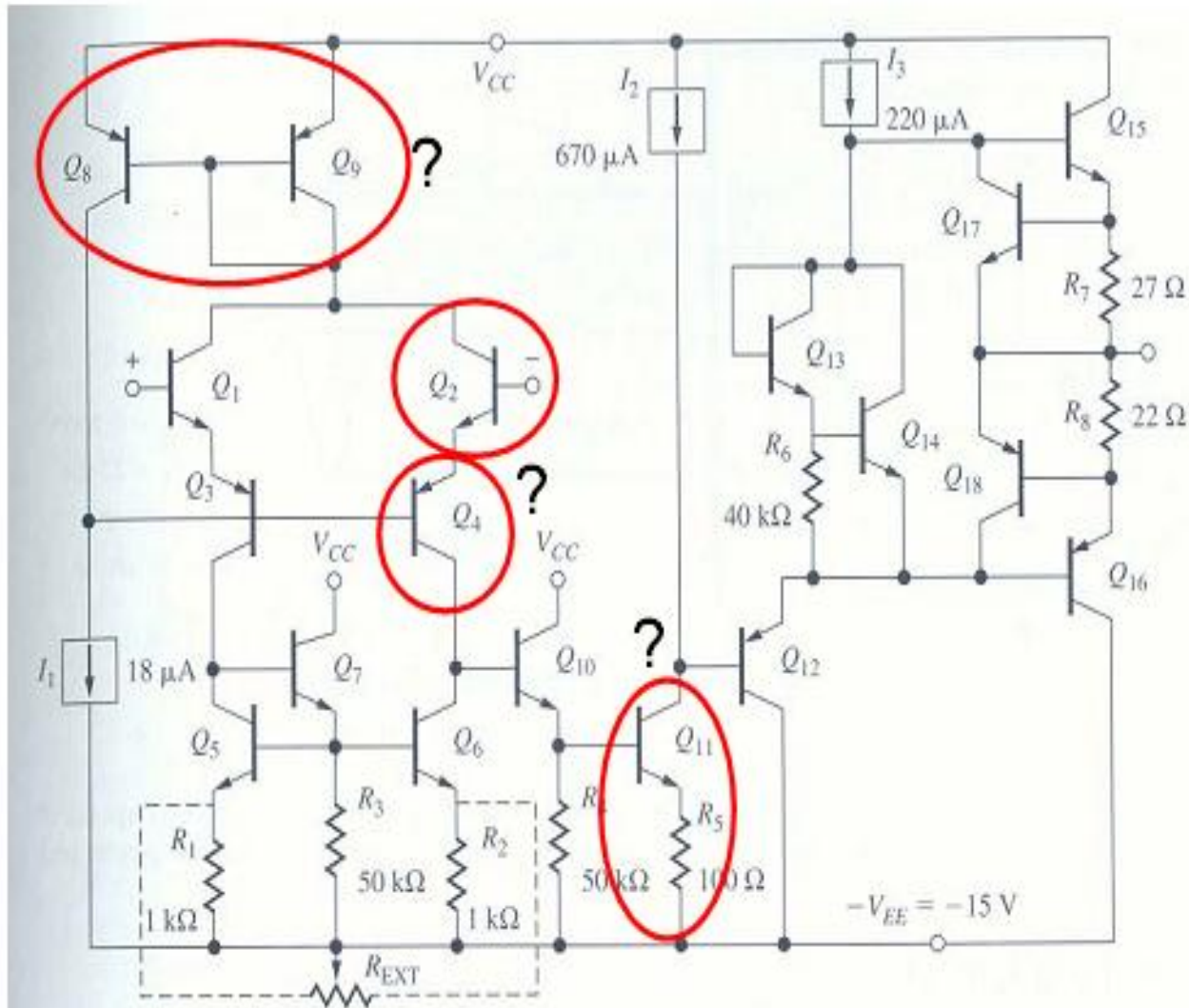

Circuit schematic for $\mu A741$ op amp

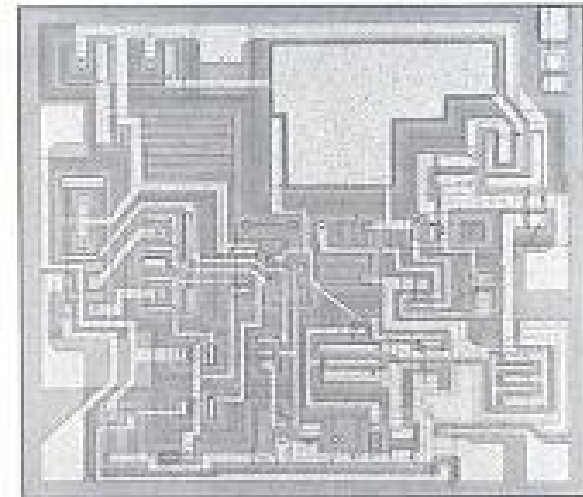

$\mu A741$ Die Photograph (Courtesy of Fairchild Semiconductor)