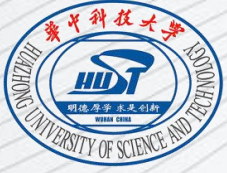


Huazhong University
of Science & Technology

Electronic Circuit of Communications


School of Electronic Information
and Communications

Jiaqing Huang





Parallel Resonance

Frequency Selective Circuits

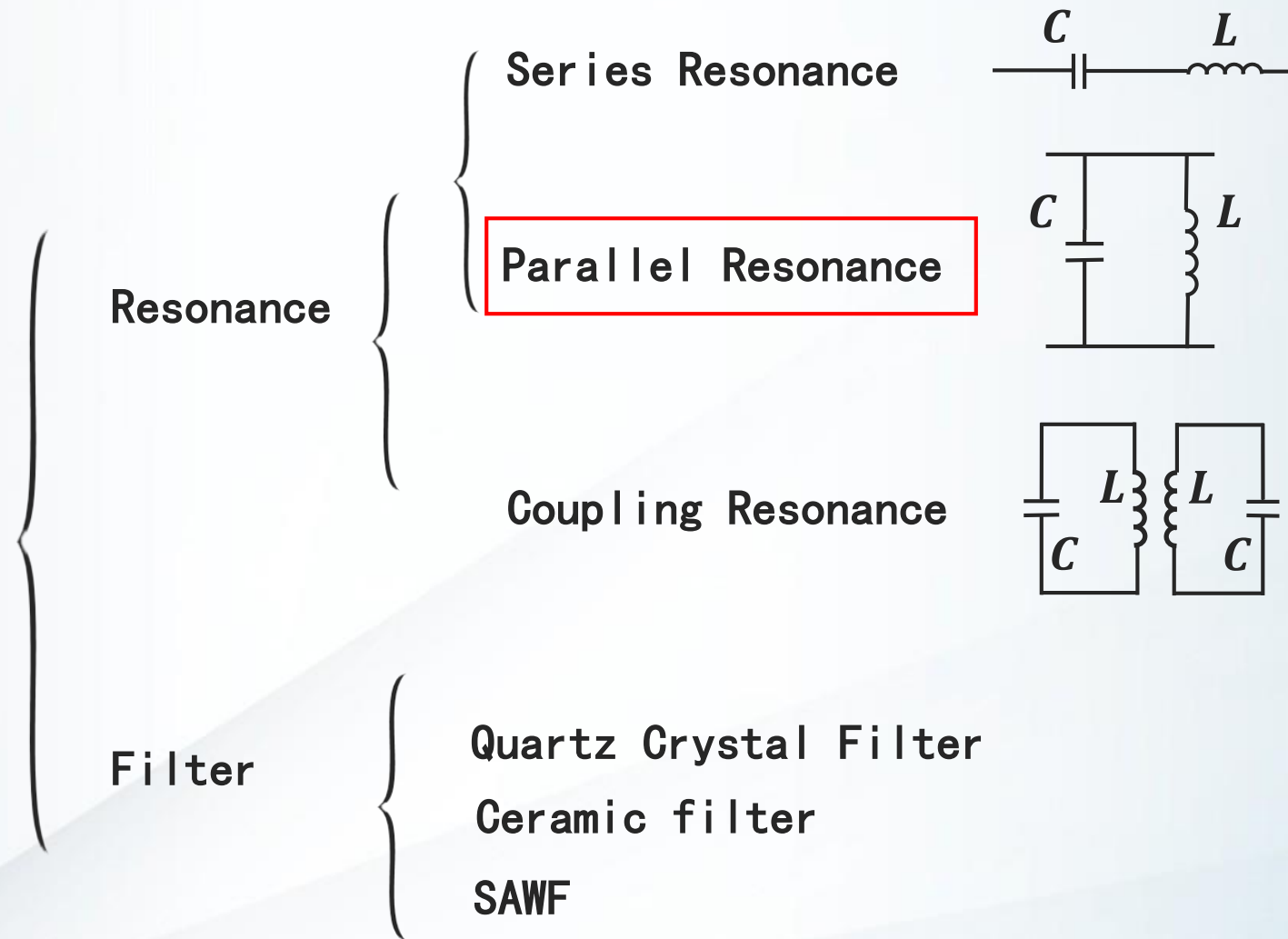


Parallel Resonant Circuit

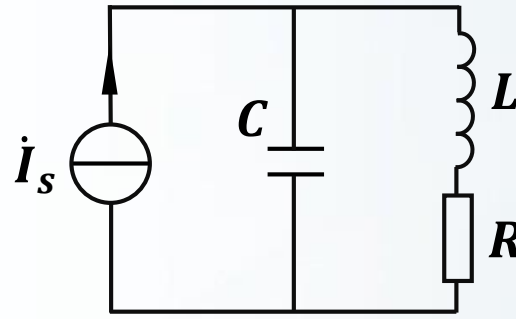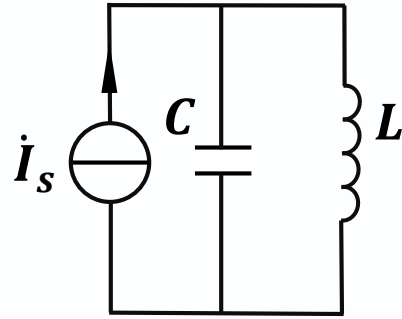

- Inductor = L with loss resistance R
- Capacitor = C with loss resistance R



non-ignorable

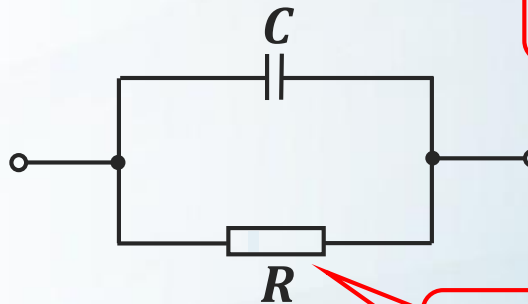

ignorable

Parallel Resonant Circuit—Impedance Z 、Admittance Y




High Q , $\omega L \gg R$

$$\left\{ \begin{array}{l} \text{Impedance } Z = \frac{(R + j\omega L) \frac{1}{j\omega C}}{(R + j\omega L) + \frac{1}{j\omega C}} = \frac{(\cancel{R} + j\omega L) \frac{1}{j\omega C}}{R + j(\omega L - \frac{1}{\omega C})} \\ \\ \approx \frac{\frac{L}{C}}{R + j(\omega L - \frac{1}{\omega C})} = \frac{1}{\frac{CR}{L} + j(\omega C - \frac{1}{\omega L})} \end{array} \right.$$

$$\left\{ \begin{array}{l} \text{Admittance } Y = G + jB = \frac{CR}{L} + j\left(\omega C - \frac{1}{\omega L}\right) \end{array} \right.$$



$$\left\{ \begin{array}{l} \text{Conductance } G = \frac{CR}{L} \end{array} \right.$$
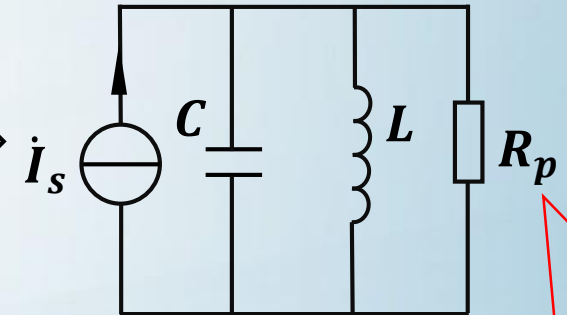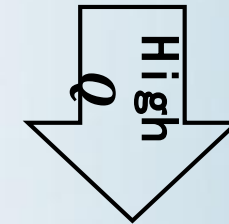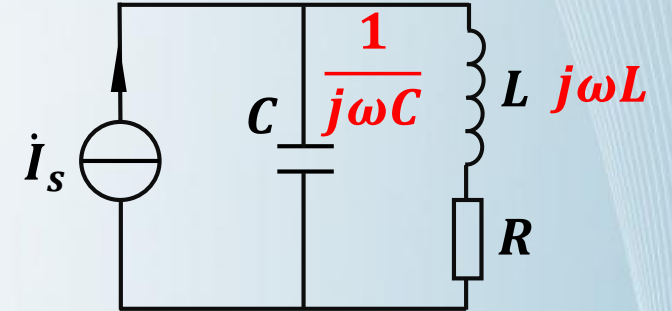
$$\left\{ \begin{array}{l} \text{Susceptance } B = \omega C - \frac{1}{\omega L} \end{array} \right.$$



$$R_p = \frac{1}{G} = \frac{L}{CR}$$

Parallel Resonant Circuit— R_p vs R

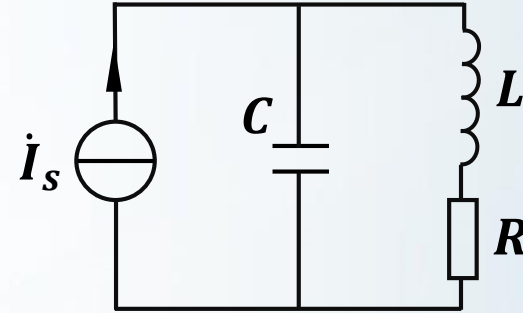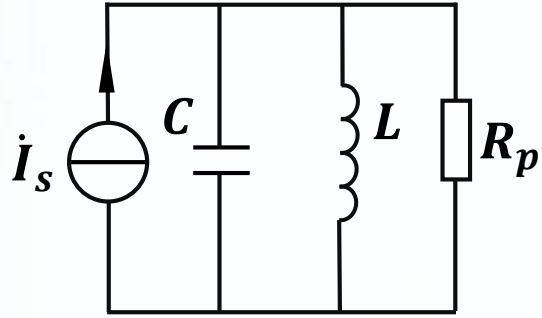


$$R_p = \frac{1}{G} = \frac{L}{CR}$$


Relationship of R_p & R



Parallel Resonant Circuit—Admittance Y

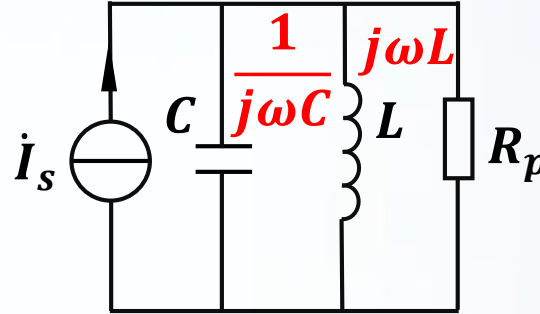
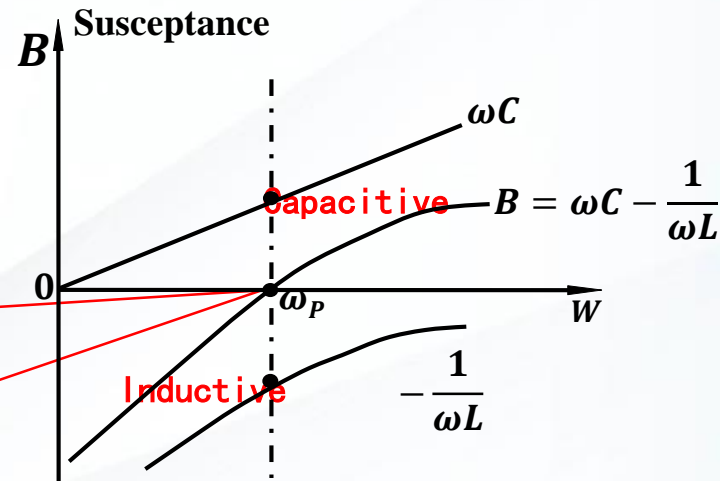
$$\text{Susceptance } B = \omega C - \frac{1}{\omega L} \Leftarrow Y = G + jB = \frac{CR}{L} + j\left(\omega C - \frac{1}{\omega L}\right)$$




Resonant Frequency ω_p :



$$B = \omega_p C - \frac{1}{\omega_p L} = 0$$
$$\Rightarrow \omega_p = \frac{1}{\sqrt{LC}}$$

- 1) $\omega > \omega_p$, $B > 0$ Capacitive, ICE
- 2) $\omega < \omega_p$, $B < 0$ Inductive, ELI
- 3) $\omega = \omega_p$, $B = 0$ purely resistive

Parallel Resonant Circuit—Admittance Y

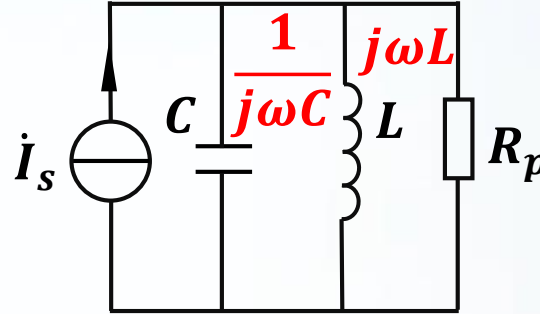
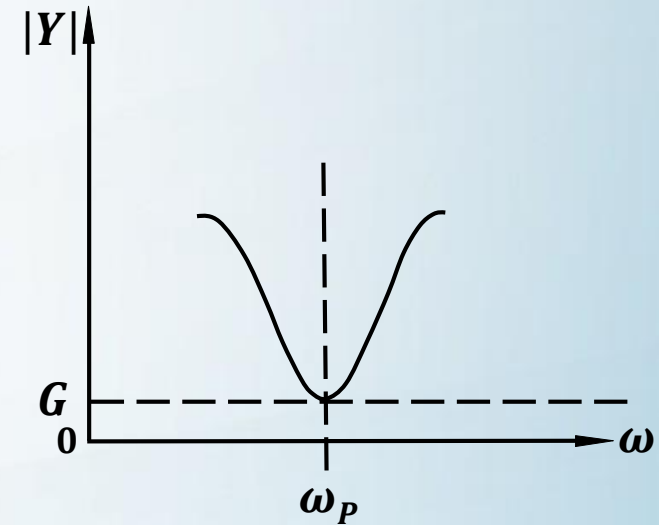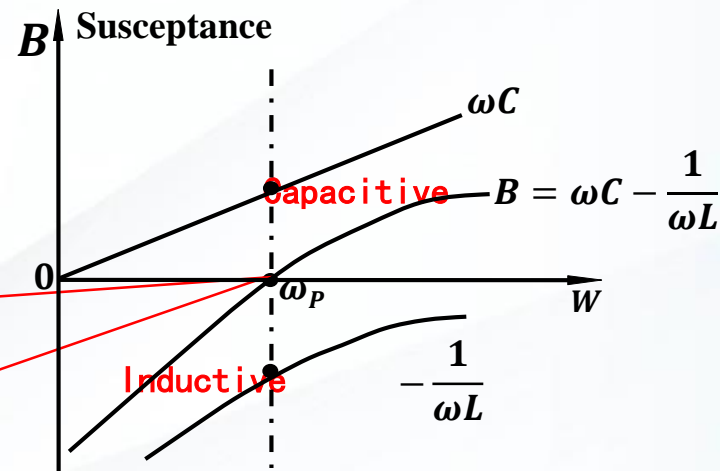
$$\text{Susceptance } B = \omega C - \frac{1}{\omega L} \Leftarrow Y = G + jB = \frac{CR}{L} + j \left(\omega C - \frac{1}{\omega L} \right)$$



Resonant Frequency ω_p :

$$B = \omega_p C - \frac{1}{\omega_p L} = 0$$

$$\Rightarrow \omega_p = \frac{1}{\sqrt{LC}}$$

Parallel Resonant Circuit— Q

$$Q_p = \frac{\omega_p L}{R} = \frac{\frac{1}{\omega_p C}}{R} = \frac{\rho}{R} = \frac{(\text{Reactance})X}{(\text{Resistance})R}$$

R version
 Q_p



$$Q_p = \frac{1}{\omega_p L} \cdot R_p = \omega_p C \cdot R_p$$

R_p version
 Q_p

$$Q_p = \frac{\frac{1}{\omega_p L}}{G} = \frac{\omega_p C}{G} = \frac{(\text{Susceptance})B}{(\text{Conductance})G}$$

G version
 Q_p

Reason: R and R_p

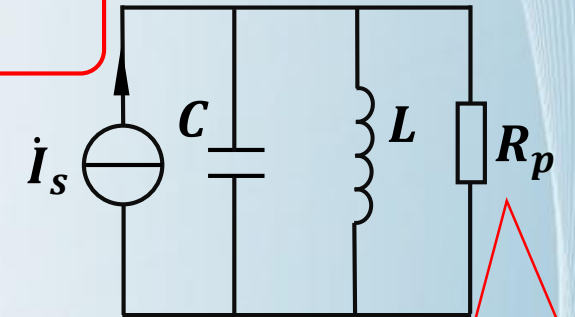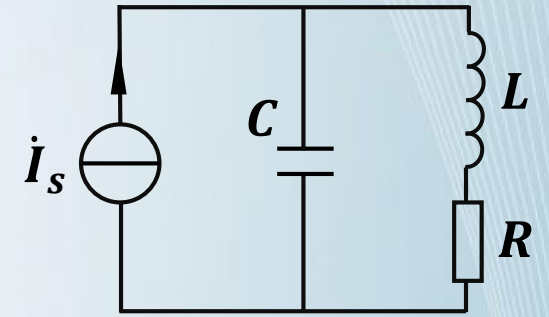


$$R_p = \frac{1}{G} = \frac{L}{CR}$$

Parallel Resonant Circuit— Current Resonance

➤ Parallel Resonant

Voltage
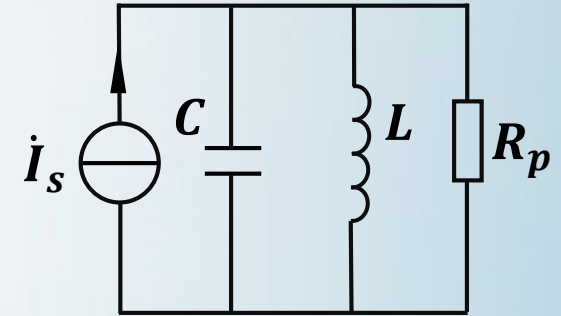
$$\begin{cases} \dot{I}_{Cp} = j\omega_p C \cdot R_p \dot{I}_s = j\omega_p C \cdot R_p \dot{I}_s = jQ_p \dot{I}_s \\ \dot{I}_{Lp} = \frac{1}{j\omega_p L} \cdot R_p \dot{I}_s = -j \frac{1}{\omega_p L} R_p \dot{I}_s = -jQ_p \dot{I}_s \end{cases}$$



$$Q_p = \frac{1}{\omega_p L} \cdot R_p = \omega_p C \cdot R_p$$

$\therefore \dot{I}_{Cp} = -\dot{I}_{Lp}$ same current value , Q_p times of source current

Parallel Resonant Circuit— Detuning Coefficient

$$Q_p = \frac{1}{\omega_p L} \cdot R_p = \omega_p C \cdot R_p$$

$$= \frac{1}{\frac{\omega_p L}{G}} = \frac{\omega_p C}{G}$$

Resonance , $Q_p = \frac{(\text{Susceptance})_B}{(\text{Conductance})_G}$

Detuning , $\xi = \frac{(\text{Susceptance sum})_B}{(\text{Conductance})_G} = \frac{\omega C - \frac{1}{\omega L}}{G}$

$\xi = 0$ denote resonance

$$\omega \approx \omega_p$$

$$= \frac{\omega_p C}{G} \left(\frac{\omega}{\omega_p} - \frac{\omega_p}{\omega} \right) = Q_p \left(\frac{\omega}{\omega_p} - \frac{\omega_p}{\omega} \right) = Q_p \frac{(\omega + \omega_p)(\omega - \omega_p)}{\omega_p \omega}$$


$$\xi \approx Q_p \frac{2(\omega - \omega_p)}{\omega_p}$$

$$\xi = Q_p \cdot \frac{2\Delta\omega}{\omega_p} \text{ 或 } \xi = Q_p \cdot \frac{2\Delta f}{f_p}$$

$\xi \neq 0$ denote detuning value

Parallel Resonant Circuit—Resonance Curve
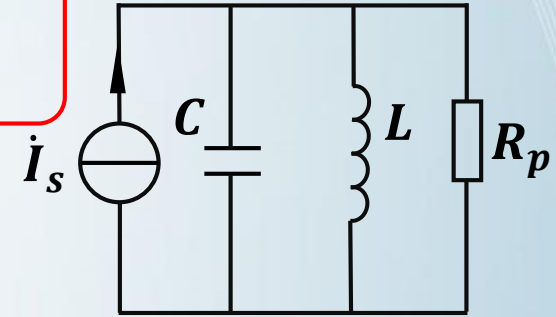
$$Y = \frac{CR}{L} + j\left(\omega C - \frac{1}{\omega L}\right) = G_p + j\left(\omega C - \frac{1}{\omega L}\right)$$




➤ Voltage: $\dot{V} = \frac{\dot{I}_s}{Y} = \frac{\dot{I}_s}{G_p + j\left(\omega C - \frac{1}{\omega L}\right)} \sim \omega$

➤ Resonance Curve :

$$N(f) = \frac{\dot{V}}{\dot{V}_0} = \frac{\frac{\dot{I}_s}{G_p + j\left(\omega C - \frac{1}{\omega L}\right)}}{\frac{\dot{I}_s}{G_p}} = \frac{G_p}{G_p + j\left(\omega C - \frac{1}{\omega L}\right)} = \frac{1}{1 + j\left(\frac{\omega C - \frac{1}{\omega L}}{G_p}\right)}$$

$$\Rightarrow N(f) = \frac{1}{1 + j\xi}$$
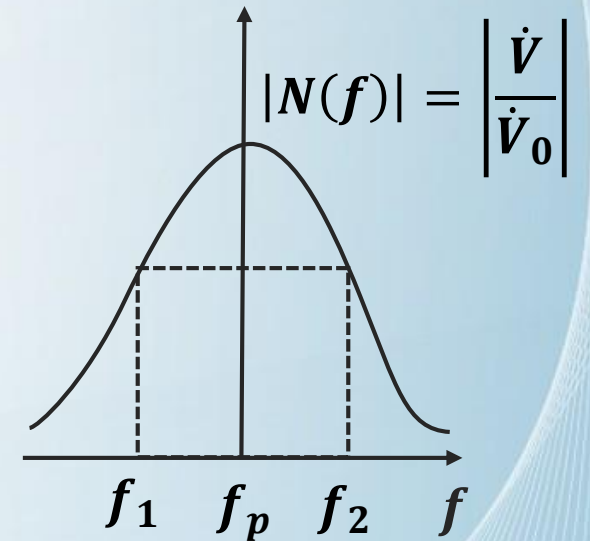
$$\xi = \frac{\omega C - \frac{1}{\omega L}}{G}$$



Amplitude-Frequency

Parallel Resonant Circuit— Bandwidth

➤ Bandwidth: scope among \dot{V} drop to 0.707 of \dot{V}_0

$$B = 2\Delta f_{0.7} = |f_2 - f_1|$$

Curve $N(f) = \frac{\dot{V}}{\dot{V}_0} = \frac{1}{1+j\xi}$

AF: $|N(f)| = \frac{1}{\sqrt{1+\xi^2}} = \frac{1}{\sqrt{2}}$



$$\left. \begin{array}{l} \Rightarrow \text{if } 2\Delta f_{0.7} \\ \xi = 1 \\ \xi = Q_p \cdot \frac{2\Delta f}{f_p} \end{array} \right\}$$

$$\Rightarrow 1 = Q_p \cdot \frac{2\Delta f_{0.7}}{f_p}$$

$$1 = Q_p \cdot \frac{B}{f_p}$$

$$2\Delta f = 2\Delta f_{0.7}$$

$$Q_p \cdot B = f_p$$

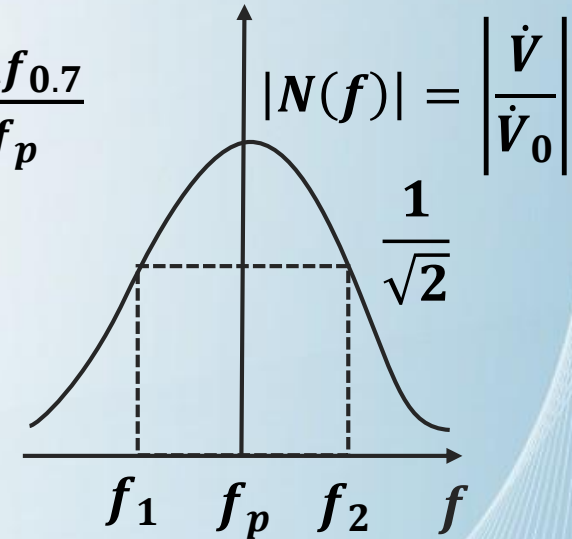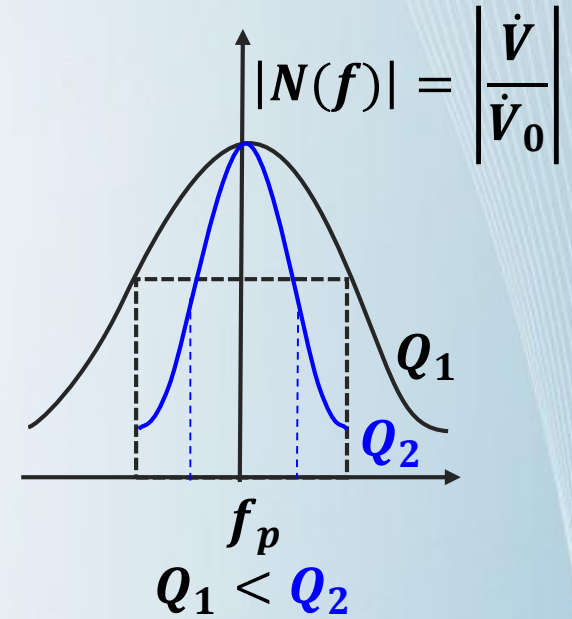


Amplitude-Frequency (AF)

Parallel Resonant Circuit— Phase-Frequency (PF) Curve

$$N(f) = \frac{\dot{V}}{\dot{V}_0} = \frac{1}{1 + j\xi}$$

➤ PF: $\psi = -\arctan \xi$

$Q \uparrow$ linearity \downarrow

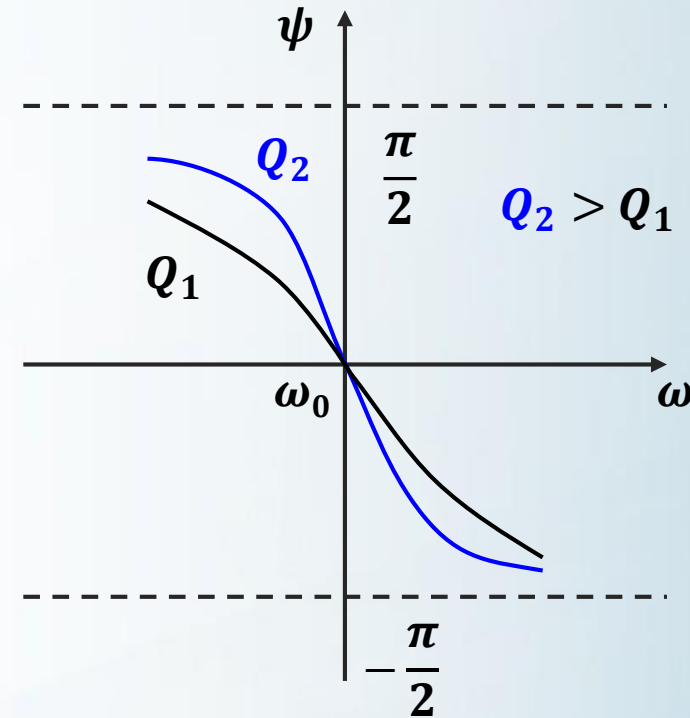

Parallel Resonant Circuit— With Load

Unloaded Q :


$$Q_p = \frac{\omega_p L}{R} = \frac{1}{\omega_p L} \cdot R_p = \frac{1}{\omega_p L} \cdot \frac{1}{G_p}$$

Loaded Q :

$$Q_L = \frac{1}{\omega_p L} \cdot \frac{1}{G_p + G_s + G_L}$$

Consider source resistance &
load resistance
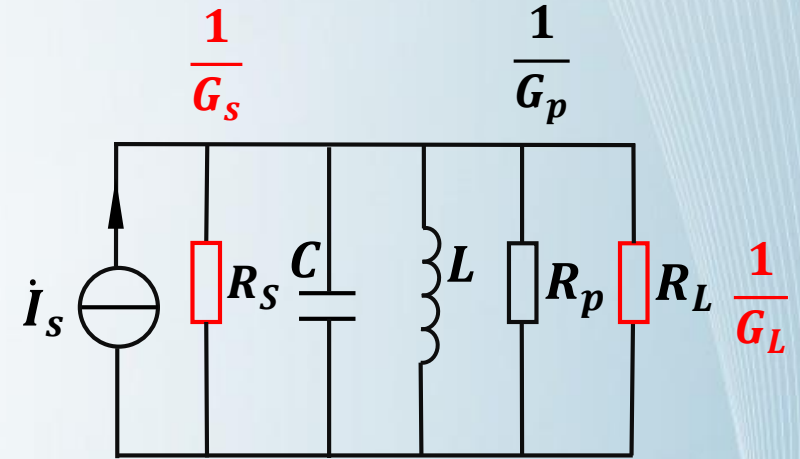
$$Q_L \downarrow \Rightarrow B \uparrow$$



Summary—Parallel Resonant Circuit

➤ Resonance Curve: $N(f) = \frac{\dot{V}}{\dot{V}_0} = \frac{1}{1+j\xi}$

$$\because \rho = \omega_p L = \frac{1}{\omega_p C}$$

Amplitude-Frequency $|N(f)| = \left| \frac{\dot{V}}{\dot{V}_0} \right|$

Resonance : $Q_p = \frac{\omega_p L}{R} = \frac{\frac{1}{\omega_p C}}{R} = \frac{\rho}{R}$

R version of Q_p

$$Q_p = \frac{1}{\omega_p L} \cdot R_p = \omega_p C \cdot R_p$$

R_p version of Q_p

$$Q_p = \frac{(\text{Susceptance})_B}{(\text{Conductance})_G} = \frac{\frac{1}{\omega_p L}}{G} = \frac{\omega_p C}{G}$$

G version of Q_p

Detuning : $\xi = \frac{(\text{Susceptance sum})_B}{(\text{Conductance})_G} = \frac{\omega C - \frac{1}{\omega L}}{G} \approx Q_p \cdot \frac{2\Delta f}{f_p} \Rightarrow Q_p \cdot B = f_p$

Phase-Frequency $\psi = -\arctan \xi$