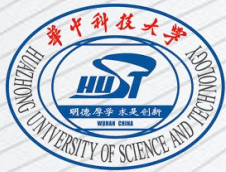


Huazhong University  
of Science & Technology

# Electronic Circuit of Communications

School of Electronic Information  
and Communications


Jiaqing Huang



# Equivalent Conversion


# Review

## Parallel Resonance $Q_p$

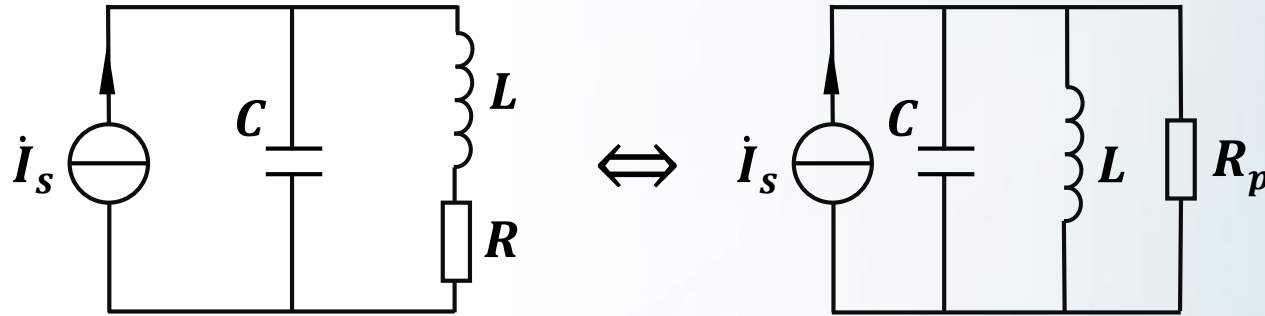

$$Q_p = \frac{\omega_p L}{R}$$

Loss Resistance

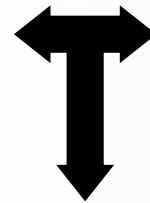


$$Q_p = \frac{R_p}{\omega_p L}$$

$$Q_p^2 \cdot R = R_p$$


$$R \overset{Q^2}{\Leftrightarrow} R_p$$


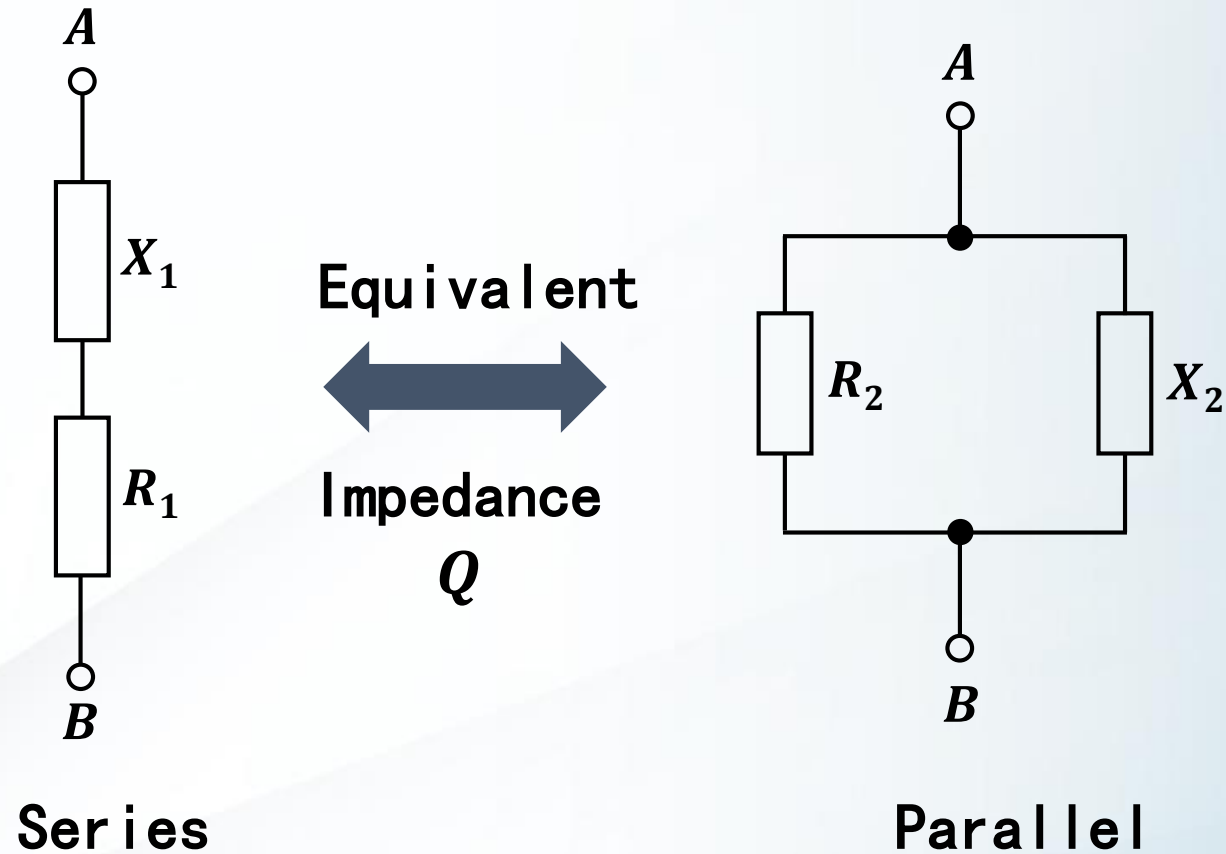
# Equivalent Conversion of Series & Parallel Circuit



# Equivalent Conversion

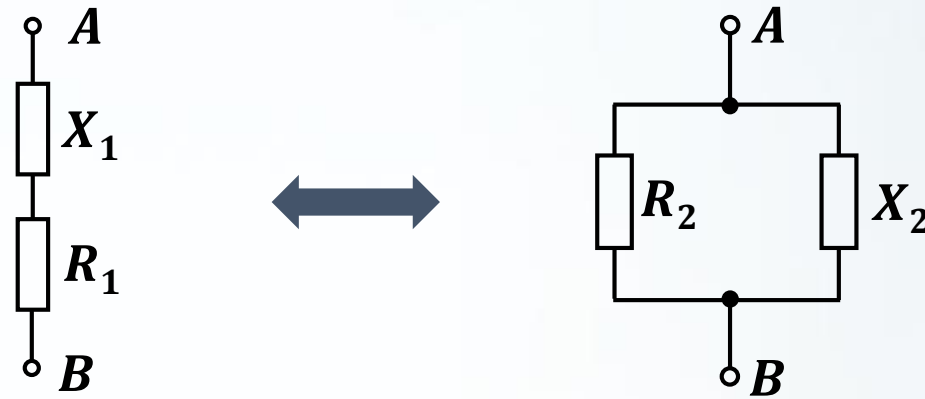

Equivalent Impedance

$$R_1 + jX_1 = \frac{R_2(jX_2)}{R_2 + jX_2} = \frac{R_2X_2^2}{R_2^2 + X_2^2} + j \frac{R_2^2X_2}{R_2^2 + X_2^2}$$

$$\Rightarrow \begin{cases} R_1 = \frac{R_2X_2^2}{R_2^2 + X_2^2} \\ X_1 = \frac{R_2^2X_2}{R_2^2 + X_2^2} \end{cases} \Rightarrow \begin{cases} R_2 = R_1 \left( 1 + \left( \frac{R_2}{X_2} \right)^2 \right) = R_1(1 + Q^2) \\ X_2 = X_1 \left( 1 + \left( \frac{X_2}{R_2} \right)^2 \right) = X_1 \left( 1 + \frac{1}{Q^2} \right) \end{cases}$$

Equivalent  $Q$

$$Q = \frac{X_1}{R_1} = \frac{R_2}{X_2}$$


High  $Q$  ( $\geq 10$ )

$$\Rightarrow \begin{cases} R_2 \approx R_1 Q^2 & \text{Parallel} \gg \text{Series} \\ X_2 \approx X_1 & \text{No change} \end{cases}$$

# Review


$R_s$   $R_L$  Small: Series

分压小

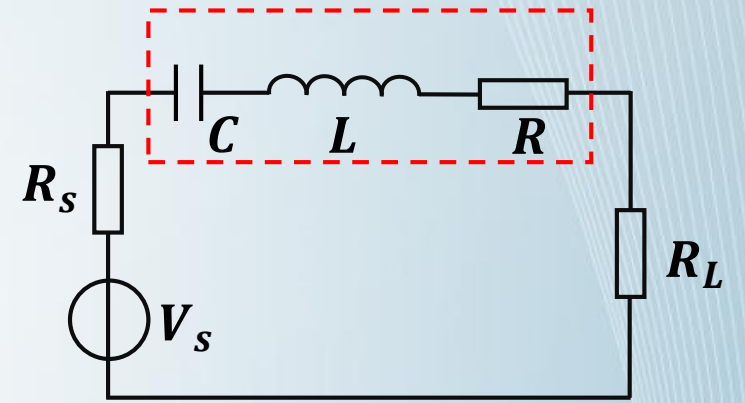

$R_s$   $R_L$  Big: Parallel

分流小

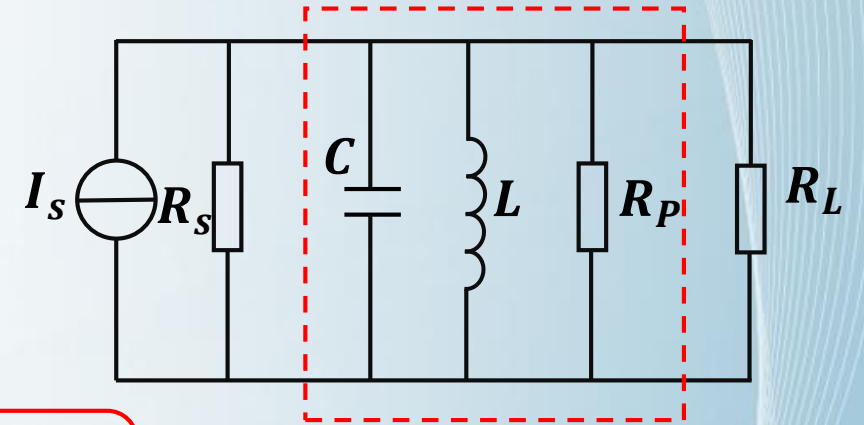


$R_s$   $R_L$  Middle:



Impedance Conversion

## Tap Connection

# Tap-Connected

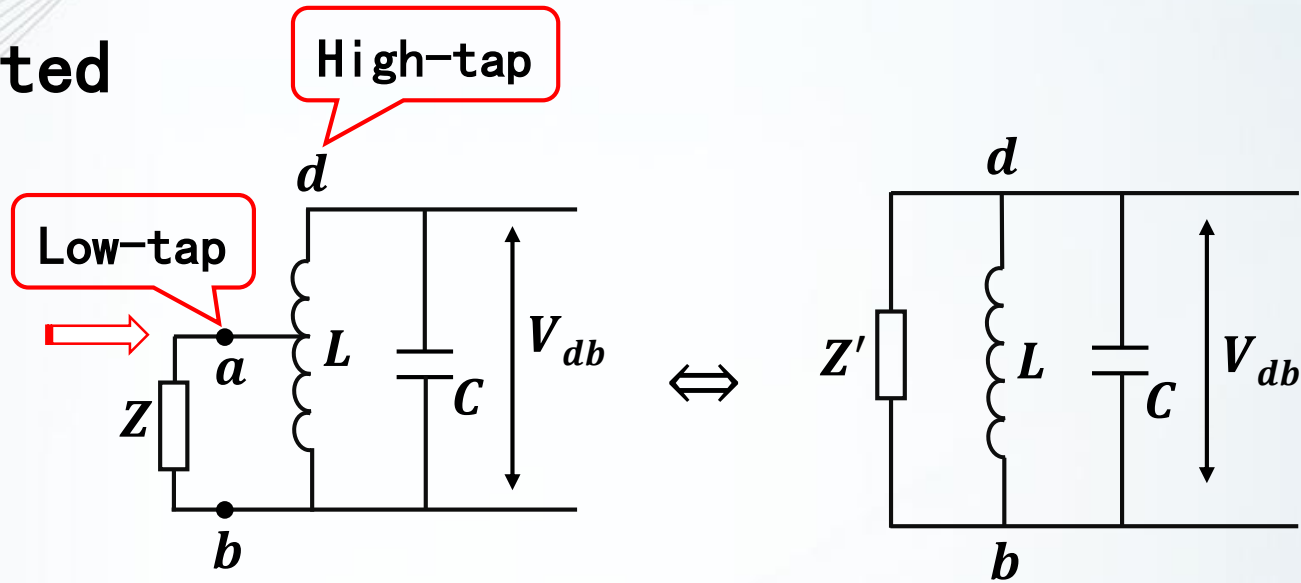

Access Factor:  $p = \frac{V_{ab}}{V_{db}} \leq 1$

Equivalent Power:  $\frac{V_{ab}^2}{Z} = \frac{V_{db}^2}{Z'} \Rightarrow Z' = \left(\frac{V_{db}}{V_{ab}}\right)^2 Z = \frac{1}{p^2} Z$


Low-tap  $\rightarrow$  High-tap    Equivalent impedance  $\uparrow \frac{1}{p^2}$

Voltage  $\uparrow \frac{1}{p}$

Current  $\downarrow p$



# Tap-Connected

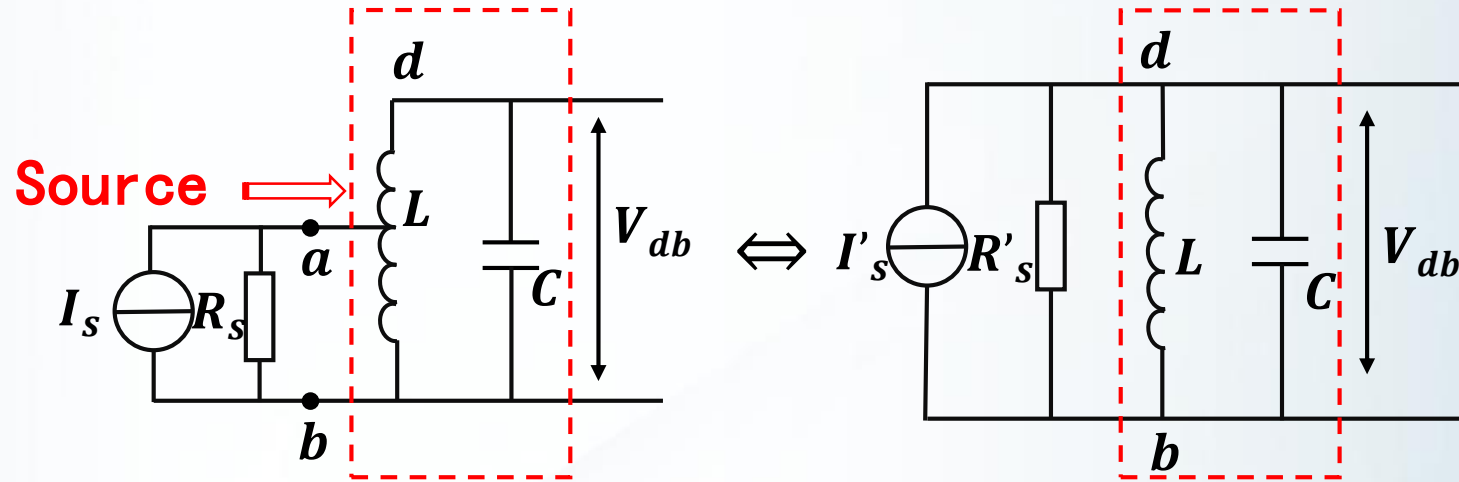

Low-tap  $\rightarrow$  High-tap :

$$R'_s = \frac{1}{p^2} R_s \Leftrightarrow R'_s \uparrow \frac{1}{p^2}$$


Equivalent Power :

$$I_s \cdot V_{ab} = I'_s \cdot V_{db}$$

$$I'_s = p \cdot I_s \Leftrightarrow I'_s \downarrow p$$



# Tap-Connected

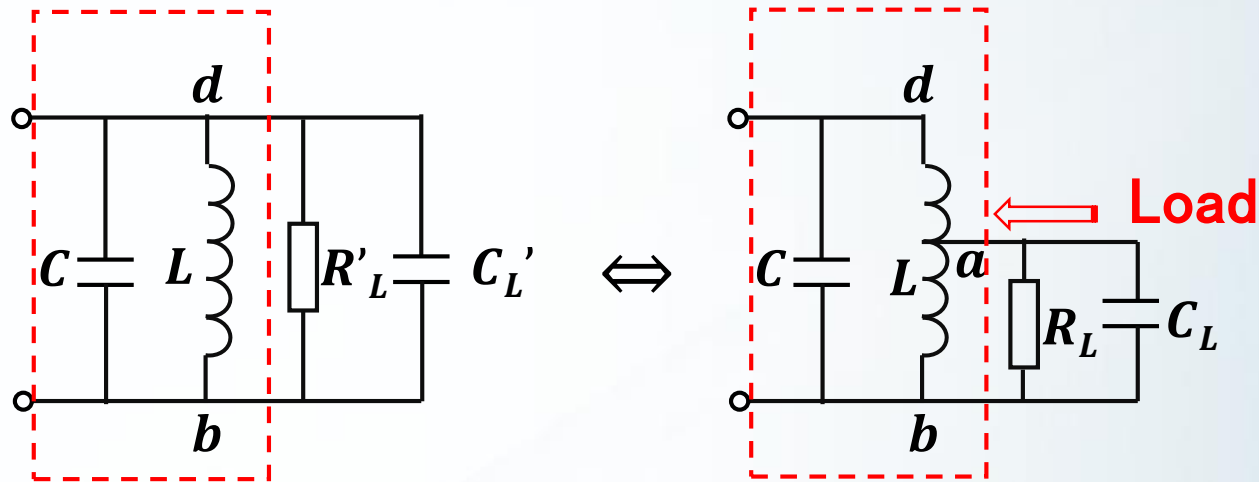



Low-tap  $\rightarrow$  High-tap :

$$R'_L = \frac{1}{p^2} R_L \Leftrightarrow R'_L \uparrow \frac{1}{p^2}$$

$$\frac{1}{\omega C'_L} = \frac{1}{p^2} \cdot \frac{1}{\omega C_L} \Leftrightarrow \frac{1}{\omega C'_L} \uparrow \frac{1}{p^2}$$

$$\Rightarrow C'_L = p^2 \cdot C_L \Leftrightarrow \text{Capacitance } C'_L \downarrow p^2$$

# Access Factor $p$

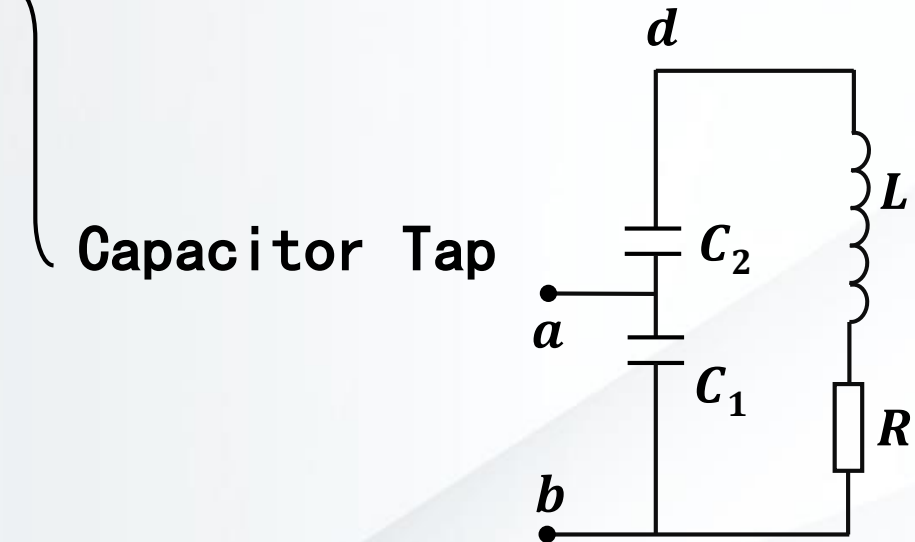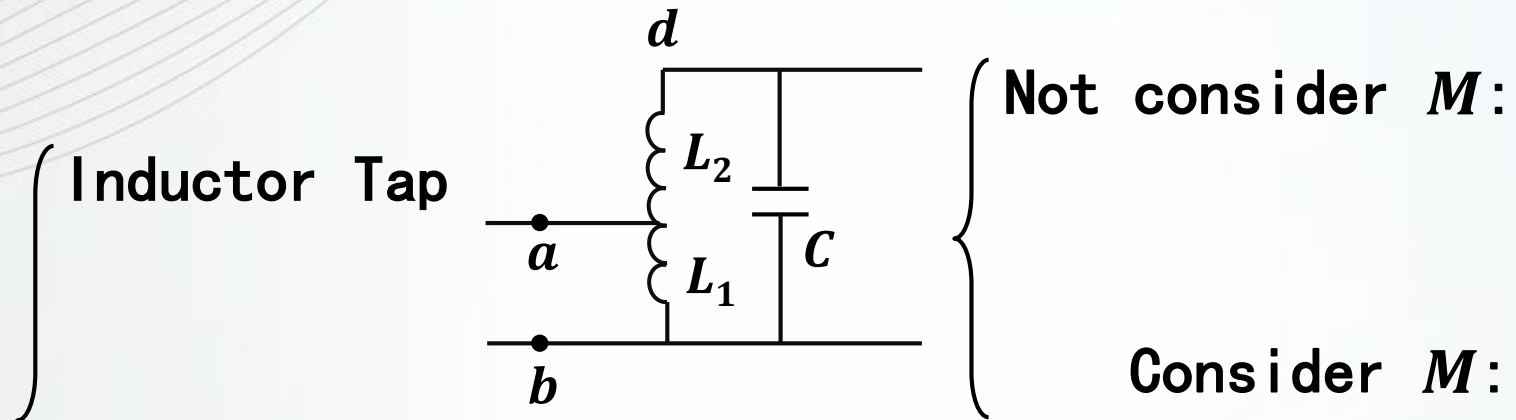

$$p = \frac{L_1}{L_1 + L_2} = \frac{N_1}{N_1 + N_2}$$

$$p = \frac{L_1 \pm M}{L_1 + L_2 \pm 2M}$$

$$C = \frac{C_1 C_2}{C_1 + C_2}$$

$$p = \frac{C}{C_1} = \frac{C_2}{C_1 + C_2}$$