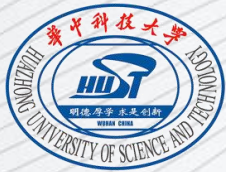


Huazhong University
of Science & Technology

Electronic Circuit of Communications


School of Electronic Information
and Communications

Jiaqing Huang




Series Resonance

Frequency Selective Circuits

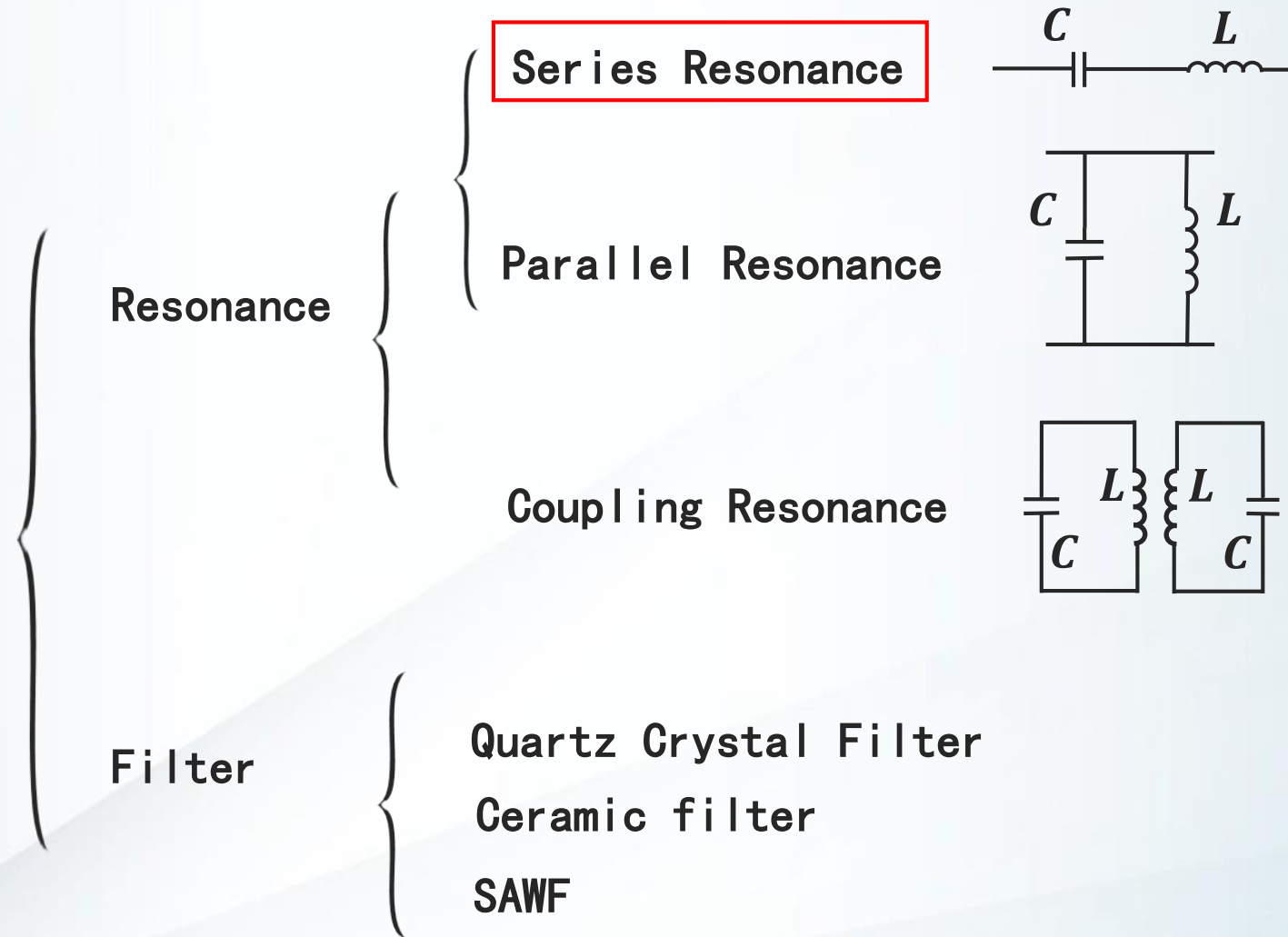

Series Resonant Circuit

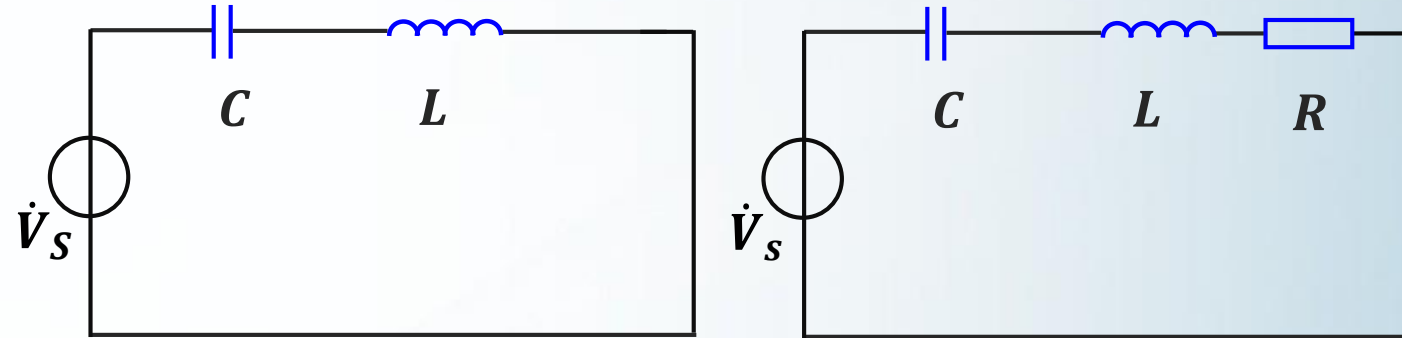


- Inductor = L with loss resistance R
 - Capacitor = C with loss resistance R
-
- The top diagram shows an inductor L in series with a resistor R . A red callout box labeled "non-ignorable" points to the resistor R .
- The bottom diagram shows a capacitor C in parallel with a resistor R . A red callout box labeled "ignorable" points to the resistor R .

Series Resonant Circuit—Impedance $Z \sim \omega$

Characteristic Impedance ρ :

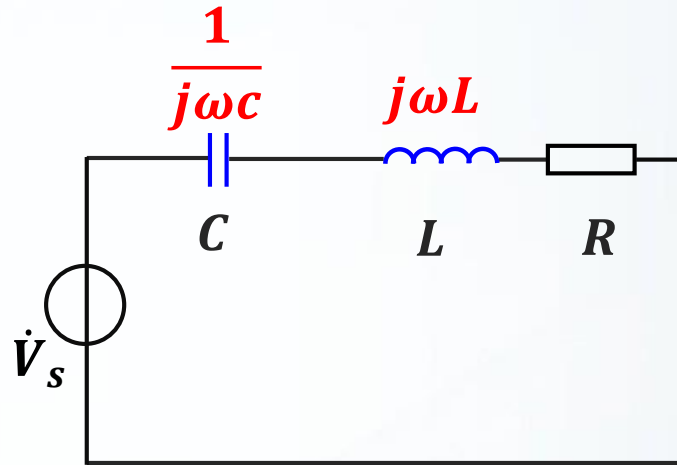
$$\rho = \omega_0 L = \frac{1}{\omega_0 C}$$
$$= \sqrt{\frac{L}{C}}$$



$$X = \omega L - \frac{1}{\omega C} \Rightarrow Z = R + jX = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

Resonant Frequency ω_0 :
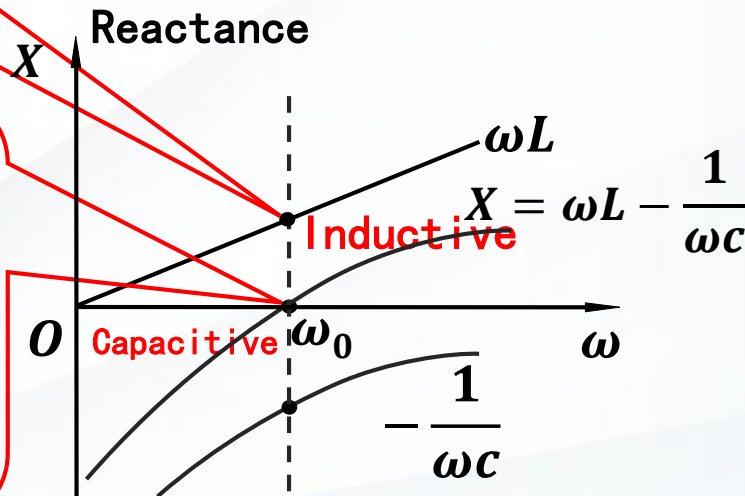
$$X = \omega_0 L - \frac{1}{\omega_0 C} = 0$$
$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$





- 1) $\omega > \omega_0$, $X > 0$ Inductive, ELI
- 2) $\omega < \omega_0$, $X < 0$ Capacitive, ICE
- 3) $\omega = \omega_0$, $X = 0$ purely resistive

Series Resonant Circuit—Impedance $Z \sim \omega$

Characteristic Impedance ρ :

$$\rho = \omega_0 L = \frac{1}{\omega_0 C}$$

$$= \sqrt{\frac{L}{C}}$$

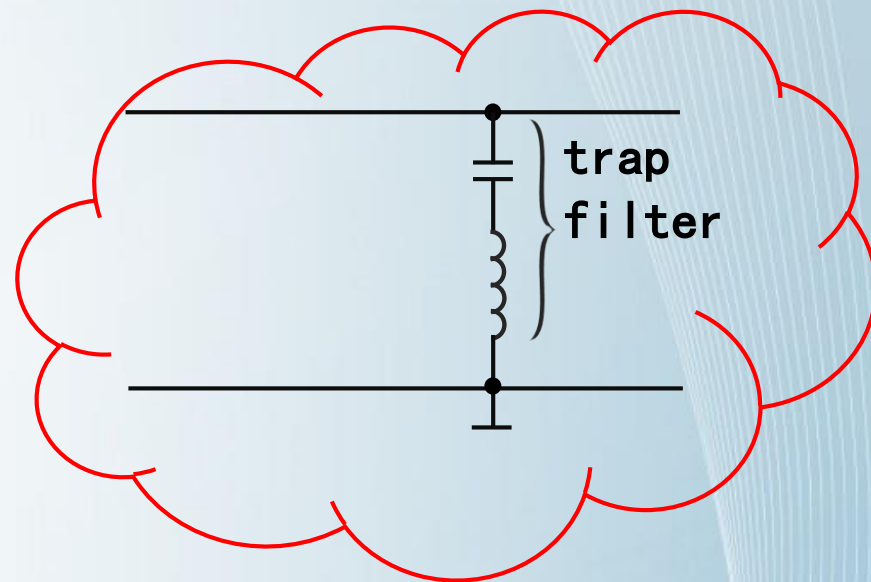
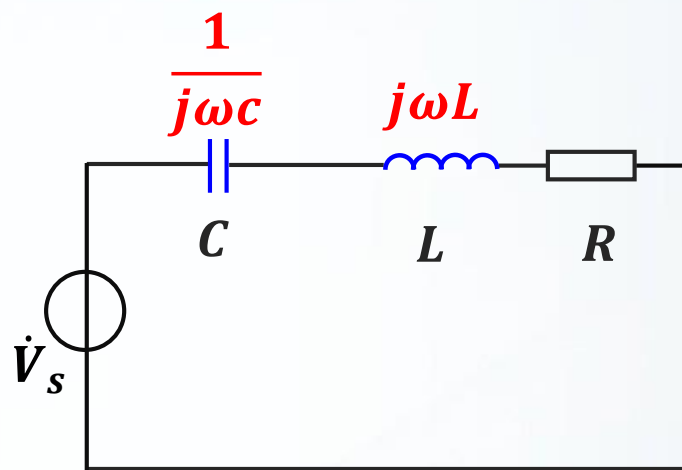


$$X = \omega L - \frac{1}{\omega C} \Rightarrow Z = R + jX = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

Resonant Frequency ω_0 :

$$X = \omega_0 L - \frac{1}{\omega_0 C} = 0$$
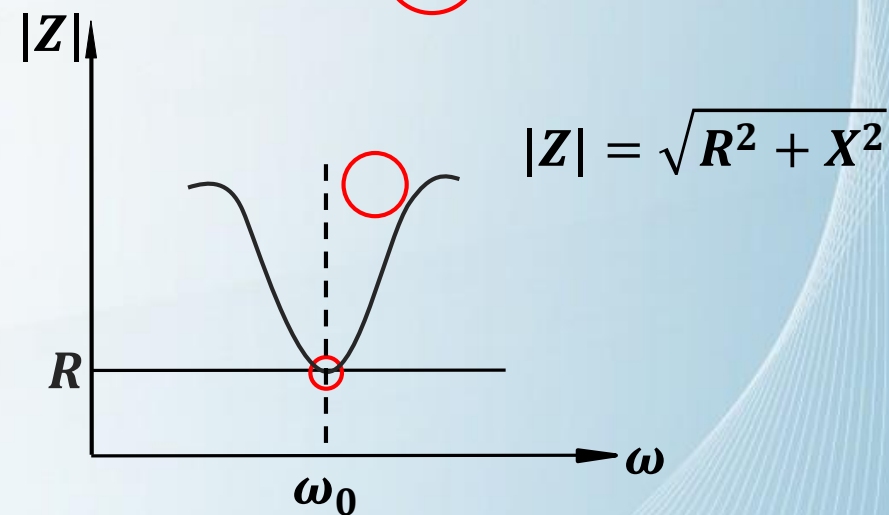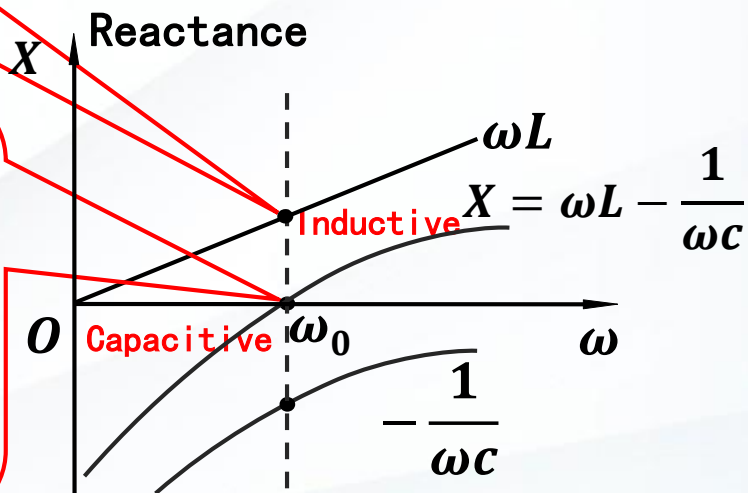
$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$



Series Resonant Circuit—Quality Factor (Q)

➤ Q of inductor


$$Q = \frac{\omega L}{R}$$



➤ Q of resonator

$$Q_0 = \frac{\omega_0 L}{R} = \frac{1}{\frac{R}{\omega_0 L}} = \frac{1}{\frac{R}{\rho}}$$

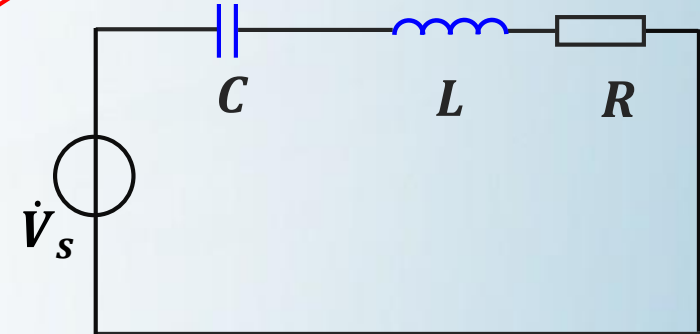
$$\because \rho = \omega_0 L = \frac{1}{\omega_0 C}$$



{ Difference: resonator Q_0 only for ω_0 , inductor Q for ω
Similarity: energy loss (from R)

Series Resonant Circuit— Voltage Resonance

➤ Series Resonance

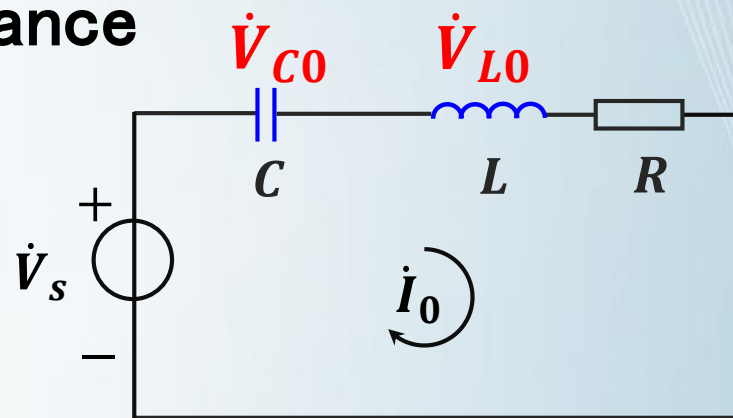

$$\begin{cases} \dot{V}_{L0} = \dot{I}_0 \cdot j\omega_0 L = \frac{\dot{V}_s}{R} j\omega_0 L = j \frac{\omega_0 L}{R} \dot{V}_s = jQ_0 \dot{V}_s \\ \dot{V}_{C0} = \dot{I}_0 \cdot \frac{1}{j\omega_0 C} = \frac{\dot{V}_s}{R} \frac{1}{j\omega_0 C} = -j \frac{\frac{1}{\omega_0 C}}{R} \dot{V}_s = -jQ_0 \dot{V}_s \end{cases}$$

$$Q_0 = \frac{\omega_0 L}{R} = \frac{\frac{1}{\omega_0 C}}{R}$$

Denote:

$\dot{V}_{L0} = -\dot{V}_{C0}$ same voltage value of, Q_0 times source voltage

★ Note: withstand voltage of L and C (esp. C)

Series Resonant Circuit— Detuning Coefficient

$$Q_0 = \frac{\omega_0 L}{R} = \frac{\frac{1}{\omega_0 C}}{R} = \frac{\rho}{R}$$

$$\left\{ \begin{array}{l} \text{Resonance, } Q_0 = \frac{(\text{Reactance})X}{(\text{Resistance})R} \end{array} \right.$$

$\xi = 0$ denote resonance

$$\left\{ \begin{array}{l} \text{Detuning, } \xi = \frac{(\text{Reactance sum})X}{(\text{Resistance})R} = \frac{\omega L - \frac{1}{\omega C}}{R} \end{array} \right.$$

$$\omega \approx \omega_0$$

$$= \frac{\omega_0 L}{R} \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = Q_0 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = Q_0 \frac{(\omega + \omega_0)(\omega - \omega_0)}{\omega_0 \omega}$$

$$\xi \approx Q_0 \frac{2(\omega - \omega_0)}{\omega_0}$$


$$\xi = Q_0 \cdot \frac{2\Delta\omega}{\omega_0} \quad \text{or} \quad \xi = Q_0 \cdot \frac{2\Delta f}{f_0}$$

$\xi \neq 0$ denote detuning value

Series Resonant Circuit— Resonance Curve

$$Z = R + jX = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

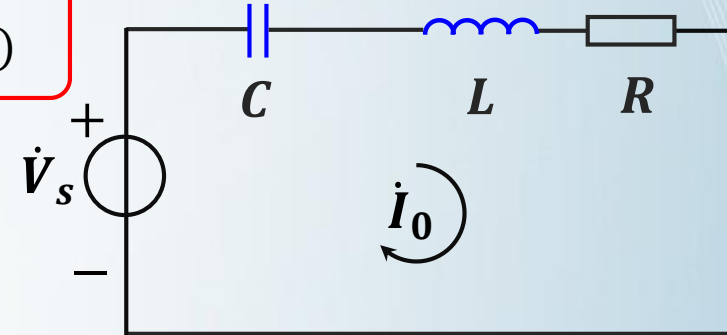➤ Current: $\dot{I} = \frac{\dot{V}_s}{R + j\left(\omega L - \frac{1}{\omega C}\right)} \sim \omega$




➤ Resonance Curve:

$$N(f) = \frac{\dot{I}}{\dot{I}_0} = \frac{\frac{\dot{V}_s}{R + j\left(\omega L - \frac{1}{\omega C}\right)}}{\frac{\dot{V}_s}{R}} = \frac{R}{R + j\left(\omega L - \frac{1}{\omega C}\right)} = \frac{1}{1 + j\left(\frac{\omega L - \frac{1}{\omega C}}{R}\right)}$$

$$\Rightarrow N(f) = \frac{\dot{I}}{\dot{I}_0} = \frac{1}{1 + j\xi}$$
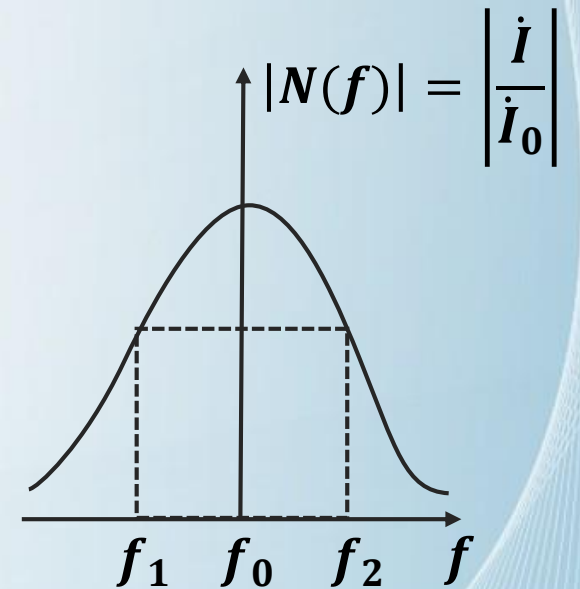
$$\xi = \frac{\omega L - \frac{1}{\omega C}}{R}$$



Amplitude-Frequency

Series Resonant Circuit— Bandwidth

➤ Bandwidth: scope among I drop to 0.707 of I_0

$$B = 2\Delta f_{0.7} = |f_2 - f_1|$$

Curve $N(f) = \frac{i}{i_0} = \frac{1}{1+j\xi}$

AF: $|N(f)| = \frac{1}{\sqrt{1+\xi^2}} = \frac{1}{\sqrt{2}}$

\Rightarrow if $2\Delta f_{0.7}$
 $\xi = \pm 1$



$\xi = Q_0 \cdot \frac{2\Delta f}{f_0}$

$\Rightarrow 1 = Q_0 \cdot \frac{2\Delta f_{0.7}}{f_0}$

$1 = Q_0 \cdot \frac{B}{f_0}$

$2\Delta f = 2\Delta f_{0.7}$

$Q_0 \cdot B = f_0$

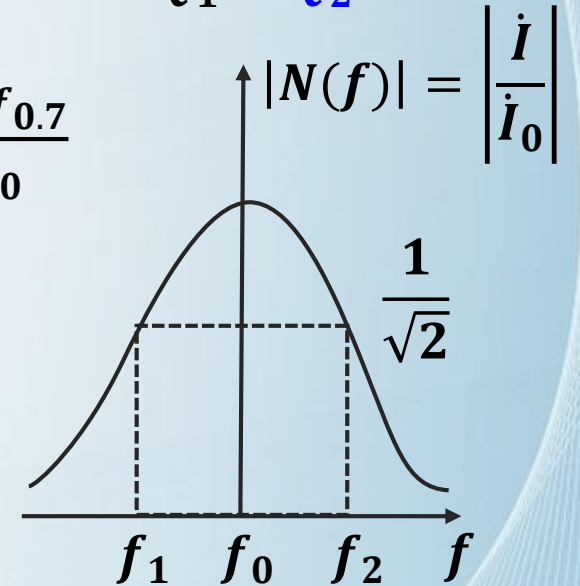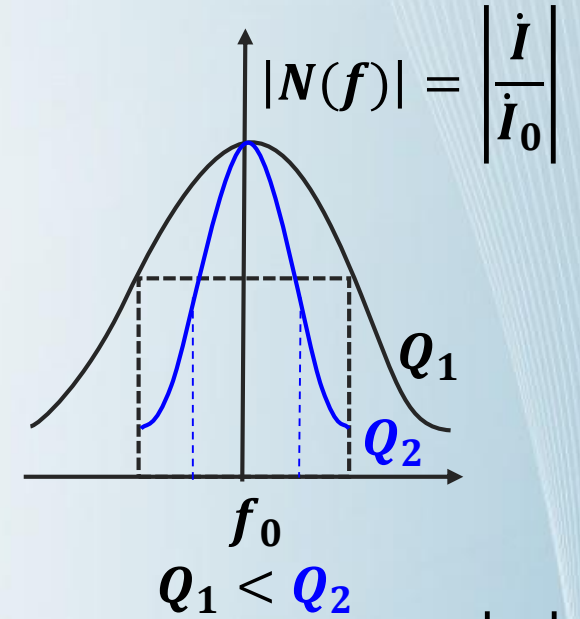


Amplitude-Frequency (AF)

Series Resonant Circuit— Phase-Frequency Curve

Resonance Curve $N(f) = \frac{i}{i_0} = \frac{1}{1+j\xi}$

➤ PF: $\psi = -\arctg\xi$

$Q \uparrow$ linearity \downarrow

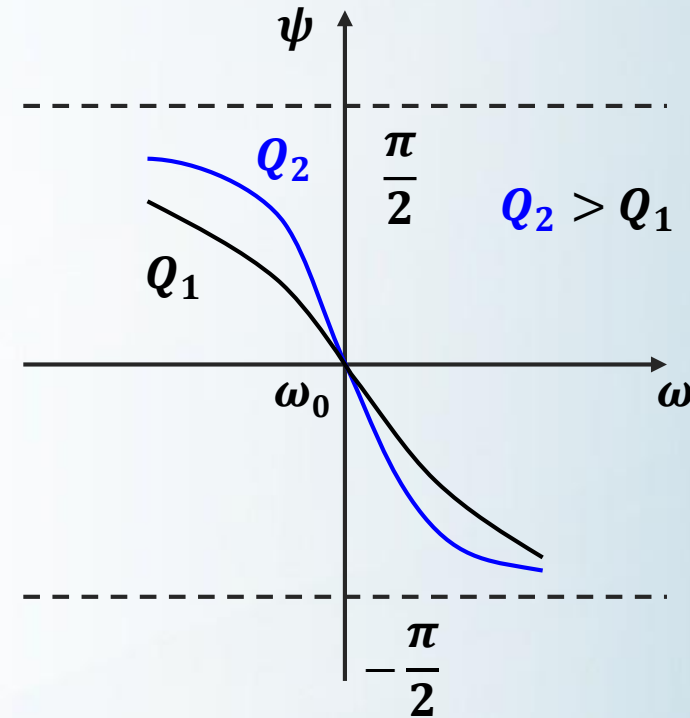

Phase-Frequency (PF)

Series Resonant Circuit— with load

➤ unloaded Q :



$$Q_0 = \frac{\omega_0 L}{R}$$

➤ loaded Q :

$$Q_L = \frac{\omega_0 L}{R + R_s + R_L}$$

Consider source resistance &
load resistance
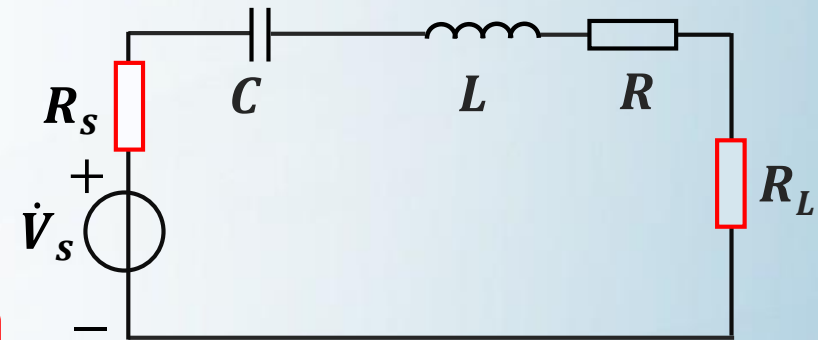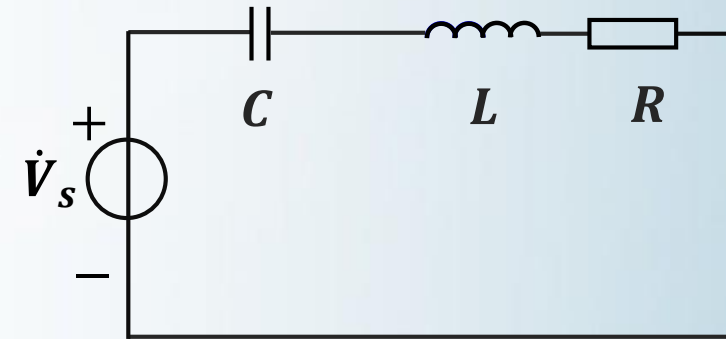
$$Q_L \downarrow \Rightarrow B \uparrow$$



Summary—Series Resonance

➤ Resonance Curve: $N(f) = \frac{i}{i_0} = \frac{1}{1+j\xi}$

Amplitude-Frequency: $|N(f)| = \left| \frac{i}{i_0} \right|$

cf. Inductor $Q = \frac{\omega L}{R}$

$\therefore \rho = \omega_0 L = \frac{1}{\omega_0 C}$

Resonance: $Q_0 = \frac{(\text{Reactance})X}{(\text{Resistance})R} = \frac{\omega_0 L}{R} = \frac{\frac{1}{\omega_0 C}}{R} = \frac{\rho}{R}$

Detuning: $\xi = \frac{(\text{Reactance Sum})X}{(\text{Resistance})R} = \frac{\omega L - \frac{1}{\omega C}}{R} \approx Q_0 \cdot \frac{2\Delta f}{f_0} \Rightarrow Q_0 \cdot B = f_0$

Phase-Frequency $\psi = -\arctan \xi$